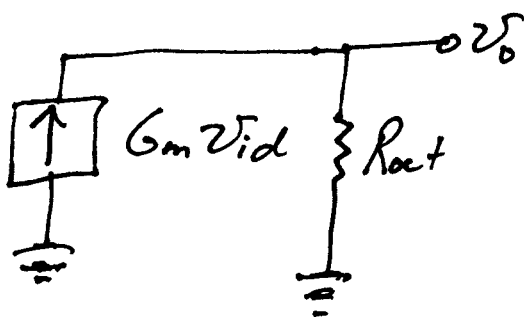



Output Stages

1/4

- So far, our designs have high output impedance
→ Generally termed "operational transconductance amplifiers" due to current source output.
(OTA)
- To drive resistive loads or large cap loads, need an output stage w/ low output impedance to buffer the load from our key gain stages ⇒ "operational amplifier"
- Equivalent models:



OTA: $R_{out} \rightarrow \text{large}$

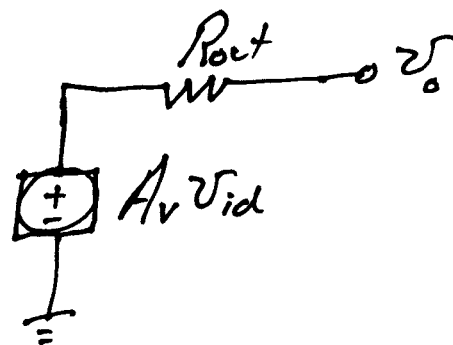


Op-Amp: $R_{out} \rightarrow \text{small}$

Next: Add buffer to OTA to realize low output impedance op-amp.


• Op-Amp Stages:

Z/4

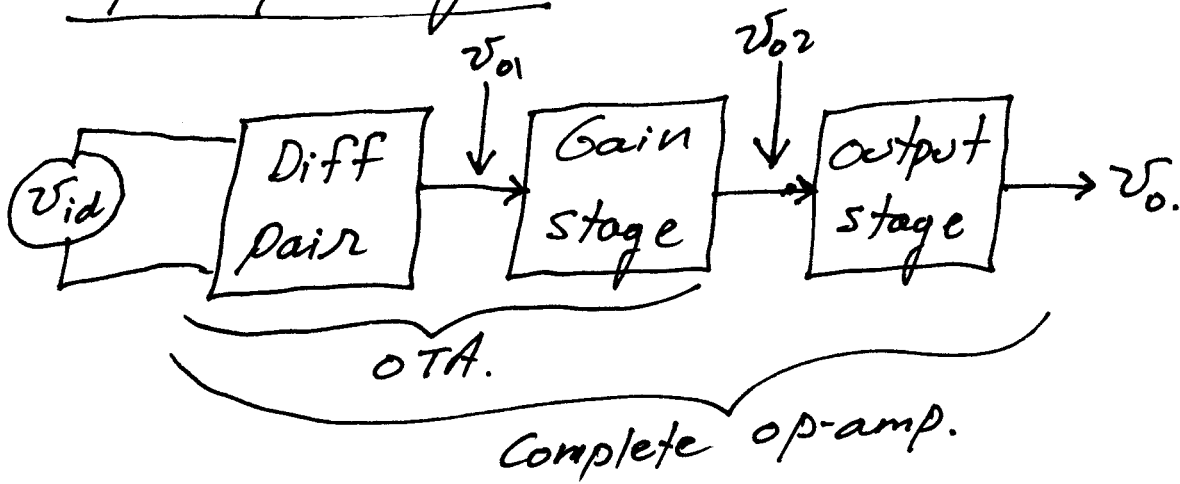

• Output Stages:

1) Common-Drain (source follower)

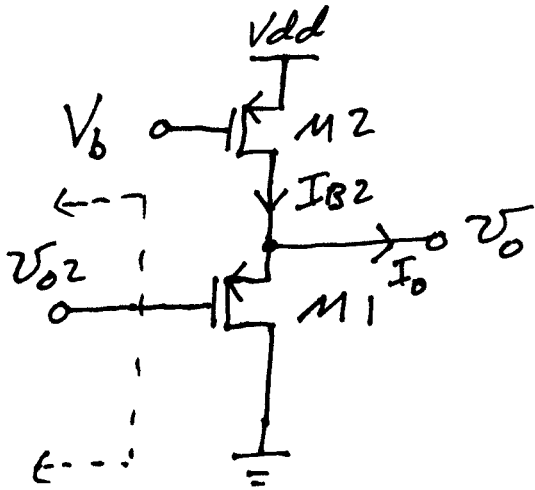

$$\left. \begin{array}{l} \frac{v_o}{v_{o2}} \approx 1, \quad R_{out} \approx 1/g_{m1} \end{array} \right\}$$

• Can source only $I_o^+ = I_{B2}$

• Can sink $I_o^- = I_{D1-max} - I_{B2}$

\Rightarrow can be large w/
large $(w/L)_1$


\Rightarrow Class A: - Constant power consumption

- I_o limited by bias I_{B2}


- Highly linear. (all devices active)

2) Two Source Followers:

3/4

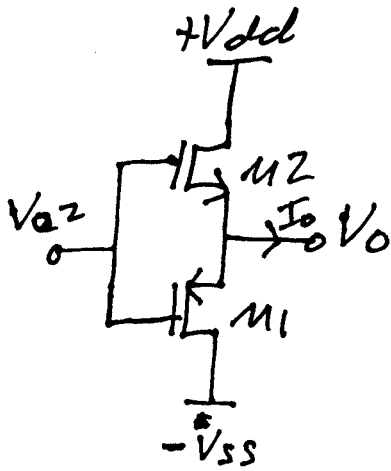

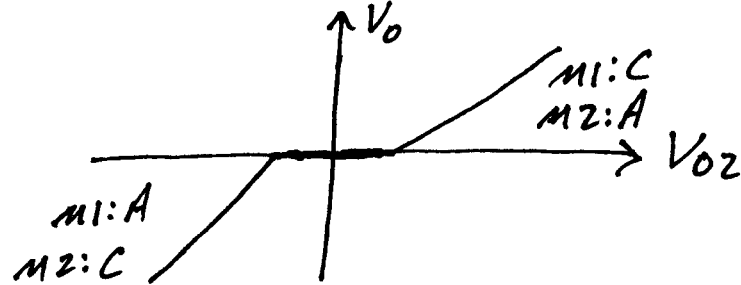- Has "cross-over" distortion for V_{o2} near V_o with M_1 & M_2 cut-off:



- @ $I_o = 0 \Rightarrow$ Zero power loss (or quiescent power)

- $(I_o)_{max}$: can be large in both directions by design (large $(W/L)_{1,2}$).

Small-signal

- $\frac{v_o}{v_{o2}} \approx 1$ } if M_1 or M_2 active; $R_{out} \approx \frac{1}{g_{m1}}$ or $\frac{1}{g_{m2}}$


\Rightarrow Class B: - no quiescent current

- I_o not limited by bias current

- Cross-over distortion (non-linear)

3) Two source followers w/ biasing:


4/4

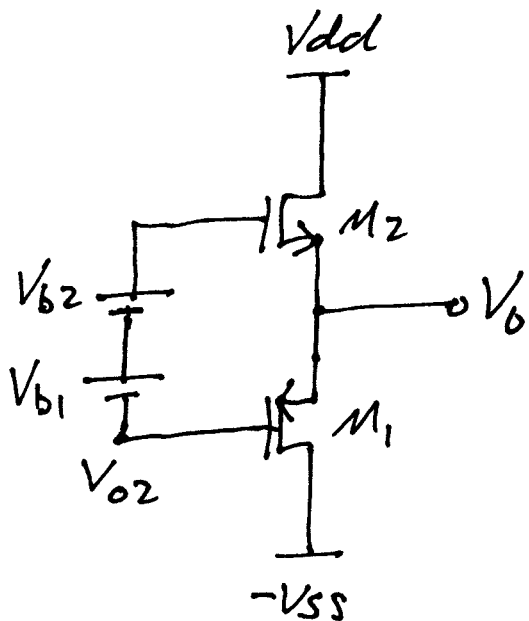

- use V_{b1} & V_{b2} to "pre-bias" M_1 & M_2 into active region
 \Rightarrow reduce or eliminate crossover distortion depending on how much I_Q is allowed.

\hookrightarrow quiescent current (@ $I_o = 0$)

possible realization

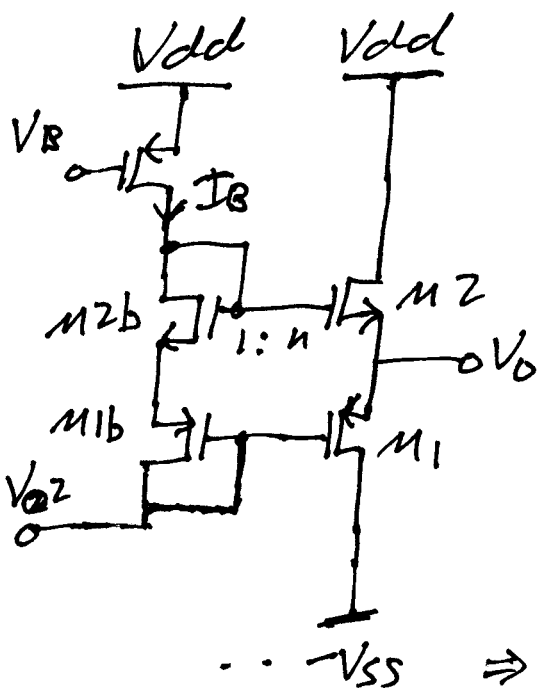

• $M1b$ & $M2b$ bias $M1/M2$ with $I_{Q_{1,2}} = n \cdot I_B$ so

both are active @ $I_o = 0$

• For large $I_o^+ \Rightarrow M2$ active
 $M1$ cutoff

For large $I_o^- \Rightarrow$ reverse.

$\dots -V_{ss} \Rightarrow$ Class AB: - compromise between

distortion & bias current

• $I_Q =$ small (not zero)

• limited distortion

• I_o not limited by bias current.