

LECTURE 320 – IMPROVED OPEN-LOOP COMPARATORS AND LATCHES

LECTURE ORGANIZATION

Outline

- Autozeroing
- Hysteresis
- Simple Latches
- Summary


CMOS Analog Circuit Design, 2nd Edition Reference

Pages 464-483

AUTOZEROING

Principle of Autozeroing

 
Use the comparator as an op amp to sample the dc input offset voltage and cancel the offset during operation.



Comments:


- The comparator must be stable in the unity-gain mode (self-compensating comparators are ideal, the two-stage comparator would require compensation to be switched in during the autozero cycle.)
- Complete offset cancellation is limited by charge injection

 Differential Implementation of Autozeroed Comparators




Single-Ended Autozeroed Comparators

Noninverting:

 

Inverting:

 


Comment on autozeroing:

Need to be careful about noise that gets sampled onto the autozeroing capacitor and is present on the comparison phase of the process.


HYSTERESIS

Influence of Input Noise on the Comparator

Comparator without hysteresis:

 

Comparator with hysteresis:

 


CMOS Analog Circuit Design

© P.E. Allen - 2010

Use of Hysteresis for Comparators in a Noisy Environment

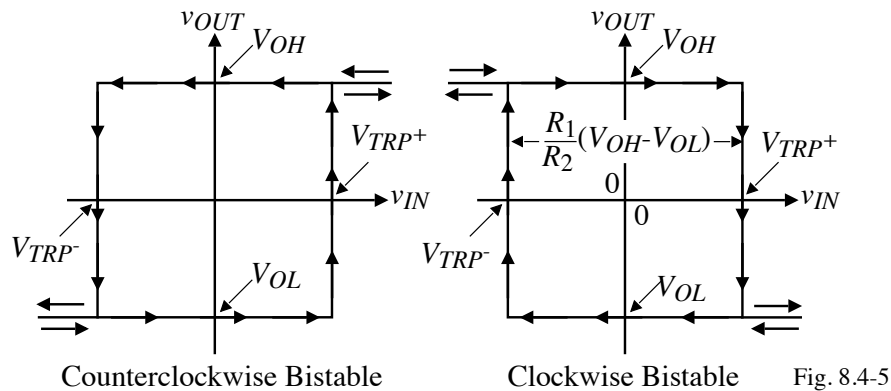Transfer curve of a comparator with hysteresis:



Hysteresis is achieved by the use of positive feedback

- Externally
- Internally

Noninverting Comparator using External Positive Feedback

Circuit:


 


Fig. 8.4-7

 

Upper Trip Point:

Assume that $v_{OUT} = V_{OL}$, the upper trip point occurs when,

$$0 = \left(\frac{R_1}{R_1+R_2}\right)V_{OL} + \left(\frac{R_2}{R_1+R_2}\right)V_{TRP^+} \quad \rightarrow \quad V_{TRP^+} = -\frac{R_1}{R_2}V_{OL}$$

Lower Trip Point:

Assume that $v_{OUT} = V_{OH}$, the lower trip point occurs when,

$$0 = \left(\frac{R_1}{R_1+R_2}\right)V_{OH} + \left(\frac{R_2}{R_1+R_2}\right)V_{TRP^-} \quad \rightarrow \quad V_{TRP^-} = -\frac{R_1}{R_2}V_{OH}$$

Width of the bistable characteristic:

$$\Delta v_{in} = V_{TRP^+} - V_{TRP^-} = \left(\frac{R_1}{R_2}\right)(V_{OH} - V_{OL})$$

Inverting Comparator using External Positive Feedback

Circuit:

 
 


Fig. 8.4-8

Upper Trip Point:

$$v_{IN} = V_{TRP^+} = \left(\frac{R_1}{R_1+R_2}\right)V_{OH}$$

Lower Trip Point:

$$v_{IN} = V_{TRP^-} = \left(\frac{R_1}{R_1+R_2}\right)V_{OL}$$

Width of the bistable characteristic:

$$\Delta v_{in} = V_{TRP^+} - V_{TRP^-} = \left(\frac{R_1}{R_1+R_2}\right)(V_{OH} - V_{OL})$$

Horizontal Shifting of the CCW Bistable Characteristic

Circuit:

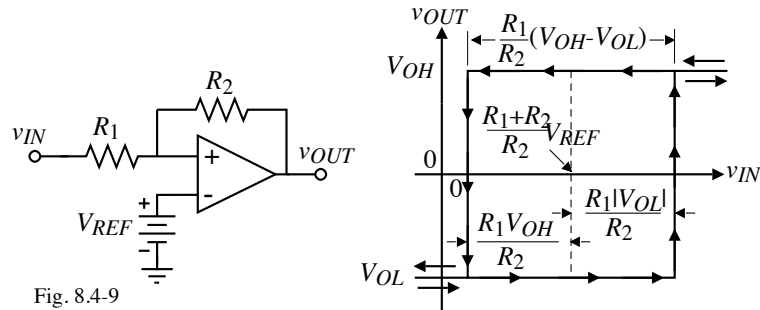


Fig. 8.4-9

Upper Trip Point:

$$V_{REF} = \left(\frac{R_1}{R_1+R_2} \right) V_{OL} + \left(\frac{R_2}{R_1+R_2} \right) V_{TRP^+} \quad \rightarrow \quad V_{TRP^+} = \left(\frac{R_1+R_2}{R_2} \right) V_{REF} - \frac{R_1}{R_2} V_{OL}$$

Lower Trip Point:

$$V_{REF} = \left(\frac{R_1}{R_1+R_2} \right) V_{OH} + \left(\frac{R_2}{R_1+R_2} \right) V_{TRP^-} \quad \rightarrow \quad V_{TRP^-} = \left(\frac{R_1+R_2}{R_2} \right) V_{REF} - \frac{R_1}{R_2} V_{OH}$$

Shifting Factor:

$$\pm \left(\frac{R_2}{R_1+R_2} \right) V_{REF}$$

Horizontal Shifting of the CW Bistable Characteristic

Circuit:

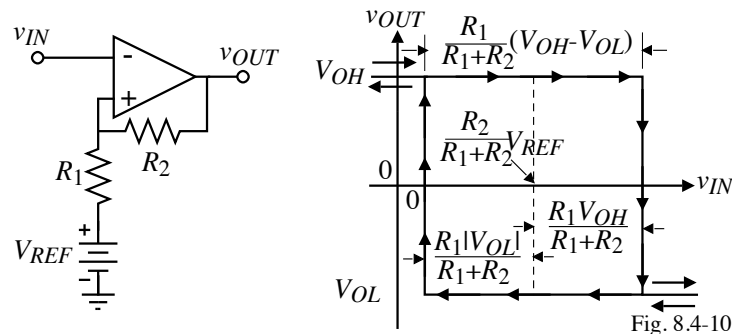


Fig. 8.4-10

Upper Trip Point:

$$v_{IN} = V_{TRP^+} = \left(\frac{R_1}{R_1+R_2} \right) V_{OH} + \left(\frac{R_2}{R_1+R_2} \right) V_{REF}$$

Lower Trip Point:

$$v_{IN} = V_{TRP^-} = \left(\frac{R_1}{R_1+R_2} \right) V_{OL} + \left(\frac{R_2}{R_1+R_2} \right) V_{REF}$$

Shifting Factor:

$$\pm \left(\frac{R_2}{R_1+R_2} \right) V_{REF}$$

Internal Positive Feedback - Upper Trip Point

Assume that the gate of M1 is on ground and the input to M2 is much smaller than zero. The resulting circuit is:

M1 on, M2 off → M3 on, M6 on (active), M4 and M7 off.

∴ v_{o2} is high.

M6 wants to source the current $i_6 = \frac{W_6/L_6}{W_3/L_3} i_1$

As v_{in} begins to increase towards the trip point, the current flow through M2 increases. When $i_2 = i_6$, the upper trip point will occur.

$$\therefore i_5 = i_1 + i_2 = i_3 + i_6 = i_3 + \left(\frac{W_6/L_6}{W_3/L_3}\right) i_3 = i_3 \left[1 + \frac{W_6/L_6}{W_3/L_3}\right] \rightarrow i_1 = i_3 = \frac{i_5}{1 + [(W_6/L_6)/(W_3/L_3)]}$$

Also, $i_2 = i_5 - i_1 = i_5 - i_3$

Knowing i_1 and i_2 allows the calculation of v_{GS1} and v_{GS2} which gives

$$V_{TRP^+} = v_{GS2} - v_{GS1} = \sqrt{\frac{2i_2}{\beta_2}} + V_{T2} - \sqrt{\frac{2i_1}{\beta_1}} - V_{T1}$$

 


Fig. 8.4-12A

Internal Positive Feedback - Lower Trip Point

Assume that the gate of M1 is on ground and the input to M2 is much greater than zero. The resulting circuit is:

M2 on, M1 off → M4 and M7 on, M3 and M6 off.

∴ v_{o1} is high.

M7 wants to source the current $i_7 = \frac{W_7/L_7}{W_4/L_4} i_2$

As v_{in} begins to decrease towards the trip point, the current flow through M1 increases. When $i_1 = i_7$, the lower trip point will occur.

$$\therefore i_5 = i_1 + i_2 = i_7 + i_4 = \left(\frac{W_7/L_7}{W_4/L_4}\right) i_4 + i_4 = i_4 \left[1 + \frac{W_7/L_7}{W_4/L_4}\right] \rightarrow i_2 = i_4 = \frac{i_5}{1 + [(W_7/L_7)/(W_4/L_4)]}$$

Also, $i_1 = i_5 - i_2 = i_5 - i_4$

Knowing i_1 and i_2 allows the calculation of v_{GS1} and v_{GS2} which gives

$$V_{TRP^-} = v_{GS2} - v_{GS1} = \sqrt{\frac{2i_2}{\beta_2}} + V_{T2} - \sqrt{\frac{2i_1}{\beta_1}} - V_{T1}$$

 


Fig. 8.4-12B

Complete Comparator with Internal Hysteresis

 


Fig. 8.4-14

Schmitt Trigger

The Schmitt trigger is a circuit that has better defined switching points.

Consider the following circuit:

 


Fig. 8.4-15

How does this circuit work?

Assume the input voltage, v_{in} , is low and the output voltage, v_{out} , is high.

M3, M4 and M5 are on and M1, M2 and M6 are off.

When v_{in} is increased from zero, M2 starts to turn on causing M3 to start turning off. Positive feedback causes M2 to turn on further and eventually both M1 and M2 are on and the output is at zero.

The upper switching point, V_{TRP}^+ is found as follows:

When v_{in} is low, the voltage at the source of M2 (M3) is

$$v_{S2} = V_{DD} - V_{TN3}$$

$V_{TRP}^+ = v_{in}$ when M2 turns on given as $V_{TRP}^+ = V_{TN2} + v_{S2}$

V_{TRP}^+ occurs when the input voltage causes the currents in M3 and M1 to be equal.

Schmitt Trigger – Continued

Thus, $i_{D1} = \beta_1 (V_{TRP^+} - V_{TN1})^2 = \beta_3 (V_{DD} - v_{S2} - V_{TN3})^2 = i_{D3}$
 which can be written as, assuming that $V_{TN2} = V_{TN3}$,

$$\beta_1 (V_{TRP^+} - V_{TN1})^2 = \beta_3 (V_{DD} - V_{TRP^+})^2 \Rightarrow V_{TRP^+} = \frac{V_{TN1} + \sqrt{\beta_3/\beta_1} V_{DD}}{1 + \sqrt{\beta_3/\beta_1}}$$

The switching point, V_{TRP^-} is found in a similar manner and is:

$$\beta_5 (V_{DD} - V_{TRP^-} - V_{TP5})^2 = \beta_6 (V_{TRP^-})^2 \Rightarrow V_{TRP^-} = \frac{\sqrt{\beta_5/\beta_6} (V_{DD} - V_{TP5})}{1 + \sqrt{\beta_5/\beta_6}}$$

The bistable characteristic is,

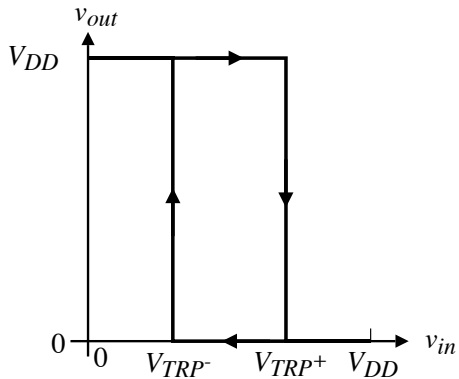


Fig. 8.4-16

SIMPLE LATCHES

Regenerative Comparators

Regenerative comparators use positive feedback to accomplish the comparison of two signals. Latches can have a faster switching speed than the previous comparators.

NMOS and PMOS latch:

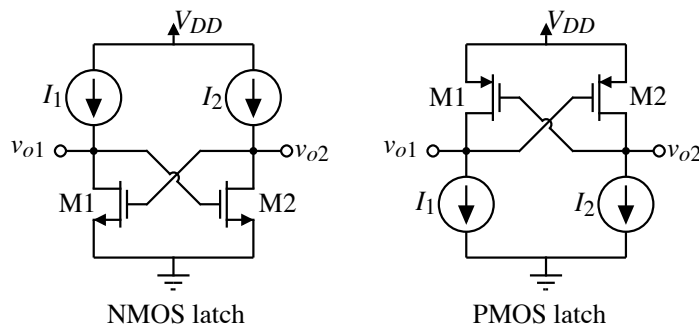


Fig. 8.5-3


Operating Modes of the Latch

The latch has two modes of operation – enable or latch and $\overline{\text{Enable}}$ (enable_bar) or $\overline{\text{Latch}}$ (latch_bar).

1.) During the Enable_bar, the latch is turned off (currents are removed) and the unknown inputs are applied to it. The parasitic capacitance at the latch nodes hold the unknown voltage.

2.) During Enable, the latch is turned on, and the positive feedback acts on the applied inputs and causes one side of the latch to go high and the other side to go low.

Enable_bar:

 

The inputs are initially applied to the outputs of the latch.

V_{o1}' = initial input applied to v_{o1}

Step Response of a Latch (Enable)

Circuit:

R_i and C_i are the resistance and capacitance seen to ground from the i -th transistor.

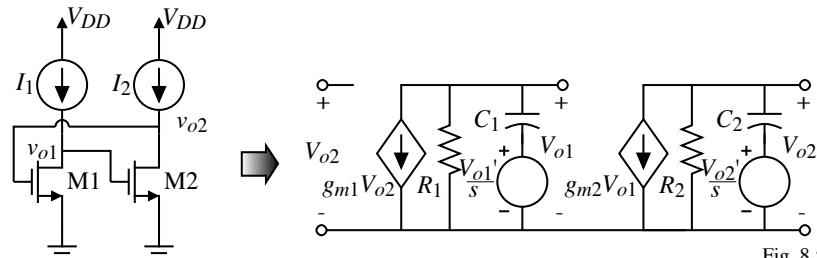


Fig. 8.5-4

Nodal equations:

$$g_{m1}V_{o2} + G_1V_{o1} + sC_1\left(V_{o1} - \frac{V_{o1}'}{s}\right) = g_{m1}V_{o2} + G_1V_{o1} + sC_1V_{o1} - C_1V_{o1}' = 0$$

$$g_{m2}V_{o1} + G_2V_{o2} + sC_2\left(V_{o2} - \frac{V_{o2}'}{s}\right) = g_{m2}V_{o1} + G_2V_{o2} + sC_2V_{o2} - C_2V_{o2}' = 0$$

Solving for V_{o1} and V_{o2} gives,

$$V_{o1} = \frac{R_1C_1}{sR_1C_1+1} V_{o1}' - \frac{g_{m1}R_1}{sR_1C_1+1} V_{o2} = \frac{\tau_1}{s\tau_1+1} V_{o1}' - \frac{g_{m1}R_1}{s\tau_1+1} V_{o2}$$

$$V_{o2} = \frac{R_2C_2}{sR_2C_2+1} V_{o2}' - \frac{g_{m2}R_2}{sR_2C_2+1} V_{o1} = \frac{\tau_2}{s\tau_2+1} V_{o2}' - \frac{g_{m2}R_2}{s\tau_2+1} V_{o1}$$

Defining the output, ΔV_o , and input, ΔV_i , as

$$\Delta V_o = V_{o2} - V_{o1} \quad \text{and} \quad \Delta V_i = V_{o2}' - V_{o1}'$$

Step Response of the Latch - Continued

Solving for ΔV_o gives,

$$\Delta V_o = V_{o2} - V_{o1} = \frac{\tau}{s\tau+1} \Delta V_i + \frac{g_m R}{s\tau+1} \Delta V_o$$

or

$$\Delta V_o = \frac{\tau \Delta V_i}{s\tau + (1 - g_m R)} = \frac{\tau \Delta V_i}{\frac{1 - g_m R}{s\tau} + 1} = \frac{\tau' \Delta V_i}{s\tau' + 1}$$

where

$$\tau' = \frac{\tau}{1 - g_m R}$$

Taking the inverse Laplace transform gives

$$\Delta v_o(t) = \Delta V_i e^{-t/\tau'} = \Delta V_i e^{-t(1 - g_m R)/\tau} \approx e^{g_m R t/\tau} \Delta V_i, \quad \text{if } g_m R \gg 1.$$

Define the latch time constant as

$$\tau_L = |\tau'| \approx \frac{\tau}{g_m R} = \frac{C}{g_m} = \frac{0.67 W L C_{ox}}{\sqrt{2 K' (W/L) I}} = 0.67 C_{ox} \sqrt{\frac{W L^3}{2 K' I}}$$

if $C \approx C_{gs}$.

$$\therefore \Delta V_{out}(t) = e^{t/\tau_L} \Delta V_i$$

Step Response of a Latch - Continued

Normalize the output voltage by $(V_{OH} - V_{OL})$ to get

$$\frac{\Delta V_{out}(t)}{V_{OH} - V_{OL}} = e^{t/\tau_L} \frac{\Delta V_i}{V_{OH} - V_{OL}}$$

which is plotted as,

 


Fig. 8.5-5

The propagation delay time is

$$t_p = \tau_L \ln \left(\frac{V_{OH} - V_{OL}}{2 \Delta V_i} \right)$$

Note that the larger the ΔV_i , the faster the response.

Example 320-3 - Time Domain Characteristics of a Latch.

Find the propagation time delay for the NMOS if the W/L of the latch transistors is $5\mu\text{m}/0.5\mu\text{m}$ and the latch dc current is $10\mu\text{A}$ when $\Delta V_i = 0.1(V_{OH}-V_{OL})$ and $\Delta V_i = 0.01(V_{OH}-V_{OL})$.

Solution

The transconductance of the latch transistors is

$$g_m = \sqrt{2 \cdot 120 \cdot 10 \cdot 10} = 155 \mu\text{S}$$

The output conductance is $0.6\mu\text{S}$ which gives $g_m R$ of 93V/V . Since $g_m R$ is greater than 1, we can use the above results. Therefore the latch time constant is found as

$$\tau_L = 0.67 C_{ox} \sqrt{\frac{WL^3}{2K'I}} = 0.67 (60.6 \times 10^{-4}) \sqrt{\frac{(5 \cdot 0.5) \times 10^{-24}}{2 \cdot 120 \times 10^{-6} \cdot 10 \times 10^{-6}}} = 0.131 \text{ns}$$

Since the propagation time delay is the time when the output is $0.5(V_{OH}-V_{OL})$, then using the above results or Fig. 8.5-5 we find for $\Delta V_i = 0.01(V_{OH}-V_{OL})$ that $t_p = 3.91\tau_L = 0.512\text{ns}$ and for $\Delta V_i = 0.1(V_{OH}-V_{OL})$ that $t_p = 1.61\tau_L = 0.211\text{ns}$.

Comparator using a Latch with a Built-In Reference[†]

How does it operate?

- 1.) Devices in shaded region operate in the triode region.
- 2.) When the latch/reset goes high, the upper cross-coupled inverter-latch regenerates. The drain currents of M5 and M6 are steered to obtain a final state determined by the mismatch between the R_1 and R_2 resistances.

$$\frac{1}{R_1} = K_N \left[\frac{W_1}{L} (v_{in}^+ - V_T) + \frac{W_2}{L} (V_{REF}^- - V_T) \right]$$

and

$$\frac{1}{R_2} = K_N \left[\frac{W_1}{L} (v_{in}^- - V_T) + \frac{W_2}{L} (V_{REF}^+ - V_T) \right]$$

- 3.) The input voltage which causes $R_1 = R_2$ is $v_{in}(\text{threshold}) = (W_2/W_1)V_{REF}$

$W_2/W_1 = 1/4$ generates a threshold of $\pm 0.25V_{REF}$.

Performance \rightarrow 20Ms/s & $200\mu\text{W}$

 


Fig. 8.5-6

[†] T.B. Cho and P.R. Gray, "A 10b, 20Msamples/s, 35mW pipeline A/D Converter," *IEEE J. Solid-State Circuits*, vol. 30, no. 3, pp. 166-172, March 1995.

Simple, Low Power Latched Comparator[†]

 


Fig. 8.5-7

Dissipated $50\mu\text{W}$ when clocked at 2MHz.


Self-referenced

[†] A. Coban, "1.5V, 1mW, 98-dB Delta-Sigma ADC", Ph.D. dissertation, School of ECE, Georgia Tech, Atlanta, GA 30332-0250.
CMOS Analog Circuit Design

Tail-Referenced Latch


The previous two latches experience poor input offset voltage characteristics because the input devices are working in the linear region during the latch phase. The latch below keeps the input devices in the saturation region. The resulting larger gain of the input devices reduces the input offset voltage as shown.

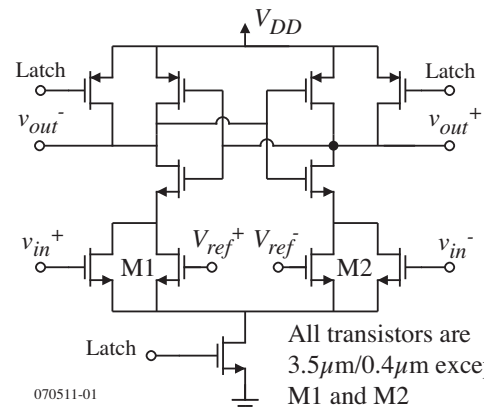The input offset voltage of the tail referenced latch is compared between two latches with the referenced latch for 100 samples. The x -axis is the deviation from the mean of the first latch and the y -axis is the deviation of the mean of the second latch.




070511-01

 All transistors are $3.5\mu\text{m}/0.4\mu\text{m}$ except M1 and M2



(A) Tail-Latch Referenced Comparator

 

(B) Referenced Comparator

CMOS Latch

Circuit:

 


Fig. 8.5-8

Input offset voltage distribution:


 


Fig. 8.5-9

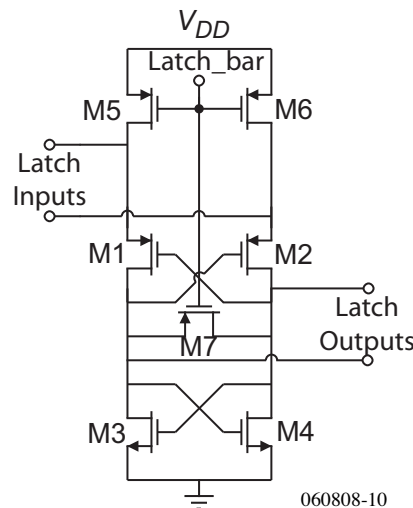CMOS Latch with Different Inputs and Outputs



060808-10

When Latch_bar is high, M5, M6 and M7 are off and the latch is disabled and the outputs are shorted together.


When Latch_bar is low, the input voltages stored at the sources of M1 and M2 will cause one of the latch outputs to be high and the other to be low.

The source of M1 and M2 that is higher will have a larger source-gate voltage resulting in a larger transconductance and more gain than the other transistor.

Metastability

Metastability is the condition where the latch cannot make a decision in the time allocated. Normally due to the fact that the input is small (within the input resolution range).

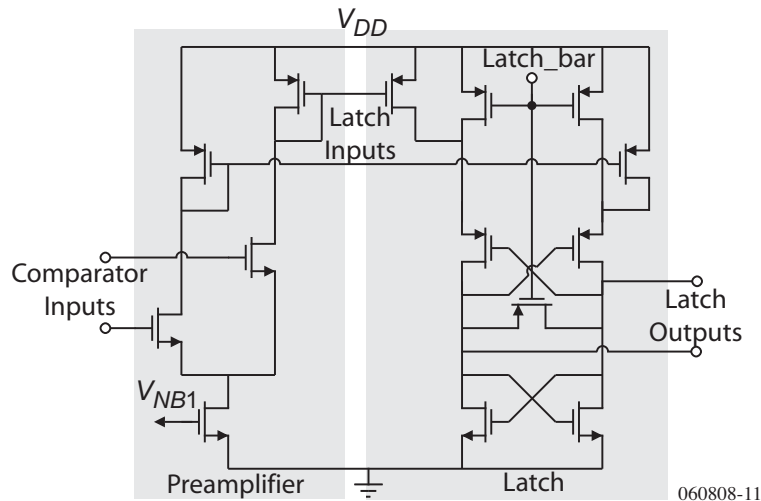Metastability can be improved (reduced) by increasing the gain of the comparator by preceding it with an amplifier to keep the signal input to the latch as large as possible under all conditions. The preamplifier also reduced the input offset voltage.



SUMMARY

- Discrete-time comparators must work with clocks
- Switched capacitor comparators use op amps to transfer charge and autozero
- Regenerative comparators (latches) use positive feedback
- The propagation delay of the regenerative comparator is slow at the beginning and speeds up rapidly as time increases
- The highest speed comparators will use a combination of open-loop comparators and latches