

MODIFICATIONS TO DIFFERENTIAL AMPLIFIERS

(READING: Text-Sec. 4.3.5)

INTRODUCTION

The objective of this presentation is:

- 1.) Show how to improve the performance of differential amplifiers
- 2.) Demonstrate the design of a MOSFET differential amplifier

Outline

- Folded load MOS differential amplifiers
- Modifications of active load amplifiers
 - Hyperbolic sine
 - Linear transconductor
 - Cross-coupled differential amplifier
- Design of a differential amplifier
- Summary

FOLDED MOS DIFFERENTIAL AMPLIFIER WITH A CURRENT MIRROR LOAD

Folding Concept

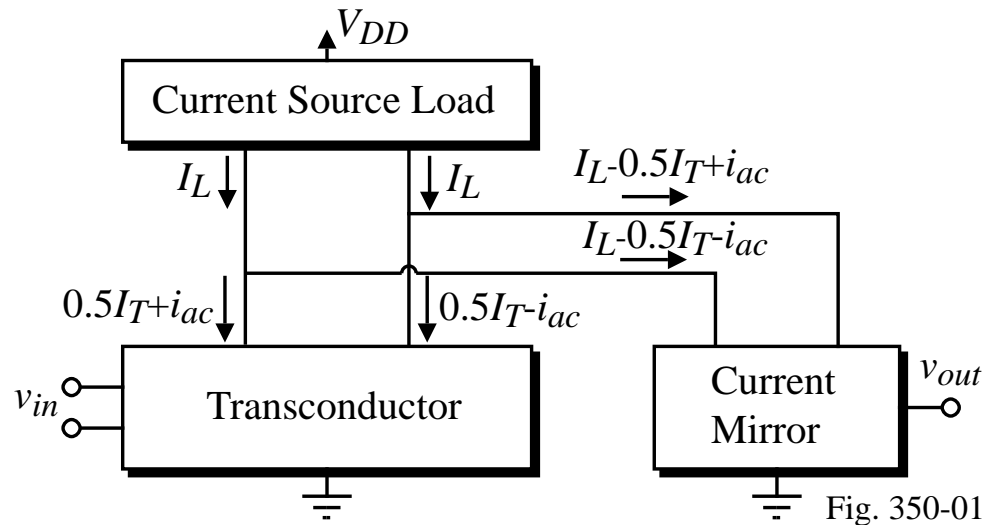


Fig. 350-01

Advantages:


- Increases the upper common-mode voltage range
- Allows balanced loads
- Smaller power supplies

Disadvantage:

- Introduces more poles (generally not dominant)
- I_L must be greater than $I_T + i_{ac}$ to prevent the current mirror from being “starved” →

Also implies more power dissipation

Small Signal Analysis

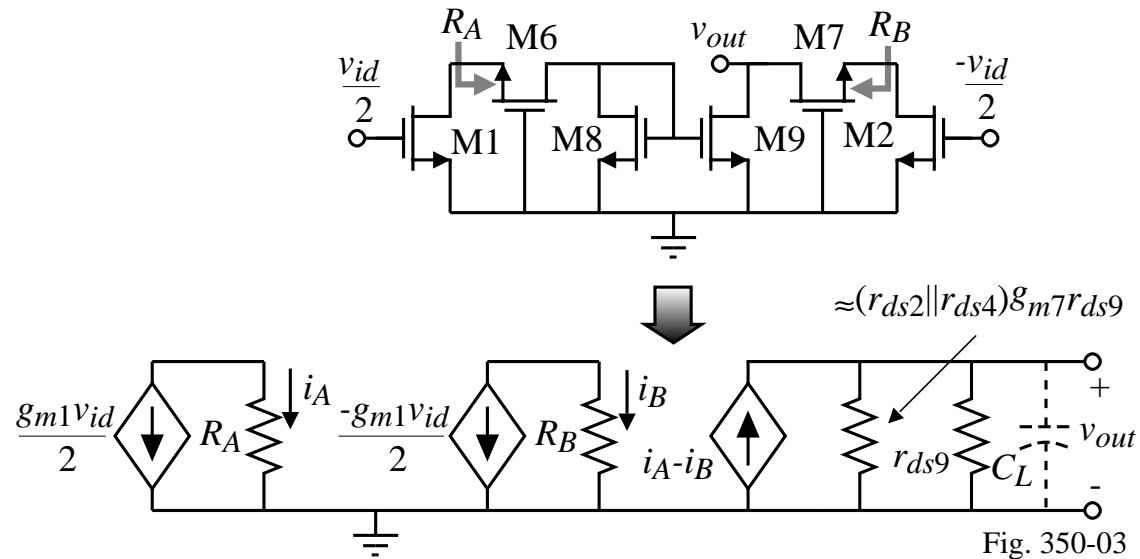

Recall: $R_A \approx 1/g_{m6}$ & $R_B \approx 1/g_{m7}$ & $r_{out7} \approx \{r_{ds7}(1 + g_{m7}[r_{ds2} // r_{ds4}]) + r_{ds2} // r_{ds4}\} // r_{ds9}$

And $v_{out} = -(i_2 + i_9)(r_{ds9} // r_{out7}) \approx -(i_2 + i_9)(r_{ds9})$

Where $i_2 \approx (-0.5v_{id}g_{m2}/g_{m7})g_{m7} = -0.5v_{id}g_{m2}$

& $i_9 \approx (0.5v_{id}[-g_{m1}]/g_{m6})(g_{m6}/g_{m8})g_{m9} = -0.5v_{id}g_{m1}$ if $g_{m8} = g_{m9}$ (design choice!)

$$\therefore v_{out} = \left(\frac{g_{m1} + g_{m2}}{2} \right) r_{ds9} v_{id} \approx g_{m1} r_{ds9} v_{id} \Rightarrow \frac{v_{out}}{v_{id}} = g_{m1} r_{ds9}$$


-3dB frequency: $\omega_{-3dB} = \frac{1}{r_{ds9} C_L}$

MODIFICATIONS OF ACTIVE LOAD AMPLIFIERS

Linear CMOS Transconductor

In many applications, it is necessary to linearize the transconductance of a differential amplifier. The following circuit[†] shows one method of doing this.

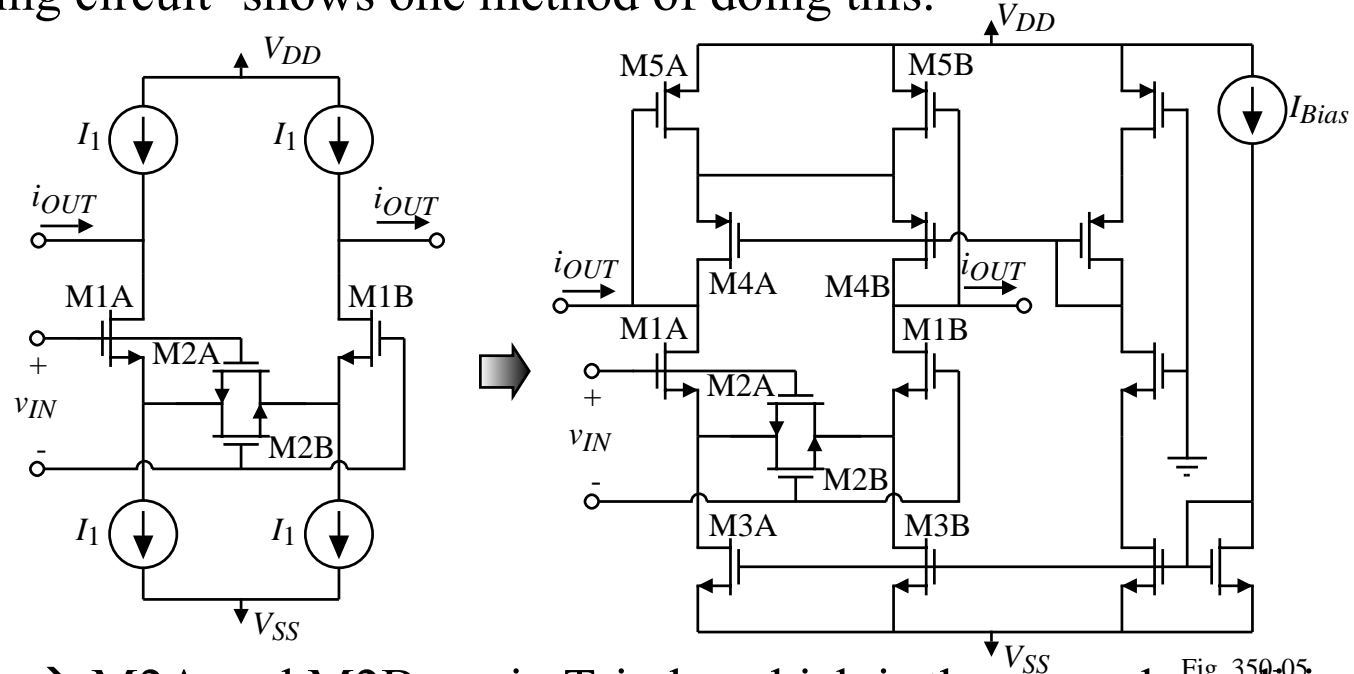Goal: Desensitize g_m of square-law depend. & sensitize to a more linear element!



$$V_{GS_1A} = V_{GS_2A}$$

$$V_{GS_1B} = V_{GS_2B}$$

$$V_{CM} - V_{GS_1A} = V_{S_A}$$

if balanced, $V_{S_A} = V_{S_B} \rightarrow$ M2A and M2B are in Triode, which is the normal condition.

The small signal drain-source resistance of M2A and M2B is

$$r_{2A} = r_{2B} \approx \frac{1}{\beta_2(V_{GS1} - V_{TN})} \rightarrow i_D = \beta[(v_{GS} - V_T)v_{DS} - v_{DS}^2] \approx \beta(v_{GS} - V_T)v_{DS}$$

[†] F. Krummenacher and N. Joehl, "A 4-MHz CMOS Continuous-Time Filter with On-Chip Automatic Tuning," *IEEE J. of Solid-State Circuits*, vol. 23, no. 3, pp. 750-758, June 1988.

Linear CMOS Transconductor - Continued

The small signal transconductance of M1A and M1B are

$$g_{m1} = g_{m1A} = g_{m1B} = \beta_1(V_{GS1} - V_{TN})$$

Using the half-circuit approach for differential operation, the small signal output current is derived as, where $r_{2a} // r_{2b} = 0.5r_{2a}$,

$$i_{out} = g_{m1}v_{gs1} = g_{m1}(0.5v_{id} - 0.5r_{2a}i_{out}) \rightarrow i_{out} = \frac{0.5g_{m1}v_{id}}{1 + 0.5g_{m1}r_{2a}}$$

$\rightarrow g_{m(\text{eff})} = \frac{0.5g_{m1}}{1 + 0.5g_{m1}r_{2a}} \rightarrow$ Intuitively, $g_{m(\text{eff})}$ is now more dependent on a more

linear element (r_{2a}) and less sensitive to the less linear component (g_{m1}).

- Substituting the value of g_{m1} and r_{2a} gives

$$g_{m(\text{eff})} = \frac{0.5\beta_1(V_{GS1} - V_{TN})}{1 + \frac{0.5\beta_1(V_{GS1} - V_{TN})}{\beta_2(V_{GS2} - V_{TN})}} = \frac{\beta_1\beta_2(V_{GS1} - V_{TN})}{\beta_1 + 2\beta_2} = \frac{\beta_1\beta_2}{\beta_1 + 2\beta_2} \sqrt{\frac{2I_1}{\beta_1}}$$

Select the ratio of β_1/β_2 to linearize the transconductance.

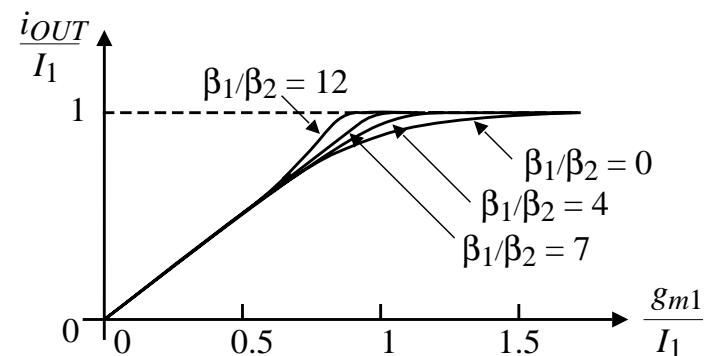


Fig. 350-06

Cross-Coupled Differential Amplifier

This input stage is good for class B operation (push/pull).

Push/pull Operation:

* If v_{id} , which is $v_1 - v_2$, increases,
M1 & M4 conduct more current and M2/M3 less.

* If v_{id} decreases, M2 & M3 conduct more current and
M1/M4 less.

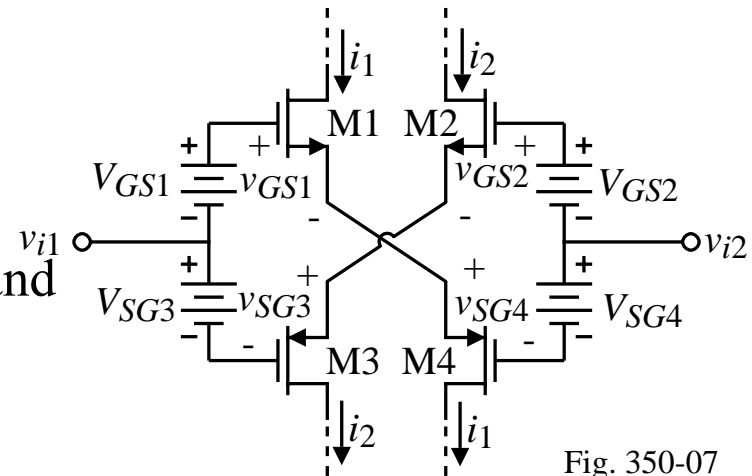


Fig. 350-07

AC Operation:

Using the notation for ac, dc, and total variables yields

$$v_{i1} - v_{i2} = -V_{GS1} + v_{GS1} + v_{SG4} - V_{SG4} = V_{SG3} - v_{SG3} - v_{GS2} + V_{GS2}$$

& canceling DC components: $v_{i1} - v_{i2} = v_{id} = (v_{gs1} + v_{sg4}) = -(v_{sg3} + v_{gs2})$

{e.g., $-V_{GS1} + v_{GS1} = v_{gs1}$ }

if $v_{i1} = v_{id}$ & $v_{i2} = 0$,


$$i_1 = v_{gs} g_{m1} = (v_{id} - i_1/g_{m4}) g_{m1} \quad \text{or} \quad i_1 = 0.5 g_{m1} v_{id} \quad (\text{if } M1=M4)$$

Cross-Coupled Differential Amplifier - Continued

If $M1=M2=M3=M4$, half of the differential input is applied across each side.

$$\therefore i_1 = \frac{g_{m1}v_{id}}{2} = \frac{g_{m4}v_{id}}{2} \quad \text{and} \quad i_2 = -\frac{g_{m2}v_{id}}{2} = -\frac{g_{m3}v_{id}}{2}$$

Implementation:

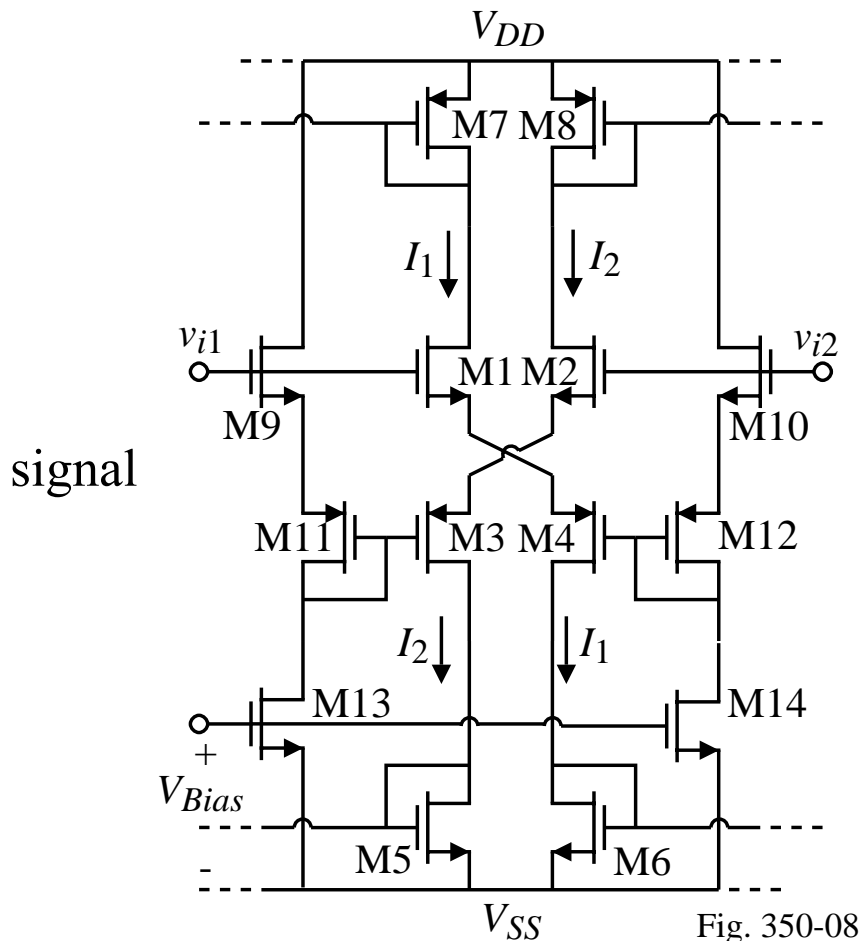

Gain is reduced by a half because the input is dropped across two gate-sources.

DESIGN OF A DIFFERENTIAL AMPLIFIER

CMOS Differential Amplifier with a Current Mirror Load

Design Considerations:

<u>Constraints</u>	<u>Specifications</u>
Power supply	Small-signal gain
Technology	(accuracy – $1+A\beta$)
Temperature	Frequency response (C_L)
Power Dissipation	ICMR
Area	Slew rate (C_L)
...	Power dissipation
	OCMR
	Offsets
	...

Architecture:

Input characteristics (R_{in} , ICMR)

Output charact. (R_{out} , OCMR)

Type of input

Type of load

Type of mirrors

Output driver

Type of feedback

Number of stages

...

Design of a CMOS Differential Amplifier with a Current Mirror Load - Continued

Sample procedure for a simple 5-transistor CMOS differential amplifier:

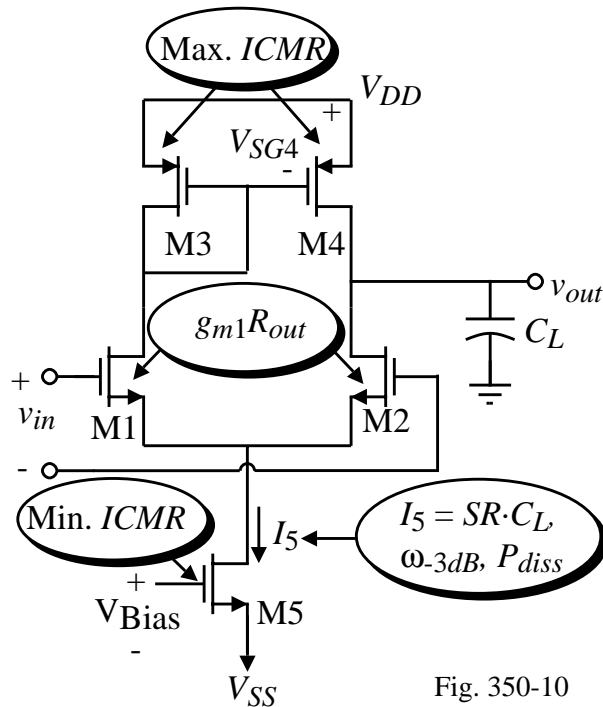


Fig. 350-10

- 1.) Pick I_{SS} to satisfy the slew rate, knowing C_L or the power dissipation.
- 2.) Check to see if R_{out} will satisfy the frequency response. If not, change I_{SS} or modify circuit.
- 3.) Design W_3/L_3 (W_4/L_4) to satisfy the upper I_{CMR} .
- 4.) Design W_1/L_1 (W_2/L_2) to satisfy the gain.
- 5.) Design W_5/L_5 to satisfy the lower I_{CMR} .
- 6.) Check functionality of the circuit
- 7.) Check all specifications
- 8.) Iterate where necessary.

Example 1 - Design of a MOS Differential Amplifier with a Current Mirror Load

Design the currents and W/L values of the MOS differential amplifier using a current mirror load to satisfy the following specifications: $V_{DD} = -V_{SS} = 2.5V$, $SR \geq 10V/\mu s$ with a 5pF load, $f_{-3dB} \geq 100kHz$ with a 5pF load, a small signal gain of 100V/V, $1.5V \leq ICMR \leq 2V$, and power loss must be less than 1mW. Assume $K_N' = 110\mu A/V^2$, $K_P' = 50\mu A/V^2$, $V_{TN} = 0.7V$, $V_{TP} = -0.7V$, $\lambda_N = 0.04V^{-1}$, and $\lambda_P = 0.05V^{-1}$.

Solution

1.) To meet the slew rate, $I_{SS} \geq 50\mu A$. For maximum P_{diss} , $I_{SS} \leq 200\mu A$.

2.) f_{-3dB} of 100kHz $\Rightarrow R_{out} \leq 318k\Omega$. This gives $R_{out} = \frac{2}{(\lambda_N + \lambda_P)I_{SS}} \leq 318k\Omega$

$\therefore I_{SS} \geq 70\mu A$ Thus, pick $I_{SS} = 100\mu A$

3.) $V_{IC(max)} = V_{DD} - V_{SG3} + V_{TN1} \rightarrow 2V = 2.5 - V_{SG3} + 0.7$

$$\therefore V_{SG3} \leq 1.2V = \sqrt{\frac{2 \cdot 50\mu A}{50\mu A/V^2 (W_3/L_3)}} + 0.7 \rightarrow \frac{W_3}{L_3} = \frac{W_4}{L_4} = \frac{2}{(0.5)^2} \geq 8$$

Maybe choose 10 for simplicity!

Example 1 - Continued

$$4.) \quad 100\text{V/V} = g_{m1}R_{out} = \frac{g_{m1}}{g_{ds2}+g_{ds4}} = \frac{\sqrt{2 \cdot 110\mu\text{A/V}^2(W_1/L_1)}}{(0.04+0.05)\sqrt{50\mu\text{A}}} = 23.31 \sqrt{\frac{W_1}{L_1}}$$

$$\therefore \frac{W_1}{L_1} = \frac{W_2}{L_2} = 18.4$$

$$5.) \quad V_{IC}(\text{min}) = V_{SS} + V_{DS5}(\text{sat}) + V_{GS1}$$

$$-1.5 = -2.5 + V_{DS5}(\text{sat}) + \sqrt{\frac{2 \cdot 50\mu\text{A}}{110\mu\text{A/V}^2(18.4)}} + 0.7$$

$$V_{DS5}(\text{sat}) \leq 0.3 - 0.222 = 0.078!! \text{ (Subthreshold!)}$$

$$\Rightarrow \frac{W_5}{L_5} = \sqrt{\frac{2I_{SS}}{K_N' V_{DS5}(\text{sat})^2}} = 300$$

6.) Increase W_1/L_1 to reduce V_{GS1} and allow a smaller W_5/L_5 . If $W_1/L_1 = 40$, then $W_5/L_5 = 9$ or 10 . (Larger than specified gain should be okay.)

SUMMARY

- Active load amplifier consists of a transconductor and a load
 - There are a large number of combinations of loads and transconductors possible. We have not considered the many cascoded possibilities and other configurations.
- The BJT amplifier generally has more gain and wider signal swing than the MOS amplifier
- The voltage gain of the MOS transconductor with a current source or current mirror load is inversely proportional to the square root of the bias current.
- The current mirror load differential amplifier is a widely used input stage
- The frequency response is generally determined by the dominant pole which is found at points in the circuit that are high impedance to ac ground and large capacitance
- The active load amplifier is the primary gain stage in operational amplifiers and other applications and will be a fundamental building block in more complex circuits
- Performances not considered include slew rate and noise