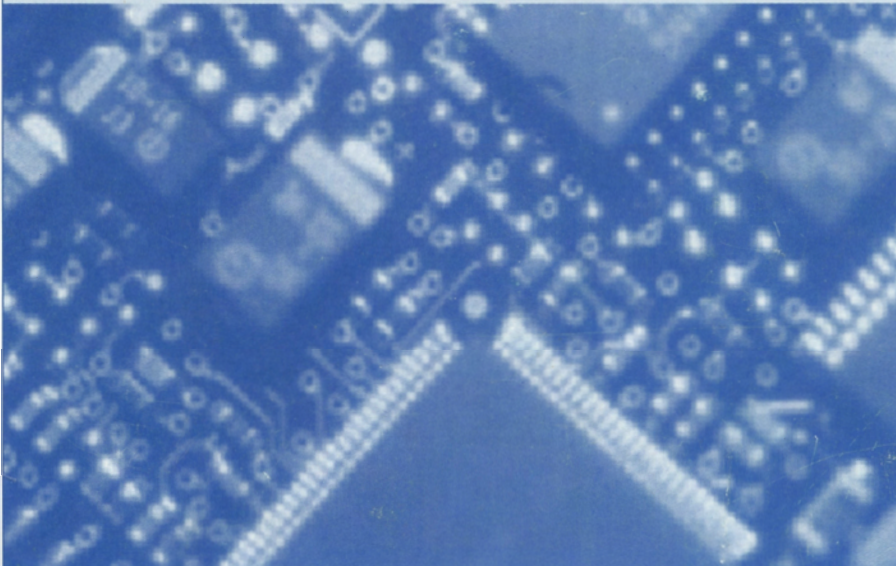


# Solutions Manual

to accompany

Electronic Circuit Analysis  
and Design Second Edition



Donald A. Neamen

Solutions Manual  
to accompany  
Electronic Circuit  
Analysis and Design

Second Edition

Donald A. Neamen  
*University of New Mexico*



Boston Burr Ridge, IL Dubuque, IA Madison, WI New York San Francisco St. Louis  
Bangkok Bogotá Caracas Kuala Lumpur Lisbon London Madrid Mexico City  
Milan Montreal New Delhi Santiago Seoul Singapore Sydney Taipei Toronto

**McGraw-Hill Higher Education**   
A Division of The McGraw-Hill Companies

Solutions Manual to accompany  
ELECTRONIC CIRCUIT ANALYSIS AND DESIGN  
Donald A. Neamen

Published by McGraw-Hill, an imprint of the McGraw-Hill Companies, Inc., 1221 Avenue of the Americas,  
New York, NY 10020. Copyright © 2001, 1996 by the McGraw-Hill Companies, Inc.  
All rights reserved.

The contents, or parts thereof, may be reproduced in print form solely for classroom use with  
ELECTRONIC CIRCUIT ANALYSIS AND DESIGN  
provided such reproductions bear copyright notice, but may not be reproduced in any other form or for any  
other purpose without the prior written consent of the McGraw-Hill Companies, Inc., including, but not limited  
to, in any network or other electronic storage or transmission, or broadcast for distance learning.

1 2 3 4 5 6 7 8 9 0 QSR/QSR 0 9 8 7 6 5 4 3 2 1

ISBN 0-07-232092-3

[www.mhhe.com](http://www.mhhe.com)

## Contents

### Part I Semiconductor Devices and Basic Applications

Chapter 1: Semiconductor Materials and Diodes .....	1
Chapter 2: Diode circuits .....	15
Chapter 3: The Bipolar Junction Transistor .....	29
Chapter 4: Basic BJT Amplifiers .....	49
Chapter 5: The Field Effect Transistor .....	87
Chapter 6: Basic FET Amplifiers .....	103
Chapter 7: Frequency Response.....	125
Chapter 8: Output Stages and Power Amplifiers.....	153

### Part II Analog Electronics

Chapter 9: The Ideal Operational Amplifier.....	165
Chapter 10: Integrated Circuit Biasing and Active Loads .....	183
Chapter 11: Differential and Multistage Amplifiers .....	203
Chapter 12: Feedback and Stability .....	237
Chapter 13: Operational Amplifier Circuits.....	275
Chapter 14: Nonideal Effects in Operational Amplifier Circuits.....	293
Chapter 15: Applications and Design of Integrated Circuits .....	313

### Part III Digital Electronics

Chapter 16: MOSFET Digital Circuits .....	343
Chapter 17: Bipolar Digital Circuits .....	365

## Chapter 1

## Exercise Solutions

E1.1

$$n_i = BT^{3/2} \exp\left(-\frac{E_g}{2kT}\right)$$

GaAs:

$$n_i = (2.1 \times 10^{14})(300)^{3/2} \exp\left(\frac{-1.4}{2(86 \times 10^{-6})(300)}\right)$$

$$\underline{n_i = 1.8 \times 10^8 \text{ cm}^{-3}}$$

Ge:

$$n_i = (1.66 \times 10^{15})(300)^{3/2} \exp\left(\frac{-0.66}{2(86 \times 10^{-6})(300)}\right)$$

$$\underline{n_i = 2.40 \times 10^{13} \text{ cm}^{-3}}$$

E1.2

Si:

$$n_i = (5.23 \times 10^{13})(400)^{3/2} \exp\left(\frac{-1.1}{2(86 \times 10^{-6})(400)}\right)$$

$$\underline{n_i = 4.76 \times 10^{12} \text{ cm}^{-3}}$$

GaAs:

$$n_i = (2.1 \times 10^{14})(400)^{3/2} \exp\left(\frac{-1.4}{2(86 \times 10^{-6})(400)}\right)$$

$$\underline{n_i = 2.44 \times 10^9 \text{ cm}^{-3}}$$

Ge:

$$n_i = (1.66 \times 10^{15})(400)^{3/2} \exp\left(\frac{-0.66}{2(86 \times 10^{-6})(400)}\right)$$

$$\underline{n_i = 9.06 \times 10^{14} \text{ cm}^{-3}}$$

E1.3

- a. majority carrier:  $p_0 = 10^{17} \text{ cm}^{-3}$   
minority carrier:

$$\underline{n_0 = \frac{n_i^2}{N_a} = \frac{(1.5 \times 10^{10})^2}{10^{17}} = 2.25 \times 10^3 \text{ cm}^{-3}}$$

- b.  $n_0 = N_d - N_a = 5 \times 10^{15}$

majority carrier:  $n_0 = 5 \times 10^{15} \text{ cm}^{-3}$ 

minority carrier:

$$\underline{p_0 = \frac{n_i^2}{n_0} = \frac{(1.5 \times 10^{10})^2}{5 \times 10^{15}} = 4.5 \times 10^4 \text{ cm}^{-3}}$$

E1.4

- (a)  $n_0 = 5 \times 10^{16} \text{ cm}^{-3}$ ,  $p_0 \ll n_0$

$$\sigma \cong e\mu_n n_0 = (1.6 \times 10^{-19})(1350)(5 \times 10^{16}) \Rightarrow$$

$$\underline{\sigma = 10.8 (\Omega \cdot \text{cm})^{-1}}$$

- (b)  $p_0 = 5 \times 10^{16} \text{ cm}^{-3}$ ,  $n_0 \ll p_0$

$$\sigma \cong e\mu_p p_0 = (1.6 \times 10^{-19})(480)(5 \times 10^{16}) \Rightarrow$$

$$\underline{\sigma = 3.84 (\Omega \cdot \text{cm})^{-1}}$$

E1.5

- a.  $n_0 = N_d = 8 \times 10^{15} \text{ cm}^{-3}$

$$p_0 = \frac{n_i^2}{n_0} = \frac{(1.5 \times 10^{10})^2}{8 \times 10^{15}} \Rightarrow$$

$$\underline{p_0 = 2.81 \times 10^4 \text{ cm}^{-3}}$$

- b.  $n = n_0 + \delta n = 8 \times 10^{15} + 0.1 \times 10^{15} \Rightarrow$

$$\underline{n = 8.1 \times 10^{15} \text{ cm}^{-3}}$$

$$p = p_0 + \delta p \Rightarrow$$

$$\underline{p \approx 10^{14} \text{ cm}^{-3}}$$

E1.6

$$J = \sigma E = (10)(15) \Rightarrow$$

$$\underline{J = 150 \text{ A/cm}^2}$$

E1.7

$$\text{a. } V_{bi} = V_T \ln\left(\frac{N_a N_d}{n_i^2}\right)$$

$$V_{bi} = (0.026) \ln\left[\frac{(10^{15})(10^{17})}{(1.5 \times 10^{10})^2}\right]$$

$$\underline{V_{bi} = 0.697 \text{ V}}$$

$$\text{b. } V_{bi} = (0.026) \ln\left[\frac{(10^{17})(10^{17})}{(1.5 \times 10^{10})^2}\right]$$

$$\underline{V_{bi} = 0.817 \text{ V}}$$

E1.8

$$V_{bi} = V_T \ln \left[ \frac{N_a N_d}{n_i^2} \right] = (0.026) \ln \left[ \frac{(10^6)(10^{17})}{(1.8 \times 10^9)^2} \right]$$

$$\underline{V_{bi} = 1.23 \text{ V}}$$

E1.9

$$C_j = C_{j0} \left( 1 + \frac{V_R}{V_{bi}} \right)^{-1/2}$$

$$V_{bi} = V_T \ln \left[ \frac{N_a N_d}{n_i^2} \right]$$

$$= (0.026) \ln \left[ \frac{(10^{17})(10^{16})}{(1.5 \times 10^{10})^2} \right] = 0.757 \text{ V}$$

$$0.8 = C_{j0} \left( 1 + \frac{5}{0.757} \right)^{-1/2} = C_{j0} (7.61)^{-1/2}$$

$$= C_{j0} (0.362)$$

$$\underline{C_{j0} = 2.21 \text{ pF}}$$

E1.10

a.  $I = I_S \left[ \exp \left( \frac{V_D}{V_T} \right) - 1 \right]$

For  $V_D = 0.5$ :  $I \approx 10^{-14} \exp \left( \frac{0.5}{0.026} \right)$

For  $V_D = 0.6$ :  $I = 10^{-14} \exp \left( \frac{0.6}{0.026} \right)$

For  $V_D = 0.7$ :  $I = 10^{-14} \exp \left( \frac{0.7}{0.026} \right)$

So we have

$V_D$	$I$
0.5	2.25 $\mu\text{A}$
0.6	0.105 mA
0.7	4.93 mA

b.  $10^{-14} \text{ A}$  both cases

E1.11

$$I = I_S \left[ \exp \left( \frac{V_D}{V_T} \right) - 1 \right]$$

$$10^{-3} = (10^{-13}) \left[ \exp \left( \frac{V_D}{0.026} \right) - 1 \right]$$

$$(0.026) \ln (10^{10}) \approx V_D$$

$$\underline{V_D = 0.599 \text{ V}}$$

E1.12


$$\Delta T = 100^\circ\text{C}$$

$$\Delta V_D \approx 2 \times 100 = 200 \text{ mV}$$

$$\Rightarrow V_D = 0.650 - 0.2$$

$$\Rightarrow \underline{V_D = 0.450 \text{ V}}$$

E1.13

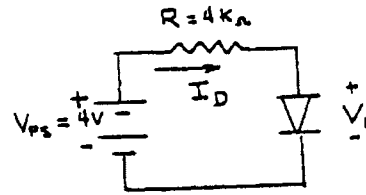

$$I_S = 10^{-12} \text{ A}$$

$$V_{PS} = I_D R + V_D \text{ and } I_D \approx I_S \exp \left( \frac{V_D}{V_T} \right)$$

So

$$4 = I_D (4) + V_D \Rightarrow I_D = (4 - V_D) / 4 \text{ mA}$$


and

$$I_D \approx I_S \exp \left( \frac{V_D}{V_T} \right) \Rightarrow I_D = 10^{-9} \exp \left( \frac{V_D}{0.026} \right) \text{ mA}$$

By trial and error:


$$I_D = 0.864 \text{ mA and } V_D = 0.535 \text{ V}$$

E1.14

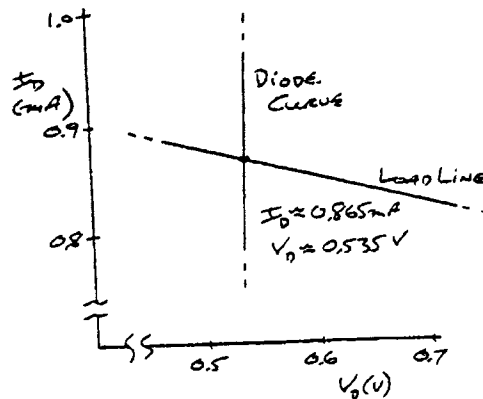

E1.15


a.

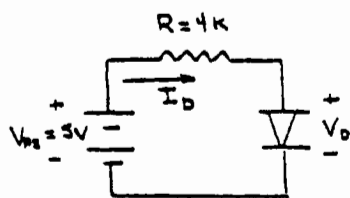


$$I_D = \frac{V_{PS} - V_T}{R} = \frac{5 - 0.7}{4} \Rightarrow I_D = 1.08 \text{ mA}$$

b.  $I_D = \frac{V_{PS} - V_T}{R} \Rightarrow R = \frac{V_{PS} - V_T}{I_D}$   
 $R = \frac{8 - 0.7}{1.075} \Rightarrow R = 6.79 \text{ k}\Omega$

c.

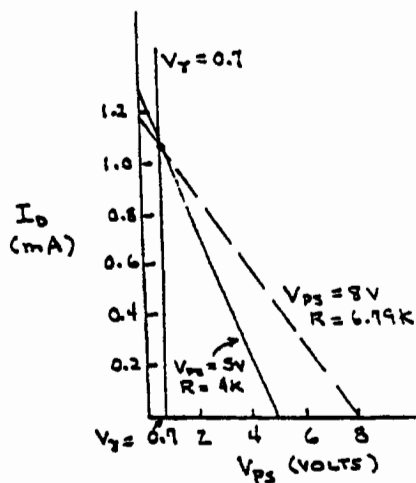

E1.16

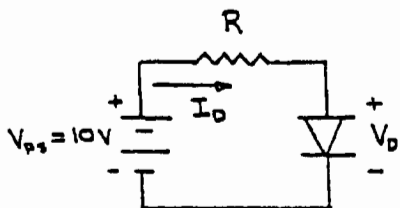

Power dissipation in diode =  $I_D V_D$

$$1.05 \text{ mW} = I_D(0.7) \Rightarrow I_D = 1.5 \text{ mA}$$

$$R = \frac{V_{PS} - V_T}{I_D} = \frac{10 - 0.7}{1.5} \Rightarrow R = 6.2 \text{ k}\Omega$$

E1.17

$$g_d = \frac{I_D}{V_T} = \frac{0.8}{0.026} = 30.8 \text{ mS}$$

E1.18

$$r_d = \frac{V_T}{I_D} \Rightarrow 50 = \frac{0.026}{I_D} \Rightarrow I_D = \frac{0.026}{50}$$
  
 $I_D = 0.52 \text{ mA}$

E1.19

$$I_D \approx I_S \exp\left(\frac{V_D}{V_T}\right)$$

$$V_D = V_T \ln\left(\frac{I_D}{I_S}\right)$$

pn junction:  $V_D = (0.026) \ln\left(\frac{10^{-3}}{10^{-12}}\right)$

$$V_D = 0.539 \text{ V}$$

Schottky Diode:  $V_D = (0.026) \ln\left(\frac{10^{-3}}{10^{-8}}\right)$

$$V_D = 0.299 \text{ V}$$

E1.20

For the pn junction diode

$$V_D = V_T \ln\left(\frac{I_D}{I_S}\right) = (0.026) \ln\left(\frac{1.2 \times 10^{-3}}{4 \times 10^{-15}}\right)$$

$$V_D = 0.6871 \text{ V}$$

Schottky diode voltage will be smaller

$$\Rightarrow V_D = 0.6871 - 0.265 = 0.4221 \text{ V}$$

$$I_D = I_S \exp\left(\frac{V_D}{V_T}\right)$$

$$I_S = \frac{1.2 \times 10^{-3}}{\exp\left(\frac{0.4221}{0.026}\right)} \Rightarrow I_S = 1.07 \times 10^{-10} \text{ A}$$

E1.21


$$\text{Power} = I \cdot V_z$$

$$10 = I(5.6) \Rightarrow I = 1.79 \text{ mA}$$

$$I = \frac{10 - 5.6}{R} = 1.79$$

$$R = \frac{10 - 5.6}{1.79} \Rightarrow \underline{R = 2.46 \text{ k}\Omega}$$

E1.22

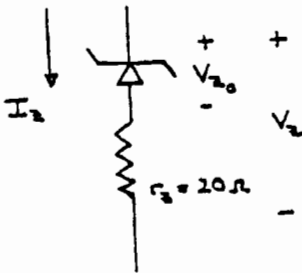

$$V_z = V_{z0} + I_z r_z$$

$$\text{So } V_{z0} = V_z - I_z r_z$$

$$V_{z0} = 5.20 - (10^{-3})(20) = 5.20 - 0.02 = 5.18$$

Then

$$V_z = 5.18 + (10 \times 10^{-3})(20) \Rightarrow \underline{V_z = 5.38 \text{ V}}$$

## Chapter 1

## Problem Solutions

1.1

(a)  $n_i = BT^{3/2} e^{-E_g/2kT}$

(i) Silicon, T=275K

$$n_i = (5.23 \times 10^{15})(275)^{3/2} e^{-1/2(86 \times 10^{-6})(275)}$$

$$n_i = 1.90 \times 10^9 \text{ cm}^{-3}$$

(ii) T=325K

$$n_i = (5.23 \times 10^{15})(325)^{3/2} e^{-1/2(86 \times 10^{-6})(325)}$$

$$n_i = 8.71 \times 10^{10} \text{ cm}^{-3}$$

(b) GaAs

(i) T=275K

$$n_i = (2.1 \times 10^{14})(275)^{3/2} e^{-1/2(86 \times 10^{-6})(275)}$$

$$n_i = 1.34 \times 10^5 \text{ cm}^{-3}$$

(ii) T=325K

$$n_i = (2.10 \times 10^{14})(325)^{3/2} e^{-1/2(86 \times 10^{-6})(325)}$$

$$n_i = 1.63 \times 10^7 \text{ cm}^{-3}$$

1.2

a.  $n_i = BT^{3/2} \exp\left(\frac{-E_g}{2kT}\right)$

$$10^{12} = 5.23 \times 10^{15} T^{3/2} \exp\left(\frac{-1.1}{2(86 \times 10^{-6})(T)}\right)$$

$$1.91 \times 10^{-4} = T^{3/2} \exp\left(-\frac{6.40 \times 10^3}{T}\right)$$

By trial and error,  $T \approx 367^\circ \text{ K}$ 

b.  $n_i = 10^9 \text{ cm}^{-3}$

$$10^9 = 5.23 \times 10^{15} T^{3/2} \exp\left(\frac{-1.1}{2(86 \times 10^{-6})(T)}\right)$$

$$1.91 \times 10^{-7} = T^{3/2} \exp\left(-\frac{6.40 \times 10^3}{T}\right)$$

By trial and error,  $T \approx 268^\circ \text{ K}$ 

1.3

a.  $N_d = 5 \times 10^{15} \text{ cm}^{-3} \Rightarrow \underline{n\text{-type}}$

$$n_0 = N_d = 5 \times 10^{15} \text{ cm}^{-3}$$

$$p_0 = \frac{n_i^2}{n_0} = \frac{(1.5 \times 10^{10})^2}{5 \times 10^{15}} \Rightarrow \underline{p_0 = 4.5 \times 10^4 \text{ cm}^{-3}}$$

b.  $N_d = 5 \times 10^{15} \text{ cm}^{-3} \Rightarrow \underline{n\text{-type}}$

$$n_0 = N_d = 5 \times 10^{15} \text{ cm}^{-3}$$

$$n_i = (2.10 \times 10^{14})(300)^{3/2} \exp\left(\frac{-1.4}{2(86 \times 10^{-6})(300)}\right)$$

$$= (2.10 \times 10^{14})(300)^{3/2}(1.65 \times 10^{-12})$$

$$= 1.80 \times 10^6 \text{ cm}^{-3}$$

$$p_0 = \frac{n_i^2}{n_0} = \frac{(1.8 \times 10^6)^2}{5 \times 10^{15}} \Rightarrow \underline{p_0 = 6.48 \times 10^{-4} \text{ cm}^{-3}}$$

1.4

a.  $N_a = 10^{16} \text{ cm}^{-3} \Rightarrow \underline{p\text{-type}}$

$$p_0 = N_a = 10^{16} \text{ cm}^{-3}$$

$$n_0 = \frac{n_i^2}{p_0} = \frac{(1.5 \times 10^{10})^2}{10^{16}} \Rightarrow \underline{n_0 = 2.25 \times 10^4 \text{ cm}^{-3}}$$

b. Germanium

$$N_a = 10^{16} \text{ cm}^{-3} \Rightarrow \underline{p\text{-type}}$$

$$p_0 = N_a = 10^{16} \text{ cm}^{-3}$$

$$n_i = (1.66 \times 10^{15})(300)^{3/2} \exp\left(\frac{-0.66}{2(86 \times 10^{-6})(300)}\right)$$

$$= (1.66 \times 10^{15})(300)^{3/2}(2.79 \times 10^{-6})$$

$$= 2.4 \times 10^{13} \text{ cm}^{-3}$$

$$n_0 = \frac{n_i^2}{p_0} = \frac{(2.4 \times 10^{13})^2}{10^{16}} \Rightarrow \underline{n_0 = 5.76 \times 10^{10} \text{ cm}^{-3}}$$

1.5

(a)  $n_0 = 5 \times 10^{15} \text{ cm}^{-3}$

$$p_0 = \frac{n_i^2}{n_0} = \frac{(1.5 \times 10^{10})^2}{5 \times 10^{15}} \Rightarrow p_0 = 4.5 \times 10^4 \text{ cm}^{-3}$$

(b)  $n_0 \gg p_0 \Rightarrow \underline{n\text{-type}}$

(c)  $n_0 \cong N_d = 5 \times 10^{15} \text{ cm}^{-3}$

1.6

a. Add Donors

$$N_d = 7 \times 10^{15} \text{ cm}^{-3}$$

b. Want  $p_0 = 10^6 \text{ cm}^{-3} = n_i^2/N_d$

So  $n_i^2 = (10^6)(7 \times 10^{15}) = 7 \times 10^{21}$

$$= B^2 T^3 \exp\left(\frac{-E_g}{kT}\right)$$

$$7 \times 10^{21} = (5.23 \times 10^{15})^2 T^3 \exp\left(\frac{-1.1}{(86 \times 10^{-6})(T)}\right)$$

By trial and error,  $T \approx 324^\circ \text{ K}$

1.7

$$I = J \cdot A = \sigma EA$$

$$I = (2.2)(15)(10^{-4}) \Rightarrow I = 3.3 \text{ mA}$$

1.8

$$J = \sigma E \Rightarrow \sigma = \frac{J}{E} = \frac{85}{12}$$

$$\sigma = 7.08 \text{ (ohm-cm)}^{-1}$$

1.9

(a) For n-type,

$$\sigma \cong e\mu_n N_d = (1.6 \times 10^{-19})(8500)N_d$$

$$\text{For } 10^{15} \leq N_d \leq 10^{19} \text{ cm}^{-3} \Rightarrow$$

$$1.36 \leq \sigma \leq 1.36 \times 10^4 \text{ (}\Omega\text{-cm)}^{-1}$$

(b)  $J = \sigma E = \sigma(0.1) \Rightarrow$

$$0.136 \leq J \leq 1.36 \times 10^3 \text{ A/cm}^2$$

1.10

a.  $N_a = 10^{17} \text{ cm}^{-3} \Rightarrow p_0 = 10^{17} \text{ cm}^{-3}$

$$n_0 = \frac{n_i^2}{p_0} = \frac{(1.8 \times 10^6)^2}{10^{17}} \Rightarrow n_0 = 3.24 \times 10^{-5} \text{ cm}^{-3}$$

b.  $n = n_0 + \delta n = 3.24 \times 10^{-5} + 10^{15} \Rightarrow n = 10^{15} \text{ cm}^{-3}$   
 $p = p_0 + \delta p = 10^{17} + 10^{15} \Rightarrow p = 1.01 \times 10^{17} \text{ cm}^{-3}$

1.11

$$V_{bi} = V_T \ln \left( \frac{N_a N_d}{n_i^2} \right)$$

a.  $V_{bi} = (0.026) \ln \left[ \frac{(10^{15})(10^{15})}{(1.5 \times 10^{10})^2} \right] \Rightarrow V_{bi} = 0.578 \text{ V}$

b.  $V_{bi} = (0.026) \ln \left[ \frac{(10^{15})(10^{18})}{(1.5 \times 10^{10})^2} \right] \Rightarrow V_{bi} = 0.757 \text{ V}$

c.  $V_{bi} = (0.026) \ln \left[ \frac{(10^{18})(10^{18})}{(1.5 \times 10^{10})^2} \right] \Rightarrow V_{bi} = 0.937 \text{ V}$

1.12

$$V_{bi} = V_T \ln \left( \frac{N_a N_d}{n_i^2} \right)$$

a.  $V_{bi} = (0.026) \ln \left[ \frac{(10^{15})(10^{15})}{(1.8 \times 10^6)^2} \right] \Rightarrow V_{bi} = 1.05 \text{ V}$

b.  $V_{bi} = (0.026) \ln \left[ \frac{(10^{15})(10^{18})}{(1.8 \times 10^6)^2} \right] \Rightarrow V_{bi} = 1.23 \text{ V}$


c.  $V_{bi} = (0.026) \ln \left[ \frac{(10^{18})(10^{18})}{(1.8 \times 10^6)^2} \right] \Rightarrow V_{bi} = 1.41 \text{ V}$

1.13

$$V_{bi} = V_T \ln \left( \frac{N_a N_d}{n_i^2} \right) = (0.026) \ln \left[ \frac{N_a (10^{16})}{(1.5 \times 10^{10})^2} \right]$$

For  $N_a = 10^{15} \text{ cm}^{-3}$ ,  $V_{bi} = 0.637 \text{ V}$

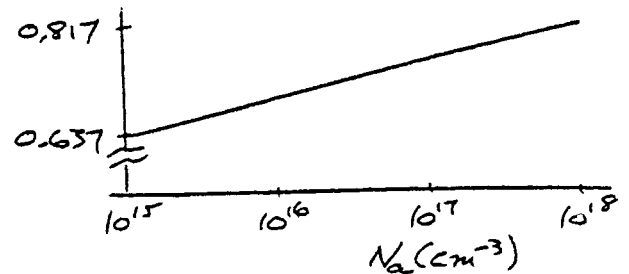For  $N_a = 10^{18} \text{ cm}^{-3}$ ,  $V_{bi} = 0.817 \text{ V}$



1.14


$$kT = (0.026) \left( \frac{T}{300} \right)$$

T	kT	(T) <sup>3/2</sup>
200	0.01733	2828.4
250	0.02167	3952.8
300	0.026	5196.2
350	0.03033	6547.9
400	0.03467	8000.0
450	0.0390	9545.9
500	0.04333	11.180.3

$$n_i = (2.1 \times 10^{14}) (T^{3/2}) \exp \left( \frac{-1.4}{2(86 \times 10^{-6})(T)} \right)$$

$$V_{bi} = V_T \ln \left( \frac{N_a N_d}{n_i^2} \right)$$

$T$	$n_i$	$V_{bi}$
200	1.256	1.405
250	$6.02 \times 10^3$	1.389
300	$1.80 \times 10^4$	1.370
350	$1.09 \times 10^4$	1.349
400	$2.44 \times 10^9$	1.327
450	$2.80 \times 10^{10}$	1.302
500	$2.00 \times 10^{11}$	1.277

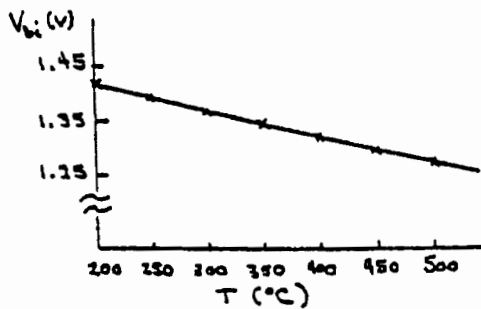

1.15

$$C_j = C_{j0} \left(1 + \frac{V_R}{V_{bi}}\right)^{-1/2}$$

$$V_{bi} = (0.026) \ln \left[ \frac{(2 \times 10^{14})(2 \times 10^{15})}{(1.5 \times 10^{10})^2} \right] = 0.673 \text{ V}$$

 a.  $V_R = 1 \text{ V}$ 

$$C_j = (1) \left(1 + \frac{1}{0.673}\right)^{-1/2} \Rightarrow \underline{C_j = 0.634 \text{ pF}}$$

 b.  $V_R = 5 \text{ V}$ 

$$C_j = (1) \left(1 + \frac{5}{0.673}\right)^{-1/2} \Rightarrow \underline{C_j = 0.344 \text{ pF}}$$

1.16

$$(a) C_j = C_{j0} \left(1 + \frac{V_R}{V_{bi}}\right)^{-1/2}$$

 For  $V_R = 5 \text{ V}$ ,

$$C_j = (0.02) \left(1 + \frac{5}{0.8}\right)^{-1/2} = 0.00743 \text{ pF}$$

 For  $V_R = 15 \text{ V}$ ,

$$C_j = (0.02) \left(1 + \frac{15}{0.8}\right)^{-1/2} = 0.0118 \text{ pF}$$

$$C_j(\text{avg}) = \frac{0.00743 + 0.0118}{2} = 0.00962 \text{ pF}$$

$$v_c(t) = v_c(\text{final}) + (v_c(\text{initial}) - v_c(\text{final}))e^{-t/\tau}$$

where

$$\tau = RC = RC_j(\text{avg}) = (47 \times 10^3)(0.00962 \times 10^{-12})$$

or

$$\tau = 4.52 \times 10^{-10} \text{ s}$$

Then

$$v_c(t) = 15 = 0 + (5 - 0)e^{-t/\tau}$$

$$\frac{5}{15} = e^{-t/\tau} \Rightarrow t_1 = \tau \ln\left(\frac{5}{15}\right)$$

$$\underline{t_1 = 5.44 \times 10^{-10} \text{ s}}$$

 (b) For  $V_R = 0 \text{ V}$ ,

$$C_j = C_{j0} = 0.02 \text{ pF}$$

 For  $V_R = 3.5 \text{ V}$ ,

$$C_j = (0.02) \left(1 + \frac{3.5}{0.8}\right)^{-1/2} = 0.00863 \text{ pF}$$

$$C_j(\text{avg}) = \frac{0.02 + 0.00863}{2} = 0.0143 \text{ pF}$$

$$\tau = RC_j(\text{avg}) = 6.72 \times 10^{-10} \text{ s}$$

$$v_c(t) = v_c(\text{final}) + (v_c(\text{initial}) - v_c(\text{final}))e^{-t/\tau}$$

$$3.5 = 5 + (0 - 5)e^{-t/\tau} = 5(1 - e^{-t/\tau})$$

$$\text{so that } \underline{t_2 = 8.09 \times 10^{-10} \text{ s}}$$

1.17

$$V_{bi} = (0.026) \ln \left[ \frac{(10^{14})(10^{15})}{(1.5 \times 10^{10})^2} \right] = 0.757 \text{ V}$$

 a.  $V_R = 1 \text{ V}$ 

$$C_j = (0.25) \left(1 + \frac{1}{0.757}\right)^{-1/2} = 0.164 \text{ pF}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{(2.2 \times 10^{-3})(0.164 \times 10^{-12})}}$$

$$\underline{f_0 = 8.38 \text{ MHz}}$$

b.  $V_R = 10 \text{ V}$

$$C_j = (0.25) \left( 1 + \frac{10}{0.757} \right)^{-1/2} = 0.0663 \text{ pF}$$

$$f_0 = \frac{1}{2\pi \sqrt{(2.2 \times 10^{-3})(0.0663 \times 10^{-12})}}$$

$$f_0 = 13.2 \text{ MHz}$$

1.18

a.  $I = I_S \left[ \exp\left(\frac{V_D}{V_T}\right) - 1 \right]$

$$-0.90 = \exp\left(\frac{V_D}{V_T}\right) - 1$$

$$\exp\left(\frac{V_D}{V_T}\right) = 1 - 0.90 = 0.10$$

$$V_D = V_T \ln(0.10) \Rightarrow \underline{V_D = -0.0599 \text{ V}}$$

b.

$$\left| \frac{I_F}{I_R} \right| = \frac{I_S}{I_S} \cdot \frac{\left[ \exp\left(\frac{V_F}{V_T}\right) - 1 \right]}{\left[ \exp\left(\frac{V_R}{V_T}\right) - 1 \right]} = \frac{\left[ \exp\left(\frac{0.2}{0.026}\right) - 1 \right]}{\left[ \exp\left(\frac{-0.2}{0.026}\right) - 1 \right]}$$

$$= \left| \frac{2190}{-1} \right|$$

$$\underline{\frac{I_F}{I_R} = 2190}$$

1.19

a.

$$I \approx (10^{-11}) \exp\left(\frac{0.5}{0.026}\right) \Rightarrow \underline{I = 2.25 \text{ mA}}$$

$$I = (10^{-11}) \exp\left(\frac{0.6}{0.026}\right) \Rightarrow \underline{I = 0.105 \text{ A}}$$

$$I = (10^{-11}) \exp\left(\frac{0.7}{0.026}\right) \Rightarrow \underline{I = 4.93 \text{ A}}$$

b.

$$I \approx (10^{-13}) \exp\left(\frac{0.5}{0.026}\right) \Rightarrow \underline{I = 22.5 \text{ } \mu\text{A}}$$

$$I = (10^{-13}) \exp\left(\frac{0.6}{0.026}\right) \Rightarrow \underline{I = 1.05 \text{ mA}}$$

$$I = (10^{-13}) \exp\left(\frac{0.7}{0.026}\right) \Rightarrow \underline{I = 49.3 \text{ mA}}$$

1.20

(a)  $I = I_S (e^{V_D/V_T} - 1)$

$$150 \times 10^{-6} = 10^{-11} (e^{V_D/V_T} - 1) \approx 10^{-11} e^{V_D/V_T}$$

Then

$$V_D = V_T \ln\left(\frac{150 \times 10^{-6}}{10^{-11}}\right) = (0.026) \ln\left(\frac{150 \times 10^{-6}}{10^{-11}}\right)$$

Or

$$\underline{V_D = 0.430 \text{ V}}$$

(b)

$$V_D = V_T \ln\left(\frac{150 \times 10^{-6}}{10^{-13}}\right)$$

Or

$$\underline{V_D = 0.549 \text{ V}}$$

1.21

a.  $I_D \approx I_S \exp\left(\frac{V_D}{nV_T}\right)$

$$10^{-3} = I_S \exp\left(\frac{0.7}{2(0.026)}\right) \Rightarrow \underline{I_S = 1.42 \times 10^{-9} \text{ A}}$$

b.  $I_D = (1.42 \times 10^{-9}) \exp\left(\frac{0.8}{2(0.026)}\right)$

$$\underline{I_D = 6.82 \text{ mA}}$$

c.  $10^{-3} = I_S \exp\left(\frac{0.7}{0.026}\right)$

$$\underline{I_S = 2.03 \times 10^{-15} \text{ A}}$$

$$I_D = (2.03 \times 10^{-15}) \exp\left(\frac{0.8}{0.026}\right)$$

$$\underline{I_D = 46.8 \text{ mA}}$$

1.22

$I_S$  doubles for every 5C increase in temperature.

$$I_S = 10^{-12} \text{ A at } T = 300\text{K}$$

$$\text{For } I_S = 0.5 \times 10^{-12} \text{ A} \Rightarrow \underline{T = 295\text{K}}$$

$$\text{For } I_S = 50 \times 10^{-12} \text{ A, } (2)^n = 50 \Rightarrow n = 5.64$$

Where n equals number of 5C increases.

Then

$$\Delta T = (5.64)(5) = 28.2\text{K}$$

So

$$\underline{295 \leq T \leq 328.2\text{K}}$$

1.23

$$\frac{I_S(T)}{I_S(-55)} = 2^{\Delta T/10}, \quad \Delta T = 155^\circ\text{C}$$

$$\frac{I_S(100)}{I_S(-55)} = 2^{155/10} = 2.147 \times 10^9$$

$$V_T @ 100^\circ\text{C} \Rightarrow 373^\circ\text{K} \Rightarrow V_T = 0.03220$$

$$V_T @ -55^\circ\text{C} \Rightarrow 216^\circ\text{K} \Rightarrow V_T = 0.01865$$

$$\frac{I_D(100)}{I_D(-55)} = (2.147 \times 10^9) \times \frac{\exp\left(\frac{0.6}{0.0322}\right)}{\exp\left(\frac{0.6}{0.01865}\right)}$$

$$= \frac{(2.147 \times 10^9)(1.237 \times 10^8)}{(9.374 \times 10^{13})}$$

$$\frac{I_D(100)}{I_D(-55)} = 2.83 \times 10^3$$

1.24


a.  $\frac{I_{D2}}{I_{D1}} = 10 = \exp\left(\frac{V_{D2} - V_{D1}}{V_T}\right)$

$$\Delta V_D = V_T \ln(10) \Rightarrow \Delta V_D = 59.9 \text{ mV} \approx 60 \text{ mV}$$

b.  $\Delta V_D = V_T \ln(100) \Rightarrow \Delta V_D = 119.7 \text{ mV} \approx 120 \text{ mV}$

1.25

a.

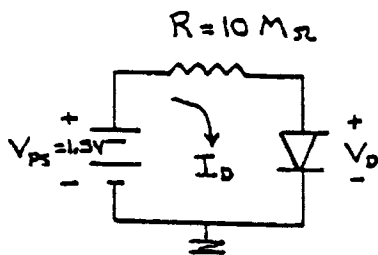

$$1.5 = I_D(10 \times 10^6) + V_D \text{ and}$$

$$I_D = I_S \left[ \exp\left(\frac{V_D}{V_T}\right) - 1 \right]$$

$$1.5 = (10 \times 10^6)(30 \times 10^{-9}) \left[ \exp\left(\frac{V_D}{V_T}\right) - 1 \right] + V_D$$

$$= 0.3 \left[ \exp\left(\frac{V_D}{V_T}\right) - 1 \right] + V_D$$

By trial and error,  $V_D = 0.046 \text{ V}$

$$\text{Then } I_D = \frac{1.5 - 0.046}{10} \Rightarrow I_D = 0.145 \mu\text{A}$$

b. Reverse-Bias


$$I = I_S = 30 \text{ nA}$$

$$V_R = (30 \times 10^{-9})(10 \times 10^6) = 0.30 \text{ V}$$


$$V_D = -1.5 + 0.3 \Rightarrow V_D = -1.2 \text{ V}$$

1.26

$$I_S = 5 \times 10^{-13} \text{ A}$$

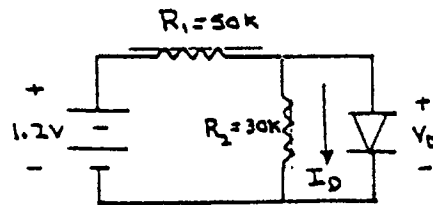
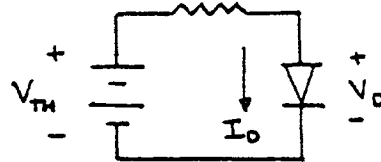
$$R_{TH} = R_1 \parallel R_2 = 18.75 \text{ k}$$




$$V_{TH} = \left(\frac{R_2}{R_1 + R_2}\right)(1.2) = \left(\frac{30}{80}\right)(1.2) = 0.45 \text{ V}$$

$$0.45 = I_D R_{TH} + V_D, \quad V_D = V_T \ln\left(\frac{I_D}{I_S}\right)$$

By trial and error:

$$I_D = 2.6 \mu\text{A}, \quad V_D = 0.402 \text{ V}$$

1.27

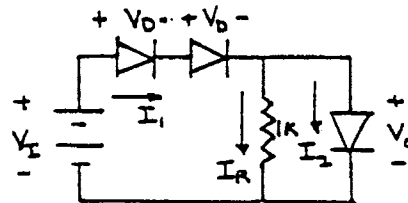

$$I_S = 2 \times 10^{-13} \text{ A}$$

$$V_D = 0.60 \text{ V}$$

$$I_2 = I_S \exp\left(\frac{V_D}{V_T}\right) = (2 \times 10^{-13}) \exp\left(\frac{0.60}{0.026}\right)$$

$$= 2.105 \text{ mA}$$

$$I_R = \frac{0.6}{1 \text{ k}} = 0.60 \text{ mA}$$


$$I_1 = I_2 + I_R = 2.705 \text{ mA}$$

$$V_D = V_T \ln\left(\frac{I_1}{I_S}\right) = (0.026) \ln\left(\frac{2.705 \times 10^{-3}}{2 \times 10^{-13}}\right)$$

$$= 0.6065$$

$$V_I = 2V_D + V_D \Rightarrow V_I = 1.81 \text{ V}$$

1.28

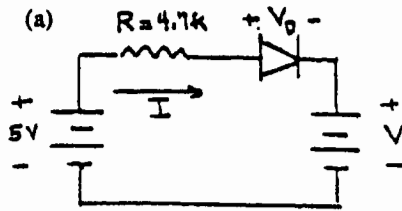

$$I_S = 5 \times 10^{-12} \text{ A}$$

$$I = 0.50 \text{ mA}$$

$$V_D = (0.026) \ln \left( \frac{0.5 \times 10^{-3}}{5 \times 10^{-12}} \right)$$

$$\underline{V_D = 0.479 \text{ V}}$$

$$5 = IR + V_D + V$$

$$= (0.5 \times 10^{-3})(4.7 \times 10^3) + 0.479 + V$$

$$\underline{V = 2.17 \text{ V}}$$

(b)  $P = I_D V_D = (0.5)(0.479)$

or

$$\underline{P = 0.24 \text{ mW}}$$

1.29

(a) Assume diode is conducting.

Then,  $V_D = V_f = 0.7 \text{ V}$

So that  $I_{R2} = \frac{0.7}{30} \Rightarrow 23.3 \mu\text{A}$

$$I_{R1} = \frac{1.2 - 0.7}{10} \Rightarrow 50 \mu\text{A}$$

Then  $I_D = I_{R1} - I_{R2} = 50 - 23.3$

Or

$$\underline{I_D = 26.7 \mu\text{A}}$$

(b) Let  $R_1 = 50 \text{ k}\Omega$  Diode is cutoff.

$$V_D = \frac{30}{30 + 50} \cdot (1.2) = 0.45 \text{ V}$$

Since  $V_D < V_f$ ,  $I_D = 0$

1.30

(a) Diode is conducting

$$5 = I_D(10) + V_f - 5$$

or

$$I_D = \frac{10 - 0.6}{10} \Rightarrow \underline{I_D = 0.94 \text{ mA}}$$

$$V_o = V_f - 5 = 0.6 - 5 \Rightarrow \underline{V_o = -4.4 \text{ V}}$$

(b) Diode is conducting

$$5 = V_f + I_D(10) - 5$$

or

$$I_D = \frac{10 - 0.6}{10} \Rightarrow \underline{I_D = 0.94 \text{ mA}}$$

$$V_o = I_D R - 5 = (0.94)(10) - 5 \Rightarrow \underline{V_o = 4.4 \text{ V}}$$

(c) Diode is reverse biased

$$I_D = 0 \quad \underline{V_D = -10 \text{ V}}$$

$$V_D = 15 \text{ VDC}$$

1.31

Minimum diode current for  $V_{RS}(\text{min})$

$$I_D(\text{min}) = 2 \text{ mA}, \quad V_D = 0.7 \text{ V}$$

$$I_2 = \frac{0.7}{R_2}, \quad I_1 = \frac{5 - 0.7}{R_1} = \frac{4.3}{R_1}$$

We have

$$I_1 = I_2 + I_D$$

so

$$(1) \frac{4.3}{R_1} = \frac{0.7}{R_2} + 2$$

Maximum diode current for  $V_{RS}(\text{max})$

$$P = I_D V_D \quad 10 = I_D(0.7) \Rightarrow I_D = 14.3 \text{ mA}$$

$$I_1 = I_2 + I_D$$

or

$$(2) \frac{9.3}{R_1} = \frac{0.7}{R_2} + 14.3$$


Using Eq. (1),

$$\frac{9.3}{R_1} = \frac{4.3}{R_1} - 2 + 14.3 \Rightarrow \underline{R_1 = 0.41 \text{ k}\Omega}$$

Then

$$\underline{R_2 = 82.5 \Omega}$$

1.32

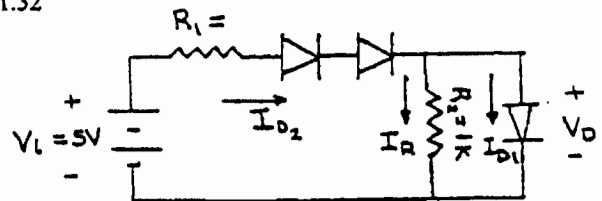


$$I_{D1} = \frac{1}{2} I_{D2} \Rightarrow I_{D1} = I_R = \frac{0.65}{1} = 0.65 \text{ mA}$$

$$I_{D2} = 1.3 \text{ mA} = \frac{5 - 3(0.65)}{R_1}$$

$$\underline{R_1 = 2.35 \text{ k}\Omega}, \quad \underline{I_{D1} = 0.65 \text{ mA}}, \quad \underline{I_{D2} = 1.30 \text{ mA}}$$

1.33

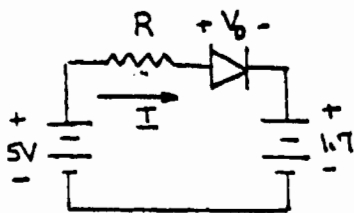

$$V_T = 0.65 \text{ V}$$

$$\text{Power} = I \cdot V_T = 0.2 \text{ mW} = I(0.65)$$

$$\Rightarrow I = 0.308 \text{ mA}$$

$$I = \frac{5 - 0.65 - 1.7}{R} = 0.308$$

$$\Rightarrow R = \frac{2.65}{0.308} \Rightarrow R = 8.60 \text{ k}\Omega$$

1.34

For forward bias

$$I_D = \frac{15 - 0.7}{10 \text{ M}\Omega} = 0.08 \mu\text{A}$$

For reverse bias

$$I_D = 0, \quad V_D = -15 \text{ V}$$

1.35

$$\text{a. } r_d = \frac{V_T}{I_{DQ}} = \frac{(0.026)}{1} = 0.026 \text{ k}\Omega = 26 \Omega$$

$$i_d = 0.05 I_{DQ} = 50 \mu\text{A peak-to-peak}$$

$$v_d = i_d r_d = (26)(50) \mu\text{V}$$

$$\Rightarrow v_d = 1.30 \text{ mV peak-to-peak}$$


$$\text{b. For } I_{DQ} = 0.1 \text{ mA} \Rightarrow r_d = \frac{(0.026)}{0.1} = 260 \Omega$$

$$i_d = 0.05 I_{DQ} = 5 \mu\text{A peak-to-peak}$$

$$v_d = i_d r_d = (260)(5) \mu\text{V}$$

$$\Rightarrow v_d = 1.30 \text{ mV peak-to-peak}$$

1.36

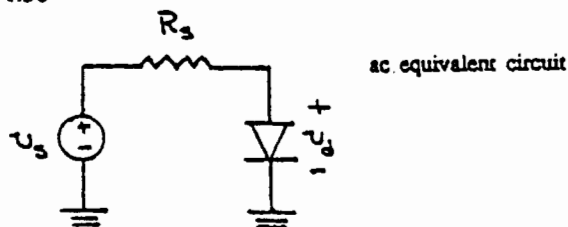

$$\text{a. diode resistance } r_d = V_T / I$$

$$v_d = \left( \frac{r_d}{r_d + R_s} \right) v_s = \left( \frac{V_T / I}{V_T / I + R_s} \right) v_s$$

$$v_d = \left( \frac{V_T}{V_T + I R_s} \right) v_s = v_o$$

$$\text{b. } R_s = 260 \Omega$$

$$I = 1 \text{ mA}, \quad \frac{v_o}{v_s} = \left( \frac{V_T}{V_T + I R_s} \right) = \frac{0.026}{0.026 + (1)(0.26)}$$

$$\Rightarrow \frac{v_o}{v_s} = 0.0909$$

$$I = 0.1 \text{ mA}, \quad \frac{v_o}{v_s} = \frac{0.026}{0.026 + (0.1)(0.26)}$$

$$\Rightarrow \frac{v_o}{v_s} = 0.50$$

$$I = 0.01 \text{ mA}, \quad \frac{v_o}{v_s} = \frac{0.026}{0.026 + (0.01)(0.26)}$$

$$\Rightarrow \frac{v_o}{v_s} = 0.909$$

1.37

$$I \approx I_S \exp\left(\frac{V_a}{V_T}\right), \quad V_a = V_T \ln\left(\frac{I}{I_S}\right)$$


$$\text{pn junction, } V_a = (0.026) \ln\left(\frac{100 \times 10^{-6}}{10^{-14}}\right)$$

$$V_a = 0.599 \text{ V}$$

$$\text{Schottky diode, } V_a = (0.026) \ln\left(\frac{100 \times 10^{-6}}{10^{-9}}\right)$$

$$V_a = 0.299 \text{ V}$$

1.38

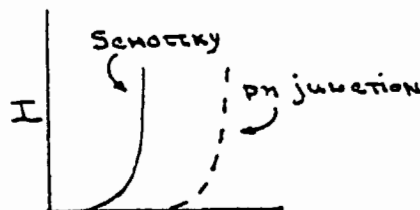

$$\text{Schottky: } I \approx I_S \exp\left(\frac{V_a}{V_T}\right)$$

$$V_a = V_T \ln\left(\frac{I}{I_S}\right) = (0.026) \ln\left(\frac{0.5 \times 10^{-3}}{5 \times 10^{-7}}\right) = 0.1796 \text{ V}$$

Then

$$V_a \text{ of pn junction} = 0.1796 + 0.30$$

$$= 0.4796$$

$$I_S = \frac{I}{\exp\left(\frac{V_a}{V_T}\right)} = \frac{0.5 \times 10^{-3}}{\exp\left(\frac{0.4796}{0.026}\right)}$$

$$I_S = 4.87 \times 10^{-12} \text{ A}$$

1.39

pn junction  $I_D = 0.5 \text{ mA}$

$$I_D \cong I_S e^{V_D/V_T} \Rightarrow V_D = V_T \ln \left( \frac{I_D}{I_S} \right)$$

Then

$$V_D = (0.026) \ln \left( \frac{0.5 \times 10^{-3}}{10^{-12}} \right) = 0.521 \text{ V}$$


Schottky diode

$$V_D = (0.026) \ln \left( \frac{0.5 \times 10^{-3}}{10^{-8}} \right) = 0.281 \text{ V}$$

Then

$$R = \frac{V_D(\text{pn}) - V_D(\text{S})}{0.5} = \frac{0.521 - 0.281}{0.5} \Rightarrow R = 480 \Omega$$

1.40

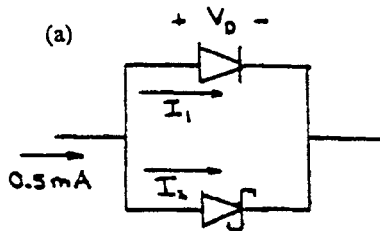

$$I_1 + I_2 = 0.5 \times 10^{-3}$$

$$5 \times 10^{-8} \exp \left( \frac{V_D}{V_T} \right) + 10^{-12} \exp \left( \frac{V_D}{V_T} \right) = 0.5 \times 10^{-3}$$


$$5.001 \times 10^{-8} \exp \left( \frac{V_D}{V_T} \right) = 0.5 \times 10^{-3}$$

$$V_D = (0.026) \ln \left( \frac{0.5 \times 10^{-3}}{5.001 \times 10^{-8}} \right) \Rightarrow V_D = 0.2395$$

Schottky diode,  $I_2 = 0.49999 \text{ mA}$

pn junction,  $I_1 = 0.00001 \text{ mA}$

(b)

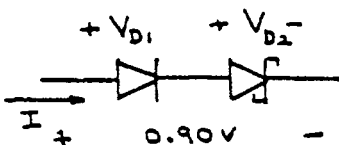

$$I = 10^{-12} \exp \left( \frac{V_{D1}}{V_T} \right) = 5 \times 10^{-8} \exp \left( \frac{V_{D2}}{V_T} \right)$$

$$V_{D1} + V_{D2} = 0.9$$

$$10^{-12} \exp \left( \frac{V_{D1}}{V_T} \right) = 5 \times 10^{-8} \exp \left( \frac{0.9 - V_{D1}}{V_T} \right)$$

$$= 5 \times 10^{-8} \exp \left( \frac{0.9}{V_T} \right) \cdot \exp \left( \frac{-V_{D1}}{V_T} \right)$$

$$\exp \left( \frac{2V_{D1}}{V_T} \right) = \left( \frac{5 \times 10^{-8}}{10^{-12}} \right) \exp \left( \frac{0.9}{0.026} \right)$$


$$2V_{D1} = V_T \ln \left( \frac{5 \times 10^{-8}}{10^{-12}} \right) + 0.9 = 1.1813$$

$$V_{D1} = 0.591 \text{ pn junction}$$

$$V_{D2} = 0.309 \text{ Schottky diode}$$

$$I = 10^{-12} \exp \left( \frac{0.5907}{0.026} \right) \Rightarrow I = 7.36 \text{ mA}$$

1.41

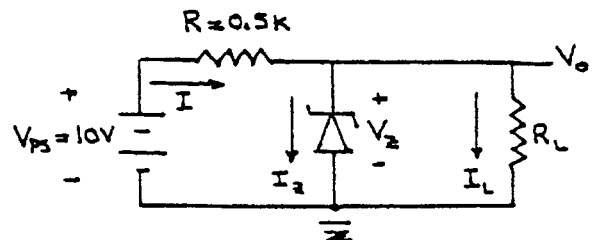

$$V_Z = V_{Z0} = 5.6 \text{ V at } I_Z = 0.1 \text{ mA}$$

$$r_z = 10 \Omega$$

$$I_Z r_z = (0.1)(10) = 1 \text{ mV}$$

$$V_{Z0} = 5.599$$

a.  $R_L \rightarrow \infty \Rightarrow$

$$I_Z = \frac{10 - 5.599}{R + r_z} = \frac{4.401}{0.50 + 0.01} = 8.63 \text{ mA}$$

$$V_Z = V_{Z0} + I_Z r_z = 5.599 + (0.00863)(10)$$

$$V_Z = V_O = 5.685 \text{ V}$$

$$\text{b. } V_{PS} = 11 \text{ V} \Rightarrow I_Z = \frac{11 - 5.599}{0.51} = 10.59 \text{ mA}$$

$$V_Z = V_O = 5.599 + (0.01059)(10) = 5.705 \text{ V}$$

$$V_{PS} = 9 \text{ V} \Rightarrow I_Z = \frac{9 - 5.599}{0.51} = 6.669 \text{ mA}$$

$$V_Z = V_O = 5.599 + (0.006669)(10) = 5.666 \text{ V}$$

$$\Delta V_O = 5.705 - 5.666 \Rightarrow \Delta V_O = 0.039 \text{ V}$$

$$c. \quad I = I_Z + I_L$$

$$I_L = \frac{V_0}{R_L}, \quad I = \frac{V_{PS} - V_0}{R}, \quad I_Z = \frac{V_0 - V_{Z0}}{r_Z}$$

$$\frac{10 - V_0}{0.50} = \frac{V_0 - 5.599}{0.010} + \frac{V_0}{2}$$

$$\frac{10}{0.50} + \frac{5.599}{0.010} = V_0 \left[ \frac{1}{0.50} + \frac{1}{0.010} + \frac{1}{2} \right]$$

$$20.0 + 559.9 = V_0(102.5)$$

$$\underline{V_0 = 5.658 \text{ V}}$$

1.42

$$a. \quad I_Z = \frac{9 - 6.8}{0.2} \Rightarrow \underline{I_Z = 11 \text{ mA}}$$

$$P_Z = (11)(6.8) \Rightarrow \underline{P_Z = 74.8 \text{ mW}}$$

$$b. \quad I_Z = \frac{12 - 6.8}{0.2} \Rightarrow \underline{I_Z = 26 \text{ mA}}$$

$$\% = \frac{26 - 11}{11} \times 100 \Rightarrow \underline{136\%}$$

$$P_Z = (26)(6.8) = 176.8 \text{ mW}$$

$$\% = \frac{176.8 - 74.8}{74.8} \times 100 = \underline{136\%}$$

1.43

$$I_Z r_Z = (0.1)(20) = 2 \text{ mV}$$

$$V_{Z0} = 6.8 - 0.002 = 6.798 \text{ V}$$

$$a. \quad R_L = \infty$$

$$I_Z = \frac{10 - 6.798}{0.5 + 0.02} \Rightarrow I_Z = 6.158 \text{ mA}$$

$$V_0 = V_Z = V_{Z0} + I_Z r_Z = 6.798 + (0.006158)(20)$$

$$\underline{V_0 = 6.921 \text{ V}}$$

$$b. \quad I = I_Z + I_L$$

$$\frac{10 - V_0}{0.50} = \frac{V_0 - 6.798}{0.020} + \frac{V_0}{1}$$

$$\frac{10}{0.50} + \frac{6.798}{0.020} = V_0 \left[ \frac{1}{0.50} + \frac{1}{0.020} + \frac{1}{1} \right]$$

$$359.9 = V_0(53)$$

$$V_0 = 6.791 \text{ V}$$

$$\Delta V_0 = 6.791 - 6.921$$


$$\underline{\Delta V_0 = -0.13 \text{ V}}$$



## Chapter 2

### Exercise Solutions


E2.1

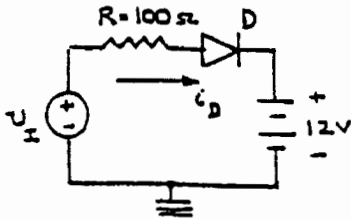

a.  $i_D(\text{peak}) = \frac{24 - 12 - 0.6}{0.10} = 114 \text{ mA}$

b.  $V_R(\text{max}) = 24 + 12 = 36 \text{ V}$

c.

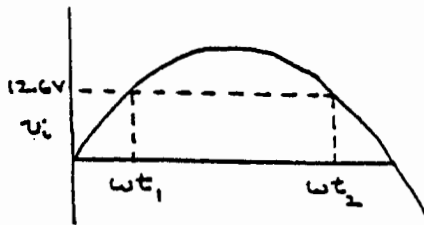


$v_s = 24 \sin \omega t = 12.6$

$\omega t_1 = \sin^{-1} \left( \frac{12.6}{24} \right) = 31.7^\circ$

By symmetry,  $\omega t_2 = 180 - 31.7 = 148.3^\circ$

$\% = \left( \frac{148.3 - 31.7}{360} \right) \times 100\% \Rightarrow 32.4\%$

E2.2

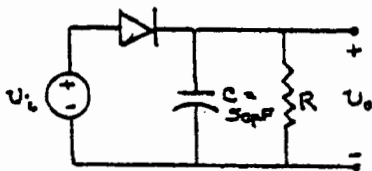

$v_s = 75 \sin(2\pi 60t)$

$V_r = \frac{V_m}{fRC}$

or  $R = \frac{V_m}{fCV_r} = \frac{75}{(60)(50 \times 10^{-6})(4)}$

$R = 6.25 \text{ k}\Omega$

E2.3

$v_s = 120 \sin(2\pi 60t)$ ,  $V_r = 0.7$ ,  $R = 2.5 \text{ k}\Omega$

Full-wave rectifier

Turns ratio 1 : 2  $\Rightarrow v_s = v$

$V_M = 120 - 0.7 = 119.3 \text{ V}$

$V_r = 119.3 - 100 = 19.3 \text{ V}$

So  $C = \frac{V_m}{2fRV_r} = \frac{119.3}{2(60)(2.5 \times 10^3)(19.3)}$

$C = 2.06 \times 10^{-5} = 20.6 \times 10^{-6} \Rightarrow C = 20.6 \mu\text{F}$

E2.4

$v_s = 50 \sin(2\pi 60t)$ ,  $V_r = 0.7$ ,  $R = 10 \text{ k}\Omega$

Full-wave rectifier

$C = \frac{V_m}{2fRV_r} = \frac{(50 - 1.4)}{2(60)(10 \times 10^3)(2)}$

$C = 2.025 \times 10^{-5} = 20.25 \times 10^{-6} \Rightarrow C = 20.3 \mu\text{F}$

E2.5

Using Eq. (2-10)

a.  $\omega \Delta t = \sqrt{\frac{2V_r}{V_M}} = \sqrt{\frac{2(4)}{75}} = 0.327$

$\% = \left( \frac{0.327}{2\pi} \right) \times 100\% = 5.2\%$


b.  $\omega \Delta t = \sqrt{\frac{2V_r}{V_M}} = \sqrt{\frac{2(19.3)}{119.3}} = 0.569$

$\% = \left( \frac{0.569}{\pi} \right) \times 100\% = 18.1\%$

c.  $\omega \Delta t = \sqrt{\frac{2V_r}{V_M}} = \sqrt{\frac{2(2)}{48.6}} = 0.287$

$\% = \left( \frac{0.287}{\pi} \right) \times 100\% = 9.14\%$

E2.6

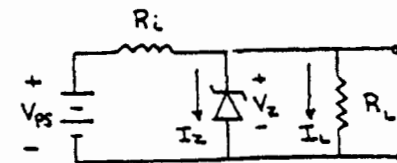

$10 \leq V_{PS} \leq 14 \text{ V}$ ,  $V_Z = 5.6$

$20 \leq R_L \leq 100$

$I_L(\text{max}) = \frac{5.6}{20} = 0.28 \text{ A}$ ,  $I_L(\text{min}) = \frac{5.6}{100} = 0.056 \text{ A}$

$$I_z(\max) = \frac{[V_{PS}(\max) - V_Z]I_L(\max)}{V_{PS}(\min) - 0.9V_Z - 0.1V_{PS}(\max)} - \frac{[V_{PS}(\min) - V_Z]I_L(\min)}{V_{PS}(\min) - 0.9V_Z - 0.1V_{PS}(\max)}$$

$$= \frac{[14 - 5.6](280) - [10 - 5.6](56)}{10 - (0.9)(5.6) - (0.1)(14)}$$

$$= \frac{2352 - 246.4}{3.56}$$

$I_z(\max) = 591.5 \text{ mA}$

Power(min) =  $I_z(\max) \cdot V_Z = (0.5915)(5.6)$

Power = 3.31 W

$$R_s = \frac{V_{PS}(\max) - V_Z}{I_z(\max) + I_L(\min)} = \frac{14 - 5.6}{0.5915 + 0.056}$$

$$= \frac{8.4}{0.6475}$$

$R_s \approx 13\Omega$

E2.7

$$I_z = \frac{V_{PS} - V_Z}{R_s} - I_L$$

For  $V_{PS}(\min)$  and  $I_L(\max)$ , then

$$I_z(\min) = \frac{11 - 9}{20} - 0.1 = 0$$

(Minimum Zener current is zero.)

For  $V_{PS}(\max)$  and  $I_L(\min)$ , then

$$I_z(\max) = \frac{13.6 - 9}{20} - 0 \Rightarrow 230 \text{ mA}$$

The characteristic of the minimum Zener current being one-tenth of the maximum value is violated. The proper circuit operation is questionable.

E2.8

$$I_z(\min) = \frac{V_{PS}(\min) - V_Z}{R_s} - I_L(\max)$$

so

$$30 = \frac{10 - 9}{0.0153} - I_L(\max)$$

Or

$$I_L(\max) = 35.4 \text{ mA}$$

E2.9

$$\% \text{ Regulation} = \frac{V_L(\max) - V_L(\min)}{V_L(\text{nominal})}$$

$V_L(\text{nominal}) = 5.6$

$$V_L(\max) = V_L(\text{nominal}) + I_z(\max)r_z$$

$$= 5.6 + (0.5915)(1.5) = 6.487$$

$$V_L(\min) = V_L(\text{nominal}) + I_z(\min)r_z$$

$$= 5.6 + (I_z(\min))(1.5)$$


$$I_z(\min) = \frac{10 - 5.6}{13} - 0.280$$

$$= 0.0585 \text{ A}$$



$$V_L(\min) = 5.6 + (0.0585)(1.5) = 5.688$$

$$\% \text{ Reg} = \frac{6.487 - 5.688}{5.6} = 0.143 \Rightarrow 14.3\%$$

E2.10

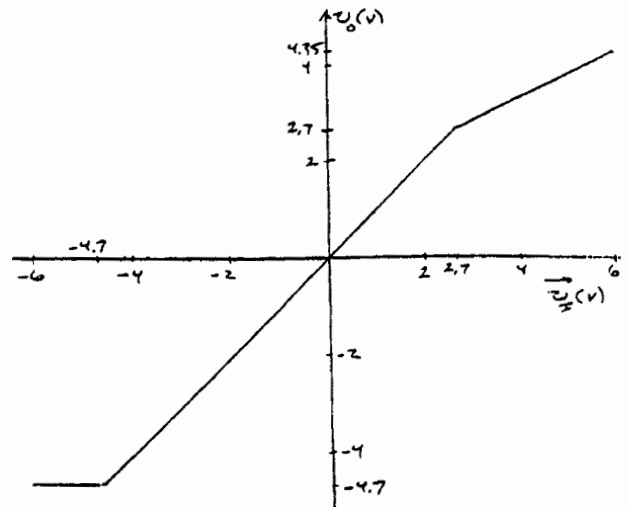

E2.11

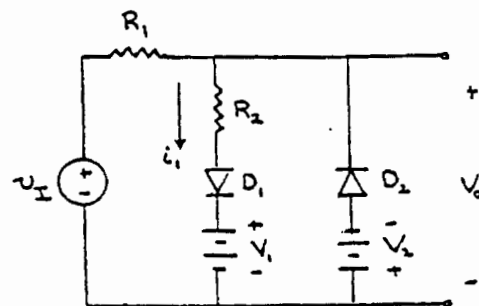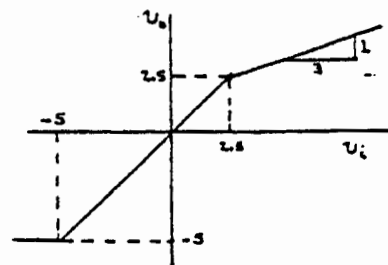

$V_T = 0.7 \text{ V}$

For  $v_I < 3$ ,  $D_2$  on  $\Rightarrow V_0 = -5 \text{ V} \Rightarrow V_2 = 4.3 \text{ V}$

$D_1$  turns on when  $v_I = 2.5 \Rightarrow V_1 = 1.8 \text{ V}$

For  $v_I > 2.5$ ,  $\frac{\Delta v_0}{\Delta v_I} = \frac{1}{3} \Rightarrow \frac{R_2}{R_1 + R_2} = \frac{1}{3}$   
 $\Rightarrow R_1 = 2R_2$

E2.12


For  $V_T = 0$ ,  $v_0(\text{max}) = -2 \text{ V}$

Now,  $\Delta v_0 = 8 \text{ V}$ , so that

$v_0(\text{min}) = -10 \text{ V}$

E2.13

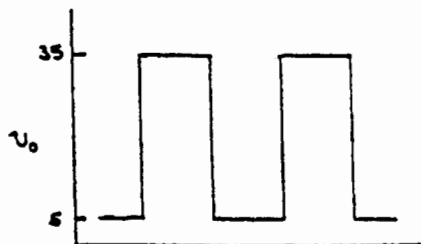As  $v_S$  goes negative,  $D$  turns on and  $v_0 = +5 \text{ V}$ .  
 As  $v_S$  goes positive,  $D$  turns off.



Output, a square wave oscillating between +5 and +35 volts.


E2.14

$v_0 = 4.4$ ,  $I = \frac{10 - 4.4}{9.5} = 0.5895 \text{ mA}$

Set  $I = I_{D1}$

$v_I = 4.4 - 0.6 - (0.5895)(0.5)$

$v_I = 3.505$

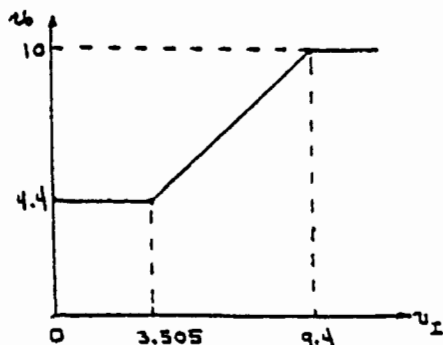

Summary:  $0 \leq v_I \leq 3.5$ ,  $v_0 = 4.4$

For  $v_I > 3.5$ ,  $D2$  turns off and when  $v_I \geq 9.4$ ,

$v_0 = 10$


E2.15

$V_0 = -0.6 \text{ V}$ ,  $I_{D1} = 0$ .


$I_{D2} = I = \frac{-0.6 - (-10)}{2.2} \Rightarrow I_{D2} = I = 4.27 \text{ mA}$

E2.16

(a)

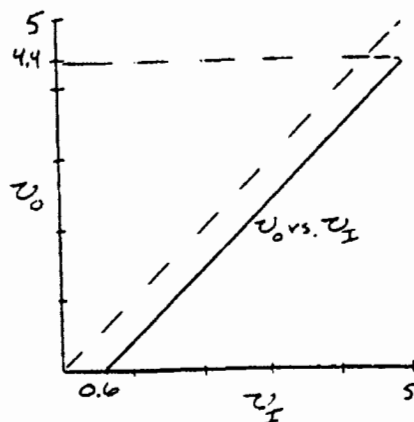


(b)

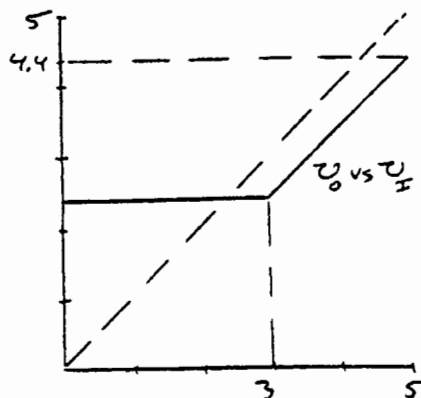

E2.17

a.  $V_0 = 0.6 \text{ V}$  for all  $V_i$

b.

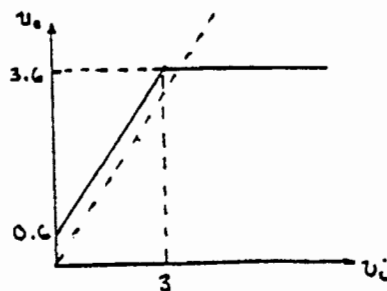

E2.18

a.  $I_{PH} = \eta e \Phi A$


$$I_{PH} = (0.8)(1.6 \times 10^{-19}) \left[ \frac{6.4 \times 10^{-2}}{(2)(1.6 \times 10^{-19})} \right] (0.5)$$

$$I_{PH} = 12.8 \text{ mA}$$

- b. We have  $v_0 = (12.8)(1) = 12.8$  volts.  
The diode must be reverse biased so that  $V_{PS} > 12.8$  volts.

E2.19

The equivalent circuit is

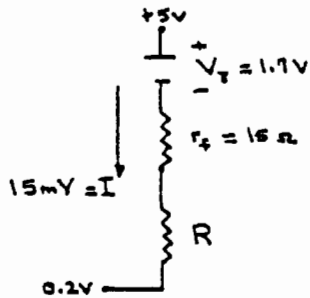

$$I = \frac{5 - 1.7 - 0.2}{r_f + R} = 15 \text{ mA}$$

$$r_f + R = \frac{5 - 1.7 - 0.2}{15} = \frac{3.1}{15} = 0.207 \text{ k}\Omega$$



$$= 207 \Omega$$

$$R = 207 - 15 \Rightarrow R = 192 \Omega$$

## Chapter 2

### Problem Solutions

2.1

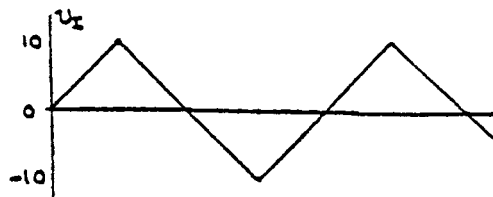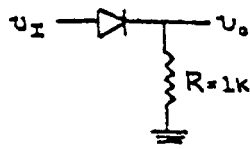


$V_T = 0.6 \text{ V}, r_f = 20 \Omega$


$$\text{For } v_i = 10 \text{ V}, v_o = \left( \frac{R}{R + r_f} \right) (10 - 0.6)$$

$$= \left( \frac{1}{1 + 0.02} \right) (9.4)$$

$v_o = 9.22$

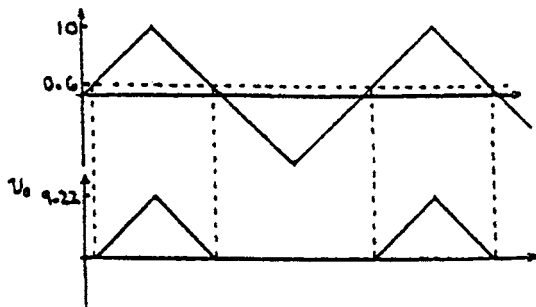

2.2

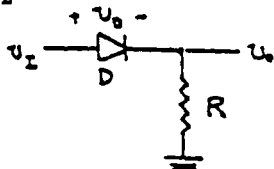

$v_o = v_i - v_D$

$v_D = V_T \ln \left( \frac{i_D}{I_S} \right)$  and  $i_D = \frac{v_o}{R}$


$v_o = v_i - V_T \ln \left( \frac{v_o}{I_S R} \right)$

2.3

(a)  $v_s(\text{max}) = \frac{160}{4} = 40 \text{ V}$

(b)  $PIV = |v_s(\text{max})| = 40 \text{ V}$

(c)

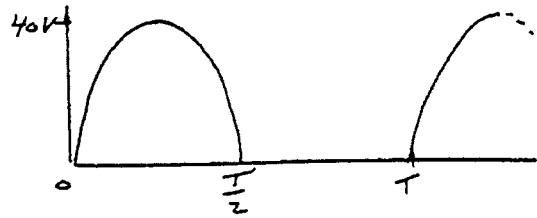

$$v_o(\text{avg}) = \frac{1}{T_o} \int_{t_o} v_o(t) dt = \frac{1}{2\pi} \int_0^\pi 40 \sin x dx$$

$$= \frac{40}{2\pi} [-\cos x]_0^\pi = \frac{40}{2\pi} [ -(-1 - 1) ] = \frac{40}{\pi}$$

or

$v_o(\text{avg}) = 12.7 \text{ V}$

(d) 50%

2.4

$v_o = v_s - 2V_T \Rightarrow v_s(\text{max}) = v_o(\text{max}) + 2V_T$

a. For  $v_o(\text{max}) = 25 \text{ V} \Rightarrow v_s(\text{max}) = 25 + 2(0.7)$   
 $= 26.4 \text{ V}$

$\frac{N_1}{N_2} = \frac{160}{26.4} \Rightarrow \frac{N_1}{N_2} = 6.06$

b. For  $v_o(\text{max}) = 100 \text{ V} \Rightarrow v_s(\text{max}) = 101.4 \text{ V}$

$\frac{N_1}{N_2} = \frac{160}{101.4} \Rightarrow \frac{N_1}{N_2} = 1.58$

From part (a)

$PIV = v_s(\text{max}) - V_T = 2(26.4) - 0.7$

or

$PIV = 52.1 \text{ V}$

$v_s(\text{max}) - V_T = PIV$

or, from part (b)

$PIV = 2(101.4) - 0.7$

or

$PIV = 202.1 \text{ V}$

Full Bridge

26.4

101.5

2.5

a.  $v_o(\max) = 24 \text{ V} \Rightarrow v_s(\max) = 24 + 2(0.7)$

$v_s(\max) = 25.4 \text{ V}$

$v_s(\text{rms}) = \frac{25.4}{\sqrt{2}} \Rightarrow v_s(\text{rms}) = 17.96 \text{ V}$

b.  $V_r = \frac{V_M}{2fRC} \Rightarrow C = \frac{V_M}{2fV_r R}$

$C = \frac{24}{2(60)(0.5)(150)} \Rightarrow C = 2667 \mu\text{F}$

c.  $i_{D,\max} = \frac{V_m}{R} \left( 1 + 2\pi \sqrt{\frac{V_M}{2V_r}} \right)$

$i_{D,\max} = \frac{24}{150} \left( 1 + 2\pi \sqrt{\frac{24}{2(0.5)}} \right)$

$i_{D,\max} = 5.08 \text{ A}$

2.6

(a)  $v_s(\max) = 24 + 0.7 = 24.7 \text{ V}$

$v_s(\text{rms}) = \frac{v_s(\max)}{\sqrt{2}} \Rightarrow v_s(\text{rms}) = 17.5 \text{ V}$

(b)  $V_r = \frac{V_M}{fRC} \Rightarrow C = \frac{V_M}{fRV_r} = \frac{24}{(60)(150)(0.5)}$


or  $C = 5333 \mu\text{F}$

(c) For the half-wave rectifier



$i_{D,\max} = \frac{V_M}{R} \left( 1 + 4\pi \sqrt{\frac{V_M}{2V_r}} \right) = \frac{24}{150} \left( 1 + 4\pi \sqrt{\frac{24}{2(0.5)}} \right)$

or  $i_{D,\max} = 10.0 \text{ A}$

2.7

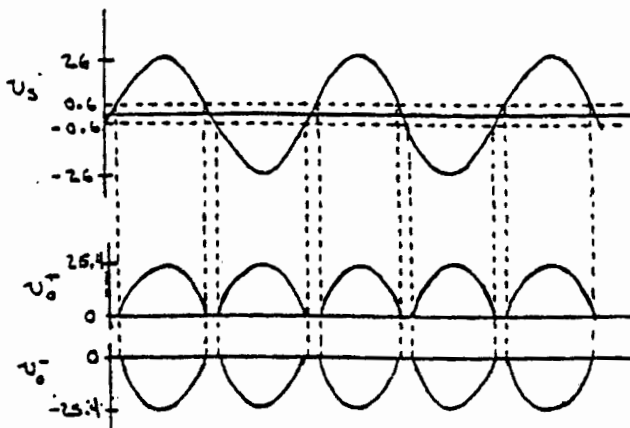

2.8

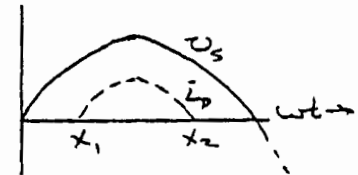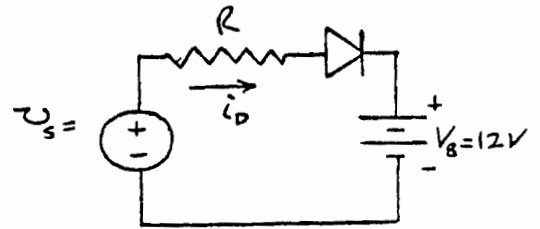

$v_s(t) = 24 \sin \omega t$

Now

$i_D(\text{avg}) = \frac{1}{T} \int_0^T i_D(t) dt$

We have for  $x_1 \leq \omega t \leq x_2$

$i_D = \frac{24 \sin x - 12.7}{R}$

To find  $x_1$  and  $x_2$ ,

$24 \sin x_1 = 12.7$

$x_1 = 0.558 \text{ rad}$

$x_2 = \pi - 0.558 = 2.584 \text{ rad}$

Then

$i_D(\text{avg}) = 2 = \frac{1}{2\pi} \int_{x_1}^{x_2} \left[ \frac{24 \sin x - 12.7}{R} \right] dx$

$= \frac{1}{2\pi} \left( \frac{24}{R} \right) (-\cos x)_{x_1}^{x_2} - \frac{1}{2\pi} \left( \frac{12.7}{R} \right) x_{x_1}^{x_2}$

or

$2 = \frac{6.482}{R} - \frac{4.095}{R} \Rightarrow R = 1.19 \Omega$

Fraction of time diode is conducting

$= \frac{x_2 - x_1}{2\pi} \times 100\% = \frac{2.584 - 0.558}{2\pi} \times 100\%$

or

Fraction = 32.2%

Power rating

$P_{\text{avg}} = R \cdot i_{\text{rms}}^2 = \frac{R}{T} \int_0^T i_D^2 dt = \frac{R}{2\pi} \int_{x_1}^{x_2} \left[ \frac{24 \sin x - 12.7}{R} \right]^2 dx$

$= \frac{1}{2\pi R} \int_{x_1}^{x_2} \left[ (24)^2 \sin^2 x - 2(12.7)(24) \sin x + (12.7)^2 \right] dx$

$= \frac{1}{2\pi R} \left[ (24)^2 \left[ \frac{x}{2} - \frac{\sin 2x}{4} \right]_{x_1}^{x_2} - 2(12.7)(24)(-\cos x)_{x_1}^{x_2} + (12.7)^2 x_{x_1}^{x_2} \right]$

For  $R = 1.19 \Omega$ , then

$P_{\text{avg}} = 17.9 \text{ W}$

2.9

$$R = \frac{15}{0.1} = 150 \Omega$$

$$v_s(\max) = v_o(\max) + V_f = 15 + 0.7$$

or

$$v_s(\max) = 15.7 \text{ V}$$

Then

$$v_s(\text{rms}) = \frac{15.7}{\sqrt{2}} = 11.24 \text{ V}$$

Now

$$\frac{N_1}{N_2} = \frac{120}{11.1} \Rightarrow \frac{N_1}{N_2} = 10.8$$

$$V_f = \frac{V_M}{2fRC} \Rightarrow C = \frac{V_M}{2fRV_f} = \frac{15 \cdot 15.2}{2(60)(150)(0.4)}$$

or

$$C = 2083 \mu\text{F}$$

$$PTV = 2v_s(\max) - V_f = 2(15.7) - 0.7$$

or



$$PTV = 30.7 \text{ V}$$

$$V_c(\text{PK}) = V_{c(\text{avg})} + \frac{V_c}{2}$$

$$V_{c(\text{max})} = 15.2$$

2.10

For  $v_i > 0$

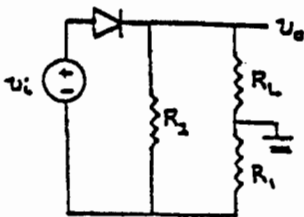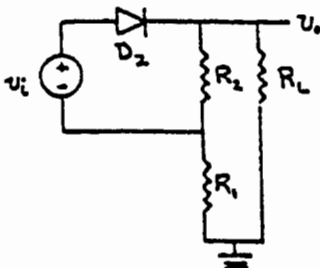

$$V_f = 0$$

Voltage across  $R_L + R_1 = v_i$


$$\text{Voltage Divider} \Rightarrow v_o = \left( \frac{R_L}{R_L + R_1} \right) v_i = \frac{1}{2} v_i$$



2.11

For  $v_i > 0$ , ( $V_f = 0$ )


a.

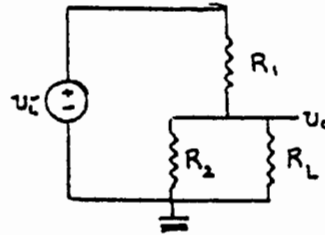

$$v_o = \left( \frac{R_2 \parallel R_L}{R_2 \parallel R_L + R_1} \right) v_i$$


$$R_2 \parallel R_L = 2.2 \parallel 6.8 = 1.66 \text{ k}\Omega$$
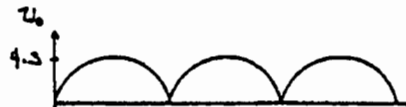
$$v_o = \left( \frac{1.66}{1.66 + 2.2} \right) v_i = 0.43 v_i$$



b.  $v_o(\text{rms}) = \frac{v_o(\max)}{\sqrt{2}} \Rightarrow v_o(\text{rms}) = 3.04 \text{ V}$

2.12

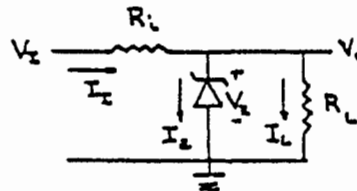

$$V_f = 6.3 \text{ V}, R_1 = 12 \Omega, V_Z = 4.8$$

a.  $I_f = \frac{6.3 - 4.8}{12} \Rightarrow 125 \text{ mA}$

$$I_L = I_f - I_Z = 125 - I_Z$$

$$25 < I_L < 120 \text{ mA} \Rightarrow 40 < R_L < 192 \Omega$$

b.  $P_Z = I_Z V_Z = (100)(4.8) \Rightarrow P_Z = 480 \text{ mW}$   
 $P_L = I_L V_o = (120)(4.8) = P_L = 576 \text{ mW}$

2.13

a.  $I_f = \frac{20 - 10}{222} \Rightarrow I_f = 45.0 \text{ mA}$

$$I_L = \frac{10}{380} \Rightarrow I_L = 26.3 \text{ mA}$$

$$I_Z = I_f - I_L \Rightarrow I_Z = 18.7 \text{ mA}$$

$$b. P_Z(\max) = 400 \text{ mW} \Rightarrow I_Z(\max) = \frac{400}{10} = 40 \text{ mA}$$

$$\Rightarrow I_L(\min) = I_I - I_Z(\max) = 45 - 40$$

$$\Rightarrow I_L(\min) = 5 \text{ mA} = \frac{10}{R_L}$$

$$\Rightarrow R_L = 2 \text{ k}\Omega$$

For  $R_i = 175 \Omega$

$$I_I = 57.1 \text{ mA} \quad I_L = 26.3 \text{ mA} \quad I_Z = 30.8 \text{ mA}$$

$$I_Z(\max) = 40 \text{ mA} \Rightarrow I_L(\min) = 57.1 - 40 = 17.1 \text{ mA}$$

$$R_L = \frac{10}{17.1} \Rightarrow R_L = 585 \Omega$$

2.14

a. From Eq. (2-23)

$$I_Z(\max) = \frac{500[20 - 10] - 50[15 - 10]}{15 - (0.9)(10) - (0.1)(20)}$$

$$= \frac{5000 - 250}{4}$$

$$I_Z(\max) = 1.1875 \text{ A}$$

$$I_Z(\min) = 0.11875 \text{ A}$$

From Eq. (2-21(b))

$$R_i = \frac{20 - 10}{1187.5 + 50} \Rightarrow R_i = 8.08 \Omega$$

$$b. P_Z = (1.1875)(10) \Rightarrow P_Z = 11.9 \text{ W}$$

$$P_L = I_L(\max)V_0 = (0.5)(10) \Rightarrow P_L = 5 \text{ W}$$

2.15

(a) As approximation, assume  $I_Z(\max)$  and  $I_Z(\min)$  are the same as in problem 2-14.

$$V_0(\max) = V_0(\text{nom}) + I_Z(\max)r_Z$$

$$= 20 + (0.453)(2) = 20.906$$

$$V_0(\min) = V_0(\text{nom}) + I_Z(\min)r_Z$$

$$= 20 + (0.0453)(2) = 20.0906$$

$$b. \% \text{ Reg} = \frac{20.906 - 20.0906}{20} \times 100\%$$

$$\Rightarrow \% \text{ Reg} = 4.08\%$$

2.16

$$\% \text{ Reg} = \frac{V_L(\max) - V_L(\min)}{V_L(\text{nom})} \times 100\%$$

$$= \frac{V_L(\text{nom}) + I_Z(\max)r_z - (V_L(\text{nom}) + I_Z(\min)r_z)}{V_L(\text{nom})}$$

$$= \frac{[I_Z(\max) - I_Z(\min)](3)}{6} = 0.05$$

So

$$I_Z(\max) - I_Z(\min) = 0.1 \text{ A}$$

Now

$$I_L(\max) = \frac{6}{500} = 0.012 \text{ A}, \quad I_L(\min) = \frac{6}{1000} = 0.006 \text{ A}$$

Now

$$R_i = \frac{V_{PS}(\min) - V_Z}{I_Z(\min) + I_L(\max)}$$

or

$$280 = \frac{15 - 6}{I_Z(\min) + 0.012} \Rightarrow I_Z(\min) = 0.020 \text{ A}$$

Then

$$I_Z(\max) = 0.1 + 0.02 = 0.12 \text{ A}$$

and

$$R_i = \frac{V_{PS}(\max) - V_Z}{I_Z(\max) + I_L(\min)}$$

or

$$280 = \frac{V_{PS}(\max) - 6}{0.12 + 0.006} \Rightarrow V_{PS}(\max) = 41.3 \text{ V}$$

2.17

Using Figure 2.17

$$a. V_{PS} = 20 \pm 25\% \Rightarrow 15 \leq V_{PS} \leq 25 \text{ V}$$

For  $V_{PS}(\min)$ :

$$I_I = I_Z(\min) + I_L(\max) = 5 + 20 = 25 \text{ mA}$$

$$R_i = \frac{V_{PS}(\min) - V_Z}{I_I} = \frac{15 - 10}{25} \Rightarrow R_i = 200 \Omega$$

b. For  $V_{PS}(\max)$

$$\Rightarrow I_I(\max) = \frac{25 - 10}{R_i} \Rightarrow I_I(\max) = 75 \text{ mA}$$

$$\text{For } I_L(\min) = 0 \Rightarrow I_Z(\max) = 75 \text{ mA}$$

$$V_{Z0} = V_Z - I_Z r_Z = 10 - (0.025)(5) = 9.875 \text{ V}$$

$$V_0(\max) = 9.875 + (0.075)(5) = 10.25$$

$$V_0(\min) = 9.875 + (0.005)(5) = 9.90$$

$$\Delta V_0 = 0.35 \text{ V}$$

$$c. \% \text{ Reg} = \frac{\Delta V_0}{V_0(\text{nom})} \times 100\% \Rightarrow \% \text{ Reg} = 3.5\%$$

2.18

From Equation (2.21(a))

$$R_i = \frac{V_{PS}(\min) - V_Z}{I_Z(\min) + I_L(\max)} = \frac{24 - 16}{40 + 400}$$

or

$$R_i = 18.2 \Omega$$

Also

$$V_r = \frac{V_w}{2fRC} \Rightarrow C = \frac{V_w}{2fRV_r}$$

$$R \cong R_i + r_z = 18.2 + 2 = 20.2 \Omega$$

Then

$$22 \quad C = \frac{24}{2(60)(1)(20.2)} \Rightarrow C = 9901 \mu\text{F}$$

2.19

$$V_Z = V_{Z0} + I_Z r_Z \quad V_Z(\text{nom}) = 8 \text{ V}$$

$$8 = V_{Z0} + (0.1)(0.5) \Rightarrow V_{Z0} = 7.95 \text{ V}$$

$$I_i = \frac{V_S(\text{max}) - V_Z(\text{nom})}{R_s} = \frac{12 - 8}{3} = 1.333 \text{ A}$$

For  $I_L = 0.2 \text{ A} \Rightarrow I_Z = 1.133 \text{ A}$

For  $I_L = 1 \text{ A} \Rightarrow I_Z = 0.333 \text{ A}$

$$V_L(\text{max}) = V_{Z0} + I_Z(\text{max})r_Z$$

$$= 7.95 + (1.133)(0.5) = 8.5165$$

$$V_L(\text{min}) = V_{Z0} + I_Z(\text{min})r_Z$$

$$= 7.95 + (0.333)(0.5) = 8.1165$$

$$\Delta V_L = 0.4 \text{ V}$$

$$\% \text{ Reg} = \frac{\Delta V_L}{V_0(\text{nom})} = \frac{0.4}{8} \Rightarrow \% \text{ Reg} = 5.0\%$$

$$V_r = \frac{V_M}{2\sqrt{RC}} \Rightarrow C = \frac{V_M}{2\sqrt{RV_r}}$$

$$R = R_f + r_f = 3 + 0.5 = 3.5 \Omega$$

Then

$$C = \frac{8}{2(60)(3.5)(0.8)} \Rightarrow C = 0.0238 \text{ F}$$

2.20

(a) For  $-10 \leq v_i \leq 0$ , both diodes are conducting  $\Rightarrow v_o = 0$

For  $0 \leq v_i \leq 3$ , Zener not in breakdown, so


$$i_1 = 0, \quad v_o = 0$$

For  $v_i > 3$

$$i_1 = \frac{v_i - 3}{20} \text{ mA}$$

$$v_o = \left(\frac{v_i - 3}{20}\right)(10) = \frac{1}{2}v_i - 1.5$$

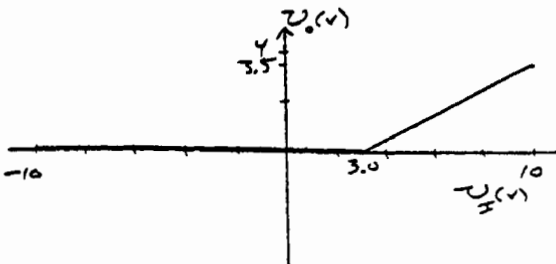
At  $v_i = 10 \text{ V}$ ,  $v_o = 3.5 \text{ V}$ ,  $i_1 = 0.35 \text{ mA}$



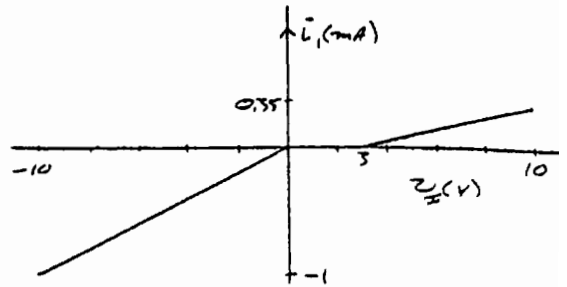
(b) For  $v_i < 0$ , both diodes forward biased

$$-i_1 = \frac{0 - v_i}{10}. \quad \text{At } v_i = -10 \text{ V}, i_1 = -1 \text{ mA}$$

For  $v_i > 3$ ,  $i_1 = \frac{v_i - 3}{20}$ . At  $v_i = 10 \text{ V}$ ,  $i_1 = 0.35 \text{ mA}$



2.21

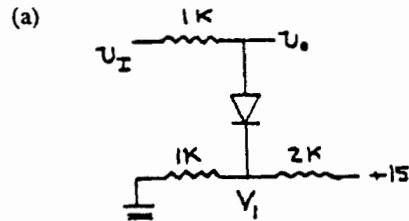

$$V_1 = \frac{1}{3} \times 15 = 5 \text{ V} \Rightarrow \text{for } v_i \leq 5.7, v_o = v_i$$

$$\frac{v_i - (V_1 + 0.7)}{1} + \frac{15 - V_1}{2} = \frac{V_1}{1}, \quad v_o = V_1 + 0.7$$


$$\frac{v_i - v_o}{1} + \frac{15 - (v_o - 0.7)}{2} = \frac{v_o - 0.7}{1}$$

$$\frac{v_i}{1} + \frac{15.7}{2} + \frac{0.7}{1} = v_o \left(\frac{1}{1} + \frac{1}{2} + \frac{1}{1}\right) = v_o(2.5)$$

$$v_i + 8.55 = v_o(2.5) \Rightarrow v_o = \frac{1}{2.5}v_i + 3.42$$

$$v_i = 5.7 \Rightarrow v_o = 5.7$$

$$v_i = 15 \Rightarrow v_o = 9.42$$

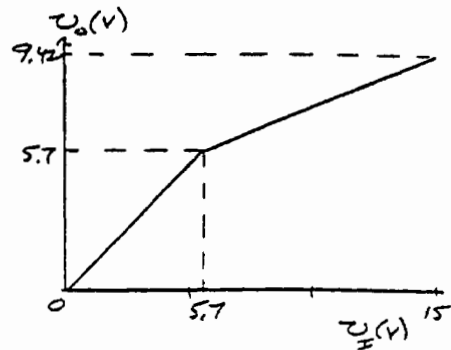


(b)  $i_D = 0$  for  $0 \leq v_i \leq 5.7$

Then

$$i_D = \frac{v_i - v_o}{1} = \frac{v_i - \left(\frac{v_i}{2.5} + 3.42\right)}{1}$$


or
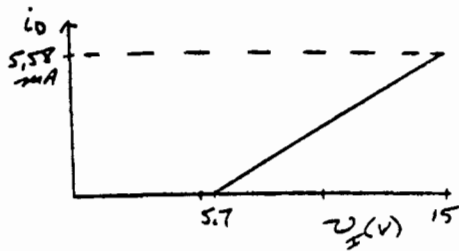
$$i_D = \frac{0.6v_i - 3.42}{1} \quad \text{For } v_i = 15, \quad i_D = 5.58 \text{ mA}$$




2.22

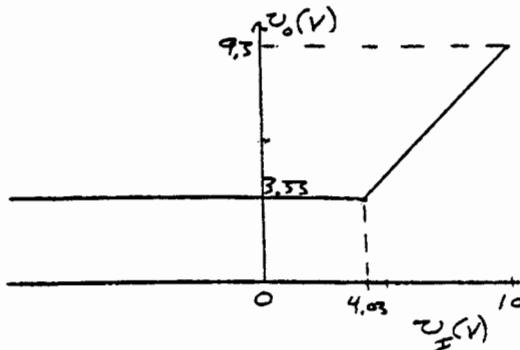
(a) For D off,  $v_o = \left(\frac{20}{30}\right)(20) - 10 = 3.33 \text{ V}$   
 Then for  $v_i \leq 3.33 + 0.7 = 4.03 \text{ V} \Rightarrow v_o = 3.33 \text{ V}$   
 For  $v_i > 4.03$ ,  $v_o = v_i - 0.7$ ;  
 For  $v_i = 10$ ,  $v_o = 9.3$



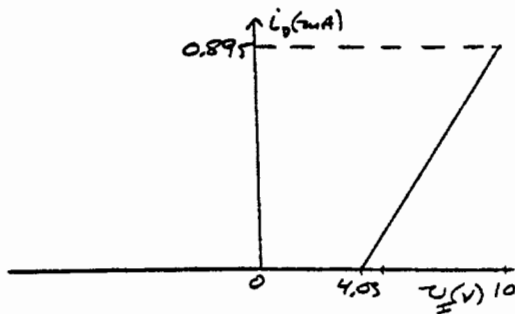(b) For  $v_i \leq 4.03 \text{ V}$ ,  $i_D = 0$   
 For  $v_i > 4.03$ ,  $i_D + \frac{10 - v_o}{10} = \frac{v_o - (-10)}{20}$   
 Which yields  $i_D = \frac{3}{20}v_i - 0.605$   
 For  $v_i = 10$ ,  $i_D = 0.895 \text{ mA}$




2.23

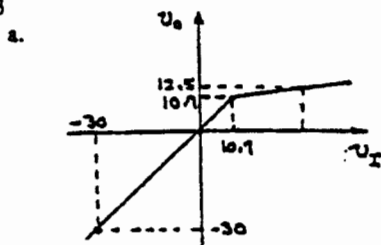


For  $v_i = 30 \text{ V}$ ,  $i = \frac{30 - 10.7}{100 + 10} = 0.175 \text{ A}$   
 $v_o = i(10) + 10.7 = 12.5 \text{ V}$


b.

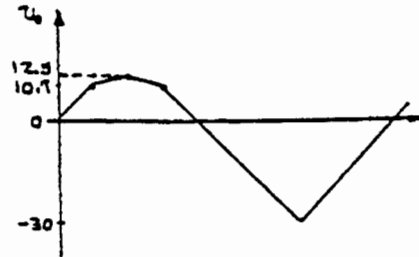

2.24

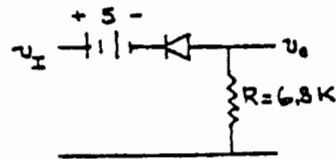


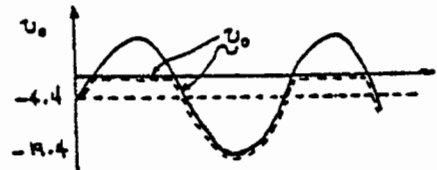$V_T = 0.6 \text{ V}$   
 $v_i = 15 \sin \omega t$




2.25


a.  $V_T = 0$

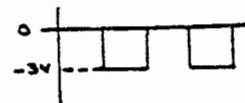


$V_T = 0.6$

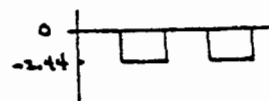

b.  $V_T = 0$

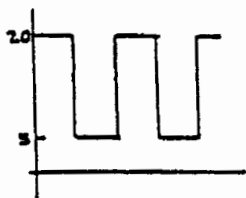


$V_T = 0.6$

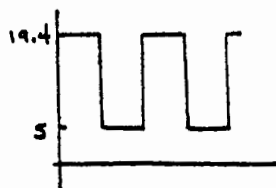

2.26

One possible example is shown.

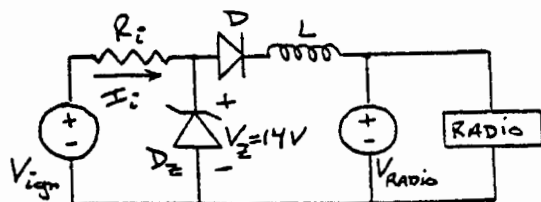


$L$  will tend to block the transient signals  
 $D_2$  will limit the voltage to  $+14\text{ V}$  and  $-0.7\text{ V}$ .  
 Power ratings depends on number of pulses per second and duration of pulse.


2.27

$V_T = 0$


a.

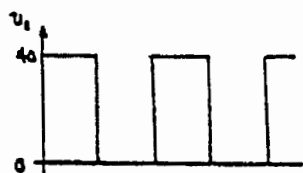

b.

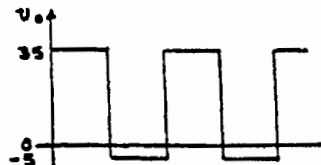


2.28

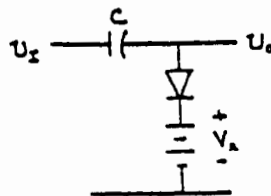

- a. For  $V_T = 0 \Rightarrow V_z = 2.7\text{ V}$
- b. For  $V_T = 0.7\text{ V} \Rightarrow V_z = 2.0\text{ V}$


2.29

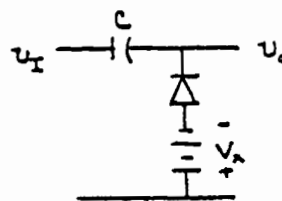

For  $V_T = 0$ ;  $V_z = 10\text{ V}$

2.30

For circuit in Figure P2.27(a)

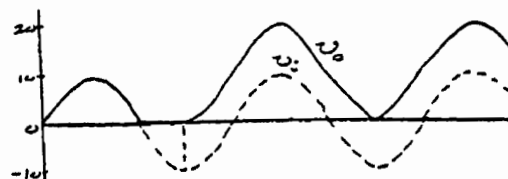


For circuit in Figure P2.27(b)

(i) For  $V_Z = +3\text{ V}$




(ii) For  $V_Z = -3\text{ V}$

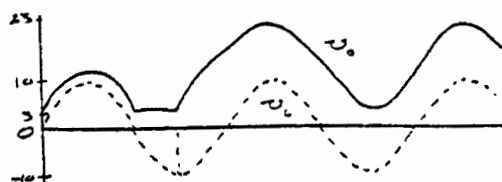

2.31

For Figure P2.27(a)

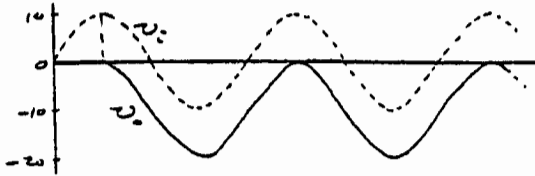

2.32

a.  $I_{D1} = \frac{10 - 0.6}{9.5 + 0.5} \Rightarrow I_{D1} = 0.94 \text{ mA}$   $I_{D2} = 0$

$V_0 = I_{D1}(9.5) \Rightarrow V_0 = 8.93 \text{ V}$

b.  $I_{D1} = \frac{5 - 0.6}{9.5 + 0.5} \Rightarrow I_{D1} = 0.44 \text{ mA}$   $I_{D2} = 0$

$V_0 = I_{D1}(9.5) \Rightarrow V_0 = 4.18 \text{ V}$

c. Same as (a)

d.  $10 = \frac{I}{2}(0.5) + 0.6 + I(9.5) \Rightarrow I = 0.964 \text{ mA}$

$V_0 = I(9.5) \Rightarrow V_0 = 9.16 \text{ V}$

$I_{D1} = I_{D2} = \frac{I}{2} \Rightarrow I_{D1} = I_{D2} = 0.482 \text{ mA}$

2.33

a.  $I = I_{D1} = I_{D2} = 0$   $V_0 = 10$

b.  $10 = I(9.5) + 0.6 + I(0.5) \Rightarrow$

$I = I_{D2} = 0.94 \text{ mA}$   $I_{D1} = 0$

$V_0 = 10 - I(9.5) \Rightarrow V_0 = 1.07 \text{ V}$

c.  $10 = I(9.5) + 0.6 + I(0.5) + 5 \Rightarrow$

$I = I_{D2} = 0.44 \text{ mA}$   $I_{D1} = 0$

$V_0 = 10 - I(9.5) \Rightarrow V_0 = 5.82 \text{ V}$

d.  $10 = I(9.5) + 0.6 + \frac{I}{2}(0.5) \Rightarrow I = 0.964 \text{ mA}$

$I_{D1} = I_{D2} = \frac{I}{2} \Rightarrow I_{D1} = I_{D2} = 0.482 \text{ mA}$

$V_0 = 10 - I(9.5) \Rightarrow V_0 = 0.842 \text{ V}$

2.34

a.  $V_1 = V_2 = 0 \Rightarrow D_1, D_2, D_3$  on  $V_0 = 4.4 \text{ V}$

$I = \frac{10 - 4.4}{9.5} \Rightarrow I = 0.589 \text{ mA}$

$I_{D1} = I_{D2} = \frac{4.4 - 0.6}{0.5} \Rightarrow I_{D1} = I_{D2} = 7.6 \text{ mA}$

$I_{D3} = I_{D1} + I_{D2} - I = 2(7.6) - 0.589 \Rightarrow$

$I_{D3} = 14.6 \text{ mA}$

b.  $V_1 = V_2 = 5 \text{ V}$   $D_1$  and  $D_2$  on,  $D_3$  off

$10 = I(9.5) + 0.6 + \frac{I}{2}(0.5) + 5 \Rightarrow I = 0.451 \text{ mA}$

$I_{D1} = I_{D2} = \frac{I}{2} \Rightarrow I_{D1} = I_{D2} = 0.226 \text{ mA}$

$I_{D3} = 0$

$V_0 = 10 - I(9.5) = 10 - (0.451)(9.5) \Rightarrow$

$V_0 = 5.72 \text{ V}$

c.  $V_1 = 5 \text{ V}$ ,  $V_2 = 0$   $D_1$  off,  $D_2, D_3$  on

$V_0 = 4.4 \text{ V}$

$I = \frac{10 - 4.4}{9.5} \Rightarrow I = 0.589 \text{ mA}$

$I_{D2} = \frac{4.4 - 0.6}{0.5} \Rightarrow I_{D2} = 7.6 \text{ mA}$

$I_{D1} = 0$

$I_{D3} = I_{D2} - I = 7.6 - 0.589 \Rightarrow I_{D3} = 7.01 \text{ mA}$

d.  $V_1 = 5 \text{ V}$ ,  $V_2 = 2 \text{ V}$   $D_1$  off,  $D_2, D_3$  on

$V_0 = 4.4 \text{ V}$

$I = \frac{10 - 4.4}{9.5} \Rightarrow I = 0.589 \text{ mA}$

$I_{D2} = \frac{4.4 - 0.6 - 2}{0.5} \Rightarrow I_{D2} = 3.6 \text{ mA}$

$I_{D1} = 0$

$I_{D3} = I_{D2} - I = 3.6 - 0.589 \Rightarrow I_{D3} = 3.01 \text{ mA}$

2.35

(a)  $D_1$  on,  $D_2$  off,  $D_3$  on

So  $I_{D2} = 0$

Now  $V_2 = -0.6 \text{ V}$ ,  $I_{D1} = \frac{10 - 0.6 - (-0.6)}{R_1 + R_2} = \frac{10}{2 + 6} \Rightarrow$

$I_{D1} = 1.25 \text{ mA}$

$V_1 = 10 - 0.6 - (1.25)(2) \Rightarrow V_1 = 6.9 \text{ V}$

$I_{R3} = \frac{-0.6 - (-5)}{2} = 2.2 \text{ mA}$

$I_{D3} = I_{R3} - I_{D1} = 2.2 - 1.25 \Rightarrow I_{D3} = 0.95 \text{ mA}$

(b)  $D_1$  on,  $D_2$  on,  $D_3$  off

So  $I_{D3} = 0$

$V_1 = 4.4 \text{ V}$ ,  $I_{D1} = \frac{10 - 0.6 - 4.4}{R_1} = \frac{5}{6}$

or

$I_{D1} = 0.833 \text{ mA}$

$I_{R2} = \frac{4.4 - (-5)}{R_2 + R_3} = \frac{9.4}{10} = 0.94 \text{ mA}$

$I_{D2} = I_{R2} - I_{D1} = 0.94 - 0.833 \Rightarrow I_{D2} = 0.107 \text{ mA}$

$V_2 = I_{R2}R_3 - 5 = (0.94)(5) - 5 \Rightarrow V_2 = -0.3 \text{ V}$


(c) All diodes are on  
 $V_1 = 4.4\text{ V}$ ,  $V_2 = -0.6\text{ V}$

$$I_{D1} = 0.5\text{ mA} = \frac{10 - 0.6 - 4.4}{R_1} \Rightarrow R_1 = 10\text{ k}\Omega$$

$$I_{R2} = 0.5 + 0.5 = 1\text{ mA} = \frac{4.4 - (-0.6)}{R_2} \Rightarrow$$

$$R_2 = 5\text{ k}\Omega$$
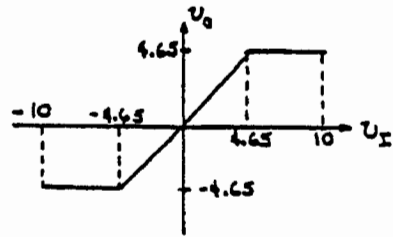
$$I_{R3} = 1.5\text{ mA} = \frac{-0.6 - (-5)}{R_3} \Rightarrow R_3 = 2.93\text{ k}\Omega$$



$$v_o = v_i \text{ for } -4.65 \leq v_i \leq 4.65$$

2.36

For  $v_i$  small, both diodes off

$$v_o = \left( \frac{0.5}{0.5+5} \right) v_i = 0.0909v_i$$

When  $v_i - v_o = 0.6$ ,  $D_1$  turns on. So we have  
 $v_i - 0.0909v_i = 0.6 \Rightarrow v_i = 0.66$ ,  $v_o = 0.06$

For  $D_1$  on

$$\frac{v_i - 0.6 - v_o}{5} + \frac{v_i - v_o}{5} = \frac{v_o}{0.5} \text{ which yields}$$

$$v_o = \frac{2v_i - 0.6}{12}$$

When  $v_o = 0.6$ ,  $D_2$  turns on. Then

$$0.6 = \frac{2v_i - 0.6}{12} \Rightarrow v_i = 3.9\text{ V}$$


Now for  $v_i > 3.9$

$$\frac{v_i - 0.6 - v_o}{5} + \frac{v_i - v_o}{5} = \frac{v_o}{0.5} + \frac{v_o - 0.6}{0.5}$$

Which yields

$$v_o = \frac{2v_i + 5.4}{22}; \text{ For } v_i = 10 \Rightarrow v_o = 1.15\text{ V}$$

2.37

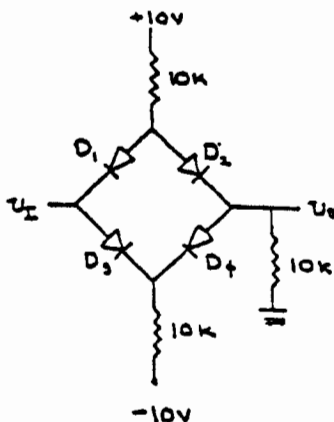


For  $v_i > 0$ , when  $D_1$  turns off

$$I = \frac{10 - 0.7}{20} = 0.465\text{ mA}$$

$$v_o = I(10\text{ k}\Omega) = 4.65\text{ V}$$

2.38

a.

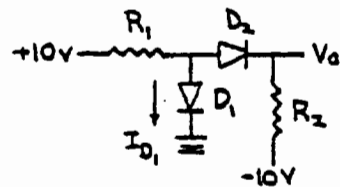

$$R_1 = 5\text{ k}\Omega, R_2 = 10\text{ k}\Omega$$

$$D_1 \text{ and } D_2 \text{ on} \Rightarrow V_o = 0$$

$$I_{D1} = \frac{10 - 0.7}{5} - \frac{0 - (-10)}{10} = 1.86 - 1.0$$

$$I_{D1} = 0.86\text{ mA}$$

b.  $R_1 = 10\text{ k}\Omega$ ,  $R_2 = 5\text{ k}\Omega$ ,  $D_1$  off,  $D_2$  on

$$I_{D1} = 0$$

$$I = \frac{10 - 0.7 - (-10)}{15} = 1.287$$

$$V_o = IR_2 - 10 \Rightarrow V_o = -3.57\text{ V}$$

2.39


$$\frac{15 - (V_o + 0.7)}{10} = \frac{V_o + 0.7}{20} + \frac{V_o}{20}$$

$$\frac{15}{10} - \frac{0.7}{10} - \frac{0.7}{20} = V_o \left( \frac{1}{10} + \frac{1}{20} + \frac{1}{20} \right) = V_o \left( \frac{4.0}{20} \right)$$

$$V_o = 6.975\text{ V}$$

$$I_D = \frac{V_o}{20} \Rightarrow I_D = 0.349\text{ mA}$$

2.40

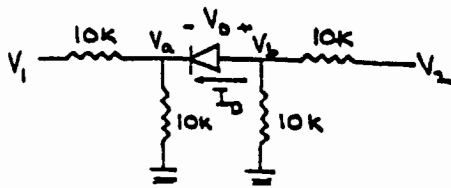

a.  $V_1 = 15 \text{ V}, V_2 = 10 \text{ V}$  Diode off

$$V_a = 7.5 \text{ V}, V_b = 5 \text{ V} \Rightarrow V_D = -2.5 \text{ V}$$

$$I_D = 0$$

b.  $V_1 = 10 \text{ V}, V_2 = 15 \text{ V}$  Diode on

$$\frac{V_2 - V_b}{10} = \frac{V_b}{10} + \frac{V_a - V_1}{10} \Rightarrow V_a = V_b - 0.6$$

$$\frac{15}{10} + \frac{10}{10} = V_b \left( \frac{1}{10} + \frac{1}{10} \right) + V_b \left( \frac{1}{10} + \frac{1}{10} \right) - 0.6 \left( \frac{1}{10} + \frac{1}{10} \right)$$

$$2.62 = V_b \left( \frac{4}{10} \right) \Rightarrow V_b = 6.55 \text{ V}$$

$$I_D = \frac{15 - 6.55}{10} - \frac{6.55}{10} \Rightarrow I_D = 0.19 \text{ mA}$$

$$V_D = 0.6 \text{ V}$$

2.41

$v_I = 0, D_1$  off,  $D_2$  on

$$I = \frac{10 - 2.5}{15} = 0.5 \text{ mA}$$

$$v_O = 10 - (0.5)(5) \Rightarrow v_O = 7.5 \text{ V for } 0 < v_I < 7.5$$


For  $v_I = 30 \text{ V}, D_2$  off,  $v_O = 10 \text{ V}$

Determine  $v_I$  when  $V_z = 10$

$$I = \frac{v_I - 2.5}{25}$$

$$V_z = 10 = I(10) + 2.5 \Rightarrow I = 0.75 \text{ mA}$$

$$v_I = (0.75)(25) + 2.5 = 21.25$$

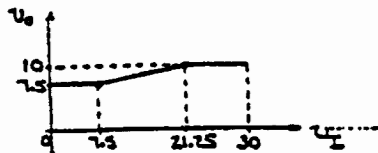

2.42

a.  $V_{O1} = V_{O2} = 0$

b.  $V_{O1} = 4.4 \text{ V}, V_{O2} = 3.8 \text{ V}$

c.  $V_{O1} = 4.4 \text{ V}, V_{O2} = 3.8 \text{ V}$

Logic "1" level degrades as it goes through additional logic gates.

2.43

a.  $V_{O1} = V_{O2} = 5 \text{ V}$

b.  $V_{O1} = 0.6 \text{ V}, V_{O2} = 1.2 \text{ V}$

c.  $V_{O1} = 0.6 \text{ V}, V_{O2} = 1.2 \text{ V}$

Logic "0" signal degrades as it goes through additional logic gates.

2.44

$$(V_1 \text{ AND } V_2) \text{ OR } (V_1 \text{ AND } V_4)$$

2.45

$$I = \frac{10 - 1.5 - 0.2}{R + 10} = 12 \text{ mA} = 0.012$$

$$R + 10 = \frac{8.3}{0.012} = 691.7 \Omega$$


$$R = 681.7 \Omega$$

2.46

$$I = \frac{10 - 1.7 - V_I}{0.75} = 8$$

$$V_I = 10 - 1.7 - 8(0.75) \Rightarrow V_I = 2.3 \text{ V}$$

2.47

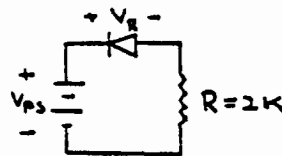

$$V_R = 1 \text{ V}, I = 0.8 \text{ mA}$$

$$V_{PS} = 1 + (0.8)(2)$$

$$V_{PS} = 2.6 \text{ V}$$

2.48

$$I_{ph} = \eta e \Phi A$$

$$0.6 \times 10^{-3} = (1)(1.6 \times 10^{-19})(10^{17}) A$$

$$A = 3.75 \times 10^{-2} \text{ cm}^2$$

## Chapter 3

### Exercise Solutions

E3.1

$$\beta = \frac{\alpha}{1 - \alpha}$$

$$\text{For } \alpha = 0.980, \beta = \frac{0.980}{1 - 0.980} = 49$$

$$\text{For } \alpha = 0.995, \beta = \frac{0.995}{1 - 0.995} = 199$$

$$\underline{49 \leq \beta \leq 199}$$

E3.2

$$\alpha = \frac{\beta}{1 + \beta} = \frac{75}{76} = \underline{0.9868}$$

$$\alpha = \frac{125}{126} = \underline{0.9921}$$

E3.3

$$I_E = (1 + \beta)I_B$$

$$\text{So } (1 + \beta) = \frac{I_E}{I_B} = \frac{0.780}{0.00960} = 81.25 \Rightarrow \underline{\beta = 80.3}$$

$$\alpha = \frac{\beta}{1 + \beta} = \frac{80.3}{81.3} \Rightarrow \underline{\alpha = 0.9877}$$

$$I_C = \beta I_B = (80.3)(9.60 \mu\text{A}) \Rightarrow \underline{I_C = 0.771 \text{ mA}}$$

E3.4

$$\beta = \frac{\alpha}{1 - \alpha} = \frac{0.990}{1 - 0.990} \Rightarrow \underline{\beta = 99}$$

$$I_B = \frac{I_E}{(1 + \beta)} = \frac{2.150}{100} \Rightarrow \underline{I_B = 21.50 \mu\text{A}}$$

$$I_C = \alpha I_E = (0.990)(2.150) \Rightarrow \underline{I_C = 2.13 \text{ mA}}$$

E3.5

$$r_o = \frac{V_A}{I_C} = \frac{150}{I_C}$$

$$I_C = 0.1 \text{ mA} \Rightarrow r_o = 1.5 \text{ M}\Omega$$

$$I_C = 1.0 \text{ mA} \Rightarrow r_o = 150 \text{ k}\Omega$$

$$I_C = 10 \text{ mA} \Rightarrow r_o = 15 \text{ k}\Omega$$

E3.6

$$I_C = I_0 \left(1 + \frac{V_{CE}}{V_A}\right)$$

$$\text{At } V_{CE} = 1, I_C = 1$$

$$\text{a. } V_A = 75$$

$$I_C = 1 = I_0 \left(1 + \frac{1}{75}\right) \Rightarrow I_0 = 0.9868 \text{ mA}$$

$$\text{At } V_{CE} = 10, I_C = (0.9868) \left(1 + \frac{10}{75}\right) \Rightarrow$$

$$\underline{I_C = 1.12 \text{ mA}}$$

$$\text{b. } V_A = 150$$

$$I_C = 1 = I_0 \left(1 + \frac{1}{150}\right) \Rightarrow I_0 = 0.9934 \text{ mA}$$

$$\text{At } V_{CE} = 10, I_C = (0.9934) \left(1 + \frac{10}{150}\right) \Rightarrow$$

$$\underline{I_C = 1.06 \text{ mA}}$$

E3.7

$$BV_{CE0} = \frac{BV_{CB0}}{\sqrt{\beta}} = \frac{200}{\sqrt{120}} = 40.5 \text{ volts}$$

E3.8

$$BV_{CE0} = \frac{BV_{CB0}}{\sqrt{\beta}}$$

$$BV_{CB0} = (\sqrt{100})(30) = 139 \text{ V}$$

E3.9

$$\text{a. } V_i = 0.2 < V_{BE(\text{on})} \Rightarrow \underline{I_B = I_C = 0, V_o = 5 \text{ V}}$$

$$P = 0$$

$$\text{b. } V_i = 3.6 \text{ Transistor is driven into saturation.}$$

$$I_B = \frac{3.6 - 0.7}{0.64} \Rightarrow \underline{I_B = 4.53 \text{ mA}}$$

$$I_C = \frac{5 - V_{CE(\text{sat})}}{R_C} = \frac{5 - 0.2}{0.44} \Rightarrow \underline{I_C = 10.9 \text{ mA}}$$

$$\text{Note that } \frac{I_C}{I_B} = \frac{10.9}{4.53} = 2.41 < \beta \text{ which shows}$$

that the transistor is indeed in saturation.

$$P = I_C V_{CE} + I_B V_{BE} = (10.9)(0.2) + (4.53)(0.7) \\ = 2.18 + 3.17$$

$$P = 5.35 \text{ mW}$$

E3.10

$$\text{For } V_{BC} = 0 \Rightarrow V_o = 0.7 \text{ V}$$

$$\text{Then } I_C = \frac{5 - 0.7}{0.44} \Rightarrow I_C = 9.77 \text{ mA}$$

$$\text{and } I_B = \frac{I_C}{\beta} = \frac{9.77}{50} = 0.195 \text{ mA}$$

$$V_i = I_B R_B + V_{BE(\text{on})} = (0.195)(0.64) + 0.7 \\ \Rightarrow V_i = 0.825 \text{ V}$$

$$\text{Power} = I_C V_{CE} + I_B V_{BE}$$

$$= (9.77)(0.7) + (0.195)(0.7)$$

$$\underline{\text{Power} = 6.98 \text{ mW}}$$

E3.11

For  $V_C = 4\text{ V}$  and  $I_{CQ} = 1.5\text{ mA}$

$$R_C = \frac{10 - 4}{1.5} \Rightarrow R_C = 4\text{ k}\Omega$$

$$I_E = \frac{-V_{BE(\text{on})} - (-10)}{R_E}$$

$$I_E = \left(\frac{101}{100}\right) I_C = 1.515\text{ mA}$$

$$R_E = \frac{10 - 0.70}{1.515} \Rightarrow R_E = 6.14\text{ k}\Omega$$

$$I_C = \beta I_B = (75)(15.1\text{ }\mu\text{A}) \Rightarrow I_C = 1.13\text{ mA}$$

$$I_E = (1 + \beta) I_B = (76)(15.1\text{ }\mu\text{A}) \Rightarrow I_E = 1.15\text{ mA}$$

$$V_{CE} = V_{CC} + V_{BB} - I_C R_C - I_E R_E$$

$$= 8 + 2 - (1.13)(2.5) - (1.15)(1)$$

$$\underline{V_{CE} = 6.03\text{ V}}$$

E3.12

$$I_C = \frac{10 - V_C}{R_C} = \frac{10 - 6.34}{4} \Rightarrow I_C = 0.915\text{ mA}$$

$$I_E = \frac{-V_{BE(\text{on})} - (-10)}{R_E} = \frac{10 - 0.7}{10} \Rightarrow$$

$$\underline{I_E = 0.930\text{ mA}}$$

$$I_C = \alpha I_E \Rightarrow \alpha = \frac{I_C}{I_E} = \frac{0.915}{0.930} \Rightarrow \underline{\alpha = 0.9839}$$

$$I_B = I_E - I_C = 0.930 - 0.915 \Rightarrow \underline{I_B = 0.0150\text{ mA}}$$

$$\beta = \frac{I_C}{I_B} = \frac{0.915}{0.015} \Rightarrow \underline{\beta = 61}$$

$$V_{CE} = V_C - V_E = 6.34 - (-0.70) \Rightarrow$$

$$\underline{V_{CE} = 7.04\text{ V}}$$

E3.16

$$V_{CE} = 2.5 \Rightarrow V_E = 2.5\text{ V} = I_E R_E$$

$$V_{BB} = I_B R_B + V_{BE(\text{on})} + V_E$$

$$I_B = \frac{V_{BB} - V_{BE(\text{on})} - V_E}{R_B} = \frac{5 - 0.7 - 2.5}{10}$$

$$I_B = 0.18\text{ mA} \Rightarrow I_E = (101)(0.18)$$

$$\Rightarrow I_E = 18.18\text{ mA}$$

$$\text{So } R_E = \frac{2.5}{18.18} \Rightarrow \underline{R_E = 0.138\text{ k}\Omega = 138\text{ }\Omega}$$

E3.17

$$V_{BB} = I_E R_E + V_{EB(\text{on})} + I_B R_B$$

$$I_E = 2.2\text{ mA} \Rightarrow I_B = \frac{2.2}{51} = 0.0431\text{ mA}$$

$$I_C = \left(\frac{\beta}{1 + \beta}\right) I_E = \left(\frac{50}{51}\right)(2.2) \Rightarrow \underline{I_C = 2.16\text{ mA}}$$

$$V_{BB} = (2.2)(1) + 0.7 + (0.0431)(50)$$

$$\Rightarrow \underline{V_{BB} = 5.06\text{ V}}$$

$$V_{EC} = 5 - I_E R_E = 5 - (2.2)(1)$$

$$\Rightarrow \underline{V_{EC} = 2.8\text{ V}}$$

E3.13

$$I_E = \frac{10 - V_{EB(\text{on})}}{R_E} = \frac{10 - 0.7}{8} \Rightarrow \underline{I_E = 1.16\text{ mA}}$$

$$I_B = \frac{I_E}{(1 + \beta)} = \frac{1.16}{51} \Rightarrow \underline{I_B = 2.27\text{ }\mu\text{A}}$$

$$I_C = \frac{\beta}{1 + \beta} I_E = \frac{50}{51}(1.16) \Rightarrow \underline{I_C = 1.14\text{ mA}}$$

$$V_C = I_C R_C - 10 = (1.14)(4) - 10 = -5.44$$

$$V_{EC} = 0.7 - (-5.44) \Rightarrow \underline{V_{EC} = 6.14\text{ V}}$$

E3.18

$$(1) 6 = I_B R_B + V_{BE(\text{on})} + I_E R_E$$

$$(2) 5 = I_C R_C + V_{CE(\text{sat})} + I_E R_E$$

$$I_E = I_B + I_C$$

$$(1) 6 = 10I_B + 0.7 + (I_B + I_C)(1)$$

$$(2) 5 = 4I_C + 0.2 + (I_B + I_C)(1)$$

$$(1) [5.3 = I_C + 11I_B] \times 5 \rightarrow 26.5 = 5I_C + 55I_B$$

$$(2) 4.8 = 5I_C + I_B \quad \underline{4.8 = 5I_C + I_B}$$

$$21.7 = 54I_B$$

$$\Rightarrow \underline{I_B = 0.402\text{ mA}}$$

$$\text{From (1), } I_C = 5.3 - 11I_B \Rightarrow \underline{I_C = 0.880\text{ mA}}$$

$$\underline{I_E = 1.28\text{ mA}, V_{CE} = V_{CE(\text{sat})} = 0.2\text{ V}}$$

E3.14

$$I_E = \frac{V_{BB} - V_{EB(\text{on})}}{R_E}$$

$$\Rightarrow R_E = \frac{4 - 0.7}{1.0} \Rightarrow \underline{R_E = 3.3\text{ k}\Omega}$$

$$I_C = \alpha I_E = (0.9920)(1.0) \Rightarrow \underline{I_C = 0.992\text{ mA}}$$

$$I_B = I_E - I_C = 1.0 - 0.9920 \Rightarrow \underline{I_B = 0.0080\text{ mA}}$$

$$V_{CB} = -V_{BC} = I_C R_C - V_{CC} = (0.992)(1) - 5$$

$$\Rightarrow \underline{V_{BC} = 4.01\text{ V}}$$

E3.15

$$V_{BB} = I_B R_B + V_{BE(\text{on})} + I_E R_E$$

$$= I_B R_B + V_{BE(\text{on})} + (1 + \beta) I_B R_E$$

$$I_B = \frac{V_{BB} - V_{BE}}{R_B + (1 + \beta) R_E} = \frac{2 - 0.7}{10 + (76)(1)}$$

$$\Rightarrow \underline{I_B = 15.1\text{ }\mu\text{A}}$$

E3.19

$$\underline{V_{EC} = V_{EC(\text{sat})} = 0.2\text{ V}}$$

$$I_C = \frac{-0.2 - (-5)}{R_C} = \frac{5 - 0.2}{10} \Rightarrow \underline{I_C = 0.48\text{ mA}}$$

$$I_B = \frac{I_C}{\beta} = \frac{0.48}{2} = 0.24 = I_E$$

$$V_I + I_B R_B + V_{EB(\text{on})} = 0$$

$$30 \Rightarrow V_I = -(0.24)(20) - 0.7 \Rightarrow \underline{V_I = -5.5\text{ V}}$$

E3.20

- a.  $V_I = -4.5 \text{ V} \Rightarrow V_{BE} < V_{BE(\text{on})} \Rightarrow$  Transistor is cutoff.  $I_B = I_C = I_E = 0$ ,  $V_{CE} = 10 \text{ V}$   
 b.  $V_I = -3.5 \text{ V}$  Transistor is active.

$$V_I = I_B R_B + V_{BE(\text{on})} + I_E R_E - 5$$

$$5 - 3.5 = I_B(10) + 0.7 + (76)I_B(4)$$

$$I_B = \frac{5 - 3.5 - 0.7}{10 + (76)(4)} = 0.00255 \text{ mA}$$

$$\Rightarrow I_B = 2.55 \mu\text{A}$$

$$I_C = \beta I_B = (75)(2.55 \mu\text{A}) \Rightarrow I_C = 0.191 \text{ mA}$$

$$I_E = (1 + \beta)I_B = (76)(2.55 \mu\text{A})$$

$$\Rightarrow I_E = 0.194 \text{ mA}$$

$$V_{CE} = 10 - I_C R_C - I_E R_E$$

$$= 10 - (0.191)(2) - (0.194)(4)$$

$$V_{CE} = 8.84 \text{ V}$$

- c.  $V_I = +3.5 \text{ V}$  Transistor is in saturation.

$$(1) 3.5 = I_B R_B + V_{BE(\text{on})} + I_E R_E - 5$$

$$(2) 5 = I_C R_C + V_{CE(\text{sat})} + I_E R_E - 5$$

$$(3) I_E = I_B + I_C$$

$$(1) 3.5 + 5 - 0.7 = 10I_B + 4(I_B + I_C)$$

$$(2) 5 + 5 - 0.2 = 2I_C + 4(I_B + I_C)$$

$$(1) 7.8 = 14I_B + 4I_C$$

$$(2) 9.8 = 4I_B + 6I_C$$

$$3 \times (1) \Rightarrow 23.4 = 42I_B + 12I_C$$

$$2 \times (2) \Rightarrow 19.6 = 8I_B + 12I_C$$

$$3.8 = 34I_B$$

$$\Rightarrow I_B = 0.112 \text{ mA}$$

$$7.8 = 14(0.112) + 4I_C = 1.568 + 4I_C$$

$$\Rightarrow I_C = 1.56 \text{ mA}$$

$$\frac{I_C}{I_B} = 13.9 < \beta \Rightarrow \text{In saturation.}$$

$$I_E = I_B + I_C \Rightarrow I_E = 1.67 \text{ mA}$$

$$V_{CE} = V_{CE(\text{sat})} = 0.2$$

E3.21

$$I_C(\text{sat}) = \frac{5 - 1.5 - 0.2}{R} = 15 \Rightarrow R = 0.220 \text{ k}\Omega$$

$$I_B = \frac{I_C}{20} = \frac{15}{20} = 0.75 \text{ mA} = \frac{5 - 0.8}{R_B}$$

or

$$R_B = 5.6 \text{ k}\Omega$$

E3.22

- a.  $V_1 = V_2 = 0$ ,  $I_{B1} = I_{B2} = I_{C1} = I_{C2} = I_R = 0$   
 $V_0 = 5 \text{ V}$

- b.  $V_1 = 5 \text{ V}$ ,  $V_2 = 0$ ,  $I_{B2} = I_{C2} = 0$

$$I_{B1} = \frac{5 - 0.7}{0.95} \Rightarrow I_{B1} = 4.53 \text{ mA}$$

$$I_{C1} = \frac{5 - 0.2}{0.6} \Rightarrow I_{C1} = I_R = 8 \text{ mA}$$

$$V_0 = 0.2 \text{ V}$$

- c.  $V_1 = V_2 = 5 \text{ V}$ ,  $I_{B1} = I_{B2} = 4.53 \text{ mA}$

$$I_R = 8 \text{ mA}, I_{C1} = I_{C2} = 4 \text{ mA}, V_0 = 0.2 \text{ V}$$

E3.23

$$v_o = 5 - i_C R_C = 5 - \beta i_B R_C$$

and

$$i_B = \frac{V_{BB} + \Delta v_I - V_{BE(\text{on})}}{R_B}$$

Then

$$\Delta v_o = \frac{-\beta R_C \Delta v_I}{R_B}$$

or

$$\frac{\Delta v_o}{\Delta v_I} = \frac{-\beta R_C}{R_B}$$

$$\text{Let } \beta = 100, R_C = 5 \text{ k}\Omega, R_B = 100 \text{ k}\Omega$$

Then

$$\frac{\Delta v_o}{\Delta v_I} = \frac{-(100)(5)}{100} = -5$$

Want Q-point to be

$$v_o(Q - pt) = 2.5 = 5 - (100)I_{BQ}(5)$$

Then

$$I_{BQ} = 0.005 \text{ mA}, I_{BQ} = 0.005 = \frac{V_{BB} - 0.7}{100}$$

or

$$V_{BB} = 1.2 \text{ V}$$

$$\text{Also } I_{CQ} = \beta I_{BQ} = (100)(0.005)$$

Or

$$I_{CQ} = 0.5 \text{ mA}$$

E3.24

- a. For  $V_{CEQ} = 2.5 \text{ V} \Rightarrow I_{CQ} = \frac{5 - 2.5}{2}$   
 $\Rightarrow I_{CQ} = 1.25 \text{ mA}$

$$I_{BQ} = \frac{I_{CQ}}{\beta} = \frac{1.25}{100} \Rightarrow I_{BQ} = 12.5 \mu\text{A}$$

$$\text{Then } R_B = \frac{5 - 0.7}{0.0125} \Rightarrow R_B = 344 \text{ k}\Omega$$

- b.  $I_{BQ}$  is independent of  $\beta$ .

$$\text{For } V_{CEQ} = 1 \text{ V}, I_C = \frac{5 - 1}{2} = 2 \text{ mA}$$

$$\beta = \frac{I_C}{I_B} = \frac{2}{0.0125} \Rightarrow \beta = 160$$

For  $V_{CEQ} = 4 \text{ V}$ ,  $I_C = \frac{5-4}{2} = 0.5 \text{ mA}$

$$\beta = \frac{I_C}{I_B} = \frac{0.5}{0.0125} \Rightarrow \beta = 40$$

So  $40 \leq \beta \leq 160$

E3.25

$$I_{BQ} = \frac{5-0.7}{800} \Rightarrow I_{BQ} = 0.005375 \text{ mA}$$

$$\beta = 75 \Rightarrow I_{CQ} = (75)(0.005375) = 0.403 \text{ mA}$$

$$\beta = 150 \Rightarrow I_{CQ} = (150)(0.005375) = 0.806 \text{ mA}$$

Largest  $I_{CQ} \Rightarrow$  Smallest  $V_{CEQ}$

$$\beta = 150 \Rightarrow R_C = \frac{5-1}{0.806} = 4.96 \text{ k}\Omega$$

$$\beta = 75 \Rightarrow R_C = \frac{5-4}{0.403} = 2.48 \text{ k}\Omega$$

For a nominal  $I_C = 0.604 \text{ mA}$  and  $V_{CEQ} = 2.5$

$$R_C = \frac{5-2.5}{0.604} = 4.14 = R_C$$

For  $I_{CQ} = 0.403$ ,

$$V_{CEQ} = 5 - (0.403)(4.14) = 3.33 \text{ V}$$

For  $I_{CQ} = 0.806$ ,

$$V_{CEQ} = 5 - (0.806)(4.14) = 1.66 \text{ V}$$

So for  $R_C = 4.14$ ,  $1.66 \text{ V} \leq V_{CEQ} \leq 3.33 \text{ V}$

E3.26

a.  $R_{TH} = R_1 \parallel R_2 = 9 \parallel 2.25 \Rightarrow R_{TH} = 1.8 \text{ k}\Omega$

$$V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right) V_{CC} = \left( \frac{2.25}{9 + 2.25} \right) (5)$$

$$\Rightarrow V_{TH} = 1.0 \text{ V}$$

b.  $I_{BQ} = \frac{V_{TH} - V_{BE(on)}}{R_{TH} + (1 + \beta)R_E} = \frac{1 - 0.7}{1.8 + (151)(0.2)}$

$$\Rightarrow I_{BQ} = 9.375 \mu\text{A}$$

$$I_{CQ} = \beta I_{BQ} = (150)(9.375 \mu\text{A})$$

$$\Rightarrow I_{CQ} = 1.41 \text{ mA}$$

$$I_{EQ} = (1 + \beta)I_{BQ} \Rightarrow I_{EQ} = 1.42 \text{ mA}$$

$$V_{CEQ} = 5 - I_{CQ}R_C - I_{EQ}R_E$$

$$= 5 - (1.41)(1) - (1.42)(0.2)$$

$$V_{CEQ} = 3.31 \text{ V}$$

c. For  $\beta = 75$

$$I_{BQ} = \frac{1 - 0.7}{1.8 + (76)(0.2)} \Rightarrow I_{BQ} = 17.6 \mu\text{A}$$

$$I_{CQ} = \beta I_{BQ} = (75)(17.6 \mu\text{A})$$

$$\Rightarrow I_{CQ} = 1.32 \text{ mA}$$


$$I_{EQ} = (1 + \beta)I_{BQ} = (76)(17.6 \mu\text{A})$$

$$\Rightarrow I_{EQ} = 1.34 \text{ mA}$$

$$V_{CEQ} = 5 - (1.32)(1) - (1.34)(0.2)$$

$$\Rightarrow V_{CEQ} = 3.41 \text{ V}$$

E3.27

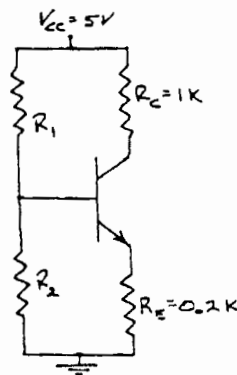

$$R_1 + R_2 = 11.25 \text{ k}\Omega, \beta = 150$$

$$I_C \approx I_E, V_{CEQ} = 2.5 \text{ V}$$

$$\text{So } I_{CQ} \approx I_{EQ} = \frac{5 - 2.5}{1 + 0.2} = 2.081 \text{ mA}$$

$$I_{BQ} = \frac{I_{CQ}}{\beta} = \frac{2.08}{150} = 13.9 \mu\text{A}$$

$$I_{BQ} = \frac{V_{TH} - V_{BE(on)}}{R_{TH} + (1 + \beta)R_E}$$

$$0.0139 = \frac{\left( \frac{R_2}{R_1 + R_2} \right) V_{CC} - V_{BE(on)}}{\frac{R_1 R_2}{R_1 + R_2} + (1 + \beta)R_E}$$

$$= \frac{\left( \frac{R_2}{11.25} \right) (5) - 0.7}{\frac{R_1 R_2}{(11.25)} + (151)(0.2)}$$

$$R_2 = 11.25 - R_1, \text{ so}$$

$$0.0139[R_1(11.25 - R_1) + (151)(0.2)(11.25)]$$

$$= 5R_2 - (0.7)(11.25)$$

$$= 5(11.25 - R_1) - (0.7)(11.25)$$

$$0.156R_1 - 0.0139R_1^2 + 4.72 = 56.25 - 5R_1 - 7.875$$


$$0.0139R_1^2 - 5.156R_1 + 43.66 = 0$$

$$R_1 = \frac{5.156 \pm \sqrt{(5.156)^2 - 4(0.0139)(43.66)}}{2(0.0139)}$$

$$\Rightarrow R_1 = 8.67 \text{ k}\Omega \text{ and } R_2 = 2.58 \text{ k}\Omega$$

E3.28

dc equivalent circuit

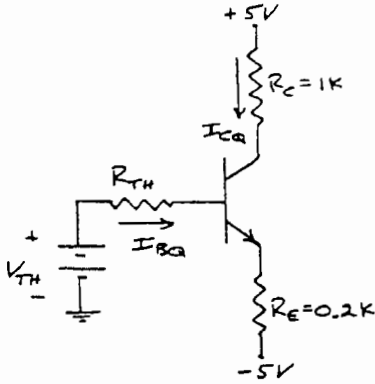

$$\beta = 150, R_{TH} = R_1 \parallel R_2,$$

$$V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right) (10) - 5$$

$$I_{CQ} = \frac{5 - 0}{1} = 5 \text{ mA}$$

$$I_{BQ} = \frac{I_{CQ}}{\beta} = \frac{5}{150} = 0.0333 \text{ mA}$$

$$I_{BQ} = \frac{V_{TH} + 5 - 0.7}{R_{TH} + (1 + \beta)R_E}$$

$$\text{Set } R_{TH} = (0.1)(1 + \beta)R_E$$

$$I_{BQ} = \frac{V_{TH} + 4.3}{(1.1)(1 + \beta)R_E}$$

$$\Rightarrow 0.0333 = \frac{\left( \frac{R_2}{R_1 + R_2} \right) (10) - 5 + 4.3}{(1.1)(151)(0.2)}$$

$$(0.0333)(1.1)(151)(0.2) = \left( \frac{R_2}{R_1 + R_2} \right) (10) - 0.7$$

$$\text{So } \left( \frac{R_2}{R_1 + R_2} \right) = 0.1806$$

$$R_{TH} = \frac{R_1 R_2}{R_1 + R_2} = (0.1)(151)(0.2) = 3.02 \text{ k}\Omega$$

$$\text{Then } R_1(0.1806) = 3.02 \Rightarrow R_1 = 16.7 \text{ k}\Omega$$

$$R_2 = (0.1806)(16.7 + R_2) \Rightarrow 0.8194 R_2 = 3.02$$

$$\Rightarrow R_2 = 3.68 \text{ k}\Omega$$

E3.29

$$\beta = 120, V_{CEQ} = 5 \text{ V}$$

$$R_{TH} = R_1 \parallel R_2, V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right) (10) - 5$$

$$I_{CQ} \approx I_{EQ}$$

$$\text{So } I_{CQ} = \frac{10 - V_{CEQ}}{R_C + R_E}$$

$$I_{CQ} = \frac{10 - 5}{1.2 + 0.3} \Rightarrow I_{CQ} = 3.33 \text{ mA}$$

$$I_{BQ} = \frac{I_{CQ}}{\beta} = \frac{3.33}{120} \Rightarrow I_{BQ} = 0.0278 \text{ mA}$$

$$I_{BQ} = \frac{V_{TH} + 5 - 0.7}{R_{TH} + (1 + \beta)R_E}$$

$$\text{Set } R_{TH} = (0.1)(1 + \beta)R_E$$

$$I_{BQ} = 0.0278 = \frac{\left( \frac{R_2}{R_1 + R_2} \right) (10) - 5 + 5 - 0.7}{(1.1)(121)(0.3)}$$

$$(0.0278)(1.1)(121)(0.3) = \left( \frac{R_2}{R_1 + R_2} \right) (10) - 0.7$$

$$\left( \frac{R_2}{R_1 + R_2} \right) = 0.181$$

$$R_{TH} = \frac{R_1 R_2}{R_1 + R_2} = R_1(0.181) = (0.1)(121)(0.3)$$

$$\Rightarrow R_1 = 20.1 \text{ k}\Omega$$

$$R_2 = (0.181)(20.1 + R_2) \Rightarrow 0.819 R_2 = 3.63 \text{ k}\Omega$$

$$\Rightarrow R_2 = 4.44 \text{ k}\Omega$$

E3.30

$$\text{a. } I_{CQ} = \left( \frac{\beta}{1 + \beta} \right) I_{EQ} = \left( \frac{100}{101} \right) (1) = 0.99 \text{ mA}$$

$$I_{BQ} = \frac{1 \text{ mA}}{1 + \beta} = \frac{1}{101} \Rightarrow 9.90 \mu\text{A}$$

$$V_B = -I_{BQ} R_B = -(0.0099)(50)$$

$$\Rightarrow V_B = -0.495 \text{ V}$$

$$V_{BE} = V_T \ln \left( \frac{I_{CQ}}{I_S} \right) = (0.026) \ln \left( \frac{0.99 \times 10^{-3}}{3 \times 10^{-14}} \right)$$

$$\Rightarrow V_{BE} = 0.630 \text{ V}$$

$$V_E = V_B - V_{BE} = -0.495 - 0.630$$

$$\Rightarrow V_E = -1.13 \text{ V}$$

$$V_C = 10 - (0.99)(5) = 5.05 \text{ V}$$

$$V_{CEQ} = V_C - V_E = 5.05 - (-1.13)$$

$$\Rightarrow V_{CEQ} = 6.18 \text{ V}$$

$$\text{b. } I_{EQ} = 1 \text{ mA}, I_B = \frac{1}{51} = 0.0196 \text{ mA}$$

$$V_B = -(0.0196)(50) = -0.98 \text{ V} = V_B$$

$$I_{CQ} = \left( \frac{50}{51} \right) (1) = 0.98 \text{ mA}$$

$$V_{BE} = (0.026) \ln \left( \frac{0.98 \times 10^{-3}}{3 \times 10^{-14}} \right) = 0.629 \text{ V}$$

$$V_E = -0.98 - 0.629 = -1.61$$

$$V_C = 10 - (0.98)(5) = 5.1 \text{ V}$$

$$V_{CEQ} = 5.1 - (-1.61) \Rightarrow V_{CEQ} = 6.71 \text{ V}$$

E3.31

$$I_B = \frac{I_Q}{1 + \beta} = \frac{I_Q}{121}, V_B = \left(\frac{I_Q}{121}\right)(20) = I_Q(0.165)$$

$$V_E = I_Q(0.165) + 0.7$$

$$I_{CQ} = \left(\frac{\beta}{1 + \beta}\right)I_{EQ} = \left(\frac{120}{121}\right)I_Q = (0.992)I_Q$$

$$V_C = I_{CQ}R_C - 5 = (0.992)I_Q(4) - 5$$

$$= 3.97I_Q - 5$$

$$V_{ECQ} = V_E - V_C$$


$$= [I_Q(0.165) + 0.7] - [3.97I_Q - 5]$$

$$= -3.805I_Q + 5.7$$

$$-3.805I_Q + 5.7 = 3$$

$$\Rightarrow I_Q = 0.710 \text{ mA}$$

E3.32

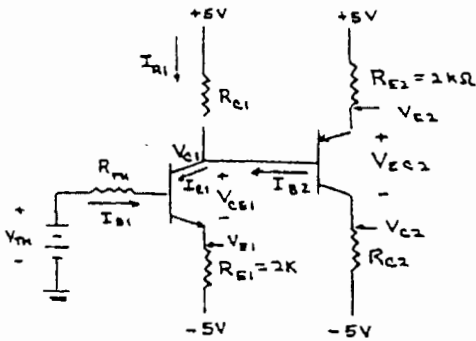

$$R_{TH} = 50 \parallel 100 = 33.3 \text{ k}\Omega$$

$$V_{TH} = \left(\frac{50}{150}\right)(10) - 5 = -1.67 \text{ V}$$

$$I_{B1} = \frac{5 - 1.67 - 0.7}{33.3 + (101)(2)} = \frac{2.63}{235} = 11.2 \mu\text{A}$$

$$I_{C1} = 1.12 \text{ mA}, I_{E1} = 1.13 \text{ mA}$$

$$V_{E1} = I_{E1}R_{E1} - 5 = (1.13)(2) - 5 = -2.74 \text{ V}$$

$$V_{CE1} = 3.25 \text{ V} \Rightarrow V_{C1} = 0.51 \text{ V}$$

$$\Rightarrow V_{E2} = 0.51 + 0.7 = 1.21 \text{ V}$$

$$I_{E2} = \frac{5 - 1.21}{2} = 1.90 \text{ mA} \Rightarrow I_{B2} = 18.8 \mu\text{A}$$

$$I_{C2} = 1.88 \text{ mA}$$

$$I_{R1} = I_{C1} - I_{B2} = 1.12 - 0.0188 = 1.10 \text{ mA}$$


$$R_{C1} = \frac{5 - 0.51}{1.10} \Rightarrow R_{C1} = 4.08 \text{ k}\Omega$$

$$V_{EC1} = 2.5 \Rightarrow V_{C2} = V_{E2} - V_{EC2}$$

$$= 1.21 - 2.5 = -1.29$$

$$R_{C2} = \frac{-1.29 - (-5)}{1.88} \Rightarrow R_{C2} = 1.97 \text{ k}\Omega$$

E3.33

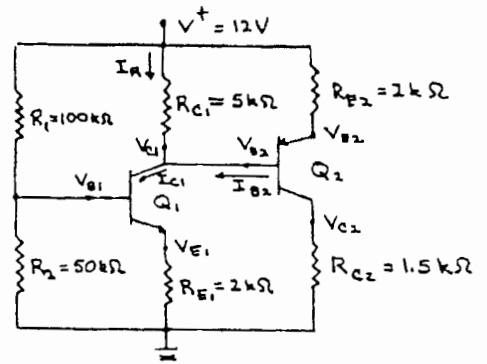

$$I_{B1} = \frac{V_{TH} - V_{BE(ON)}}{R_{TH} + (1 + \beta)R_{E1}} = \frac{4 - 0.7}{33.3 + (101)(2)}$$

$$I_{B1} = 14 \mu\text{A}, I_{C1} = 1.40 \text{ mA}, I_{E1} = 1.42 \text{ mA},$$

$$V_{B1} = 4 - (0.014)(33.3)$$

$$\Rightarrow V_{B1} = 3.53 \text{ V}, V_{E1} = 2.83 \text{ V}$$

$$I_R + I_{B2} = I_{C1}$$

$$\Rightarrow \frac{12 - V_{C1}}{5} + \frac{12 - (V_{C1} + 0.7)}{(101)(2)} = 1.40$$

$$\frac{12}{5} + \frac{(12 - 0.7)}{(101)(2)} - 1.40 = \frac{V_{C1}}{5} + \frac{V_{C1}}{(101)(2)}$$

$$2.4 + 0.0559 - 1.40 = V_{C1}(0.2 + 0.00495)$$

$$V_{C1} = V_{B2} = 5.15 \text{ V}, V_{E2} = 5.85$$

$$I_{E2} = \frac{12 - 5.85}{2} \Rightarrow I_{E2} = 3.08 \text{ mA},$$

$$I_{C2} = 3.04 \text{ mA}, I_{B2} = 30.4 \mu\text{A}$$

$$V_{C2} = (3.04)(1.5) \Rightarrow V_{C2} = 4.56 \text{ V}$$

## Chapter 3

### Problem Solutions

3.1

$$(a) \beta_F = \frac{i_C}{i_B} = \frac{510}{6} \Rightarrow \beta_F = 85$$

$$\alpha_F = \frac{\beta_F}{1 + \beta_F} = \frac{85}{86} \Rightarrow \alpha_F = 0.9884$$

$$i_E = (1 + \beta_F)i_B = (86)(6) \Rightarrow i_E = 516 \mu A$$

$$(b) \beta_F = \frac{2.65}{0.050} \Rightarrow \beta_F = 53$$

$$\alpha_F = \frac{53}{54} \Rightarrow \alpha_F = 0.9815$$

$$i_E = (1 + \beta_F)i_B = (54)(0.050) \Rightarrow i_E = 2.70 mA$$

3.2

(a)

For  $\beta = 110$ :

$$\alpha = \frac{\beta}{1 + \beta} = \frac{110}{111} = 0.99099$$

For  $\beta = 180$ :

$$\alpha = \frac{180}{181} = 0.99448$$

$$0.99099 < \alpha < 0.99448$$

$$(b) I_C = \beta I_B = 110(50 \mu A) \Rightarrow I_C = 5.50 mA$$


or

$$I_C = 180(50 \mu A) \Rightarrow I_C = 9.00 mA$$

so

$$5.50 \leq I_C \leq 9.0 mA$$

3.3

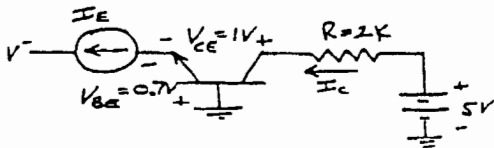

$$5 = I_C R + V_{CE} - V_{BE} = I_C(2) + 1 - 0.7$$

$$\Rightarrow I_C = 2.35 mA$$

$$I_E = \frac{I_C}{\alpha} = \frac{2.35}{0.982} \Rightarrow I_E = 2.39 mA$$

3.4

Same Figure as Problem 3.3

$$v_C = -0.7 + 2 = 1.3 V; i_C = \frac{5 - 1.3}{2} \Rightarrow i_C = 1.85 mA$$

$$\text{For } \beta_F = 120, i_B = \frac{i_C}{\beta_F} = \frac{1.85}{120} \Rightarrow i_B = 15.4 \mu A$$

$$i_E = \left( \frac{1 + \beta_F}{\beta_F} \right) i_C = \left( \frac{121}{120} \right) (1.85) \Rightarrow i_E = 1.865 mA$$

3.5

$$\alpha = \frac{\beta}{1 + \beta} = \frac{60}{61} \Rightarrow \alpha = 0.9836$$

$$I_E = \frac{I_C}{\alpha} = \frac{0.85}{0.9836} \Rightarrow I_E = 0.864 mA$$

$$I_B = \frac{I_C}{\beta} = \frac{0.85}{60} \Rightarrow I_B = 14.2 \mu A$$

3.6

$$i_E = I_S e^{v_{BE}/V_T} = (10^{-13}) e^{0.685/0.026} \Rightarrow i_E = 27.7 mA$$

$$i_C = \left( \frac{90}{91} \right) (27.7) \Rightarrow i_C = 27.4 mA$$

$$i_B = \frac{i_E}{1 + \beta} = \frac{27.7}{91} \Rightarrow i_B = 0.304 mA$$

3.7

$$\text{Device 1: } i_E = I_{S1} e^{v_{BE}/V_T} \Rightarrow 0.5 \times 10^{-3} = I_{S1} e^{0.650/0.026}$$

So that

$$I_{S1} = 6.94 \times 10^{-15} A$$

$$\text{Device 2: } 12.2 \times 10^{-3} = I_{S2} e^{0.650/0.026}$$

Or

$$I_{S2} = 1.69 \times 10^{-13} A$$

$$\text{Ratio of areas} = \frac{I_{S2}}{I_{S1}} = \frac{1.69 \times 10^{-13}}{6.94 \times 10^{-15}} \Rightarrow \text{Ratio} = 24.4$$

3.8

$$(a) r_o = \frac{V_A}{I_C} = \frac{250}{1} \Rightarrow r_o = 250 k\Omega$$

$$(b) r_o = \frac{V_A}{I_C} = \frac{250}{0.1} \Rightarrow r_o = 2.50 M\Omega$$

3.9

$$BV_{CE0} = \frac{BV_{CB0}}{\sqrt[3]{\beta}} = \frac{60}{\sqrt[3]{100}}$$

$$BV_{CE0} = 12.9 V$$

3.10

$$BV_{CE0} = \frac{BV_{CEB0}}{\sqrt[3]{\beta}}$$

$$56 = \frac{220}{\sqrt[3]{\beta}} \Rightarrow \sqrt[3]{\beta} = \frac{220}{56} = 3.93$$

$$\underline{\beta = 60.6}$$

3.11

$$BV_{CE0} = \frac{BV_{CEB0}}{\sqrt[3]{\beta}}$$

$$BV_{CE0} = (BV_{CEB0})\sqrt[3]{\beta} = (50)\sqrt[3]{50}$$

$$\underline{BV_{CE0} = 184 \text{ V}}$$

3.12

$$(a) I_E = \frac{12 - 0.7}{10} \Rightarrow \underline{I_E = 1.13 \text{ mA}}$$

$$I_C = \left(\frac{75}{76}\right)(1.13) = 1.12 \text{ mA}$$

$$V_{CE} = 24 - (1.13)(10) - (1.12)R_C = 6$$

so that

$$\underline{R_C = 5.98 \text{ k}\Omega}$$

$$(b) I_B = \frac{1}{76} = 0.0132 \text{ mA}$$

$$V_B = -I_B R_B = -(0.0132)(50) \Rightarrow \underline{V_B = -0.658 \text{ V}}$$

$$I_C = \left(\frac{75}{76}\right)(1) = 0.987 \text{ mA}$$

$$R_C = \frac{5 - 2}{0.987} \Rightarrow \underline{R_C = 3.04 \text{ k}\Omega}$$

$$c. I_B = \frac{8 - 0.7 - (-2)}{10 + (76)(10)} \Rightarrow I_B = 12.1 \mu\text{A}$$

$$\underline{I_C = 0.906 \text{ mA}}$$

$$V_E = 0.7 + (0.0121)(10) - 2$$

$$V_E = -1.18 \text{ V}$$

$$V_C = I_C R_C - 8 = (0.906)(3) - 8$$

$$\Rightarrow V_C = -5.28 \text{ V}$$

$$V_{EC} = V_E - V_C = -1.18 - (-5.28)$$

$$\Rightarrow \underline{V_{EC} = 4.1 \text{ V}}$$

$$d. 5 = (1 + \beta)I_B(10) + I_B(20) + 0.7 + (1 + \beta)I_B(2)$$

$$5 = I_B[760 + 20 + 152] + 0.7 \Rightarrow \underline{I_B = 4.61 \mu\text{A}}$$

$$I_C = \beta I_B = (75)(4.61) \Rightarrow I_C = 0.346 \text{ mA}$$

$$V_C = 5 - (1 + \beta)I_B R_C = 5 - (76)(0.00461)(10)$$

$$\Rightarrow \underline{V_C = 1.50}$$

3.13

(a) Figure P3.12(c)

$$8 = (76)I_B(10) + 0.7 + I_B(10) - 2$$

$$I_B = \frac{10 - 0.7}{10 + (76)(10)} = 0.01208 \text{ mA}$$

Then

$$I_C = (75)I_B \Rightarrow \underline{I_C = 0.906 \text{ mA}}$$

$$\text{and } \underline{I_E = 0.918 \text{ mA}}$$

$$V_{EC} = 8 - I_E R_E - I_C R_C - (-8)$$

$$V_{EC} = 16 - (0.918)(10) - (0.906)(R_C)$$

$$V_{EC} = 6.82 - (0.906)R_C$$

$$R_C = 3 \text{ k}\Omega \pm 5\% \Rightarrow 2.85 \leq R_C \leq 3.15 \text{ k}\Omega$$

Then

$$\underline{3.97 \leq V_{EC} \leq 4.24 \text{ V}}$$

(b) Figure P3.12(d)

$$5 = (1 + \beta)I_B R_C + I_B(20) + 0.7 + (1 + \beta)I_B(2)$$

$$5 = (76)I_B R_C + I_B(20) + 0.7 + (76)I_B(2)$$

$$\text{Now } R_C = 10 \text{ k}\Omega \pm 5\% \Rightarrow 9.5 \leq R_C \leq 10.5 \text{ k}\Omega$$

$$\text{Then } 0.00443 \leq I_B \leq 0.00481 \text{ mA}$$

$$\text{And } V_C = 5 - (1 + \beta)I_B R_C$$

$$\text{So that } \underline{1.46 \leq V_C \leq 1.53 \text{ V}}$$

3.14

$$R_B = \frac{V_{BB} - V_{EB}}{I_B} = \frac{2.5 - 0.7}{0.015} \Rightarrow \underline{R_B = 120 \text{ k}\Omega}$$

$$I_{CQ} = (70)(15 \mu\text{A}) \Rightarrow 1.05 \text{ mA}$$

$$R_C = \frac{V_{CC} - V_{ECQ}}{I_{CQ}} = \frac{5 - 2.5}{1.05} \Rightarrow \underline{R_C = 2.38 \text{ k}\Omega}$$

3.15

$$a. V_B = -I_B R_B \Rightarrow I_B = \frac{-V_B}{R_B} = \frac{-(-1)}{500}$$

$$I_B = 2.0 \mu\text{A}$$

$$V_E = -1 - 0.7 = -1.7 \text{ V}$$

$$I_E = \frac{V_E - (-3)}{R_E} = \frac{-1.7 + 3}{4.8} = 0.2708 \text{ mA}$$

$$\frac{I_E}{I_B} = (1 + \beta) = \frac{0.2708}{0.002} = 135.4 \Rightarrow \underline{\beta = 134.4}$$

$$\alpha = \frac{\beta}{1 + \beta} \Rightarrow \underline{\alpha = 0.9926}$$

$$I_C = \beta I_B \Rightarrow \underline{I_C = 0.269 \text{ mA}}$$

$$V_{CE} = 3 - V_E = 3 - (-1.7) \Rightarrow \underline{V_{CE} = 4.7 \text{ V}}$$

$$b. \quad I_E = \frac{5-4}{2} \Rightarrow I_E = 0.5 \text{ mA}$$

$$4 = 0.7 + I_B R_B + (I_B + I_C) R_C - 5$$

$$I_B + I_C = I_E$$

$$4 = 0.7 + I_B(100) + (0.5)(8) - 5$$

$$I_B = 0.043 \Rightarrow \frac{I_E}{I_B} = (1 + \beta) = \frac{0.5}{0.043} = 11.63$$

$$\underline{\beta = 10.63}, \quad \alpha = \frac{\beta}{1 + \beta} \Rightarrow \underline{\alpha = 0.9140}$$

3.16

$$a. \quad V_B = 0 \Rightarrow \text{Cutoff} \Rightarrow \underline{I_E = 0}, \quad \underline{V_C = 6 \text{ V}}$$

$$b. \quad V_B = 1 \text{ V}, \quad I_E = \frac{1-0.7}{1} \Rightarrow \underline{I_E = 0.3 \text{ mA}}$$

$$I_C \approx I_E \Rightarrow V_C = 6 - (0.3)(10) \Rightarrow \underline{V_C = 3 \text{ V}}$$

$$c. \quad V_B = 2 \text{ V. Assume active-mode}$$

$$I_E = \frac{2-0.7}{1} = I_E = 1.3 \text{ mA} \approx I_C$$

$$V_C = 6 - (1.3)(10) = -7 \text{ V!}$$

Transistor in saturation

$$I_E = \frac{2-0.7}{1} \Rightarrow \underline{I_E = 1.3 \text{ mA}}$$

$$V_E = 1.3 \text{ V}, \quad V_{CE}(\text{sat}) = 0.2 \text{ V}$$

$$V_C = V_E + V_{CE}(\text{sat}) = 1.3 + 0.2$$

$$\Rightarrow \underline{V_C = 1.5 \text{ V}}$$

3.17

$$a. \quad V_{BB} = 0,$$

$$\text{Cutoff } V_0 = \left( \frac{R_L}{R_C + R_L} \right) V_{CC} = \left( \frac{10}{10 + 5} \right) (5)$$

$$\underline{V_0 = 3.33 \text{ V}}$$

$$b. \quad V_{BB} = 1 \text{ V}$$

$$I_B = \frac{1-0.7}{50} \Rightarrow 6 \mu\text{A}$$

$$I_C = \beta I_B = (75)(6) \Rightarrow I_C = 0.45 \text{ mA}$$

$$\frac{5 - V_0}{5} = I_C + \frac{V_0}{10}$$

$$1 - 0.45 = V_0 \left( \frac{1}{5} + \frac{1}{10} \right) \Rightarrow \underline{V_0 = 1.83 \text{ V}}$$

c. Transistor in saturation

$$\underline{V_0 = V_{CE}(\text{sat}) = 0.2 \text{ V}}$$

3.18

$$(a) \quad \beta_F = 100$$

$$(i) \quad I_Q = 0.1 \text{ mA} \quad I_C = \left( \frac{100}{101} \right) (0.1) = 0.0990 \text{ mA}$$

$$V_o = 5 - (0.099)(5) \Rightarrow \underline{V_o = 4.505 \text{ V}}$$

$$(ii) \quad I_Q = 0.5 \text{ mA} \quad I_C = \left( \frac{100}{101} \right) (0.5) = 0.495 \text{ mA}$$

$$V_o = 5 - (0.495)(5) \Rightarrow \underline{V_o = 2.525 \text{ V}}$$

$$(iii) \quad I_Q = 2 \text{ mA} \quad \text{Transistor is in saturation}$$

$$V_o = -V_{BE}(\text{sat}) + V_{CE}(\text{sat}) = -0.8 + 0.2 \Rightarrow$$

$$\underline{V_o = -0.6 \text{ V}}$$

$$(b) \quad \beta_F = 150$$

$$(i) \quad I_Q = 0.1 \text{ mA} \quad I_C = \left( \frac{150}{151} \right) (0.1) = 0.09934 \text{ mA}$$

$$V_o = 5 - (0.09934)(5) \Rightarrow \underline{V_o = 4.503 \text{ V}}$$

$$\% \text{ change} = \frac{4.503 - 4.505}{4.503} \times 100\% = \underline{-0.044\%}$$

$$(ii) \quad I_Q = 0.5 \text{ mA} \quad I_C = \left( \frac{150}{151} \right) (0.5) = 0.4967 \text{ mA}$$

$$V_o = 5 - (0.4967)(5) \Rightarrow \underline{V_o = 2.517 \text{ V}}$$

$$\% \text{ change} = \frac{2.517 - 2.525}{2.525} \times 100\% = \underline{-0.32\%}$$

$$(iii) \quad I_Q = 2 \text{ mA} \quad \text{Transistor in saturation}$$

$$\underline{V_o = -0.6 \text{ V} \quad \text{No change}}$$

3.19

$$I_E = \frac{V_B - 0.7}{1}$$

$$I_C = \left( \frac{\beta}{1 + \beta} \right) I_E = \left( \frac{50}{51} \right) (V_B - 0.7) = \frac{6 - V_C}{10}$$

and  $V_C = V_B$

$$\left( \frac{50}{51} \right) (V_B - 0.7) = \frac{6 - V_B}{10}$$

$$9.80(V_B - 0.7) = 6 - V_B$$

$$10.80V_B = 6 + (0.7)(9.80) \Rightarrow \underline{V_B = 1.19 \text{ V}}$$

$$I_E = \frac{1.19 - 0.7}{1} \Rightarrow \underline{I_E = 0.49 \text{ mA}}$$

3.20

$$V_{CB} = 0.5 \text{ V} \Rightarrow V_o = 0.5 \text{ V}, \quad I_C = \frac{5-0.5}{5} = 0.90 \text{ mA}$$

$$I_Q = \left( \frac{101}{100} \right) (0.90) \Rightarrow \underline{I_Q = 0.909 \text{ mA}}$$

3.21

$$I_E = \frac{10 - V_E}{10} = \frac{10 - 2}{10} \Rightarrow \underline{I_E = 0.80 \text{ mA}}$$

$$V_B = V_E - 0.7 = 2 - 0.7 = 1.3 \text{ V}$$

$$I_B = \frac{V_B}{R_B} = \frac{1.3}{50} \Rightarrow \underline{I_B = 0.026 \text{ mA}}$$

$$I_C = I_E - I_B = 0.80 - 0.026 \Rightarrow \underline{I_C = 0.774 \text{ mA}}$$

$$\beta = \frac{I_C}{I_B} = \frac{0.774}{0.026} \Rightarrow \underline{\beta = 29.77}$$


$$\alpha = \frac{\beta}{1 + \beta} = \frac{29.77}{30.77} \Rightarrow \underline{\alpha = 0.9675}$$

$$V_{EC} = V_E - V_C = V_E - (I_C R_C - 10)$$

$$= 2 - [(0.774)(10) - 10]$$

$$\underline{V_{EC} = 4.26 \text{ V}}$$

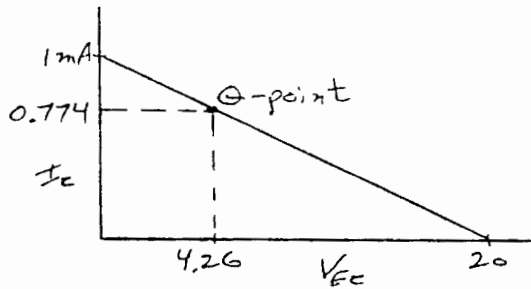Load line developed assuming the  $V_B$  voltage can change and the  $R_B$  resistor is removed.



3.22

$$I_C = \left(\frac{50}{51}\right)(1) = 0.98 \text{ mA}$$

$$V_C = I_C R_C - 9 = (0.98)(4.7) - 9$$

$$\text{or } \underline{V_C = -4.39 \text{ V}}$$

$$I_B = \frac{1}{51} = 0.0196 \text{ mA}$$

$$V_E = I_B R_B + V_{EB}(\text{on}) = (0.0196)(50) + 0.7$$

$$\text{or } \underline{V_E = 1.68 \text{ V}}$$

3.23

$$I_C = \left(\frac{50}{51}\right)(0.5) = 0.49 \text{ mA}, \quad I_B = \frac{0.5}{51} = 0.0098 \text{ mA}$$

$$V_E = I_B R_B + V_{EB}(\text{on}) = (0.0098)(50) + 0.7$$

$$\text{or } \underline{V_E = 1.19 \text{ V}}$$

$$V_C = I_C R_C - 9 = (0.49)(4.7) - 9 = -6.70 \text{ V}$$

$$\text{Then } \underline{V_{EC} = V_E - V_C = 1.19 - (-6.7) = 7.89 \text{ V}}$$

$$P_Q = I_C V_{EC} + I_B V_{EB} = (0.49)(7.89) + (0.0098)(0.7)$$

$$\text{or } \underline{P_Q = 3.87 \text{ mW}}$$

$$\text{Power Supplied} = P_s = I_Q(9 - V_E) = (0.5)(9 - 1.19)$$

$$\text{Or } \underline{P_s = 3.91 \text{ mW}}$$

3.24

$$\text{For } I_Q = 0, \text{ then } \underline{P_Q = 0}$$

$$\text{For } I_Q = 0.5 \text{ mA}, \quad I_C = \left(\frac{50}{51}\right)(0.5) = 0.49 \text{ mA}$$

$$I_B = \frac{0.5}{51} = 0.0098 \text{ mA}, \quad V_B = 0.490 \text{ V}, \quad V_E = 1.19 \text{ V}$$

$$V_C = (0.49)(4.7) - 9 = -6.70 \text{ V} \Rightarrow \underline{V_{EC} = 7.89 \text{ V}}$$

$$P \approx I_C V_{EC} = (0.49)(7.89) \Rightarrow \underline{P = 3.87 \text{ mW}}$$

For  $I_Q = 1.0 \text{ mA}$ , Using the same calculations as above, we find  $P = 5.95 \text{ mW}$

$$\text{For } I_Q = 1.5 \text{ mA}, \quad P = 6.26 \text{ mW}$$

$$\text{For } I_Q = 2 \text{ mA}, \quad P = 4.80 \text{ mW}$$

$$\text{For } I_Q = 2.5 \text{ mA}, \quad P = 1.57 \text{ mW}$$

For  $I_Q = 3 \text{ mA}$ , Transistor is in saturation.

$$0.7 + I_B(50) = 0.2 + I_C(4.7) - 9$$

$$I_E = I_Q = I_B + I_C \Rightarrow I_B = 3 - I_C$$

$$\text{Then, } 0.7 + (3 - I_C)(50) = 0.2 + I_C(4.7) - 9$$

$$\text{Which yields } \underline{I_C = 2.916 \text{ mA}} \text{ and } \underline{I_B = 0.084 \text{ mA}}$$

$$P = I_B V_{EB} + I_C V_{EC} = (0.084)(0.7) + (2.916)(0.2)$$

$$\text{or } \underline{P = 0.642 \text{ mW}}$$

3.25

$$I_{E1} = I_{E2} = \frac{I}{2} \Rightarrow \underline{I_{E1} = I_{E2} = 0.5 \text{ mA}}$$

$$I_{C1} = I_{C2} \approx 0.5 \text{ mA}$$

$$V_{C1} = V_{C2} = 5 - (0.5)(4) \Rightarrow \underline{V_{C1} = V_{C2} = 3 \text{ V}}$$

3.26

$$\text{a. } I_{BQ} = \frac{V_{CC} - V_{BE}(\text{on})}{R_B}$$

$$I_{BQ} = \frac{I_{CQ}}{\beta} = \frac{2}{60} = 0.0333 \text{ mA}$$

$$R_B = \frac{24 - 0.7}{0.0333} \Rightarrow \underline{R_B = 699 \text{ k}\Omega}$$

$$I_{CQ} = \frac{V_{CC} - V_{CEQ}}{R_C} \Rightarrow R_C = \frac{24 - 12}{2}$$

$$\Rightarrow \underline{R_C = 6 \text{ k}\Omega}$$

$$\text{b. } I_{BQ} = \frac{V_{CC} - V_{BE}(\text{on})}{R_B} = \frac{24 - 0.7}{699}$$

$$= 0.0333 \text{ mA (Unchanged)}$$


$$I_{CQ} = \beta I_{BQ} = (100)(0.0333)$$

$$\Rightarrow \underline{I_{CQ} = 3.33 \text{ mA}}$$

$$V_{CEQ} = V_{CC} - I_{CQ} R_C = 24 - (3.33)(6)$$

$$\Rightarrow \underline{V_{CEQ} = 4.02 \text{ V}}$$

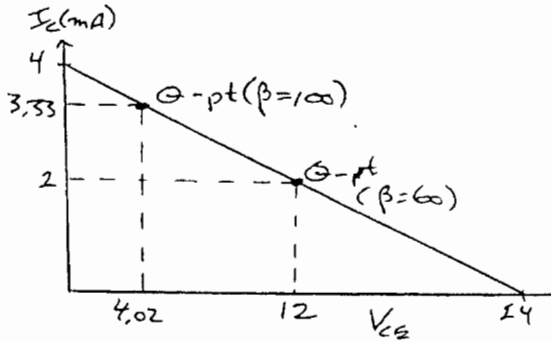(c)  $V_{CE} = V_{CC} - I_C R_C = 24 - I_C(6)$




$I_{R2} = 0.057 \text{ mA}$

$I_{R1} = I_{R2} + I_{BQ} = 0.057 + 0.16 = 0.217 \text{ mA}$

$V_1 = (0.217)(15) + 0.7 \Rightarrow 3.96 \text{ V}$

So  $1.86 < V_1 < 3.96 \text{ V}$

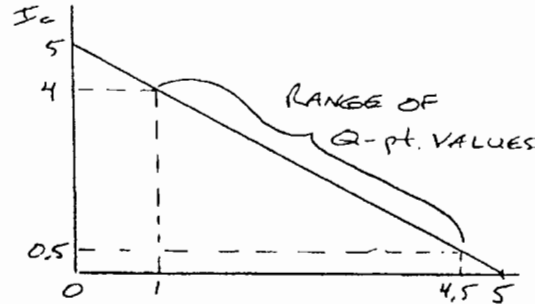

3.27

$I_E = \frac{V_{EE} - V_{EB(ON)}}{R_E} = \frac{9 - 0.7}{4}$

$\Rightarrow I_E = 2.075 \text{ mA}$

$I_C = \alpha I_E = (0.9920)(2.075)$

$\Rightarrow I_C = 2.06 \text{ mA}$

$V_{BC} + I_C R_C = V_{CC}$

$V_{BC} = 9 - (2.06)(2.2) \Rightarrow V_{BC} = 4.47 \text{ V}$

3.28

$I_{CQ} = \frac{V_{CC} - V_{CEQ}}{R_C} = \frac{12 - 6}{2.2} = 2.73 \text{ mA}$

$I_{BQ} = \frac{I_{CQ}}{\beta} = \frac{2.73}{30} \Rightarrow I_{BQ} = 0.091 \text{ mA}$

$I_{R2} = \frac{0.7 - (-12)}{100} = 0.127 \text{ mA}$

$I_{R1} = I_{R2} + I_{BQ} = 0.127 + 0.091 = 0.218 \text{ mA}$

$V_1 = I_{R1} R_1 + 0.7 = (0.218)(15) + 0.7$

$\Rightarrow V_1 = 3.97 \text{ V}$

3.29

For  $V_{CE} = 4.5$

$I_{CQ} = \frac{5 - 4.5}{1} = 0.5 \text{ mA}$

$I_{BQ} = \frac{0.5}{25} = 0.02 \text{ mA}$

$I_{R2} = \frac{0.7 - (-5)}{100} = 0.057 \text{ mA}$

$I_{R1} = I_{R2} + I_{BQ} = 0.057 + 0.02 = 0.077 \text{ mA}$

$V_1 = I_{R1} R_1 + V_{BE(ON)} = (0.077)(15) + 0.7$

$= 1.86 \text{ V}$

For  $V_{CE} = 1.0$

$I_{CQ} = \frac{5 - 1}{1} = 4 \text{ mA}$

$I_{BQ} = \frac{4}{25} = 0.16 \text{ mA}$

3.30

$R_{TH} = R_1 \parallel R_2 = 33 \parallel 10 = 7.67 \text{ k}\Omega$

$V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right) V_{CC} = \left( \frac{10}{10 + 33} \right) (18)$   
 $= 4.19 \text{ V}$

$I_{BQ} = \frac{V_{TH} - V_{BE(ON)}}{R_{TH} + (1 + \beta)R_E} = \frac{4.19 - 0.7}{7.67 + (51)(1)}$

$I_{BQ} = 0.0595 \text{ mA}$

$I_{CQ} = \beta I_{BQ} \Rightarrow I_{CQ} = 2.97 \text{ mA}$

$I_{EQ} = 3.03 \text{ mA}$

$V_{CEQ} = V_{CC} - I_{CQ} R_C - I_{EQ} R_E$

$= 18 - (2.97)(2.2) - (3.03)(1)$

$\Rightarrow V_{CEQ} = 8.44 \text{ V}$

3.31

$I_{CQ} = 1.2 \text{ mA}, V_{CEQ} = 9 \text{ V}, R_{TH} = 50 \text{ k}\Omega$

Also  $I_B = \frac{1.2}{80} = 0.015 \text{ mA}$

$V_{TH} = I_{BQ} R_{TH} + V_{BE(ON)} + (1 + \beta) I_{BQ} R_E$

$V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right) (V_{CC}) = \frac{1}{R_1} \cdot R_{TH} \cdot V_{CC} = \frac{1}{R_1} (50)(18)$

Then

$\frac{1}{R_1} (50)(18) = (0.015)(50) + 0.7 + (81)(0.015)(1)$

or  $R_1 = 338 \text{ k}\Omega$ . Then  $\frac{338 R_2}{338 + R_2} = 50 \Rightarrow$

$R_2 = 58.7 \text{ k}\Omega \quad I_{EQ} = \left( \frac{81}{80} \right) (1.2) = 1.215 \text{ mA}$

$18 = I_{CQ} R_C + V_{CEQ} + I_{BQ} R_E$

$18 = (1.2) R_C + 9 + (1.215)(1) \Rightarrow R_C = 6.49 \text{ k}\Omega$

3.32

$$R_{TH} = R_1 \parallel R_2 = 20 \parallel 15 = 8.57 \text{ k}\Omega$$

$$V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right) V_{CC} = \left( \frac{15}{15 + 20} \right) (10) = 4.29 \text{ V}$$

$$V_{CC} = I_{EQ} R_E + V_{BE(on)} + \frac{I_{EQ}}{1 + \beta} \cdot R_{TH} + V_{TH}$$

$$10 = I_{EQ}(1) + 0.7 + I_{EQ} \left( \frac{8.57}{101} \right) + 4.29$$

Then

$$I_{EQ} = \frac{10 - 0.7 - 4.29}{1 + \frac{8.57}{101}} = \frac{5.01}{1.085} \Rightarrow I_{EQ} = 4.62 \text{ mA}$$

$$V_B = \frac{I_{EQ}}{1 + \beta} \cdot R_{TH} + V_{TH} = \left( \frac{4.62}{101} \right) (8.57) + 4.29$$

or

$$V_B = 4.68 \text{ V}$$

3.33

a.  $R_{TH} = R_1 \parallel R_2 = 58 \parallel 42 = 24.36 \text{ k}\Omega$

$$V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right) V_{CC} = \left( \frac{42}{42 + 58} \right) (24) = 10.1 \text{ V}$$

$$I_{BQ} = \frac{V_{TH} - V_{BE(on)}}{R_{TH} + (1 + \beta)R_E} = \frac{10.1 - 0.7}{24.36 + (126)(10)}$$

$$I_{BQ} = 0.00732 \text{ mA}$$

$$I_{CQ} = \beta I_{BQ} = (125)(0.00732)$$

$$\Rightarrow I_{CQ} = 0.915 \text{ mA}$$

$$I_{EQ} = 0.922 \Rightarrow V_{CEQ} = 24 - (0.922)(10)$$

$$\Rightarrow V_{CEQ} = 14.8 \text{ V}$$

b. Let

$$R_2 = 42 \text{ k}\Omega + 5\% = 44.1 \text{ k}\Omega$$

$$R_1 = 58 \text{ k}\Omega - 5\% = 55.1 \text{ k}\Omega$$

$$R_E = 10 \text{ k}\Omega - 5\% = 9.5 \text{ k}\Omega$$

$$R_{TH} = R_1 \parallel R_2 = 24.5 \text{ k}\Omega$$

$$V_{TH} = \left( \frac{44.1}{44.1 + 55.1} \right) (24) = 10.7 \text{ V}$$

$$I_{BQ} = \frac{10.7 - 0.7}{24.5 + (126)(9.5)} = 0.00819$$

$$I_{CQ} = 1.02 \text{ mA}, I_{EQ} = 1.03 \text{ mA}$$

$$V_{CEQ} = 24 - (1.03)(9.5) \Rightarrow V_{CEQ} = 14.2 \text{ V}$$

Let

$$R_2 = 42 \text{ k}\Omega - 5\% = 39.9 \text{ k}\Omega$$

$$R_1 = 58 \text{ k}\Omega + 5\% = 60.9 \text{ k}\Omega$$

$$R_E = 10 \text{ k}\Omega + 5\% = 10.5 \text{ k}\Omega$$

$$R_{TH} = R_1 \parallel R_2 = 24.1 \text{ k}\Omega$$

$$V_{TH} = \left( \frac{39.9}{39.9 + 60.9} \right) (24) = 9.5 \text{ V}$$

$$I_{BQ} = \frac{9.5 - 0.7}{24.1 + (126)(10.5)} = 0.00653 \text{ mA}$$

$$I_{CQ} = 0.817 \text{ mA}, I_{EQ} = 0.823 \text{ mA}$$

$$V_{CEQ} = 24 - (0.823)(10.5) \Rightarrow V_{CEQ} = 15.4 \text{ V}$$

$$\text{So } 0.817 \leq I_{CQ} \leq 1.02 \text{ mA and } 14.2 \leq V_{CEQ} \leq 15.4 \text{ V.}$$

3.34

a.  $R_{TH} = R_1 \parallel R_2 = 25 \parallel 8 = 6.06 \text{ k}\Omega$

$$V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right) V_{CC} = \left( \frac{8}{8 + 25} \right) (24) = 5.82 \text{ V}$$

$$I_{BQ} = \frac{V_{TH} - V_{BE(on)}}{R_{TH} + (1 + \beta)R_E} = \frac{5.82 - 0.7}{6.06 + (76)(1)}$$

$$I_{BQ} = 0.0624 \text{ mA}, I_{CQ} = 4.68 \text{ mA}$$

$$I_{EQ} = 4.74$$

$$V_{CEQ} = V_{CC} - I_{CQ} R_C - I_{EQ} R_E$$

$$= 24 - (4.68)(3) - (4.74)(1)$$

$$V_{CEQ} = 5.22 \text{ V}$$

b.  $I_{BQ} = \frac{5.82 - 0.7}{6.06 + (151)(1)} \Rightarrow I_{BQ} = 0.0326 \text{ mA}$

$$I_{CQ} = 4.89 \text{ mA}$$

$$I_{EQ} = 4.92$$

$$V_{CEQ} = 24 - (4.89)(3) - (4.92)(1)$$

$$V_{CEQ} = 4.41 \text{ V}$$

3.35

(a)  $I_{CQ} \cong I_{EQ} = 0.4 \text{ mA}$

$$R_C = \frac{3}{0.4} \Rightarrow R_C = 7.5 \text{ k}\Omega; R_E = \frac{3}{0.4} \Rightarrow R_E = 7.5 \text{ k}\Omega$$

$$R_1 + R_2 \cong \frac{9}{(0.2)(0.4)} = 112.5 \text{ k}\Omega$$

$$V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right) V_{CC} = I_{BQ} R_{TH} + V_{BE(on)} + (1 + \beta) I_{BQ} R_E$$

$$R_{TH} = \frac{R_1 R_2}{R_1 + R_2} = \frac{(112.5 - R_2) R_2}{112.5}$$

$$I_{BQ} = \frac{0.4}{100} = 0.004 \text{ mA}$$

$$R_2 \left( \frac{9}{112.5} \right) = (0.004) \left[ \frac{(112.5 - R_2) R_2}{112.5} \right] + 0.7$$

$$+ (101)(0.004)(7.5)$$

We obtain

$$R_2(0.08) = 0.004 R_2 - 3.56 \times 10^{-3} R_2^2 + 3.73$$

From this quadratic, we find

$$R_2 = 48 \text{ k}\Omega \Rightarrow R_1 = 64.5 \text{ k}\Omega$$

(b) Standard resistor values:

Set  $R_E = R_C = 7.5 \text{ k}\Omega$  and

$R_1 = 62 \text{ k}\Omega$ ,  $R_2 = 47 \text{ k}\Omega$

Now  $R_{TH} = R_1 \parallel R_2 = 62 \parallel 47 = 26.7 \text{ k}\Omega$

$$V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right) (V_{CC}) = \left( \frac{47}{47 + 62} \right) (9) = 3.88 \text{ V}$$

$$V_{TH} = I_{BQ} R_{TH} + V_{BE}(\text{on}) + (1 + \beta) I_{BQ} R_E$$

So

$$I_{BQ} = \frac{3.88 - 0.7}{26.7 + (101)(7.5)} = 0.00406 \text{ mA}$$

Then

$$I_{CQ} = 0.406 \text{ mA}$$

$$V_{RC} = V_{RE} = (0.406)(7.5) = 3.05 \text{ V}$$

3.36

a.  $R_{TH} = R_1 \parallel R_2 = 12 \parallel 2 = 1.71 \text{ k}\Omega = R_{TH}$

$$V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right) (10) - 5 = \left( \frac{2}{12 + 2} \right) (10) - 5 = -3.57 \text{ V} = V_{TH}$$

b.

$$I_{BQ} = \frac{V_{TH} - V_{BE}(\text{on}) - (-5)}{R_{TH} + (1 + \beta) R_E} = \frac{-3.57 - 0.7 + 5}{1.71 + (101)(0.5)} = \frac{0.73}{52.2}$$


$$\Rightarrow I_{BQ} = 0.0140 \text{ mA}$$

$$I_{CQ} = 1.40 \text{ mA}, I_{EQ} = 1.41 \text{ mA}$$

$$V_{CEQ} = 10 - I_{CQ} R_C - I_{EQ} R_E = 10 - (1.40)(5) - (1.41)(0.5) = 2.30 \text{ V}$$

$$V_{CEQ} = 2.30 \text{ V}$$

c.

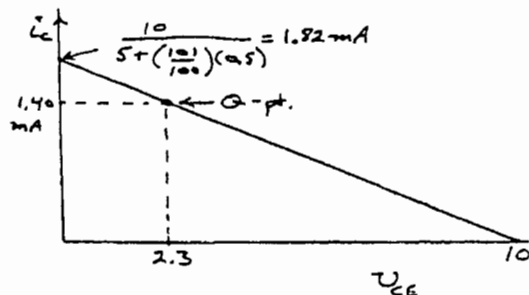

d. For

$$R_2 = 2 \text{ k}\Omega + 5\% = 2.1 \text{ k}\Omega$$

$$R_1 = 12 \text{ k}\Omega - 5\% = 11.4 \text{ k}\Omega$$

$$R_E = 0.5 \text{ k}\Omega - 5\% = 0.475 \text{ k}\Omega$$

$$R_{TH} = R_1 \parallel R_2 = 1.77 \text{ k}\Omega$$

$$V_{TH} = \left( \frac{2.1}{2.1 + 1.4} \right) (10) - 5 = -3.44 \text{ V}$$

$$I_{BQ} = \frac{-3.44 - 0.7 + 5}{1.77 + (101)(0.475)} = \frac{0.86}{49.7} = 0.0173 \text{ mA}$$

$$I_{CQ} = 1.73 \text{ mA}, I_{EQ} = 1.75 \text{ mA}$$

$$\text{For } R_C = 5 \text{ k}\Omega + 5\% = 5.25 \text{ k}\Omega$$

$$V_{CEQ} = 10 - (1.73)(5.25) - (1.75)(0.475)$$

$$\Rightarrow V_{CEQ} = 0.0863 \text{ V (Saturation)}$$

For

$$R_2 = 2 \text{ k}\Omega - 5\% = 1.9 \text{ k}\Omega$$

$$R_1 = 12 \text{ k}\Omega + 5\% = 12.6 \text{ k}\Omega$$

$$R_E = 0.5 \text{ k}\Omega + 5\% = 0.525 \text{ k}\Omega$$

$$R_{TH} = R_1 \parallel R_2 = 1.65 \text{ k}\Omega$$

$$V_{TH} = \left( \frac{1.9}{12.6 + 1.9} \right) (10) - 5 = -3.69 \text{ V}$$

$$I_{BQ} = \frac{-3.69 - 0.7 + 5}{1.65 + (101)(0.525)} = \frac{0.61}{54.7} = 0.0112 \text{ mA}$$

$$I_{CQ} = 1.12 \text{ mA}, I_{EQ} = 1.13 \text{ mA}$$

$$\text{For } R_C = 5 \text{ k}\Omega - 5\% = 4.75 \text{ k}\Omega$$

$$V_{CEQ} = 10 - (1.12)(4.75) - (1.13)(0.525)$$

$$\Rightarrow V_{CEQ} = 4.09 \text{ V}$$

$$\text{So } 1.12 \leq I_{CQ} \leq 1.73 \text{ mA and}$$

$$\underbrace{0.0863}_{\text{Saturation}} \leq V_{CEQ} \leq 4.09 \text{ V.}$$

Saturation

3.37

$$R_{TH} = R_1 \parallel R_2 = 9 \parallel 1 = 0.90 \text{ k}\Omega$$

$$V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right) (-12) = \left( \frac{1}{1 + 9} \right) (-12) = -1.2 \text{ V}$$

$$I_{EQ} R_E + V_{EB}(\text{on}) + I_{BQ} R_{TH} + V_{TH} = 0$$

$$I_{BQ} = \frac{-V_{TH} - V_{EB}(\text{on})}{R_{TH} + (1 + \beta) R_E} = \frac{1.2 - 0.7}{0.90 + (76)(0.1)}$$

$$I_{BQ} = 0.0588, I_{CQ} = 4.41 \text{ mA}$$

$$I_{EQ} = 4.47 \text{ mA}$$

$$\text{Center of load line} \Rightarrow V_{ECQ} = 6 \text{ V}$$

$$I_{EQ} R_E + V_{ECQ} + I_{CQ} R_C - 12 = 0$$

$$(4.47)(0.1) + 6 + (4.41) R_C = 12$$

$$\Rightarrow R_C = 1.26 \text{ k}\Omega$$

3.38

$$(a) R_{TH} = (0.1)(1 + \beta)R_E = (0.1)(101)(0.5) = 5.05 \text{ k}\Omega$$

$$V_{TH} = \frac{1}{R_1} \cdot R_{TH} \cdot V_{CC} = I_{BQ}R_{TH} + V_{BE(on)} + (1 + \beta)I_{BQ}R_E$$

$$I_{BQ} = \frac{I_{CQ}}{\beta} = \frac{0.8}{100} = 0.008 \text{ mA}$$

Then

$$\frac{1}{R_1}(5.05)(10) = (0.008)(5.05) + 0.7 + (101)(0.008)(0.5)$$

or

$$R_1 = 44.1 \text{ k}\Omega, \quad \frac{44.1R_2}{44.1 + R_2} = 5.05 \Rightarrow R_2 = 5.70 \text{ k}\Omega$$

$$\text{Now } I_{EQ} = \left(\frac{101}{100}\right)(0.8) = 0.808 \text{ mA}$$

$$V_{CC} = I_{CQ}R_C + V_{CEQ} + I_{EQ}R_E$$

$$10 = (0.8)R_C + 5 + (0.808)(0.5)$$

$$R_C = 5.75 \text{ k}\Omega$$

(b) For  $75 \leq \beta \leq 150$ 

$$V_{TH} = \left(\frac{R_2}{R_1 + R_2}\right)(V_{CC}) = \left(\frac{5.7}{5.7 + 44.1}\right)(10) = 1.145 \text{ V}$$

$$V_{TH} = I_{BQ}R_{TH} + V_{BE(on)} + (1 + \beta)I_{BQ}R_E$$

$$\text{For } \beta = 75, \quad I_{BQ} = \frac{1.145 - 0.7}{5.05 + (76)(0.5)} = 0.0103 \text{ mA}$$

$$\text{Then } I_{CQ} = (75)(0.0103) = 0.775 \text{ mA}$$

$$\text{For } \beta = 150, \quad I_{BQ} = \frac{1.145 - 0.7}{5.05 + (151)(0.5)} = 0.00552 \text{ mA}$$

$$\text{Then } I_{CQ} = 0.829 \text{ mA}$$

$$\% \text{ Change} = \frac{\Delta I_{CQ}}{I_{CQ}} = \frac{0.829 - 0.775}{0.80} \times 100\% \Rightarrow$$

$$\% \text{ Change} = 6.75\%$$

(c) For  $R_E = 1 \text{ k}\Omega$ 

$$R_{TH} = (0.1)(101)(1) = 10.1 \text{ k}\Omega$$

$$V_{TH} = \frac{1}{R_1} \cdot R_{TH} \cdot V_{CC} = \frac{1}{R_1}(10.1)(10) =$$

$$(0.008)(10.1) + 0.7 + (101)(0.008)(1)$$

$$\text{which yields } R_1 = 63.6 \text{ k}\Omega$$

$$\text{And } \frac{63.6R_2}{63.6 + R_2} = 10.1 \Rightarrow R_2 = 12.0 \text{ k}\Omega$$

$$\text{Now } V_{TH} = \left(\frac{R_2}{R_1 + R_2}\right)(V_{CC}) = \left(\frac{12}{12 + 63.6}\right)(10) = 1.587 \text{ V}$$

$$\text{For } \beta = 75, \quad I_{BQ} = \frac{1.587 - 0.7}{10.1 + (76)(1)} = 0.0103 \text{ mA}$$

$$\text{So } I_{CQ} = 0.773 \text{ mA}$$

$$\text{For } \beta = 150, \quad I_{BQ} = \frac{1.587 - 0.7}{10.1 + (151)(1)} = 0.00551 \text{ mA}$$

$$\text{Then } I_{CQ} = 0.826 \text{ mA}$$

$$\% \text{ Change} = \frac{\Delta I_{CQ}}{I_{CQ}} = \frac{0.826 - 0.773}{0.8} \times 100\% \Rightarrow$$

$$\% \text{ Change} = 6.63\%$$

3.39

$$V_{CC} \cong I_{CQ}(R_C + R_E) + V_{CEQ}$$

$$10 = (0.8)(R_C + R_E) + 5 \Rightarrow R_C + R_E = 6.25 \text{ k}\Omega$$

$$\text{Let } R_E = 1 \text{ k}\Omega$$

$$\text{Then, for bias stable } R_{TH} = (0.1)(121)(1) = 12.1 \text{ k}\Omega$$

$$I_{BQ} = \frac{0.8}{120} = 0.00667 \text{ mA}$$

$$\frac{1}{R_1}(12.1)(10) = (0.00667)(12.1) + 0.7 + (121)(0.00667)(1)$$

$$\text{So } R_1 = 76.2 \text{ k}\Omega \text{ and } \frac{76.2R_2}{76.2 + R_2} = 12.1 \Rightarrow$$

$$R_2 = 14.4 \text{ k}\Omega$$

$$\text{Then } I_R \cong \frac{10}{76.2 + 14.4} = 0.110 \text{ mA}$$

This is close to the design specification.

3.40

$$I_{CQ} \approx I_{EQ} \Rightarrow V_{CEQ} = V_{CC} - I_{CQ}(R_C + R_E)$$

$$6 = 12 - I_{CQ}(2 + 0.2)$$

$$I_{CQ} = 2.73 \text{ mA}, \quad I_{BQ} = 0.0218 \text{ mA}$$

$$V_{CEQ} = 6 \text{ V}$$

$$V_{TH} = I_{BQ}R_{TH} + V_{BE(on)} + (1 + \beta)I_{BQ}R_E - 6$$

$$V_{TH} = \left(\frac{R_2}{R_1 + R_2}\right)(12) - 6, \quad R_{TH} = R_1 \parallel R_2$$

Bias stable  $\Rightarrow$ 

$$R_{TH} = (0.1)(1 + \beta)R_E = (0.1)(126)(0.2) = 2.52 \text{ k}\Omega$$

$$V_{TH} = \left(\frac{1}{R_1}\right)(R_{TH})(12) - 6$$

$$\frac{1}{R_1}(2.52)(12) - 6 = (0.0218)(2.52) + 0.7$$

$$+ (126)(0.0218)(0.2) - 6$$

$$\frac{1}{R_1}(30.24) = 0.7549 + 0.5494$$

$$R_1 = 23.2 \text{ k}\Omega, \quad \frac{23.2R_2}{23.2 + R_2} = 2.52$$

$$R_2 = 2.83 \text{ k}\Omega$$

3.41

$$\begin{aligned}
 \text{a. } I_{CQ} &= 1 \text{ mA. } I_{BQ} = \left(\frac{80}{81}\right)(1) = 1.01 \text{ mA} \\
 V_{CEQ} &= 12 - (1)(2) - (1.01)(0.2) \Rightarrow \underline{V_{CEQ} = 9.80 \text{ V}} \\
 I_{BQ} &= \frac{1}{80} = 0.0125 \text{ mA} \\
 R_{TH} &= +(0.1)(1 + \beta)R_E = (0.1)(81)(0.2) = 1.62 \text{ k}\Omega \\
 V_{TH} &= \left(\frac{R_2}{R_1 + R_2}\right)(12) - 6 = \frac{1}{R_1}(R_{TH})(12) - 6 \\
 &= \frac{1}{R_1}(19.44) - 6 \\
 V_{TH} &= I_{BQ}R_{TH} + V_{BE(on)} + (1 + \beta)I_{BQ}R_E - 6 \\
 \frac{1}{R_1}(19.44) - 6 &= (0.0125)(1.62) + 0.7 \\
 &\quad + (81)(0.0125)(0.2) - 6 \\
 \frac{1}{R_1}(19.44) &= 0.923 \\
 \underline{R_1} &= 21.1 \text{ k}\Omega, \quad \frac{21.1R_2}{21.1 + R_2} = 1.62 \\
 \underline{R_2} &= 1.75 \text{ k}\Omega
 \end{aligned}$$

b.

$$\begin{aligned}
 R_1 &= 22.2 \text{ k}\Omega \text{ or } R_1 = 20.0 \text{ k}\Omega \\
 R_2 &= 1.84 \text{ k}\Omega \text{ or } R_2 = 1.66 \text{ k}\Omega \\
 R_E &= 0.21 \text{ k}\Omega \text{ or } R_E = 0.19 \text{ k}\Omega \\
 R_C &= 2.1 \text{ k}\Omega \text{ or } R_C = 1.9 \text{ k}\Omega \\
 R_2(\text{max}), R_1(\text{min}), R_E(\text{min}) \\
 R_{TH} &= (1.84) \parallel (20.0) = 1.685 \text{ k}\Omega
 \end{aligned}$$

$$\begin{aligned}
 V_{TH} &= \left(\frac{1.84}{1.84 + 20.0}\right)(12) - 6 = -4.99 \text{ V} \\
 I_{BQ} &= \frac{-4.99 - 0.7 - (-6)}{1.685 + (81)(0.19)} = \frac{0.31}{17.08} = 0.0182 \text{ mA} \\
 \underline{I_{CQ}} &= 1.45 \text{ mA}
 \end{aligned}$$

For max.  $R_C \Rightarrow$ 

$$\begin{aligned}
 V_{CE} &= 12 - (1.45)(2.1) - (1.47)(0.19) \\
 \underline{V_{CE}} &= 8.68 \text{ V}
 \end{aligned}$$

 $R_2(\text{min}), R_1(\text{max}), R_E(\text{max})$ 

$$\begin{aligned}
 R_{TH} &= (1.66) \parallel (22.2) = 1.547 \text{ k}\Omega \\
 V_{TH} &= \left(\frac{1.66}{1.66 + 22.2}\right)(12) - 6 = -5.165 \text{ V} \\
 I_{BQ} &= \frac{-5.165 - 0.7 + 6}{1.547 + (81)(0.21)} = \frac{0.135}{18.56} = 0.00727 \text{ mA}
 \end{aligned}$$

For min.  $R_C \Rightarrow \underline{I_{CQ}} = 0.582 \text{ mA}$ ,  $I_E = 0.589$ 

$$V_{CEQ} = 12 - (0.582)(1.9) - (0.589)(0.21)$$

$$\underline{V_{CEQ}} = 10.77 \text{ V}$$

So  $0.582 \leq I_C \leq 1.45 \text{ mA}$ 

$$8.68 \leq V_{CEQ} \leq 10.77 \text{ V}$$

3.42

$$\begin{aligned}
 V_{CEQ} &\cong V_{CC} - I_{CQ}(R_C + R_E) \\
 5 &= 12 - 3(R_C + R_E) \Rightarrow R_C + R_E = 2.33 \text{ k}\Omega \\
 \text{Let } \underline{R_E} &= 0.33 \text{ k}\Omega \text{ and } \underline{R_C} = 2 \text{ k}\Omega \\
 \text{Nominal value of } \beta &= 100 \\
 R_{TH} &= (0.1)(1 + \beta)R_E = (0.1)(101)(0.33) = 3.33 \text{ k}\Omega \\
 I_{BQ} &= \frac{3}{100} = 0.03 \text{ mA} \\
 V_{TH} &= \frac{1}{R_1} \cdot R_{TH} \cdot (12) - 6 = \frac{1}{R_1}(3.33)(12) - 6 \\
 \text{Then} \\
 V_{TH} &= I_{BQ}R_{TH} + V_{BE(on)} + (1 + \beta)I_{BQ}R_E - 6 \\
 \frac{1}{R_1}(3.33)(12) - 6 &= (0.03)(3.33) + 0.7 + (101)(0.03)(0.33) - 6 \\
 \text{which yields } \underline{R_1} &= 22.2 \text{ k}\Omega \text{ and } \underline{R_2} = 3.92 \text{ k}\Omega
 \end{aligned}$$

Now

$$V_{TH} = \left(\frac{R_2}{R_1 + R_2}\right)(12) - 6 = \left(\frac{3.92}{3.92 + 22.2}\right)(12) - 6$$

or

$$V_{TH} = -4.20 \text{ V}$$

For  $\beta = 75$ ,

$$\begin{aligned}
 V_{TH} &= I_{BQ}R_{TH} + V_{BE(on)} + (1 + \beta)I_{BQ}R_E - 6 \\
 I_{BQ} &= \frac{V_{TH} + 6 - 0.7}{R_{TH} + (1 + \beta)R_E} = \frac{-4.2 + 6 - 0.7}{3.33 + (76)(0.33)} \\
 &= 0.0387 \text{ mA} \Rightarrow \underline{I_C} = 2.90 \text{ mA}
 \end{aligned}$$

For  $\beta = 150$ ,

$$I_{BQ} = \frac{-4.2 + 6 - 0.7}{3.33 + (151)(0.33)} = 0.0207 \text{ mA}$$

Then

$$\underline{I_C} = 3.10 \text{ mA}$$

Specifications are met.

3.43

$$\begin{aligned}
 R_{TH} &= R_1 \parallel R_2 = 3 \parallel 12 = 2.4 \text{ k}\Omega \\
 V_{TH} &= \left(\frac{R_2}{R_1 + R_2}\right)V_{CC} = \left(\frac{12}{12 + 3}\right)(20) = 16 \text{ V}
 \end{aligned}$$

(a) For  $\beta = 75$ 

$$\begin{aligned}
 20 &= (1 + \beta)I_{BQ}R_E + V_{BE(on)} + I_{BQ}R_{TH} + V_{TH} \\
 20 - 0.7 - 16 &= I_{BQ}[(76)(2) + 2.4]
 \end{aligned}$$

So

$$I_{BQ} = 0.0214 \text{ mA}, \quad I_{CQ} = 1.60 \text{ mA}, \quad I_{EQ} = 1.62 \text{ mA}$$

$$V_{ECQ} = 20 - (1.6)(1) - (1.62)(2)$$

or

$$\underline{V_{ECQ}} = 15.16 \text{ V}$$

(b) For  $\beta = 100$ , we find

$$I_{BQ} = 0.0161 \text{ mA}, \quad I_{CQ} = 1.61 \text{ mA}, \quad V_{ECQ} = 15.13 \text{ V}$$

3.44

$$I_{CQ} = 4.8 \text{ mA} \rightarrow I_{EQ} = 4.84 \text{ mA}$$

$$V_{CEQ} = V_{CC} - I_{CQ}R_C - I_{EQ}R_E$$

$$6 = 18 - (4.8)(2) - (4.84)R_E \Rightarrow \underline{R_E = 0.496 \text{ k}\Omega}$$

$$R_{TH} = (0.1)(1 + \beta)R_E = (0.1)(121)(0.496) = 6.0 \text{ k}\Omega$$

$$V_{TH} = I_{BQ}R_{TH} + V_{BE(on)} + (1 + \beta)I_{BQ}R_E$$

$$I_{BQ} = 0.040 \text{ mA}$$

$$V_{TH} = \frac{1}{R_1} \cdot R_{TH} \cdot V_{CC} = \frac{1}{R_1}(6.0)(18)$$

$$\frac{1}{R_1}(6.0)(18) = (0.04)(6.0) + 0.70$$

$$+ (121)(0.04)(0.496)$$

$$\frac{1}{R_1}(108) = 3.34$$

$$\underline{R_1 = 32.3 \text{ k}\Omega}, \quad \frac{32.3R_2}{32.3 + R_2} = 6.0$$

$$\underline{R_2 = 7.37 \text{ k}\Omega}$$

3.45

For nominal  $\beta = 70$ 

$$I_{BQ} = \frac{2}{70} = 0.0286 \text{ mA} \rightarrow I_{EQ} = 2.03 \text{ mA}$$

$$V_{CEQ} = V_{CC} - I_{CQ}R_C - I_{EQ}R_E$$

$$10 = 20 - (2)(4) - (2.03)R_E \Rightarrow \underline{R_E = 0.985 \text{ K}}$$

$$R_{TH} = (0.1)(1 + \beta)R_E = (0.1)(71)(0.985) = 6.99 \text{ K}$$

$$V_{TH} = I_{BQ}R_{TH} + V_{BE(on)} + I_{EQ}R_E$$

$$\frac{1}{R_1} \cdot R_{TH} \cdot V_{CC} = I_{BQ}R_{TH} + V_{BE(on)} + I_{EQ}R_E$$

$$\frac{1}{R_1}(6.99)(20) = (0.0286)(6.99) + 0.70$$

$$+ (2.03)(0.985)$$

$$\frac{1}{R_1}(139.8) = 2.90$$

$$\underline{R_1 = 48.2 \text{ K}}, \quad \frac{48.2R_2}{48.2 + R_2} = 6.99$$

$$\underline{R_2 = 8.18 \text{ K}}$$

Check: For  $\beta = 50$ 

$$V_{TH} = \left( \frac{8.18}{8.18 + 48.2} \right) (20) = 2.90$$

$$I_{BQ} = \frac{V_{TH} - V_{BE(on)}}{R_{TH} + (1 + \beta)R_E} = \frac{2.90 - 0.7}{6.99 + (51)(0.985)} = 0.0384 \text{ mA}$$

$$\underline{I_{CQ} = 1.92 \text{ mA}}$$

For  $\beta = 90$ 

$$I_{BQ} = \frac{2.90 - 0.7}{6.99 + (91)(0.985)} = 0.0228 \text{ mA}$$

$$\underline{I_{CQ} = 2.05 \text{ mA}}$$

Design criterion is satisfied.

3.46

$$I_{CQ} = 1 \text{ mA} \rightarrow I_{EQ} = 1.02 \text{ mA}$$

$$V_{CEQ} = V_{CC} - I_{CQ}R_C - I_{EQ}R_E$$

$$5 = 15 - (1)(5) - (1.02)R_E \Rightarrow \underline{R_E = 4.90 \text{ k}\Omega}$$

Bias stable:

$$R_{TH} = (0.1)(1 + \beta)R_E = (0.1)(61)(4.9) = 29.9 \text{ k}\Omega$$

$$I_{BQ} = \frac{1}{60} = 0.0167 \text{ mA}$$

$$V_{TH} = \frac{1}{R_1} \cdot R_{TH} \cdot V_{CC} = I_{BQ}R_{TH} + V_{BE(on)} + I_{EQ}R_E$$

$$\frac{1}{R_1}(29.9)(15) = (0.0167)(29.9) + 0.70$$

$$+ (1.02)(4.90)$$

$$\frac{1}{R_1}(448.5) = 6.197$$

$$\underline{R_1 = 72.4 \text{ k}\Omega}, \quad \frac{72.4R_2}{72.4 + R_2} = 29.9$$

$$\underline{R_2 = 50.9 \text{ k}\Omega}$$

Check: For  $\beta = 45$ 

$$V_{TH} = \left( \frac{50.9}{50.9 + 72.4} \right) (15) = 6.19 \text{ V}$$

$$I_{BQ} = \frac{V_{TH} - V_{BE(on)}}{R_{TH} + (1 + \beta)R_E} = \frac{6.19 - 0.7}{29.9 + (46)(4.90)} = 0.0215 \text{ mA}$$

$$\underline{I_{CQ} = 0.968 \text{ mA}}, \quad \frac{\Delta I_C}{I_C} = 3.2\%$$

Check: For  $\beta = 75$ 

$$I_{BQ} = \frac{6.19 - 0.7}{29.9 + (76)(4.90)} = 0.0136 \text{ mA}$$

$$\underline{I_{CQ} = 1.02 \text{ mA}}, \quad \frac{\Delta I_C}{I_C} = 2.0\%$$

Design criterion is satisfied.

3.47

$$(a) V_{CC} \cong I_{CQ}(R_C + R_E) + V_{CEQ}$$

$$3 = (0.1)(5R_E + R_E) + 1.4 \Rightarrow \underline{R_E = 2.67 \text{ k}\Omega}$$

$$\underline{R_C = 13.3 \text{ k}\Omega}, \quad I_{BQ} = \frac{100}{120} = 0.833 \text{ }\mu\text{A}$$

$$R_{TH} = (0.1)(1 + \beta)R_E = (0.1)(121)(2.67) = 32.3 \text{ k}\Omega$$

$$V_{TH} = \frac{1}{R_1} \cdot R_{TH} \cdot V_{CC} = \frac{1}{R_1}(32.3)(3)$$

$$= I_{BQ}R_{TH} + V_{BE(on)} + (1 + \beta)I_{BQ}R_E$$

$$= (0.000833)(32.3) + 0.7 + (121)(0.000833)(2.67)$$

$$\text{which gives } \underline{R_1 = 97.3 \text{ k}\Omega}, \text{ and } \underline{R_2 = 48.4 \text{ k}\Omega}$$

$$(b) I_R \cong \frac{3}{R_1 + R_2} = \frac{3}{97.3 + 48.4} \Rightarrow 20.6 \mu\text{A}$$

$$I_{CQ} = 100 \mu\text{A}$$

$$P = (I_{CQ} + I_R)V_{CC} = (100 + 20.6)(3)$$

or

$$P = 362 \mu\text{W}$$

3.48

$$I_E = \frac{5 - V_E}{R_E} = \frac{5}{3} = 1.67 \text{ mA}$$

$$R_{TH} = R_1 \parallel R_2 = (0.1)(1 + \beta)R_E \\ = (0.1)(101)(3) = 30.3 \text{ k}\Omega$$

$$V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right)(4) - 2 = \frac{1}{R_1} \cdot R_{TH} \cdot (4) - 2$$

$$I_{BQ} = \frac{I_{EQ}}{1 + \beta} = 0.0165 \text{ mA}$$

$$5 = I_{EQ}R_E + V_{EB}(\text{on}) + I_B R_{TH} + V_{TH}$$

$$5 = (1.67)(3) + 0.7 + (0.0165)(30.3) \\ + \frac{1}{R_1}(30.3)(4) - 2$$

$$0.80 = \frac{1}{R_1}(30.3)(4) \Rightarrow R_1 = 152 \text{ k}\Omega$$

$$\frac{152R_2}{152 + R_2} = 30.3 \Rightarrow R_2 = 37.8 \text{ k}\Omega$$

3.49

$$a. R_{TH} = R_1 \parallel R_2 = 10 \parallel 20 \Rightarrow R_{TH} = 6.67 \text{ k}\Omega$$

$$V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right)(10) - 5 = \left( \frac{20}{20 + 10} \right)(10) - 5 \\ \Rightarrow V_{TH} = 1.67 \text{ V}$$

$$b. 10 = (1 + \beta)I_{BQ}R_E + V_{EB}(\text{on}) + I_{BQ}R_{TH} + V_{TH}$$

$$I_{BQ} = \frac{10 - 0.7 - 1.67}{6.67 + (61)(2)} = \frac{7.63}{128.7}$$

$$\Rightarrow I_{BQ} = 0.0593 \text{ mA}$$

$$I_{CQ} = 3.65 \text{ mA}, I_{EQ} = 3.62 \text{ mA}$$

$$V_E = 10 - I_{EQ}R_E = 10 - (3.62)(2)$$

$$V_E = 2.76 \text{ V}$$

$$V_C = I_{CQ}R_C - 10 = (3.56)(2.2) - 10$$

$$V_C = -2.17 \text{ V}$$

3.50

$$V^* - V^- \cong I_{CQ}(R_C + R_E) + V_{ECQ}$$

$$20 = (0.5)(R_C + R_E) + 8 \Rightarrow (R_C + R_E) = 24 \text{ k}\Omega$$

$$\text{Let } R_E = 10 \text{ k}\Omega \text{ then } R_C = 14 \text{ k}\Omega$$

$$\text{Let } \beta = 60 \text{ from previous problem.}$$

$$R_{TH} = (0.1)(1 + \beta)R_E = (0.1)(61)(10)$$

$$\text{Or } R_{TH} = 61 \text{ k}\Omega$$

$$I_{BQ} = \frac{0.5}{60} = 0.00833 \text{ mA}$$

$$V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right)(10) - 5 = \frac{1}{R_1} \cdot R_{TH} \cdot 10 - 5$$

Now

$$10 = (1 + \beta)I_{BQ}R_E + V_{EB}(\text{on}) + I_{BQ}R_{TH} + V_{TH}$$

$$10 = (61)(0.00833)(10) + 0.7 + (0.00833)(61) \\ + \frac{1}{R_1}(61)(10) - 5$$

$$\text{Then } R_1 = 70.0 \text{ k}\Omega \text{ and } R_2 = 474 \text{ k}\Omega$$

$$I_R \cong \frac{10}{R_1 + R_2} = \frac{10}{70 + 474} \Rightarrow 18.4 \mu\text{A}$$

So the  $40 \mu\text{A}$  current limit is met.

3.51

$$a. R_{TH} = R_1 \parallel R_2 = 35 \parallel 20 \Rightarrow R_{TH} = 12.7 \text{ k}\Omega$$

$$V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right)(7) - 5 = \left( \frac{20}{20 + 35} \right)(7) - 5 \\ \Rightarrow V_{TH} = -2.45 \text{ V}$$

b.

$$I_{BQ} = \frac{V_{TH} - V_{BE}(\text{on}) - (-10)}{R_{TH} + (1 + \beta)R_E}$$

$$= \frac{-2.45 - 0.7 + 10}{12.7 + (76)(0.5)}$$

$$\Rightarrow I_{BQ} = 0.135 \text{ mA}$$

$$I_{CQ} = 10.1 \text{ mA}, I_{EQ} = 10.3 \text{ mA}$$

$$V_{CEQ} = 20 - I_{CQ}R_C - I_{EQ}R_E$$

$$= 20 - (10.1)(0.8) - (10.3)(0.5)$$

$$V_{CEQ} = 6.77 \text{ V}$$

c.

$$R_2 = 20 + 5\% = 21 \text{ k}\Omega$$

$$R_1 = 35 - 5\% = 33.25 \text{ k}\Omega$$

$$R_E = 0.5 - 5\% = 0.475 \text{ k}\Omega$$

$$R_{TH} = R_1 \parallel R_2 = 21 \parallel 33.25 = 12.9 \text{ k}\Omega$$

$$V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right)(7) - 5$$

$$= \left( \frac{21}{21 + 33.25} \right)(7) - 5 = -2.29 \text{ V}$$

$$I_{BQ} = \frac{-2.29 - 0.7 - (-10)}{12.9 + (76)(0.475)} = 0.143 \text{ mA}$$

$$I_{CQ} = 10.7 \text{ mA}, I_{EQ} = 10.9 \text{ mA}$$

$$\text{For } R_C = 0.8 + 5\% = 0.84 \text{ k}\Omega$$

$$V_{CEQ} = 20 - (10.7)(0.84) - (10.9)(0.475)$$

$$\Rightarrow V_{CEQ} = 5.83 \text{ V}$$

For  $R_C = 0.8 - 5\% = 0.76 \text{ k}\Omega$

$$V_{CEQ} = 20 - (10.7)(0.76) - (10.9)(0.475)$$

$$\Rightarrow V_{CEQ} = 6.69 \text{ V}$$

$$R_2 = 20 - 5\% = 19 \text{ k}\Omega$$

$$R_1 = 35 + 5\% = 36.75 \text{ k}\Omega$$

$$R_E = 0.5 + 5\% = 0.525 \text{ k}\Omega$$

$$R_{TH} = R_1 || R_2 = 19 || 36.75 = 12.5 \text{ k}\Omega$$

$$V_{TH} = \left( \frac{19}{19 + 36.75} \right) (7) - 5 = -2.61 \text{ V}$$

$$I_{BQ} = \frac{-2.61 - 0.7 - (-10)}{12.5 + (76)(0.525)} = 0.128 \text{ mA}$$

$$I_{CQ} = 9.58 \text{ mA}, \quad I_{EQ} = 9.70 \text{ mA}$$

For  $R_C = 0.84 \text{ k}\Omega$

$$V_{CEQ} = 20 - (9.58)(0.84) - (9.70)(0.525)$$

$$\Rightarrow V_{CEQ} = 6.86 \text{ V}$$

For  $R_C = 0.76 \text{ k}\Omega$

$$V_{CEQ} = 20 - (9.58)(0.76) - (9.70)(0.525)$$

$$\Rightarrow V_{CEQ} = 7.63 \text{ V}$$

So  $9.58 \leq I_{CQ} \leq 10.7 \text{ mA}$

and

$$5.83 \leq V_{CEQ} \leq 7.63 \text{ V}$$

3.52

a.  $R_{TH} = 500 \text{ k}\Omega || 500 \text{ k}\Omega || 70 \text{ k}\Omega = 250 \text{ k}\Omega || 70 \text{ k}\Omega$

$$\Rightarrow R_{TH} = 54.7 \text{ k}\Omega$$

$$\frac{5 - V_{TH}}{500} + \frac{3 - V_{TH}}{500} = \frac{V_{TH} - (-5)}{70}$$

$$\frac{5}{500} + \frac{3}{500} - \frac{5}{70} = V_{TH} \left( \frac{1}{500} + \frac{1}{500} + \frac{1}{70} \right)$$

$$-0.0554 = V_{TH}(0.0183)$$

$$V_{TH} = -3.03 \text{ V}$$

b.

$$I_{BQ} = \frac{V_{TH} - V_{BE(\text{on})} - (-5)}{R_{TH} + (1 + \beta)R_E}$$

$$= \frac{-3.03 - 0.7 + 5}{54.7 + (101)(5)}$$

$$I_{BQ} = 0.00227 \text{ mA}$$

$$I_{CQ} = 0.227 \text{ mA}, \quad I_{EQ} = 0.229$$

$$V_{CEQ} = 20 - (0.227)(50) - (0.229)(5)$$

$$V_{CEQ} = 7.51 \text{ V}$$

3.53

$$R_{TH} = 30 || 60 || 20 \Rightarrow R_{TH} = 10 \text{ k}\Omega$$

$$\frac{5 - V_{TH}}{30} + \frac{5 - V_{TH}}{60} = \frac{V_{TH}}{20}$$

$$\left( \frac{5}{30} + \frac{5}{60} \right) = V_{TH} \left( \frac{1}{30} + \frac{1}{60} + \frac{1}{20} \right)$$

$$V_{TH} = 2.5 \text{ V}$$

For  $\beta = 100$

$$I_{BQ} = \frac{V_{TH} - V_{BE(\text{on})} - (-5)}{R_{TH} + (1 + \beta)R_E}$$

$$= \frac{2.5 - 0.7 + 5}{10 + (101)(0.2)}$$

$$I_{BQ} = 0.225 \text{ mA}$$

$$I_{CQ} = 22.5 \text{ mA}, \quad I_{EQ} = 22.7 \text{ mA}$$

$$V_{CEQ} = 15 - (22.5)(0.5) - (22.7)(0.2)$$

$$V_{CEQ} = -0.79 \text{ V} \text{ In saturation}$$

$$\Rightarrow V_{CEQ} = 0.2 \text{ V}$$

$$V_E = V_{TH} - I_{BQ}R_{TH} - V_{BE(\text{on})}$$

$$= 2.5 - (0.225)(10) - 0.7$$

$$V_E = -0.45 \text{ V} \Rightarrow V_C = -0.45 + 0.2 = -0.25 \text{ V}$$

$$I_{CQ} = \frac{10 - (-0.25)}{0.5} \Rightarrow I_{CQ} = 20.5 \text{ mA}$$

3.54

$$R_{TH} = R_1 || R_2 = 100 || 40 = 28.6 \text{ k}\Omega$$

$$V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right) (10) = \left( \frac{40}{40 + 100} \right) (10) = 2.86 \text{ V}$$

$$I_{B1} = \frac{V_{TH} - V_{BE(\text{on})}}{R_{TH} + (1 + \beta)R_{E1}} = \frac{2.86 - 0.7}{28.6 + (121)(1)}$$

$$I_{B1} = 0.0144 \text{ mA}$$

$$I_{C1} = 1.73 \text{ mA}, \quad I_{E1} = 1.75 \text{ mA}$$

$$\frac{10 - V_{B2}}{3} = I_{C1} + I_{B2}$$

$$I_{E2} = \frac{V_{B2} - V_{BE(\text{on})} - (-10)}{5}$$

$$\frac{10 - V_{B2}}{3} = I_{C1} + \frac{V_{B2} - 0.7 + 10}{(121)(5)}$$

$$\frac{10}{3} - 1.73 - \frac{9.3}{605} = V_{B2} \left( \frac{1}{3} + \frac{1}{(121)(5)} \right)$$

$$1.59 = V_{B2}(0.335) \Rightarrow V_{B2} = 4.75 \text{ V}$$

$$I_{E2} = \frac{4.75 - 0.7 - (-10)}{5} \Rightarrow I_{E2} = 2.81 \text{ mA}$$

$$I_{B2} = 0.0232 \text{ mA}$$

$$I_{C2} = 2.79 \text{ mA}$$

$$V_{CEQ1} = 4.75 - (1.75)(1) \Rightarrow V_{CEQ1} = 3.0 \text{ V}$$

$$V_{CEQ2} = 10 - (4.75 - 0.7) \Rightarrow V_{CEQ2} = 5.95 \text{ V}$$

3.55

$$V_{E1} = -0.7$$

$$I_{R1} = \frac{-0.7 - (-5)}{20} = 0.215 \text{ mA}$$

$$V_{E2} = -0.7 - 0.7 = -1.4$$

$$I_{E2} = \frac{-1.4 - (-5)}{1} \Rightarrow I_{E2} = 3.6 \text{ mA}$$

$$I_{B2} = 0.0444 \text{ mA}$$

$$I_{C2} = 3.56 \text{ mA}$$

$$I_{E1} = I_{R1} + I_{B2} = 0.215 + 0.0444$$

$$I_{E1} = 0.259 \text{ mA}$$

$$I_{B1} = 0.00320 \text{ mA}$$

$$I_{C1} = 0.256 \text{ mA}$$

3.56

Current through  $V^-$  source =  $I_{E1} + I_{E2}$  and

$$I_{E1} = I_{E2} = (1 + \beta)I_{B1} = (51)(8.26) \mu\text{A}$$

So total current =  $2(51)(8.26) \mu\text{A} = 843 \mu\text{A}$

$$P^- = I \cdot |V^-| = (0.843)(5) \Rightarrow P^- = 4.22 \text{ mW}$$

(From  $V^-$  source)

From Example 3.15,  $I_Q = 0.413 \text{ mA}$

$$\text{So } I_{C0} = \left(\frac{50}{51}\right)(0.413) = 0.405 \text{ mA}$$

$$P^+ = I \cdot V^+ = (0.405)(5) \Rightarrow P^+ = 2.03 \text{ mW}$$

(From  $V^+$  source)

3.57

$$R_{TH} = R_1 \parallel R_2 = 50 \parallel 100 = 33.3 \text{ k}\Omega$$

$$V_{TH} = \left(\frac{R_2}{R_1 + R_2}\right)(10) - 5$$

$$= \left(\frac{100}{100 + 50}\right)(10) - 5 = 1.67 \text{ V}$$

$$5 = I_{E1} R_{E1} + V_{EB(\text{on})} + I_{B1} R_{TH} + V_{TH}$$

$$I_{E1} = \left(\frac{101}{100}\right)(0.8) = 0.808 \text{ mA}$$

$$I_{B1} = 0.008 \text{ mA}$$

$$5 = (0.808)R_{E1} + 0.7 + (0.008)(33.3) + 1.67$$

$$R_{E1} = 2.93 \text{ k}\Omega$$

$$V_{E1} = 5 - (0.808)(2.93) = 2.63 \text{ V}$$

$$V_{C1} = V_{E1} - V_{ECQ1} = 2.63 - 3.5 = -0.87 \text{ V}$$

$$V_{E2} = -0.87 - 0.70 = -1.57 \text{ V}$$

$$I_{E2} = \frac{-1.57 - (-5)}{R_{E2}} = 0.808 \Rightarrow R_{E2} = 4.25 \text{ k}\Omega$$

$$V_{CEQ2} = 4 \Rightarrow V_{C2} = -1.57 + 4 = 2.43 \text{ V}$$

$$R_{C2} = \frac{5 - 2.43}{0.8} \Rightarrow R_{C2} = 3.21 \text{ k}\Omega$$

$$I_{RC1} = I_{C1} - I_{B2} = 0.8 - 0.008 = 0.792 \text{ mA}$$

$$R_{C1} = \frac{-0.87 - (-5)}{0.792} \Rightarrow R_{C1} = 5.21 \text{ k}\Omega$$



## Chapter 4

### Exercise Solutions

E4.1

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.25}{0.026} \Rightarrow g_m = 9.62 \text{ mA/V}$$

$$r_\pi = \frac{V_T \beta}{I_{CQ}} = \frac{(0.026)(120)}{0.25} \Rightarrow r_\pi = 12.5 \text{ k}\Omega$$

$$r_o = \frac{V_A}{I_{CQ}} = \frac{150}{0.25} \Rightarrow r_o = 600 \text{ k}\Omega$$

E4.2

$$r_o = \frac{V_A}{I_{CQ}} \Rightarrow I_{CQ} = \frac{V_A}{r_o} = \frac{75}{200 \text{ k}\Omega}$$

$$\Rightarrow I_{CQ} = 0.375 \text{ mA}$$

E4.3

$$I_{BQ} = \frac{V_{BB} - V_{BE(\text{on})}}{R_B} = \frac{0.92 - 0.7}{100}$$

$$\Rightarrow I_{BQ} = 0.0022 \text{ mA}$$

$$I_{CQ} = (150)(0.0022) = 0.33 \text{ mA}$$

a.  $g_m = \frac{I_{CQ}}{V_T} = \frac{0.33}{0.026} \Rightarrow g_m = 12.7 \text{ mA/V}$

$$r_\pi = \frac{V_T \beta}{I_{CQ}} = \frac{(0.0026)(150)}{0.33} \Rightarrow r_\pi = 11.8 \text{ k}\Omega$$

$$r_o = \frac{V_A}{I_{CQ}} = \frac{200}{0.33} \Rightarrow r_o = 606 \text{ k}\Omega$$

b.  $v_o = -g_m v_\pi (r_o \parallel R_C), \quad v_\pi = \left( \frac{r_\pi}{r_\pi + R_B} \right) v_s$

$$A_v = \frac{v_o}{v_s} = -g_m \left( \frac{r_\pi}{r_\pi + R_B} \right) (r_o \parallel R_C)$$

$$= -(12.7) \left( \frac{11.8}{11.8 + 100} \right) (606 \parallel 15)$$

$$= -(12.7)(0.1055)(14.64)$$

$$\Rightarrow A_v = -19.6$$

E4.4

$$g_m = \frac{I_{CQ}}{V_T}$$

a.  $I_{BQ} = \frac{V_{BB} - V_{EB(\text{on})}}{R_B} = \frac{1.145 - 0.70}{50}$

$$\Rightarrow I_{BQ} = 0.0089 \text{ mA}$$

$$I_{CQ} = (90)(0.0089) \Rightarrow I_{CQ} = 0.801 \text{ mA}$$

$$g_m = \frac{0.801}{0.026} \Rightarrow g_m = 30.8 \text{ mA/V}$$

$$r_\pi = \frac{V_T \beta}{I_{CQ}} = \frac{(0.0026)(90)}{0.801} \Rightarrow r_\pi = 2.92 \text{ k}\Omega$$

$$r_o = \frac{V_A}{I_{CQ}} = \frac{120}{0.801} \Rightarrow r_o = 150 \text{ k}\Omega$$

b.  $v_o = g_m v_\pi (r_o \parallel R_C), \quad v_\pi = - \left( \frac{r_\pi}{r_\pi + R_B} \right) v_s$

$$A_v = \frac{v_o}{v_s} = -g_m \left( \frac{r_\pi}{r_\pi + R_B} \right) (r_o \parallel R_C)$$

$$= -(30.8) \left( \frac{2.92}{2.92 + 50} \right) (150 \parallel 2.5)$$

$$= -(30.8)(0.055)(2.46)$$

$$\Rightarrow A_v = -4.17$$

E4.5

$$R_{TH} = 250 \parallel 75 = 57.7 \text{ k}\Omega$$

$$V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right) (5) = \left( \frac{75}{75 + 250} \right) (5) = 1.154$$

$$I_{BQ} = \frac{1.154 - 0.7}{57.7 + (121)(0.6)} = 3.48 \mu\text{A}$$

$$I_{CQ} = 0.418 \text{ mA}$$

a.  $r_\pi = \frac{(120)(0.026)}{0.418} = 7.46 \text{ k}\Omega$

$$g_m = \frac{0.418}{0.026} = 16.08 \text{ mA/V}$$

$$V_o = -g_m V_\pi R_C$$

$$R_{ib} = r_\pi + (1 + \beta) R_E = 7.46 + (121)(0.6) = 80.1 \text{ k}\Omega$$

$$R_1 \parallel R_2 = 250 \parallel 75 = 57.7 \text{ k}\Omega$$

$$R_1 \parallel R_2 \parallel R_{ib} = 57.7 \parallel 80.1 = 33.54 \text{ k}\Omega$$

$$V_s' = \left( \frac{R_1 \parallel R_2 \parallel R_{ib}}{R_1 \parallel R_2 \parallel R_{ib} + R_s} \right) V_s = \left( \frac{33.54}{33.54 + 0.5} \right) V_s$$

$$V_s' = (0.985) V_s$$

$$V_s' = V_\pi \left[ 1 + \left( \frac{1 + \beta}{r_\pi} \right) R_E \right]$$

Then

$$A_v = (0.985)(-8.39) = -8.27$$

b.  $R_{ib} = r_\pi + (1 + \beta)(R_E) = 7.46 + (121)(0.6)$   
 $\Rightarrow R_{ib} = 80.1 \text{ k}\Omega$

E4.6

As a first approximation,

$$A_v \approx - \frac{R_C}{R_E}$$

Resulting gain is always smaller than this value. The effect of  $R_s$  is very small.

Set  $\frac{R_C}{R_E} = 10$

$$5 \cong I_C(R_C + R_E) + V_{CEQ}$$

$$5 = 0.5(R_C + R_E) + 2.5$$

So that  $R_E = 0.454 \text{ k}\Omega$  and  $R_C = 4.54 \text{ k}\Omega$

$$I_{BQ} = \frac{0.5}{100} = 0.005 \text{ mA}$$

$$R_{TH} = (0.1)(1 + \beta)R_E = (0.1)(101)(0.454) = 4.59 \text{ k}\Omega$$

$$V_{TH} = \left(\frac{R_2}{R_1 + R_2}\right) \cdot V_{CC} = \frac{1}{R_1} \cdot R_{TH} \cdot V_{CC} = \frac{1}{R_1}(4.59)(5)$$

$$\text{or } V_{TH} = \frac{23}{R_1}$$

$$V_{TH} = I_{BQ}R_{TH} + V_{BE}(\text{on}) + (1 + \beta)I_{BQ}R_E$$

$$\frac{23}{R_1} = (0.005)(4.59) + 0.7 + (101)(0.005)(0.454)$$

which yields,  $R_1 = 24.1 \text{ k}\Omega$  and  $R_2 = 5.67 \text{ k}\Omega$

E4.7

dc analysis

$$R_{TH} = R_1 \parallel R_2 = 15 \parallel 85 = 12.75$$

$$V_{TH} = \left(\frac{R_2}{R_1 + R_2}\right) V_{CC} = \left(\frac{85}{85 + 15}\right)(12)$$

$$V_{TH} = 10.2 \text{ V}$$

$$I_{BQ} = \frac{12 - 0.7 - V_{TH}}{R_{TH} + (1 + \beta)R_E} = \frac{12 - 0.7 - 10.2}{12.75 + (101)(0.5)} = \frac{1.1}{63.25} = 0.0174$$

$$I_{CQ} = 1.74 \text{ mA}$$

ac analysis

$$V_o = h_{fe}I_b(R_C \parallel R_L)$$

$$I_b = \frac{-V_s}{h_{ie} + (1 + h_{fe})R_E}$$

$$A_v = \frac{-h_{fe}(R_C \parallel R_L)}{h_{ie} + (1 + h_{fe})R_E}$$

For  $I_{CQ} = 1.7 \text{ mA}$

$$h_{fe}(\text{max}) = 110 \quad h_{fe}(\text{min}) = 70$$

$$h_{ie}(\text{max}) = 2 \text{ k}\Omega \quad h_{ie}(\text{min}) = 1.1 \text{ k}\Omega$$

$$A_v(\text{max}) = \frac{-110(4 \parallel 2)}{2 + (111)(0.5)} = -2.54$$

$$A_v(\text{min}) = \frac{-70(4 \parallel 2)}{1.1 + (71)(0.5)} = -2.54$$

E4.8

First approximation,  $A_v = -\frac{R_C}{R_E}$  which predicts a

low value. Set  $\frac{R_C}{R_E} = 9$ . Now

$$V_{CC} \cong I_{CQ}(R_C + R_E) + V_{ECQ}$$

$$7.5 = (0.6)(9R_E + R_E) + 3.75$$

So  $R_E = 0.625 \text{ k}\Omega$  and  $R_C = 5.62 \text{ k}\Omega$

$$R_{TH} = (0.1)(1 + \beta)R_E = (0.1)(101)(0.625) = 6.31 \text{ k}\Omega$$

$$V_{TH} = \frac{1}{R_1} \cdot R_{TH} \cdot V_{CC} = \frac{1}{R_1}(6.31)(7.5)$$

$$V_{CC} = (1 + \beta)I_{BQ}R_E + V_{EB}(\text{on}) + I_{BQ}R_{TH} + V_{TH}$$

$$I_{BQ} = \frac{0.6}{100} = 0.006 \text{ mA}$$

$$7.5 = (101)(0.006)(0.625) + 0.7 + (0.006)(6.31) + \frac{1}{R_1}(6.31)(7.5)$$

Then  $R_1 = 7.40 \text{ k}\Omega$  and  $R_2 = 42.8 \text{ k}\Omega$

E4.9

dc analysis

$$I_{BQ} = \frac{10 - 0.7}{100 + (101)(20)} = 0.00439 \text{ mA}$$

$$I_{CQ} = 0.439 \text{ mA} \quad I_{EQ} = 0.443 \text{ mA}$$

$$r_\pi = \frac{V_T \beta}{I_{CQ}} = \frac{(0.026)(100)}{0.439} = 5.92 \text{ k}\Omega$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.439}{0.026} = 16.88 \text{ mA/V}$$

$$r_o = \frac{V_A}{I_{CQ}} = \frac{100}{0.439} = 228 \text{ k}\Omega$$

$$(a) V_o = -g_m V_\pi (r_o \parallel R_C)$$

$$V_\pi = V_s' = \left(\frac{R_B \parallel r_\pi}{R_B \parallel r_\pi + R_s}\right) \cdot V_s$$

$$R_B \parallel r_\pi = 100 \parallel 5.92 = 5.59 \text{ k}\Omega$$

Then

$$V_\pi = \left(\frac{5.59}{5.59 + 0.5}\right) \cdot V_s = 0.918 V_s$$

Then

$$A_v = -(161.7)(0.918) = -148$$

$$b. R_{in} = R_B \parallel r_\pi = (100) \parallel (5.92)$$

$$\Rightarrow R_{in} = 5.59 \text{ k}\Omega$$

$$R_o = R_C \parallel r_o = 10 \parallel 228 \Rightarrow R_o = 9.58 \text{ k}\Omega$$

E4.10

$$A_v = \frac{-\beta R_C}{r_\pi + (1 + \beta)R_E} = -(0.95) \left(\frac{R_C}{R_E}\right) = -(0.95) \left(\frac{2}{0.4}\right)$$

or  $A_v = -4.75$

Assume  $r_\pi = 1.2 \text{ k}\Omega$  from Example 4.5. Then

$$\frac{-\beta(2)}{1.2 + (1 + \beta)(0.4)} = -4.75$$

which yields  $\beta = 76$

E4.11

dc analysis:  $V_{TH} = 0, R_{TH} = R_1 \parallel R_2 = 10 \text{ k}\Omega$

$$I_{BQ} = \frac{5 - 0.7}{10 + (126)(5)} = 0.00672$$

$$I_{CQ} = 0.84 \text{ mA}$$

$$r_{\pi} = \frac{V_T \beta}{I_{CQ}} = \frac{(0.026)(125)}{0.84} = 3.87 \text{ k}\Omega$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.84}{0.026} = 32.3 \text{ mA/V}$$


$$r_o = \frac{V_A}{I_{CQ}} = \frac{200}{0.84} = 238 \text{ k}\Omega$$

a.  $v_o = -g_m v_{\pi} (r_o \parallel R_C \parallel R_L), v_{\pi} = v_s$

$$A_v = -g_m (r_o \parallel R_C \parallel R_L) = -(32.3)(238 \parallel 2.3 \parallel 5)$$

$$A_v = -(32.3)(1.56) \Rightarrow \underline{A_v = -50.4}$$

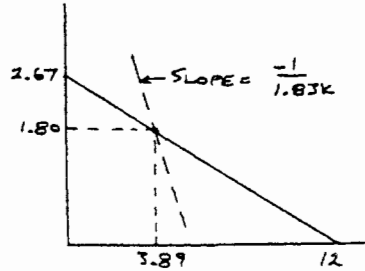b.  $R_0 = r_o \parallel R_C \Rightarrow \underline{R_0 = 2.28 \text{ k}\Omega}$



$$I_{BQ} = \frac{12 - 0.7 - 10.2}{12.75 + (121)(0.5)} = \frac{1.1}{73.25}$$

$$I_{BQ} = 0.0150$$

$$I_{CQ} = 1.80, I_{EQ} = 1.82$$

$$\Rightarrow V_{ECQ} = 3.89$$


b. For  $\Delta I_C = 1.8 \Rightarrow \Delta V_{EC} = (1.8)(1.83) = 3.29$

For  $\Delta V_{EC} = -3.29 \Rightarrow \Delta V_{CE} = 3.89 - 3.29 = 0.6$

$$\Rightarrow \text{Max. symmetrical swing}$$

$$= 2 \times (3.29) = \underline{6.58 \text{ V peak-to-peak}}$$

E4.12

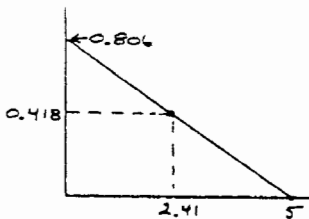

$$V_{CEQ} = 5 - (0.418)(5.6) - \left(\frac{121}{120}\right)(0.418)(0.6)$$

$$= 5 - 2.34 - 0.253$$

$$V_{CEQ} = 2.41$$

$$\Delta V_{CE} \text{ variation } (2.41 - 0.5)2 = 3.82 \text{ V}$$

peak-to-peak

E4.13

a. dc load line:

$$V_{EC} = V_{CC} - I_E R_E - I_C R_C$$

$$V_{EC} = 12 - I_C (R_E + R_C) = 12 - I_C (4.5)$$

ac load line:

$$v_{ec} \approx -i_C (R_E + R_C \parallel R_L)$$

$$v_{ec} = -i_C (0.5 + 4 \parallel 2) = -i_C (1.83)$$

E4.14


dc load line:

$$V_{CE} \approx (10 + 10) - I_C (R_C + R_E)$$

$$V_{CE} = 20 - I_C (10 + R_E)$$

$$v_{ce} = -i_C R_C = -i_C (10)$$

ac load line:

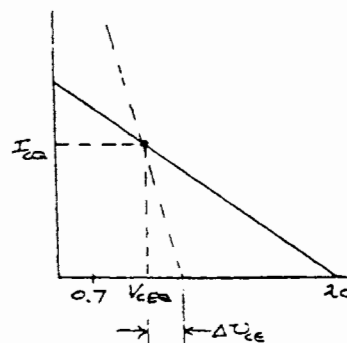

$$\Delta v_{ce} = V_{CEQ} - 0.7 = \Delta i_C (10) = I_{CQ} (10)$$

$$\text{So } V_{CEQ} - 0.7 = I_{CQ} (10)$$

We have

$$V_{CEQ} = 20 - I_{CQ} (10 + R_E)$$

$$I_{CQ} (10) + 0.7 = 20 - I_{CQ} (10 + R_E) \quad (1)$$

$$I_{BQ} = \frac{10 - 0.7}{100 + (101)R_E} \Rightarrow I_{CQ} = \frac{(100)(9.3)}{100 + (101)R_E} \quad (2)$$

From (1)

$$I_{CQ}[10 + 10 + R_E] = 20 - 0.7$$

Substitute (2)

$$\left[ \frac{(100)(9.3)}{100 + (101)R_E} \right] (20 + R_E) = 19.3$$

$$930(20 + R_E) = 19.3[100 + (101)R_E]$$

$$18,600 + 930R_E = 1930 + 1949.3R_E$$

$$16,670 = 1019.3R_E \Rightarrow R_E = 16.35 \text{ k}\Omega$$

So

$$I_{CQ} = \frac{(100)(9.3)}{100 + (101)(16.35)} \Rightarrow I_{CQ} = 0.531 \text{ mA}$$

$$V_{CEQ} = 20 - (0.531)(10 + 16.35) \Rightarrow V_{CEQ} = 6.0 \text{ V}$$

$$\Delta v_{CE} = V_{CEQ} - 0.7 = 6 - 0.7 = 5.3$$

Max symmetrical swing

$$2 \times (5.3) = \underline{10.6 \text{ V peak-to-peak}}$$

E4.15


$$a. \quad I_{BQ} = \frac{5 - 0.7}{10 + (126)(5)} = 0.00672$$

$$I_{CQ} = 0.84 \text{ mA}, \quad I_{EQ} = 0.847 \text{ mA}$$

$$r_o = \frac{V_A}{I_{CQ}} = \frac{200}{0.84} = 238 \text{ k}\Omega$$

$$V_{CEQ} = 10 - (0.84)(2.3) - (0.847)(5) \\ = 10 - 1.932 - 4.235$$

$$V_{CEQ} = 3.83 \text{ V}$$

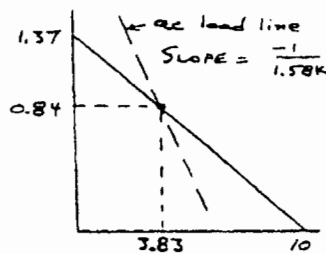

dc load line

$$V_{CE} \approx 10 - I_C(7.3)$$

ac load line

$$v_{ce} = -i_c(R_C \parallel R_L) = -i_c(2.3 \parallel 5) = -i_c(1.58) \\ \text{(neglecting } r_o)$$

$$b. \quad \Delta i_c = 0.84$$

$$\Rightarrow \Delta v_{CE} = (0.84)(1.58) = 1.33 \text{ V}$$

$$V_{CE}(\text{min}) = 3.83 - 1.33 = 2.5 \text{ V}$$

$$V_{CE}(\text{max}) = 3.83 + 1.33 = 5.16 \text{ V}$$

So max symmetrical swing

$$= 2 \times (1.33) = \underline{2.66 \text{ V peak-to-peak}}$$

E4.16

$$a. \quad V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right) (12). \quad V_{TH} = \frac{1}{R_1} (R_{TH})(12)$$

$$R_{TH} = (0.1)(1 + \beta)R_E = (0.1)(121)R_E$$

$$= 12.1R_E = 12.1 \text{ k}\Omega$$

$$I_{BQ} = \frac{12 - 0.7 - V_{TH}}{R_{TH} + (1 + \beta)R_E} = \frac{11.3 - \frac{1}{R_1}(12.1)(12)}{12.1 + (121)(1)}$$

$$I_{CQ} = 1.6 \Rightarrow I_{BQ} = \frac{1.6}{120} = 0.01333 \text{ mA}$$

$$0.01333 = \frac{11.3 - \frac{1}{R_1}(145.2)}{133.1}$$

$$\frac{1}{R_1}(145.2) = 11.3 - (0.01333)(133.1)$$

$$\Rightarrow R_1 = 15.24 \text{ k}\Omega$$

$$\frac{R_1 R_2}{R_1 + R_2} = 12.1 = \frac{15.24 R_2}{15.24 + R_2}$$

$$(12.1)(15.24) = (15.24 - 12.1)R_2$$


$$\Rightarrow R_2 = 58.7 \text{ k}\Omega$$

$$V_{ECQ} = 12 - (16)(4) - (1.61)(1) \Rightarrow V_{ECQ} = 3.99 \text{ V}$$

$$b. \quad v_o = g_m v_{\pi} (R_C \parallel R_L) = -g_m (R_C \parallel R_L) v_{ec} = -v_{ec}$$

$$i_c = g_m v_{\pi} = -g_m v_{ec}$$
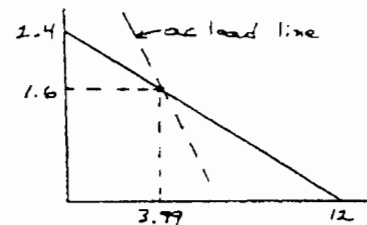
$$\text{or } -v_{ec} = i_c (R_C \parallel R_L)$$



$$\text{Want } \Delta i_c = 1.6 - 0.1 = 1.5$$

$$\Delta v_{ec} = 3.99 - 0.5 = 3.49$$

$$\frac{\Delta v_{ec}}{\Delta i_c} = \frac{3.49}{1.5} = 2.327 \text{ k}\Omega = R_C \parallel R_L$$

$$\frac{R_C R_L}{R_C + R_L} = \frac{4 R_L}{4 + R_L} = 2.327$$

$$(4 - 2.327)R_L = (4)(2.327) \Rightarrow R_L = 5.56 \text{ k}\Omega$$

E4.17

$$R_{TH} = R_1 \parallel R_2 = 25 \parallel 50 = 16.7 \text{ k}\Omega$$

$$V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right) V_{CC} = \left( \frac{50}{50 + 25} \right) (5)$$

$$V_{TH} = 3.33 \text{ V}$$

$$I_{BQ} = \frac{V_{BB} - V_{BE}(\text{on})}{R_{TH} + (1 + \beta)R_E} = \frac{3.33 - 0.70}{16.7 + (121)(1)}$$

$$= \frac{2.63}{137.7}$$

$$\Rightarrow I_{BQ} = 0.0191$$

$$I_{CQ} = 2.29 \text{ mA}$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{2.29}{0.026} = 88.1 \text{ mA/V}$$

$$r_\pi = \frac{V_T \beta}{I_{CQ}} = \frac{(0.026)(120)}{2.29} = 1.36 \text{ k}\Omega$$

$$r_o = \frac{V_A}{I_{CQ}} = \frac{100}{2.29} = 43.7 \text{ k}\Omega$$

a.

$$V'_s = \left( \frac{R_1 \parallel R_2 \parallel R_{ib}}{R_1 \parallel R_2 \parallel R_{ib} + R_s} \right) \cdot V_s$$

$$R_{ib} = r_\pi + (1 + \beta)(R_E \parallel r_o) = (1.36) + (121)(1 \parallel 43.7) \Rightarrow$$

$$R_{ib} = 120 \text{ k}\Omega \text{ and } R_1 \parallel R_2 = 16.7 \text{ k}\Omega$$

$$\text{Then } R_1 \parallel R_2 \parallel R_{ib} = 16.7 \parallel 120 = 14.7 \text{ k}\Omega$$

Then

$$V'_s = \left( \frac{14.7}{14.7 + 0.5} \right) \cdot V_s = (0.967)V_s$$

Now

$$V_o = \left( \frac{V_\pi}{r_\pi} + g_m V_\pi \right) (R_E \parallel r_o) = V_\pi \left( \frac{1 + \beta}{r_\pi} \right) R_E \parallel r_o$$

$$V_\pi = \frac{V'_s}{1 + \left( \frac{1 + \beta}{r_\pi} \right) R_E \parallel r_o} = \frac{(0.967)V_s}{1 + \left( \frac{1 + \beta}{r_\pi} \right) R_E \parallel r_o}$$

So

$$\frac{V_o}{V_s} = \frac{(0.967) \left( \frac{1 + \beta}{r_\pi} \right) R_E \parallel r_o}{1 + \left( \frac{1 + \beta}{r_\pi} \right) R_E \parallel r_o} = \frac{(0.967)(1 + \beta) R_E \parallel r_o}{r_\pi + (1 + \beta) R_E \parallel r_o}$$

$$R_E \parallel r_o = 1 \parallel 43.7 = 0.978 \text{ k}\Omega$$

Then

$$A_v = \frac{(0.967)(121)(0.978)}{1.36 + (121)(0.978)} \Rightarrow A_v = 0.956$$

b.  $R_{ib} = r_\pi + (1 + \beta) R_E \parallel r_o = 1.36 + (121)(0.978)$   
 $\Rightarrow R_{ib} = 120 \text{ k}\Omega$

(c)

$$R_o = R_E \parallel r_o \parallel \frac{r_\pi + R_1 \parallel R_2 \parallel R_s}{1 + \beta} = 1 \parallel 43.7 \parallel \frac{1.36 + 16.7 \parallel 0.5}{121}$$

which yields

$$R_o = 15.1 \Omega$$

E4.18

$$V_{CEQ} = 5 \text{ V} \Rightarrow I_{EQ} = \frac{5}{2} = 2.5 \text{ mA}$$

$$I_{BQ} = \frac{2.5}{101} = 0.0248 \text{ mA}$$

$$V_{TH} = I_{BQ} R_{TH} + V_{BE(on)} + (1 + \beta) I_{BQ} R_E$$

$$R_{in} = R_{TH} \parallel [r_\pi + (1 + \beta) R_E]$$

$$r_\pi = 1.05 \text{ k}\Omega$$

$$65 = R_{TH} \parallel 203 = \frac{R_{TH} \cdot 203}{R_{TH} + 203}$$

$$\Rightarrow R_{TH} = 95.6 \text{ k}\Omega$$

$$\frac{1}{R_1} (95.6)(10) = (0.0248)(95.6) + 0.7 + 2.5(2)$$

$$= 8.07$$

$$R_1 = 118 \text{ k}\Omega, \quad \frac{118 R_2}{118 + R_2} = 95.6$$

$$R_2 = 504 \text{ k}\Omega$$

$$R_{in} = 65 \text{ k}\Omega$$

$$V'_s = \left( \frac{R_{in}}{R_{in} + R_s} \right) \cdot V_s = \left( \frac{65}{65 + 0.5} \right) \cdot V_s = 0.992 V_s$$

Then

$$A_v = \frac{(0.992)(1 + \beta) R_E}{r_\pi + (1 + \beta) R_E} = \frac{(0.992)(101)(2)}{1.05 + (101)(2)} \Rightarrow$$

$$A_v = 0.987$$

Neglecting  $R_s$ ,  $A_v = 0.995$

$$R_o = R_E \parallel \frac{r_\pi + R_1 \parallel R_2 \parallel R_s}{1 + \beta} = 2 \parallel \frac{1.05 + 95.6 \parallel 0.5}{101}$$

or

$$R_o = 15.2 \Omega$$

$$\text{Neglecting } R_s, \quad R_o = 2 \parallel \frac{1.05}{102} \Rightarrow R_o = 10.3 \Omega$$

E4.19

$$V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right) (10) - 5$$

$$\beta = 100, \quad V_A = 125 \text{ V}, \quad V_{BE(on)} = 0.7 \text{ V}$$


$$I_{CQ} = 0.75 \text{ mA}$$

$$\text{Then } r_o = \frac{125}{0.75} = 167 \text{ k}\Omega$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{(100)(0.026)}{0.75} \Rightarrow r_\pi = 3.47 \text{ k}\Omega$$

$$I_{BQ} = \frac{V_{TH} - V_{BE(on)} - (-5)}{R_{TH} + (1 + \beta) R_E}$$

$$I_{CQ} = \beta I_{BQ}$$

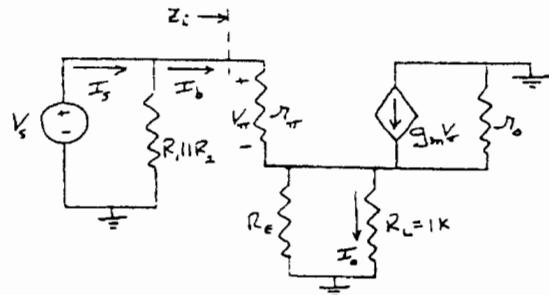

$$Z_i = r_\pi + (1 + \beta)[R_E \parallel R_L \parallel r_o]$$

$$I_o = \left( \frac{R_E \parallel r_o}{R_E \parallel r_o + R_L} \right) (1 + \beta) I_b$$

$$I_b = \left( \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + Z_i} \right) I_S$$

$$A_I = \frac{I_o}{I_S} = \left( \frac{R_E \parallel r_o}{R_E \parallel r_o + R_L} \right) (1 + \beta) \left( \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + Z_i} \right)$$

Assume that  $R_E \parallel r_o \approx R_E$

$$R_1 \parallel R_2 = (0.1)(1 + \beta) R_E = (0.1)(101) R_E = 10.1 R_E$$

Assume  $R_L = 1 \text{ k}\Omega$

Then

$$A_I = 15 = \left( \frac{R_E}{R_E + 1} \right) (101) \times \left( \frac{10.1 R_E}{10.1 R_E + 3.47 + (101)[R_E \parallel 1 \text{ k}\Omega]} \right)$$

where  $R_E \parallel R_L \parallel r_o \approx R_E \parallel R_L = R_E \parallel 1 \text{ k}\Omega$

$$15 = \frac{(101)(10.1)R_E^2}{R_E + 1} \times \frac{1}{\left[ 10.1 R_E + 3.47 + \frac{101 R_E}{1 + R_E} \right]}$$

$$15 = \frac{(101)(10.1)R_E^2}{R_E + 1} \times \frac{1}{(1 + R_E)[10.1 R_E + 3.47] + 101 R_E}$$

$$15 = \frac{(101)(10.1)R_E^2}{10.1 R_E + 3.47 + 10.1 R_E^2 + 3.47 R_E + 101 R_E}$$

$$15 = \frac{(101)(10.1)R_E^2}{10.1 R_E^2 + 114.57 R_E + 3.47}$$

$$(101)(10.1)R_E^2 = 15[10.1 R_E^2 + 114.57 R_E + 3.47]$$

$$1020.1 R_E^2 = 151.5 R_E^2 + 1718.55 R_E + 52.05$$

$$868.6 R_E^2 - 1718.55 R_E - 52.05 = 0$$

$$16.7 R_E^2 - 33.0 R_E - 1 = 0$$

$$R_E = \frac{33 \pm \sqrt{(33)^2 + 4(16.7)}}{2(16.7)}$$

Must use + sign  $\Rightarrow R_E = 2.0 \text{ k}\Omega$

Then  $R_1 \parallel R_2 = 10.1 R_E = 20.2 \text{ k}\Omega$

$$V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right) (10) - 5 = \frac{1}{R_1} \left( \frac{R_1 R_2}{R_1 + R_2} \right) (10) - 5 = \frac{1}{R_1} (20.2)(10) - 5$$

$$I_{CQ} = 0.75 = (100) \left\{ \frac{\frac{1}{R_1} (20.2)(10) - 5 - 0.7 + 5}{20.2 + (101)(2)} \right\}$$

$$1.67 = \frac{1}{R_1} (202) - 0.7 \Rightarrow R_1 = 85.2 \text{ k}\Omega$$

$$\frac{R_1 R_2}{R_1 + R_2} = 20.2 = \frac{85.2 R_2}{85.2 + R_2} \Rightarrow R_2 = 26.5 \text{ k}\Omega$$

E4.20

a.  $\beta = 100$ ,  $V_{BE(\text{on})} = 0.7$ ,  $I_{CQ} = 1.25 \text{ mA}$

$$I_{EQ} = 1.26 \text{ mA}, I_{BQ} = 0.0125 \text{ mA}$$

$$V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right) (10) - 5$$

$$V_{TH} = \frac{1}{R_1} (R_1 \parallel R_2) (10) - 5$$

$$I_{BQ} = \frac{V_{TH} - 0.7 - (-5)}{R_{TH} + (1 + \beta) R_E}$$

$$V_{CEQ} = 10 - I_{EQ} R_E = 4$$

$$I_{EQ} R_E = 6 \Rightarrow I_{EQ} = \frac{6}{R_E} \Rightarrow R_E = \frac{6}{1.26} = 4.76 \text{ k}\Omega$$

$$\Rightarrow R_E = 4.76 \text{ k}\Omega$$

$$R_{TH} = (0.1)(1 + \beta) R_E = 10.1 R_E$$

Then

$$I_{BQ} = \frac{I_{EQ}}{101} = \frac{\frac{1}{R_1} (101) R_E (10) - 5 - 0.7 + 5}{10.1 R_E + (101) R_E}$$

$$0.0125 = \frac{\frac{1}{R_1} (101)(4.76) - 0.7}{(111.1)(4.76)} \Rightarrow R_1 = 65.8 \text{ k}\Omega$$


$$\frac{R_1 R_2}{R_1 + R_2} = (10.1) R_E = (10.1)(4.76) = 48.1 \text{ k}\Omega$$

$$(65.8) R_2 = (48.1)(65.8) + (48.1) R_2$$

$$(65.8 - 48.1) R_2 = (48.1)(65.8)$$

$$\Rightarrow R_2 = 178.8 \text{ k}\Omega$$

b.

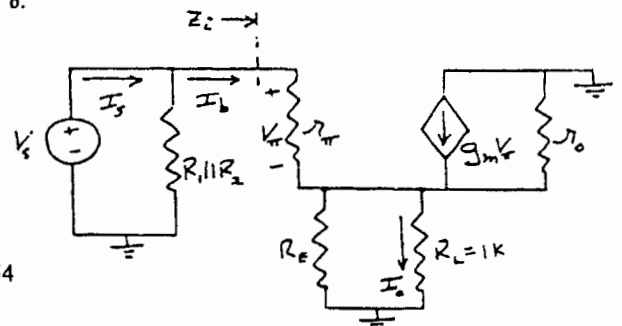

$$r_o = \frac{V_A}{I_{CQ}} = \frac{125}{1.25} = 100 \text{ k}\Omega$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{(100)(0.026)}{1.25} = 2.08 \text{ k}\Omega$$

$$g_m V_\pi = g_m (i_b r_\pi) = \beta I_b$$

$$Z_i = r_\pi + (1 + \beta)[R_E \parallel R_L \parallel r_o]$$

$$= 2.08 + (101)[4.76 \parallel 1 \parallel 100]$$

$$= 2.08 + (101)[0.826 \parallel 100]$$

$$= 2.08 + (101)(0.819)$$

$$Z_i = 84.8 \text{ k}\Omega$$

Assume  $R_L = 1 \text{ k}\Omega$

$$I_o = \left( \frac{R_E \parallel r_o}{R_E \parallel r_o + R_L} \right) (1 + \beta) I_b$$

$$I_b = \left( \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + Z_i} \right) I_S$$

$$A_I = \frac{I_o}{I_S} = \left( \frac{R_E \parallel r_o}{R_E \parallel r_o + R_L} \right) (1 + \beta) \left( \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + Z_i} \right)$$

$$R_E \parallel r_o = 4.76 \parallel 100 = 4.54$$

$$A_I = \left( \frac{4.54}{4.54 + 1} \right) (101) \left( \frac{48.1}{48.1 + 84.8} \right)$$


$$= \left( \frac{4.54}{5.54} \right) (101) \left( \frac{48.1}{132.9} \right)$$

$$\Rightarrow \underline{A_I = 30.0}$$

c.  $R_o = \frac{r_\pi}{1 + \beta} \parallel R_E \parallel r_o = \frac{2.08}{101} \parallel 4.76 \parallel 100$

$$\Rightarrow R_o = 20.4 \Omega$$

d.

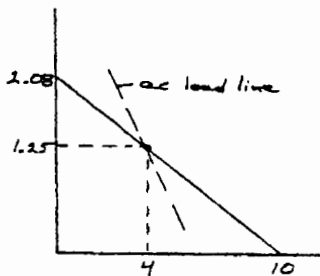

$$v_o = v_{ce} = (1 + \beta) i_b (R_E \parallel R_L \parallel r_o)$$

$$i_b = \frac{i_C}{\beta}$$

$$v_{ce} = i_C \left( \frac{1 + \beta}{\beta} \right) (R_E \parallel R_L \parallel r_o)$$

$$= i_C \left( \frac{101}{100} \right) (4.76 \parallel 1 \parallel 100)$$

$$= i_C (0.828)$$

If  $\Delta i_C = 1.25 \text{ mA}$ ,  $\rightarrow \Delta v_{ce} = 1.035 \text{ V}$

Maximum symmetrical swing in output voltage

$$i_s = 2\Delta v_{ce} = \underline{2.07 \text{ V peak-to-peak}}$$

E4.21

For  $\beta = 130$

$$I_{BQ} = \frac{10 - 0.7}{100 + (131)(10)} \Rightarrow 6.596 \mu\text{A}$$

$$I_{CQ} = 0.857 \text{ mA}$$

From Figure 4.21

$$3 < h_{ie} < 5 \text{ k}\Omega \quad \text{Let } h_{re} = 0$$

$$98 < h_{fe} < 170$$

$$8 < h_{oe} < 16 \mu\text{S}$$

$$h_{ie} = 4 \text{ k}\Omega$$

$$h_{fe} = 134$$

$$h_{oe} = 12 \mu\text{S} \Rightarrow \frac{1}{h_{oe}} = 83.3 \text{ k}\Omega$$

a.  $R_S = R_L = 10 \text{ k}\Omega$

$$R_{i,b} = h_{ie} + (1 + h_{fe}) \left( R_E \parallel R_L \parallel \frac{1}{h_{oe}} \right)$$

$$= 4 + (135)(10 \parallel 10 \parallel 83.3)$$

$$\Rightarrow \underline{R_{i,b} = 641 \text{ k}\Omega}$$

$$A_v = \left( \frac{R_E \parallel R_{i,b}}{R_S + R_E \parallel R_{i,b}} \right) \times$$

$$\left( \frac{(1 + h_{fe}) \left( R_E \parallel R_L \parallel \frac{1}{h_{oe}} \right)}{h_{ie} + (1 + h_{fe}) \left( R_E \parallel R_L \parallel \frac{1}{h_{oe}} \right)} \right)$$

$$A_v = \left( \frac{100 \parallel 641}{10 + 100 \parallel 641} \right) \left[ \frac{(135)(10 \parallel 10 \parallel 83.3)}{4 + (135)(10 \parallel 10 \parallel 83.3)} \right]$$

$$= \left( \frac{86.5}{10 + 86.5} \right) \left[ \frac{637}{641} \right]$$

$$\Rightarrow \underline{A_v = 0.891}$$

$$A_i = \left( \frac{R_E \parallel \frac{1}{h_{oe}}}{R_E \parallel \frac{1}{h_{oe}} + R_L} \right) (1 + h_{fe}) \left( \frac{R_E}{R_E + R_{i,b}} \right)$$

$$= \left( \frac{10 \parallel 83.3}{10 \parallel 83.3 + 10} \right) (135) \left( \frac{100}{100 + 641} \right)$$

$$\Rightarrow \underline{A_i = 8.59}$$

$$R_o = R_E \parallel \frac{1}{h_{oe}} \parallel \frac{h_{ie} + R_S \parallel R_B}{1 + h_{fe}}$$

$$= 10 \parallel 83.3 \parallel \frac{4 + 10 \parallel 100}{135} = 8.93 \parallel 0.0970$$

$$\Rightarrow \underline{R_o = 96.0 \Omega}$$

b.  $R_S = 1 \text{ k}\Omega$ ,  $R_{i,b} = 641 \text{ k}\Omega$ ,  $A_i = 8.59$

$$A_v = \left( \frac{86.5}{1 + 86.5} \right) \left( \frac{637}{641} \right) \Rightarrow \underline{A_v = 0.982}$$

$$R_o = 10 \parallel 8.33 \parallel \left[ \frac{4 + 1 \parallel 100}{135} \right]$$

$$= 8.93 \parallel 0.03696 \Rightarrow \underline{R_o = 36.8 \Omega}$$

E4.22

$$V_{TH} = 2.5V, R_{TH} = 25\text{ k}\Omega$$

$$I_{BQ} = \frac{5 - 0.7 - 2.5}{25 + (101)(2)} = \frac{1.8}{227} = 0.00793\text{ mA}$$

$$I_{CQ} = 0.793\text{ mA}$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.793}{0.026} = 30.5\text{ mA/V}$$

$$r_\pi = \frac{V_T \beta}{I_{CQ}} = \frac{(0.026)(100)}{0.793} = 3.28\text{ k}\Omega$$

$$r_o = \frac{V_A}{I_{CQ}} = \frac{125}{0.793} = 158\text{ k}\Omega$$

a.  $R_E \parallel R_L \parallel r_o = 2 \parallel 0.5 \parallel 158 = 0.4 \parallel 158 \approx 0.4$

$$A_v = \frac{(1 + \beta)(R_E \parallel R_L \parallel r_o)}{r_\pi + (1 + \beta)(R_E \parallel R_L \parallel r_o)}$$

$$= \frac{(101)(0.4)}{3.28 + (101)(0.4)} \Rightarrow A_v = 0.925$$

b.  $R_{i_b} = r_\pi + (1 + \beta)(R_E \parallel R_L \parallel r_o)$

$$R_{i_b} = 3.28 + (101)(0.4)$$

$$\Rightarrow R_{i_b} = 43.7\text{ k}\Omega$$

$$R_o = \frac{r_\pi}{1 + \beta} \parallel R_E \parallel r_o = \frac{3.28}{101} \parallel 2 \parallel 98.3$$

$$\Rightarrow R_o = 32.0\text{ }\Omega$$

c.  $I_B(\text{max}) -$

$$R_E(\text{min}) = 1.9\text{ k}\Omega$$

$$R_2(\text{min}) = 47.5\text{ k}\Omega$$

$$R_1(\text{max}) = 52.5\text{ k}\Omega$$

$$R_{TH} = 24.9\text{ k}\Omega$$

$$V_{TH} = \left(\frac{R_2}{R_1 + R_2}\right)V_{CC} = \left(\frac{47.5}{100}\right)(5) = 2.375$$

$$I_{BQ} = \frac{5 - 0.7 - 2.375}{24.9 + (101)(1.9)} = \frac{1.925}{216.8}$$

$$I_{CQ} = 0.888\text{ mA}$$

$$R_E(\text{max}) = 2.1\text{ k}\Omega$$

$$R_2(\text{max}) = 52.5\text{ k}\Omega$$

$$R_1(\text{min}) = 47.5\text{ k}\Omega$$

$$R_{TH} = 24.9\text{ k}\Omega$$

$$V_{TH} = \left(\frac{52.5}{100}\right)(5) = 2.625$$

$$I_{CQ} = (100) \left[ \frac{5 - 0.7 - 2.625}{24.9 + (101)(2.1)} \right] = \frac{(100)(1.675)}{237}$$

$$I_{CQ} = 0.707\text{ mA}$$

$$r_\pi(\text{max}) = \frac{(100)(0.026)}{0.707} = 3.68\text{ k}\Omega$$


$$R_o = 1.96 \parallel \frac{3.68}{101} = 1.96 \parallel 0.0364 = 35.7\text{ }\Omega$$

$$r_\pi(\text{min}) = 2.93\text{ k}\Omega$$

$$R_o = 1.96 \parallel \frac{2.93}{101} = 1.96 \parallel 0.0290 = 28.6\text{ }\Omega$$

$$\Rightarrow 28.6 \leq R_o \leq 35.7\text{ }\Omega$$

E4.23

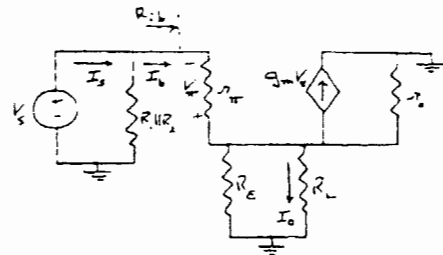

For  $V_{ECQ} = 2.5V$ ,

$$I_{EQ} = \frac{5 - 2.5}{R_E} = \frac{5 - 2.5}{0.5} = 5\text{ mA}$$

$$I_{CQ} = \left(\frac{75}{76}\right)(5) = 4.93\text{ mA} \Rightarrow I_{BQ} = 0.0658\text{ mA}$$

$$V_\pi = -I_b r_\pi$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{(75)(0.026)}{4.93} = 0.396\text{ k}\Omega$$

$$r_o = \frac{V_A}{I_{CQ}} = \frac{75}{4.93} = 15.2\text{ k}\Omega$$

$$g_m V_\pi = g_m (-I_b r_\pi) = -\beta I_b$$

$$I_o = \left(\frac{R_E \parallel r_o}{R_E \parallel r_o + R_L}\right) \times (1 + \beta) I_b$$

$$I_b = \left(\frac{R_1 \parallel R_2}{R_1 \parallel R_2 + Z_{i_b}}\right) I_S$$

$$A_I = \frac{I_o}{I_S} = \left(\frac{R_E \parallel r_o}{R_E \parallel r_o + R_L}\right) (1 + \beta) \left(\frac{R_1 \parallel R_2}{R_1 \parallel R_2 + Z_{i_b}}\right)$$

a.  $R_E = R_L = 0.5\text{ k}\Omega$

$$R_{i_b} = r_\pi + (1 + \beta)(R_E \parallel R_L \parallel r_o)$$

$$= 0.396 + (76)[0.5 \parallel 0.5 \parallel 15.2]$$

$$= 0.396 + (76)(0.246)$$

$$\Rightarrow R_{i_b} = 19.1\text{ k}\Omega$$

$$R_E \parallel r_o = 0.5 \parallel 15.2 = 0.484\text{ k}\Omega$$

$$A_I = 10 = \left(\frac{0.484}{0.484 + 0.5}\right) (76) \left(\frac{R_1 \parallel R_2}{R_1 \parallel R_2 + 19.1}\right)$$

$$10 = 37.38 \left(\frac{R_1 \parallel R_2}{R_1 \parallel R_2 + 19.1}\right)$$

$$0.2675(R_1 \parallel R_2 + 19.1) = R_1 \parallel R_2$$

$$R_1 \parallel R_2 = 6.975\text{ k}\Omega$$

$$V_{TH} = \left(\frac{R_2}{R_1 + R_2}\right)V_{CC} = \frac{1}{R_1}(R_1 \parallel R_2)V_{CC}$$

$$= \frac{1}{R_1}(6.975)(5)$$

$$I_{BQ} = \frac{5 - V_{EB(\text{on})} - V_{TH}}{R_{TH} + (1 + \beta)R_E}$$

$$0.0638 = \frac{5 - 0.7 - V_{TH}}{6.975 + (76)(0.5)}$$

$$2.96 = 4.3 - V_{TH} \Rightarrow V_{TH} = 1.34 = \frac{1}{R_1}(6.975)(5)$$

$$\Rightarrow R_1 = 26.0 \text{ k}\Omega$$

$$\frac{R_1 R_2}{R_1 + R_2} = 6.975 = \frac{26 R_2}{26 + R_2}$$

$$6.975(26 + R_2) = 26 R_2$$

$$\Rightarrow R_2 = 9.53 \text{ k}\Omega$$

b. For  $R_E = 4R_L = 4(0.5) \Rightarrow R_E = 2 \text{ k}\Omega$

$$I_{EQ} = \frac{5 - 2.5}{2} = 1.25 \text{ mA} \rightarrow I_{CQ} = 1.23 \text{ mA}$$

$$\rightarrow I_{BQ} = 0.0164 \text{ mA}$$

$$r_\pi = \frac{(75)(0.026)}{1.23} = 1.59 \text{ k}\Omega$$

$$r_o = \frac{75}{1.23} = 60.9 \text{ k}\Omega$$

$$Z_{ib} = r_\pi + (1 + \beta)[R_E \parallel R_L \parallel r_o]$$

$$= 1.59 + (76)[2 \parallel 0.5 \parallel 60.9]$$

$$\Rightarrow Z_{ib} = 31.8 \text{ k}\Omega$$

$$R_E \parallel r_o = 2 \parallel 60.9 = 1.94 \text{ k}\Omega$$

$$A_I = \left( \frac{1.94}{1.94 + 0.5} \right) (76) \left( \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + 31.8} \right) = 10$$

$$10 = 60.4 \left( \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + 31.8} \right)$$

$$0.166(R_1 \parallel R_2 + 31.8) = R_1 \parallel R_2$$

$$R_1 \parallel R_2 = 6.33 \text{ k}\Omega$$

Then  $I_{BQ} = 0.0164 = \frac{4.3 - V_{TH}}{6.33 + (76)(2)}$

$$V_{TH} = 1.70 = \frac{1}{R_1}(R_1 \parallel R_2)V_{CC} = \frac{1}{R_1}(6.33)(5)$$

$$\Rightarrow R_1 = 18.6 \text{ k}\Omega$$

$$\frac{R_1 R_2}{R_1 + R_2} = 6.33 = \frac{(18.6)R_2}{18.6 + R_2}$$

$$6.33(18.6 + R_2) = (18.6)R_2$$

$$\Rightarrow R_2 = 9.6 \text{ k}\Omega$$

E4.24

a.  $I_{EQ} = \frac{10 - 0.7}{10} = 0.93 \text{ mA}$

$$I_{CQ} = \left( \frac{\beta}{1 + \beta} \right) I_{EQ} = \left( \frac{100}{101} \right) (0.93)$$

$$\Rightarrow I_{CQ} = 0.921 \text{ mA}$$

$$V_{ECQ} = 10 + 10 - I_{CQ}R_C - I_{EQ}R_E$$

$$V_{ECQ} = 20 - (0.921)(5) - (0.93)(10)$$

$$\Rightarrow V_{ECQ} = 6.1 \text{ V}$$

b.  $r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{(100)(0.026)}{0.921} = 2.82 \text{ k}\Omega$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.921}{0.026} = 35.42 \text{ mA/V}$$

$i_o = g_m V_\pi$  and  $V_\pi = v_s$

$$i_i = \frac{v_s}{R_E \parallel r_\pi} + g_m V_\pi = v_s \left( \frac{1}{R_E \parallel r_\pi} + g_m \right)$$

$$A_I = \frac{i_o}{i_i} = \frac{g_m v_s}{v_s \left( \frac{1}{R_E \parallel r_\pi} + g_m \right)} = \frac{g_m (R_E \parallel r_\pi)}{1 + g_m (R_E \parallel r_\pi)}$$

$$= \frac{(35.42)(10 \text{ k}\Omega \parallel 2.82 \text{ k}\Omega)}{1 + (35.42)(10 \text{ k}\Omega \parallel 2.82 \text{ k}\Omega)}$$

$$\Rightarrow A_I = 0.987$$

$$A_v = \frac{v_o}{v_s} \text{ and } v_o = g_m V_\pi R_C = g_m v_s R_C$$

$$A_v = g_m R_C = (35.42)(5) \Rightarrow A_v = 177.1$$

c.  $V_{ECQ} = 6.1 \text{ V} \Rightarrow V_{ECQ} = V_E - V_C$

$$V_C = V_E - V_{ECQ} = 0.7 - 6.1 = -5.4 \text{ V}$$

$$v_C = V_C + i_o R_C$$

For  $v_{EC} = 0.5 \Rightarrow v_C = +0.2$

$$+0.2 = -5.4 + i_o R_C$$

$$i_o = \frac{0.2 + 5.4}{5} = 1.12 \text{ mA}$$

$\Rightarrow$  Current limited

$$i_o(\text{max}) = 0.921$$

$$\Rightarrow v_o(\text{peak}) = (0.921)(5) = 4.61$$

$\Rightarrow$  9.21 V peak-to-peak

E4.25

a.  $I_{BQ} = \frac{V_{EE} - V_{BE(\text{on})}}{R_B + (1 + \beta)R_E} = \frac{10 - 0.7}{100 + (101)(10)}$


$$\Rightarrow I_{BQ} = 8.38 \text{ }\mu\text{A}, I_{CQ} = 0.838 \text{ mA}$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{(100)(0.026)}{0.838} \Rightarrow r_\pi = 3.10 \text{ k}\Omega$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.838}{0.026} \Rightarrow g_m = 32.23 \text{ mA/V}$$

$$r_o = \frac{V_A}{I_{CQ}} = \frac{\infty}{0.838} \Rightarrow r_o = \infty$$

b.

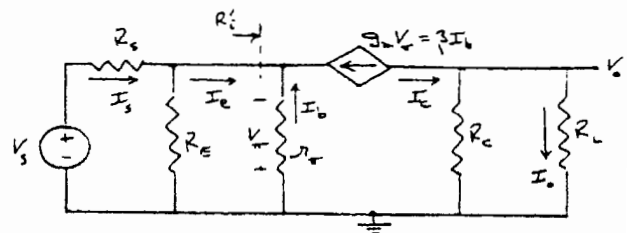

$$g_m V_\pi + \frac{V_\pi}{r_\pi} = \left( \frac{-V_\pi}{R_E} \right) + \frac{(-V_\pi - V_S)}{R_S}$$

$$V_\pi \left[ \left( \frac{1+\beta}{r_\pi} \right) + \frac{1}{R_E} + \frac{1}{R_S} \right] = -\frac{V_S}{R_S}$$

$$V_\pi = -\frac{V_S}{R_S} \left[ \left( \frac{1+\beta}{r_\pi} \right) \parallel R_E \parallel R_S \right]$$

$$V_o = -g_m V_\pi (R_C \parallel R_L)$$

$$A_v = \frac{V_o}{V_S} = g_m \frac{(R_C \parallel R_L)}{R_S} \left[ \left( \frac{r_\pi}{1+\beta} \right) \parallel R_E \parallel R_S \right]$$

$$= \frac{(32.23)[10 \parallel 1]}{(1)} \left\{ \frac{3.10}{101} \parallel 10 \parallel 1 \right\}$$

$$= (32.23)(0.909)(0.0297) \Rightarrow \underline{A_v = 0.870}$$

$$R'_i = \frac{r_\pi}{1+\beta} = \frac{3.10}{101} = 0.0307 \text{ k}\Omega$$

$$I_e = \left( \frac{R_E}{R_E + R'_i} \right) I_S \approx I_S$$

$$I_C = \left( \frac{\beta}{1+\beta} \right) I_e, \quad I_o = \left( \frac{R_C}{R_C + R_L} \right) I_C$$

$$I_e = \left( \frac{R_C}{R_C + R_L} \right) \left( \frac{\beta}{1+\beta} \right) I_S$$

$$A_I = \frac{I_o}{I_S} = \left( \frac{10}{10+1} \right) \left( \frac{100}{101} \right) \Rightarrow \underline{A_I = 0.900}$$

c.  $R_i = R_E \parallel R'_i = 10 \parallel 0.0307$

$$\Rightarrow \underline{R_i \approx 30.7 \Omega}$$

$$\underline{R_o = R_C = 10 \text{ k}\Omega}$$

E4.26

$$5 = I_B R_B + V_{BE(ON)} + I_E R_E$$

$$I_B = \frac{5 - 0.7}{R_B + (101)R_E} = \frac{4.3}{R_B + (101)R_E}$$

$$I_C = \frac{(100)(4.3)}{R_B + (101)R_E}$$

$$5 = I_C R_C + V_{CE} + I_E R_E - 5$$

$$V_{CE} = 10 - I_C \left( R_C + \left( \frac{101}{100} \right) R_E \right)$$

ac analysis

$$V_o = -g_m V_\pi (R_C \parallel R_L)$$

$$V_S = -V_\pi - \frac{V_\pi}{r_\pi} \cdot R_B = -V_\pi \left( 1 + \frac{R_B}{r_\pi} \right)$$

or  $V_\pi = -\left( \frac{r_\pi}{r_\pi + R_B} \right) V_S$

$$\frac{V_o}{V_S} = -g_m \left[ -\left( \frac{r_\pi}{r_\pi + R_B} \right) \right] (R_C \parallel R_L)$$

$$A_v = \frac{V_o}{V_S} = \frac{\beta}{r_\pi + R_B} (R_C \parallel R_L)$$

For  $I_C = 1 \text{ mA}$ ,

$$r_\pi = \frac{\beta V_T}{I_C} = \frac{(100)(0.026)}{1} = 2.6 \text{ k}\Omega$$

$$A_v = 20 = \frac{(100)(1)}{2.6 + R_B}$$

$$R_B = \frac{(100)(1)}{20} - 2.6 \Rightarrow \underline{R_B = 2.4 \text{ k}\Omega}$$

$$I_C = 1 = \frac{(100)(4.3)}{2.4 + (101)R_E}$$

$$R_E = \frac{(100)(4.3) - 2.4}{(101)} \Rightarrow \underline{R_E = 4.23 \text{ k}\Omega}$$

E4.27

a.  $R_{TH} = 70 \parallel 6 = 5.526 \text{ k}\Omega$

$$V_{TH} = \left( \frac{6}{6+70} \right) (10) - 5 = -4.21 \text{ V}$$

$$I_{B1} = \frac{5 - 4.21 - 0.70}{5.526 + (126)(0.2)} = \frac{0.090}{30.726}$$

$$\Rightarrow I_{B1} = 2.93 \mu\text{A}, \quad I_{CQ1} = 0.366 \text{ mA}$$

$$\frac{5 - V_{C1}}{5} = I_{C1} + \frac{(V_{C1} - 0.7) - (-5)}{(1+\beta)1.5}$$

$$\frac{5 - V_{C1}}{5} = 0.366 + \frac{V_{C1}}{(126)(1.5)} + \frac{4.3}{(126)(1.5)}$$

$$1 - 0.366 - \frac{4.3}{(126)(1.5)} = \frac{V_{C1}}{5} + \frac{V_{C1}}{(126)(1.5)}$$

$$0.6112 = V_{C1}(0.2053) \Rightarrow V_{C1} = 2.977 \text{ V}$$

$$I_{E1} = 0.369 \text{ mA}$$

$$V_{E1} = (0.369)(0.2) - 5 \Rightarrow V_{E1} = -4.926 \text{ V}$$

$$\Rightarrow V_{CE1} = V_{C1} - V_{E1} = 2.977 - (-4.926)$$

$$\Rightarrow \underline{V_{CE1} = 7.90 \text{ V}}$$


$$I_{EQ2} = \frac{(V_{C1} - 0.7) - (-5)}{1.5} = \frac{5 + 2.98 - 0.7}{1.5}$$

$$= 4.85 \text{ mA}$$

$$I_{CQ2} = \left( \frac{\beta}{1+\beta} \right) I_{EQ2} \Rightarrow \underline{I_{CQ2} = 4.81 \text{ mA}}$$

$$V_{E2} = V_{C1} - 0.7 = 2.98 - 0.7 = 2.28$$
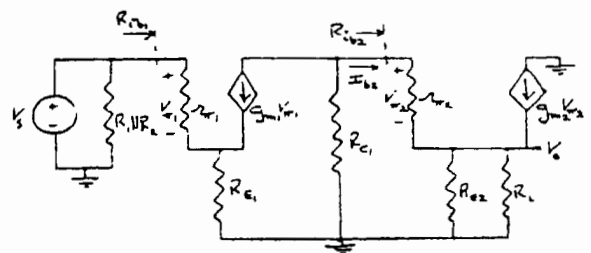
$$V_{CEQ2} = 5 - V_{E2} = 5 - 2.28 \Rightarrow \underline{V_{CEQ2} = 2.72 \text{ V}}$$



$$r_{\pi 1} = \frac{\beta V_T}{I_{CQ1}} = \frac{(125)(0.026)}{0.366} = 8.88 \text{ k}\Omega$$

$$r_{\pi 2} = \frac{\beta V_T}{I_{CQ2}} = \frac{(125)(0.026)}{4.81} = 0.676 \text{ k}\Omega$$

$$g_{m1} = \frac{I_{CQ1}}{V_T} = \frac{0.366}{0.026} = 14.1 \text{ mA/V}$$

$$g_{m2} = \frac{I_{CQ2}}{V_T} = \frac{4.81}{0.026} = 185 \text{ mA/V}$$

$$R_{ib1} = r_{\pi 1} + (1 + \beta)R_{E1} = 8.88 + (126)(0.2) = 34.08 \text{ k}\Omega$$

$$R_{ib2} = r_{\pi 2} + (1 + \beta)(R_{E2} \parallel R_L) = 0.676 + (126)(1.5 \parallel 10) = 165 \text{ k}\Omega$$

$$V_o = (1 + \beta)I_{b2}(R_{E2} \parallel R_L)$$

$$I_{b2} = \left( \frac{R_{C1}}{R_{C1} + R_{ib2}} \right) (-g_{m1} V_{\pi 1})$$

$$V_{\pi 1} = \frac{V_S}{Z_1} \cdot r_{\pi 1}$$

$$A_v = (1 + \beta)(R_{E2} \parallel R_L) \left( \frac{R_{C1}}{R_{C1} + R_{ib2}} \right) \left( \frac{-g_{m1} r_{\pi 1}}{R_{ib1}} \right)$$

$$A_v = \frac{V_o}{V_S}$$

$$= -(126)(125)(1.5 \parallel 10) \left( \frac{5}{5 + 165} \right) \left( \frac{1}{34.08} \right)$$

$$= -(126)(125)(1.30) \left( \frac{5}{170} \right) \left( \frac{1}{34.08} \right)$$

$$\underline{A_v = -17.7}$$

c.  $R_i = R_1 \parallel R_2 \parallel R_{ib1} = (5.53) \parallel (34.1)$

$$\Rightarrow \underline{R_i = 4.76 \text{ k}\Omega}$$

$$R_o = \left( \frac{r_{\pi 2} + R_{C1}}{1 + \beta} \right) \parallel R_{E2} = \left( \frac{0.676 + 5}{126} \right) \parallel 1.5$$

$$= 0.0450 \parallel 1.5$$

$$\Rightarrow \underline{R_o = 43.7 \Omega}$$

E4.28

a.  $I_{CQ2} = \left( \frac{100}{101} \right) (1 \text{ mA}) \Rightarrow I_{CQ2} = 0.990 \text{ mA}$

$$I_{EQ1} = \frac{I_{EQ2}}{1 + \beta} = \frac{1}{101} \Rightarrow I_{EQ1} = 0.0099 \text{ mA}$$

$$I_{BQ1} = \frac{I_{EQ1}}{1 + \beta} = \frac{0.0099}{101}$$

$$\Rightarrow I_{BQ1} = 0.000098 \text{ mA}, I_{CQ1} = 0.0098 \text{ mA}$$

$$V_{B1} = -I_{BQ1} R_B = -(0.000098)(10)$$

$$= -0.00098 \text{ V} \approx 0$$

$$V_{E1} = -0.7 \text{ V}, V_{E2} = -1.4 \text{ V}$$

$$I_1 = I_{CQ2} + I_{CQ1} = 0.990 + 0.0098$$

$$I_1 \approx 1 \text{ mA} \Rightarrow V_o = 5 - (1)(4) = 1 \text{ V}$$

$$V_{CEQ2} = 1 - (-1.4) = 2.4$$

$$\Rightarrow \underline{V_{CEQ2} = 2.4 \text{ V}}, I_{CQ2} = 0.990 \text{ mA}$$

$$V_{CEQ1} = 1 - (-0.7) = 1.7$$

$$\Rightarrow \underline{V_{CEQ1} = 1.7 \text{ V}}, I_{CQ1} = 0.0098 \text{ mA}$$

b.  $r_{\pi} = \frac{\beta V_T}{I_{CQ}}$  and  $g_m = \frac{I_{CQ}}{V_T}$

For  $Q_1$ :

$$r_{\pi 1} = \frac{(100)(0.026)}{0.0098} \Rightarrow r_{\pi 1} = 265 \text{ k}\Omega$$

$$g_{m1} = \frac{0.0098}{0.026} \Rightarrow g_{m1} = 0.377 \text{ mA/V}$$


For  $Q_2$ :

$$r_{\pi 2} = \frac{(100)(0.026)}{0.990} \Rightarrow r_{\pi 2} = 2.63 \text{ k}\Omega$$

$$g_{m2} = \frac{0.99}{0.026} \Rightarrow g_{m2} = 38.1 \text{ mA/V}$$

$$r_{o1} = r_{o2} = \infty$$

c.

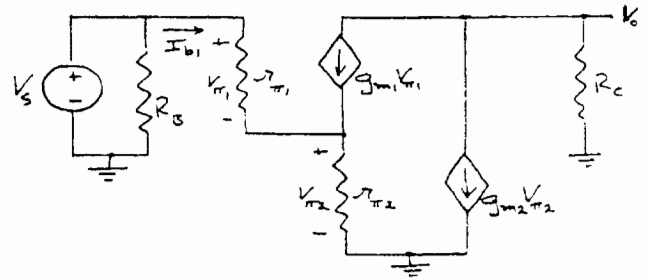

$$V_o = -(g_{m1} V_{\pi 1} + g_{m2} V_{\pi 2}) R_C$$

$$V_S = V_{\pi 1} + V_{\pi 2}$$

$$V_{\pi 2} = \left( \frac{V_{\pi 1}}{r_{\pi 1}} + g_{m1} V_{\pi 1} \right) r_{\pi 2} = \frac{(1 + \beta)}{r_{\pi 1}} V_{\pi 1} r_{\pi 2}$$

Then

$$V_o = - \left[ g_{m1} V_{\pi 1} + g_{m2} \left( \frac{(1 + \beta) r_{\pi 2}}{r_{\pi 1}} \right) V_{\pi 1} \right] \cdot R_C$$

Also

$$V_S = V_{\pi 1} + \left( \frac{1 + \beta}{r_{\pi 1}} \right) V_{\pi 1} r_{\pi 2}$$

$$= V_{\pi 1} \left[ 1 + (1 + \beta) \left( \frac{r_{\pi 2}}{r_{\pi 1}} \right) \right]$$

$$V_{\pi 1} = \frac{V_S}{1 + (1 + \beta) \left( \frac{r_{\pi 2}}{r_{\pi 1}} \right)}$$

$$V_o = - \left[ g_{m1} + g_{m2} (1 + \beta) \left( \frac{r_{\pi 2}}{r_{\pi 1}} \right) \right] R_C$$

$$+ \frac{V_S}{1 + (1 + \beta) \left( \frac{r_{\pi 2}}{r_{\pi 1}} \right)}$$

$$A_v = - \frac{\left[ g_{m1} + g_{m2} (1 + \beta) \left( \frac{r_{\pi 2}}{r_{\pi 1}} \right) \right] R_C}{1 + (1 + \beta) \left( \frac{r_{\pi 2}}{r_{\pi 1}} \right)}$$

$$A_v = - \frac{\left[ 0.377 + (38.08)(101) \left( \frac{2.626}{265.3} \right) \right] (4)}{1 + (101) \left( \frac{2.626}{265.3} \right)}$$

$$A_v = - \frac{153.8}{1.9997} \Rightarrow A_v = -76.9$$

d.  $R_i = r_{\pi 1} + (1 + \beta)r_{\pi 2}$

$$R_i = 265.3 + (101)(2.626)$$

$$\Rightarrow R_i = 531 \text{ k}\Omega$$

E4.29

a.  $I_{E1} = \frac{V_{E1} - (-10)}{20} + \frac{(V_{E1} - 0.7) - (-10)}{(1 + \beta)(10)}$

$$-I_{B1}R_B - V_{BE(on)} = V_{E1}$$

So

$$(1 + \beta)I_{B1} = \frac{10 - I_{B1}R_B - 0.7}{20} + \frac{10 - 0.7 - I_{B1}R_B - 0.7}{(101)(10)}$$

$$(101)I_{B1} + I_{B1} \left( \frac{20}{20} \right) + I_{B1} \cdot \frac{20}{(101)(10)} = \frac{9.3}{20} + \frac{8.6}{(101)(10)}$$

$$(102)I_{B1} = 0.465 + 0.00851$$

$$I_{B1} = 0.00464 \text{ mA} \Rightarrow V_{B1} = -0.09281$$

$$\Rightarrow V_{E1} = -0.793 \text{ V} \Rightarrow V_{E2} = -1.493 \text{ V}$$

$$I_{C1} = 0.464 \text{ mA}, I_{E1} = 0.469 \text{ mA}$$

$$I_1 = \frac{10 - 0.793}{20} = 0.46035 \text{ mA}$$

$$\Rightarrow I_{B2} = I_{E1} - I_1$$

$$I_{B2} = 0.00865 \text{ mA} \Rightarrow I_{C2} = 0.865 \text{ mA}$$

$$\text{or } I_{E2} = \frac{10 - 1.493}{10} = 0.851 \Rightarrow I_{C2} = 0.842 \text{ mA}$$

$$I_C = I_{C1} + I_{C2} = 0.464 + 0.842$$

$$= 1.306 \text{ mA}$$

$$V_0 = 10 - (1.306)(2) = 7.39 \text{ V}$$

$$V_{CEQ2} = 7.39 - (-1.493)$$

$$\Rightarrow V_{CEQ2} = 8.88 \text{ V}, I_{CQ2} = 0.842 \text{ mA}$$

$$V_{CEQ1} = 7.39 - (-0.793)$$

$$\Rightarrow V_{CEQ1} = 8.18 \text{ V}, I_{CQ1} = 0.464 \text{ mA}$$

b.  $r_{\pi} = \frac{\beta V_T}{I_{CQ}}, g_m = \frac{I_{CQ}}{V_T}$

For  $Q_1$ :

$$r_{\pi 1} = \frac{(100)(0.026)}{0.464} \Rightarrow r_{\pi 1} = 5.60 \text{ k}\Omega$$


$$g_{m1} = \frac{0.464}{0.026} \Rightarrow g_{m1} = 17.8 \text{ mA/V}$$

$$r_{\pi 2} = \frac{(100)(0.026)}{0.842} \Rightarrow r_{\pi 2} = 3.09 \text{ k}\Omega$$

$$g_{m2} = \frac{0.842}{0.026} \Rightarrow g_{m2} = 32.4 \text{ mA/V}$$

$$r_{o1} = r_{o2} = \infty$$

c.

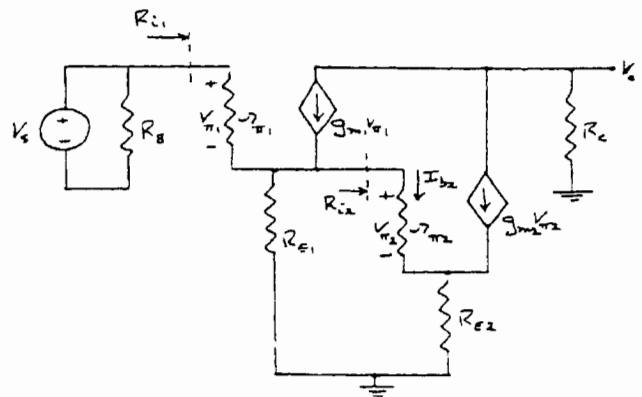

$$R_{i2} = r_{\pi 2} + (1 + \beta)R_{E2} = 3.09 + (101)(10) = 1013.1 \text{ k}\Omega$$

$$R_{i1} = r_{\pi 1} + (1 + \beta)[R_{E1} \parallel R_{i2}] = 5.60 + (101)[20 \parallel 1013.1]$$

d.  $R_{i1} = 1.986 \text{ M}\Omega$

Note that  $g_{m1}V_{\pi 1} = \beta I_{b1}$  and  $g_{m2}V_{\pi 2} = \beta I_{b2}$

$$\text{So } V_0 = -[\beta I_{b1} + \beta I_{b2}]R_C$$

$$I_{b1} = \frac{V_{\pi 1}}{r_{\pi 1}} \text{ and } I_{b2} = \left( \frac{R_{E1}}{R_{E1} + R_{i2}} \right) (1 + \beta)I_{b1}$$

So

$$V_0 = -[I_{b1} + I_{b2}]\beta R_C$$

$$= - \left\{ I_{b1} + \left( \frac{R_{E1}}{R_{E1} + R_{i2}} \right) (1 + \beta)I_{b1} \right\} \beta R_C$$

$$A_v = \frac{V_0}{V_{\pi 1}} = - \left[ 1 + \left( \frac{R_{E1}}{R_{E1} + R_{i2}} \right) (1 + \beta) \right] \frac{\beta R_C}{r_{\pi 1}}$$

$$= - \left[ 1 + \left( \frac{20}{20 + 1013.1} \right) (101) \right] \frac{(100)(2)}{1986}$$

$$A_v = -0.298$$

E4.30

a. dc analysis

$$\beta = 100, V_{BE(on)} = 0.7 \text{ V}, V_A = \infty$$

Want:  $I_{CQ2} = 0.5 \text{ mA}, V_{CE1} = V_{CE2} = 4 \text{ V}$

$$R_1 + R_2 + R_3 = 100 \text{ k}\Omega$$

Neglecting base currents:

$$I_1 = \frac{12}{100} = 0.12 \text{ mA}$$

$$V_{E1} = I_{CQ2} R_E = (0.5)(0.5) = 0.25 \text{ V}$$

$$V_{C1} = V_{CEQ1} + V_{E1} = 4 + 0.25 = 4.25$$

So

$$V_{C2} = V_{C1} + V_{CEQ2} = 4.25 + 4 = 8.25 \text{ V}$$

$$R_C = \frac{V_{CC} - V_{C2}}{I_{CQ}} = \frac{12 - 8.25}{0.5} \Rightarrow R_C = 7.5 \text{ k}\Omega$$

$$V_{B1} = V_{E1} + 0.7 = 0.25 + 0.7 = 0.95 \text{ V}$$

$$V_{B1} = \left( \frac{R_3}{R_1 + R_2 + R_3} \right) (12) \Rightarrow 0.95 = \frac{R_3}{100} (12)$$

$$\Rightarrow R_3 = 7.92 \text{ k}\Omega$$

$$V_{B2} = V_{C1} + 0.7 = 4.25 + 0.7 = 4.95$$

$$V_{B2} = \left( \frac{R_2 + R_3}{R_1 + R_2 + R_3} \right) (12)$$

$$\Rightarrow 4.95 = \frac{R_2 + 7.92}{100} (12)$$

$$R_2 = \frac{(4.95)(100)}{12} - 7.92 \Rightarrow R_2 = 33.3 \text{ k}\Omega$$

$$R_1 = 100 - R_2 - R_3 = 100 - 33.3 - 7.92$$

$$\Rightarrow R_1 = 58.8 \text{ k}\Omega$$

b. For both  $Q_1$  and  $Q_2$

$$r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{(100)(0.026)}{0.5}$$


$$\Rightarrow r_{\pi 1} = r_{\pi 2} = 5.2 \text{ k}\Omega$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.5}{0.026}$$

$$\Rightarrow g_{m1} = g_{m2} = 19.23 \text{ mA/V}$$

$$r_{o1} = r_{o2} = \infty$$

c.

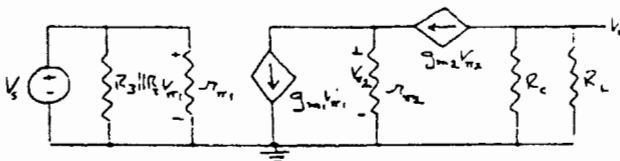

$$v_o = -g_{m2} V_{\pi 2} (R_C \parallel R_L)$$

$$\frac{V_{\pi 2}}{r_{\pi 2}} + g_{m2} V_{\pi 2} = g_{m1} V_{\pi 1}$$

$$V_{\pi 2} \left( \frac{1 + \beta}{r_{\pi 2}} \right) = g_{m1} V_{\pi 1}$$

$$V_{\pi 2} = g_{m1} V_{\pi 1} \left( \frac{r_{\pi 2}}{1 + \beta} \right) \text{ and } V_{\pi 1} = v_i$$

So

$$A_v = \frac{v_o}{v_i} = -g_{m2} (R_C \parallel R_L) \cdot g_{m1} \left( \frac{r_{\pi 2}}{1 + \beta} \right)$$

$$= -g_{m2} (R_C \parallel R_L) \left( \frac{\beta}{1 + \beta} \right)$$

$$A_v = - \left( \frac{100}{101} \right) (19.23)(7.5 \parallel 2) \Rightarrow A_v = -30.1$$

E4.31

a. dc analysis

$$\beta = 80, V_{BE(\text{on})} = 0.7, V_A = \infty$$

$$I_{BQ} = \frac{2.32 - 0.7}{24.2 + (81)(0.5)} = \frac{1.62}{64.7}$$

$$I_{BQ} = 0.0250 \text{ mA}, I_{CQ} = 2.00 \text{ mA}$$

$$\text{Power dissipated in } R_C = I_{CQ}^2 R_C = (2.0)^2 (2)$$

$$\Rightarrow P_C = 8.0 \text{ mW}$$

$$\text{Power dissipated in } R_L = 0, P_L = 0$$

$$V_{CE} = V_{CC} - I_C \left[ R_C + \left( \frac{1 + \beta}{\beta} \right) R_E \right]$$

$$= 12 - 2 \left[ 2 + \left( \frac{81}{80} \right) (0.5) \right]$$

$$V_{CE} = 6.99 \text{ V}$$

$$P_T = I_B V_{BE} + I_C V_{CE} = (0.0259)(0.7) + (2)(6.99)$$

$$\Rightarrow P_T = 14.0 \text{ mW}$$

$$\text{b. } r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{(80)(0.026)}{2.0} \Rightarrow r_\pi = 1.04 \text{ k}\Omega$$

$$\text{For } v_s = 18 \cos \omega t \text{ mV}$$

From the text, power dissipation in the transistor

$$P_T = V_{CEQ} I_{CQ} - \left( \frac{\beta}{r_\pi} \right)^2 \left( \frac{V_P}{\sqrt{2}} \right)^2 (R_C \parallel R_L)$$

$$= (6.99)(2 \times 10^{-3})$$

$$- \left( \frac{80}{1.04 \times 10^3} \right)^2 \left( \frac{0.018}{\sqrt{2}} \right)^2 (2 \times 10^3 \parallel 2 \times 10^3)$$

$$P_T = (14 - 0.96) \text{ mW} \Rightarrow P_T = 13.0 \text{ mW}$$

From notes

$$|v_{ce}| = \frac{\beta}{r_\pi} (R_C \parallel R_L) V_P \cos \omega t$$

Power dissipated in  $R_L$

$$P_L = \frac{|v_{ce}|^2}{R_L} \Big|_{\text{rms}} = \left[ \frac{\beta}{r_\pi} (R_C \parallel R_L) \right]^2 \times \frac{1}{R_L} \times \frac{V_P^2}{2}$$

$$= \left[ \frac{80}{1.04} (1.0) \right]^2 \times \frac{1}{2 \times 10^3} \times \left( \frac{0.018}{2} \right)^2$$

$$\Rightarrow P_L = 0.479 \text{ mW}$$

$$R_C = 2 \text{ k}\Omega \text{ also so } P_C = 8.0 + 0.479$$

$$\Rightarrow P_C = 8.48 \text{ mW}$$

E4.32

$$\beta = 100, V_{BE(\text{on})} = 0.7 \text{ V}, V_A = \infty$$

$$\text{a. } R_{TH} = R_1 \parallel R_2 = 10 \parallel 53.8 = 8.43 \text{ k}\Omega$$

$$V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right) (5) = \left( \frac{10}{10 + 53.8} \right) (5)$$

$$V_{TH} = 0.7837$$

$$I_{BQ} = \frac{0.7837 - 0.7}{8.43} = 0.00993 \text{ mA}$$

$$I_{CQ} = 0.993 \text{ mA}$$

$$V_{CEQ} = V_{CC} - I_{CQ} R_C$$

$$2.5 = 5 - (0.993) R_C \Rightarrow \underline{R_C = 2.52 \text{ k}\Omega}$$

$$\text{b. } \text{Power in } R_C = P_R = I_C^2 R_C = (0.993)^2 (2.52)$$

$$\Rightarrow \underline{P_R = 2.48 \text{ mW}}$$

$$\text{Power in } Q \hat{=} P_Q \approx I_{CQ} V_{CEQ} = (0.993)(2.5)$$

$$\Rightarrow \underline{P_Q = 2.48 \text{ mW}}$$

$$\text{c. } i_C = 0.993 \cos \omega t$$

$$\text{ac power} = \frac{1}{2} \times (0.993)^2 \times R_C = 1.24 \text{ mW}$$

in  $R_C$ 

$$\frac{1.24}{2.48 + 2.48} = \underline{0.25}$$

## Chapter 4

## Problem Solutions

4.1

$$a. \quad g_m = \frac{I_{CQ}}{V_T} = \frac{2}{0.026} \Rightarrow g_m = 76.9 \text{ mA/V}$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{(180)(0.026)}{2} \Rightarrow r_\pi = 2.34 \text{ k}\Omega$$

$$r_o = \frac{V_A}{I_{CQ}} = \frac{150}{2} \Rightarrow r_o = 75 \text{ k}\Omega$$

$$b. \quad g_m = \frac{0.5}{0.026} \Rightarrow g_m = 19.2 \text{ mA/V}$$

$$r_\pi = \frac{(180)(0.026)}{0.5} \Rightarrow r_\pi = 9.36 \text{ k}\Omega$$

$$r_o = \frac{150}{0.5} \Rightarrow r_o = 300 \text{ k}\Omega$$

4.2

$$g_m = \frac{I_{CQ}}{V_T} \Rightarrow 200 = \frac{I_{CQ}}{0.026} \Rightarrow I_{CQ} = 5.2 \text{ mA}$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{(125)(0.026)}{5.2} \Rightarrow r_\pi = 0.625 \text{ k}\Omega$$

$$r_o = \frac{V_A}{I_{CQ}} = \frac{200}{5.2} \Rightarrow r_o = 38.5 \text{ k}\Omega$$

4.3

$$(a) \quad I_{BQ} = \frac{2-0.7}{250} = 0.0052 \text{ mA}$$

$$I_C = (120)(0.0052) = 0.624 \text{ mA}$$

$$g_m = \frac{0.624}{0.026} \Rightarrow g_m = 24 \text{ mA/V}$$

$$r_\pi = \frac{(120)(0.026)}{0.624} \Rightarrow r_\pi = 5 \text{ k}\Omega$$

$$r_o = \infty$$

$$(b) \quad A_v = -g_m R_C \left( \frac{r_\pi}{r_\pi + R_B} \right) = -(24)(4) \left( \frac{5}{5+250} \right) \Rightarrow$$

$$A_v = -1.88$$

$$(c) \quad v_s = \frac{v_o}{A_v} = \frac{v_o}{-1.88} \Rightarrow$$

$$v_s = -0.426 \sin 100t \text{ V}$$

4.4

$$g_m = \frac{I_{CQ}}{V_T}, \quad 1.08 \leq I_{CQ} \leq 1.32 \text{ mA}$$

$$\frac{1.08}{0.026} \leq g_m \leq \frac{1.32}{0.026} \Rightarrow 41.5 \leq g_m \leq 50.8 \text{ mA/V}$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}}; \quad r_\pi(\text{max}) = \frac{(120)(0.026)}{1.08} = 2.89 \text{ k}\Omega$$

$$r_\pi(\text{min}) = \frac{(80)(0.026)}{1.32} = 1.58 \text{ k}\Omega$$

$$1.58 < r_\pi < 2.89 \text{ k}\Omega$$

4.5

$$a. \quad r_\pi = 5.4 = \frac{\beta V_T}{I_{CQ}} = \frac{(120)(0.026)}{I_{CQ}}$$

$$\Rightarrow I_{CQ} = 0.578 \text{ mA}$$

$$V_{CEQ} = \frac{1}{2} V_{CC} = \frac{1}{2}(5) = 2.5 \text{ V}$$

$$V_{CEQ} = V_{CC} - I_{CQ} R_C \Rightarrow 2.5 = 5.0 - (0.578) R_C$$

$$\Rightarrow R_C = 4.33 \text{ k}\Omega$$

$$I_{BQ} = \frac{I_{CQ}}{\beta} = \frac{0.578}{120} = 0.00482 \text{ mA}$$

$$V_{BB} = I_{BQ} R_B + V_{BE(\text{on})}$$

$$= (0.00482)(25) + 0.70$$

$$\Rightarrow V_{BB} = 0.821$$

$$b. \quad r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{(120)(0.026)}{0.578} = 5.40 \text{ k}\Omega$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.578}{0.026} = 22.2 \text{ mA/V}$$

$$r_o = \frac{V_A}{I_{CQ}} = \frac{100}{0.578} = 173 \text{ k}\Omega$$

$$V_o = -g_m (r_o \parallel R_C) V_\pi, \quad V_\pi = \left( \frac{r_\pi}{r_\pi + R_B} \right) V_s$$

$$A_v = -g_m \left( \frac{r_\pi}{r_\pi + R_B} \right) (r_o \parallel R_C) = -\frac{\beta (r_o \parallel R_C)}{r_\pi + R_B}$$

$$A_v = -\frac{(120)[173 \parallel 4.33]}{5.40 + 25} = -\frac{(120)(4.22)}{30.4}$$

$$\Rightarrow A_v = -16.7$$

4.6

$$a. \quad V_{ECQ} = \frac{1}{2} V_{CC} = 5 \text{ V}$$

$$V_{ECQ} = 10 - I_{CQ} R_C \Rightarrow 5 = 10 - (0.5) R_C$$

$$\Rightarrow R_C = 10 \text{ k}\Omega$$

$$I_{BQ} = \frac{I_{CQ}}{\beta} = \frac{0.5}{100} = 0.005$$

$$V_{EB(\text{on})} + I_{BQ} R_B = V_{BB} = (0.70) + (0.005)(50)$$

$$\Rightarrow V_{BB} = 0.95 \text{ V}$$

$$b. \quad g_m = \frac{I_{CQ}}{V_T} = \frac{0.5}{0.026} \Rightarrow g_m = 19.2 \text{ mA/V}$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{(100)(0.026)}{0.5} \Rightarrow r_\pi = 5.2 \text{ k}\Omega$$

$$r_o = \frac{V_A}{I_{CQ}} = \frac{\infty}{0.5} \Rightarrow r_o = \infty$$

$$c. \quad A_v = -\frac{\beta R_C}{r_\pi + R_B} = -\frac{(100)(10)}{5.2 + 50} \Rightarrow A_v = -18.1$$

4.7 a.  $I_E = 0.35 \text{ mA}$ ,  $I_B = \frac{0.35}{101} = 0.00347 \text{ mA}$

$V_B = -I_B R_B = -(0.00347)(10)$

$\Rightarrow V_B = -0.0347 \text{ V}$

$V_E = V_B - V_{BE(\text{on})} \Rightarrow V_E = -0.735 \text{ V}$

b.  $V_C = V_{CEQ} + V_E = 3.5 - 0.735 = 2.77 \text{ V}$

$I_C = \left(\frac{\beta}{1+\beta}\right) I_E = \left(\frac{100}{101}\right) (0.35) = 0.347 \text{ mA}$

$R_C = \frac{V^+ - V_C}{I_C} = \frac{5 - 2.77}{0.347} \Rightarrow R_C = 6.43 \text{ k}\Omega$

(c)  $A_v = -g_m \left(\frac{R_B \parallel r_\pi}{R_B \parallel r_\pi + R_S}\right) (R_C \parallel r_o)$

$g_m = \frac{0.347}{0.026} = 13.3 \text{ mA/V}$ ,  $r_o = \frac{100}{0.347} = 288 \text{ k}\Omega$

$r_\pi = \frac{(100)(0.026)}{0.347} = 7.49 \text{ k}\Omega$

$R_B \parallel r_\pi = 10 \parallel 7.49 = 4.28 \text{ k}\Omega$

$A_v = -(13.3) \left(\frac{4.28}{4.28 + 0.1}\right) (6.43 \parallel 288) \Rightarrow$

$A_v = -81.7$

d.  $A_v = -g_m \left(\frac{R_B \parallel r_\pi}{R_B \parallel r_\pi + R_S}\right) (R_C \parallel r_o)$

$R_B \parallel r_\pi = 10 \parallel 7.49 = 4.28 \text{ k}\Omega$

$A_v = -(13.3) \left(\frac{4.28}{4.28 + 0.5}\right) (6.43 \parallel 288)$

$\Rightarrow A_v = -74.9$

4.8

a.  $R_{TH} = R_1 \parallel R_2 = 6 \parallel 1.5 = 1.2 \text{ k}\Omega$

$V_{TH} = \left(\frac{R_2}{R_1 + R_2}\right) V^+ = \left(\frac{1.5}{1.5 + 6}\right) (5) = 1.0 \text{ V}$

$I_{BQ} = \frac{V_{TH} - V_{BE(\text{on})}}{R_{TH} + (1 + \beta)R_E} = \frac{1.0 - 0.7}{1.2 + (181)(0.1)} = 0.0155 \text{ mA}$

$I_{CQ} = 2.80 \text{ mA}$ ,  $I_{EQ} = 2.81$

$V_{CEQ} = V^+ - I_{CQ}R_C - I_{EQ}R_E$

$= 5 - (2.8)(1) - (2.81)(0.1)$

$\Rightarrow V_{CEQ} = 1.92 \text{ V}$

b.  $r_\pi = \frac{(180)(0.026)}{2.80} \Rightarrow r_\pi = 1.67 \text{ k}\Omega$

$g_m = \frac{2.80}{0.026} \Rightarrow g_m = 108 \text{ mA/V}$ ,  $r_o = \infty$

(c)  $A_v = -g_m \left(\frac{R_1 \parallel R_2 \parallel r_\pi}{R_1 \parallel R_2 \parallel r_\pi + R_S}\right) (R_C \parallel R_L)$

$R_1 \parallel R_2 \parallel r_\pi = 6 \parallel 1.5 \parallel 1.67 = 0.698 \text{ k}\Omega$

$A_v = -(108) \left(\frac{0.698}{0.698 + 0.2}\right) (1 \parallel 1.2) \Rightarrow$

$A_v = -45.8$

4.9

a.  $I_{CQ} \approx I_{EQ}$

$V_{CEQ} = 5 = 10 - I_{CQ}(R_C + R_E)$

$= 10 - I_{CQ}(1.2 + 0.2)$

$I_{CQ} = 3.57 \text{ mA}$

$I_{BQ} = \frac{3.57}{150} = 0.0238 \text{ mA}$

$R_1 \parallel R_2 = R_{TH} = (0.1)(1 + \beta)R_E$

$= (0.1)(151)(0.2) = 3.02 \text{ k}\Omega$

$V_{TH} = \frac{1}{R_1} \cdot R_{TH} \cdot (10) - 5$

$V_{TH} = I_{BQ}R_{TH} + V_{BE(\text{on})} + (1 + \beta)I_{BQ}R_E - 5$

$\frac{1}{R_1}(3.02)(10) - 5 = (0.0238)(3.02) + 0.7$


$+ (151)(0.0238)(0.2) - 5$

$\frac{1}{R_1}(30.2) = 1.49 \Rightarrow R_1 = 20.3 \text{ k}\Omega$

$\frac{20.3R_2}{20.3 + R_2} = 3.02 \Rightarrow R_2 = 3.55 \text{ k}\Omega$

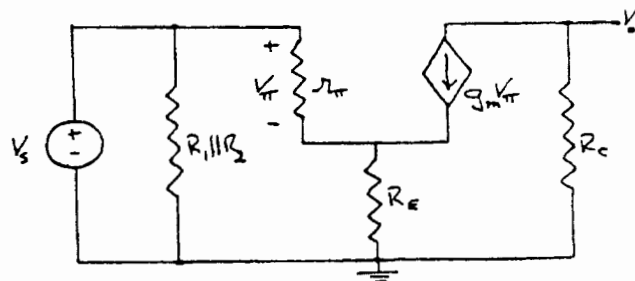b.  $r_\pi = \frac{(150)(0.026)}{3.57} = 1.09 \text{ k}\Omega$

$g_m = \frac{3.57}{0.026} = 137 \text{ mA/V}$



$A_v = \frac{-\beta R_C}{r_\pi + (1 + \beta)R_E} = -\frac{(150)(1.2)}{1.09 + (151)(0.2)}$

$\Rightarrow A_v = -5.75$

4.10

$$a. \quad V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right) V_{CC} = \left( \frac{50}{50 + 10} \right) (12) = 10 \text{ V}$$


$$R_{TH} = R_1 \parallel R_2 = 50 \parallel 10 = 8.33 \text{ k}\Omega$$

$$I_{BQ} = \frac{12 - 0.7 - 10}{8.33 + (101)(1)} = 0.0119 \text{ mA}$$


$$I_{CQ} = 1.19 \text{ mA}, \quad I_{EQ} = 1.20 \text{ mA}$$

$$V_{ECQ} = 12 - (1.20)(1) - (1.19)(2)$$

$$\underline{V_{ECQ} = 8.42 \text{ V}}$$

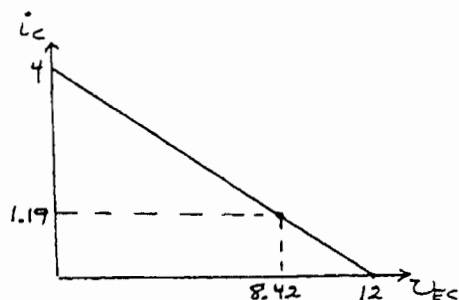

b.

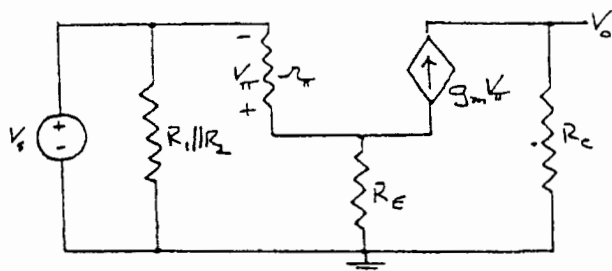

$$r_{\pi} = \frac{(100)(0.026)}{1.19} = 2.18 \text{ k}\Omega$$

$$V_o = g_m V_{\pi} R_C$$

$$V_s = -V_{\pi} - \left( \frac{V_{\pi}}{r_{\pi}} + g_m V_{\pi} \right) R_E$$

$$= -V_{\pi} \left[ \frac{r_{\pi} + (1 + \beta) R_E}{r_{\pi}} \right]$$

$$A_v = \frac{-\beta R_C}{r_{\pi} + (1 + \beta) R_E} = \frac{-(100)(2)}{2.18 + (101)(1)}$$

$$\Rightarrow \underline{A_v = -1.94}$$

c. Approximation: Assume  $r_{\pi}$  does not vary significantly.

$$R_C = 2 \text{ k}\Omega \pm 5\% = 2.1 \text{ k}\Omega \text{ or } 1.9 \text{ k}\Omega$$

$$R_E = 1 \text{ k}\Omega \pm 5\% = 1.05 \text{ k}\Omega \text{ or } 0.95 \text{ k}\Omega$$

For  $R_C(\text{max}) = 2.1 \text{ k}\Omega$  and  $R_E(\text{min})$

$$A_v = \frac{-(100)(2.1)}{2.18 + (101)(0.95)} = -2.14$$

For  $R_C(\text{min}) = 1.9 \text{ k}\Omega$  and  $R_E(\text{max}) = 1.05 \text{ k}\Omega$

$$A_v = \frac{-(100)(1.9)}{2.18 + (101)(1.05)} = -1.76$$

So  $1.76 \leq |A_v| \leq 2.14$

4.11

$$(a) \quad V_{CC} = \left( \frac{1 + \beta}{\beta} \right) I_{CQ} R_E + V_{ECQ} + I_{CQ} R_C$$

$$12 = \left( \frac{101}{100} \right) I_{CQ} (1) + 6 + I_{CQ} (2)$$

so that  $I_{CQ} = 1.99 \text{ mA}$

$$I_{BQ} = \frac{1.99}{100} = 0.0199 \text{ mA}$$

$$R_{TH} = (0.1)(1 + \beta) R_E = (0.1)(101)(1) = 10.1 \text{ k}\Omega$$

$$V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right) V_{CC} = \frac{1}{R_1} \cdot R_{TH} \cdot V_{CC} = \frac{1}{R_1} (10.1)(12)$$

$$V_{CC} = (1 + \beta) I_{BQ} R_E + V_{EB}(\text{on}) + I_{BQ} R_{TH} + V_{TH}$$

$$12 = (101)(0.0199)(1) + 0.7 + (0.0199)(10.1) + \frac{121.2}{R_1}$$

which yields  $R_1 = 13.3 \text{ k}\Omega$  and  $R_2 = 42 \text{ k}\Omega$

$$(b) \quad A_v = \frac{-\beta R_C}{r_{\pi} + (1 + \beta) R_E} = \frac{-(100)(2)}{1.31 + (101)(1)}$$

$$\underline{A_v = -1.95}$$

4.12

$$I_{CQ} = 0.25 \text{ mA}, \quad I_{EQ} = 0.2525 \text{ mA}$$

$$I_{BQ} = 0.0025 \text{ mA}$$

$$I_{BQ} R_B + V_{BE}(\text{on}) + I_{EQ} (R_S + R_E) - 5 = 0$$

$$(0.0025)(50) + 0.7 + (0.2525)(0.1 + R_E) = 5$$

$$\underline{R_E = 16.4 \text{ k}\Omega}$$

$$V_E = -(0.0025)(50) - 0.7 = -0.825 \text{ V}$$

$$V_C = V_{CEQ} + V_E = 3 - 0.825 = 2.175 \text{ V}$$

$$R_C = \frac{5 - 2.175}{0.25} \Rightarrow \underline{R_C = 11.3 \text{ k}\Omega}$$

$$A_v = \frac{-\beta R_C}{r_{\pi} + (1 + \beta) R_E}$$

$$r_{\pi} = \frac{(100)(0.026)}{0.25} = 10.4 \text{ k}\Omega$$

$$A_v = \frac{-(100)(11.3)}{10.4 + (101)(0.1)} \Rightarrow \underline{A_v = -55.1}$$

$$R_i = R_B \parallel [r_{\pi} + (1 + \beta) R_E]$$

$$= 50 \parallel [10.4 + (101)(0.1)]$$

$$R_i = 50 \parallel 20.5 \Rightarrow \underline{R_i = 14.5 \text{ k}\Omega}$$

4.13

a.  $9 = I_{EQ}R_E + V_{EB(on)} + I_{BQ}R_S$

$I_{EQ} = 0.75 \text{ mA}, I_{BQ} = \frac{0.75}{81} = 0.00926 \text{ mA}$

$I_{CQ} = 0.741 \text{ mA}$

$9 = (0.75)R_E + 0.7 + (0.00926)(2)$

$\Rightarrow R_E = 11.0 \text{ k}\Omega$

b.  $V_E = 9 - (0.75)(11) = 0.75 \text{ V}$

$V_C = V_E - V_{ECQ} = 0.75 - 7 = -6.25 \text{ V}$

$R_C = \frac{V_C - (-9)}{I_{CQ}} = \frac{9 - 6.25}{0.741} \Rightarrow R_C = 3.71 \text{ k}\Omega$

c.  $A_v = -g_m \left( \frac{r_\pi}{r_\pi + R_S} \right) (R_C \parallel R_L \parallel r_o)$

$r_\pi = \frac{(80)(0.026)}{0.741} = 2.81 \text{ k}\Omega$

$r_o = \frac{80}{0.741} = 108 \text{ k}\Omega$

$A_v = \frac{-80}{2.81 + 2} (3.71 \parallel 10 \parallel 108)$

$A_v = -43.9$

d.  $R_i = R_S + r_\pi = 2 + 2.81 \Rightarrow R_i = 4.81 \text{ k}\Omega$

4.14

(a)  $V_{CC} \equiv I_{CQ}(R_C + R_E) + V_{CEQ}$

$9 = I_{CQ}(2.2 + 2) + 3.75$  So that

$I_{CQ} = 1.25 \text{ mA}$


(b)  $g_m = \frac{1.25}{0.026} = 48.1 \text{ mA/V}$

$r_\pi = \frac{(120)(0.026)}{1.25} = 2.50 \text{ k}\Omega$

$r_o = \frac{100}{1.25} = 80 \text{ k}\Omega$

Assume circuit is to be designed to be bias stable.

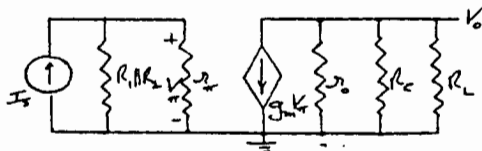$R_{TH} = R_1 \parallel R_2 = (0.1)(1 + \beta)R_E = (0.1)(121)(2) = 24.2 \Omega$



$V_o = -g_m V_\pi (r_o \parallel R_C \parallel R_L)$

$V_\pi = I_s (R_1 \parallel R_2 \parallel r_\pi)$

Then

$R_m = \frac{V_o}{I_s} = -g_m (R_1 \parallel R_2 \parallel r_\pi) (r_o \parallel R_C \parallel R_L)$

$R_m = -48.1(24.2 \parallel 2.5)(80 \parallel 2.2 \parallel 1) = -48.1(2.27)(0.682)$

or

$R_m = \frac{V_o}{I_s} = -74.5 \text{ k}\Omega = -74.5 \text{ V/mA}$

4.15

a.  $I_{EQ} = 0.80 \text{ mA}, I_{BQ} = \frac{0.80}{66} = 0.0121 \text{ mA}$

$I_{CQ} = 0.788 \text{ mA}$

$V_B = I_{BQ}R_B \Rightarrow R_B = \frac{0.3}{0.0121} \Rightarrow R_B = 24.8 \text{ k}\Omega$

$R_C = \frac{V_C - (-5)}{I_{CQ}} = \frac{5 - 3}{0.788} \Rightarrow R_C = 2.54 \text{ k}\Omega$

b.  $g_m = \frac{0.788}{0.026} = 30.3 \text{ mA/V}$

$r_\pi = \frac{(65)(0.026)}{0.788} = 2.14 \text{ k}\Omega$

$r_o = \frac{75}{0.788} = 95.2 \text{ k}\Omega$

$i_o = \left( \frac{R_C \parallel r_o}{R_C \parallel r_o + R_L} \right) g_m V_\pi, V_\pi = -v_s$

$G_f = \frac{i_o}{v_s} = -g_m \left( \frac{R_C \parallel r_o}{R_C \parallel r_o + R_L} \right)$   
 $= -(30.3) \left( \frac{2.54 \parallel 95.2}{2.54 \parallel 95.2 + 4} \right)$

$G_f = -11.6 \text{ mA/V}$


4.16

$I_{BQ} = \frac{4 - 0.7}{5 + (101)(5)} = 0.00647$

$I_{CQ} = 0.647 \text{ mA}$

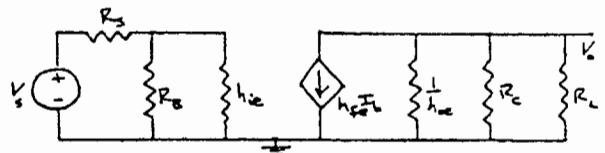a.  $80 \leq h_{fe} \leq 120, 10 \leq h_{oe} \leq 20 \mu\text{S}$

$2.45 \text{ k}\Omega \leq h_{ie} \leq 3.7 \text{ k}\Omega$   
 low gain                      high gain



$V_o = -h_{fe} I_b \left( \frac{1}{h_{oe}} \parallel R_C \parallel R_L \right)$

$I_b = \frac{R_B}{R_{TH} + h_{ie}} \cdot V_s$

$R_{TH} = R_B \parallel R_S = 5 \parallel 1 = 0.833 \text{ k}\Omega$

High-gain

$$I_b = \frac{\left(\frac{5}{5+1}\right)V_S}{0.833 + 3.7} = 0.1838V_S$$

Low-gain

$$I_b = \frac{\left(\frac{5}{5+1}\right)V_S}{0.833 + 2.45} = 0.2538V_S$$

For

$$h_{oe} = 10 \Rightarrow \frac{1}{h_{oc}} \parallel R_C \parallel R_L = \frac{1}{0.010} \parallel 4 \parallel 4$$

$$= 100 \parallel 2 = 1.96 \text{ k}\Omega$$

For

$$h_{oe} = 20 \Rightarrow \frac{1}{0.020} \parallel 4 \parallel 4 = 50 \parallel 2 = 1.92 \text{ k}\Omega$$

$$|A_v|_{\max} = (120)(0.1838)(1.96) = 43.2$$

$$|A_v|_{\min} = (80)(0.2538)(1.92) = 39.0$$

$$39.0 \leq |A_v| \leq 43.2$$

b.  $R_i = R_B \parallel h_{ie} = 5 \parallel 3.7 = 2.13 \text{ k}\Omega$

or  $R_i = 5 \parallel 2.45 = 1.64 \text{ k}\Omega$


$$1.64 < R_i < 2.13 \text{ k}\Omega$$

$$R_o = \frac{1}{h_{oc}} \parallel R_C = \frac{1}{0.010} \parallel 4 = 100 \parallel 4 = 3.85 \text{ k}\Omega$$

or  $R_o = \frac{1}{0.020} \parallel 4 = 50 \parallel 4 = 3.70 \text{ k}\Omega$

$$3.70 \leq R_o \leq 3.85 \text{ k}\Omega$$

4.17

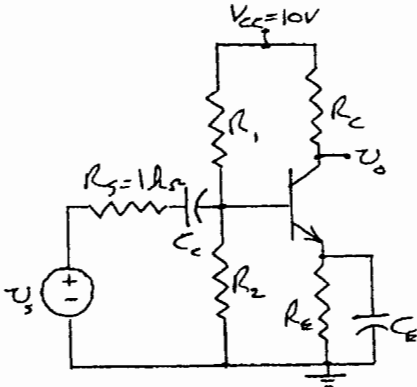

Assume an npn transistor with  $\beta = 100$  and  $V_A = \infty$ . Let  $V_{CC} = 10 \text{ V}$ .

$$|A_v| = \frac{0.5}{0.01} = 50$$

Bias at  $I_{CQ} = 1 \text{ mA}$  and let  $R_E = 1 \text{ k}\Omega$

For a bias stable circuit

$$R_{TH} = (0.1)(1 + \beta)R_E = (0.1)(101)(1) = 10.1 \text{ k}\Omega$$

$$V_{TH} = \frac{1}{R_1} \cdot R_{TH} \cdot V_{CC} = \frac{1}{R_1} (10.1)(10) = \frac{101}{R_1}$$

$$I_{BQ} = \frac{1}{100} = 0.01 \text{ mA}$$

$$V_{TH} = I_{BQ}R_{TH} + V_{BE}(on) + (1 + \beta)I_{BQ}R_E$$

$$\frac{101}{R_1} = (0.01)(10.1) + 0.7 + (101)(0.01)(1)$$

which yields  $R_1 = 55.8 \text{ k}\Omega$  and  $R_2 = 12.3 \text{ k}\Omega$

Now

$$r_\pi = \frac{(100)(0.026)}{1} = 2.6 \text{ k}\Omega$$

$$g_m = \frac{1}{0.026} = 38.46 \text{ mA/V}$$

$$V_o = -g_m V_\pi R_C$$

where

$$V_\pi = \left( \frac{R_1 \parallel R_2 \parallel r_\pi}{R_1 \parallel R_2 \parallel r_\pi + R_S} \right) \cdot V_s = \left( \frac{10.1 \parallel 2.6}{10.1 \parallel 2.6 + 1} \right) \cdot V_s$$

or

$$V_\pi = 0.674V_s$$

Then

$$A_v = \frac{V_o}{V_s} = -(0.674)g_m R_C = -(0.674)(38.46)R_C = -50$$

which yields  $R_C = 1.93 \text{ k}\Omega$

With this  $R_C$ , the dc bias is OK.

4.18

a.  $I_{BQ} = \frac{6 - 0.7}{10 + (101)(3)} = 0.0169 \text{ mA}$

$$I_{CQ} = 1.69 \text{ mA}, \quad I_{EQ} = 1.71 \text{ mA}$$

$$V_{CEQ} = (16 + 6) - (1.69)(6.8) - (1.71)(3)$$

$$V_{CEQ} = 5.38 \text{ V}$$

b.  $g_m = \frac{1.69}{0.026} \Rightarrow g_m = 65 \text{ mA/V}$

$$r_\pi = \frac{(100)(0.026)}{1.69} \Rightarrow r_\pi = 1.54 \text{ k}\Omega, \quad r_o = \infty$$

(c)  $A_v = \frac{-\beta(R_C \parallel R_L)}{r_\pi + (1 + \beta)R_E} \cdot \frac{R_B \parallel R_{ib}}{R_B \parallel R_{ib} + R_S}$

$$R_{ib} = r_\pi + (1 + \beta)R_E = 1.54 + (101)(3) = 304.5 \text{ k}\Omega$$

$$R_B \parallel R_{ib} = 10 \parallel 304.5 = 9.68 \text{ k}\Omega$$

Then

$$A_v = \frac{-(100)(6.8 \parallel 6.8)}{1.54 + (101)(3)} \cdot \left( \frac{9.68}{9.68 + 0.5} \right) \Rightarrow$$

$$A_v = -1.06$$

$$i_o = \left( \frac{R_C}{R_C + R_L} \right) (-\beta i_b)$$

$$i_b = \left( \frac{R_B}{R_B + r_\pi + (1 + \beta)R_E} \right) i_s$$

$$A_i = -(\beta) \left( \frac{R_C}{R_C + R_L} \right) \left( \frac{R_B}{R_B + r_\pi + (1 + \beta)R_E} \right)$$

$$= -(100) \left( \frac{6.8}{6.8 + 6.8} \right) \left( \frac{10}{10 + 1.54 + (101)(3)} \right)$$

$$\Rightarrow A_i = -1.59$$

(d)  $R_{is} = R_s + R_B \parallel R_{ib} = 0.5 + 10 \parallel 304.5 = 10.2 \text{ k}\Omega$


(e)  $A_v = \frac{-\beta(R_C \parallel R_L)}{r_x + (1 + \beta)R_E} \cdot \frac{R_B \parallel R_{ib}}{R_B \parallel R_{ib} + R_s}$

$A_v = \frac{-(100)(6.8 \parallel 6.8)}{1.54 + (101)(3)} \cdot \left( \frac{9.68}{9.68 + 1} \right) \Rightarrow$

$A_v = -1.01$

$A_i = \text{same as (c)} \Rightarrow A_i = -1.59$

4.19

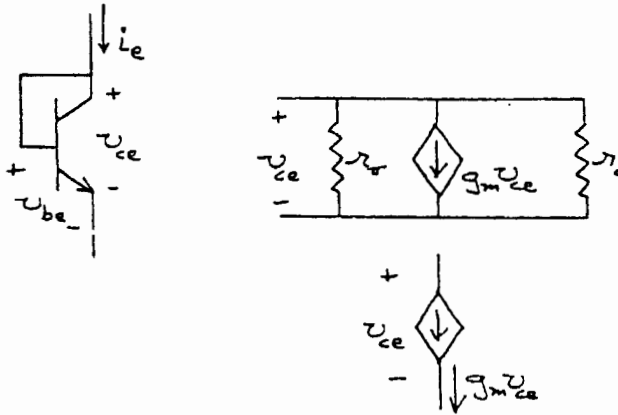


$r = \frac{v_{ce}}{g_m v_{ce}} = \frac{1}{g_m}$

So  $r_e = r_\pi \parallel \left( \frac{1}{g_m} \right) \parallel r_o$

4.20

Let  $\beta = 100$ ,  $V_A = \infty$

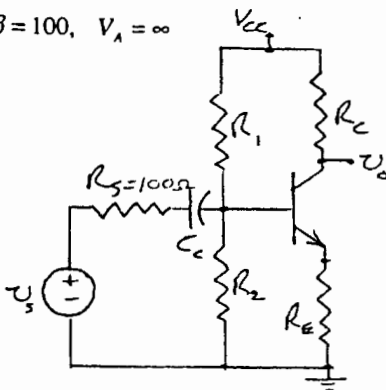

Let  $V_{CC} = 2.5 \text{ V}$

$P = (I_R + I_C)V_{CC} \Rightarrow 0.12 = (I_R + I_C)(2.5) \Rightarrow$

$I_R + I_C = 48 \mu\text{A}$ , Let  $I_R = 8 \mu\text{A}$ ,  $I_C = 40 \mu\text{A}$

$R_1 + R_2 \cong \frac{V_{CC}}{I_R} = \frac{2.5}{8} \Rightarrow 312.5 \text{ k}\Omega$

$I_{BQ} = \frac{40}{100} = 0.4 \mu\text{A}$

Let  $R_E = 2 \text{ k}\Omega$ . For a bias stable circuit

$R_{TH} = (0.1)(1 + \beta)R_E = (0.1)(101)(2) = 20.2 \text{ k}\Omega$

$V_{TH} = \frac{1}{R_1} \cdot R_{TH} \cdot V_{CC} = I_{BQ}R_{TH} + V_{BE}(on) + (1 + \beta)I_{BQ}R_E$

$\frac{1}{R_1}(20.2)(2.5) = (0.0004)(20.2) + 0.7$

$+ (101)(0.0004)(2)$

which yields  $R_1 = 64 \text{ k}\Omega$  and  $R_2 = 29.5 \text{ k}\Omega$

$r_x = \frac{(100)(0.026)}{0.04} = 65 \text{ k}\Omega$  Neglect  $R_s$

$A_v = \frac{V_o}{V_i} \cong \frac{-\beta R_C}{r_x + (1 + \beta)R_E}$

$-10 = \frac{-100R_C}{65 + (101)(2)} \Rightarrow R_C = 26.7 \text{ k}\Omega$

With this  $R_C$ , dc biasing is OK.

4.21

Need a voltage gain of  $\frac{100}{5} = 20$ .

Assume a sign inversion from a common-emitter is not important. Use the configuration for Figure 4.28. Need an input resistance of

$R_i = \frac{5 \times 10^{-3}}{0.2 \times 10^{-6}} = 25 \times 10^3 = 25 \text{ k}\Omega$

$R_i = R_{TH} \parallel R_{ib}$ . Let  $R_{TH} = 50 \text{ k}\Omega$ ,  $R_{ib} = 50 \text{ k}\Omega$

$R_{ib} = r_x + (1 + \beta)R_E \cong (1 + \beta)R_E$

For  $\beta = 100$ ,  $R_E = \frac{R_{ib}}{1 + \beta} = \frac{50}{101} = 0.495 \text{ k}\Omega$

Let  $R_E = 0.5 \text{ k}\Omega$ ,  $V_{CC} = 10 \text{ V}$ ,  $I_{CQ} = 0.2 \text{ mA}$

Then  $I_{BQ} = \frac{0.2}{100} = 0.002 \text{ mA}$

$V_{TH} = I_{BQ}R_{TH} + V_{BE}(on) + (1 + \beta)I_{BQ}R_E$

$\frac{1}{R_1} \cdot R_{TH} \cdot V_{CC} = \frac{1}{R_1}(50)(10) = (0.002)(50) + 0.7$

$+ (101)(0.002)(0.5)$

which yields  $R_1 = 555 \text{ k}\Omega$  and  $R_2 = 55 \text{ k}\Omega$

Now


$A_v = \frac{-\beta R_C}{r_x + (1 + \beta)R_E}$ ,  $r_x = \frac{(100)(0.026)}{0.2} = 13 \text{ k}\Omega$

so

$-20 = \frac{-(100)R_C}{13 + (101)(0.5)} \Rightarrow R_C = 12.7 \text{ k}\Omega$

[Note:  $I_{CQ}R_C = (0.2)(12.7) = 2.54 \text{ V}$ . So dc biasing is OK.]

4.22

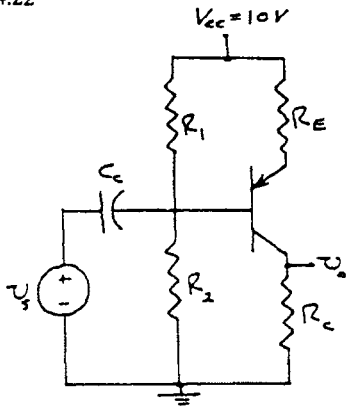

$$\beta = 80, A_v = \frac{-\beta R_C}{r_\pi + (1 + \beta)R_E}$$

First approximation:

$$(A_v) \approx \frac{R_C}{R_E} = 10 \Rightarrow R_C = 10R_E$$

Set  $R_C = 12R_E$

$$V_{EC} \approx V_{CC} - I_C(R_C + R_E) = 10 - I_C(13R_E)$$

$$\text{For } V_{EC} = \frac{1}{2}V_{CC} = 5$$

$$5 = 10 - I_C(13R_E)$$

For  $I_C = 0.7 \text{ mA}$

$$I_E = 0.709, I_B = 0.00875 \text{ mA}$$

$$\Rightarrow R_E = 0.55 \text{ k}\Omega \rightarrow R_C = 6.6 \text{ k}\Omega$$

Bias stable  $\Rightarrow$

$$R_1 \parallel R_2 = R_{TH} = (0.1)(1 + \beta)R_E$$

$$= (0.1)(81)(0.55) = 4.46 \text{ k}\Omega$$

$$10 = (0.709)(0.55) + 0.7 + (0.00875)(4.46)$$

$$+ \frac{1}{R_1}(4.46)(10)$$

$$8.87 = \frac{1}{R_1}(4.46) \Rightarrow R_1 = 5.03 \text{ k}\Omega$$

$$\frac{5.03R_2}{5.03 + R_2} = 4.46 \Rightarrow R_2 = 39.4 \text{ k}\Omega$$


$$\frac{10}{R_1 + R_2} = \frac{10}{5.03 + 39.4} = 0.225 \text{ mA}$$

$0.7 + 0.225 \approx 0.925 \text{ mA}$  from  $V_{CC}$  source.

$$\text{Now } r_\pi = \frac{(80)(0.026)}{0.7} = 2.97 \text{ k}\Omega$$

$$|A_v| = \frac{(80)(6.6)}{2.97 + (81)(0.55)} = 11.1$$

4.23

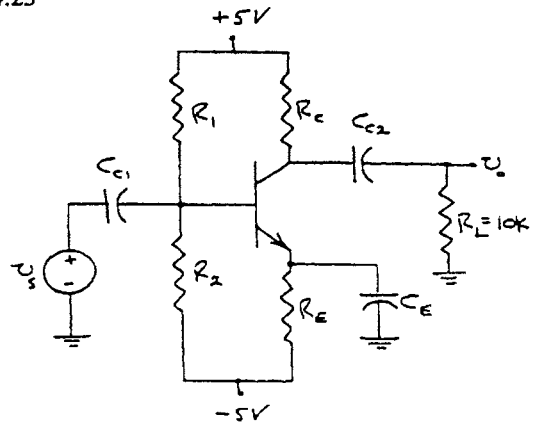

$$\beta = 120$$

$$\text{Let } I_{CQ} = 0.35 \text{ mA}, I_{EQ} = 0.353 \text{ mA}$$

$$I_{BQ} = 0.00292 \text{ mA}$$

Let  $R_E = 2 \text{ k}\Omega$ . For  $V_{CEQ} = 4 \text{ V} \Rightarrow$

$$10 = 4 + (0.35)R_C + (0.353)(2)$$

$$R_C = 15.1 \text{ k}\Omega, r_\pi = \frac{(120)(0.026)}{0.35} = 8.91 \text{ k}\Omega$$

$$A_v = \frac{-\beta(R_C \parallel R_L)}{r_\pi} = -\frac{(120)(15.1 \parallel 10)}{8.91}$$

$$A_v = -81.0$$

For bias stable circuit:

$$R_1 \parallel R_2 = R_{TH} = (0.1)(1 + \beta)R_E$$

$$= (0.1)(121)(2) = 24.2 \text{ k}\Omega$$

$$V_{TH} = \left(\frac{R_2}{R_1 + R_2}\right)(10) - 5 = \frac{1}{R_1} \cdot R_{TH} \cdot (10) - 5$$

$$V_{TH} = I_{BQ}R_{TH} + V_{BE(on)} + (1 + \beta)I_{BQ}R_E - 5$$

$$\frac{1}{R_1}(24.2)(10) - 5 = (0.00292)(24.2) + 0.7$$

$$+ (121)(0.00292)(2) - 5$$

$$\frac{1}{R_1}(242) = 1.477, R_1 = 164 \text{ k}\Omega$$

$$\frac{164R_2}{164 + R_2} = 24.2 \Rightarrow R_2 = 28.4 \text{ k}\Omega$$

$$\frac{10}{164 + 28.4} = 0.052, 0.35 + 0.052 = 0.402 \text{ mA}$$

4.24

From Prob. 4-10:


$$R_{TH} = R_1 \parallel R_2 = 10 \parallel 50 = 8.33 \text{ k}\Omega$$

$$V_{TH} = \left(\frac{R_2}{R_1 + R_2}\right)(12) = \left(\frac{50}{50 + 10}\right)(12) = 10 \text{ V}$$

$$I_{BQ} = \frac{12 - 0.7 - 10}{8.33 + (101)(1)} = 0.0119 \text{ mA}$$

$$I_{CQ} = 1.19 \text{ mA}, I_{EQ} = 1.20 \text{ mA}$$
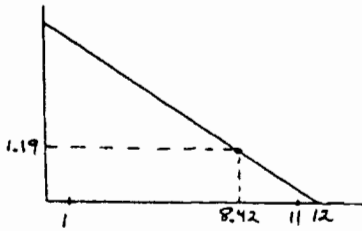
$$V_{ECQ} = 12 - (1.19)(2) - (120)(1) = 8.42 \text{ V}$$



For  $1 \leq v_{EC} \leq 11$

$$\Delta v_{EC} = 11 - 8.42 = 2.58$$

⇒ Output voltage swing = 5.16 V  
(peak-to-peak)


4.25

$$I_{BQ} = \frac{5 - 0.7}{50 + (101)(0.1 + 12.9)} = 0.00315 \text{ mA}$$

$$I_{CQ} = 0.315 \text{ mA}, I_{EQ} = 0.319 \text{ mA}$$

$$V_{CEQ} = (5 + 5) - (0.315)(6) - (0.319)(13)$$

$$V_{CEQ} = 3.96 \text{ V}$$

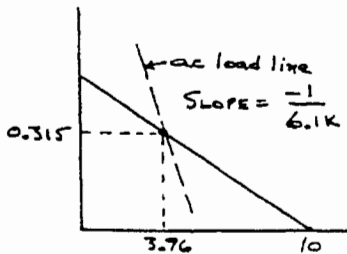

$$\Delta i_C = -\frac{1}{6.1} \Delta v_{EC}$$

$$\text{For } \Delta i_C = 0.315 - 0.05 = 0.265$$

$$\Rightarrow |\Delta v_{EC}| = 1.62$$

$$v_{EC}(\text{min}) = 3.96 - 1.62 = 2.34$$

Output signal swing determined by current:

Max. output swing = 3.24 V peak-to-peak

4.26

$$\text{For } R_C = 6 \text{ k}\Omega, V_C = 5 - \left(\frac{100}{101}\right)(0.35)(6) = 2.92 \text{ V}$$

$$V_E = -I_{BQ}R_B - V_{BE}(\text{on}) = -\frac{0.35}{100}(10) - 0.7 = -0.735 \text{ V}$$

$$\text{Then } V_{CE} = V_C - V_E = 2.92 - (-0.735) = 3.66 \text{ V}$$

$$\Delta v_{CE} = \Delta i_C \cdot R_C \Rightarrow (4.5 - 3.66) = \Delta i_C(6)$$

so that  $\Delta i_C = 0.14 \text{ mA}$

(a) Total  $\Delta v_{CE} = 2(4.5 - 3.66) = 1.68 \text{ V peak-to-peak}$

(b) Total  $\Delta i_C = 2(0.14) = 0.28 \text{ mA peak-to-peak}$

4.27

$$I_{EQ} = 0.80 \text{ mA}, I_{CQ} = 0.792 \text{ mA}$$


$$I_{BQ} = 0.008 \text{ mA}$$

$$V_E = 0.7 + (0.008)(10) = 0.78 \text{ V}$$

$$V_C = I_{CQ}R_C - 5 = (0.792)(4) - 5 = -1.83 \text{ V}$$

$$V_{ECQ} = 0.78 - (-1.83) = 2.61 \text{ V}$$

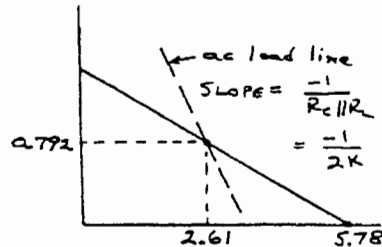Load line: Assume  $V_E$  remains constant at  $\approx 0.78 \text{ V}$



$$\Delta i_C = \frac{-1}{2 \text{ k}\Omega} \cdot v_{ec}$$

$$\text{Collector current swing} = 0.792 - 0.08$$

$$= 0.712 \text{ mA}$$

$$|\Delta v_{ec}| = (0.712)(2) = 1.42 \text{ V}$$

Output swing determined by current.

Max. output swing = 2.84 V peak-to-peak

$$\text{Swing in } i_o \text{ current} = \frac{2.84}{4}$$

$$= \underline{0.71 \text{ mA peak-to-peak}}$$


4.28

$$I_{BQ} = \frac{6 - 0.7}{10 + (101)(3)} = 0.0169 \text{ mA}$$

$$I_{CQ} = 1.69 \text{ mA}, I_{EQ} = 1.71 \text{ mA}$$

$$V_{CEQ} = (16 + 6) - (1.69)(6.8) - (1.71)(3)$$

$$V_{CEQ} = 5.38 \text{ V}$$

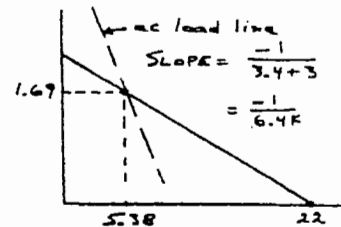

$$\Delta i_C = -\frac{1}{6.4} \Delta v_{CE}$$

For  $v_{CE}(\min) = 1\text{ V}$ ,  $\Delta v_{CE} = 5.38 - 1 = 4.38\text{ V}$


$$\Rightarrow |\Delta i_C| = \frac{4.38}{6.4} = 0.684\text{ mA}$$

Output swing limited by voltage:

$$\Delta v_{CE} = \text{Max. swing in output voltage} \\ = 8.76\text{ V peak-to-peak}$$

$$\Delta i_0 = \frac{1}{2} \Delta i_C \Rightarrow \Delta i_0 = 0.342\text{ mA} \\ \text{(peak-to-peak)}$$

4.29

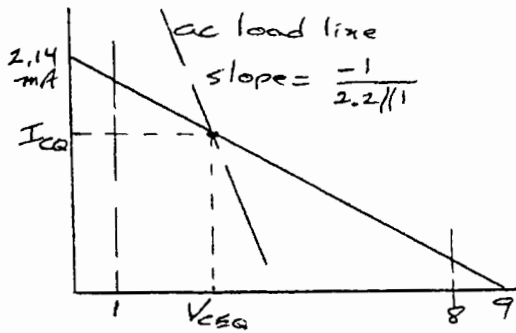

$$\Delta v_{CE}(\max) = V_{CEQ} - 1, \quad \Delta i_C(\max) = I_{CQ}$$

$$\Delta v_{CE} = \Delta i_C(0.6875). \text{ So}$$

$$V_{CEQ} - 1 = I_{CQ}(0.6875) \text{ and}$$

$$V_{CEQ} = V_{CC} - I_{CQ}(R_C + R_E) \Rightarrow V_{CEQ} = 9 - I_{CQ}(4.2)$$

Then

$$9 - I_{CQ}(4.2) - 1 = I_{CQ}(0.6875)$$

$$\text{So } I_{CQ} = 1.64\text{ mA} \text{ and } V_{CEQ} = 2.11\text{ V}$$

$$V_{TH} = \frac{1}{R_1} \cdot R_{TH} \cdot V_{CC} \text{ and } R_{TH} = (0.1)(1 + \beta)R_E$$

$$R_{TH} = (0.1)(151)(2) = 30.2\text{ k}\Omega$$

$$V_{TH} = I_{BQ}R_{TH} + V_{BE}(\text{on}) + (1 + \beta)I_{BQ}R_E$$


$$I_{BQ} = \frac{1.64}{150} = 0.0109\text{ mA}$$

$$\frac{1}{R_1}(30.2)(9) = (0.0109)(30.2) + 0.7 + (151)(0.0109)(2)$$

$$\text{which yields } R_1 = 62.9\text{ k}\Omega \text{ and } R_2 = 58.1\text{ k}\Omega$$

4.30

dc load line

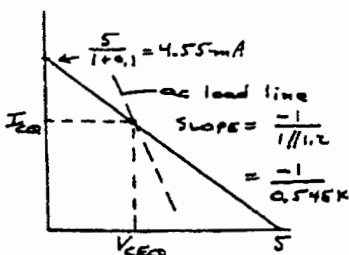

For maximum symmetrical swing

$$\Delta i_C = I_{CQ} - 0.25$$

$$\Delta v_{CE} = V_{CEQ} - 0.5$$

$$\text{and } |\Delta i_C| = \frac{1}{0.545\text{ k}\Omega} \cdot |\Delta v_{CE}|$$

$$I_{CQ} - 0.25 = \frac{V_{CEQ} - 0.5}{0.545}$$

$$V_{CEQ} = 5 - I_{CQ}(1.1)$$

$$0.545(I_{CQ} - 0.25) = [5 - I_{CQ}(1.1)] - 0.5$$

$$(0.545 + 1.1)I_{CQ} = 5 - 0.5 + 0.136$$

$$I_{CQ} = 2.82\text{ mA}, \quad I_{BQ} = 0.0157\text{ mA}$$

$$R_{TH} = R_1 \parallel R_2 = (0.1)(1 + \beta)R_E$$

$$= (0.1)(181)(0.1) = 1.81\text{ k}\Omega$$

$$V_{TH} = \frac{1}{R_1} \cdot R_{TH} \cdot V^+ = I_{BQ}R_{TH} + V_{BE}(\text{on})$$

$$+ (1 + \beta)I_{BQ}R_E$$

$$\frac{1}{R_1}(1.81)(5) = (0.0157)(1.81) + 0.7$$

$$+ (181)(0.0157)(0.1)$$

$$\frac{1}{R_1}(9.05) = 1.01 \Rightarrow R_1 = 8.96\text{ k}\Omega$$

$$\frac{8.96R_2}{8.96 + R_2} = 1.81 \Rightarrow R_2 = 2.27\text{ k}\Omega$$

4.31

$$I_{CQ} = 0.647\text{ mA}, \quad V_{CEQ} = 10 - (0.647)(9) = 4.18\text{ V}$$

$$\Delta i_C = I_{CQ} = 0.647\text{ mA}$$

$$\text{So } \Delta v_{CE} = \Delta i_C(4 \parallel 4) = (0.647)(2) = 1.294\text{ V}$$

Voltage swing is well within the voltage specification. Then

$$\Delta v_{CE} = 2(1.294) = 2.59\text{ V peak-to-peak}$$

4.32


a.  $R_{TH} = R_1 \parallel R_2 = 10 \parallel 10 = 5\text{ k}\Omega$

$$V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right) (18) - 9 = \left( \frac{10}{10 + 10} \right) (18) - 9 = 0$$

$$I_{BQ} = \frac{0 - 0.7 - (-9)}{5 + (181)(0.5)} = 0.0869\text{ mA}$$

$$I_{CQ} = 15.6\text{ mA}, \quad I_{EQ} = 15.7\text{ mA}$$
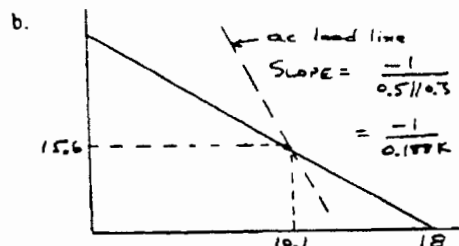
$$V_{CEQ} = 18 - (15.7)(0.5) \Rightarrow V_{CEQ} = 10.1\text{ V}$$



c.  $r_{\pi} = \frac{(180)(0.026)}{15.6} = 0.30 \text{ k}\Omega$

$$A_v = \frac{(1+\beta)(R_E \parallel R_L)}{r_{\pi} + (1+\beta)(R_E \parallel R_L)} \cdot \left( \frac{R_1 \parallel R_2 \parallel R_{ib}}{R_1 \parallel R_2 \parallel R_{ib} + R_s} \right)$$

$$R_{ib} = r_{\pi} + (1+\beta)(R_E \parallel R_L) = 0.30 + (181)(0.5 \parallel 0.3)$$

or  $R_{ib} = 34.2 \text{ k}\Omega$

$$R_1 \parallel R_2 \parallel R_{ib} = 5 \parallel 34.2 = 4.36 \text{ k}\Omega$$

$$A_v = \frac{(181)(0.5 \parallel 0.3)}{0.3 + (181)(0.5 \parallel 0.3)} \cdot \left( \frac{4.36}{4.36 + 1} \right) \Rightarrow A_v = 0.806$$

d.  $R_{ib} = r_{\pi} + (1+\beta)(R_E \parallel R_L)$

$$R_{ib} = 0.30 + (181)(0.188) \Rightarrow R_{ib} = 34.3 \text{ k}\Omega$$

$$R_o = R_E \parallel \left( \frac{r_{\pi} + R_1 \parallel R_2 \parallel R_s}{1+\beta} \right) = 0.5 \parallel \left( \frac{0.3 + 5 \parallel 1}{181} \right)$$

$$R_o = 6.18 \Omega$$

4.33

a.  $R_{TH} = R_1 \parallel R_2 = 10 \parallel 10 = 5 \text{ k}\Omega$

$$V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right) (-10) = -5 \text{ V}$$


$$V_{TH} = I_{BQ} R_{TH} + V_{BE(on)} + (1+\beta) I_{BQ} R_E - 10$$

$$I_{BQ} = \frac{-5 - 0.7 - (-10)}{5 + (121)(2)} = 0.0174 \text{ mA}$$

$$I_{CQ} = 2.09 \text{ mA}, I_{EQ} = 2.11 \text{ mA}$$

$$V_{CEQ} = 10 - (2.09)(1) - (2.11)(2)$$

$$\Rightarrow V_{CEQ} = 3.69 \text{ V}$$

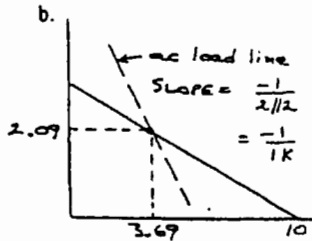

c.  $r_{\pi} = \frac{(120)(0.026)}{2.09} = 1.49 \text{ k}\Omega$

$$A_v = \frac{(1+\beta)(R_E \parallel R_L)}{r_{\pi} + (1+\beta)(R_E \parallel R_L)} \cdot \left( \frac{R_1 \parallel R_2 \parallel R_{ib}}{R_1 \parallel R_2 \parallel R_{ib} + R_s} \right)$$

$$R_{ib} = r_{\pi} + (1+\beta)(R_E \parallel R_L) = 1.49 + (121)(2 \parallel 2)$$

$$R_{ib} = 122.5 \text{ k}\Omega, R_1 \parallel R_2 \parallel R_{ib} = 5 \parallel 122.5 = 4.80 \text{ k}\Omega$$

$$A_v = \frac{(121)(2 \parallel 2)}{1.49 + (121)(2 \parallel 2)} \cdot \left( \frac{4.80}{4.80 + 5} \right) \Rightarrow$$

$$A_v = 0.484$$


d.  $R_{ib} = r_{\pi} + (1+\beta)(R_E \parallel R_L)$

$$R_{ib} = 1.49 + (121)(2 \parallel 2) \Rightarrow R_{ib} = 122 \text{ k}\Omega$$

$$R_o = R_E \parallel \left( \frac{r_{\pi} + R_1 \parallel R_2 \parallel R_s}{1+\beta} \right) = 2 \parallel \left( \frac{1.49 + 5 \parallel 5}{121} \right)$$

$$R_o = 32.5 \Omega$$

4.34

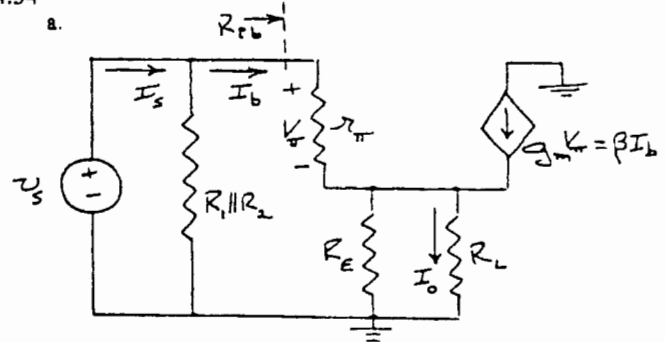

$$I_o = (1+\beta) I_b \left( \frac{R_E}{R_E + R_L} \right)$$

$$I_b = I_s \left( \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_{ib}} \right)$$

$$R_{ib} = r_{\pi} + (1+\beta)(R_E \parallel R_L)$$

$$V_{CC} = 10 \text{ V, For } V_{CEQ} = 5 \text{ V}$$

$$5 = 10 - \left( \frac{1+\beta}{\beta} \right) I_{CQ} R_E$$

$$\beta = 80, \text{ For } R_E = 0.5 \text{ k}\Omega$$

$$I_{CQ} = 9.88 \text{ mA}, I_{EQ} = 10 \text{ mA}, I_{BQ} = 0.123 \text{ mA}$$

$$r_{\pi} = \frac{(80)(0.026)}{9.88} = 0.211 \text{ k}\Omega$$

$$R_{ib} = 0.211 + (81)(0.5 \parallel 0.5) \Rightarrow R_{ib} = 20.46 \text{ k}\Omega$$

$$A_i = \frac{I_o}{I_s} = (1+\beta) \left( \frac{R_E}{R_E + R_L} \right) \left( \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_{ib}} \right)$$

$$8 = (81) \left( \frac{1}{2} \right) \left( \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + 20.46} \right)$$

$$0.1975 [R_1 \parallel R_2 + 20.46] = R_1 \parallel R_2$$

$$R_1 \parallel R_2 \Rightarrow 5.04 \text{ k}\Omega$$

$$V_{TH} = I_{BQ} R_{TH} + V_{BE(on)} + (1+\beta) I_{BQ} R_E$$

$$\frac{1}{R_1} (5.04)(10) = (0.123)(5.04) + 0.7 + (10)(0.5)$$

$$\Rightarrow R_1 = 7.97 \text{ k}\Omega$$

$$\frac{7.97 R_2}{7.97 + R_2} = 5.04 \Rightarrow R_2 = 13.7 \text{ k}\Omega$$


(b)  $R_{ib} = 0.211 + (81)(0.5 \parallel 2) = 32.6 \text{ k}\Omega$   
 $A_i = (81) \left( \frac{0.5}{0.5 + 2} \right) \left( \frac{5.04}{5.04 + 32.6} \right) = (81)(0.2)(0.134)$   
 $A_i = 2.17$

4.35

$R_i = R_{TH} \parallel R_{ib}$  where  $R_{ib} = r_\pi + (1 + \beta)R_E$   
 $V_{CEQ} = 3.5, I_{CQ} = \frac{5 - 3.5}{2} = 0.75 \text{ mA}$   
 $r_\pi = \frac{(120)(0.026)}{0.75} = 4.16 \text{ k}\Omega$   
 $R_{ib} = 4.16 + (121)(2) = 246 \text{ k}\Omega$   
 Then  $R_i = 120 = R_{TH} \parallel 245 \Rightarrow R_{TH} = 235 \text{ k}\Omega$   
 $I_{BQ} = \frac{0.75}{120} = 0.00625 \text{ mA}$   
 $V_{TH} = I_{BQ}R_{TH} + V_{BE(on)} + (1 + \beta)I_{BQ}R_E$   
 $\frac{1}{R_1} \cdot R_{TH} \cdot V_{CC} = \frac{1}{R_1} (235)(5) = (0.00625)(235)$   
 $+ 0.7 + (121)(0.00625)(2)$   
 which yields  $R_1 = 319 \text{ k}\Omega$  and  $R_2 = 892 \text{ k}\Omega$

4.36

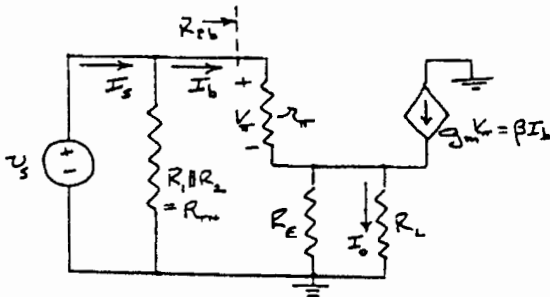a. Let  $R_E = 24 \Omega$  and  $V_{CEQ} = \frac{1}{2}V_{CC} = 12 \text{ V}$   
 $\Rightarrow I_{EQ} = \frac{12}{24} = 0.5 \text{ A}$   
 $I_{CQ} = 0.493 \text{ A}, I_{BQ} = 6.58 \text{ mA}$   
 $r_\pi = \frac{(75)(0.026)}{0.493} = 3.96 \Omega$




$I_0 = (1 + \beta)I_b \left( \frac{R_E}{R_E + R_L} \right)$   
 $I_b = I_s \left( \frac{R_{TH}}{R_{TH} + R_{ib}} \right)$   
 $R_{ib} = r_\pi + (1 + \beta)(R_E \parallel R_L)$   
 $= 3.96 + (76)(24 \parallel 8) \Rightarrow R_{ib} = 460 \Omega$   
 $A_i = \frac{I_0}{I_s} = (1 + \beta) \left( \frac{R_E}{R_E + R_L} \right) \left( \frac{R_{TH}}{R_{TH} + R_{ib}} \right)$

$8 = (76) \left( \frac{24}{24 + 8} \right) \left( \frac{R_{TH}}{R_{TH} + 460} \right)$   
 $0.140 = \frac{R_{TH}}{R_{TH} + 460}$   
 $\Rightarrow R_{TH} = 74.9 \Omega$  (Minimum value)

dc analysis:

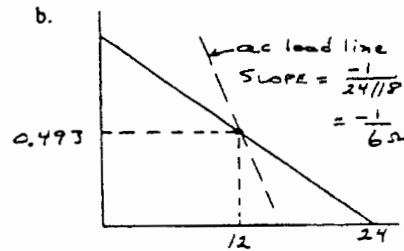$V_{TH} = \frac{1}{R_1} \cdot R_{TH} \cdot V_{CC}$   
 $= I_{BQ}R_{TH} + V_{BE(on)} + I_{EQ}R_E$   
 $\frac{1}{R_1} (74.9)(24) = (0.00658)(74.9) + 0.70$   
 $+ (0.5)(24)$   
 $= 12.75$   
 $R_1 = 136 \Omega, \frac{136R_2}{136 + R_2} = 74.9 \Rightarrow R_2 = 167 \Omega$




$\Delta i_c = -\frac{1}{6} \Delta v_{ce}$   
 For  $\Delta i_c = 0.493$   
 $\Rightarrow |\Delta v_{ce}| = (0.493)(6)$   
 $\Rightarrow \text{Max. swing in output voltage for this design}$   
 $= 5.92 \text{ V peak-to-peak}$

c.  $R_0 = \frac{r_\pi}{1 + \beta} \parallel R_E = \frac{3.96}{76} \parallel 24 = 0.0521 \parallel 24$   
 $\Rightarrow R_0 = 52 \text{ m}\Omega$

4.37

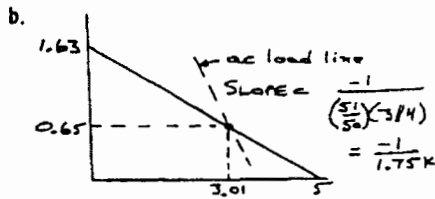a.  $R_{TH} = R_1 \parallel R_2 = 60 \parallel 40 = 24 \text{ k}\Omega$   
 $V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right) V_{CC} = \left( \frac{40}{40 + 60} \right) (5) = 2 \text{ V}$   
 $I_{BQ} = \frac{5 - 0.7 - 2}{24 + (51)(3)} = 0.0130 \text{ mA}$   
 $I_{CQ} = 0.650 \text{ mA}, I_{EQ} = 0.663 \text{ mA}$   
 $V_{ECQ} = 5 - I_{EQ}R_E = 5 - (0.663)(3)$   
 $\Rightarrow V_{CEQ} = 3.01 \text{ V}$



c.  $r_{\pi} = \frac{(50)(0.026)}{0.650} = 2 \text{ k}\Omega$ ,  $r_o = \frac{80}{0.65} = 123 \text{ k}\Omega$

Define  $R'_L = R_E \parallel R_L \parallel r_o = 3 \parallel 4 \parallel 123 = 1.69 \text{ k}\Omega$

$A_v = \frac{(1 + \beta)R'_L}{r_{\pi} + (1 + \beta)R'_L} = \frac{(51)(1.69)}{2 + (51)(1.69)}$

$\Rightarrow A_v = 0.977$

$A_i = (1 + \beta)I_b \left( \frac{R_E \parallel r_o}{R_E \parallel r_o + R_L} \right)$

$I_b = I_S \left( \frac{R_{TH}}{R_{TH} + R_{i_b}} \right)$

$R_{i_b} = r_{\pi} + (1 + \beta)R'_L = 2 + (51)(1.69) = 88.2$

$R_E \parallel r_o = 3 \parallel 123 = 2.93$

$A_i = (51) \left( \frac{2.93}{2.93 + 4} \right) \left( \frac{24}{24 + 88.2} \right)$

$\Rightarrow A_i = 4.61$

d.  $R_{i_b} = r_{\pi} + (1 + \beta)R_E \parallel R_L \parallel r_o = 2 + (51)(1.69)$

$\Rightarrow R_{i_b} = 88.2 \text{ k}\Omega$

$R_o = \frac{r_{\pi}}{1 + \beta} \parallel R_E = \left( \frac{2}{51} \right) \parallel 3 = 0.0392 \parallel 3$

$R_o = 38.7 \Omega$

e. Assume variations in  $r_{\pi}$  and  $r_o$  have negligible effects

$R_1 = 60 \pm 5\% \rightarrow R_1 = 63 \text{ k}\Omega, R_1 = 57 \text{ k}\Omega$

$R_2 = 40 \pm 5\% \rightarrow R_2 = 42 \text{ k}\Omega, R_2 = 38 \text{ k}\Omega$

$R_E = 3 \pm 5\% \rightarrow R_E = 3.15 \text{ k}\Omega, R_E = 2.85 \text{ k}\Omega$

$R_L = 4 \pm 5\% \rightarrow R_L = 4.2 \text{ k}\Omega, R_L = 3.8 \text{ k}\Omega$

$A_i = (1 + \beta) \left( \frac{R_E \parallel r_o}{R_E \parallel r_o + R_L} \right) \left( \frac{R_{TH}}{R_{TH} + R_{i_b}} \right)$

$R_{i_b} = r_{\pi} + (1 + \beta)(R_E \parallel R_L \parallel r_o)$

$R_{TH}(\text{max}) = 25.2 \text{ k}\Omega, R_{TH}(\text{min}) = 22.8 \text{ k}\Omega$

$R_{i_b}(\text{max}) = 92.5 \text{ k}\Omega, R_{i_b}(\text{min}) = 84.0 \text{ k}\Omega$

$R_E(\text{max}), R_L(\text{min}), R_{i_b} = 88.6 \text{ k}\Omega$

$R_E(\text{min}), R_L(\text{max}), R_{i_b} = 87.4 \text{ k}\Omega$

$R_E(\text{max}) \parallel r_o = 3.07 \text{ k}\Omega$

$R_E(\text{min}) \parallel r_o = 2.79 \text{ k}\Omega$

For  $R_E(\text{min}), R_L(\text{max}), R_{TH}(\text{min})$

$A_i = (51) \left( \frac{2.79}{2.79 + 4.2} \right) \left( \frac{22.8}{22.8 + 87.4} \right)$

$\Rightarrow A_i = 4.21$

For  $R_E(\text{max}), R_L(\text{min}), R_{TH}(\text{max})$


$A_i = (51) \left( \frac{3.07}{3.07 + 3.8} \right) \left( \frac{25.2}{25.2 + 88.6} \right)$

$\Rightarrow A_i = 5.05$

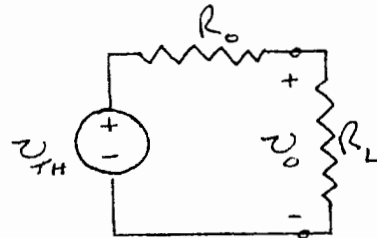4.38

The output of the emitter follower is

$v_o = \left( \frac{R_L}{R_L + R_o} \right) v_{TH}$



For  $v_o$  to be within 5% for a range of  $R_L$ , we have

$\frac{R_L(\text{min})}{R_L(\text{min}) + R_o} = (0.95) \frac{R_L(\text{max})}{R_L(\text{max}) + R_o}$

$\frac{4}{4 + R_o} = (0.95) \frac{10}{10 + R_o}$  which yields

$R_o = 0.364 \text{ k}\Omega$

We have  $R_o = \left( \frac{r_{\pi} + R_1 \parallel R_2 \parallel R_S}{1 + \beta} \right) \parallel R_E \parallel r_o$

The first term dominates

Let  $R_1 \parallel R_2 \parallel R_S \cong R_S$ , then

$R_o \cong \frac{r_{\pi} + R_S}{1 + \beta} \Rightarrow 0.364 = \frac{r_{\pi} + 4}{1 + \beta}$

or

$0.364 = \frac{r_{\pi}}{1 + \beta} + \frac{4}{1 + \beta} = \frac{\beta V_T}{I_{CQ}(1 + \beta)} + \frac{4}{1 + \beta}$

$0.364 \cong \frac{V_T}{I_{CQ}} + \frac{4}{1 + \beta}$

The factor  $\frac{4}{1 + \beta}$  is in the range of  $\frac{4}{91} = 0.044$  to

$\frac{4}{131} = 0.0305$ . We can set  $R_o \cong 0.32 = \frac{V_T}{I_{CQ}}$

Or  $I_{CQ} = 0.08125 \text{ mA}$ . To take into account other factors, set  $I_{CQ} = 0.15 \text{ mA}$ ,

$I_{BQ} = \frac{0.15}{110} = 0.00136 \text{ mA}$

For  $V_{CEQ} \cong 5 \text{ V}$ , set  $R_E = \frac{5}{0.15} = 33.3 \text{ k}\Omega$

Design a bias stable circuit.

$$V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right) (10) - 5 = \frac{1}{R_1} (R_{TH})(10) - 5$$

$$R_{TH} = (0.1)(1 + \beta)R_E = (0.1)(111)(33.3) = 370 \text{ k}\Omega$$

$$V_{TH} = I_{BQ}R_{TH} + V_{BE(on)} + (1 + \beta)I_{BQ}R_E - 5$$

$$\text{So } \frac{1}{R_1}(370)(10) - 5 = (0.00136)(370) + 0.7$$

$$+ (111)(0.00136)(33.3) - 5$$

which yields  $R_1 = 594 \text{ k}\Omega$  and  $R_2 = 981 \text{ k}\Omega$

Now

$$A_v = \frac{(1 + \beta)(R_E \parallel R_L)}{r_x + (1 + \beta)(R_E \parallel R_L)} \cdot \left( \frac{R_{TH} \parallel R_{ib}}{R_{TH} \parallel R_{ib} + R_S} \right)$$

$$R_{ib} = r_x + (1 + \beta)(R_E \parallel R_L) \text{ and } r_x = \frac{\beta V_T}{I_{CQ}}$$

For  $\beta = 90$ ,  $R_L = 4 \text{ k}\Omega$ ,

$$r_x = 15.6 \text{ k}\Omega, R_{ib} = 340.6 \text{ k}\Omega$$

$$A_v = \frac{(91)(33.3 \parallel 4)}{15.6 + (91)(33.3 \parallel 4)} \cdot \frac{370 \parallel 340.6}{370 \parallel 340.6 + 4} \Rightarrow$$

$$A_v = 0.9332$$

For  $\beta = 90$ ,  $R_L = 10 \text{ k}\Omega$

$$R_{ib} = 715.4 \text{ k}\Omega$$

$$A_v = \frac{(91)(33.3 \parallel 10)}{15.6 + (91)(33.3 \parallel 10)} \cdot \frac{370 \parallel 715.4}{370 \parallel 715.4 + 4} \Rightarrow$$

$$A_v = 0.9625$$

For  $\beta = 130$ ,  $R_L = 4 \text{ k}\Omega$

$$r_x = 22.5 \text{ k}\Omega, R_{ib} = 490 \text{ k}\Omega$$

$$A_v = \frac{(131)(33.3 \parallel 4)}{22.5 + (131)(33.3 \parallel 4)} \cdot \frac{370 \parallel 490}{370 \parallel 490 + 4} \Rightarrow$$

$$A_v = 0.9360$$

For  $\beta = 130$ ,  $R_L = 10 \text{ k}\Omega$

$$R_{ib} = 1030 \text{ k}\Omega$$

$$A_v = \frac{(131)(33.3 \parallel 10)}{22.5 + (131)(33.3 \parallel 10)} \cdot \frac{370 \parallel 1030}{370 \parallel 1030 + 4} \Rightarrow$$

$$A_v = 0.9645$$

$$\text{Now } v_o(\text{min}) = |A_v(\text{min})| \cdot v_s = 3.73 \sin \omega t$$

$$v_o(\text{max}) = |A_v(\text{max})| \cdot v_s = 3.86 \sin \omega t$$

$$\frac{\Delta v_o}{v_o} = 3.5\%$$

4.39

a.  $R_{TH} = R_1 \parallel R_2 = 40 \parallel 60 = 24 \text{ k}\Omega$

$$V_{TH} = \left( \frac{60}{60 + 40} \right) (10) = 6 \text{ V}$$

$$\beta = 75$$

$$I_{BQ} = \frac{6 - 0.7}{24 + (76)(5)} = 0.0131 \text{ mA}$$

$$I_{CQ} = 0.984 \text{ mA}$$

$$\beta = 150$$

$$I_{BQ} = \frac{6 - 0.7}{24 + (151)(5)} = 0.00680 \text{ mA}$$

$$I_{CQ} = 1.02 \text{ mA}$$

$$\beta = 75$$

$$r_x = \frac{(75)(0.026)}{0.984} = 1.98 \text{ k}\Omega$$

$$\beta = 150$$

$$r_x = 3.82 \text{ k}\Omega$$

$$\beta = 75$$

$$R_{ib} = r_x + (1 + \beta)(R_E \parallel R_L) = 65.3 \text{ k}\Omega$$

$$\beta = 150$$

$$R_{ib} = 130 \text{ k}\Omega$$

$$A_v = \frac{(1 + \beta)(R_E \parallel R_L)}{r_x + (1 + \beta)(R_E \parallel R_L)} \cdot \frac{R_1 \parallel R_2 \parallel R_{ib}}{R_1 \parallel R_2 \parallel R_{ib} + R_S}$$

For  $\beta = 75$ ,  $R_1 \parallel R_2 \parallel R_{ib} = 40 \parallel 60 \parallel 65.3 = 17.5 \text{ k}\Omega$

$$A_v = \frac{(76)(0.833)}{1.98 + (76)(0.833)} \cdot \frac{17.5}{17.5 + 4} \Rightarrow$$

$$A_v = 0.789$$

For  $\beta = 150$ ,  $R_1 \parallel R_2 \parallel R_{ib} = 40 \parallel 60 \parallel 130 = 20.3 \text{ k}\Omega$

$$A_v = \frac{(151)(0.833)}{3.82 + (151)(0.833)} \cdot \frac{20.3}{20.3 + 4} \Rightarrow$$

$$A_v = 0.811$$

$$A_i = (1 + \beta) \left( \frac{R_E}{R_E + R_L} \right) \left( \frac{R_{TH}}{R_{TH} + R_{ib}} \right)$$

$$\beta = 75$$

$$A_i = (76) \left( \frac{5}{5 + 1} \right) \left( \frac{24}{24 + 65.3} \right) \Rightarrow A_i = 17.0$$

$$\beta = 150$$

$$A_i = (151) \left( \frac{5}{6} \right) \left( \frac{24}{24 + 130} \right) \Rightarrow A_i = 19.6$$

$$17.0 < A_i < 19.6$$

b. Current gain is the same as part (a)

(b) For  $R_S = 5 \text{ k}\Omega$

$$\beta = 75 \Rightarrow A_v = 0.754$$

$$\beta = 150 \Rightarrow A_v = 0.779$$

4.40

(a)  $I_{BQ} = \frac{0.5}{81} = 0.00617 \text{ mA}$

$$V_B = I_{BQ}R_B = (0.00617)(10) \Rightarrow V_B = 0.0617 \text{ V}$$

$$V_E = V_B + 0.7 \Rightarrow V_E = 0.7617 \text{ V}$$


(b)  $I_{CQ} = (0.5) \left( \frac{80}{81} \right) = 0.494 \text{ mA}$

$g_m = \frac{I_{CQ}}{V_T} = \frac{0.494}{0.026} \Rightarrow g_m = 19 \text{ mA/V}$

$r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{(80)(0.026)}{0.494} \Rightarrow r_\pi = 4.21 \text{ k}\Omega$

$r_o = \frac{V_A}{I_{CQ}} = \frac{150}{0.494} \Rightarrow r_o = 304 \text{ k}\Omega$

(c)

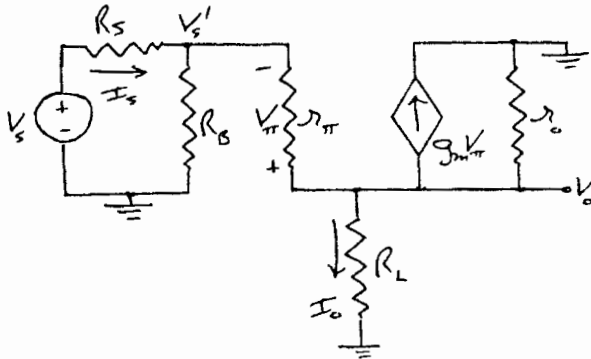

For  $R_s = 0$

$V_o = - \left( \frac{V_\pi}{r_\pi} + g_m V_\pi \right) (R_L \parallel r_o)$

so that

$V_\pi = \frac{-V_o}{\left( \frac{1+\beta}{r_\pi} \right) (R_L \parallel r_o)}$

Now

$V_s + V_\pi = V_o$

or

$V_s = V_o - V_\pi = V_o + \frac{V_o}{\left( \frac{1+\beta}{r_\pi} \right) (R_L \parallel r_o)}$

We find

$A_v = \frac{V_o}{V_s} = \frac{(1+\beta)(R_L \parallel r_o)}{r_\pi + (1+\beta)(R_L \parallel r_o)} = \frac{(81)(0.5 \parallel 304)}{4.21 + (81)(0.5 \parallel 304)}$   
 $\cong \frac{(81)(0.5)}{4.21 + (81)(0.5)} \Rightarrow A_v = 0.906$

$R_b = r_\pi + (1+\beta)(R_L \parallel r_o) \cong 4.21 + (81)(0.5) = 44.7 \text{ k}\Omega$

$I_b = \left( \frac{R_B}{R_B + R_b} \right) \cdot I_s$  and  $I_o = \left( \frac{r_o}{r_o + R_L} \right) (1+\beta) I_b$

Then

$A_i = \frac{I_o}{I_s} = (1+\beta) \left( \frac{R_B}{R_B + R_b} \right) \left( \frac{r_o}{r_o + R_L} \right)$

$A_i \cong (81) \left( \frac{10}{10 + 44.7} \right) (1) \Rightarrow A_i = 14.8$

(d)

$V_i' = \left( \frac{R_B \parallel R_{ib}}{R_B \parallel R_{ib} + R_s} \right) \cdot V_s = \left( \frac{10 \parallel 44.7}{10 \parallel 44.7 + 2} \right) \cdot V_s = (0.803) V_s$

Then

$A_v = (0.803)(0.906) \Rightarrow A_v = 0.728$

$A_i = 14.8$  (Unchanged)

4.41

$V_o = (1+\beta) I_b R_L$

$I_b = \frac{V_s}{r_\pi + (1+\beta) R_L}$

so  $A_v = \frac{(1+\beta) R_L}{r_\pi + (1+\beta) R_L}$

For  $\beta = 100$ ,  $R_L = 0.5 \text{ k}\Omega$

$r_\pi = \frac{(100)(0.026)}{0.5} = 5.2 \text{ k}\Omega$

Then  $A_v(\text{min}) = \frac{(101)(0.5)}{5.2 + (101)(0.5)} = 0.9066$

For  $\beta = 180$ ,  $R_L = 500 \text{ k}\Omega$

$r_\pi = \frac{(180)(0.026)}{0.5} = 9.36 \text{ k}\Omega$

Then  $A_v(\text{max}) = \frac{(181)(500)}{9.36 + (181)(500)} = 0.9999$

4.42

a.  $I_{EQ} = 1 \text{ mA}$ ,  $V_{CEQ} = V_{CC} - I_{EQ} R_E$

$5 = 10 - (1)(R_E) \Rightarrow R_E = 5 \text{ k}\Omega$


$I_{BQ} = \frac{1}{101} = 0.0099$

$10 = I_{BQ} R_B + V_{BE(\text{on})} + I_{EQ} R_E$

$10 = (0.0099) R_B + 0.7 + (1)(5)$

$\Rightarrow R_B = 434 \text{ k}\Omega$

b.

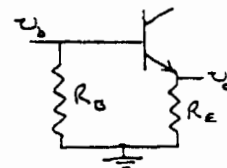


$r_\pi = \frac{(100)(0.026)}{0.99} = 2.63 \text{ k}\Omega$

$\frac{v_o}{v_b} = \frac{(1+\beta) R_E}{r_\pi + (1+\beta) R_E} = \frac{(101)(5)}{2.63 + (101)(5)} = 0.995$

$\Rightarrow v_b = \frac{v_o}{0.995} = \frac{4}{0.995}$

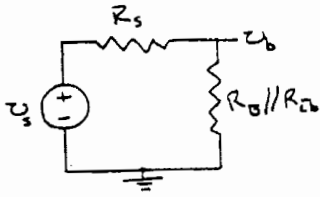$\Rightarrow v_b = 4.02 \text{ V peak-to-peak at base}$



$$R_{i,b} = r_{\pi} + (1 + \beta)R_E = 508 \text{ k}\Omega$$

$$R_B \parallel R_{i,b} = 434 \parallel 508 = 234 \text{ k}\Omega$$

$$\nu_b = \frac{R_B \parallel R_{i,b}}{R_B \parallel R_{i,b} + R_S} \cdot \nu_s = \frac{234 \nu_s}{234 + 0.7} = \frac{234}{234.7} \nu_s$$

$$\nu_b = 0.997 \nu_s$$

$$\Rightarrow \nu_s = \frac{4.02}{0.997} \Rightarrow \nu_s = 4.03 \text{ V peak-to-peak}$$

c.  $R_{i,b} = r_{\pi} + (1 + \beta)(R_E \parallel R_L)$

$$R_{i,b} = 2.63 + (101)(5 \parallel 1) = 86.8 \text{ k}\Omega$$

$$R_B \parallel R_{i,b} = 434 \parallel 86.8 = 72.3 \text{ k}\Omega$$

$$\nu_b = \left( \frac{72.3}{72.3 + 0.7} \right) \nu_s = 0.99 \nu_s = (0.99)(4.03)$$

$$\nu_b = 3.99 \text{ V peak-to-peak}$$

$$\nu_o = \frac{(1 + \beta)(R_E \parallel R_L)}{r_{\pi} + (1 + \beta)(R_E \parallel R_L)} \cdot \nu_b$$

$$= \frac{(101)(0.833)}{2.63 + (101)(0.833)} (3.99)$$

$$\nu_o = 3.87 \text{ V peak-to-peak}$$

4.43

$$P_{AVG} = i_L^2(rms)R_L \Rightarrow 1 = i_L^2(rms)(12)$$

so  $i_L(rms) = 0.289 \text{ A} \Rightarrow i_L(peak) = \sqrt{2}(0.289)$

$$i_L(peak) = 0.409 \text{ A}$$

$$\nu_L(peak) = i_L(peak) \cdot R_L = (0.409)(12) = 4.91 \text{ V}$$

Need a gain of  $\frac{4.91}{5} = 0.982$

With  $R_S = 10 \text{ k}\Omega$ , we will not be able to meet this voltage gain requirement. Need to insert a buffer or an op-amp voltage follower (see Chapter 9) between  $R_S$  and  $C_{i1}$ .

Set  $I_{EQ} = 0.5 \text{ A}$ ,  $V_{CEQ} = \frac{1}{3}(12 - (-12)) = 8 \text{ V}$

$$24 = I_{EQ}R_E + V_{CEQ} = (0.5)R_E + 8 \Rightarrow R_E = 32 \Omega$$

Let  $\beta = 50$ ,  $I_{CQ} = \frac{50}{51}(0.5) = 0.49 \text{ A}$

$$r_{\pi} = \frac{\beta V_T}{I_{CQ}} = \frac{(50)(0.026)}{0.49} = 2.65 \Omega$$

$$R_{i,b} = r_{\pi} + (1 + \beta)(R_E \parallel R_L) = 2.65 + (51)(32 \parallel 12)$$

$$R_{i,b} = 448 \Omega$$

$$I_{BQ} = \frac{0.49}{50} = 0.0098 \text{ A} = 9.8 \text{ mA}$$

Let  $I_R \equiv \frac{24}{R_1 + R_2} \equiv 10I_B = 98 \text{ mA}$

So that  $R_1 + R_2 = 245 \Omega$

$$V_{TH} = \frac{R_2}{R_1 + R_2}(24) - 12 = I_{BQ}R_{TH} + V_{BE}(on) + I_{EQ}R_E - 12$$

$$\left( \frac{R_2}{245} \right) (24) = \frac{(0.0098)R_1 R_2}{245} + 0.7 + (0.5)(32)$$

Now  $R_1 = 245 - R_2$

So we obtain

$$4 \times 10^{-5} R_2^2 + 0.0882 R_2 - 16.7 = 0$$

which yields  $R_2 = 175 \Omega$  and  $R_1 = 70 \Omega$

4.44

(a)  $R_{TH} = R_1 \parallel R_2 = 25.6 \parallel 10.4 = 7.40 \text{ k}\Omega$

$$V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right) (V_{CC}) = \left( \frac{10.4}{10.4 + 25.6} \right) (18) = 5.2 \text{ V}$$

$$V_{TH} = I_{BQ}R_{TH} + V_{BE}(on) + (1 + \beta)I_{BQ}R_E$$

$$I_{BQ} = \frac{5.2 - 0.7}{7.40 + (126)(3)}$$

Then  $I_{CQ} = 1.46 \text{ mA}$  and  $I_{EQ} = 1.47 \text{ mA}$


$$V_{CEQ} = V_{CC} - I_{CQ}R_C - I_{EQ}R_E$$

$$V_{CEQ} = 18 - (1.46)(4) - (1.47)(3) \Rightarrow V_{CEQ} = 7.75 \text{ V}$$

(b)

$$r_{\pi} = \frac{(125)(0.026)}{1.46} = 2.23 \text{ k}\Omega$$
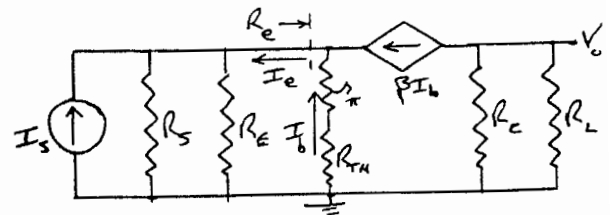
$$g_m = \frac{1.46}{0.026} = 56.2 \text{ mA/V}$$



$$R_c = \frac{r_{\pi} + R_{TH}}{1 + \beta} = \frac{2.23 + 7.40}{126} = 0.0764 \text{ k}\Omega$$

$$I_c = \frac{-(R_s \parallel R_E)}{(R_s \parallel R_E) + R_c} \cdot I_s = \frac{-(100 \parallel 3)}{(100 \parallel 3) + 0.0764} \cdot I_s$$

or  $I_c = -(0.974)I_s$

$$V_o = -I_c(R_C \parallel R_L) = -\left( \frac{\beta}{1 + \beta} \right) I_c(R_C \parallel R_L)$$

Then

$$\frac{V_o}{I_s} = -\left(\frac{\beta}{1+\beta}\right)(-0.974)(R_C \parallel R_L) = \left(\frac{125}{126}\right)(0.974)(4 \parallel 4)$$

Then

$$R_m = \frac{V_o}{I_s} = 1.93 \text{ k}\Omega = 1.93 \text{ V / mA}$$

(c)

$$V_s = I_s (R_s \parallel R_E \parallel R_r) = I_s (100 \parallel 3 \parallel 0.0764) = I_s (0.0744)$$

$$\text{or } I_s = \frac{V_s}{0.0744}$$

$$\text{which yields } \frac{V_o}{I_s} = \frac{V_o}{V_s} (0.0744) = 1.93$$

$$\text{or } A_v = \frac{V_o}{V_s} = 25.9$$

4.45

$$(a) A_v = \frac{\beta(R_C \parallel R_L)}{r_\pi + R_1 \parallel R_2}, \quad R_L = 12 \text{ k}\Omega, \quad \beta = 100$$

Let  $R_1 \parallel R_2 = 50 \text{ k}\Omega$ ,  $I_{CQ} = 0.5 \text{ mA}$

$$V_{TH} = I_{BQ} R_{TH} + V_{BE(on)} + (1 + \beta) I_{BQ} R_E$$

$$I_{BQ} = \frac{0.5}{100} = 0.005 \text{ mA}, \quad r_\pi = \frac{(100)(0.026)}{0.5} = 5.2 \text{ k}\Omega$$

$$\frac{1}{R_1} \cdot R_{TH} \cdot V_{CC} = \frac{1}{R_1} (50)(12) = (0.005)(50) + 0.7 + (101)(0.005)(0.5)$$

which yields  $R_1 = 500 \text{ k}\Omega$  and  $R_2 = 55.6 \text{ k}\Omega$

$$A_v = \frac{(100)(12 \parallel 12)}{5.2 + 50} = 10.7, \text{ Design criterion is met.}$$

(b)

$$I_{CQ} = 0.5 \text{ mA}, \quad I_{EQ} = 0.505 \text{ mA}$$

$$V_{CEQ} = 12 - (0.5)(12) - (0.505)(0.5) \Rightarrow$$

$$V_{CEQ} = 5.75 \text{ V}$$

$$A_v = g_m (R_C \parallel R_L), \quad g_m = \frac{0.5}{0.026} = 19.23 \text{ mA/V}$$

$$A_v = (19.23)(12 \parallel 12) \Rightarrow A_v = 115$$

4.46

$$i_s(\text{peak}) = 2.5 \mu\text{A}, \quad v_o(\text{peak}) = 5 \text{ mV}$$

$$\text{So we need } R_m = \frac{v_o}{i_s} = \frac{5 \times 10^{-3}}{2.5 \times 10^{-6}} = 2 \times 10^3 = 2 \text{ k}\Omega$$

From Problem 4.44

$$\frac{V_o}{I_s} = \left(\frac{\beta}{1+\beta}\right)(R_C \parallel R_L) \left(\frac{R_s \parallel R_E}{R_s \parallel R_E + R_r}\right)$$

Let  $R_C = 4 \text{ k}\Omega$ ,  $R_L = 5 \text{ k}\Omega$ ,  $R_E = 2 \text{ k}\Omega$

Now  $\beta = 120$ , so we have

$$2 = \left(\frac{120}{121}\right)(4 \parallel 5) \left(\frac{R_s \parallel R_E}{R_s \parallel R_E + R_r}\right) = 2.20 \left(\frac{R_s \parallel R_E}{R_s \parallel R_E + R_r}\right)$$

$$\text{Then } \frac{R_s \parallel R_E}{R_s \parallel R_E + R_r} = 0.909$$

$$R_s \parallel R_E = 50 \parallel 2 = 1.92 \text{ k}\Omega, \text{ so that } R_r = 0.192 \text{ k}\Omega$$

Assume  $V_{CEQ} = 6 \text{ V}$

$$V_{CC} \equiv I_{CQ}(R_C + R_E) + V_{CEQ}$$

$$12 = I_{CQ}(4 + 2) + 6 \Rightarrow I_{CQ} = 1 \text{ mA}$$

$$r_\pi = \frac{(120)(0.026)}{1} = 3.12 \text{ k}\Omega$$

$$R_r = \frac{r_\pi + R_{TH}}{1 + \beta} \Rightarrow 0.192 = \frac{3.12 + R_{TH}}{121}$$

which yields  $R_{TH} = 20.1 \text{ k}\Omega$

Now  $V_{TH} = I_{BQ} R_{TH} + V_{BE(on)} + I_{EQ} R_E$

$$I_{BQ} = \frac{1}{120} = 0.00833 \text{ mA}, \quad I_{EQ} = \left(\frac{121}{120}\right)(1) = 1.008 \text{ mA}$$

$$V_{TH} = \frac{1}{R_1} \cdot R_{TH} \cdot V_{CC} = \frac{1}{R_1} (20.1)(5) = (0.00833)(20.1) + 0.7 + (1.008)(2)$$

which yields  $R_1 = 34.9 \text{ k}\Omega$  and  $R_2 = 47.4 \text{ k}\Omega$

4.47

a. Emitter current

$$I_{EQ} = I_{CC} = 0.5 \text{ mA}$$

$$I_{BQ} = \frac{0.5}{101} = 0.00495 \text{ mA}$$

$$V_E = I_{EQ} R_E = (0.5)(1) \Rightarrow V_E = 0.5 \text{ V}$$



$$V_B = V_E + V_{BE(on)} = 0.5 + 0.7 \Rightarrow V_B = 1.20 \text{ V}$$

$$V_C = V_B + I_{BQ} R_B = 1.20 + (0.00495)(100)$$

$$\Rightarrow V_C = 1.7 \text{ V}$$

$$b. \quad r_\pi = \frac{(100)(0.026)}{(100)(0.00495)} = 5.25 \text{ k}\Omega$$
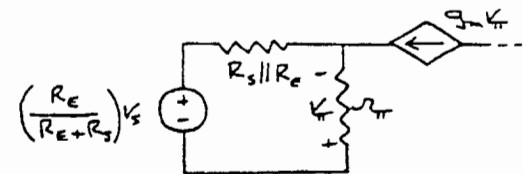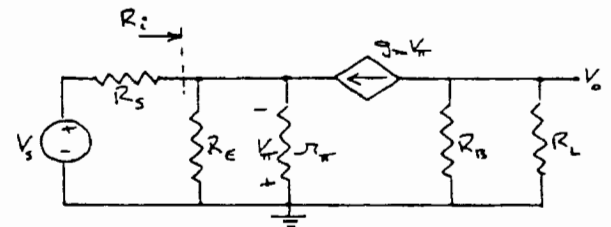
$$g_m = \frac{(100)(0.00495)}{0.026} = 19.0 \text{ mA/V}$$



$$V_o = -g_m V_\pi (R_B \parallel R_L)$$

$$g_m V_\pi + \frac{V_\pi}{r_\pi} + \frac{\left(\frac{R_E}{R_E + R_S}\right) V_S - (-V_\pi)}{R_S \parallel R_E} = 0$$

$$V_\pi \left[ g_m + \frac{1}{r_\pi} + \frac{1}{R_S \parallel R_E} \right] = \frac{-\left(\frac{R_E}{R_E + R_S}\right) V_S}{R_S \parallel R_E}$$


$$V_\pi \left[ 19.0 + \frac{1}{5.25} + \frac{1}{0.05 \parallel 1} \right] = \frac{-\left(\frac{1}{1 + 0.05}\right) V_S}{0.05 \parallel 1}$$

$$V_\pi (40.19) = -20 V_S \Rightarrow V_\pi = -(0.4976) V_S$$

$$V_o = (19)(0.4976) V_S (100 \parallel 1)$$

$$\underline{A_v = 9.36}$$

c.

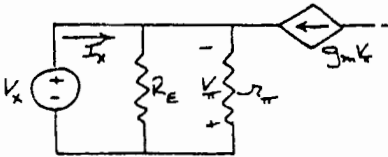

$$I_X = \frac{V_X}{R_E} + \frac{V_X}{r_\pi} - g_m V_\pi, \quad V_\pi = -V_X$$

$$\frac{I_X}{V_X} = \frac{1}{R_i} = \frac{1}{R_E} + \frac{1}{r_\pi} + g_m$$

$$\text{or } R_i = R_E \parallel r_\pi \parallel \frac{1}{g_m} = 1 \parallel 5.25 \parallel \frac{1}{19}$$

$$R_i = 0.84 \parallel 0.0526$$

$$\Rightarrow \underline{R_i = 49.5 \Omega}$$

4.48

a.  $I_{EQ} = \frac{20 - 0.7}{10} = 1.93 \text{ mA}$


$I_{CQ} = 1.91 \text{ mA}$

$$V_{ECQ} = V_{CC} + V_{EB(on)} - I_C R_C$$

$$= 25 + 0.7 - (1.91)(6.5)$$

$$\Rightarrow \underline{V_{ECQ} = 13.3 \text{ V}}$$

b.

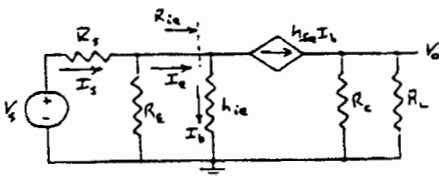

Neglect effect of  $h_{oe}$

From Problem 4-16, assume

$$2.45 \leq h_{ie} \leq 3.7 \text{ k}\Omega$$

$$80 \leq h_{fe} \leq 120$$

$$V_o = (h_{fe} I_b)(R_C \parallel R_L)$$

$$R_{ie} = \frac{h_{ie}}{1 + h_{fe}}, \quad I_e = \left(\frac{R_E}{R_E + R_{ie}}\right) I_S$$

$$I_b = \left(\frac{I_e}{1 + h_{fe}}\right), \quad I_S = \frac{V_S}{R_S + R_E \parallel R_{ie}}$$

$$A_v = \left(\frac{h_{fe}}{1 + h_{fe}}\right) (R_C \parallel R_L) \left(\frac{R_E}{R_E + R_{ie}}\right) \times \left(\frac{1}{R_S + R_E \parallel R_{ie}}\right)$$

High gain device:  $h_{ie} = 3.7 \text{ k}\Omega$ ,  $h_{fe} = 120$

$$R_{ie} = \frac{3.7}{121} = 0.0306 \text{ k}\Omega$$

$$R_E \parallel R_{ie} = 10 \parallel 0.0306 = 0.0305$$

$$A_v = \left(\frac{120}{121}\right) (6.5 \parallel 5) \left(\frac{10}{10 + 0.0306}\right) \left(\frac{1}{1 + 0.0305}\right)$$

$$\Rightarrow A_v = 2.711$$

Low gain device:  $h_{ie} = 2.45 \text{ k}\Omega$ ,  $h_{fe} = 80$

$$R_{ie} = \frac{2.45}{81} = 0.03025 \text{ k}\Omega$$

$$R_E \parallel R_{ie} = 10 \parallel 0.03025 = 0.0302$$

$$A_v = \left(\frac{80}{81}\right) (6.5 \parallel 5) \left(\frac{10}{10 + 0.03025}\right) \left(\frac{1}{1 + 0.0302}\right)$$

$$\Rightarrow A_v = 2.70 \quad \text{So } A_v \approx \text{constant}$$

$$\underline{2.70 \leq A_v \leq 2.71}$$

c.  $R_i = R_E \parallel R_{ie}$

We found  $0.0302 < R_i < 0.0305 \text{ k}\Omega$

Neglecting  $h_{oe}$ ,  $\underline{R_o = R_C = 6.5 \text{ k}\Omega}$

4.49

a. Small-signal voltage gain

$$A_v = g_m (R_C \parallel R_L) \Rightarrow 25 = g_m (R_C \parallel 1)$$

For  $V_{ECQ} = 3 \text{ V}$

$$\Rightarrow V_C = -V_{ECQ} + V_{EB(on)} = -3 + 0.7$$

$$\Rightarrow V_C = -2.3$$

$$V_{CC} - I_{CQ} R_C + V_C = 0$$

$$\Rightarrow I_{CQ} = \frac{5 - 2.3}{R_C} = \frac{2.7}{R_C} = I_{CQ}$$

For  $I_{CQ} = 1 \text{ mA}$ ,  $\underline{R_C = 2.7 \text{ k}\Omega}$

$$g_m = \frac{1}{0.026} = 38.5 \text{ mA/V}$$

$$A_v = (38.5)(2.7 \parallel 1) = \underline{28.1}$$

Design criterion satisfied and  $V_{ECQ}$  satisfied.

$$I_E = \left(\frac{101}{100}\right)(1) = 1.01 \text{ mA}$$

$$V_{EE} = I_E R_E + V_{EB(ON)}$$

$$\Rightarrow R_E = \frac{5 - 0.7}{1.01} \Rightarrow \underline{R_E = 4.26 \text{ k}\Omega}$$

$$b. \quad r_{\pi} = \frac{\beta V_T}{I_{CQ}} = \frac{(100)(0.026)}{1}$$

$$\Rightarrow \underline{r_{\pi} = 2.6 \text{ k}\Omega}, \quad \underline{g_m = 38.5 \text{ mA/V}}, \quad \underline{r_o = \infty}$$

4.50

$$a. \quad V_{TH1} = \left(\frac{R_2}{R_1 + R_2}\right)V_{CC} = \left(\frac{20}{20 + 80}\right)(10)$$

$$\Rightarrow V_{TH1} = 2.0 \text{ V}$$

$$R_{TH1} = R_1 \parallel R_2 = 20 \parallel 80 = 16 \text{ k}\Omega$$

$$I_{B1} = \frac{2 - 0.7}{16 + (101)(1)} = 0.0111 \text{ mA}$$

$$I_{C1} = 1.11 \text{ mA}$$

$$\Rightarrow g_{m1} = \frac{1.11}{0.026} \Rightarrow \underline{g_{m1} = 42.7 \text{ mA/V}}$$

$$r_{\pi 1} = \frac{(100)(0.026)}{1.11} \Rightarrow \underline{r_{\pi 1} = 2.34 \text{ k}\Omega}$$

$$r_{o1} = \frac{\infty}{1.11} \Rightarrow \underline{r_{o1} = \infty}$$

$$V_{TH2} = \left(\frac{R_4}{R_3 + R_4}\right)V_{CC} = \left(\frac{15}{15 + 85}\right)(10) = 1.50 \text{ V}$$

$$R_{TH2} = R_3 \parallel R_4 = 15 \parallel 85 = 12.75 \text{ k}\Omega$$

$$I_{B2} = \frac{1.50 - 0.70}{12.75 + (101)(0.5)} = 0.0126 \text{ mA}$$

$$I_{C2} = 1.26 \text{ mA}$$

$$\Rightarrow g_{m2} = \frac{1.26}{0.026} \Rightarrow \underline{g_{m2} = 48.5 \text{ mA/V}}$$

$$r_{\pi 2} = \frac{(100)(0.026)}{1.26} \Rightarrow \underline{r_{\pi 2} = 2.06 \text{ k}\Omega}$$

$$\underline{r_{o2} = \infty}$$

$$b. \quad A_{v1} = -g_{m1} R_{C1} = -(42.7)(2)$$

$$\Rightarrow \underline{A_{v1} = -85.4}$$

$$A_{v2} = -g_{m2}(R_{C2} \parallel R_L) = -(48.5)(4 \parallel 4)$$

$$\Rightarrow \underline{A_{v2} = -97}$$

c. Input resistance of 2nd stage

$$R_{i2} = R_3 \parallel R_4 \parallel r_{\pi 2} = 15 \parallel 85 \parallel 2.06$$

$$= 12.75 \parallel 2.06 \Rightarrow R_{i2} = 1.77 \text{ k}\Omega$$

$$A'_{v1} = -g_{m1}(R_{C1} \parallel R_{i2}) = -(42.7)(2 \parallel 1.77)$$

$$A'_{v1} = -40.1$$

$$\text{Overall gain: } A_v = (-40.1)(-97) \Rightarrow \underline{A_v = 3890}$$

$$\text{If we had } A_{v1} \cdot A_{v2} = (-85.4)(-97) = \underline{8284}$$

Loading effect reduces overall gain

4.51

$$a. \quad V_{TH1} = \left(\frac{R_2}{R_1 + R_2}\right)V_{CC} = \left(\frac{12.7}{12.7 + 67.3}\right)(12)$$

$$\Rightarrow V_{TH1} = 1.905 \text{ V}$$

$$R_{TH1} = R_1 \parallel R_2 = 12.7 \parallel 67.3 = 10.68 \text{ k}\Omega$$

$$I_{B1} = \frac{1.905 - 0.70}{10.68 + (121)(2)} = 0.00477 \text{ mA}$$

$$I_{C1} = 0.572 \text{ mA}$$

$$g_{m1} = \frac{0.572}{0.026} \Rightarrow \underline{g_{m1} = 22 \text{ mA/V}}$$

$$r_{\pi 1} = \frac{(120)(0.026)}{0.572} \Rightarrow \underline{r_{\pi 1} = 5.45 \text{ k}\Omega}$$

$$r_{o1} = \frac{\infty}{0.572} \Rightarrow \underline{r_{o1} = \infty}$$

$$V_{TH2} = \left(\frac{R_4}{R_3 + R_4}\right)V_{CC} = \left(\frac{45}{45 + 15}\right)(12)$$

$$\Rightarrow V_{TH2} = 9.0 \text{ V}$$

$$R_{TH2} = R_3 \parallel R_4 = 15 \parallel 45 = 11.25 \text{ k}\Omega$$

$$I_{B2} = \frac{9.0 - 0.70}{11.25 + (121)(1.6)} = 0.0405 \text{ mA}$$

$$I_{C2} = 4.86 \text{ mA}$$

$$g_{m2} = \frac{4.86}{0.026} \Rightarrow \underline{g_{m2} = 187 \text{ mA/V}}$$

$$r_{\pi 2} = \frac{(120)(0.026)}{4.86} \Rightarrow \underline{r_{\pi 2} = 0.642 \text{ k}\Omega}$$

$$\underline{r_{o2} = \infty}$$



$$b. \quad I_{E1} = 0.577 \text{ mA}$$

$$V_{CEQ1} = 12 - (0.572)(10) - (0.577)(2)$$

$$\Rightarrow \underline{V_{CEQ1} = 5.13 \text{ V}}$$

$$I_{E2} = 4.90$$
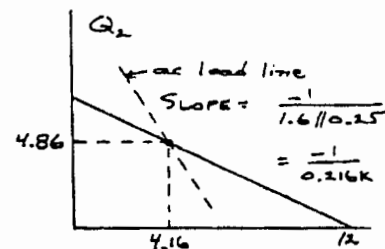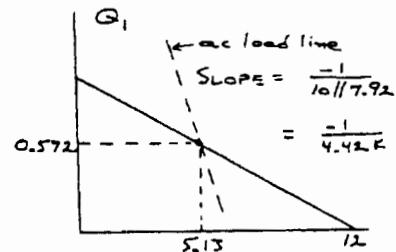
$$V_{CEQ2} = 12 - (4.90)(1.6) \Rightarrow \underline{V_{CEQ2} = 4.16 \text{ V}}$$



$$R_{i2} = R_3 \parallel R_4 \parallel R_{i_b}$$

$$R_{i_b} = r_{\pi 2} + (1 + \beta)(R_{E2} \parallel R_L)$$

$$= 0.642 + (121)(1.6 \parallel 0.25)$$

$$R_{i_b} = 26.8$$

$$R_{i2} = 15 \parallel 45 \parallel 26.8$$

$$R_{i2} = 7.92 \text{ k}\Omega$$

c.  $A_{v1} = -g_{m1}(R_{C1} \parallel R_{i2}) = -(22)(10 \parallel 7.92)$   
 $\Rightarrow A_{v2} = -97.2$

$$A_{v2} = \frac{(1 + \beta)(R_{E2} \parallel R_L)}{r_{\pi 2} + (1 + \beta)(R_{E2} \parallel R_L)}$$

$$= \frac{(121)(0.216)}{0.642 + (121)(0.216)} = 0.976$$

Overall gain =  $(-97.2)(0.976) = \underline{-94.9}$

d.  $R_{iS} = R_1 \parallel R_2 \parallel r_{\pi 1} = 67.3 \parallel 12.7 \parallel 5.45$

$$\Rightarrow R_{iS} = 3.61 \text{ k}\Omega$$

$$R_0 = \frac{r_{\pi 2} + R_S}{1 + \beta} \parallel R_{E2} \text{ where}$$

$$R_S = R_3 \parallel R_4 \parallel R_{C1}$$

$$= 15 \parallel 45 \parallel 10 \Rightarrow R_S = 5.29 \text{ k}\Omega$$

$$R_0 = \frac{0.642 + 5.29}{121} \parallel 1.6 \Rightarrow 0.049 \parallel 1.6$$

$$\Rightarrow R_0 = \underline{47.5 \Omega}$$

e.  $\Delta i_C = \frac{-1}{0.216 \text{ k}\Omega} \cdot \Delta v_{ce}$ .  $\Delta i_C = 4.86$

$$|\Delta v_{ce}| = (4.86)(0.216) = 1.05 \text{ V}$$

Max. output voltage swing  
 $= \underline{2.10 \text{ V peak-to-peak}}$

4.52

(a)  $I_{R1} = \frac{5 - 2(0.7)}{0.050} = 72 \text{ mA}$


$$I_{R2} = \frac{0.7}{0.5} = 1.4 \text{ mA}$$

$$I_{C2} = \left( \frac{\beta}{1 + \beta} \right) (72 - 1.4) \Rightarrow I_{C2} = \underline{69.9 \text{ mA}}$$

$$I_{B2} = \frac{69.9}{100} = 0.699 \text{ mA}$$

$$I_{C1} = \left( \frac{\beta}{1 + \beta} \right) (1.4 + 0.699) \Rightarrow I_{C1} = \underline{2.08 \text{ mA}}$$

(b)

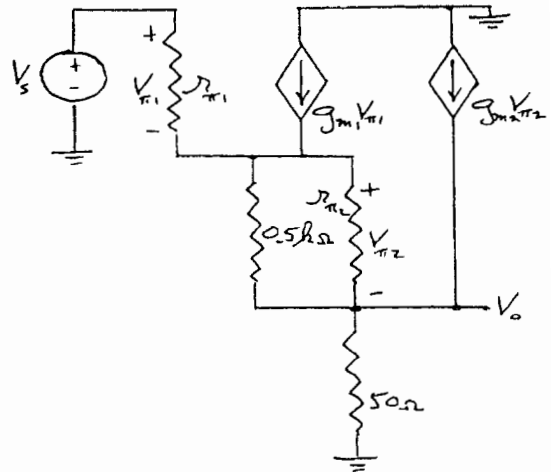

$$V_s = V_{\pi 1} + V_{\pi 2} + V_o$$

(1)  $V_o = \left( \frac{V_{\pi 2}}{0.5} + \frac{V_{\pi 2}}{r_{\pi 2}} + g_{m2} V_{\pi 2} \right) (0.05)$

$$r_{\pi 2} = \frac{(100)(0.026)}{69.9} = 0.0372 \text{ k}\Omega$$

$$g_{m2} = \frac{69.9}{0.026} = 2688 \text{ mA/V}$$

$$V_o = V_{\pi 2} \left( \frac{1}{0.05} + \frac{1}{0.0372} + 2688 \right) (0.05)$$

so that (1)  $V_{\pi 2} = \frac{V_o}{136.7}$

(2)  $\frac{V_{\pi 1}}{r_{\pi 1}} + g_{m1} V_{\pi 1} = \frac{V_{\pi 2}}{0.5} + \frac{V_{\pi 2}}{r_{\pi 2}}$

$$r_{\pi 1} = \frac{(100)(0.026)}{2.08} = 1.25 \text{ k}\Omega$$

$$g_{m1} = \frac{2.08}{0.026} = 80 \text{ mA/V}$$

$$V_{\pi 1} \left( \frac{1}{1.25} + 80 \right) = V_{\pi 2} \left( \frac{1}{0.5} + \frac{1}{0.0372} \right)$$

$$V_{\pi 1} (80.8) = V_{\pi 2} (28.88) = \left( \frac{V_o}{136.7} \right) (28.88)$$

or (2)  $V_{\pi 1} = V_o (0.00261)$


Then

$$V_s = V_o (0.00261) + \frac{V_o}{136.7} + V_o = V_o (1.00993)$$

or  $A_v = \frac{V_o}{V_s} = 0.990$

(c)
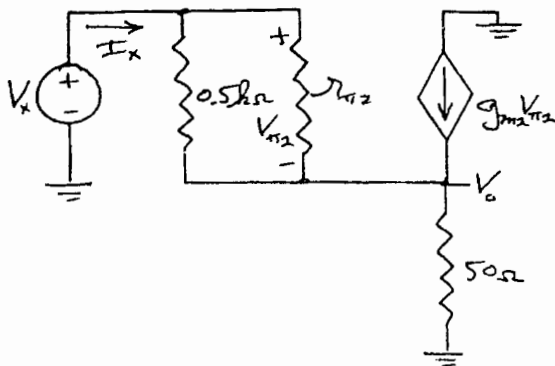
$$R_{i_b} = r_{\pi 1} + (1 + \beta)[R_s]$$




$$I_x = \frac{V_{x2}}{0.5} + \frac{V_{x2}}{r_{x2}} = V_{x2} \left( \frac{1}{0.5} + \frac{1}{r_{x2}} \right)$$

$$\frac{V_o}{0.05} = \frac{V_x - V_{x2}}{0.05} = I_x + g_{m2} V_{x2}$$

$$\frac{V_x}{0.05} - I_x = V_{x2} \left( \frac{1}{0.05} + g_{m2} \right) = \frac{I_x \left( \frac{1}{0.05} + g_{m2} \right)}{\left( \frac{1}{0.05} + \frac{1}{r_{x2}} \right)}$$

We find  $\frac{V_x}{I_x} = R_x = 2.89 \text{ k}\Omega$

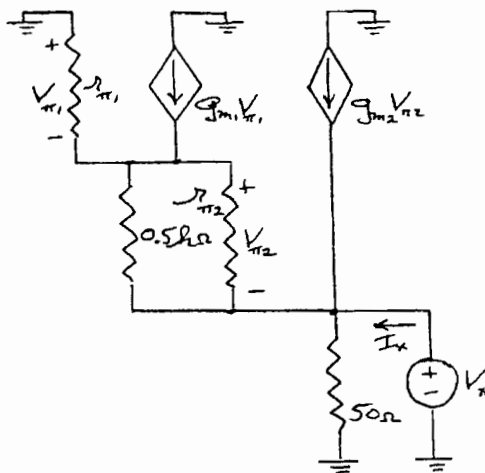Then  $R_{ib} = 1.25 + (101)(2.89) \Rightarrow R_{ib} = 293 \text{ k}\Omega$



To find  $R_o$ :

$$(1) I_x = \frac{V_x}{0.05} - g_{m2} V_{x2} - \frac{V_{x2}}{0.05 \parallel r_{x2}}$$

$$(2) V_{x2} = \left( \frac{V_{x1}}{r_{x1}} + g_{m1} V_{x1} \right) (0.05 \parallel r_{x2}) = V_{x1} \left( \frac{1}{1.25} + 80 \right) (0.05 \parallel 0.0372)$$

or  $V_{x2} = (1.72) V_{x1}$

$$(3) V_{x1} + V_{x2} + V_x = 0 \Rightarrow V_{x1} + (1.72) V_{x1} + V_x = 0$$

so that  $V_{x1} = -(0.368) V_x$

$$\text{and } V_{x2} = (1.72) [-(0.368) V_x] = -(0.633) V_x$$

$$\text{Now } I_x = \frac{V_x}{0.05} - V_{x2} \left( g_{m2} + \frac{1}{0.05 \parallel r_{x2}} \right)$$

So that

$$I_x = \frac{V_x}{0.05} + (0.633) V_x \left[ 2688 + \frac{1}{0.05 \parallel 0.0372} \right]$$

which yields

$$R_o = \frac{V_x}{I_x} = 0.583 \Omega$$

4.53

a.  $R_{TH} = R_1 \parallel R_2 = 335 \parallel 125 = 91.0 \text{ k}\Omega$

$$V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right) V_{CC}$$

$$= \left( \frac{125}{125 + 335} \right) (10) = 2.717 \text{ V}$$

$$V_{TH} = I_{B1} R_{TH} + V_{BE1} + V_{BE2} + I_{E2} R_{E2}$$

$$I_{E2} = (1 + \beta) I_{E1} = (1 + \beta)^2 I_{B1}$$

$$I_{B1} = \frac{2.717 - 1.40}{91.0 + (101)^2(1)} \Rightarrow I_{B1} = 0.128 \mu\text{A}$$

$$I_{C1} = 12.8 \mu\text{A}$$

$$I_{C2} = \beta I_{E1} = \beta(1 + \beta) I_{B1} = (100)(101)(0.128 \mu\text{A})$$

$$I_{C2} = 1.29 \text{ mA}, \quad I_{E2} = 1.31 \text{ mA}$$

$$I_{RC} = I_{C2} + I_{C1} = 1.29 + 0.0128 = 1.31 \text{ mA}$$

$$V_C = 10 - I_{RC} R_C = 10 - (1.31)(2.2) = 7.12 \text{ V}$$

$$V_E = I_{E2} R_{E2} = (1.31)(1) = 1.31 \text{ V}$$

$$V_{CE2} = 7.12 - 1.31 = 5.81 \text{ V}$$

$$V_{CE1} = V_{CE2} - V_{BE2} = 5.81 - 0.7$$

$$V_{CE1} = 5.11 \text{ V}$$


Summary:

$$I_{C1} = 12.8 \mu\text{A} \quad I_{C2} = 1.29 \text{ mA}$$

$$V_{CE1} = 5.11 \text{ V} \quad V_{CE2} = 5.81 \text{ V}$$

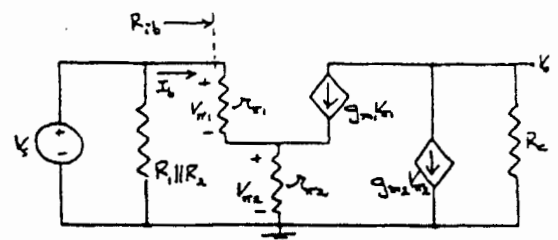b.  $g_{m1} = \frac{0.0128}{0.026} = 0.492 \text{ mA/V}$

$$g_{m2} = \frac{1.29}{0.026} = 49.6 \text{ mA/V}$$



$$V_0 = -(g_{m1}V_{\pi1} + g_{m2}V_{\pi2})R_C$$

$$V_S = V_{\pi1} + V_{\pi2}, \quad V_{\pi1} = V_S - V_{\pi2}$$

$$V_{\pi2} = \left( \frac{V_{\pi1}}{r_{\pi1}} + g_{m1}V_{\pi1} \right) r_{\pi2}$$

$$V_{\pi2} = V_{\pi1} \left( \frac{1 + \beta}{r_{\pi1}} \right) r_{\pi2}$$

$$r_{\pi1} = \frac{(100)(0.026)}{0.0128} = 203 \text{ k}\Omega$$

$$r_{\pi2} = \frac{(100)(0.026)}{1.29} = 2.02 \text{ k}\Omega$$

$$V_0 = -[g_{m1}(V_S - V_{\pi2}) + g_{m2}V_{\pi2}]R_C$$

$$V_0 = -[g_{m1}V_S + (g_{m2} - g_{m1})V_{\pi2}]R_C$$

$$V_{\pi2} = (V_S - V_{\pi2})(1 + \beta) \left( \frac{r_{\pi2}}{r_{\pi1}} \right)$$

$$V_{\pi2} \left[ 1 + (1 + \beta) \left( \frac{r_{\pi2}}{r_{\pi1}} \right) \right] = V_S(1 + \beta) \left( \frac{r_{\pi2}}{r_{\pi1}} \right)$$

$$V_0 = - \left\{ g_{m1}V_S + (g_{m2} - g_{m1}) \cdot \frac{V_S(1 + \beta) \left( \frac{r_{\pi2}}{r_{\pi1}} \right)}{1 + (1 + \beta) \left( \frac{r_{\pi2}}{r_{\pi1}} \right)} \right\} R_C$$

$$A_v = \frac{V_0}{V_S}$$

$$= - \left\{ (0.492) + \frac{(49.6 - 0.492)(101) \left( \frac{2.02}{203} \right)}{1 + (101) \left( \frac{2.02}{203} \right)} \right\} 2.2$$

$$A_v = -55.2$$

c.  $R_{i_s} = R_1 \parallel R_2 \parallel R_{i_b}$


$$R_{i_b} = r_{\pi1} + (1 + \beta)r_{\pi2}$$

$$= 203 + (101)(2.02) = 407 \text{ k}\Omega$$

$$R_{i_s} = 91 \parallel 407 = 74.4 \text{ k}\Omega = R_{i_s}$$

$$R_0 = R_C = 2.2 \text{ k}\Omega$$

4.54

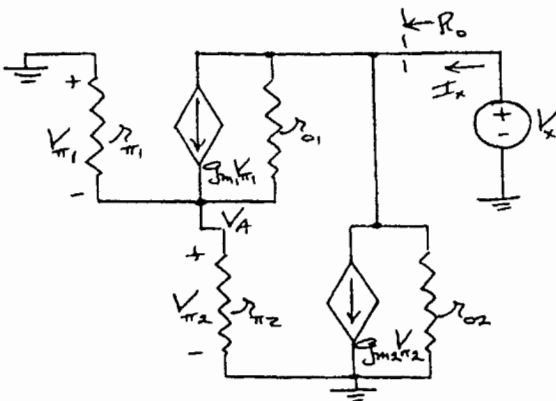

$$(1) I_x = g_{m2}V_{\pi2} + \frac{V_x}{r_{o2}} + \frac{V_x - V_A}{r_{o1}} + g_{m1}V_{\pi1}$$

$$(2) \frac{V_x - V_A}{r_{o1}} + g_{m1}V_{\pi1} = \frac{V_A}{r_{\pi1} \parallel r_{\pi2}}$$

$$(3) V_{\pi2} = V_A = -V_{\pi1}$$

Then from (2)

$$\frac{V_x}{r_{o1}} = V_A \left( \frac{1}{r_{o1}} + g_{m1} + \frac{1}{r_{\pi1} \parallel r_{\pi2}} \right)$$

$$(1) I_x = g_{m2}V_A + \frac{V_x}{r_{o2}} + \frac{V_x}{r_{o1}} - \frac{V_A}{r_{o1}} - g_{m1}V_A$$

$$\text{or } I_x = V_x \left( \frac{1}{r_{o1}} + \frac{1}{r_{o2}} \right) + V_A \left( g_{m2} - \frac{1}{r_{o1}} - g_{m1} \right)$$

Solving for  $V_A$  from Equation (2) and substituting into Equation (1), we find

$$R_o = \frac{V_x}{I_x} = \frac{\frac{1}{r_{o1}} + g_{m1} + \frac{1}{r_{\pi1} \parallel r_{\pi2}}}{\frac{1}{r_{o2}} \left( \frac{1}{r_{o1}} + g_{m1} + \frac{1}{r_{\pi1} \parallel r_{\pi2}} \right) + \frac{1}{r_{o1}} \left( \frac{1}{r_{\pi1} \parallel r_{\pi2}} + g_{m2} \right)}$$

For  $\beta = 100, V_A = 100 \text{ V}, I_{C1} = I_{Bias} = 1 \text{ mA}$

$$r_{o1} = r_{o2} = \frac{100}{1} = 100 \text{ k}\Omega$$

$$r_{\pi1} = r_{\pi2} = \frac{(100)(0.026)}{1} = 2.6 \text{ k}\Omega$$

$$g_{m1} = g_{m2} = \frac{1}{0.026} = 38.46 \text{ mA/V}$$

Then

$$R_o = \frac{\frac{1}{100} + 38.46 + \frac{1}{2.6 \parallel 2.6}}{\frac{1}{100} \left( \frac{1}{100} + 38.46 + \frac{1}{2.6 \parallel 2.6} \right) + \frac{1}{100} \left( \frac{1}{2.6 \parallel 2.6} + 38.46 \right)}$$

or

$$R_o = 50.0 \text{ k}\Omega$$

Now

$$I_{C2} = 1 \text{ mA}, I_{Bias} = 0$$

$$\text{Replace } I_{Bias} \text{ by } \frac{I_{C2}}{\beta} \cdot \frac{\beta}{1 + \beta} = \frac{I_{C2}}{1 + \beta}, \quad I_{C1} \cong 0.01 \text{ mA}$$

$$r_{o2} = \frac{100}{1} = 100 \text{ k}\Omega, \quad r_{o1} = \frac{100}{0.01} = 10,000 \text{ k}\Omega$$

$$g_{m2} = \frac{1}{0.026} = 38.46 \text{ mA/V}, \quad g_{m1} = 0.3846 \text{ mA/V}$$

$$r_{\pi2} = \frac{(100)(0.026)}{1} = 2.6 \text{ k}\Omega, \quad r_{\pi1} = 260 \text{ k}\Omega$$

Then

$$R_o = 66.4 \text{ k}\Omega$$


4.55

a.  $R_{TH} = R_1 || R_2 = 93.7 || 6.3 = 5.90 \text{ k}\Omega$   
 $V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right) V_{CC}$   
 $= \left( \frac{6.3}{6.3 + 93.7} \right) (12) = 0.756 \text{ V}$   
 $I_{BQ} = \frac{0.756 - 0.70}{5.90} = 0.00949 \text{ mA}$   
 $I_{CQ} = 0.949 \text{ mA}$   
 $V_{CEQ} = 12 - (0.949)(6) \Rightarrow V_{CEQ} = 6.31 \text{ V}$

Transistor:

$P_Q \approx I_{CQ} V_{CEQ} = (0.949)(6.31)$   
 $\Rightarrow \underline{P_Q = 5.99 \text{ mW}}$   
 $R_C: P_R = I_{CQ}^2 R_C = (0.949)^2 (6)$   
 $\Rightarrow \underline{P_R = 5.40 \text{ mW}}$

b.

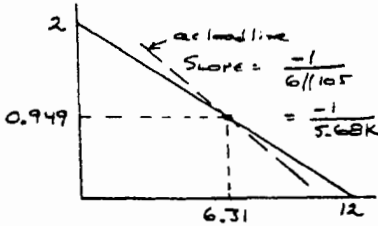

$r_o = \frac{100}{0.949} = 105 \text{ k}\Omega$

Peak signal current = 0.949 mA

$|V_o(\text{max})| = (5.68)(0.949) = 5.39 \text{ V}$

$P_{RC} = \frac{1}{2} \cdot \frac{V_o^2(\text{max})}{R_C} = \frac{1}{2} \left[ \frac{(5.39)^2}{6} \right]$

$\Rightarrow \underline{P_{RC} = 2.42 \text{ mW}}$

4.56

(a)  $10 = I_{BQ} R_B + V_{BE}(\text{on}) + (1 + \beta) I_{BQ} R_E$

$I_{BQ} = \frac{10 - 0.7}{100 + (121)(20)} = 0.00369 \text{ mA}$

$I_{CQ} = 0.443 \text{ mA}, I_{EQ} = 0.447 \text{ mA}$

For  $R_C: P_{RC} = (0.443)^2 (10) \Rightarrow \underline{P_{RC} = 1.96 \text{ mW}}$

For  $R_E: P_{RE} = (0.447)^2 (20) \Rightarrow \underline{P_{RE} = 4.0 \text{ mW}}$

(b)

$\Delta i_C = 0.443 \text{ mA}, \Delta v_{CE} = (0.443)(10) = 4.43 \text{ V}$

Then

$\overline{P_{RC}} = \frac{1}{2} (\Delta i_C)^2 R_C = \frac{1}{2} (0.443)^2 (10)$

$\underline{\overline{P_{RC}} = 0.981 \text{ mW}}$

4.57

a.  $I_{BQ} = \frac{10 - 0.7}{50 + (151)(10)} = 0.00596 \text{ mA}$

$I_{CQ} = 0.894 \text{ mA}, I_{EQ} = 0.90 \text{ mA}$

$V_{ECQ} = 20 - (0.894)(5) - (0.90)(10)$


$\Rightarrow V_{ECQ} = 6.53 \text{ V}$

$P_Q \approx I_{CQ} V_{ECQ} = (0.894)(6.53) \Rightarrow \underline{P_Q = 5.84 \text{ mW}}$

$P_{RC} \approx I_{CQ}^2 R_C = (0.894)^2 (5) \Rightarrow \underline{P_{RC} = 4.0 \text{ mW}}$

$P_{RE} \approx I_{EQ}^2 R_E = (0.90)^2 (10) \Rightarrow \underline{P_{RE} = 8.1 \text{ mW}}$

b.

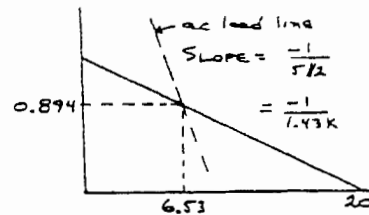

$\Delta i_C = \frac{-1}{1.43 \text{ k}\Omega} \cdot \Delta v_{ec}$

$\Delta i_C = 0.894 \Rightarrow |\Delta v_{ec}| = (0.894)(1.43) = 1.28 \text{ V}$

$\Delta i_o = \left( \frac{5}{5+2} \right) \Delta i_C = 0.639 \text{ mA}$

$\overline{P_{RL}} = \frac{1}{2} (0.639)^2 (2) \Rightarrow \underline{\overline{P_{RL}} = 0.408 \text{ mW}}$

$\overline{P_{RC}} = \frac{1}{2} \cdot (0.894 - 0.639)^2 (5) \Rightarrow \underline{\overline{P_{RC}} = 0.163 \text{ mW}}$

$\underline{\overline{P_{RE}} = 0}$

$\underline{\overline{P_Q} = 5.84 - 0.408 - 0.163 \Rightarrow \overline{P_Q} = 5.27 \text{ mW}}$


4.58

$$I_{BQ} = \frac{10 - 0.70}{100 + (101)(10)} = 0.00838 \text{ mA}$$

$$I_{CQ} = 0.838 \text{ mA}, \quad I_{EQ} = 0.846 \text{ mA}$$

$$V_{CEQ} = 20 - (0.838)(10) - (0.846)(10)$$

$$\Rightarrow V_{CEQ} = 3.16 \text{ V}$$

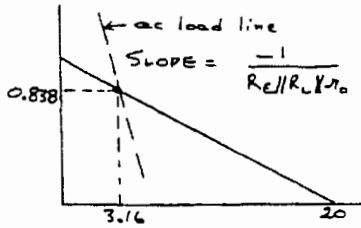

$$r_o = \frac{100}{0.838} = 119 \text{ k}\Omega$$

Neglecting base currents:

a.  $R_L = 1 \text{ k}\Omega$

$$\text{slope} = \frac{-1}{10 \parallel 1 \parallel 119} = \frac{-1}{0.902 \text{ k}\Omega}$$

$$\Delta i_C = \frac{-1}{0.902 \text{ k}\Omega} \cdot \Delta v_{ce}$$

$$\Delta i_C = 0.838 \Rightarrow |\Delta v_{ce}| = (0.902)(0.838) = 0.756 \text{ V}$$

$$\overline{P_{RL}} = \frac{1}{2} \frac{(0.756)^2}{1} \Rightarrow \overline{P_{RL}} = 0.286 \text{ mW}$$

b.  $R_L = 10 \text{ k}\Omega$

$$\text{slope} = \frac{-1}{10 \parallel 10 \parallel 119} = \frac{-1}{4.80}$$

For

$$\Delta i_C = 0.838 \Rightarrow |\Delta v_{ce}| = (0.838)(4.80) = 4.02$$

Max. swing determined by voltage

$$\overline{P_{RL}} = \frac{1}{2} \frac{(3.16)^2}{10} \Rightarrow \overline{P_{RL}} = 0.499 \text{ mW}$$

4.59

a.  $I_{BQ} = \frac{10 - 0.7}{100 + (101)(10)} = 0.00838 \text{ mA}$

$$I_{CQ} = 0.838 \text{ mA}, \quad I_{EQ} = 0.846 \text{ mA}$$


$$V_{CEQ} = 20 - (0.838)(10) - (0.846)(10)$$

$$\Rightarrow V_{CEQ} = 3.16 \text{ V}$$

$$P_Q \approx I_{CQ} V_{CEQ} = (0.838)(3.16) \Rightarrow \underline{P_Q = 2.65 \text{ mW}}$$

$$P_{RC} \approx I_{CQ}^2 R_C = (0.838)^2 (10) \Rightarrow \underline{P_{RC} = 7.02 \text{ mW}}$$

b.

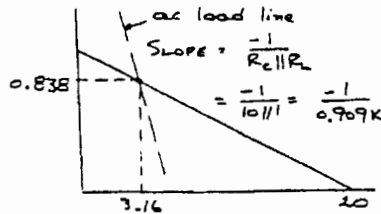

$$\Delta i_C = \frac{-1}{0.909 \text{ k}\Omega} \cdot \Delta v_{ce}$$

For

$$\Delta i_C = 0.838 \Rightarrow |\Delta v_{ce}| = (0.909)(0.838) = 0.762 \text{ V}$$

$$\Delta i_o = \left( \frac{R_C}{R_C + R_L} \right) \Delta i_C = \left( \frac{10}{10 + 1} \right) \Delta i_C = 0.762 \text{ mA}$$

$$\overline{P_{RL}} = \frac{1}{2} (0.762)^2 (1) \Rightarrow \overline{P_{RL}} = 0.290 \text{ mW}$$

$$\overline{P_{RC}} = \frac{1}{2} \cdot (0.838 - 0.762)^2 (10) \Rightarrow \overline{P_{RC}} = 0.0289 \text{ mW}$$

$$\overline{P_Q} = 2.65 - 0.290 - 0.0289 \Rightarrow \underline{\overline{P_Q} = 2.33 \text{ mW}}$$



## Chapter 5

## Exercise Solutions

E5.1

(a)  $V_{TN} = 1.2\text{ V}$ ,  $V_{GS} = 2\text{ V}$

$V_{DS}(sat) = V_{GS} - V_{TN} = 2 - 1.2 = 0.8\text{ V}$

(i)  $V_{DS} = 0.4 \Rightarrow$  Nonsaturation

(ii)  $V_{DS} = 1 \Rightarrow$  Saturation

(iii)  $V_{DS} = 5 \Rightarrow$  Saturation

(b)  $V_{TN} = -1.2\text{ V}$ ,  $V_{GS} = 2\text{ V}$

$V_{DS}(sat) = V_{GS} - V_{TN} = 2 - (-1.2) = 3.2\text{ V}$

(i)  $V_{DS} = 0.4 \Rightarrow$  Nonsaturation

(ii)  $V_{DS} = 1 \Rightarrow$  Nonsaturation

(iii)  $V_{DS} = 5 \Rightarrow$  Saturation

E5.2

(a)  $K_n = \frac{W\mu_n C_{ox}}{2L}$

$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = \frac{(3.9)(8.85 \times 10^{-14})}{450 \times 10^{-8}} = 7.67 \times 10^{-8}\text{ F/cm}$

$K_n = \frac{(100)(500)(7.67 \times 10^{-8})}{2(7)} \Rightarrow K_n = 0.274\text{ mA/V}^2$

(b)  $V_{TN} = 1.2\text{ V}$ ,  $V_{GS} = 2\text{ V}$

(i)  $V_{DS} = 0.4\text{ V} \Rightarrow$  Nonsaturation

$I_D = (0.274) \left[ 2(2 - 1.2)(0.4) - (0.4)^2 \right] \Rightarrow$

$I_D = 0.132\text{ mA}$

(ii)  $V_{DS} = 1\text{ V} \Rightarrow$  Saturation

$I_D = (0.274)(2 - 1.2)^2 \Rightarrow I_D = 0.175\text{ mA}$

(iii)  $V_{DS} = 5\text{ V} \Rightarrow$  Saturation

$I_D = (0.274)(2 - 1.2)^2 \Rightarrow I_D = 0.175\text{ mA}$

$V_{TN} = -1.2\text{ V}$ ,  $V_{GS} = 2\text{ V}$

(i)  $V_{DS} = 0.4\text{ V} \Rightarrow$  Nonsaturation

$I_D = (0.274) \left[ 2(2 + 1.2)(0.4) - (0.4)^2 \right] \Rightarrow$

$I_D = 0.658\text{ mA}$

(ii)  $V_{DS} = 1\text{ V} \Rightarrow$  Nonsaturation

$I_D = (0.274) \left[ 2(2 + 1.2)(1) - (1)^2 \right] \Rightarrow I_D = 1.48\text{ mA}$

(iii)  $V_{DS} = 5\text{ V} \Rightarrow$  Saturation

$I_D = (0.274)(2 + 1.2)^2 \Rightarrow I_D = 2.81\text{ mA}$

E5.3

$V_{TN} = 1\text{ V}$ ,  $V_{GS} = 3\text{ V}$ ,  $V_{DS} = 4.5\text{ V}$

$V_{DS} = 4.5 > V_{DS}(sat) = V_{GS} - V_{TN} = 3 - 1 = 2\text{ V}$

Transistor biased in the saturation region

$I_D = K_n(V_{GS} - V_{TN})^2 \Rightarrow 0.8 = K_n(3 - 1)^2 \Rightarrow$

$K_n = 0.2\text{ mA/V}^2$

(a)  $V_{GS} = 2\text{ V}$ ,  $V_{DS} = 4.5\text{ V}$

Saturation region:

$I_D = (0.2)(2 - 1)^2 \Rightarrow I_D = 0.2\text{ mA}$

(b)  $V_{GS} = 3\text{ V}$ ,  $V_{DS} = 1\text{ V}$

Nonsaturation region:

$I_D = (0.2) \left[ 2(3 - 1)(1) - (1)^2 \right] \Rightarrow I_D = 0.6\text{ mA}$

E5.4

(a)  $V_{TP} = -2\text{ V}$ ,  $V_{SG} = 3\text{ V}$

$V_{SD}(sat) = V_{SG} + V_{TP} = 3 - 2 = 1\text{ V}$

(i)  $V_{SD} = 0.5\text{ V} \Rightarrow$  Nonsaturation

(ii)  $V_{SD} = 2\text{ V} \Rightarrow$  Saturation

(iii)  $V_{SD} = 5\text{ V} \Rightarrow$  Saturation

(b)  $V_{TP} = 0.5\text{ V}$ ,  $V_{SG} = 3\text{ V}$

$V_{SD}(sat) = V_{SG} + V_{TP} = 3 + 0.5 = 3.5\text{ V}$

(i)  $V_{SD} = 0.5\text{ V} \Rightarrow$  Nonsaturation

(ii)  $V_{SD} = 2\text{ V} \Rightarrow$  Nonsaturation

(iii)  $V_{SD} = 5\text{ V} \Rightarrow$  Saturation

E5.5

(a)  $\lambda = 0$ ,  $V_{DS}(sat) = 2.5 - 0.8 = 1.7\text{ V}$

For  $V_{DS} = 2\text{ V}$ ,  $V_{DS} = 10\text{ V} \Rightarrow$  Saturation Region

$I_D = (0.1)(2.5 - 0.8)^2 \Rightarrow I_D = 0.289\text{ mA}$

(b)  $\lambda = 0.02\text{ V}^{-1}$

$I_D = K_n(V_{GS} - V_{TN})^2(1 + \lambda V_{DS})$

For  $V_{DS} = 2\text{ V}$ 

$I_D = (0.1)(2.5 - 0.8)^2 [1 + (0.02)(2)] \Rightarrow$

$I_D = 0.300\text{ mA}$

$V_{DS} = 10\text{ V}$

$I_D = (0.1) \left[ (2.5 - 0.8)^2 (1 + (0.02)(10)) \right] \Rightarrow$

$I_D = 0.347\text{ mA}$

(c) For part (a),  $\lambda = 0 \Rightarrow r_o = \infty$

For part (b),  $\lambda = 0.02\text{ V}^{-1}$ ,

$r_o = \left[ \lambda K_n (V_{GS} - V_{TN})^2 \right]^{-1} = \left[ (0.02)(0.1)(2.5 - 0.8)^2 \right]^{-1}$

or  $r_o = 173\text{ k}\Omega$

E5.6

$$V_{TN} = V_{TNO} + \gamma \left[ \sqrt{2\phi_f + V_{SB}} - \sqrt{2\phi_f} \right]$$

$$2\phi_f = 0.70 \text{ V}, \quad V_{TNO} = 1 \text{ V}$$

(a)  $V_{SB} = 0 \Rightarrow V_{TN} = 1 \text{ V}$

(b)  $V_{SB} = 1 \text{ V},$   
 $V_{TN} = 1 + (0.35) \left[ \sqrt{0.7 + 1} - \sqrt{0.7} \right] \Rightarrow V_{TN} = 1.16 \text{ V}$

(c)  $V_{SB} = 4 \text{ V},$   
 $V_{TN} = 1 + (0.35) \left[ \sqrt{0.7 + 4} - \sqrt{0.7} \right] \Rightarrow V_{TN} = 1.47 \text{ V}$

E5.7

$$V_G = \left( \frac{R_2}{R_1 + R_2} \right) (10) - 5 = \left( \frac{40}{40 + 60} \right) (10) - 5$$

$$V_G = -1 \text{ V}$$

$$V_S = I_D R_S - 5$$

Then

$$V_{GS} = V_G - V_S = -1 - (I_D R_S - 5) = 4 - I_D R_S$$

Assume transistor is biased in saturation region

$$I_D = K_n (V_{GS} - V_{TN})^2 = \frac{4 - V_{GS}}{R_S}$$

$$4 - V_{GS} = (0.5)(0.1) [V_{GS} - 1]^2 \Rightarrow$$

$$0.5V_{GS}^2 - 3.5 = 0 \Rightarrow V_{GS} = 2.65 \text{ V}$$

$$I_D = (0.5)(2.65 - 1)^2 \Rightarrow I_D = 1.36 \text{ mA}$$

$$V_{DS} = 10 - I_D (R_S + R_D) = 10 - (1.36)(1 + 2) \Rightarrow$$

$$V_{DS} = 5.92 \text{ V}$$

$V_{DS} > V_{DS}(sat)$ , Yes

E5.8

$$V_G = \left( \frac{R_2}{R_1 + R_2} \right) (10) - 5$$

$$= \left( \frac{200}{350} \right) (10) - 5 = 0.714 \text{ V}$$

$$V_S = 5 - I_D R_S = 5 - (1.2)I_D$$

So

$$V_{SG} = V_S - V_G = 5 - (1.2)I_D - 0.714$$

$$= 4.286 - (1.2)I_D$$

$$I_D = \frac{4.286 - V_{SG}}{1.2}$$

$$I_D = K_p (V_{SG} + V_{TP})^2$$

$$4.286 - V_{SG} = (1.2)(0.25) \times$$

$$(V_{SG}^2 - 2V_{SG}(-1) + (-1)^2)$$

$$4.286 - V_{SG} = (0.3)V_{SG}^2 - 0.6V_{SG} + 0.3$$

$$0.3V_{SG}^2 + 0.4V_{SG} - 3.986 = 0$$

$$V_{SG} = \frac{-0.4 \pm \sqrt{(0.4)^2 + 4(0.3)(3.986)}}{2(0.3)}$$

Must use + sign  $\Rightarrow V_{SG} = 3.04 \text{ V}$

$$I_D = (0.25)(3.04 - 1)^2 \Rightarrow I_D = 1.04 \text{ mA}$$

$$V_{SD} = 10 - I_D (R_S + R_D) = 10 - (1.04)(1.2 + 4)$$

$$\Rightarrow V_{SD} = 4.59 \text{ V}$$

$V_{SD} > V_{SD}(sat)$ , Yes

E5.9

$$I_D = K_n (V_{GS} - V_{TN})^2$$

$$0.4 = 0.25(V_{GS} - 0.8)^2 \Rightarrow V_{GS} = 2.06 \text{ V}$$

$$V_{GS} = \left( \frac{R_2}{R_1 + R_2} \right) V_{DD}$$

$$2.06 = \left( \frac{R_2}{250} \right) (7.5) \Rightarrow R_2 = 68.7 \text{ k}\Omega$$

$$R_1 = 181.3 \text{ k}\Omega$$

$$V_{DS} = 4 = V_{DD} - I_D R_D$$

$$R_D = \frac{7.5 - 4}{0.4} \Rightarrow R_D = 8.75 \text{ k}\Omega$$

$V_{DS} > V_{DS}(sat)$ , Yes

E5.10

$$I_D = \frac{V_S - (-5)}{R_S} \text{ and } V_S = -V_{GS}$$

$$\text{So } R_S = \frac{5 - V_{GS}}{0.1}$$

$$I_D = K_n (V_{GS} - V_{TN})^2$$

$$0.1 = (0.080)(V_{GS} - 1.2)^2 \Rightarrow V_{GS} = 2.32 \text{ V}$$

$$\text{So } R_S = \frac{5 - 2.32}{0.1} \Rightarrow R_S = 26.8 \text{ k}\Omega$$

$$V_{DS} = V_D - V_S \Rightarrow V_D = V_{DS} + V_S = 4.5 - 2.32$$

$$V_D = 2.18$$

$$R_D = \frac{5 - V_D}{I_D} = \frac{5 - 2.18}{0.1} \Rightarrow R_D = 28.2 \text{ k}\Omega$$

$V_{DS} > V_{DS}(sat)$ , Yes

E5.11

$$I_D = \frac{10 - V_{SG}}{R_S} \text{ and } I_D = K_p (V_{SG} + V_{TP})^2$$

$$0.12 = (0.050)(V_{SG} - 0.8)^2$$

$$V_{SG} = 2.35 \text{ V}$$

$$R_S = \frac{10 - 2.35}{0.12} \Rightarrow R_S = 63.75 \text{ k}\Omega$$

$$V_{SD} = 8 = 20 - I_D (R_S + R_D)$$

$$8 = 20 - (0.12)(63.75) - (0.12)R_D$$

$$R_D = \frac{20 - (0.12)(63.75) - 8}{0.12}$$

$$\Rightarrow R_D = 36.25 \text{ k}\Omega$$

E5.12

$$I_D = \frac{V_{DD} - V_{GS}}{R_S}, \quad I_D = K_n (V_{GS} - V_{TN})^2$$

$$10 - V_{GS} = (10)(0.2)(V_{GS}^2 - 2V_{GS}V_{TN} + V_{TN}^2)$$

$$10 - V_{GS} = 2V_{GS}^2 - 8V_{GS} + 8$$

$$2V_{GS}^2 - 7V_{GS} - 2 = 0$$

$$V_{GS} = \frac{7 \pm \sqrt{(7)^2 + 4(2)2}}{2(2)}$$

Use + sign:  $V_{GS} = V_{DS} = 3.77 \text{ V}$

$$I_D = \frac{10 - 3.77}{10} \Rightarrow I_D = 0.623 \text{ mA}$$

$$\text{Power} = I_D V_{DS} = (0.623)(3.77)$$

$$\Rightarrow \text{Power} = 2.35 \text{ mW}$$

E5.13

For  $V_{DS} = 2.2 \text{ V}$

$$I_D = \frac{5 - 2.2}{5} \Rightarrow I_D = 0.56 \text{ mA}$$

$$I_D = K_n (V_{GS} - V_{TN})^2$$

$$0.56 = K_n (2.2 - 1)^2$$

$$K_n = 0.389 \text{ mA/V} = \frac{W}{L} \cdot \frac{\mu_n C_{ox}}{2}$$

$$\frac{W}{L} = \frac{(389)(2)}{(40)} \Rightarrow \frac{W}{L} = 19.5$$

E5.14

(a) The transition point is

$$V_h = \frac{V_{DD} - V_{TNL} + V_{TND}(1 + \sqrt{K_{nD}/K_{nL}})}{1 + \sqrt{K_{nD}/K_{nL}}}$$

$$= \frac{5 - 1 + 1(1 + \sqrt{0.05/0.01})}{1 + \sqrt{0.05/0.01}}$$

$$= \frac{7.236}{3.236} \Rightarrow V_{IL} = 2.24 \text{ V}$$

$$V_{OL} = V_h - V_{TND} = 2.24 - 1 \Rightarrow V_{OL} = 1.24 \text{ V}$$

(b) We may write

$$I_D = K_{nD}(V_{GSD} - V_{TND})^2 = (0.05)(2.24 - 1)^2$$

$$\Rightarrow I_D = 76.9 \mu\text{A}$$

E5.15

$$V_h = \frac{V_{DD} - V_{TNL} + V_{TND}(1 + \sqrt{K_{nD}/K_{nL}})}{1 + \sqrt{K_{nD}/K_{nL}}}$$

$$2.5 = \frac{5 - 1 + 1(1 + \sqrt{K_{nD}/K_{nL}})}{1 + \sqrt{K_{nD}/K_{nL}}}$$

$$2.5 + 2.5\sqrt{K_{nD}/K_{nL}} = 5 + \sqrt{K_{nD}/K_{nL}} \Rightarrow$$

$$\sqrt{K_{nD}/K_{nL}} = \frac{5 - 2.5}{1.5} = 1.67 \Rightarrow$$

$$K_{nD}/K_{nL} = 2.78$$

b. For  $V_I = 5$ , driver in nonsaturated region.

$$I_{DD} = I_{DL}$$

$$K_{nD}[2(V_I - V_{TND})V_O - V_O^2] = K_{nL}(V_{GSL} - V_{TNL})^2$$

$$\frac{K_{nD}}{K_{nL}}[2(V_I - V_{TND})V_O - V_O^2] = [V_{DD} - V_O - V_{TNL}]^2$$

$$2.78[2(5 - 1)V_O - V_O^2] = [5 - V_O - 1]^2$$

$$22.24V_O - 2.78V_O^2 = (4 - V_O)^2$$

$$= 16 - 8V_O + V_O^2$$

$$3.78V_O^2 - 30.24V_O + 16 = 0$$

$$V_O = \frac{30.24 \pm \sqrt{(30.24)^2 - 4(3.78)(16)}}{2(3.78)}$$

$$\Rightarrow V_O = 0.57 \text{ V}$$

E5.16

If the transistor is biased in the saturation region

$$I_D = K_n (V_{GS} - V_{TN})^2 = K_n (-V_{TN})^2$$

$$I_D = (0.25)(2.5)^2 \Rightarrow I_D = 1.56 \text{ mA}$$

$$V_{DS} = V_{DD} - I_D R_S = 10 - (1.56)(4)$$

$$\Rightarrow V_{DS} = 3.76$$

$$V_{DS} > V_{GS} - V_{TN} = -V_{TN}$$

$$3.76 > -(-2.5)$$

Yes  $\rightarrow$  biased in the saturation region

$$\text{Power} = I_D V_{DS} = (1.56)(3.76)$$

$$\Rightarrow \text{Power} = 5.87 \text{ mW}$$

E5.17

We have  $V_{DS} = 1.2 \text{ V} < V_{GS} - V_{TN} = -V_{TN} = 1.8 \text{ V}$   
 Transistor is biased in the nonsaturation region.

$$I_D = K_n [2(V_{GS} - V_{TN})V_{DS} - V_{DS}^2]$$

and

$$I_D = \frac{V_{DD} - V_{DS}}{R_S} = \frac{5 - 1.2}{8} \Rightarrow$$

$$I_D = 0.475 \text{ mA}$$

$$0.475 = K_n [2(0 - (-1.8))(1.2) - (1.2)^2]$$

$$0.475 = K_n (2.88) \Rightarrow K_n = 0.165 \text{ mA/V}^2$$

$$K_n = \frac{W}{L} \cdot \frac{\mu_n C_{ox}}{2}$$

$$\frac{W}{L} = \frac{(165)(2)}{35} \Rightarrow \frac{W}{L} = 9.43$$

E5.18

(a) Transition point for the load transistor – Driver is in the saturation region.

$$I_{DD} = I_{DL}$$

$$K_{nD}(V_{GS D} - V_{TND})^2 = K_{nL}(V_{GS L} - V_{TNL})^2$$

$$V_{DSL}(sat) = V_{GSL} - V_{TNL} = -V_{TNL}$$

$$\Rightarrow V_{DSL} = V_{DD} - V_{OL} = 2V$$

$$\text{Then } V_{OL} = 5 - 2 = 3V, \quad V_{OL} = 3V$$

$$\sqrt{\frac{K_{nD}}{K_{nL}}}(V_{IL} - 1) = (-V_{TNL})$$

$$\sqrt{\frac{0.08}{0.01}}(V_{IL} - 1) = 2 \Rightarrow \underline{V_{IL} = 1.89V}$$

(b) For the driver:

$$V_{OL} = V_{IL} - V_{TND}$$

$$\underline{V_{IL} = 1.89V, \quad V_{OL} = 0.89V}$$

E5.19

(a) For  $V_I = 5V$ , Load in saturation and driver in nonsaturation.

$$I_{DD} = I_{DL}$$

$$K_{nD}[2(V_I - V_{TND})V_O - V_O^2] = K_{nL}(-V_{TNL})^2$$

$$\frac{K_{nD}}{K_{nL}}[2(5-1)(0.25) - (0.25)^2] = 4 \Rightarrow$$

$$\frac{K_{nD}}{K_{nL}} = 2.06$$

$$(b) I_{DL} = K_{nL}(-V_{TNL})^2 \Rightarrow 0.2 = K_{nL}[(-2)]^2$$

$$\underline{K_{nL} = 50 \mu A/V^2 \quad \text{and} \quad K_{nD} = 103 \mu A/V^2}$$

E5.20

$$(a) I_{REF} = K_{n3}(V_{GS3} - V_{TN})^2 = K_{n4}(V_{GS4} - V_{TN})^2$$

$$V_{GS3} = 2V \Rightarrow V_{GS4} = 3V$$

$$(2-1)^2 = \frac{K_{n4}}{K_{n3}}(3-1)^2 \Rightarrow \frac{K_{n4}}{K_{n3}} = \frac{1}{4}$$

$$(b) I_Q = K_{n2}(V_{GS2} - V_{TN})^2$$

$$\text{But } V_{GS2} = V_{GS3} = 2V$$

$$0.1 = K_{n2}(2-1)^2 \Rightarrow \underline{K_{n2} = 0.1 \text{ mA}/V^2}$$

$$(c) 0.2 = K_{n3}(2-1)^2 \Rightarrow \underline{K_{n3} = 0.2 \text{ mA}/V^2}$$

$$0.2 = K_{n4}(3-1)^2 \Rightarrow \underline{K_{n4} = 0.05 \text{ mA}/V^2}$$

E5.21

For  $R_D = 10 \text{ k}\Omega$ ,  $V_{DD} = 5V$ , and  $V_o = 1V$

$$I_D = \frac{5-1}{10} = 0.4 \text{ mA}$$

$$I_D = K_n[2(V_{GS} - V_{TN})V_{DS} - V_{DS}^2]$$

$$I_D = 0.4 = K_n[2(5-1)(1) - (1)^2] \Rightarrow$$

$$\underline{K_n = 0.057 \text{ mA}/V^2}$$

$$P = I_D \cdot V_{DS} = (0.4)(1) \Rightarrow \underline{P = 0.4 \text{ mW}}$$

E5.22

$$I_D = K_n[2(V_{GS} - V_{TN})V_{DS} - V_{DS}^2]$$

$$= (0.050)[2(10 - 0.7)(0.35) - (0.35)^2];$$

$$I_D = 0.319 \text{ mA}$$

$$R_D = \frac{V_{DD} - V_o}{I_D} = \frac{10 - 0.35}{0.319}$$

$$\Rightarrow \underline{R_D = 30.3 \text{ k}\Omega}$$

E5.23

(a) Transistor biased in the nonsaturation region

$$I_D = \frac{5-1.5-V_{DS}}{R} = 12$$

$$I_D = K_n[2(V_{GS} - V_{TN})V_{DS} - V_{DS}^2]$$

$$12 = 4[2(5-0.8)V_{DS} - V_{DS}^2]$$

$$4V_{DS}^2 - 33.6V_{DS} + 12 = 0 \Rightarrow \underline{V_{DS} = 0.374V}$$

Then

$$R = \frac{5-1.5-0.374}{12} \Rightarrow \underline{R = 261 \Omega}$$

E5.24

a.  $V_1 = 5V$ ,  $V_2 = 0$ ,  $M_2$  cutoff  $\Rightarrow I_{D2} = 0$

$$I_D = K_n[2(V_I - V_{TN})V_O - V_O^2] = \frac{5-V_O}{R_D}$$

$$(0.05)(30)[2(5-1)V_O - V_O^2] = 5 - V_O$$

$$1.5V_O^2 - 13V_O + 5 = 0$$

$$V_O = \frac{13 \pm \sqrt{(13)^2 - 4(1.5)(5)}}{2(1.5)} \Rightarrow \underline{V_O = 0.40V}$$

$$I_R = I_{D1} = \frac{5-0.40}{30} \Rightarrow \underline{I_R = I_{D1} = 0.153 \text{ mA}}$$

b.  $V_1 = V_2 = 5V$

$$\frac{5-V_O}{R_D} = 2\{K_n[2(V_I - V_{TN})V_O - V_O^2]\}$$

$$5 - V_O = 2(0.05)(30)[2(5-1)V_O - V_O^2];$$

$$3V_O^2 - 25V_O + 5 = 0$$

$$V_0 = \frac{25 \pm \sqrt{(25)^2 - 4(3)(5)}}{2(3)} \Rightarrow \underline{V_0 = 0.205 \text{ V}}$$

$$I_R = \frac{5 - 0.205}{30} \Rightarrow \underline{I_R = 0.160 \text{ mA}}$$

$$\underline{I_{D1} = I_{D2} = 0.080 \text{ mA}}$$

E5.25

$$(a) I_D = \frac{5 - V_0}{R_D} = K_n [2(V_2 - V_{TN})V_0 - V_0^2]$$

$$\frac{5 - (0.10)}{25} = K_n [2(5 - 1)(0.10) - (0.10)^2] \Rightarrow$$

$$\underline{K_n = 0.248 \text{ mA/V}^2}$$

$$b. \frac{5 - V_0}{25} = 2(0.248)[2(5 - 1)V_0 - V_0^2]$$

$$5 - V_0 = 12.4[8V_0 - V_0^2]$$

$$12.4V_0^2 - 100.2V_0 + 5 = 0$$

$$V_0 = \frac{100.2 \pm \sqrt{(100.2)^2 - 4(12.4)(5)}}{2(12.4)}$$

$$\Rightarrow \underline{V_0 = 0.0502 \text{ V}}$$

E5.26

$$V_{DS}(\text{sat}) = V_{GS} - V_P = -1.2 - (-4.5)$$

$$\Rightarrow \underline{V_{DS}(\text{sat}) = 3.3 \text{ V}}$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2 = 12 \left(1 - \frac{(-1.2)}{(-4.5)}\right)^2$$

$$\Rightarrow \underline{I_D = 6.45 \text{ mA}}$$

E5.27

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$1.2 = 2 \left(1 - \frac{V_{GS}}{(-2.5)}\right)^2 \Rightarrow \underline{V_{GS} = -0.564 \text{ V}}$$

E5.28

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$3 = I_{DSS} \left(1 - \frac{0.8}{3.8}\right)^2 \Rightarrow \underline{I_{DSS} = 4.81 \text{ mA}}$$

$$V_{SD}(\text{sat}) = V_P - V_{GS} = 3.8 - 0.8$$

$$\underline{V_{SD}(\text{sat}) = 3.0 \text{ V}}$$

E5.29

$$I_D = K(V_{GS} - V_{TN})^2$$

$$a. V_{GS} = 0.35 \Rightarrow I_D = 25(0.35 - 0.25)^2$$

$$\Rightarrow \underline{I_D = 0.25 \mu\text{A}}$$

$$b. V_{GS} = 0.50 \Rightarrow I_D = 25(0.50 - 0.25)^2$$

$$\Rightarrow \underline{I_D = 1.56 \mu\text{A}}$$

E5.30

Assume the transistor is biased in the saturation region.

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$8 = 18 \left(1 - \frac{V_{GS}}{(-3.5)}\right)^2 \Rightarrow \underline{V_{GS} = -1.17 \text{ V}}$$

$$\Rightarrow V_S = -V_{GS} = 1.17$$

$$V_D = 15 - (8)(0.8) = 8.6$$

$$V_{DS} = 8.6 - (1.17) = 7.43 \text{ V}$$

$$V_{DS} = 7.43 > V_{GS} - V_P = -1.17 - (-3.5)$$

$$= 2.33$$

Yes, the transistor is biased in the saturation region.

E5.31

$$I_D = 2.5 \text{ mA}$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$2.5 = 6 \left(1 - \frac{V_{GS}}{(-4)}\right)^2 \Rightarrow \underline{V_{GS} = -1.42 \text{ V}}$$

$$V_S = I_D R_S - 5 = (2.5)(0.25) - 5$$

$$V_S = -4.375$$

$$V_{DS} = 6 \Rightarrow V_D = 6 - 4.375 = 1.625$$

$$R_D = \frac{5 - 1.625}{2.5} \Rightarrow \underline{R_D = 1.35 \text{ k}\Omega}$$

$$\frac{(20)^2}{R_1 + R_2} = 2 \Rightarrow R_1 + R_2 = 200 \text{ k}\Omega$$

$$V_G = V_{GS} + V_S = -1.42 - 4.375 = -5.795$$

$$V_G = \left(\frac{R_2}{R_1 + R_2}\right)(20) - 10$$

$$-5.795 = \left(\frac{R_2}{200}\right)(20) - 10 \Rightarrow$$

$$\underline{R_2 = 42.05 \text{ k}\Omega} \rightarrow \underline{42 \text{ k}\Omega}$$

$$\underline{R_1 = 157.95 \text{ k}\Omega} \rightarrow \underline{158 \text{ k}\Omega}$$

E5.32

$$V_S = -V_{GS}, \quad I_D = \frac{0 - V_S}{R_S} = \frac{V_{GS}}{R_S}$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$\frac{V_{GS}}{1} = 6 \left(1 - \frac{V_{GS}}{4}\right)^2 = 6 \left(1 - \frac{V_{GS}}{2} + \frac{V_{GS}^2}{16}\right)$$

$$0.375V_{GS}^2 - 4V_{GS} + 6 = 0$$

$$V_{GS} = \frac{4 \pm \sqrt{16 - 4(0.375)(6)}}{2(0.375)}$$

$$\underline{V_{GS} = 8.86} \quad \text{or} \quad \underline{V_{GS} = 1.81 \text{ V}}$$

impossible

$$I_D = \frac{V_{GS}}{R_S} = 1.81 \text{ mA}$$

$$V_D = I_D R_D - 5 = (1.81)(0.4) - 5 = -4.276$$

$$V_{SD} = V_S - V_D = -1.81 - (-4.276)$$

$$\Rightarrow \underline{V_{SD} = 2.47 \text{ V}}$$

$$V_{SD}(\text{sat}) = V_P - V_{GS} = 4 - 1.81 = 2.19$$

So  $V_{SD} > V_{SD}(\text{sat})$ 

E5.34

$$I_{DQ} = K(V_{GS} - V_{TN})^2 \Rightarrow 5 = 50(V_{GS} - 0.15)^2$$

$$\Rightarrow \underline{V_{GS} = 0.466 \text{ V}}$$

$$V_S = (0.005)(10) = 0.050 \text{ V}$$

$$\Rightarrow V_{GG} = V_{GS} + V_S = 0.466 + 0.050$$

$$\Rightarrow \underline{V_{GG} = 0.516 \text{ V}}$$

$$V_D = 5 - (0.005)(100) \Rightarrow V_D = 4.5 \text{ V}$$

$$V_{DS} = V_D - V_S = 4.5 - 0.050$$

$$\Rightarrow \underline{V_{DS} = 4.45 \text{ V}}$$

E5.35

$$I_D = K[2(V_{GS} - V_{TN})V_{DS} - V_{DS}^2]$$

$$= 100[2(0.7 - 0.2)(0.1) - (0.1)^2]$$

$$I_D = 9 \mu\text{A}$$

$$R_D = \frac{2.5 - 0.1}{0.009} \Rightarrow \underline{R_D = 267 \text{ k}\Omega}$$

E5.33

$$R_{in} = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2} = 100 \text{ k}\Omega$$

$$I_{DQ} = 5 \text{ mA}, \quad V_S = -I_{DQ} R_S = -(5)(1.2) = -6 \text{ V}$$

$$V_{SDQ} = 12 \text{ V} \Rightarrow V_D = V_S - V_{SDQ}$$

$$= -6 - 12 = -18 \text{ V}$$

$$R_D = \frac{-18 - (-20)}{5} \Rightarrow \underline{R_D = 0.4 \text{ k}\Omega}$$

$$I_{DQ} = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2 \Rightarrow 5 = 8 \left(1 - \frac{V_{GS}}{4}\right)^2$$

$$V_{GS} = 0.838 \text{ V}$$

$$V_G = V_{GS} + V_S = 0.838 - 6 = -5.162$$

$$V_G = \left(\frac{R_2}{R_1 + R_2}\right)(-20)$$

$$-5.162 = \frac{1}{R_1}(100)(-20) \Rightarrow \underline{R_1 = 387 \text{ k}\Omega}$$

$$\frac{R_1 R_2}{R_1 + R_2} = 100 \Rightarrow (387)R_2 = 100(387) + 100R_2$$

$$(387 - 100)R_2 = (100)(387)$$

$$\Rightarrow \underline{R_2 = 135 \text{ k}\Omega}$$

## Chapter 5

## Problem Solutions

5.1

$$(a) V_{DS} = 6V > V_{GS} - V_{TN} = 5 - 1.5 = 3.5V$$

Biased in the saturation region

$$I_D = K_n (V_{GS} - V_{TN})^2 = (0.25)(5 - 1.5)^2 \Rightarrow$$

$$I_D = 3.06 \text{ mA}$$

$$(b) V_{DS} = 2.5V < V_{DS}(\text{sat}) = 3.5V$$

Biased in nonsaturation region

$$I_D = K_n [2(V_{GS} - V_{TN})V_{DS} - V_{DS}^2]$$

$$I_D = (0.25)[2(5 - 1.5)(2.5) - (2.5)^2] \Rightarrow$$

$$I_D = 2.81 \text{ mA}$$

5.2

$$(a) I_D = \frac{k'_n}{2} \cdot \frac{W}{L} (V_{GS} - V_{TN})^2$$

$$0.5 = \left(\frac{0.080}{2}\right)(5)(V_{GS} - 0.8)^2$$

$$\sqrt{\frac{0.5}{0.2}} + 0.8 = V_{GS} \Rightarrow V_{GS} = 2.38V$$

$$V_{DS}(\text{sat}) = V_{GS} - V_{TN} = 2.38 - 0.8 \Rightarrow$$

$$V_{DS}(\text{sat}) = 1.58V$$

$$(b) 1.5 = \left(\frac{0.080}{2}\right)(5)(V_{GS} - 0.8)^2$$

$$\sqrt{\frac{1.5}{0.2}} + 0.8 = V_{GS} \Rightarrow V_{GS} = 3.54V$$

$$V_{DS}(\text{sat}) = 3.54 - 0.8 \Rightarrow V_{DS}(\text{sat}) = 2.74V$$

5.3

$$a. V_{GS} = 0$$

$$V_{DS}(\text{sat}) = V_{GS} - V_{TN} = 0 - (-2.5) = 2.5V$$

$$i. V_{DS} = 0.5V \Rightarrow \text{Biased in nonsaturation}$$

$$I_D = (1.1)[2(0 - (-2.5))(0.5) - (0.5)^2]$$

$$\Rightarrow I_D = 2.48 \text{ mA}$$

$$ii. V_{DS} = 2.5V \Rightarrow \text{Biased in saturation}$$

$$I_D = (1.1)(0 - (-2.5))^2$$

$$\Rightarrow I_D = 6.88 \text{ mA}$$

$$iii. V_{DS} = 5V \text{ Same as (ii)} \Rightarrow I_D = 6.88 \text{ mA}$$

$$b. V_{GS} = 2V$$

$$V_{DS}(\text{sat}) = 2 - (-2.5) = 4.5V$$

$$i. V_{DS} = 0.5V \Rightarrow \text{Nonsaturation}$$

$$I_D = (1.1)[2(2 - (-2.5))(0.5) - (0.5)^2]$$

$$\Rightarrow I_D = 4.68 \text{ mA}$$

$$ii. V_{DS} = 2.5V \Rightarrow \text{Nonsaturation}$$

$$I_D = (1.1)[2(2 - (-2.5))(2.5) - (2.5)^2]$$

$$\Rightarrow I_D = 17.9 \text{ mA}$$

$$iii. V_{DS} = 5V \Rightarrow \text{Saturation}$$

$$I_D = (1.1)(2 - (-2.5))^2$$

$$\Rightarrow I_D = 22.3 \text{ mA}$$

5.4

$$V_{DS} > V_{GS} - V_{TN} = 0 - (-2) = 2V$$

Biased in the saturation region

$$I_D = \frac{k'_n}{2} \cdot \frac{W}{L} (V_{GS} - V_{TN})^2$$

$$1.5 = \left(\frac{0.080}{2}\right)\left(\frac{W}{L}\right)[0 - (-2)]^2 \Rightarrow \frac{W}{L} = 9.375$$

5.5

$$a. C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = \frac{(3.9)(8.85 \times 10^{-14})}{450 \times 10^{-8}}$$

$$\Rightarrow \frac{\epsilon_{ox}}{t_{ox}} = 7.67 \times 10^{-8} \text{ F/cm}^2$$

$$K_n = \frac{\mu_n C_{ox}}{2} \cdot \frac{W}{L}$$

$$= \frac{1}{2}(650)(7.67 \times 10^{-8})\left(\frac{64}{4}\right)$$

$$K_n = 0.399 \text{ mA/V}^2$$

$$b. V_{GS} = V_{DS} = 3V \Rightarrow \text{Saturation}$$

$$I_D = K_n (V_{GS} - V_{TN})^2 = (0.399)(3 - 0.8)^2$$

$$\Rightarrow I_D = 1.93 \text{ mA}$$

5.6

$$a. C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = \frac{(3.9)(8.85 \times 10^{-14})}{600 \times 10^{-8}}$$

$$\Rightarrow \frac{\epsilon_{ox}}{t_{ox}} = 5.75 \times 10^{-8} \text{ F/cm}^2$$

$$K_n = \frac{\mu_n C_{ox}}{2} \cdot \frac{W}{L}$$

$$= \frac{1}{2}(500)(5.75 \times 10^{-8})\left(\frac{100}{5}\right) \Rightarrow$$

$$K_n = 0.288 \text{ mA/V}^2$$

b. i.  $V_{GS} = 0, V_{DS} = 5 \text{ V}$

$$V_{DS}(\text{sat}) = 0 - (-2) = 2 \text{ V}$$

Biased in saturation

$$I_D = (0.288)(0 - (-2))^2 \Rightarrow \underline{I_D = 1.15 \text{ mA}}$$

ii.  $V_{GS} = 2 \text{ V}, V_{DS} = 1 \text{ V}$

$$V_{DS}(\text{sat}) = 2 - (-2) = 4 \text{ V}$$

Nonsaturation

$$I_D = (0.288)[2(2 - (-2))(1) - (1)^2]$$

$$\Rightarrow \underline{I_D = 2.02 \text{ mA}}$$

5.7

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = \frac{(3.9)(8.85 \times 10^{-14})}{400 \times 10^{-8}}$$

$$= 8.63 \times 10^{-8} \text{ F/cm}^2$$

$$K_n = \frac{\mu_n C_{ox} \cdot W}{2 \cdot L}$$

$$= \frac{1}{2}(600)(8.63 \times 10^{-8}) \left( \frac{W}{2.5} \right)$$

$$\underline{K_n = (1.04 \times 10^{-5})W}$$

$$I_D = K_n (V_{GS} - V_{TN})^2$$

$$1.2 \times 10^{-3} = (1.04 \times 10^{-5})W(5 - 1)^2$$

$$\Rightarrow \underline{W = 7.21 \text{ } \mu\text{m}}$$

5.8

Biased in the saturation region in both cases.

$$I_D = \frac{k'_p}{2} \cdot \frac{W}{L} (V_{SG} + V_{TP})^2$$

$$(1) 0.225 = \left( \frac{0.040}{2} \right) \left( \frac{W}{L} \right) (3 + V_{TP})^2$$

$$(2) 1.40 = \left( \frac{0.040}{2} \right) \left( \frac{W}{L} \right) (4 + V_{TP})^2$$

Take ratio of (2) to (1):

$$\frac{1.40}{0.225} = 6.222 = \frac{(4 + V_{TP})^2}{(3 + V_{TP})^2}$$

$$\sqrt{6.222} = 2.49 = \frac{4 + V_{TP}}{3 + V_{TP}} \Rightarrow \underline{V_{TP} = -2.33 \text{ V}}$$

Then

$$0.225 = \left( \frac{0.040}{2} \right) \left( \frac{W}{L} \right) (3 - 2.33)^2 \Rightarrow \underline{\frac{W}{L} = 25.1}$$

5.9

$$V_S = 5 \text{ V}, V_G = 0 \Rightarrow V_{SG} = 5 \text{ V}$$

$$V_{TP} = -0.5 \text{ V}$$

$$\Rightarrow V_{SD}(\text{sat}) = V_{SG} + V_{TP} = 5 - 0.5 = 4.5 \text{ V}$$

a.  $V_D = 0 \Rightarrow V_{SD} = 5 \text{ V}$

$\Rightarrow$  Biased in saturation

$$I_D = 2(5 - 0.5)^2 \Rightarrow \underline{I_D = 40.5 \text{ mA}}$$

b.  $V_D = 2 \text{ V} \Rightarrow V_{SD} = 3 \text{ V}$

$\Rightarrow$  Nonsaturation

$$I_D = 2[2(5 - 0.5)(3) - (3)^2]$$

$$\Rightarrow \underline{I_D = 36 \text{ mA}}$$

c.  $V_D = 4 \text{ V} \Rightarrow V_{SD} = 1 \text{ V}$

$\Rightarrow$  Nonsaturation

$$I_D = 2[2(5 - 0.5)(1) - (1)^2]$$

$$\Rightarrow \underline{I_D = 16 \text{ mA}}$$

d.  $V_D = 5 \text{ V} \Rightarrow V_{SD} = 0 \Rightarrow \underline{I_D = 0}$

5.10

$$V_{SD}(\text{sat}) = V_{SG} + V_{TP}$$

(a)  $V_{SD}(\text{sat}) = -1 + 2 \Rightarrow V_{SD}(\text{sat}) = 1 \text{ V}$

(b)  $V_{SD}(\text{sat}) = 0 + 2 \Rightarrow V_{SD}(\text{sat}) = 2 \text{ V}$

(c)  $V_{SD}(\text{sat}) = 1 + 2 \Rightarrow V_{SD}(\text{sat}) = 3 \text{ V}$

$$I_D = \frac{k'_p}{2} \cdot \frac{W}{L} (V_{SG} + V_{TP})^2 = \frac{k'_p}{2} \cdot \frac{W}{L} [V_{SD}(\text{sat})]^2$$

(a)  $I_D = \left( \frac{0.040}{2} \right) (6)(1)^2 \Rightarrow \underline{I_D = 0.12 \text{ mA}}$

(b)  $I_D = \left( \frac{0.040}{2} \right) (6)(2)^2 \Rightarrow \underline{I_D = 0.48 \text{ mA}}$

(c)  $I_D = \left( \frac{0.040}{2} \right) (6)(3)^2 \Rightarrow \underline{I_D = 1.08 \text{ mA}}$

5.11

$$V_{SD}(\text{sat}) = V_{SG} + V_{TP} = 0 + 2 = 2 \text{ V}$$

(a)  $V_{SD} = 1 \text{ V}$ , Nonsaturation

$$I_D = K_p [2(V_{SG} + V_{TP})V_{SD} - V_{SD}^2]$$

$$I_D = (0.5)[2(0 + 2)(1) - (1)^2] \Rightarrow \underline{I_D = 1.5 \text{ mA}}$$

(b)  $V_{SD} = 2 \text{ V}$ , Saturation

$$I_D = K_p (V_{SG} + V_{TP})^2 = (0.5)(0 + 2)^2 \Rightarrow$$

$$\underline{I_D = 2 \text{ mA}}$$

(c)  $V_{SD} = 3 \text{ V}$ , Saturation

Same as (b),  $\underline{I_D = 2 \text{ mA}}$

5.12

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = \frac{(3.9)(8.85 \times 10^{-14})}{500 \times 10^{-8}} = 6.90 \times 10^{-8} \text{ F/cm}^2$$

$$k'_n = (\mu_n C_{ox}) = (675)(6.90 \times 10^{-8}) \Rightarrow 46.6 \mu\text{A/V}^2$$

$$k'_p = (\mu_p C_{ox}) = (375)(6.90 \times 10^{-8}) \Rightarrow 25.9 \mu\text{A/V}^2$$

PMOS:

$$I_D = \frac{k'_p}{2} \left(\frac{W}{L}\right)_p (V_{SG} + V_{TP})^2$$

$$0.8 = \left(\frac{0.0259}{2}\right) \left(\frac{W}{L}\right)_p (5 - 0.6)^2$$

$$\Rightarrow \left(\frac{W}{L}\right)_p = 3.19$$

$$L = 4 \mu\text{m} \Rightarrow \underline{W_p = 12.8 \mu\text{m}}$$

$$K_p = \left(\frac{0.0259}{2}\right)(3.19) \Rightarrow \underline{K_p = 41.3 \mu\text{A/V}^2 = K_n}$$

Want  $K_n = K_p$

$$\frac{k'_n}{2} \left(\frac{W}{L}\right)_n = \frac{k'_p}{2} \left(\frac{W}{L}\right)_p = 41.3$$

$$\left(\frac{46.6}{2}\right) \left(\frac{W}{L}\right)_n = 41.3 \Rightarrow \left(\frac{W}{L}\right)_n = 1.77$$

$$L = 4 \mu\text{m} \Rightarrow \underline{W_n = 7.08 \mu\text{m}}$$

5.13

$$V_{GS} = 2 \text{ V}, I_D = (0.2)(2 - 1.2)^2 = 0.128 \text{ mA}$$

$$r_o = \frac{1}{\lambda I_D} = \frac{1}{(0.01)(0.128)} \Rightarrow \underline{r_o = 781 \text{ k}\Omega}$$

$$V_{GS} = 4 \text{ V}, I_D = (0.2)(4 - 1.2)^2 = 1.57 \text{ mA}$$

$$r_o = \frac{1}{(0.01)(1.57)} \Rightarrow \underline{r_o = 63.7 \text{ k}\Omega}$$

$$V_A = \frac{1}{\lambda} = \frac{1}{(0.01)} \Rightarrow \underline{V_A = 100 \text{ V}}$$

5.14

$$I_D = \left(\frac{0.080}{2}\right)(4)(3 - 0.8)^2 = (0.16)(3 - 0.8)^2 \Rightarrow$$

$$I_D = 0.774 \text{ mA}$$

$$r_o = \frac{1}{\lambda I_D} \Rightarrow \lambda = \frac{1}{r_o I_D} = \frac{1}{(200)(0.774)} \Rightarrow$$

$$\underline{\lambda(\text{max}) = 0.00646 \text{ V}^{-1}}$$

$$V_A(\text{min}) = \frac{1}{\lambda(\text{max})} = \frac{1}{0.00646} \Rightarrow \underline{V_A(\text{min}) = 155 \text{ V}}$$

5.15

$$V_{TN} = V_{TNO} + \gamma \left[ \sqrt{2\phi_f + V_{SB}} - \sqrt{2\phi_f} \right]$$

$$\Delta V_{TN} = 2 = (0.8) \left[ \sqrt{2\phi_f + V_{SB}} - \sqrt{2(0.35)} \right]$$

$$2.5 + 0.837 = \sqrt{2(0.35) + V_{SB}} \Rightarrow \underline{V_{SB} = 10.4 \text{ V}}$$

5.16

$$\Delta V_{TN} = \gamma \left[ \sqrt{2\phi_f + V_{SB}} - \sqrt{2\phi_f} \right]$$

$$1.2 = \gamma \left[ \sqrt{2(0.37) + 10} - \sqrt{2(0.37)} \right] = \gamma(2.42)$$

$$\text{Then } \gamma = 0.496 \text{ V}^{1/2}$$

5.17

$$\text{a. } V_G = \epsilon_{ox} t_{ox} = (6 \times 10^6)(275 \times 10^{-8})$$

$$\underline{V_G = 16.5 \text{ V}}$$

$$\text{b. } V_G = \frac{16.5}{3} \Rightarrow \underline{V_G = 5.5 \text{ V}}$$

5.18

$$\text{Want } V_G = (3)(24) = \epsilon_{ox} t_{ox} = (6 \times 10^6) t_{ox}$$

$$\underline{t_{ox} = 1.2 \times 10^{-5} \text{ cm} = 1200 \text{ Angstroms}}$$

5.19

$$V_{GS} = \left(\frac{R_2}{R_1 + R_2}\right) V_{DD} = \left(\frac{18}{18 + 32}\right)(10) = 3.6 \text{ V}$$

Assume transistor biased in saturation region

$$I_D = \frac{V_S}{R_S} = \frac{V_G - V_{GS}}{R_S} = K_n (V_{GS} - V_{TN})^2$$

$$3.6 - V_{GS} = (0.5)(2)(V_{GS} - 0.8)^2 = V_{GS}^2 - 1.6V_{GS} + 0.64$$

$$V_{GS}^2 - 0.6V_{GS} - 2.96 = 0$$

$$V_{GS} = \frac{0.6 \pm \sqrt{(0.6)^2 + 4(2.96)}}{2}$$

$$\Rightarrow \underline{V_{GS} = 2.05 \text{ V}}$$

$$I_D = \frac{V_G - V_{GS}}{R_S} = \frac{3.6 - 2.05}{2} \Rightarrow \underline{I_D = 0.775 \text{ mA}}$$

$$V_{DS} = V_{DD} - I_D(R_D + R_S)$$

$$= 10 - (0.775)(4 + 2)$$

$$\Rightarrow \underline{V_{DS} = 5.35 \text{ V}}$$

$$\underline{V_{DS} > V_{DS}(\text{sat})}$$

5.20

$$V_G = \left( \frac{R_2}{R_1 + R_2} \right) (20) - 10 = \left( \frac{6}{14 + 6} \right) (20) - 10 \Rightarrow$$

$$V_G = -4 \text{ V}$$

Assume transistor is biased in saturation region

$$I_D = \frac{V_S - (-10)}{R_S} = \frac{V_G - V_{GS} + 10}{R_S} = K_n (V_{GS} - V_{TN})^2$$

$$K_n = \left( \frac{0.060}{2} \right) (60) \Rightarrow 1.8 \text{ mA/V}^2$$

$$-4 - V_{GS} + 10 = (1.8)(0.5)(V_{GS} - 2)^2$$

$$= 0.9V_{GS}^2 - 3.6V_{GS} + 3.6$$

$$\text{Then } 0.9V_{GS}^2 - 2.6V_{GS} - 2.4 = 0$$

$$V_{GS} = \frac{2.6 \pm \sqrt{(2.6)^2 + 4(0.9)(2.4)}}{2(0.9)} \Rightarrow \underline{V_{GS} = 3.62 \text{ V}}$$

$$I_D = \frac{V_G - V_{GS} + 10}{R_S} = \frac{-4 - 3.62 + 10}{0.5} \Rightarrow$$

$$\underline{I_D = 4.76 \text{ mA}}$$

$$V_{DS} = 20 - I_D(R_D + R_S) = 20 - (4.76)(1.2 + 0.5) \Rightarrow$$

$$\underline{V_{DS} = 11.9 \text{ V}}$$

$$\underline{V_{DS} = 11.9 \text{ V} > V_{GS} - V_{TN} = 3.62 - 2 = 1.62 \text{ V}}$$

5.21

$$I_D = \frac{10 - V_S}{R_S} = K_p (V_{SG} + V_{TP})^2$$

Assume transistor biased in saturation region

$$V_G = \left( \frac{R_2}{R_1 + R_2} \right) (20) - 10$$

$$= \left( \frac{22}{8 + 22} \right) (20) - 10$$

$$\Rightarrow \underline{V_G = 4.67 \text{ V}}$$

$$V_S = V_G + V_{SG}$$

$$10 - (4.67 + V_{SG}) = (1)(0.5)(V_{SG} - 2)^2$$

$$5.33 - V_{SG} = 0.5(V_{SG}^2 - 4V_{SG} + 4)$$

$$0.5V_{SG}^2 - V_{SG} - 3.33 = 0$$

$$V_{SG} = \frac{1 \pm \sqrt{(1)^2 + 4(0.5)(3.33)}}{2(0.5)}$$

$$\Rightarrow \underline{V_{SG} = 3.77 \text{ V}}$$

$$I_D = \frac{10 - (4.67 + 3.77)}{0.5} \Rightarrow \underline{I_D = 3.12 \text{ mA}}$$

$$V_{SD} = 20 - I_D(R_S + R_D)$$

$$= 20 - (3.12)(0.5 + 2)$$

$$\Rightarrow \underline{V_{SD} = 12.2 \text{ V}}$$

$$\underline{V_{SD} > V_{SD}(\text{sat})}$$

5.22

$$V_G = 0, \quad V_{SG} = V_S$$

Assume saturation region

$$I_D = 0.4 = K_p (V_{SG} + V_{TP})^2$$

$$0.4 = (0.2)(V_S - 0.8)^2$$

$$V_S = \sqrt{\frac{0.4}{0.2}} + 0.8 \Rightarrow \underline{V_S = 2.21 \text{ V}}$$

$$V_D = I_D R_D - 5 = (0.4)(5) - 5 = -3 \text{ V}$$

$$V_{SD} = V_S - V_D = 2.21 - (-3)$$

$$\Rightarrow \underline{V_{SD} = 5.21 \text{ V}}$$

$$\underline{V_{SD} > V_{SD}(\text{sat})}$$

5.23

$$V_{DD} = I_{DQ} R_D + V_{DSQ} + I_{DQ} R_S$$

$$(1) \quad 10 = I_{DQ}(5) + 5 + V_{GS} \text{ and}$$

$$I_{DQ} = \left( \frac{k'_n}{2} \right) \left( \frac{W}{L} \right) (V_{GS} - V_{TN})^2$$

$$\text{or (2) } I_{DQ} = \left( \frac{0.060}{2} \right) \left( \frac{W}{L} \right) (V_{GS} - 1.2)^2$$

$$\text{Let } \underline{V_{GS} = 2.5 \text{ V}}$$

$$\text{Then from (1), } 10 = I_{DQ}(5) + 5 + 2.5 \Rightarrow \underline{I_D = 0.5 \text{ mA}}$$

$$\text{Then from (2), } 0.5 = \left( \frac{0.060}{2} \right) \left( \frac{W}{L} \right) (2.5 - 1.2)^2 \Rightarrow$$

$$\underline{\frac{W}{L} = 9.86}$$

$$I_{DQ} R_S = V_{GS} \Rightarrow R_S = \frac{V_{GS}}{I_{DQ}} = \frac{2.5}{0.5} \Rightarrow \underline{R_S = 5 \text{ k}\Omega}$$

$$I_R = \frac{10}{R_1 + R_2} = (0.5)(0.05) = 0.025 \text{ mA}$$

$$\text{Then } R_1 + R_2 = \frac{10}{0.025} = 400 \text{ k}\Omega$$

$$\left( \frac{R_2}{R_1 + R_2} \right) (V_{DD}) = 2V_{GS} \Rightarrow \left( \frac{R_2}{400} \right) (10) = 2(2.5) \Rightarrow$$

$$\underline{R_1 = R_2 = 200 \text{ k}\Omega}$$

5.24

$$V_G = \left( \frac{R_2}{R_1 + R_2} \right) (10) - 5$$

$$= \left( \frac{5.5}{14.5 + 5.5} \right) (10) - 5 = -2.25 \text{ V}$$

$$I_D = \frac{V_G - V_{GS} - (-5)}{R_S} = K_n (V_{GS} - V_{TN})^2$$

Assume transistor biased in saturation region

$$-2.25 - V_{GS} + 5 = (0.5)(0.6)(V_{GS} - (-1))^2$$

$$2.75 - V_{GS} = (0.3)(V_{GS}^2 + 2V_{GS} + 1)$$

$$0.3V_{GS}^2 + 1.6V_{GS} - 2.45 = 0$$

$$V_{GS} = \frac{-1.6 \pm \sqrt{(1.6)^2 + 4(0.3)(2.45)}}{2(0.3)}$$

$$\Rightarrow V_{GS} = 1.24 \text{ V}$$

$$I_D = \frac{-2.25 - 1.24 + 5}{0.6} \Rightarrow I_D = 2.52 \text{ mA}$$

$$V_{DS} = 10 - I_D(R_S + R_D) \\ = 10 - (2.52)(0.6 + 0.8)$$

$$\Rightarrow V_{DS} = 6.47 \text{ V}$$

$$V_{DS} > V_{DS}(\text{sat})$$

5.25

$$20 = I_{DQ}R_S + V_{SDQ} + I_{DQ}R_D$$

$$(1) 20 = V_{SG} + 10 + I_{DQ}R_D$$

$$I_{DQ} = \left(\frac{k'_p}{2}\right)\left(\frac{W}{L}\right)(V_{SG} + V_{TP})^2$$

$$(2) I_{DQ} = \left(\frac{0.040}{2}\right)\left(\frac{W}{L}\right)(V_{SG} - 2)^2$$

$$\text{For example, let } I_{DQ} = 0.8 \text{ mA and } V_{SG} = 4 \text{ V}$$

$$\text{Then } 0.8 = \left(\frac{0.040}{2}\right)\left(\frac{W}{L}\right)(4 - 2)^2 \Rightarrow \frac{W}{L} = 10$$

$$I_{DQ}R_S = V_{SG} \Rightarrow (0.8)R_S = 4 \Rightarrow R_S = 5 \text{ k}\Omega$$

$$\text{From (1) } 20 = 4 + 10 + (0.8)R_D \Rightarrow R_D = 7.5 \text{ k}\Omega$$

$$I_R = \frac{20}{R_1 + R_2} = (0.8)(0.1) \Rightarrow R_1 + R_2 = 250 \text{ k}\Omega$$

$$\left(\frac{R_1}{R_1 + R_2}\right)(20) = 2V_{SG} = (2)(4)$$

$$\frac{R_1}{250}(20) = 8 \Rightarrow R_1 = 100 \text{ k}\Omega, R_2 = 150 \text{ k}\Omega$$

5.26

$$(a) (i) I_Q = 50 = 500(V_{GS} - 1.2)^2 \Rightarrow V_{GS} = 1.516 \text{ V}$$

$$V_{DS} = 5 - (-1.516) \Rightarrow V_{DS} = 6.516 \text{ V}$$

$$(iv) I_Q = 1 = (0.5)(V_{GS} - 1.2)^2 \Rightarrow V_{GS} = 2.61 \text{ V}$$

$$V_{DS} = 5 - (-2.61) \Rightarrow V_{DS} = 7.61 \text{ V}$$

$$(b) (i) \text{ Same as (a) } V_{GS} = V_{DS} = 1.516 \text{ V}$$

$$(iv) V_{GS} = V_{DS} = 2.61 \text{ V}$$

5.27

$$I_D = K_n(V_{GS} - V_{TN})^2$$

$$0.25 = (0.2)(V_{GS} - 0.6)^2$$

$$V_{GS} = \sqrt{\frac{0.25}{0.2}} + 0.6 \Rightarrow V_{GS} = 1.72 \text{ V}$$

$$\Rightarrow V_S = -1.72 \text{ V}$$

$$V_D = 9 - (0.25)(24) \Rightarrow V_D = 3 \text{ V}$$

5.28

$$I_D = \frac{5 - V_D}{R_D} \Rightarrow 0.8 = \frac{5 - 1}{R_D} \Rightarrow R_D = 5 \text{ k}\Omega$$

$$V_G = 0$$

$$I_D = K_n(V_{GS} - V_{TN})^2 \Rightarrow 0.8 = (0.4)(V_{GS} - 1.7)^2$$

$$V_{GS} = \sqrt{\frac{0.8}{0.4}} + 1.7 \Rightarrow V_{GS} = 3.11 \text{ V}$$

$$\Rightarrow V_S = -3.11 \text{ V}$$

$$I_D = 0.8 = \frac{-3.11 - (-5)}{R_S} \Rightarrow R_S = 2.36 \text{ k}\Omega$$

5.29

$$V_{DD} = V_{SD} + I_{DQ}R$$

$$9 = 2.5 + (0.1)R \Rightarrow R = 65 \text{ k}\Omega$$

$$I_{DQ} = \left(\frac{k'_p}{2}\right)\left(\frac{W}{L}\right)(V_{SG} + V_{TP})^2$$

$$(0.1) = \left(\frac{0.025}{2}\right)\left(\frac{W}{L}\right)(2.5 - 1.5)^2 \Rightarrow \frac{W}{L} = 8$$

$$\text{Then for } L = \mu\text{m, } W = 32 \mu\text{m}$$

5.30

$$5 = I_{DQ}R_S + V_{SDQ} = I_{DQ}(2) + 2.5$$

$$I_{DQ} = 1.25 \text{ mA}$$

$$I_R = \frac{10}{R_1 + R_2} = (1.25)(0.1) \Rightarrow R_1 + R_2 = 80 \text{ k}\Omega$$

$$I_{DQ} = K_p(V_{SG} + V_{TP})^2$$

$$1.25 = 0.5(V_{SG} + 1.5)^2 \Rightarrow \sqrt{\frac{1.25}{0.5}} - 1.5 = V_{SG}$$

$$V_{SG} = 0.0811 \text{ V}$$

$$V_G = V_S - V_{SG} = 2.5 - 0.0811 = 2.42 \text{ V}$$

$$V_G = \left(\frac{R_2}{R_1 + R_2}\right)(10) - 5$$

$$2.42 = \left(\frac{R_2}{80}\right)(10) - 5 \Rightarrow$$

$$R_2 = 59.4 \text{ k}\Omega, R_1 = 20.6 \text{ k}\Omega$$

5.31

$$K_p = \left(\frac{0.030}{2}\right)(20) \Rightarrow 0.30 \text{ mA/V}^2$$

$$I_D = K_p(V_{SG} + V_{TP})^2$$

$$0.5 = 0.30(V_{SG} - 1.2)^2 \Rightarrow V_{SG} = 2.49 \text{ V}$$

$$V_S = V_{SG} = 2.49 \text{ V}$$

$$I_D = \frac{5 - V_S}{R_S} \Rightarrow R_S = \frac{5 - 2.49}{0.5} \Rightarrow R_S = 5.02 \text{ k}\Omega$$

$$R_D = \frac{V_D - (-5)}{I_D} = \frac{5 - 3}{0.5} \Rightarrow R_D = 4 \text{ k}\Omega$$

5.32

$$I_D = \frac{-V_{SD} - (-10)}{R_D} \Rightarrow 5 = \frac{-6 + 10}{R_D}$$

$$\Rightarrow \underline{R_D = 0.8 \text{ k}\Omega}$$

$$I_D = K_p (V_{SG} + V_{TP})^2 \Rightarrow 5 = 3(V_{SG} - 1.75)^2$$

$$V_{SG} = \sqrt{\frac{5}{3}} + 1.75 = 3.04 \text{ V} \Rightarrow V_G = -3.04$$

$$V_G = \left( \frac{R_2}{R_1 + R_2} \right) (10) - 5 = -3.04$$

$$R_{in} = R_1 \parallel R_2 = 80 \text{ k}\Omega$$

$$\frac{1}{R_1} \cdot (80)(10) = 5 - 3.04 \Rightarrow \underline{R_1 = 408 \text{ k}\Omega}$$

$$\frac{408 R_2}{408 + R_2} = 80 \Rightarrow \underline{R_2 = 99.5 \text{ k}\Omega}$$

5.33

$$(a) K_{n1} = \left( \frac{60}{2} \right) (4) = 120 \mu\text{A}/\text{V}^2$$

$$K_{n2} = \left( \frac{60}{2} \right) (1) = 30 \mu\text{A}/\text{V}^2$$

For  $v_i = 1 \text{ V}$ ,  $M_1$  Sat. region,  $M_2$  Non-sat region.

$$I_{D2} = I_{D1}$$

$$30[2(-V_{TNL})(5 - v_o) - (5 - v_o)^2] = 120(1 - 0.8)^2$$

$$\text{We find } v_o^2 - 6.4v_o + 7.16 = 0 \Rightarrow \underline{v_o = 4.955 \text{ V}}$$

(b) For  $v_i = 3 \text{ V}$ ,  $M_1$  Non-sat region,  $M_2$  Sat. region.  $I_{D2} = I_{D1}$

$$30[(-1.8)]^2 = 120[2(3 - 0.8)v_o - v_o^2]$$

$$\text{We find } 4v_o^2 - 17.6v_o + 3.24 = 0 \Rightarrow \underline{v_o = 0.193 \text{ V}}$$

(c) For  $v_i = 5 \text{ V}$ , biasing same as (b)

$$30[(-1.8)]^2 = 120[2(5 - 0.8)v_o - v_o^2]$$

$$\text{We find } 4v_o^2 - 33.6v_o + 3.24 = 0 \Rightarrow \underline{v_o = 0.0976 \text{ V}}$$

5.34

For  $v_i = 5 \text{ V}$ ,  $M_1$  Non-sat region,  $M_2$  Sat. region.

$$I_{D1} = I_{D2}$$

$$\left( \frac{k'_n}{2} \right) \left( \frac{W}{L} \right)_1 [2(V_{GS1} - V_{TN1})V_{DS1} - V_{DS1}^2] =$$

$$\left( \frac{k'_n}{2} \right) \left( \frac{W}{L} \right)_2 (V_{GS2} - V_{TN2})^2$$

$$\left( \frac{W}{L} \right)_1 [2(5 - 0.8)(0.15) - (0.15)^2] = (1)[0 - (-2)]^2$$

$$\text{which yields } \underline{\left( \frac{W}{L} \right)_1 = 3.23}$$

5.35

a.  $M_1$  and  $M_2$  in saturation

$$K_{n1}(V_{GS1} - V_{TN1})^2 = K_{n2}(V_{GS2} - V_{TN2})^2$$

$$K_{n1} = K_{n2}, \quad V_{TN1} = V_{TN2}$$

$$\Rightarrow \underline{V_{GS1} = V_{GS2} = 2.5 \text{ V}}, \quad \underline{V_0 = 2.5 \text{ V}}$$

$$I_D = (15)(40)(2.5 - 0.8)^2 \Rightarrow \underline{I_D = 1.73 \text{ mA}}$$

$$b. \left( \frac{W}{L} \right)_1 > \left( \frac{W}{L} \right)_2 \Rightarrow V_{GS1} < V_{GS2}$$

$$40(V_{GS1} - 0.8)^2 = (15)(V_{GS2} - 0.8)^2$$

$$V_{GS2} = 5 - V_{GS1}$$

$$1.63(V_{GS1} - 0.8) = (5 - V_{GS1} - 0.8)$$

$$2.63V_{GS1} = 5.50 \Rightarrow \underline{V_{GS1} = 2.09 \text{ V}}$$

$$\underline{V_{GS2} = 2.91 \text{ V}}, \quad \underline{V_0 = V_{GS1} = 2.09 \text{ V}}$$

$$I_D = (15)(15)(2.91 - 0.8)^2 \Rightarrow \underline{I_D = 1.0 \text{ mA}}$$

5.36

Each transistor biased in saturation.

$$M_3: V_1 = V_{GS3} = 2 \text{ V}$$

$$I_D = 0.5 = 0.018 \left( \frac{W}{L} \right)_3 (2 - 1)^2$$

$$\Rightarrow \underline{\left( \frac{W}{L} \right)_3 = 27.8}$$

$$M_2: V_{GS2} = V_2 - V_1 = 5 - 2 = 3 \text{ V}$$

$$I_D = 0.5 = 0.018 \left( \frac{W}{L} \right)_2 (3 - 1)^2$$

$$\Rightarrow \underline{\left( \frac{W}{L} \right)_2 = 6.94}$$

$$M_1: V_{GS1} = 10 - V_2 = 10 - 5 = 5 \text{ V}$$

$$I_D = 0.5 = 0.018 \left( \frac{W}{L} \right)_1 (5 - 1)^2$$

$$\Rightarrow \underline{\left( \frac{W}{L} \right)_1 = 1.74}$$

5.37

$M_L$  in saturation

$M_D$  in nonsaturation

$$\left( \frac{W}{L} \right)_L (V_{GSL} - V_{TNL})^2$$

$$= \left( \frac{W}{L} \right)_D [2(V_{GSD} - V_{TND})V_{DSD} - V_{DSD}^2]$$

$$(1)(5 - 0.1 - 0.8)^2$$

$$= \left( \frac{W}{L} \right)_D [2(5 - 0.8)(0.1) - (0.1)^2]$$

$$16.81 = \left( \frac{W}{L} \right)_D [0.83]$$

$$\underline{\left( \frac{W}{L} \right)_D = 20.3}$$

5.38

 $M_L$  in saturation $M_D$  in nonsaturation

$$\left(\frac{W}{L}\right)_L (V_{GSL} - V_{TNL})^2 = \left(\frac{W}{L}\right)_D [2(V_{GSD} - V_{TND})V_{DSD} - V_{DSD}^2]$$

$$(1)(1.8)^2$$

$$= \left(\frac{W}{L}\right)_D [2(5 - 0.8)(0.05) - (0.05)^2]$$

$$3.24 = \left(\frac{W}{L}\right)_D [0.4175]$$

$$\left(\frac{W}{L}\right)_D = 7.76$$

5.39

$$I_{REF} = K_{n4}(V_{GS4} - V_{TN})^2 = K_{n3}(V_{GS3} - V_{TN})^2$$

$$V_{GS4} = 5 - V_{GS3}$$

$$\sqrt{\frac{400}{200}}(5 - V_{GS3} - 1) = (V_{GS3} - 1)$$

$$2.41V_{GS3} = 6.66 \Rightarrow V_{GS3} = 2.76 \text{ V}$$

$$V_{GS4} = 2.24 \text{ V}, \quad V_{GS2} = V_{GS3} = 2.76 \text{ V}$$

$$I_{REF} = K_{n3}(V_{GS3} - V_{TN})^2 = (0.2)(2.76 - 1)^2$$

$$I_{REF} = 0.620 \text{ mA}$$

$$I_Q = K_{n2}(V_{GS2} - V_{TN})^2 = (0.1)(2.76 - 1)^2$$

$$I_Q = 0.310 \text{ mA}$$

$$I_Q = K_{n1}(V_{GS1} - V_{TN})^2$$

$$\Rightarrow 0.310 = (0.08)(V_{GS1} - 1)^2$$

$$\text{Then } V_{GS1} = \sqrt{\frac{0.310}{0.08}} + 1 \Rightarrow V_{GS1} = 2.97 \text{ V}$$

5.40

$$I_D = \frac{V_{DD} - V_0}{R_D} = \frac{5 - 0.1}{10} = 0.49 \text{ mA}$$

Transistor biased in nonsaturation

$$I_D = 0.49$$

$$= (0.015) \left(\frac{W}{L}\right) [2(4.2 - 0.8)(0.1) - (0.1)^2]$$

$$0.49 = \left(\frac{W}{L}\right) [0.67] \Rightarrow \frac{W}{L} = 0.731$$

5.41

$$5 = I_D R_D + V_\gamma + V_{DS}$$

$$5 = (12)R_D + 1.6 + 0.2 \Rightarrow R_D = 267 \Omega$$

$$I_D = \left(\frac{k'_n}{2}\right) \left(\frac{W}{L}\right) (V_{GS} - V_{TN})^2$$

$$12 = \left(\frac{0.040}{2}\right) \left(\frac{W}{L}\right) (5 - 0.8)^2 \Rightarrow \frac{W}{L} = 34$$

5.42

$$5 = V_{SD} + I_D R_D + V_\gamma$$

$$5 = 0.15 + (15)R_D + 1.6 \Rightarrow R_D = 217 \Omega$$

$$I_D = \left(\frac{k'_p}{2}\right) \left(\frac{W}{L}\right) (V_{SG} + V_{TP})^2$$

$$15 = \left(\frac{0.020}{2}\right) \left(\frac{W}{L}\right) (5 - 0.8)^2 \Rightarrow \frac{W}{L} = 85$$

5.43

$$V_{DS}(\text{sat}) = V_{GS} - V_P$$

$$\text{So } V_{DS} > V_{DS}(\text{sat}) = -V_P, \quad I_D = I_{DSS}$$

5.44

$$V_{DS}(\text{sat}) = V_{GS} - V_P = V_{GS} + 3 = V_{DS}(\text{sat})$$

$$\text{a. } V_{GS} = 0 \Rightarrow I_D = I_{DSS} = 6 \text{ mA}$$

$$\text{b. } I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2 = 6 \left(1 - \frac{-1}{-3}\right)^2$$

$$\Rightarrow I_D = 2.67 \text{ mA}$$

$$\text{c. } I_D = 6 \left(1 - \frac{-2}{-3}\right)^2 \Rightarrow I_D = 0.667 \text{ mA}$$

$$\text{d. } I_D = 0$$

5.45

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$2.8 = I_{DSS} \left(1 - \frac{1}{V_P}\right)^2$$

$$0.30 = I_{DSS} \left(1 - \frac{3}{V_P}\right)^2$$

$$\frac{2.8}{0.30} = \frac{\left(1 - \frac{1}{V_P}\right)^2}{\left(1 - \frac{3}{V_P}\right)^2} = 9.33$$

$$\frac{\left(1 - \frac{1}{V_P}\right)}{\left(1 - \frac{3}{V_P}\right)} = 3.055$$

$$1 - \frac{1}{V_P} = 3.055 - \frac{9.165}{V_P}$$

$$\frac{8.165}{V_P} = 2.055 \Rightarrow V_P = 3.97 \text{ V}$$

$$2.8 = I_{DSS} \left(1 - \frac{1}{3.97}\right)^2 = I_{DSS}(0.560)$$

$$\Rightarrow I_{DSS} = 5.0 \text{ mA}$$

5.46

$$V_S = -V_{GS}, \quad V_{SD} = V_S - V_{DD}$$

$$\text{Want } V_{SD} \geq V_{SD}(\text{sat}) = V_P - V_{GS}$$

$$V_S - V_{DD} \geq V_P - V_{GS}$$

$$-V_{GS} - V_{DD} \geq V_P - V_{GS} \Rightarrow \underline{V_{DD} \leq -V_P}$$

$$\text{So } \underline{V_{DD} \leq -2.5 \text{ V}}$$

$$I_D = 2 = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$2 = 6 \left(1 - \frac{V_{GS}}{2.5}\right)^2 \Rightarrow V_{GS} = 1.06 \text{ V}$$

$$\Rightarrow \underline{V_S = -1.06 \text{ V}}$$

5.47

$$I_D = K_n (V_{GS} - V_{TN})^2$$

$$18.5 = K_n (0.35 - V_{TN})^2$$

$$86.2 = K_n (0.5 - V_{TN})^2$$

Then

$$\frac{18.5}{86.2} = 0.2146 = \frac{(0.35 - V_{TN})^2}{(0.50 - V_{TN})^2} \Rightarrow \underline{V_{TN} = 0.221 \text{ V}}$$

$$18.5 = K_n (0.35 - 0.221)^2 \Rightarrow \underline{K_n = 1.11 \text{ mA/V}^2}$$

5.48

$$I_D = K(V_{GS} - V_{TN})^2$$

$$250 = K(0.75 - 0.24)^2 \Rightarrow \underline{K = 0.961 \text{ mA/V}^2}$$

5.49

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2 = \frac{V_S}{R_S} = -\frac{V_{GS}}{R_S}$$

$$10 \left(1 - \frac{V_{GS}}{-5}\right)^2 = -\frac{V_{GS}}{0.2}$$

$$2 \left(1 + \frac{2V_{GS}}{5} + \frac{V_{GS}^2}{25}\right) = -V_{GS}$$

$$\frac{2}{25} V_{GS}^2 + \frac{9}{5} V_{GS} + 2 = 0$$

$$2V_{GS}^2 + 45V_{GS} + 50 = 0$$

$$V_{GS} = \frac{-45 \pm \sqrt{(45)^2 - 4(2)(50)}}{2(2)}$$

$$\Rightarrow \underline{V_{GS} = -1.17 \text{ V}}$$

$$I_D = -\frac{V_{GS}}{R_S} = \frac{1.17}{0.2} \Rightarrow \underline{I_D = 5.85 \text{ mA}}$$

$$V_D = 20 - (5.85)(2) = 8.3 \text{ V}$$

$$V_{DS} = V_D - V_S = 8.3 - 1.17 \Rightarrow \underline{V_{DS} = 7.13 \text{ V}}$$

5.50

$$V_{DS} = V_{DD} - V_S$$

$$8 = 10 - V_S \Rightarrow V_S = 2 \text{ V} = I_D R_S = (5) R_S$$

$$\Rightarrow \underline{R_S = 0.4 \text{ k}\Omega}$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$5 = I_{DSS} \left(1 - \frac{-1}{V_P}\right)^2 \quad \text{Let } \underline{I_{DSS} = 10 \text{ mA}}$$

$$5 = 10 \left(1 - \frac{-1}{V_P}\right)^2 \Rightarrow \underline{V_P = -3.41 \text{ V}}$$

$$V_G = V_{GS} + V_S = -1 + 2 = 1 \text{ V}$$

$$V_G = \left(\frac{R_2}{R_1 + R_2}\right) V_{DD} = \frac{1}{R_1} \cdot R_{1n} \cdot V_{DD}$$

$$1 = \frac{1}{R_1} (500)(10) \Rightarrow \underline{R_1 = 5 \text{ M}\Omega}$$

$$\frac{5R_2}{5 + R_2} = 0.5 \Rightarrow \underline{R_2 = 0.556 \text{ M}\Omega}$$

5.51

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$5 = 8 \left(1 - \frac{V_{GS}}{4}\right)^2 \Rightarrow \underline{V_{GS} = 0.838 \text{ V}}$$

$$V_{SD} = V_{DD} - I_D (R_S + R_D)$$

$$= 20 - (5)(0.5 + 2) \Rightarrow \underline{V_{SD} = 7.5 \text{ V}}$$

$$V_S = 20 - (5)(0.5) = 17.5 \text{ V}$$

$$V_G = V_S + V_{GS} = 17.5 + 0.838 = 18.3 \text{ V}$$

$$V_G = \left(\frac{R_2}{R_1 + R_2}\right) V_{DD} = \frac{1}{R_1} \cdot R_{1n} \cdot V_{DD}$$

$$18.3 = \frac{1}{R_1} (100)(20) \Rightarrow \underline{R_1 = 109 \text{ k}\Omega}$$

$$\frac{109R_2}{109 + R_2} = 100 \Rightarrow \underline{R_2 = 1.21 \text{ M}\Omega}$$

5.52

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$5 = 7 \left(1 - \frac{V_{GS}}{3}\right)^2 \Rightarrow \underline{V_{GS} = 0.465 \text{ V}}$$

$$V_{SD} = V_{DD} - I_D (R_S + R_D)$$

$$6 = 12 - (5)(0.3 + R_D) \Rightarrow \underline{R_D = 0.9 \text{ k}\Omega}$$

$$V_S = 12 - (5)(0.3) = 10.5 \text{ V}$$

$$V_G = V_S + V_{GS} = 10.5 + 0.465 = 10.965 \text{ V}$$

$$V_G = \left(\frac{R_2}{R_1 + R_2}\right) V_{DD}$$

$$10.965 = \left(\frac{R_2}{100}\right) (12) \Rightarrow \underline{R_2 = 91.4 \text{ k}\Omega}$$

$$\Rightarrow \underline{R_1 = 8.6 \text{ k}\Omega}$$

5.53

$$V_G = \left( \frac{R_2}{R_1 + R_2} \right) V_{DD} = \left( \frac{60}{140 + 60} \right) (20)$$

$$\Rightarrow \underline{V_G = 6 \text{ V}}$$

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2 = \frac{V_S}{R_S} = \frac{V_G - V_{GS}}{R_S}$$

$$(8)(2) \left( 1 - \frac{V_{GS}}{(-4)} \right)^2 = 6 - V_{GS}$$

$$16 \left( 1 + \frac{V_{GS}}{2} + \frac{V_{GS}^2}{16} \right) = 6 - V_{GS}$$

$$V_{GS}^2 + 9V_{GS} + 10 = 0$$

$$V_{GS} = \frac{-9 \pm \sqrt{(9)^2 - 4(10)}}{2} \Rightarrow \underline{V_{GS} = -1.30}$$

$$I_D = 8 \left( 1 - \frac{(-1.30)}{(-4)} \right)^2 \Rightarrow \underline{I_D = 3.65 \text{ mA}}$$

$$V_{DS} = V_{DD} - I_D(R_S + R_D)$$

$$= 20 - (3.65)(2 + 2.7)$$

$$V_{DS} = 2.85 \text{ V}$$

$$V_{DS} > V_{DS}(\text{sat}) = V_{GS} - V_P$$

$$= -1.30 - (-4)$$

$$= 2.7 \text{ V (Yes)}$$

5.54

$$V_{DS} = V_{DD} - I_D(R_S + R_D)$$

$$5 = 12 - I_D(0.5 + 1) \Rightarrow \underline{I_D = 4.67 \text{ mA}}$$

$$V_S = I_D R_S = (4.67)(0.5) \Rightarrow V_S = 2.33 \text{ V}$$

$$V_G = \left( \frac{R_2}{R_1 + R_2} \right) V_{DD} = \left( \frac{20}{450 + 20} \right) (12)$$

$$\Rightarrow V_G = 0.511 \text{ V}$$

$$V_{GS} = V_G - V_S = 0.511 - 2.33$$

$$\Rightarrow \underline{V_{GS} = -1.82 \text{ V}}$$

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$$

$$4.67 = 10 \left( 1 - \frac{(-1.82)}{V_P} \right)^2 \Rightarrow \underline{V_P = -5.75 \text{ V}}$$

5.55

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2, \quad V_{GS} = 0$$

$$\underline{I_D = I_{DSS} = 4 \text{ mA}}$$

$$R_D = \frac{V_{DD} - V_{DS}}{I_D} = \frac{10 - 3}{4} \Rightarrow \underline{R_D = 1.75 \text{ k}\Omega}$$

5.56

$$V_{SD} = V_{DD} - I_D R_S$$

$$10 = 20 - (1)R_S \Rightarrow \underline{R_S = 10 \text{ k}\Omega}$$

$$R_1 + R_2 = \frac{V_{DD}}{I} = \frac{20}{0.1} = 200 \text{ k}\Omega$$

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$$

$$1 = 2 \left( 1 - \frac{V_{GS}}{2} \right)^2 \Rightarrow \underline{V_{GS} = 0.586 \text{ V}}$$

$$V_G = V_S + V_{GS} = 10 + 0.586 = 10.586$$

$$V_G = \left( \frac{R_2}{R_1 + R_2} \right) V_{DD}$$

$$10.586 = \left( \frac{R_2}{200} \right) (20) \Rightarrow \underline{R_2 = 106 \text{ k}\Omega}$$

$$\underline{R_1 = 94 \text{ k}\Omega}$$

5.57

$$V_{DS} = V_{DD} - I_D(R_S + R_D)$$

$$2 = 3 - (0.040)(10 + R_D) \Rightarrow \underline{R_D = 15 \text{ k}\Omega}$$

$$I_D = K(V_{GS} - V_{TN})^2$$

$$40 = 250(V_{GS} - 0.20)^2 \Rightarrow \underline{V_{GS} = 0.60 \text{ V}}$$

$$V_G = V_{GS} + V_S = 0.60 + (0.040)(10) = 1.0 \text{ V}$$

$$V_G = \left( \frac{R_2}{R_1 + R_2} \right) V_{DD}$$

$$1 = \left( \frac{R_2}{150} \right) (3) \Rightarrow \underline{R_2 = 50 \text{ k}\Omega}$$

$$\underline{R_1 = 100 \text{ k}\Omega}$$

5.58

$$\text{For } V_O = 0.70 \text{ V} \Rightarrow$$

$$V_{DS} = 0.70 > V_{DS}(\text{sat}) = V_{GS} - V_{TN}$$

$$0.75 - 0.15 = 0.6$$

Biased in the saturation region

$$I_D = \frac{V_{DD} - V_{DS}}{R_D} = \frac{3 - 0.7}{50} \Rightarrow \underline{I_D = 46 \mu\text{A}}$$

$$I_D = K(V_{GS} - V_{TN})^2 \Rightarrow 46 = K(0.75 - 0.15)^2 \Rightarrow$$

$$\underline{K = 128 \mu\text{A/V}^2}$$



## Chapter 6

## Exercise Solutions

E6.1

$$g_m = 2K_n(V_{GS} - V_{TN}) \text{ and}$$

$$I_D = K_n(V_{GS} - V_{TN})^2$$

$$0.75 = 0.5(V_{GS} - 0.8)^2 \Rightarrow V_{GS} = 2.025 \text{ V}$$

$$g_m = 2(0.5)(2.025 - 0.8) \Rightarrow \underline{g_m = 1.22 \text{ mA/V}}$$

$$r_o = \left[ \lambda K_n (V_{GS} - V_{TN})^2 \right]^{-1}$$

$$= \left[ (0.01)(0.5)(2.025 - 0.8)^2 \right]^{-1} \Rightarrow$$

$$\underline{r_o = 133 \text{ k}\Omega}$$

E6.2

$$g_m = 2K_n(V_{GS} - V_{TN}) \text{ and } I_D = K_n(V_{GS} - V_{TN})^2$$

$$\Rightarrow V_{GS} - V_{TN} = \sqrt{\frac{I_{DQ}}{K_n}} \text{ and}$$

$$g_m = 2K_n \sqrt{\frac{I_{DQ}}{K_n}} = 2\sqrt{K_n I_{DQ}}$$

$$K_n = \frac{g_m^2}{4I_{DQ}} = \frac{(3.4)^2}{4(2)} = 1.45 \text{ mA/V}$$

$$K_n = \frac{\mu_n C_{ox} W}{2L}$$

$$1.45 = (0.018) \left( \frac{W}{L} \right) \Rightarrow \underline{\frac{W}{L} = 80.6}$$

$$r_o = \left[ \lambda K_n (V_{GS} - V_{TN})^2 \right]^{-1} = \left[ \lambda I_{DQ} \right]^{-1}$$

$$r_o = \left[ (0.015)(2) \right]^{-1} \Rightarrow \underline{r_o = 33.3 \text{ k}\Omega}$$

E6.3

$$\text{a. } I_{DQ} = K_n(V_{GS} - V_{TN})^2$$

$$0.4 = 0.5(V_{GS} - 2)^2 \Rightarrow \underline{V_{GS} = 2.89 \text{ V}}$$

$$V_{DSQ} = V_{DD} - I_{DQ}R_D = 10 - (0.4)(10)$$

$$\Rightarrow \underline{V_{DSQ} = 6 \text{ V}}$$

$$\text{b. } g_m = 2K_n(V_{GS} - V_{TN}) = 2(0.5)(2.89 - 2)$$

$$\Rightarrow \underline{g_m = 0.89 \text{ mA/V}}$$

$$r_o = \left[ \lambda I_{DQ} \right]^{-1}, \lambda = 0 \Rightarrow \underline{r_o = \infty}$$

$$A_v = \frac{v_o}{v_i} = -g_m R_D = -(0.89)(10)$$

$$\Rightarrow \underline{A_v = -8.9}$$

$$\text{c. } v_i = 0.4 \sin \omega t \Rightarrow v_{ds} = -(8.9)(0.4) \sin \omega t$$

$$v_{ds} = -3.56 \sin \omega t$$

$$\text{At } V_{DS1} = 6 - 3.56 = 2.44$$

$$V_{GS1} = 2.89 + 0.4 = 3.29$$

$$V_{GS1} - V_{TN} = 3.29 - 2 = 1.29$$

So  $V_{DS1} > V_{GS1} - V_{TN} \Rightarrow$  Biased in saturation region

E6.4

$$\text{a. } V_{SDQ} = V_{DD} - I_{DQ}R_D$$


$$7 = 12 - I_{DQ}(6) \Rightarrow I_{DQ} = 0.833 \text{ mA}$$

$$I_{DQ} = K_p(V_{SG} - |V_{TP}|)^2$$

$$0.833 = 2(V_{SG} - 1)^2 \Rightarrow \underline{V_{SG} = 1.65 \text{ V}}$$

$$\text{b. } g_m = 2K_p(V_{SG} - |V_{TP}|) = 2(2)(1.65 - 1)$$
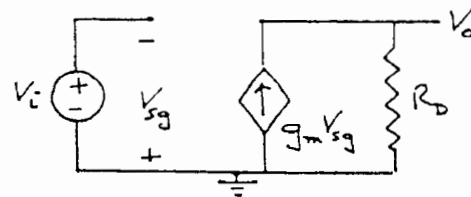
$$\Rightarrow \underline{g_m = 2.6 \text{ mA/V}}, \underline{r_o = \infty}$$



$$A_v = \frac{v_o}{v_i} = -g_m R_D = -(2.6)(6)$$

$$\Rightarrow \underline{A_v = -15.6}$$

E6.5

$$I_{DQ} = K_n(V_{GS} - V_{TN})^2 \Rightarrow V_{GS} - V_{TN} = \sqrt{\frac{I_{DQ}}{K_n}}$$

$$g_m = 2K_n(V_{GS} - V_{TN}) = 2K_n \sqrt{\frac{I_{DQ}}{K_n}}$$

$$\text{So } g_m = 2\sqrt{K_n I_{DQ}}$$

E6.6

$$\eta = \frac{\gamma}{2\sqrt{2\phi_f + v_{SB}}}$$

$$\text{(a) } \eta = \frac{0.40}{2\sqrt{2(0.35) + 1}} \Rightarrow \underline{\eta = 0.153}$$

(b)  $\eta = \frac{0.40}{2\sqrt{2(0.35)+3}} \Rightarrow \eta = 0.104$

$g_m = 2\sqrt{K_n I_{DQ}} = 2\sqrt{(0.5)(0.75)} = 1.22 \text{ mA/V}$

For (a),  $g_{mb} = g_m \eta = (1.22)(0.153) \Rightarrow$

$g_{mb} = 0.187 \text{ mA/V}$

For (b),  $g_{mb} = (1.22)(0.104) \Rightarrow g_{mb} = 0.127 \text{ mA/V}$

E6.7

a.  $I_{DQ} = K_n (V_{GS} - V_{TN})^2 = (0.25)(2 - 0.8)^2$

$\Rightarrow I_{DQ} = 0.36 \text{ mA}$

$V_{DSQ} = V_{DD} - I_{DQ} R_D = 5 - (0.36)(5)$

$\Rightarrow V_{DSQ} = 3.2 \text{ V}$

b.  $g_m = 2K_n (V_{GS} - V_{TN}) = 2(0.25)(2 - 0.8)$

$\Rightarrow g_m = 0.6 \text{ mA/V}, r_o = \infty$

c.  $A_v = \frac{v_o}{v_i} = -g_m R_D = -(0.6)(5)$

$\Rightarrow A_v = -3.0$

E6.8

$v_i = v_{gs} = 0.1 \sin \omega t$

$i_d = g_m v_{gs} = (0.6)(0.1) \sin \omega t$

$i_d = 0.06 \sin \omega t \text{ mA}$

$v_{ds} = (-3)(0.1) \sin \omega t = -0.3 \sin \omega t$

Then  $i_D = I_{DQ} + i_d = 0.36 + 0.06 \sin \omega t$   
 $= i_D \text{ mA}$

$v_{DS} = V_{DSQ} + v_{ds} = 3.2 - 0.3 \sin \omega t = v_{DS}$

E6.9

$V_{SDQ} = 3 \text{ V}$  and  $I_{DQ} = 0.5 \text{ mA}$

$\Rightarrow R_D = \frac{5-3}{0.5} \Rightarrow R_D = 4 \text{ k}\Omega$

$I_{DQ} = K_p (V_{SG} - |V_{TP}|)^2$

$0.5 = 1(V_{SG} - 1)^2 \Rightarrow V_{SG} = 1.71 \text{ V}$

$\Rightarrow V_{GG} = 5 - 1.71 \Rightarrow V_{GG} = 3.29 \text{ V}$

$A_v = -g_m R_D$

$g_m = 2\sqrt{K_p I_{DQ}} = 2\sqrt{(1)(0.5)}$

$g_m = 1.41 \text{ mA/V}$

$A_v = -(1.41)(4) \Rightarrow A_v = -5.64$

$A_v = \frac{v_o}{v_i} = \frac{-v_{ds}}{v_i} = -\frac{0.46 \sin \omega t}{v_i} = -5.64$

$\Rightarrow v_i = 0.0816 \sin \omega t$

E6.10

a.  $V_{SG} = 9 - I_{DQ} R_S, I_{DQ} = K_p (V_{SG} - |V_{TP}|)^2$

$V_{SG} = 9 - (2)(1.2)(V_{SG} - 2)^2$

$= 9 - 2.4(V_{SG}^2 - 4V_{SG} + 4)$

$2.4V_{SG}^2 - 8.6V_{SG} + 0.6 = 0$

$V_{SG} = \frac{8.6 \pm \sqrt{(8.6)^2 - 4(2.4)(0.6)}}{2(2.4)}$


$V_{SG} = 3.51 \text{ V}, I_{DQ} = 2(3.51 - 2)^2$

$\Rightarrow I_{DQ} = 4.56 \text{ mA}$

$V_{SDQ} = 9 + 9 - I_{DQ}(1.2 + 1) = 18 - (4.56)(2.2)$

$\Rightarrow V_{SDQ} = 7.97 \text{ V}$

b.

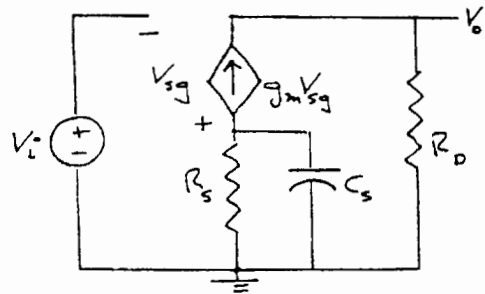

$V_o = g_m V_{SG} R_D$

$A_v = -g_m R_D = -(6.04)(1) \Rightarrow A_v = -6.04$

E6.11

$I_{DQ} = I_Q = 0.5 \text{ mA}$

Let  $\frac{W}{L} = 25$

$K_n = (20)(25) = 500 \mu\text{A/V}^2$

$V_{GS} = \sqrt{\frac{0.5}{0.5}} + 1.5 = 2.5 \text{ V} \Rightarrow V_S = -2.5 \text{ V}$

$A_v = -g_m R_D$

$g_m = 2(0.5)(2.5 - 1.5) = 1 \text{ mA/V}$

For  $A_v = -4.0 \Rightarrow R_D = 4 \text{ k}\Omega$

$V_D = 5 - (0.5)(4) = 3 \text{ V}$

$\Rightarrow V_{DSQ} = 3 - (-2.5) = 5.5 \text{ V}$

E6.12

a. With  $R_G \Rightarrow V_{GS} = V_{DS} \Rightarrow$  transistor biased in sat. region

$I_D = K_n (V_{GS} - V_{TN})^2 = K_n (V_{DS} - V_{TN})^2$

$V_{DS} = V_{DD} - I_D R_D$

$= V_{DD} - K_n R_D (V_{DS} - V_{TN})^2$

$$\begin{aligned}
 V_{DS} &= 15 - (0.15)(10)(V_{DS} - 1.8)^2 \\
 &= 15 - 1.5(V_{DS}^2 - 3.6V_{DS} + 3.24) \\
 1.5V_{DS}^2 - 4.4V_{DS} - 10.14 &= 0 \\
 V_{DS} &= \frac{4.4 \pm \sqrt{(4.4)^2 + (4)(1.5)(10.14)}}{2(1.5)} \\
 \Rightarrow V_{DSQ} &= 4.45 \text{ V} \\
 I_{DQ} &= (0.15)(4.45 - 1.8)^2 \Rightarrow I_{DQ} = 1.05 \text{ mA}
 \end{aligned}$$

b. Neglecting effect of  $R_G$  :

$$\begin{aligned}
 A_v &= -g_m(R_D \parallel R_2) \\
 g_m &= 2K_n(V_{GS} - V_{TN}) = 2(0.15)(4.45 - 1.8) \\
 \Rightarrow g_m &= 0.795 \text{ mA/V} \\
 A_v &= -(0.795)(10 \parallel 5) \Rightarrow A_v = -2.65
 \end{aligned}$$

c.  $R_G \Rightarrow$  establishes  $V_{GS} = V_{DS} \Rightarrow$  essentially no effect on small-signal voltage gain.


E6.13

$$\begin{aligned}
 \text{a. } I_{DQ} &= K_n(V_{GS} - V_{TN})^2 \\
 I_{DQ} &= 0.8(2 - V_{SG})^2 = \frac{V_{SG}}{R_S} = \frac{V_{SG}}{4} \\
 3.2(4 - 4V_{SG} + V_{SG}^2) &= V_{SG} \\
 3.2V_{SG}^2 - 13.8V_{SG} + 12.8 &= 0 \\
 V_{SG} &= \frac{13.8 \pm \sqrt{(13.8)^2 - 4(3.2)(12.8)}}{2(3.2)} \\
 V_{SG} &= 1.35 \text{ V} \Rightarrow I_{DQ} = 0.8(2 - 1.35)^2 \\
 \Rightarrow I_{DQ} &= 0.338 \text{ mA}
 \end{aligned}$$

$$\text{b. } V_{DSQ} = V_{DD} - I_{DQ}(R_D + R_S)$$

$$\begin{aligned}
 6 &= 10 - (0.338)(R_D + 4) \\
 R_D &= \frac{10 - (0.338)(4) - 6}{0.338} \Rightarrow R_D = 7.83 \text{ k}\Omega
 \end{aligned}$$

c.

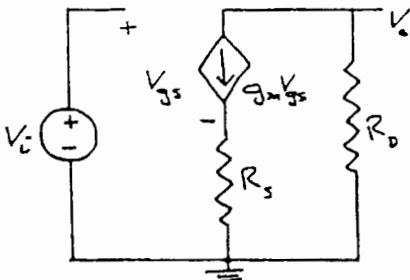


$$\begin{aligned}
 V_i &= V_{gs} + g_m V_{gs} R_S \Rightarrow V_{gs} = \frac{V_i}{1 + g_m R_S} \\
 V_o &= -g_m V_{gs} R_D \\
 g_m &= 2K_n(V_{GS} - V_{TN}) = 2(0.8)(-1.35 + 2) \\
 &= 1.04 \text{ mA/V} \\
 A_v &= \frac{V_o}{V_i} = \frac{-g_m R_D}{1 + g_m R_S} = \frac{-(1.04)(7.83)}{1 + (1.04)(4)} \\
 \Rightarrow A_v &= -1.58
 \end{aligned}$$

E6.14

$$\begin{aligned}
 \text{a. } 5 &= I_{DQ}R_S + V_{SG} \text{ and} \\
 I_{DQ} &= K_p(V_{SG} + V_{TP})^2 \\
 0.8 &= 0.5(V_{SG} + 0.8)^2 \Rightarrow V_{SG} = 0.465 \text{ V} \\
 5 &= (0.8)R_S + 0.465 \Rightarrow R_S = 5.67 \text{ k}\Omega \\
 V_{SDQ} &= 10 - I_{DQ}(R_S + R_D) \\
 3 &= 10 - (0.8)(5.67 + R_D) \\
 R_D &= \frac{10 - (0.8)(5.67) - 3}{0.8} \Rightarrow R_D = 3.08 \text{ k}\Omega
 \end{aligned}$$


b.

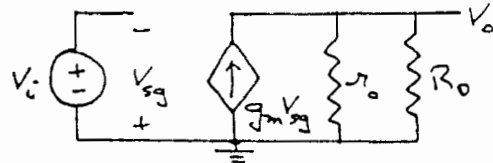

$$\begin{aligned}
 V_o &= g_m V_{sg}(R_D \parallel r_o) = -g_m V_i(R_D \parallel r_o) \\
 A_v &= \frac{V_o}{V_i} = -g_m(R_D \parallel r_o) \\
 g_m &= 2K_p(V_{SG} + V_{TP}) = 2(0.5)(0.465 + 0.8) \\
 &= 1.27 \text{ mA/V} \\
 r_o &= \frac{1}{\lambda I_o} = \frac{1}{(0.02)(0.8)} = 62.5 \text{ k}\Omega \\
 A_v &= -(1.27)(3.08 \parallel 62.5) \Rightarrow A_v = -3.73
 \end{aligned}$$

E6.15
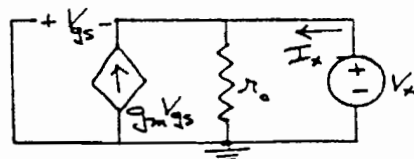
$$\begin{aligned}
 V_o &= g_m V_{gs} r_o \\
 V_i &= V_{gs} + V_o \Rightarrow V_{gs} = V_i - V_o \\
 \text{So } V_o &= g_m r_o (V_i - V_o) \\
 A_v &= \frac{V_o}{V_i} = \frac{g_m r_o}{1 + g_m r_o} = \frac{(4)(50)}{1 + (4)(50)} \\
 \Rightarrow A_v &= 0.995
 \end{aligned}$$



$$I_x + g_m V_{gs} = \frac{V_x}{r_o} \text{ and } V_{gs} = -V_x$$

$$I_x = g_m V_x + \frac{V_x}{r_o} \Rightarrow R_o = r_o \parallel \frac{1}{g_m} = 50 \parallel \frac{1}{4}$$

$$\Rightarrow \underline{R_o \approx 0.25 \text{ k}\Omega}$$

With  $R_S = 4 \text{ k}\Omega \Rightarrow A_v = \frac{g_m(r_o \parallel R_S)}{1 + g_m(r_o \parallel R_S)}$

$$r_o \parallel R_S = 50 \parallel 4 = 3.7 \text{ k}\Omega \Rightarrow A_v = \frac{(4)(3.7)}{1 + (4)(3.7)}$$

$$\Rightarrow \underline{A_v = 0.937}$$

E6.16

$$V_{DSQ} = V_{DD} - I_{DQ} R_S$$

$$5 = 10 - (1.5) R_S \Rightarrow \underline{R_S = 3.33 \text{ k}\Omega}$$

$$I_{DQ} = K_n (V_{GS} - V_{TN})^2 \Rightarrow 15 = (1)(V_{GS} - 0.8)^2$$

$$V_{GS} = 2.02 \text{ V} = V_G - V_S = V_G - 5$$

$$\Rightarrow V_G = 7.02 \text{ V} = \left( \frac{R_2}{R_1 + R_2} \right) V_{DD} = \frac{R_2}{400} \cdot 10$$

So  $\underline{R_2 = 280.8 \text{ k}\Omega}$ ,  $\underline{R_1 = 119.2 \text{ k}\Omega}$

Neglecting  $R_{Si}$ ,

$$A_v = \frac{g_m(R_S \parallel r_o)}{1 + g_m(R_S \parallel r_o)}$$

$$r_o = [\lambda I_{DQ}]^{-1} = [(0.015)(1.5)]^{-1} = 44.4 \text{ k}\Omega$$

$$R_S \parallel r_o = 3.33 \parallel 44.4 = 3.1 \text{ k}\Omega$$

$$g_m = 2\sqrt{K_n I_{DQ}} = 2\sqrt{(1)(15)} = 2.45 \text{ mA/V}$$

$$A_v = \frac{(2.45)(3.1)}{1 + (2.45)(3.1)} \Rightarrow \underline{A_v = 0.884}$$

$$R_o = \frac{1}{g_m} \parallel R_S \parallel r_o = \frac{1}{2.45} \parallel 3.33 \parallel 44.4$$

$$= 0.408 \parallel 3.1$$

$$\Rightarrow \underline{R_o = 0.36 \text{ k}\Omega}$$

E6.17

$$V_G = \left( \frac{R_2}{R_1 + R_2} \right) V_{DD} = \left( \frac{9.3}{70.7 + 9.3} \right) (5)$$

$$= 0.581 \text{ V}$$

$$I_{DQ} = K_p (V_{SG} - |V_{TP}|)^2 = K_p (V_S - V_G - |V_{TP}|)^2$$

$$= \frac{5 - V_S}{R_S}$$

Then  $(0.4)(5)(V_S - 0.581 - 0.8)^2 = 5 - V_S$

$$2(V_S - 1.381)^2 = 5 - V_S$$

$$2(V_S^2 - 2.762V_S + 1.907) = 5 - V_S$$

$$2V_S^2 - 4.52V_S - 1.19 = 0$$

$$V_S = \frac{4.52 \pm \sqrt{(4.52)^2 + 4(2)(1.19)}}{2(2)}$$

$$V_S = 2.50 \text{ V} \Rightarrow I_{DQ} = \frac{5 - 2.5}{5} = 0.5 \text{ mA}$$

$$g_m = 2\sqrt{K_p I_{DQ}} = 2\sqrt{(0.4)(0.5)} = 0.894 \text{ mA/V}$$

$$A_v = \frac{g_m R_S}{1 + g_m R_S} \cdot \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_{Si}}$$

$$= \frac{(0.894)(5)}{1 + (0.894)(5)} \cdot \frac{70.7 \parallel 9.3}{70.7 \parallel 9.3 + 0.5} \Rightarrow \underline{A_v = 0.770}$$

Neglecting  $R_{Si}$ ,  $A_v = 0.817$

$$R_o = R_S \parallel \frac{1}{g_m} = 5 \parallel \frac{1}{0.894} = 5 \parallel 1.12$$

$$\Rightarrow \underline{R_o = 0.915 \text{ k}\Omega}$$

E6.18

(a)  $g_m = 2\sqrt{K_n I_{DQ}} \Rightarrow 2 = 2\sqrt{K_n(0.8)} \Rightarrow$

$$K_n = 1.25 \text{ mA/V}^2$$

$$K_n = \frac{\mu_n C_{ox}}{2} \cdot \frac{W}{L} \Rightarrow 1.25 = (0.020) \left( \frac{W}{L} \right)$$

So  $\frac{W}{L} = 62.5$

$$I_{DQ} = K_n (V_{GS} - V_{TN})^2 \Rightarrow 0.8 = 1.25(V_{GS} - 2)^2$$

$$\Rightarrow \underline{V_{GS} = 2.8 \text{ V}}$$

b.  $r_o = [\lambda I_{DQ}]^{-1} = [(0.01)(0.8)]^{-1} = 125 \text{ k}\Omega$

$$A_v = \frac{g_m(r_o \parallel R_L)}{1 + g_m(r_o \parallel R_L)}$$

$$r_o \parallel R_L = 125 \parallel 4 = 3.88$$

$$A_v = \frac{(2)(3.88)}{1 + (2)(3.88)} \Rightarrow \underline{A_v = 0.886}$$

$$R_o = \frac{1}{g_m} \parallel r_o = \frac{1}{2} \parallel 125 \Rightarrow \underline{R_o \approx 0.5 \text{ k}\Omega}$$

E6.19

$$I_{DQ} = K_p (V_{SG} - |V_{TP}|)^2$$

$$3 = 2(V_{SG} - 2)^2 \Rightarrow V_{SG} = 3.22 \text{ V}$$

$$I_{DQ} = \frac{5 - V_{SG}}{R_S} \Rightarrow 3 = \frac{5 - 3.22}{R_S}$$

$$\Rightarrow \underline{R_S = 0.593 \text{ k}\Omega}$$

$$r_o = [\lambda I_{DQ}]^{-1} = [(0.02)(3)]^{-1} = 16.7 \text{ k}\Omega$$

$$g_m = 2\sqrt{K_p I_{DQ}} = 2\sqrt{(2)(3)} = 4.9 \text{ mA/V}$$

For  $R_L = \infty$ ,  $A_v = \frac{g_m(r_o \parallel R_S)}{1 + g_m(r_o \parallel R_S)}$

$$r_o \parallel R_S = 16.7 \parallel 0.593 = 0.573 \text{ k}\Omega$$

$$A_v = \frac{(4.9)(0.573)}{1 + (4.9)(0.573)} \Rightarrow \underline{A_v = 0.737}$$

If  $A_v$  is reduced by 10%

$$\Rightarrow A_v = 0.737 - 0.0737 = 0.663$$

$$A_v = \frac{g_m(r_o \parallel R_S \parallel R_L)}{1 + g_m(r_o \parallel R_S \parallel R_L)}$$

Let  $r_o \parallel R_S \parallel R_L = x$

$$0.663 = \frac{(4.9)x}{1 + (4.9)x} \Rightarrow 0.663 = 4.9x(1 - 0.663)$$

$$x = 0.402 = 0.573 \parallel R_L$$

$$\frac{0.573 R_L}{R_L + 0.573} = 0.402$$

$$\Rightarrow (0.573 - 0.402)R_L = (0.402)(0.573)$$

$$\Rightarrow R_L = 1.35 \text{ k}\Omega$$

E6.20

$$R_{in} = \frac{1}{g_m} = 0.35 \text{ k}\Omega \Rightarrow g_m = 2.86 \text{ mA/V}$$

$$\frac{V_o}{I_i} = R_D \parallel R_L = 2.4 = R_D \parallel 4 = \frac{4R_D}{4 + R_D}$$

$$(4 - 2.4)R_D = (2.4)(4) \Rightarrow R_D = 6 \text{ k}\Omega$$

$$g_m = 2\sqrt{K_n I_{DQ}}$$

$$2.86 = 2\sqrt{K_n(0.5)} \Rightarrow K_n = 4.09 \text{ mA/V}^2$$

$$I_{DQ} = K_n(V_{GS} - V_{TN})^2$$

$$0.5 = 4.09(V_{GS} - 1)^2 \Rightarrow V_{GS} = 1.35 \text{ V}$$

$$\Rightarrow V_S = -1.35 \text{ V}, \quad V_D = 5 - (0.5)(6) = 2 \text{ V}$$


$$V_{DS} = V_D - V_S = 2 - (-1.35) = 3.35 \text{ V}$$

We have

$$V_{DS} = 3.35 > V_{GS} - V_{TN} = 1.35 - 1 = 0.35 \text{ V}$$

$\Rightarrow$  Biased in the saturation region

E6.21

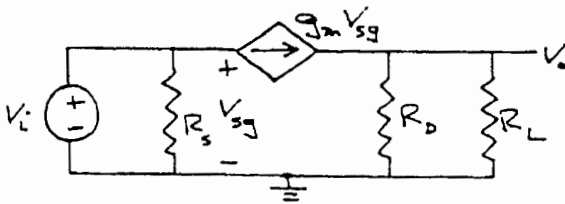

$$V_o = g_m V_{sg}(R_D \parallel R_L) \text{ and } V_{sg} = V_i$$

$$A_v = g_m(R_D \parallel R_L)$$

$$I_{DQ} = \frac{5 - V_{SG}}{R_S} = K_p(V_{SG} - |V_{TP}|)^2$$

$$5 - V_{SG} = (1)(4)(V_{SG} - 0.8)^2$$

$$5 - V_{SG} = 4(V_{SG}^2 - 1.6V_{SG} + 0.64)$$

$$4V_{SG}^2 - 5.4V_{SG} - 2.44 = 0$$

$$V_{SG} = \frac{5.4 \pm \sqrt{(5.4)^2 + (4)(4)(2.44)}}{2(4)}$$

$$V_{SG} = 1.71 \text{ V}$$

$$I_{DQ} = \frac{5 - 1.71}{4} = 0.822 \text{ mA}$$

$$g_m = 2\sqrt{K_p I_{DQ}} = 2\sqrt{(1)(0.822)} = 1.81 \text{ mA/V}$$

$$A_v = (1.81)(2 \parallel 4) = (1.81)(1.33) \Rightarrow A_v = 2.41$$

$$R_{in} = R_S \parallel \frac{1}{g_m} = 4 \parallel \frac{1}{1.81} = 4 \parallel 0.552$$

$$\Rightarrow R_{in} = 0.485 \text{ k}\Omega$$

E6.22

$$K_{n1} = \frac{\mu_n C_{ox}}{2} \cdot \left(\frac{W}{L}\right)_1 = (0.020)(80) = 1.6 \text{ mA/V}^2$$

$$K_{n2} = \frac{\mu_n C_{ox}}{2} \cdot \left(\frac{W}{L}\right)_2 = (0.020)(1) = 0.020 \text{ mA/V}^2$$

$$A_v = -\sqrt{\frac{K_{n1}}{K_{n2}}} = -\sqrt{\frac{1.6}{0.020}} \Rightarrow A_v = -8.94$$

The transition point is determined from

$$V_{GS1} - V_{TND} = V_{DD} - V_{TNL} - \sqrt{\frac{K_{n1}}{K_{n2}}}(V_{GS1} - V_{TND})$$

$$V_{GS1} - 0.8 = (5 - 0.8) - (8.94)(V_{GS1} - 0.8)$$

$$V_{GS1} = \frac{(5 - 0.8) + (8.94)(0.8) + 0.8}{1 + 8.94}$$

$$V_{GS1} = 1.22 \text{ V}$$

For Q-point in middle of saturation region

$$V_{GS} = \frac{1.22 - 0.8}{2} + 0.8 \Rightarrow V_{GS} = 1.01 \text{ V}$$

E6.23

$$K_{n2} = \frac{\mu_n C_{ox}}{2} \cdot \left(\frac{W}{L}\right)_2 = (0.015)(2) = 0.030 \text{ mA/V}^2$$

$$A_v = -\sqrt{\frac{K_{n1}}{K_{n2}}} = -6 \Rightarrow \frac{K_{n1}}{K_{n2}} = 36$$

$$K_{n1} = (36)(0.030) = 1.08 \text{ mA/V}^2$$

$$1.08 = (0.015)\left(\frac{W}{L}\right)_1 \Rightarrow \left(\frac{W}{L}\right)_1 = 72$$

The transition point is found from

$$V_{GS1} - 1 = (10 - 1) - (6)(V_{GS1} - 1)$$

$$V_{GS1} = \frac{10 - 1 + 6 + 1}{1 + 6} = 2.29 \text{ V}$$

For Q-point in middle of saturation region

$$V_{GS} = \frac{2.29 - 1}{2} + 1 \Rightarrow V_{GS} = 1.645 \text{ V}$$

E6.24

(a) Transition points:

$$\text{For } M_2: v_{oB} = V_{DD} - |V_{TNL}| = 5 - 1.2 = 3.8 \text{ V}$$

For  $M_1$ :

$$K_{n1}[(v_{oA})^2(1 + \lambda v_{oA})]$$

$$= K_{n2}[(V_{TNL})^2(1 + \lambda_2[V_{DD} - v_{oA}])]$$

$$250[v_{oA}^2 + (0.01)v_{oA}^3]$$

$$= 25[(1.2)^2(1 + (0.01)(5)) - (0.01)v_{oA}]$$

$$10[v_{\alpha 1}^2 + (0.01)v_{\alpha 1}^3] = 1512 - 0.0144v_{\alpha 1}$$

$$(0.01)v_{\alpha 1}^3 + v_{\alpha 1}^2 + 0.00144v_{\alpha 1} - 0.512 = 0$$

which yields  $v_{\alpha 1} \cong 0.388 \text{ V}$

Then middle of saturation region

$$v_{0Q} = \frac{3.8 - 0.388}{2} + 0.388 \Rightarrow V_{DSQ1} = 2.094 \text{ V}$$

$$K_{n1}[(V_{GS1} - V_{TND})^2(1 + \lambda_1 v_o)]$$

$$= K_{n2}[(V_{TNL})^2(1 + \lambda_2[V_{DD} - v_o])]$$

$$250[(V_{GS1} - 0.8)^2(1 + [0.01][2.094])]$$

$$= 25[(1.2)^2(1 + [0.01][5 - 2.094])]$$

$$10[(V_{GS1} - 0.8)^2(1.0209)] = 1.482$$

$$(V_{GS1} - 0.8)^2 = 0.145 \Rightarrow \underline{V_{GS1} = 1.18 \text{ V}}$$

b.  $I_{DQ} = K_{n1}[(V_{GS1} - 0.8)^2(1 + (0.01)(2.094))]$

$$I_{DQ} = (0.25)[(0.145)^2(1.02094)]$$

$$\Rightarrow \underline{I_{DQ} = 37.0 \mu\text{A}}$$

c.  $A_v = \frac{-g_{m1}}{I_{DQ}(\lambda_1 + \lambda_2)} = -g_{m1}(\tau_{01} \parallel \tau_{02})$

$$g_{m1} = 2K_{n1}(V_{GS1} - V_{TND})$$

$$= 2(0.25)(1.18 - 0.8) = 0.19 \text{ mA/V}$$

$$A_v = \frac{-0.19}{(0.037)(0.01 + 0.01)} \Rightarrow \underline{A_v = -257}$$

E6.25

$$R_0 = R_{S2} \parallel \frac{1}{g_{m2}}$$

$$g_{m2} = 0.632 \text{ mA/V}, \quad R_{S2} = 8 \text{ k}\Omega$$

$$R_0 = 8 \parallel \frac{1}{0.632} = 8 \parallel 1.58 \Rightarrow \underline{R_0 = 1.32 \text{ k}\Omega}$$

E6.26

a.  $I_{DQ2} = 2 \text{ mA}, \quad V_{SDQ2} = 10 \text{ V}$

$$I_{DQ2} \cdot R_{S2} = 10 = 2R_{S2} \Rightarrow \underline{R_{S2} = 5 \text{ k}\Omega}$$

$$I_{DQ2} = K_{n2}(V_{GS2} - V_{TN2})^2$$

$$2 = 1(V_{GS2} - 2)^2 \Rightarrow V_{GS2} = 3.41 \text{ V}$$

$$\Rightarrow V_{G2} = 3.41 \text{ V}$$

$$\text{Then } R_{D1} = \frac{10 - 3.41}{2} \Rightarrow \underline{R_{D1} = 3.3 \text{ k}\Omega}$$

$$\text{For } V_{DSQ1} = 10 \text{ V} \Rightarrow V_{S1} = 3.41 - 10 = -6.59 \text{ V}$$

$$\text{Then } R_{S1} = \frac{-6.59 - (-10)}{2} \Rightarrow \underline{R_{S1} = 1.71 \text{ k}\Omega}$$

$$I_{D1} = K_{n1}(V_{GS1} - V_{TN1})^2$$

$$2 = 1(V_{GS1} - 2)^2 \Rightarrow V_{GS1} = 3.41 \text{ V}$$

$$V_{GS1} = \left(\frac{R_2}{R_1 + R_2}\right)(20) - I_{DQ1}R_{S1}$$

$$\frac{R_2}{R_1 + R_2} = \frac{1}{R_1} \cdot R_{1n}$$

$$3.41 = \frac{1}{R_1}(200)(20) - (2)(1.71)$$

$$\Rightarrow \underline{R_1 = 586 \text{ k}\Omega}$$

$$\frac{586R_2}{586 + R_2} = 200 \Rightarrow (586 - 200)R_2 = (200)(586)$$

$$\Rightarrow \underline{R_2 = 304 \text{ k}\Omega}$$

b.  $g_{m1} = 2\sqrt{K_{n1}I_{DQ1}} = 2\sqrt{(1)(2)}$

$$\Rightarrow g_{m1} = g_{m2} = 2.83 \text{ mA/V}$$

From Example 6-16

$$A_v = \frac{-g_{m1}g_{m2}R_{D1}(R_{S2} \parallel R_L)}{1 + g_{m2}(R_{S2} \parallel R_L)}$$

$$R_{S2} \parallel R_L = 5 \parallel 4 = 2.22 \text{ k}\Omega$$

$$A_v = \frac{-(2.83)(2.83)(3.3)(2.22)}{1 + (2.83)(2.22)}$$

$$\Rightarrow \underline{A_v = -8.06}$$

$$R_0 = \frac{1}{g_{m2}} \parallel R_{S2} = \frac{1}{2.83} \parallel 5 = 0.353 \parallel 5$$

$$\Rightarrow \underline{R_0 = 0.330 \text{ k}\Omega}$$

E6.27

a.  $I_{DQ1} = K_{n1}(V_{GS1} - V_{TN1})^2$

$$1 = 1.2(V_{GS1} - 2)^2 \Rightarrow V_{GS1} = V_{GS2} = 2.91 \text{ V}$$

$$R_S = 10 \text{ k}\Omega \Rightarrow V_{S1} = I_{DQ1}R_S - 10$$

$$= (1)(10) - 10 = 0$$

$$V_{G1} = 2.91 = \left(\frac{R_3}{R_1 + R_2 + R_3}\right)(10)$$

$$= \left(\frac{R_3}{500}\right)(10)$$

$$\Rightarrow \underline{R_3 = 145.5 \text{ k}\Omega}$$

$$V_{DSQ1} = 3.5 \Rightarrow V_{S2} = 3.5 \text{ V} \Rightarrow 3.5 + 2.91$$

$$\Rightarrow V_{G2} = 6.41$$

$$V_{G2} = \left(\frac{R_2 + R_3}{R_1 + R_2 + R_3}\right)(10) = 6.41$$

$$= \left(\frac{R_2 + R_3}{500}\right)(10)$$

$$R_2 + R_3 = 320.5 = R_2 + 145.5 \Rightarrow \underline{R_2 = 175 \text{ k}\Omega}$$

$$\text{Then } R_1 + R_2 + R_3 = 500 = R_1 + 175 + 145.5$$

$$\Rightarrow \underline{R_1 = 179.5 \text{ k}\Omega}$$

$$\text{Now } V_{S2} = 3.5 \Rightarrow V_{D2} = V_{S2} + V_{SDQ2}$$

$$= 3.5 + 3.5 = 7 \text{ V}$$

$$\text{So } R_D = \frac{10 - 7}{1} \Rightarrow R_D = 3 \text{ k}\Omega$$

b. From Example 6-18:

$$A_v = -g_{m1} R_D$$

$$g_{m1} = 2\sqrt{K_n I_{DQ}} = 2\sqrt{(1.2)(1)} = 2.19 \text{ mA/V}$$

$$A_v = -(2.19)(3) \Rightarrow A_v = -6.57$$

E6.28

From Example 6-18:

$$g_m = 2.98 \text{ mA/V}, \quad r_o = 42.1 \text{ k}\Omega$$

$$R_1 \parallel R_2 = 420 \parallel 180 = 126 \text{ k}\Omega$$

$$V_{gs} = \left( \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_i} \right) V_i$$

$$= \left( \frac{126}{126 + 20} \right) V_i = 0.863 V_i$$

$$A_v = \frac{-g_m V_{gs} (r_o \parallel R_D \parallel R_L)}{V_i}$$

$$= -(2.98)(0.863)(42.1 \parallel 2.7 \parallel 4)$$

$$= -(2.57)(42.1 \parallel 1.61) = -(2.57)(1.55)$$

$$\Rightarrow A_v = -3.98$$

E6.29

$$V_S = I_{DQ} R_S = (1.2)(2.7) = 3.24 \text{ V}$$

$$V_D = V_S + V_{DSQ} = 3.24 + 12 = 15.24$$

$$R_D = \frac{20 - 15.24}{1.2} \Rightarrow R_D = 3.97 \text{ k}\Omega$$

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$$

$$1.2 = 4 \left( 1 - \frac{V_{GS}}{V_P} \right)^2 \Rightarrow \frac{V_{GS}}{V_P} = 0.452$$

$$V_{GS} = (0.452)(-3) = -1.356$$

$$V_G = V_S + V_{GS} = 3.24 - 1.356 = 1.88 \text{ V}$$

$$V_G = \left( \frac{R_2}{R_1 + R_2} \right) (20) = \left( \frac{R_2}{500} \right) (20) = 1.88$$

$$\Rightarrow R_2 = 47 \text{ k}\Omega, \quad R_1 = 453 \text{ k}\Omega$$

$$r_o = \frac{1}{\lambda I_{DQ}} = \frac{1}{(0.005)(1.2)} = 167 \text{ k}\Omega$$

$$g_m = \frac{2I_{DSS}}{(-V_P)} \left( 1 - \frac{V_{GS}}{V_P} \right) = \frac{2(4)}{3} \left( 1 - \frac{1.356}{3} \right) = 1.46 \text{ mA/V}$$

$$A_v = -g_m (r_o \parallel R_D \parallel R_L) = -(1.46)(167 \parallel 3.97 \parallel 4)$$

$$\Rightarrow A_v = -2.87$$

E6.30

$$\text{a. } V_{G1} = \left( \frac{R_2}{R_1 + R_2} \right) (V_{DD})$$

$$V_{G1} = \left( \frac{430}{430 + 70} \right) (20) = 17.2 \text{ V}$$

$$I_{DQ1} = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2 = 6 \left( 1 - \frac{V_{G1} - V_{S1}}{2} \right)^2$$

$$= 6 \left( 1 - \frac{17.2}{2} + \frac{V_{S1}}{2} \right)^2 = 6 \left( \frac{V_{S1}}{2} - 7.6 \right)^2$$

$$\text{and } I_{DQ1} = \frac{20 - V_{S1}}{4}$$

$$\text{Then } \frac{20 - V_{S1}}{4} = 6 \left( \frac{V_{S1}}{2} - 7.6 \right)^2$$

$$20 - V_{S1} = 24 \left( \frac{V_{S1}^2}{4} - 7.6V_{S1} + 57.76 \right)$$

$$= 6V_{S1}^2 - 182.4V_{S1} + 1386.24$$

$$6V_{S1}^2 - 181.4V_{S1} + 1366.24 = 0$$

$$V_{S1} = \frac{181.4 \pm \sqrt{(181.4)^2 - 4(6)(1366.24)}}{2(6)}$$

$$V_{S1} = 14.2 \text{ V} \Rightarrow V_{GS1} = 17.2 - 14.2$$

$$= 3 \text{ V} > V_P$$

$$\text{So } V_{S1} = 16.0 \Rightarrow V_{GS1} = 17.2 - 16$$

$$= 1.2 < V_P - Q$$

$$\text{on } I_{DQ1} = \frac{20 - 16}{4} \Rightarrow I_{DQ1} = 1 \text{ mA}$$

$$V_{SDQ1} = 20 - I_{DQ1}(R_{S1} + R_{D1})$$

$$= 20 - (1)(8)$$

$$\Rightarrow V_{SDQ1} = 12 \text{ V}$$

$$V_{D1} = I_{DQ1} R_{D1} = (1)(4) = 4 \text{ V} = V_{G2}$$

$$I_{DQ2} = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2 = 6 \left( 1 - \frac{V_{G2} - V_{S2}}{(-2)} \right)^2$$

$$= 6 \left( 1 + \frac{4}{2} - \frac{V_{S2}}{2} \right)^2 = 6 \left( 3 - \frac{V_{S2}}{2} \right)^2$$

$$\text{and } I_{DQ2} = \frac{V_{S2}}{R_{S2}} = \frac{V_{S2}}{4}$$

Then

$$\frac{V_{S2}}{4} = 6 \left( 3 - \frac{V_{S2}}{2} \right)^2$$

$$V_{S2} = 24 \left( 9 - 3V_{S2} + \frac{V_{S2}^2}{4} \right)$$

$$6V_{S2}^2 - 73V_{S2} + 216 = 0$$

$$V_{S2} = \frac{73 \pm \sqrt{(73)^2 - 4(6)(216)}}{2(6)}$$

$$\Rightarrow V_{S2} = 7.09 \text{ V or } = 5.08 \text{ V}$$


$$\text{For } V_{S2} = 5.08 \text{ V}$$

$$\Rightarrow V_{GS2} = 4 - 5.08 = -1.08 \text{ transistor biased ON}$$

$$I_{DQ2} = \frac{5.08}{4} \Rightarrow I_{DQ2} = 1.27 \text{ mA}$$

$$V_{DS2} = 20 - V_{S2} = 20 - 5.08 \Rightarrow \underline{V_{DS2} = 14.9 \text{ V}}$$

b.

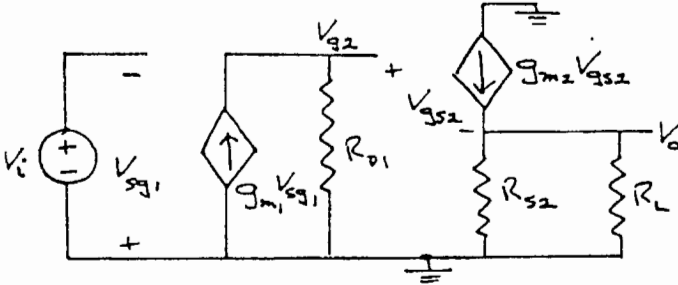

$$V_{g2} = g_{m1} V_{gs1} R_{D1} = -g_{m1} V_i R_{D1}$$

$$V_o = g_{m2} V_{gs2} (R_{S2} \parallel R_L)$$

$$V_{g2} = V_{gs2} + V_o \Rightarrow V_{gs2} = \frac{V_{g2}}{1 + g_{m2} (R_{S2} \parallel R_L)}$$

$$A_v = \frac{V_o}{V_i} = \frac{-g_{m1} R_{D1}}{1 + g_{m2} (R_{S2} \parallel R_L)}$$

$$g_{m1} = \frac{2I_{DSS}}{|V_P|} \left(1 - \frac{V_{GS}}{V_P}\right)$$

$$= \frac{2(6)}{2} \left(1 - \frac{1.2}{2}\right) = 2.4 \text{ mA/V}$$

$$g_{m2} = \frac{2(6)}{2} \left(1 - \frac{1.08}{2}\right) = 2.76 \text{ mA/V}$$

$$\text{Then } A_v = \frac{-(2.4)(4)}{1 + (2.76)(4)(2)} = \underline{-2.05 = A_v}$$

E6.31

a.

$$I_{DQ} = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$


$$2 = 8 \left(1 - \frac{V_{GS}}{V_P}\right)^2 \Rightarrow \frac{V_{GS}}{V_P} = 0.5$$

$$V_{GS} = (0.5)(-3.5) \Rightarrow V_{GS} = -1.75$$

$$\text{Also } I_{DQ} = \frac{-V_{GS} - (-10)}{R_S}$$

$$2 = \frac{1.75 + 10}{R_S} \Rightarrow \underline{R_S = 5.88 \text{ k}\Omega}$$

b.

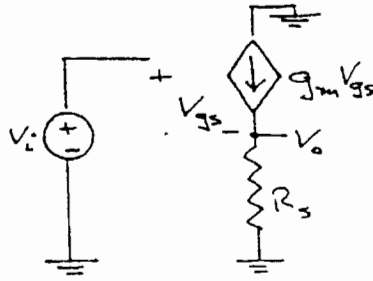

$$g_m = \frac{2I_{DSS}}{|V_P|} \left(1 - \frac{V_{GS}}{V_P}\right) = \frac{2(8)}{3.5} \left(1 - \frac{1.75}{3.5}\right)$$

$$= 2.29 \text{ mA/V}$$

$$r_o = \frac{1}{(0.01)(2)} = 50 \text{ k}\Omega$$

$$V_i = V_{gs} + g_m R_S V_{gs} \Rightarrow V_{gs} = \frac{V_i}{1 + g_m R_S}$$

$$A_v = \frac{V_o}{V_i} = \frac{g_m R_S \parallel r_o}{1 + g_m R_S \parallel r_o} = \frac{(2.29)[5.88 \parallel 50]}{1 + (2.29)[5.88 \parallel 50]}$$

$$\Rightarrow \underline{A_v = 0.923}$$

c.

$$A_v = \frac{g_m (R_S \parallel R_L)}{1 + g_m (R_S \parallel R_L)} = 0.931 - 0.186 = 0.745$$

$$\frac{(2.29)(R_S \parallel R_L)}{1 + (2.29)(R_S \parallel R_L)} = 0.745$$

$$(2.29)(R_S \parallel R_L)(1 - 0.745) = 0.745$$

$$\Rightarrow R_S \parallel R_L = 1.28 \text{ k}\Omega$$

$$\frac{5.88 R_L}{5.88 + R_L} = 1.28$$

$$\Rightarrow (5.88 - 1.28) R_L = (1.28)(5.88)$$

$$\Rightarrow \underline{R_L = 1.64 \text{ k}\Omega}$$

## Chapter 6

## Problem Solutions

6.1

$$(a) \quad g_m = 2\sqrt{K_n I_D} = 2\sqrt{\left(\frac{\mu_n C_{ox}}{2}\right)\left(\frac{W}{L}\right)I_D}$$

$$0.5 = 2\sqrt{(0.020)\left(\frac{W}{L}\right)(0.5)} \Rightarrow \frac{W}{L} = 12.5$$

$$(b) \quad I_D = \left(\frac{\mu_n C_{ox}}{2}\right)\left(\frac{W}{L}\right)(V_{GS} - V_{TN})^2$$

$$0.5 = (0.02)(12.5)(V_{GS} - 0.8)^2$$

$$\Rightarrow \underline{V_{GS} = 2.21 \text{ V}}$$

6.2

$$(a) \quad g_m = 2\sqrt{K_p I_D} = 2\sqrt{\left(\frac{\mu_p C_{ox}}{2}\right)\left(\frac{W}{L}\right)I_D}$$

$$\left(\frac{50}{2}\right)^2 = (10)\left(\frac{W}{L}\right)(100) \Rightarrow \frac{W}{L} = 0.625$$

$$(b) \quad I_D = \left(\frac{\mu_p C_{ox}}{2}\right)\left(\frac{W}{L}\right)(V_{SG} + V_{TP})^2$$

$$100 = (10)(0.625)(V_{SG} - 1.2)^2$$

$$\Rightarrow \underline{V_{SG} = 4.2 \text{ V}}$$

6.3

$$I_D = K_n(V_{GS} - V_{TN})^2(1 + \lambda V_{DS})$$

$$\frac{I_{D1}}{I_{D2}} = \frac{1 + \lambda V_{DS1}}{1 + \lambda V_{DS2}} \Rightarrow \frac{3.4}{3.0} = \frac{1 + \lambda(10)}{1 + \lambda(5)}$$

$$3.4[1 + 5\lambda] = 3.0[1 + 10\lambda]$$

$$3.4 - 3.0 = \lambda(3 \cdot 10 - (3.4) \cdot 5)$$

$$\Rightarrow \underline{\lambda = 0.0308}$$

$$r_o \approx \frac{1}{\lambda I_D} = \frac{1}{(0.0308)(3)} \Rightarrow \underline{r_o = 10.8 \text{ k}\Omega}$$

6.4

$$r_o = \frac{1}{\lambda I_D}$$

$$I_D = \frac{1}{\lambda r_o} = \frac{1}{(0.012)(100)} \Rightarrow \underline{I_D = 0.833 \text{ mA}}$$

6.5

$$A_v = -g_m(r_o \parallel R_D) = -(1)(50 \parallel 10)$$

$$\Rightarrow \underline{A_v = -8.33}$$

6.6

$$a. \quad R_D = \frac{V_{DD} - V_{DSQ}}{I_{DQ}} = \frac{10 - 6}{0.5} \Rightarrow \underline{R_D = 8 \text{ k}\Omega}$$

For  $V_{GSQ} = 2 \text{ V}$ , for example,

$$I_{DQ} = \left(\frac{\mu_n C_{ox}}{2}\right)\left(\frac{W}{L}\right)(V_{GSQ} - V_{TN})^2$$

$$0.5 = (0.030)\left(\frac{W}{L}\right)(2 - 0.8)^2$$

$$\Rightarrow \underline{\frac{W}{L} = 11.6}$$

$$b. \quad g_m = 2\sqrt{K_n I_{DQ}} = 2K_n(V_{GSQ} - V_{TN})$$

$$g_m = 2(0.030)(11.6)(2 - 0.8)$$

$$\Rightarrow \underline{g_m = 0.835 \text{ mA/V}}$$

$$I_{DQ} = (0.030)(11.6)(2 - 0.8)^2 = 0.501 \text{ mA}$$

$$r_o = \frac{1}{\lambda I_{DQ}} = \frac{1}{(0.015)(0.501)} \Rightarrow \underline{r_o = 133 \text{ k}\Omega}$$

$$c. \quad A_v = -g_m(r_o \parallel R_D) = -(0.835)(133 \parallel 8)$$

$$\Rightarrow \underline{A_v = -6.30}$$

6.7

$$K_n v_{gs}^2 = K_n [V_{gs} \sin \omega t]^2 = K_n V_{gs}^2 \sin^2 \omega t$$

$$\sin^2 \omega t = \frac{1}{2}[1 - \cos 2\omega t]$$

$$\text{So } K_n v_{gs}^2 = \frac{K_n V_{gs}^2}{2}[1 - \cos 2\omega t]$$

Ratio of signal at  $2\omega$  to that at  $\omega$ :

$$\frac{\frac{K_n V_{gs}^2}{2} \cdot \cos 2\omega t}{2K_n(V_{GSQ} - V_{TN})V_{gs} \cdot \sin \omega t}$$

$$\frac{V_{gs}}{4(V_{GSQ} - V_{TN})}$$

The coefficient of this expression is then:

$$\frac{V_{gs}}{4(V_{GSQ} - V_{TN})}$$

6.8

$$0.01 = \frac{V_{gs}}{4(V_{GSQ} - V_{TN})}$$

$$\text{So } V_{gs} = (0.01)(4)(3 - 1)$$

$$\Rightarrow \underline{V_{gs} = 0.08 \text{ V}}$$

6.9

$$V_o = -g_m V_{gs}(r_o \parallel R_D)$$

$$V_{gs} = \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_{si}} \cdot V_i = \left(\frac{50}{50 + 2}\right) \cdot V_i = (0.962)V_i$$

$$A_v = -g_m(0.962)(r_o \parallel R_D) = -(1)(0.962)(50 \parallel 10) \Rightarrow$$

$$\underline{A_v = -8.02}$$

6.10

$$A_v = -g_m(r_o \parallel R_D)$$

$$-10 = -g_m(100 \parallel 5)$$

$$\Rightarrow \underline{g_m = 2.1 \text{ mA/V}}$$

6.11

a.  $V_G = \left(\frac{R_2}{R_1 + R_2}\right) V_{DD}$

$$V_G = \left(\frac{200}{200 + 300}\right)(12) = 4.8 \text{ V}$$

$$I_D = \frac{V_G - V_{GS}}{R_S} = K_n(V_{GS} - V_{TN})^2$$

$$4.8 - V_{GS} = (1)(2)(V_{GS}^2 - 4V_{GS} + 4)$$

$$2V_{GS}^2 - 7V_{GS} + 3.2 = 0$$

$$V_{GS} = \frac{7 \pm \sqrt{(7)^2 - 4(2)(3.2)}}{2(2)} = 2.96 \text{ V}$$

$$I_D = (1)(2.96 - 2)^2 \Rightarrow \underline{I_D = 0.920 \text{ mA}}$$

$$V_{DS} = V_{DD} - I_D(R_D + R_S)$$

$$= 12 - (0.92)(3 + 2)$$

$$\Rightarrow \underline{V_{DS} = 7.4 \text{ V}}$$

(b)  $V_o = \frac{-g_m V_{gs}(R_D \parallel R_L)}{1 + g_m R_S}$

where  $V_{gs} = \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_{Si}} \cdot V_i = \frac{300 \parallel 200}{300 \parallel 200 + 2} \cdot V_i$

$$= \frac{120}{120 + 2} \cdot V_i = (0.984)V_i$$


Then

$$A_v = \frac{-g_m(0.984)(R_D \parallel R_L)}{1 + g_m R_S}$$

$$g_m = 2(1)(2.96 - 2) = 1.92 \text{ mA/V}$$

$$\text{So } A_v = \frac{-(1.92)(0.984)(3 \parallel 3)}{1 + (1.92)(2)} \Rightarrow \underline{A_v = -0.586}$$

c.

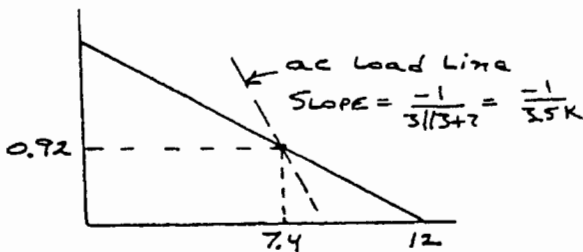

$$\Delta i_D = \frac{-1}{3.5 \text{ k}\Omega} \cdot \Delta v_{DS}$$

$$\Delta i_D = 0.92 \text{ mA}$$

$$\Rightarrow |\Delta v_{DS}| = (0.92)(3.5) = 3.22$$

$$\Rightarrow \underline{6.44 \text{ V peak-to-peak}}$$

6.12

a.  $I_{DQ} = 3 \text{ mA} \Rightarrow V_S = I_{DQ} R_S = (3)(0.5) = 1.5 \text{ V}$

$$I_{DQ} = K_n(V_{GS} - V_{TN})^2$$

$$3 = (2)(V_{GS} - 2)^2 \Rightarrow V_{GS} = 3.22 \text{ V}$$

$$V_G = V_{GS} + V_S = 3.22 + 1.5 = 4.72 \text{ V}$$

$$V_G = \left(\frac{R_2}{R_1 + R_2}\right) V_{DD} = \frac{1}{R_1} \cdot R_{in} \cdot V_{DD}$$

$$4.72 = \frac{1}{R_1}(200)(15) \Rightarrow \underline{R_1 = 636 \text{ k}\Omega}$$

$$\frac{636 R_2}{636 + R_2} = 200 \Rightarrow \underline{R_2 = 292 \text{ k}\Omega}$$

b.  $A_v = \frac{-g_m(R_D \parallel R_L)}{1 + g_m R_S}$

$$g_m = 2(2)(3.22 - 2) = 4.88 \text{ mA/V}$$

$$A_v = \frac{-(4.88)(2 \parallel 5)}{1 + (4.88)(0.5)} \Rightarrow \underline{A_v = -2.03}$$

6.13

From Problem 6-11:  $I_D = 0.920 \text{ mA}$


$$V_{DS} = 7.4 \text{ V}$$

$$g_m = 1.92 \text{ mA/V}$$

$$A_v = -g_m(R_D \parallel R_L) \left(\frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_{Si}}\right)$$

$$= -(1.92)(3 \parallel 3) \left(\frac{200 \parallel 300}{200 \parallel 300 + 2}\right) = -(2.88)(0.984)$$

$$\underline{A_v = -2.83}$$

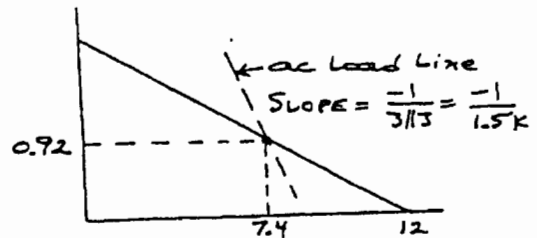


$$\Delta i_D = \frac{-1}{1.5 \text{ k}\Omega} \cdot \Delta v_{DS}, \Delta i_D = 0.92 \text{ mA}$$

$$\Rightarrow |\Delta v_{DS}| = (0.92)(1.5) = 1.38$$

$$\Rightarrow \underline{2.76 \text{ V peak-to-peak output voltage swing}}$$

6.14

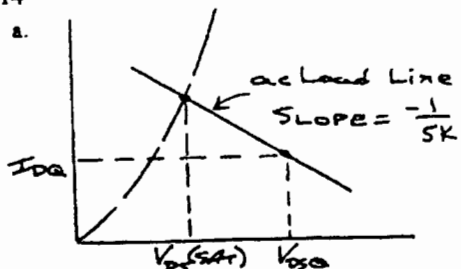

$$V_{DSQ} = V^+ - I_{DQ}R_D - (-V_{GSQ})$$

$$\text{Output Voltage Swing} = V_{DSQ} - V_{DS}(\text{sat})$$

$$= [V^+ - I_{DQ}R_D + V_{GSQ}] - (V_{GSQ} - V_{TN})$$

$$= V^+ - I_{DQ}R_D + V_{TN}$$

$$\text{So } |\Delta I_D| = I_{DQ} = \frac{1}{5 \text{ k}\Omega} \cdot |\Delta V_{DS}|$$

$$= \frac{1}{5 \text{ k}\Omega} [V^+ - I_{DQ}R_D + V_{TN}]$$

$$I_{DQ} = \frac{1}{5 \text{ k}\Omega} [5 - I_{DQ}(10) + 1]$$

$$= 1.2 - 2I_{DQ} = I_{DQ}$$

$$\Rightarrow \underline{I_{DQ} = 0.4 \text{ mA} = I_Q}$$

$$\text{b. } g_m = 2\sqrt{K_n I_{DQ}} = 2\sqrt{(0.5)(0.4)} = 0.894 \text{ mA/V}$$

$$r_o = \frac{1}{\lambda I_{DQ}} = \frac{1}{(0.01)(0.4)} = 250 \text{ k}\Omega$$

$$A_v = -g_m(R_D \parallel R_L \parallel r_o)$$

$$= -(0.894)(10 \parallel 10 \parallel 250)$$

$$\Rightarrow \underline{A_v = -4.38}$$

6.15

$$\text{a. } I_D = K_n(V_{GS} - V_{TN})^2$$

$$2 = 4(V_{GS} - (-1))^2$$

$$V_{GS} = -0.293 \text{ V}$$

$$\Rightarrow V_S = 0.293 \text{ V} = I_D R_S = (2)R_S$$

$$\Rightarrow \underline{R_S = 0.146 \text{ k}\Omega}$$

$$V_D = V_{DS} + V_S = 6 + 0.293 = 6.293$$

$$R_D = \frac{10 - 6.293}{2} \Rightarrow \underline{R_D = 1.85 \text{ k}\Omega}$$


$$\text{b. } A_v = \frac{-g_m(R_D \parallel R_L)}{1 + g_m R_S}$$

$$g_m = 2K_n(V_{GS} - V_{TN})$$

$$g_m = 2(4)(-0.293 + 1) = 5.66 \text{ mA/V}$$

$$A_v = \frac{-(5.66)(1.85 \parallel 2)}{1 + (5.66)(0.146)} \Rightarrow \underline{A_v = -2.98}$$

c.

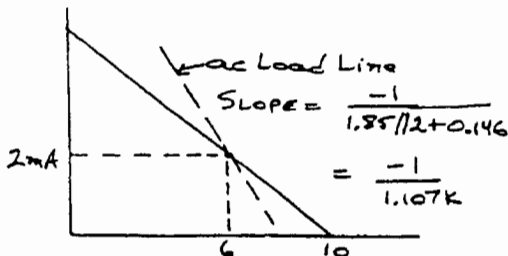

$$\Delta v_o = (\Delta i_D)(1.85 \parallel 2) = (2)(1.85 \parallel 2)$$

$$= 1.92 \text{ V}$$

$$\Delta v_i = \frac{1.92}{2.98} = 0.645 \Rightarrow \underline{V_i = 0.645 \text{ V}}$$

6.16

$$\text{a. } V_{DSQ} = V_{DD} - I_{DQ}(R_D + R_S)$$

$$2.5 = 5 - I_{DQ}(2 + R_S)$$

$$I_{DQ} = \frac{2.5}{2 + R_S}$$

$$I_{DQ} = K_n(V_{GS} - V_{TN})^2 = \frac{-V_{GS}}{R_S}$$

$$\Rightarrow V_{GS} = -I_{DQ}R_S = \frac{-2.5R_S}{2 + R_S}$$

$$K_n \left[ \frac{-2.5R_S}{2 + R_S} - V_{TN} \right]^2 = \frac{2.5}{2 + R_S}$$

$$4 \left[ 1 - \frac{2.5R_S}{2 + R_S} \right]^2 = \frac{2.5}{2 + R_S}$$

$$4 \left[ \frac{2 + R_S - 2.5R_S}{2 + R_S} \right]^2 = \frac{2.5}{2 + R_S}$$

$$4 \frac{(2 - 1.5R_S)^2}{2 + R_S} = 2.5$$

$$4(4 - 6R_S + 2.25R_S^2) = 2.5(2 + R_S)$$

$$9R_S^2 - 26.5R_S + 11 = 0$$

$$R_S = \frac{26.5 \pm \sqrt{(26.5)^2 - 4(9)(11)}}{2(9)}$$

$$R_S = 0.5 \text{ k}\Omega \text{ or } 2.44 \text{ k}\Omega$$

But  $R_S = 2.44 \text{ k}\Omega \Rightarrow V_{GS} = -1.37 \text{ V}$  Cut off.

$$\Rightarrow \underline{R_S = 0.5 \text{ k}\Omega}, \quad \underline{I_{DQ} = 1.0 \text{ mA}}$$

$$\text{b. } A_v = \frac{-g_m(R_D \parallel R_L)}{1 + g_m R_S}$$

$$g_m = 2\sqrt{K_n I_{DQ}} = 2\sqrt{(4)(1)} = 4 \text{ mA/V}$$

$$A_v = \frac{-(4)(2 \parallel 2)}{1 + (4)(0.5)} \Rightarrow \underline{A_v = -1.33}$$

6.17

$$\text{a. } 5 = I_{DQ}R_S + V_{SDQ} + I_{DQ}R_D - 5$$

$$5 = I_{DQ}R_S + 6 + I_{DQ}(10) - 5$$

$$1. \quad \underline{I_{DQ} = \frac{4}{R_S + 10}}$$

$$V_S = V_{SDQ} + I_{DQ}R_D - 5 = V_{SGQ}$$

$$2. \quad 1 + I_{DQ}(10) = V_{SGQ}$$

$$3. \quad I_{DQ} = K_p(V_{SGQ} - 2)^2$$

Choose  $R_S = 10 \text{ k}\Omega \Rightarrow I_{DQ} = \frac{4}{20} = 0.20 \text{ mA}$

$V_{SGQ} = 1 + (0.2)(10) = 3 \text{ V}$

$0.20 = K_p(3-2)^2 \Rightarrow K_p = 0.20 \text{ mA/V}^2$

b.  $I_{DQ} = (0.20)(3-2)^2 = 0.20 \text{ mA}$

$g_m = 2\sqrt{K_p I_{DQ}} = 2\sqrt{(0.2)(0.2)} = 0.4 \text{ mA/V}$

$A_v = -g_m(R_D \parallel R_L) = -(0.4)(10 \parallel 10)$

$\Rightarrow A_v = -2.0$

c. Choose  $R_S = 20 \text{ k}\Omega \Rightarrow I_{DQ} = \frac{4}{30} = 0.133 \text{ mA}$

$V_{SGQ} = 1 + (0.133)(10) = 2.33 \text{ V}$

$0.133 = K_p(2.33-2)^2 \Rightarrow K_p = 1.22 \text{ mA/V}^2$

$g_m = 2\sqrt{(1.22)(0.133)} = 0.806 \text{ mA/V}$

$A_v = -(0.806)(10 \parallel 10) \Rightarrow A_v = -4.03$

A larger gain can be achieved.

6.18

a.  $I_{DQ} = 1 = K_p(V_{SGQ} + V_{TP})^2$

$1 = 5(V_{SGQ} - 1.5)^2 \Rightarrow V_{SGQ} = 1.95 \text{ V}$

$R_S = \frac{5-1.95}{1} \Rightarrow R_S = 3.05 \text{ k}\Omega$

$V_{SDQ} = 10 - I_{DQ}(R_S + R_D)$


$5 = 10 - (1)(3.05 + R_D) \Rightarrow R_D = 1.95 \text{ k}\Omega$

b.  $g_m = 2\sqrt{K_p I_{DQ}} = 2\sqrt{(5)(1)} = 4.47 \text{ mA/V}$

$A_v = -g_m(R_D \parallel R_L) = -(4.47)(1.95 \parallel 2)$

$\Rightarrow A_v = -4.41$

c.

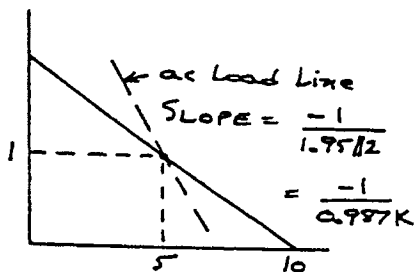

$\Delta i_D = -\frac{1}{0.987 \text{ k}\Omega} \cdot \Delta v_{DS}$

$\Rightarrow |\Delta v_{DS}| = (1)(0.987) = 0.987 \text{ V}$

Swing in output voltage = 1.97 V peak-to-peak

6.19

$I_{DQ} = K_n(V_{GSQ} - V_{TN})^2$

$g_m = 2\sqrt{K_n I_{DQ}}$

$2.2 = 2\sqrt{K_n(6)} \Rightarrow K_n = 0.202 \text{ mA/V}^2$

$6 = 0.202(2.8 - V_{TN})^2 \Rightarrow V_{TN} = -2.65 \text{ V}$

$V_{DSQ} = 18 - I_{DQ}(R_S + R_D)$

$R_S + R_D = \frac{18-10}{6} = 1.33 \text{ k}\Omega \Rightarrow R_S = 1.33 - R_D$

$A_v = -\frac{g_m(R_D \parallel R_L)}{1 + g_m R_S}$

$-1 = \frac{-2.2 \left( \frac{R_D \cdot 1}{R_D + 1} \right)}{1 + (2.2)(1.33 - R_D)}$

$1 + 2.93 - 2.2R_D = \frac{2.2R_D}{1 + R_D}$

$(3.93 - 2.2R_D)(1 + R_D) = 2.2R_D$

$3.93 + 1.73R_D - 2.2R_D^2 = 2.2R_D$

$2.2R_D^2 + 0.47R_D - 3.93 = 0$

$R_D = \frac{-0.47 + \sqrt{(0.47)^2 + 4(2.2)(3.93)}}{2(2.2)}$

$\Rightarrow R_D = 1.23 \text{ k}\Omega, R_S = 0.10 \text{ k}\Omega$


$V_G = V_{GS} + V_S = 2.8 + (6)(0.1) = 3.4 \text{ V}$

$V_G = \frac{1}{R_1} \cdot R_{in} \cdot V_{DD} = \frac{1}{R_1}(100)(18) = 3.4$

$\Rightarrow R_1 = 529 \text{ k}\Omega$

$\frac{529R_2}{529 + R_2} = 100 \Rightarrow R_2 = 123 \text{ k}\Omega$

6.20

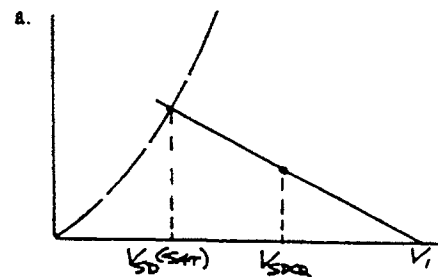

$V_i = 9 + V_{SG}, V_{SD}(\text{sat}) = V_{SG} + V_{TP}$

$V_{SDQ} = \frac{V_i - V_{SD}(\text{sat})}{2} + V_{SD}(\text{sat})$

$= \frac{(9 + V_{SG}) - (V_{SG} + V_{TP})}{2} + (V_{SG} + V_{TP})$

$= \frac{9 + 1.5}{2} + V_{SG} - 1.5$

$V_{SDQ} = 3.75 + V_{SG} = 9 + V_{SG} - I_{DQ}R_D$

$I_{DQ} = K_p(V_{SG} + V_{TP})^2$

Set  $R_D = 0.1R_L = 2 \text{ k}\Omega$

$3.75 = 9 - I_{DQ}(2) \Rightarrow I_{DQ} = 2.625 \text{ mA}$

b.  $g_m = 2\sqrt{K_p I_{DQ}} = 2\sqrt{(2)(2.625)} = 4.58 \text{ mA/V}$

$r_o = \frac{1}{\lambda I_{DQ}} = \frac{1}{(0.01)(2.625)} = 38.1 \text{ k}\Omega$

Open circuit.

$A_v = -g_m(R_D \parallel r_o)$

$A_v = -4.58(2 \parallel 38.1) \Rightarrow \underline{A_v = -8.70}$

c. With  $R_L$

$A_v = -4.58(2 \parallel 20 \parallel 38.1) \Rightarrow \underline{A_v = -7.95}$

$\Rightarrow \underline{\text{Change} = 8.62\%}$

6.21

a.  $I_{DQ} = K_p(V_{SG} + V_{TP})^2$

$2 = (0.5)(V_{SG} + 2)^2 \Rightarrow V_{SG} = 0 \text{ V}$

$R_S = \frac{10 - 0}{2} \Rightarrow \underline{R_S = 5 \text{ k}\Omega}$

$V_D = 0 - V_{SDQ} = 0 - 6 \Rightarrow R_D = \frac{-6 - (-10)}{2}$

$\Rightarrow \underline{R_D = 2 \text{ k}\Omega}$

$A_v = -g_m R_D$

b.  $g_m = 2\sqrt{K_p I_{DQ}} = 2\sqrt{(0.5)(2)} = 2 \text{ mA/V}$

$A_v = -(2)(2) \Rightarrow \underline{A_v = -4.0}$

6.22

$A_v = -g_m(R_D \parallel R_L)$

$V_{DSQ} = V_{DD} - I_{DQ}(R_S + R_D)$

$10 = 20 - (1)(R_S + R_D) \Rightarrow R_S + R_D = 10 \text{ k}\Omega$

Let  $R_D = 8 \text{ k}\Omega$ .  $R_S = 2 \text{ k}\Omega$

$A_v = -10 = -g_m(8 \parallel 20)$

$g_m = 1.75 \text{ mA/V} = 2\sqrt{K_n I_{DQ}} = 2\sqrt{K_n(1)} \Rightarrow$

$K_n = 0.766 \text{ mA/V}^2$

$V_S = I_{DQ} R_S = (1)(2) = 2 \text{ V}$

$I_{DQ} = K_n(V_{GS} - V_{TN})^2 \Rightarrow 1 = 0.766(V_{GS} - 2)^2$

$\Rightarrow V_{GS} = 3.31 \text{ V}$

$V_G = V_{GS} + V_S = 3.31 + 2 = 5.31$

$V_G = \frac{1}{R_1} \cdot R_{in} \cdot V_{DD}$

$\Rightarrow \frac{1}{R_1}(200)(20) = 5.31 \Rightarrow \underline{R_1 = 753 \text{ k}\Omega}$

$\frac{753 R_2}{753 + R_2} = 200 \Rightarrow \underline{R_2 = 272 \text{ k}\Omega}$

6.23

$A_v = \frac{g_m r_o}{1 + g_m r_o} = \frac{(4)(50)}{1 + (4)(50)} \Rightarrow \underline{A_v = 0.995}$

$R_o = \frac{1}{g_m} \parallel r_o = \frac{1}{4} \parallel 50 \Rightarrow \underline{R_o = 0.249 \text{ k}\Omega}$

$A_v = \frac{g_m(r_o \parallel R_S)}{1 + g_m(r_o \parallel R_S)} = \frac{4(50 \parallel 2.5)}{1 + 4(50 \parallel 2.5)}$

$= \frac{4(2.38)}{1 + 4(2.38)} \Rightarrow \underline{A_v = 0.905}$

$R_o = \frac{1}{g_m} \parallel r_o \parallel R_S = \frac{1}{4} \parallel 50 \parallel 2.5$

$\Rightarrow \underline{R_o = 0.226 \text{ k}\Omega}$

6.24

a.  $V_G = \left(\frac{R_2}{R_1 + R_2}\right)V_{DD} = \left(\frac{396}{396 + 1240}\right)(10)$

$\Rightarrow V_G = 2.42 \text{ V}$

$I_{DQ} = \frac{10 - (V_{SG} + 2.42)}{R_S} = K_p(V_{SG} + V_{TP})^2$

$7.58 - V_{SG} = (2)(4)(V_{SG}^2 - 4V_{SG} + 4)$

$8V_{SG}^2 - 31V_{SG} + 24.4 = 0$

$V_{SG} = \frac{31 \pm \sqrt{(31)^2 - 4(8)(24.4)}}{2(8)}$

$\Rightarrow V_{SG} = 2.78 \text{ V}$

$I_{DQ} = (2)(2.78 - 2)^2 \Rightarrow \underline{I_{DQ} = 1.21 \text{ mA}}$

$V_{SDQ} = 10 - I_{DQ} R_S = 10 - (1.21)(4)$


$\Rightarrow \underline{V_{SDQ} = 5.16 \text{ V}}$

b.  $g_m = 2\sqrt{K_p I_{DQ}} = 2\sqrt{(2)(1.21)} = 3.11 \text{ mA/V}$

$r_o = \frac{1}{\lambda I_{DQ}} = \frac{1}{(0.02)(1.21)} = 41.3 \text{ k}\Omega$

$A_v = \frac{g_m(R_S \parallel R_L \parallel r_o)}{1 + g_m(R_S \parallel R_L \parallel r_o)}$

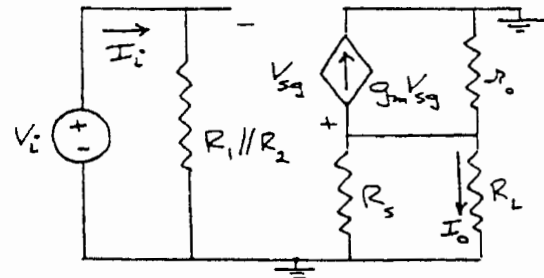$= \frac{3.11(4 \parallel 4 \parallel 41.3)}{1 + (3.11)(4 \parallel 4 \parallel 41.3)} \Rightarrow \underline{A_v = 0.886}$



$I_o = -(g_m V_{sg}) \left( \frac{R_S \parallel r_o}{R_S \parallel r_o + R_L} \right)$

$V_{sg} = \frac{-V_i}{1 + g_m(R_S \parallel R_L \parallel r_o)}$

$V_i = I_i(R_1 \parallel R_2)$

$$A_i = \frac{I_o}{I_i} = \frac{g_m(R_1 \parallel R_2)}{1 + g_m(R_S \parallel R_L \parallel r_o)} \cdot \frac{R_S \parallel r_o}{R_S \parallel r_o + R_L}$$

$$= \frac{(3.11)(396 \parallel 1240)}{1 + (3.11)(4 \parallel 4 \parallel 41.3)} \cdot \frac{4 \parallel 41.3}{4 \parallel 41.3 + 4}$$

$$= \frac{(3.11)(300)}{1 + (3.11)(1.908)} \cdot \frac{3.647}{3.647 + 4}$$

$$\Rightarrow A_v = 64.2$$

$$R_o = \frac{1}{g_m} \parallel R_S \parallel R_L \parallel r_o = \frac{1}{3.11} \parallel 4 \parallel 4 \parallel 41.3$$

$$\Rightarrow R_o = 0.275 \text{ k}\Omega$$

6.25

$$g_m = 2\sqrt{K_n I_Q} = 2\sqrt{(1)(1)} = 2 \text{ mA/V}$$

$$r_o = \frac{1}{\lambda I_Q} = \frac{1}{(0.01)(1)} = 100 \text{ k}\Omega$$

$$A_v = \frac{g_m(r_o \parallel R_L)}{1 + g_m(r_o \parallel R_L)} = \frac{2(100 \parallel 4)}{1 + 2(100 \parallel 4)}$$

$$\Rightarrow A_v = 0.885$$

$$R_o = \frac{1}{g_m} \parallel r_o = \frac{1}{2} \parallel 100 \Rightarrow R_o = 0.490 \text{ k}\Omega$$

6.26

a.  $A_v = \frac{g_m R_L}{1 + g_m R_L} \Rightarrow 0.95 = \frac{g_m(4)}{1 + g_m(4)}$

$$0.95 = 4(1 - 0.95)g_m \Rightarrow g_m = 4.75 \text{ mA/V}$$

$$g_m = 2\sqrt{\left(\frac{1}{2}\mu_n C_{ox}\right)\left(\frac{W}{L}\right)I_Q}$$

$$4.75 = 2\sqrt{(0.030)\left(\frac{W}{L}\right)(4)} \Rightarrow \frac{W}{L} = 47.0$$

b.  $g_m = 2\sqrt{\left(\frac{1}{2}\mu_n C_{ox}\right)\left(\frac{W}{L}\right)I_Q}$

$$4.75 = 2\sqrt{(0.030)(60)I_Q} \Rightarrow I_Q = 3.13 \text{ mA}$$

6.27

$$I_{DQ} = K_n(V_{GS} - V_{TN})^2$$

$$5 = 5(V_{GS} + 2)^2 \Rightarrow V_{GS} = -1 \text{ V}$$

$$\Rightarrow V_S = -V_{GS} = 1 \text{ V}$$

$$I_{DQ} = \frac{V_S - (-5)}{R_S} \Rightarrow R_S = \frac{1 + 5}{5} \Rightarrow R_S = 1.2 \text{ k}\Omega$$

$$g_m = 2\sqrt{K_n I_{DQ}} = 2\sqrt{(5)(5)} = 10 \text{ mA/V}$$

$$r_o = \frac{1}{\lambda I_{DQ}} = \frac{1}{(0.01)(5)} = 20 \text{ k}\Omega$$

$$A_v = \frac{g_m(r_o \parallel R_S \parallel R_L)}{1 + g_m(r_o \parallel R_S \parallel R_L)}$$

$$= \frac{(10)(20 \parallel 1.2 \parallel 2)}{1 + (10)(20 \parallel 1.2 \parallel 2)} \Rightarrow A_v = 0.878$$

$$R_o = \frac{1}{g_m} \parallel r_o \parallel R_S = \frac{1}{10} \parallel 20 \parallel 1.2$$

$$\Rightarrow R_o = 91.9 \Omega$$

6.28

$$A_v = \frac{g_m R_S}{1 + g_m R_S} \Rightarrow 0.90 = \frac{g_m(10)}{1 + g_m(10)}$$

$$0.90 = 10(1 - 0.90)g_m \Rightarrow g_m = 0.90 \text{ mA/V}$$

$$R_o = \frac{1}{g_m} \parallel R_S = \frac{1}{0.90} \parallel 10 \Rightarrow R_o = 1 \text{ k}\Omega$$

With  $R_L$  :

$$A_v = \frac{g_m(R_S \parallel R_L)}{1 + g_m(R_S \parallel R_L)} = \frac{(0.90)(10 \parallel 2)}{1 + (0.90)(10 \parallel 2)}$$

$$\Rightarrow A_v = 0.60$$

6.29

$$R_o = \frac{1}{g_m} \parallel R_S$$

Output resistance determined primarily by  $g_m$

Set  $\frac{1}{g_m} = 0.2 \text{ k}\Omega \Rightarrow g_m = 5 \text{ mA/V}$

$$g_m = 2\sqrt{K_n I_{DQ}}$$

$$\Rightarrow 5 = 2\sqrt{(4)I_{DQ}} \Rightarrow I_{DQ} = 1.56 \text{ mA}$$

$$I_{DQ} = K_n(V_{GS} - V_{TN})^2$$

$$1.56 = 4(V_{GS} + 2)^2$$

$$V_{GS} = -1.38 \text{ V}, \quad V_S = -V_{GS} = 1.38 \text{ V}$$

$$R_S = \frac{1.38 - (-5)}{1.56} \Rightarrow R_S = 4.09 \text{ k}\Omega$$

$$A_v = \frac{g_m(R_S \parallel R_L)}{1 + g_m(R_S \parallel R_L)} = \frac{5(4.09 \parallel 2)}{1 + 5(4.09 \parallel 2)}$$

$$\Rightarrow A_v = 0.870$$

6.30

a.  $g_m = 2\sqrt{K_p I_{DQ}} = 2\sqrt{(5)(5)} = 10 \text{ mA/V}$

$$R_o = \frac{1}{g_m} = \frac{1}{10} \Rightarrow R_o = 100 \Omega$$

b. Open-circuit gain

$$A_v = \frac{g_m r_o}{1 + g_m r_o} \text{ But } r_o = \infty \text{ so } A_v = 1.0$$

With  $R_L$  :

$$A_v = \frac{g_m R_L}{1 + g_m R_L}$$

$$0.50 = \frac{10 R_L}{1 + 10 R_L} \Rightarrow 0.50 = 10(1 - 0.5)R_L$$

$$\Rightarrow R_L = 0.1 \text{ k}\Omega$$

6.31

$$|\Delta i_D| = I_{DQ} = \frac{-1}{R_S \parallel R_L} \cdot \Delta v_o$$

$$\Delta v_o = -I_{DQ} \cdot R_S \parallel R_L = -\frac{I_{DQ} \cdot R_S R_L}{R_S + R_L}$$

$$v_o(\min) = -\frac{I_{DQ} R_S}{1 + \frac{R_S}{R_L}}$$

$$A_v = \frac{g_m(R_S \parallel R_L)}{1 + g_m(R_S \parallel R_L)} = \frac{v_o}{v_i}$$

$$v_i = \frac{-I_{DQ}(R_S \parallel R_L)[1 + g_m(R_S \parallel R_L)]}{g_m(R_S \parallel R_L)}$$

$$v_i(\min) = -\frac{I_{DQ}}{g_m}[1 + g_m(R_S \parallel R_L)]$$

6.32

$$a. \quad V_{DSQ} = V_{DD} - I_{DQ} R_S$$

$$3 = 5 - (1.7)R_S \Rightarrow R_S = 1.18 \text{ k}\Omega$$

$$I_{DQ} = K_n(V_{GS} - V_{TN})^2$$

$$1.7 = (1)(V_{GS} - 1)^2 \Rightarrow V_{GS} = 2.30 \text{ V}$$

$$V_S = V_{DD} - V_{DSQ} = 5 - 3 = 2 \text{ V}$$

$$V_G = V_S + V_{GS} = 2 + 2.30 = 4.30 \text{ V}$$

$$V_G = \frac{1}{R_1} \cdot R_1 \cdot V_{DD} = \frac{1}{R_1}(300)(5) = 4.30$$

$$\Rightarrow R_1 = 349 \text{ k}\Omega$$

$$\frac{349 R_2}{349 + R_2} = 300 \Rightarrow R_2 = 2.14 \text{ M}\Omega$$

$$b. \quad g_m = 2\sqrt{K_n I_{DQ}} = 2\sqrt{(1)(1.7)} = 2.61 \text{ mA/V}$$

$$A_v = \frac{g_m R_S}{1 + g_m R_S} = \frac{2.61(1.18)}{1 + (2.61)(1.18)}$$

$$\Rightarrow A_v = 0.755$$

$$R_o = \frac{1}{g_m} \parallel R_S = \frac{1}{2.61} \parallel 1.18 = 0.383 \parallel 1.18$$

$$\Rightarrow R_o = 0.289 \text{ k}\Omega$$

6.33

$$a. \quad V_{GS} + I_{DQ} R_S = 5$$

$$I_{DQ} = \frac{5 - V_{GS}}{R_S} = K_n(V_{GS} - V_{TN})^2$$

$$5 - V_{GS} = (10)(3)(V_{GS}^2 - 2V_{GS} + 1)$$

$$30V_{GS}^2 - 59V_{GS} + 25 = 0$$

$$V_{GS} = \frac{59 \pm \sqrt{(59)^2 - 4(30)(25)}}{2(30)} \Rightarrow V_{GS} = 1.35 \text{ V}$$

$$I_{DQ} = (3)(1.35 - 1)^2 \Rightarrow I_{DQ} = 0.365 \text{ mA}$$

$$V_{DSQ} = 10 - (0.365)(5 + 10) \Rightarrow V_{DSQ} = 4.53 \text{ V}$$

$$b. \quad g_m = 2\sqrt{K_n I_{DQ}} = 2\sqrt{(3)(0.365)} \Rightarrow$$

$$g_m = 2.09 \text{ mA/V}$$

$$r_o = \frac{1}{\lambda I_{DQ}} = \frac{1}{(0)(0.365)} \Rightarrow r_o = \infty$$

$$c. \quad A_v = g_m(R_D \parallel R_L) = (2.09)(5 \parallel 4)$$

$$\Rightarrow A_v = 4.64$$

6.34

$$a. \quad I_{DQ} = K_p(V_{SG} + V_{TP})^2$$

$$0.75 = (0.5)(V_{SG} - 1)^2 \Rightarrow V_{SG} = 2.22 \text{ V}$$

$$5 = I_{DQ} R_S + V_{SG} \Rightarrow R_S = \frac{5 - 2.22}{0.75}$$

$$\Rightarrow R_S = 3.71 \text{ k}\Omega$$

$$V_{SDQ} = 10 - I_{DQ}(R_S + R_D)$$

$$6 = 10 - (0.75)(3.71 + R_D) \Rightarrow R_D = 1.62 \text{ k}\Omega$$

$$b. \quad R_i = \frac{1}{g_m}$$

$$g_m = 2\sqrt{K_p I_{DQ}} = 2\sqrt{(0.5)(0.75)} = 1.22 \text{ mA/V}$$

$$R_i = \frac{1}{1.22} \Rightarrow R_i = 0.816 \text{ k}\Omega$$

$$R_o = R_D \Rightarrow R_o = 1.62 \text{ k}\Omega$$

$$c. \quad i_o = \left( \frac{R_D}{R_D + R_L} \right) \left( \frac{R_S}{R_S + [1/g_m]} \right) \cdot i_i$$

$$i_o = \left( \frac{1.62}{1.62 + 2} \right) \left( \frac{3.71}{3.71 + 0.816} \right) i_i$$

$$i_o = 0.367 i_i \Rightarrow i_o = 1.84 \sin \omega t \text{ (}\mu\text{A)}$$

$$v_o = i_o R_L = (1.84)(2) \sin \omega t$$

$$\Rightarrow v_o = 3.68 \sin \omega t \text{ (mV)}$$

6.35

$$a. \quad I_{DQ} = K_n(V_{GS} - V_{TN})^2$$

$$5 = 4(V_{GS} - 2)^2 \Rightarrow V_{GS} = 3.12 \text{ V}$$

$$V^+ = I_{DQ} R_D + V_{DSQ} - V_{GS}$$

$$10 = (5)R_D + 12 - 3.12 \Rightarrow R_D = 0.224 \text{ k}\Omega$$

$$b. \quad g_m = 2\sqrt{K_n I_{DQ}} = 2\sqrt{(4)(5)} \Rightarrow g_m = 8.94 \text{ mA/V}$$

$$R_i = \frac{1}{g_m} = \frac{1}{8.94} \Rightarrow R_i = 0.112 \text{ k}\Omega$$

$$c. \quad A_v = g_m(R_D \parallel R_L) = (8.94)(0.224 \parallel 2)$$

$$\Rightarrow A_v = 1.80$$

6.36

$$a. \quad I_{DQ} = K_p (V_{SG} + V_{TP})^2$$

$$3 = 2(V_{SG} - 2)^2 \Rightarrow V_{SG} = 3.22 \text{ V}$$

$$V^+ = I_{DQ} R_S + V_{SG}$$

$$R_S = \frac{10 - 3.22}{3} \Rightarrow R_S = 2.26 \text{ k}\Omega$$

$$V_{SDQ} = 20 - I_{DQ}(R_S + R_D)$$

$$10 = 20 - (3)(2.26 + R_D) \Rightarrow R_D = 1.07 \text{ k}\Omega$$

$$b. \quad A_v = g_m (R_D \parallel R_L)$$

$$g_m = 2\sqrt{K_p I_{DQ}} = 2\sqrt{(2)(3)} = 4.90 \text{ mA/V}$$

$$A_v = (4.90)(1.07 \parallel 10) \Rightarrow A_v = 4.74$$

6.37

$$a. \quad |A_v| = \sqrt{\frac{(W/L)_D}{(W/L)_L}} = 5$$

$$\Rightarrow (W/L)_D = 25(0.5) \Rightarrow (W/L)_D = 12.5$$

$$K_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_D = (30)(12.5) = 375 \mu\text{A/V}^2$$

$$K_L = (30)(0.5) = 15 \mu\text{A/V}^2$$


Transition point:

$$V_{GSD} - V_{TND} = (V_{DD} - V_{TNL}) - \sqrt{\frac{K_D}{K_L}} (V_{GSD} - V_{TND})$$

$$V_{GSD} - 2 = (10 - 2) - \sqrt{\frac{375}{15}} (V_{GSD} - 2)$$

$$V_{GSD}(1 + 5) = (10 - 2) + 2 + 5(2)$$
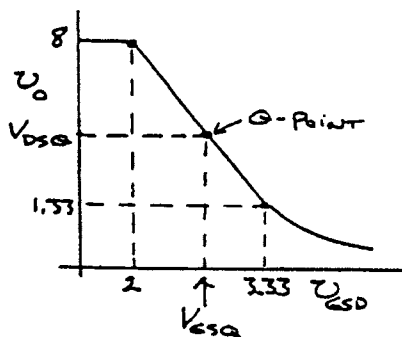
$$V_{GSD} = 3.33 \text{ V and } V_{DSQ} = 1.33 \text{ V}$$



$$V_{GSQ} = \frac{3.33 - 2}{2} + 2 \Rightarrow V_{GSQ} = 2.67 \text{ V}$$

$$b. \quad I_{DQ} = K_D (V_{GSQ} - V_{TND})^2$$

$$I_{DQ} = 0.375(2.67 - 2)^2 \Rightarrow I_{DQ} = 0.167 \text{ mA}$$

$$V_{DSQ} = \frac{8 - 1.33}{2} + 1.33 \Rightarrow V_{DSQ} = 4.67 \text{ V}$$

6.38

(a) Transition point: Load:

$$v_{OB} = V_{DD} - |V_{TNL}| = 10 - 2 = 8 \text{ V}$$

Driver:

$$K_D [(v_{OA})^2 (1 + \lambda_D v_{OA})] \\ = K_L [(-V_{TNL})^2 (1 + \lambda_L (V_{DD} - v_{OA}))]$$

$$0.5 [v_{OA}^2 + (0.02)v_{OA}^3] \\ = 0.1 [(4)(1 + 0.02(10 - v_{OA}))]$$

We have

$$0.01v_{OA}^3 + 0.5v_{OA}^2 + 0.008v_{OA} - 0.48 = 0$$

 Therefore  $v_{OA} = 0.963 \text{ V}$ 

Now

$$v_{OQ} = \frac{8 - 0.963}{2} + 0.963 = 4.48 \text{ V} = V_{DSQ}$$

Then

$$K_D [(V_{GSD} - V_{TND})^2 (1 + \lambda_D v_{OQ})] \\ = K_L [(-V_{TNL})^2 (1 + \lambda_L (V_{DD} - v_{OQ}))]$$

$$0.5 [(V_{GSD} - 1.2)^2 (1 + (0.02)(4.48))] \\ = 0.1 [(4)(1 + 0.02(10 - 4.48))]$$

 which yields  $V_{GSD} = 2.103 \text{ V}$ 

$$b. \quad I_{DQ} = K_D [(V_{GSD} - V_{TND})^2 (1 + \lambda_D v_{OQ})]$$

$$I_{DQ} = 0.5 [(2.103 - 1.2)^2 (1 + (0.02)(4.48))]$$

 So  $I_{DQ} = 0.444 \text{ mA}$ 

$$c. \quad r_{oD} = r_{oL} = \frac{1}{\lambda I_{DQ}} = \frac{1}{(0.02)(0.444)} = 113 \text{ k}\Omega$$

$$g_{mD} = 2K_D (V_{GSD} - V_{TND}) = 2(0.5)(2.103 - 1.2) \Rightarrow \\ g_{mD} = 0.903 \text{ mA/V}$$

Then

$$A_v = -g_{mD} (r_{oD} \parallel r_{oL}) = -(0.903)(113 \parallel 113)$$

 or  $A_v = -51.0$

6.39

$$\begin{aligned}
 I_D &= K_n(V_{GS} - V_{TN})^2, \quad V_{DS} = V_{GS} \\
 I_D &= 0 \quad \text{when } V_{DS} = 1.5 \text{ V} \Rightarrow V_{TN} = 1.5 \text{ V} \\
 0.8 &= K_n(3 - 1.5)^2 \Rightarrow K_n = 0.356 \text{ mA/V}^2 \\
 g_m &= \frac{dI_D}{dV_{DS}} = \frac{1}{R_n} = 2K_n(V_{DS} - V_{TN}) \\
 &= 2(0.356)(3 - 1.5) \\
 \Rightarrow R_o &= \underline{0.936 \text{ k}\Omega}
 \end{aligned}$$

6.40

a.

$$\begin{aligned}
 I_{DQ} &= K_{nD}(V_{GS} - V_{TND})^2 = (0.5)(0 - (-1))^2 \\
 I_{DQ} &= 0.5 \text{ mA} \\
 I_{DQ} &= K_{nL}(V_{GSL} - V_{TNL})^2 = K_{nL}(V_{DD} - V_o - V_{TNL})^2 \\
 0.5 &= 0.030(10 - V_o - 1)^2 \\
 \sqrt{\frac{0.5}{0.030}} &= 9 - V_o \Rightarrow \underline{V_o = 4.92 \text{ V}}
 \end{aligned}$$

b.  $I_{DD} = I_{DL}$

$$\begin{aligned}
 K_{nD}(V_i - V_{TND})^2 &= K_{nL}(V_{DD} - V_o - V_{TNL})^2 \\
 \sqrt{\frac{K_{nD}}{K_{nL}}}(V_i - V_{TND}) &= V_{DD} - V_o - V_{TNL} \\
 V_o &= V_{DD} - V_{TNL} - \sqrt{\frac{K_{nD}}{K_{nL}}}(V_i - V_{TND}) \\
 A_v &= \frac{dV_o}{dV_i} = -\sqrt{\frac{K_{nD}}{K_{nL}}} = -\sqrt{\frac{(W/L)_D}{(W/L)_L}} \\
 A_v &= -\sqrt{\frac{500}{30}} \Rightarrow \underline{A_v = -4.08}
 \end{aligned}$$

6.41

$$\begin{aligned}
 \text{(a)} \quad I_{DQ} &= K_L(V_{GSL} - V_{TNL})^2 = K_L(V_{DSL} - V_{TNL})^2 \\
 I_D &= (0.1)(4 - 1)^2 = 0.9 \text{ mA} \\
 I_{DQ} &= K_D(V_{GSD} - V_{TND})^2 \\
 0.9 &= (1)(V_{GSD} - 1)^2 \Rightarrow V_{GSD} = 1.95 \text{ V} \\
 V_{GG} &= V_{GSD} + V_{DSL} = 1.95 + 4 \\
 \Rightarrow \underline{V_{GG} = 5.95 \text{ V}}
 \end{aligned}$$

b.  $I_{DD} = I_{DL}$

$$\begin{aligned}
 K_D(V_{GSD} - V_{TND})^2 &= K_L(V_{GSL} - V_{TNL})^2 \\
 \sqrt{\frac{K_D}{K_L}}(V_{GG} + V_i - V_o - V_{TND}) &= V_o - V_{TNL} \\
 V_o \left( 1 + \sqrt{\frac{K_D}{K_L}} \right) &= \sqrt{\frac{K_D}{K_L}}(V_{GG} + V_i - V_{TND}) + V_{TNL} \\
 A_v &= \frac{dV_o}{dV_i} = \frac{\sqrt{K_D/K_L}}{1 + \sqrt{K_D/K_L}} \Rightarrow \underline{A_v = \frac{1}{1 + \sqrt{K_L/K_D}}}
 \end{aligned}$$

(c) From Problem 6.39:

$$\begin{aligned}
 R_{LD} &= \frac{1}{2K_L(V_{DSL} - V_{TNL})} \\
 &= \frac{1}{2(0.1)(4 - 1)} = 1.67 \text{ k}\Omega \\
 g_m &= 2\sqrt{K_D I_{DQ}} = 2\sqrt{(1)(0.9)} = 1.90 \text{ mA/V} \\
 A_v &= \frac{g_m(R_{LD} \parallel R_L)}{1 + g_m(R_{LD} \parallel R_L)} = \frac{(1.90)(1.67 \parallel 4)}{1 + (1.90)(1.67 \parallel 4)} \\
 \Rightarrow \underline{A_v = 0.691}
 \end{aligned}$$

6.42

a. From Problem 6-41:

$$\begin{aligned}
 A_v &= \frac{g_m(R_{LD} \parallel R_L)}{1 + g_m(R_{LD} \parallel R_L)} = \frac{(1.90)(1.67 \parallel 10)}{1 + (1.90)(1.67 \parallel 10)} \\
 \underline{A_v = 0.731}
 \end{aligned}$$

b.  $R_o = \frac{1}{g_m} \parallel R_{LD} = \frac{1}{1.90} \parallel 1.67 = 0.526 \parallel 1.67$

$$\underline{R_o = 0.40 \text{ k}\Omega}$$

6.43

a.  $I_{D1} = K_1(V_{GS1} - V_{TN1})^2$

$$0.4 = 0.1(V_{GS1} - 2)^2 \Rightarrow V_{GS1} = 4 \text{ V}$$

$$V_{S1} = I_{D1}R_{S1} = (0.4)(4) = 1.6 \text{ V}$$

$$V_{G1} = V_{S1} + V_{GS1} = 1.6 + 4 = 5.6 \text{ V}$$

$$V_{G1} = \left( \frac{R_2}{R_1 + R_2} \right) V_{DD} = \frac{1}{R_1} \cdot R_{in} \cdot V_{DD}$$

$$5.6 = \frac{1}{R_1}(200)(10) \Rightarrow \underline{R_1 = 357 \text{ k}\Omega}$$

$$\frac{357R_2}{357 + R_2} = 200 \Rightarrow \underline{R_2 = 455 \text{ k}\Omega}$$

$$V_{DS1} = V_{DD} - I_{D1}(R_{S1} + R_{D1})$$

$$4 = 10 - (0.4)(4 + R_{D1}) \Rightarrow \underline{R_{D1} = 11 \text{ k}\Omega}$$

$$V_{D1} = 10 - (0.4)(11) = 5.6 \text{ V}$$

$$I_{D2} = K_2(V_{SG2} + V_{TP2})^2$$


$$2 = 1(V_{SG2} - 2)^2 \Rightarrow V_{SG2} = 3.41 \text{ V}$$

$$V_{S2} = V_{D1} + V_{SG2} = 5.6 + 3.41 = 9.01$$

$$R_{S2} = \frac{10 - 9.01}{2} \Rightarrow \underline{R_{S2} = 0.495 \text{ k}\Omega}$$

$$V_{SD2} = V_{DD} - I_{D2}(R_{S2} + R_{D2})$$
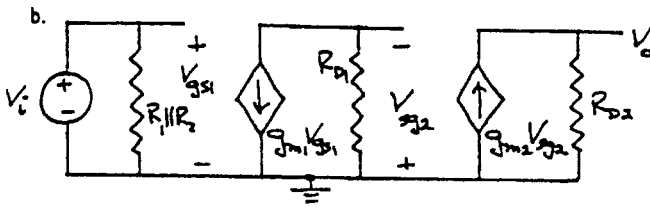
$$5 = 10 - (2)(0.495 + R_{D2}) \Rightarrow \underline{R_{D2} = 2.01 \text{ k}\Omega}$$



$$V_o = g_{m2} V_{s2} R_{D2} = (g_{m2} R_{D2})(g_{m1} V_{s1} R_{D1})$$

$$V_{s1} = V_i$$


$$A_v = \frac{V_o}{V_i} = g_{m1} g_{m2} R_{D1} R_{D2}$$

$$g_{m1} = 2\sqrt{K_1 I_{D1}} = 2\sqrt{(0.1)(0.4)} = 0.4 \text{ mA/V}$$

$$g_{m2} = 2\sqrt{K_2 I_{D2}} = 2\sqrt{(1)(2)} = 2.83 \text{ mA/V}$$

$$A_v = (0.4)(2.83)(11)(2.01) \Rightarrow A_v = 25.0$$

c.

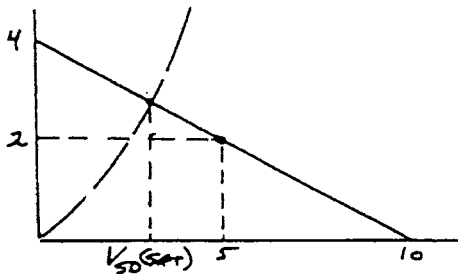

$$V_{SD}(\text{sat}) = V_{SG} + V_{Th}$$

$$= V_{DD} - I_{D2}(R_{D2} + R_{S2})$$

$$= V_{DD} - k_{p2}(R_{D2} + R_{S2})V_{SD}^2(\text{sat})$$

So

$$(1)(2.01 + 0.495)V_{SD}^2(\text{sat}) + V_{SD}(\text{sat}) - V_{DD} = 0$$

$$2.505V_{SD}^2(\text{sat}) + V_{SD}(\text{sat}) - 10 = 0$$

$$V_{SD}(\text{sat}) = \frac{-1 \pm \sqrt{1 + 4(2.505)(10)}}{2(2.505)}$$


$$V_{SD}(\text{sat}) = 1.81 \text{ V}$$

$$5 - 1.81 = 3.19$$

$$\Rightarrow \text{Max. output swing} = 6.38 \text{ V peak-to-peak}$$

6.44

a.

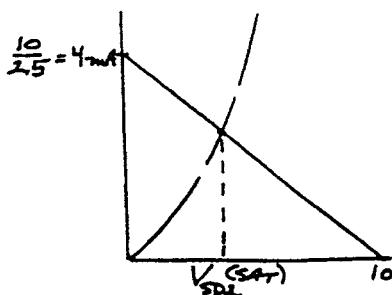

$$V_{SD2}(\text{sat}) = V_{DD} - I_{D2}(R_{D2} + R_{S2})$$

$$= V_{DD} - K_{p2}(R_{D2} + R_{S2})V_{SD2}^2(\text{sat})$$

$$(1)(2 + 0.5)V_{SD2}^2(\text{sat}) + V_{SD2}(\text{sat}) - 10 = 0$$

$$2.5V_{SD2}^2(\text{sat}) + V_{SD2}(\text{sat}) - 10 = 0$$

$$V_{SD2}(\text{sat}) = \frac{-1 \pm \sqrt{1 + 4(2.5)(10)}}{2(2.5)} = 1.81 \text{ V}$$

$$V_{SDQ2} = \frac{10 - 1.81}{2} + 1.81 \Rightarrow V_{SDQ2} = 5.91 \text{ V}$$

$$V_{SDQ2} = V_{DD} - I_{DQ2}(R_{D2} + R_{S2})$$

$$5.91 = 10 - I_{DQ2}(2 + 0.5) \Rightarrow I_{DQ2} = 1.64 \text{ mA}$$

$$V_{S2} = 10 - (1.64)(0.5) = 9.18 \text{ V}$$

$$I_{DQ2} = K_{p2}(V_{SG2} + V_{TP2})^2$$

$$1.64 = (1)(V_{SG2} - 2)^2 \Rightarrow V_{SG2} = 3.28 \text{ V}$$

$$V_{D1} = V_{S2} - V_{SG2} = 9.18 - 3.28 = 5.90 \text{ V}$$

$$R_{D1} = \frac{10 - 5.90}{0.4} \Rightarrow R_{D1} = 10.25 \text{ k}\Omega$$

$$I_{DQ1} = K_{n1}(V_{GS1} - V_{TN1})^2$$

$$0.4 = (0.1)(V_{GS1} - 2)^2 \Rightarrow V_{GS1} = 4 \text{ V}$$

$$V_{S1} = (0.4)(1) = 0.4 \text{ V}$$

$$V_{G1} = V_{S1} + V_{GS1} = 0.4 + 4 = 4.4 \text{ V}$$

$$V_{G1} = \left(\frac{R_2}{R_1 + R_2}\right)V_{DD} = \frac{1}{R_1} \cdot R_{in} \cdot V_{DD}$$

$$4.4 = \frac{1}{R_1} \cdot (200)(10) \Rightarrow R_1 = 455 \text{ k}\Omega$$

$$\frac{455R_2}{455 + R_2} = 200 \Rightarrow R_2 = 357 \text{ k}\Omega$$

b.  $I_{DQ2} = 1.64 \text{ mA}$

$$V_{SDQ2} = 10 - (1.64)(2 + 0.5) \Rightarrow V_{SDQ2} = 5.90 \text{ V}$$

$$V_{DSQ1} = 10 - (0.4)(10.25 + 1) \Rightarrow V_{DSQ1} = 5.50 \text{ V}$$

(c)  $g_{m1} = 2\sqrt{K_{n1}I_{DQ1}} = 2\sqrt{(0.1)(0.4)} = 0.4 \text{ mA/V}$

$$g_{m2} = 2\sqrt{K_{p2}I_{DQ2}} = 2\sqrt{(1)(1.64)} = 2.56 \text{ mA/V}$$

$$A_v = g_{m1}g_{m2}R_{D1}R_{D2} = (0.4)(2.56)(10.25)(2) \Rightarrow A_v = 21.0$$

6.45

a.  $V_{DSQ2} = 7 = V_{DD} - I_{DQ2}R_{S2} = 10 - I_{DQ2}(6)$

$$I_{DQ2} = 0.5 \text{ mA}$$

$$I_{DQ2} = K_2(V_{GS2} - V_{TN2})^2$$

$$0.5 = (0.2)(V_{GS2} - 0.8)^2 \Rightarrow V_{GS2} = 2.38 \text{ V}$$

$$V_{S1} = V_{S2} + V_{GS2} = 3 + 2.38 = 5.38$$

$$I_{DQ1} = \frac{V_{S1}}{R_{S1}} = \frac{5.38}{20} = 0.269 \text{ mA}$$

$$I_{DQ1} = K_1(V_{GS1} - V_{TN1})^2$$

$$0.269 = (0.2)(V_{GS1} - 0.8)^2 \Rightarrow V_{GS1} = 1.96 \text{ V}$$

$$V_{G1} = V_{S1} + V_{GS1} = 5.38 + 1.96 = 7.34 \text{ V}$$

$$V_{G1} = \left( \frac{R_2}{R_1 + R_2} \right) V_{DD} = \frac{1}{R_1} \cdot R_{in} \cdot V_{DD}$$

$$7.34 = \frac{1}{R_1} (400)(10) \Rightarrow R_1 = 545 \text{ k}\Omega$$

$$\frac{545 R_2}{545 + R_2} = 400 \Rightarrow R_2 = 1.50 \text{ M}\Omega$$

b.  $I_{DQ1} = 0.269 \text{ mA}$ ,  $I_{DQ2} = 0.5 \text{ mA}$

$$V_{DSQ1} = 10 - (0.269)(20) \Rightarrow V_{DSQ1} = 4.62 \text{ V}$$

c.  $A_v = \frac{g_{m1} R_{S1}}{1 + g_{m1} R_{S1}} \cdot \frac{g_{m2} R_{S2}}{1 + g_{m2} R_{S2}}$


$$g_{m1} = 2\sqrt{K_1 I_{DQ1}} = 2\sqrt{(0.2)(0.269)} = 0.464 \text{ mA/V}$$

$$g_{m2} = 2\sqrt{K_2 I_{DQ2}} = 2\sqrt{(0.2)(0.5)} = 0.632 \text{ mA/V}$$

$$A_v = \frac{(0.464)(20)}{1 + (0.464)(20)} \cdot \frac{(0.632)(6)}{1 + (0.632)(6)}$$

$$= (0.9027)(0.7913)$$

$$= A_v = 0.714$$

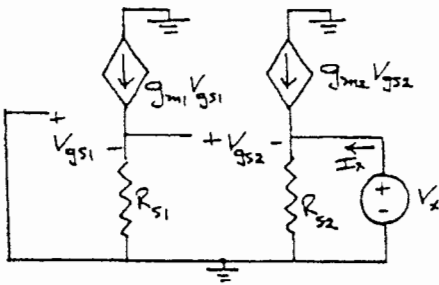

$$R_0 = \frac{1}{g_{m2}} \parallel R_{S2} = \frac{1}{0.632} \parallel 6 = 1.582 \parallel 6$$

$$\Rightarrow R_0 = 1.25 \text{ k}\Omega$$

6.46

(a)  $I_{DQ1} = \frac{10 - V_{GS1}}{R_{S2}} = K_{n1} (V_{GS1} - V_{TN1})^2$

$$10 - V_{GS1} = (4)(10)(V_{GS1}^2 - 4V_{GS1} + 4)$$

$$40V_{GS1}^2 - 159V_{GS1} + 150 = 0$$

$$V_{GS1} = \frac{159 \pm \sqrt{(159)^2 - 4(40)(150)}}{2(40)}$$

$$\Rightarrow V_{GS1} = 2.435 \text{ V}$$

$$I_{DQ1} = (4)(2.435 - 2)^2 \Rightarrow I_{DQ1} = 0.757 \text{ mA}$$


$$V_{DSQ1} = 20 - (0.757)(10) \Rightarrow V_{DSQ1} = 12.4 \text{ V}$$

Also  $I_{DQ2} = 0.757 \text{ mA}$

$$V_{DSQ2} = 20 - (0.757)(10 + 5) \Rightarrow V_{DSQ2} = 8.65 \text{ V}$$

(b)  $g_{m1} = g_{m2} = 2\sqrt{K I_{DQ}} = 2\sqrt{(4)(0.757)} \Rightarrow$   
 $g_{m1} = g_{m2} = 3.48 \text{ mA/V}$

c.

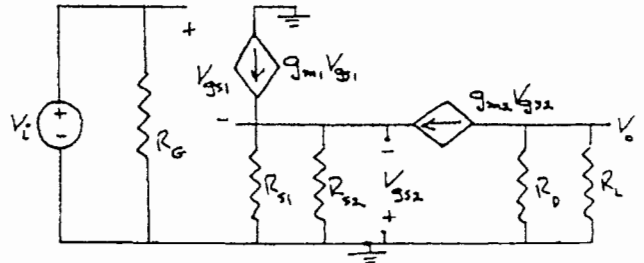

$$V_0 = -(g_{m2} V_{gs2})(R_D \parallel R_L)$$

$$V_{gs2} = (-g_{m1} V_{gs1} - g_{m2} V_{gs2})(R_{S1} \parallel R_{S2})$$

$$V_i = V_{gs1} - V_{gs2} \Rightarrow V_{gs1} = V_i + V_{gs2}$$

$$V_{gs2} + g_{m2} V_{gs2}(R_{S1} \parallel R_{S2})$$

$$= -g_{m1}(V_i + V_{gs2})(R_{S1} \parallel R_{S2})$$

$$V_{gs2} + g_{m2} V_{gs2}(R_{S1} \parallel R_{S2}) + g_{m1} V_{gs2}(R_{S1} \parallel R_{S2})$$

$$= -g_{m1} V_i (R_{S1} \parallel R_{S2})$$

$$V_{gs2} = \frac{-g_{m1} V_i (R_{S1} \parallel R_{S2})}{1 + g_{m2}(R_{S1} \parallel R_{S2}) + g_{m1}(R_{S1} \parallel R_{S2})}$$

$$A_v = \frac{V_0}{V_i} = \frac{g_{m1} g_{m2} (R_{S1} \parallel R_{S2})(R_D \parallel R_L)}{1 + (g_{m1} + g_{m2})(R_{S1} \parallel R_{S2})}$$

$$A_v = \frac{(3.48)^2 (10 \parallel 10)(5 \parallel 2)}{1 + (3.48 + 3.48)(10 \parallel 10)}$$

$$\Rightarrow A_v = 2.42$$

6.47

a.  $I_{DQ} = 3 \text{ mA}$

$$V_{S1} = I_{DQ} R_S - 5 = (3)(1.2) - 5 = -1.4 \text{ V}$$

$$I_{DQ} = K_1 (V_{GS} - V_{TN})^2$$

$$3 = 2(V_{GS} - 1)^2 \Rightarrow V_{GS} = 2.22 \text{ V}$$

$$V_{G1} = V_{GS} + V_{S1} = 2.22 - 1.4 = 0.82 \text{ V}$$

$$V_{G1} = \left( \frac{R_3}{R_1 + R_2 + R_3} \right) (5) \Rightarrow 0.82 = \left( \frac{R_3}{500} \right) (5)$$

$$\Rightarrow R_3 = 82 \text{ k}\Omega$$

$$V_{D1} = V_{S1} + V_{DSQ1} = -1.4 + 2.5 = 1.1 \text{ V}$$

$$V_{G2} = V_{D1} + V_{GS} = 1.1 + 2.22 = 3.32 \text{ V}$$

$$V_{G2} = \left( \frac{R_2 + R_3}{R_1 + R_2 + R_3} \right) (5)$$

$$\Rightarrow 3.32 = \left( \frac{R_2 + R_3}{500} \right) (5)$$

$$R_2 + R_3 = 332 \Rightarrow R_2 = 250 \text{ k}\Omega$$

$$R_1 = 500 - 250 - 82 \Rightarrow \underline{R_1 = 168 \text{ k}\Omega}$$

$$V_{D2} = V_{D1} + V_{DSQ2} = 1.1 + 2.5 = 3.6 \text{ V}$$

$$R_D = \frac{5 - 3.6}{3} \Rightarrow \underline{R_D = 0.467 \text{ k}\Omega}$$

$$\text{b. } A_v = -g_{m1} R_D$$

$$g_{m1} = 2\sqrt{K_n I_{DQ}} = 2\sqrt{(2)(3)} = 4.90 \text{ mA/V}$$

$$A_v = -(4.90)(0.467) \Rightarrow \underline{A_v = -2.29}$$

6.48

$$\text{a. } V_{S1} = I_{DQ} R_S - 10 = (5)(2) - 10 \Rightarrow V_{S1} = 0$$

$$I_{DQ} = K_1 (V_{GS1} - V_{TN})^2$$

$$5 = 4(V_{GS1} - 1.5)^2 \Rightarrow V_{GS1} = 2.618 \text{ V}$$

$$V_{G1} = V_{GS1} + V_{S1} = 2.618 \text{ V} = I R_3 = (0.1) R_3$$

$$\Rightarrow \underline{R_3 = 26.2 \text{ k}\Omega}$$

$$V_{D1} = V_{S1} + V_{DSQ1} = 0 + 3.5 = 3.5 \text{ V}$$

$$V_{G2} = V_{D1} + V_{GS} = 3.5 + 2.62 = 6.12 \text{ V}$$

$$= (0.1)(R_2 + R_3)$$

$$R_2 + R_3 = 61.2 \text{ k}\Omega \Rightarrow \underline{R_2 = 35 \text{ k}\Omega}$$

$$V_{D2} = V_{D1} + V_{DSQ2} = 3.5 + 3.5 = 7.0 \text{ V}$$

$$R_D = \frac{10 - 7}{5} \Rightarrow \underline{R_D = 0.6 \text{ k}\Omega}$$

$$R_1 = \frac{10 - 6.12}{0.1} \Rightarrow \underline{R_1 = 38.8 \text{ k}\Omega}$$

$$\text{b. } A_v = -g_{m1} R_D$$

$$g_{m1} = 2\sqrt{K_n I_{DQ}} = 2\sqrt{(4)(5)} = 8.94 \text{ mA/V}$$

$$A_v = -(8.94)(0.6) \Rightarrow \underline{A_v = -5.36}$$

6.49

$$\text{a. } I_{DQ} = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$4 = 6 \left(1 - \frac{V_{GS}}{-3}\right)^2$$

$$V_{GS} = (-3) \left[1 - \sqrt{\frac{4}{6}}\right] \Rightarrow \underline{V_{GS} = -0.551 \text{ V}}$$

$$V_{DSQ} = V_{DD} - I_{DQ} R_D$$

$$6 = 10 - (4) R_D \Rightarrow \underline{R_D = 1 \text{ k}\Omega}$$

$$\text{b. } g_m = \frac{2I_{DSS}}{(-V_P)} \left(1 - \frac{V_{GS}}{V_P}\right) = \frac{2(6)}{3} \left(1 - \frac{-0.551}{-3}\right)$$

$$\Rightarrow \underline{g_m = 3.27 \text{ mA/V}}$$

$$r_o = \frac{1}{\lambda I_{DQ}} = \frac{1}{(0.01)(4)} \Rightarrow \underline{r_o = 25 \text{ k}\Omega}$$

$$\text{c. } A_v = -g_m (r_o \parallel R_D) = -(3.27)(25 \parallel 1)$$

$$\Rightarrow \underline{A_v = -3.14}$$

6.50

$$V_{GS} + I_{DQ}(R_{S1} + R_{S2}) = 0$$

$$I_{DQ} = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$V_{GS} + I_{DSS}(R_{S1} + R_{S2}) \left(1 - \frac{V_{GS}}{V_P}\right)^2 = 0$$

$$V_{GS} + (2)(0.1 + 0.25) \left(1 - \frac{V_{GS}}{V_P}\right)^2 = 0$$

$$V_{GS} + 0.7 \left(1 - \frac{2V_{GS}}{(-2)} + \frac{V_{GS}^2}{(-2)^2}\right) = 0$$

$$0.175 V_{GS}^2 + 1.7 V_{GS} + 0.7 = 0$$

$$V_{GS} = \frac{-1.7 \pm \sqrt{(1.7)^2 - 4(0.175)(0.7)}}{2(0.175)}$$

$$\Rightarrow V_{GS} = -0.431 \text{ V}$$

$$g_m = \frac{2I_{DSS}}{-V_P} \left(1 - \frac{V_{GS}}{V_P}\right) = \frac{2(2)}{2} \left(1 - \frac{-0.431}{-2}\right)$$

$$\Rightarrow \underline{g_m = 1.57 \text{ mA/V}}$$

$$A_v = \frac{-g_m (R_D \parallel R_L)}{1 + g_m R_{S1}} = \frac{-(1.57)(8 \parallel 4)}{1 + (1.57)(0.1)}$$

$$\Rightarrow \underline{A_v = -3.62}$$

$$A_i = \frac{i_o}{i_i} = \frac{(v_o/R_L)}{(v_i/R_G)} = \frac{v_o}{v_i} \cdot \frac{R_G}{R_L} = (-3.62) \left(\frac{50}{4}\right)$$

$$\Rightarrow \underline{A_i = -45.3}$$

6.51

$$I_{DQ} = \frac{I_{DSS}}{2} = 4 \text{ mA}$$

$$V_{DSQ} = \frac{V_{DD}}{2} = 10 \text{ V}$$

$$V_{DSQ} = V_{DD} - I_{DQ}(R_S + R_D)$$

$$10 = 20 - (4)(R_S + R_D) \Rightarrow R_S + R_D = 2.5 \text{ k}\Omega$$

$$V_S = 2 \text{ V} = I_{DQ} R_S = 4 R_S$$

$$\Rightarrow \underline{R_S = 0.5 \text{ k}\Omega}, \quad \underline{R_D = 2.0 \text{ k}\Omega}$$

$$I_{DQ} = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$4 = 8 \left(1 - \frac{V_{GS}}{(-4.2)}\right)^2 \Rightarrow V_{GS} = (-4.2) \left(1 - \sqrt{\frac{4}{8}}\right)$$

$$\Rightarrow \underline{V_{GS} = -1.23 \text{ V}}$$

$$V_G = V_S + V_{GS} = 2 - 1.23$$

$$V_G = 0.77 \text{ V} = \left(\frac{R_2}{R_1 + R_2}\right)(20) = \left(\frac{R_2}{100}\right)(20)$$

$$\Rightarrow \underline{R_2 = 3.85 \text{ k}\Omega}, \quad \underline{R_1 = 96.2 \text{ k}\Omega}$$

6.52

$$a. \quad I_{DQ} = \frac{I_{DSS}}{2} = 5 \text{ mA}$$

$$V_{DSQ} = \frac{V_{DD}}{2} = \frac{12}{2} = 6 \text{ V}$$

$$R_S = \frac{12 - 6}{5} \Rightarrow R_S = 1.2 \text{ k}\Omega$$

$$I_{DQ} = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$5 = 10 \left(1 - \frac{V_{GS}}{(-5)}\right)^2 \Rightarrow V_{GS} = (-5) \left(1 - \sqrt{\frac{5}{10}}\right)$$

$$\Rightarrow V_{GS} = -1.46 \text{ V}$$

$$V_G = V_S + V_{GS} = 6 - 1.46 = 4.54 \text{ V}$$

$$V_G = \left(\frac{R_2}{R_1 + R_2}\right) V_{DD} = \frac{1}{R_1} \cdot R_{in} \cdot V_{DD}$$

$$4.54 = \frac{1}{R_1} (100)(12) \Rightarrow R_1 = 264 \text{ k}\Omega$$

$$\frac{264 R_2}{264 + R_2} = 100 \Rightarrow R_2 = 161 \text{ k}\Omega$$

$$b. \quad g_m = \frac{2I_{DSS}}{(-V_P)} \left(1 - \frac{V_{GS}}{V_P}\right) = \frac{2(10)}{5} \left(1 - \frac{-1.46}{-5}\right)$$

$$\Rightarrow g_m = 2.83 \text{ mA/V}$$

$$r_o = \frac{1}{\lambda I_{DQ}} = \frac{1}{(0.01)(5)} = 20 \text{ k}\Omega$$

$$A_v = \frac{g_m(r_o \parallel R_S \parallel R_L)}{1 + g_m(r_o \parallel R_S \parallel R_L)}$$

$$A_v = \frac{(2.83)(20 \parallel 1.2 \parallel 0.5)}{1 + (2.83)(20 \parallel 1.2 \parallel 0.5)}$$

$$\Rightarrow A_v = 0.495$$

$$R_o = \frac{1}{g_m} \parallel R_S = \frac{1}{2.83} \parallel 1.2 = 0.353 \parallel 1.2$$

$$\Rightarrow R_o = 0.273 \text{ k}\Omega$$

6.53

$$a. \quad V_G = \left(\frac{R_2}{R_1 + R_2}\right) V_{DD} = \left(\frac{110}{110 + 90}\right) (10) = 5.5 \text{ V}$$

$$I_{DQ} = \frac{10 - (V_G - V_{GS})}{R_S} = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$10 - 5.5 + V_{GS} = (2)(5) \left(1 - \frac{V_{GS}}{1.75}\right)^2$$

$$4.5 + V_{GS} = 10 \left(1 - 1.143 V_{GS} + 0.3265 V_{GS}^2\right)$$

$$3.265 V_{GS}^2 - 12.43 V_{GS} + 5.5 = 0$$

$$V_{GS} = \frac{12.43 \pm \sqrt{(12.43)^2 - 4(3.265)(5.5)}}{2(3.265)}$$

$$\Rightarrow V_{GS} = 0.511 \text{ V}$$

$$I_{DQ} = (2) \left(1 - \frac{0.511}{1.75}\right)^2 \Rightarrow I_{DQ} = 1.42 \text{ mA}$$

$$V_{SDQ} = 10 - (1.42)(5) \Rightarrow V_{SDQ} = 2.9 \text{ V}$$

$$b. \quad g_m = \frac{2I_{DSS}}{V_P} \left(1 - \frac{V_{GS}}{V_P}\right) = \frac{2(2)}{1.75} \left(1 - \frac{0.511}{1.75}\right)$$

$$\Rightarrow g_m = 1.62 \text{ mA/V}$$

$$A_v = \frac{g_m(R_S \parallel R_L)}{1 + g_m(R_S \parallel R_L)} = \frac{(1.62)(5 \parallel 10)}{1 + (1.62)(5 \parallel 10)}$$


$$\Rightarrow A_v = 0.844$$

$$A_i = \frac{i_o}{i_i} = \frac{(v_o/R_L)}{(v_i/R_i)} = A_v \cdot \left(\frac{R_i}{R_L}\right)$$

$$R_i = R_1 \parallel R_2 = 90 \parallel 110 = 49.5 \text{ k}\Omega$$

$$A_i = (0.844) \left(\frac{49.5}{10}\right) \Rightarrow A_i = 4.18$$

c.

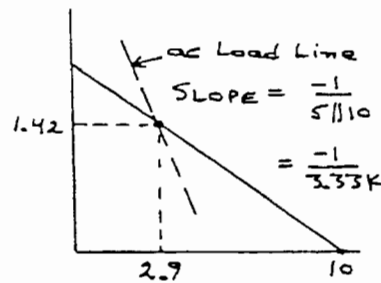

Maximum swing in output voltage

$$= 5.8 \text{ V peak-to-peak}$$

6.54

$$I_{DQ} = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$4 = 8 \left(1 - \frac{V_{GS}}{4}\right)^2 \Rightarrow V_{GS} = 4 \left(1 - \sqrt{\frac{4}{8}}\right)$$

$$\Rightarrow V_{GS} = 1.17 \text{ V}$$

$$V_{SDQ} = V_{DD} - I_{DQ}(R_S + R_D)$$

$$7.5 = 20 - 4(R_S + R_D) \Rightarrow R_S + R_D = 3.125 \text{ k}\Omega$$

$$g_m = \frac{2I_{DSS}}{V_P} \left(1 - \frac{V_{GS}}{V_P}\right) = \frac{2(8)}{4} \left(1 - \frac{1.17}{4}\right)$$

$$\Rightarrow g_m = 2.83 \text{ mA/V}$$

$$R_S = 3.125 - R_D$$

$$A_v = \frac{-g_m R_D}{1 + g_m R_S}$$

$$-3(1 + g_m R_S) = -g_m R_D$$

$$3[1 + (2.83)(3.125 - R_D)] = (2.83)R_D$$

$$9.844 - 2.83R_D = 0.7075R_D \Rightarrow \underline{R_D = 2.78 \text{ k}\Omega}$$

$$\underline{R_S = 0.345 \text{ k}\Omega}$$

$$V_S = 20 - (4)(0.345) \Rightarrow V_S = 18.6 \text{ V}$$

$$V_G = V_S - V_{GS} = 18.6 - 1.17 = 17.4 \text{ V}$$

$$V_G = \left( \frac{R_2}{R_1 + R_2} \right) V_{DD} = \left( \frac{R_2}{400} \right) (20)$$

$$\Rightarrow \underline{R_2 = 348 \text{ k}\Omega} \quad \underline{R_1 = 52 \text{ k}\Omega}$$

## Chapter 7

## Exercise Solutions

E7.1

$$a. \quad R_S = R_P = 4 \text{ k}\Omega$$

$$\omega = \frac{1}{r_S} = \frac{1}{(R_S + R_P)C_S}$$

$$C_S = \frac{1}{2\pi f(R_S + R_P)} = \frac{1}{2\pi(20)(4 + 4) \times 10^3}$$

$$C_S = 0.995 \text{ }\mu\text{F}$$

$$b. \quad |T(j\omega)| = \left( \frac{R_P}{R_S + R_P} \right) \frac{\omega r_S}{\sqrt{1 + \omega^2 r_S^2}}$$

$$r_S = (R_S + R_P)C_S = 7.96 \times 10^{-3}$$

$$\frac{R_P}{R_S + R_P} = \frac{4}{4 + 4} = 0.5$$

$$f = 40 \text{ Hz}$$

$$|T(j\omega)| = \frac{(0.5)(2\pi)(40)(7.96 \times 10^{-3})}{\sqrt{1 + [2\pi(40)(7.96 \times 10^{-3})]^2}}$$

$$|T(j\omega)| = 0.447$$

$$f = 80 \text{ Hz}$$

$$|T(j\omega)| = \frac{(0.5)(2\pi)(80)(7.96 \times 10^{-3})}{\sqrt{1 + [2\pi(80)(7.96 \times 10^{-3})]^2}}$$

$$|T(j\omega)| = 0.485$$

$$f = 200 \text{ Hz}$$

$$|T(j\omega)| = \frac{(0.5)(2\pi)(200)(7.96 \times 10^{-3})}{\sqrt{1 + [2\pi(200)(7.96 \times 10^{-3})]^2}}$$

$$|T(j\omega)| = 0.498$$

E7.2

$$\omega = \frac{1}{r_P} = \frac{1}{(R_S || R_P)C_P}$$

$$C_P = \frac{1}{2\pi f(R_S || R_P)}$$

$$= \frac{1}{2\pi(500 \times 10^3)(10 || 10) \times 10^3}$$

$$C_P = 63.7 \text{ pF}$$

E7.3

$$a. \quad V_O = -(g_m V_\pi) R_L$$

$$V_\pi = \frac{r_\pi}{r_\pi + \frac{1}{sC_C} + R_S} \times V_i$$

$$T(s) = \frac{V_O(s)}{V_i(s)} = \frac{-g_m r_\pi R_L}{r_\pi + R_S + (1/sC_C)} = \frac{-g_m r_\pi R_L (sC_C)}{1 + s(r_\pi + R_S)C_C}$$

$$g_m r_\pi = \beta$$

$$T(s) = \frac{-\beta R_L}{r_\pi + R_S} \times \left( \frac{s(r_\pi + R_S)C_C}{1 + s(r_\pi + R_S)C_C} \right)$$


$$b. \quad f_{3-dB} = \frac{1}{2\pi(r_\pi + R_S)C_C}$$

$$f_{3-dB} = \frac{1}{2\pi[2 \times 10^3 + 1 \times 10^3][10^{-6}]} \Rightarrow f_{3-dB} = 53.1 \text{ Hz}$$

$$|T(j\omega)|_{\max} = \frac{r_\pi g_m R_L}{r_\pi + R_S} = \frac{(2)(50)(4)}{2 + 1}$$

$$|T(j\omega)|_{\max} = 133$$

c.

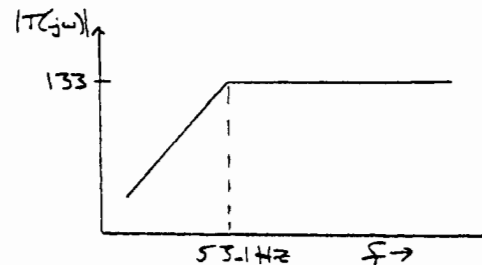

E7.4

$$a. \quad V_O = -g_m V_\pi \left( R_L || \frac{1}{sC_L} \right)$$

$$V_\pi = \left( \frac{r_\pi}{r_\pi + R_S} \right) \times V_i$$

$$T(s) = \frac{V_O(s)}{V_i(s)} = -g_m \frac{r_\pi}{r_\pi + R_S} \left( \frac{R_L \times \frac{1}{sC_L}}{R_L + \frac{1}{sC_L}} \right)$$

$$T(s) = \frac{-\beta R_L}{r_\pi + R_S} \times \left( \frac{1}{1 + sR_L C_L} \right)$$


$$b. \quad f_{3-dB} = \frac{1}{2\pi R_L C_L} = \frac{1}{2\pi(5 \times 10^3)(10 \times 10^{-12})}$$

$$\Rightarrow f_{3dB} = 3.18 \text{ MHz}$$

$$|T(j\omega)| = \frac{g_m r_\pi R_L}{r_\pi + R_S} = \frac{(75)(1.5)(5)}{1.5 + 0.5}$$

$$|T(j\omega)|_{\max} = 281$$

c.

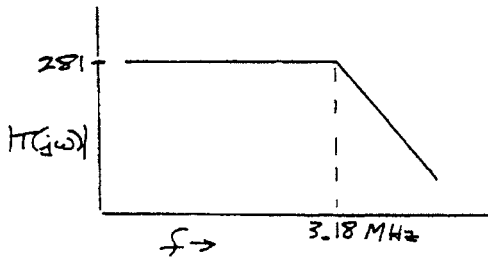

E7.5

$$a. \quad 20 \log_{10} \left( \frac{R_P}{R_P + R_S} \right) = -1$$

$$\Rightarrow \frac{R_P}{R_P + R_S} = 0.891 = \frac{R_P}{R_P + 1}$$

$$\Rightarrow (1 - 0.891)R_P = 0.891 \Rightarrow \underline{R_P = 8.17 \text{ k}\Omega}$$

$$f_L = \frac{1}{2\pi(R_S + R_P)C_S}$$

$$\Rightarrow C_S = \frac{1}{2\pi(100)(1 + 8.17) \times 10^3}$$

$$\underline{C_S = 0.174 \text{ }\mu\text{F}}$$

$$f_H = \frac{1}{2\pi(R_S || R_P)C_P}$$

$$\Rightarrow C_P = \frac{1}{2\pi(10^6)(1 || 8.17) \times 10^3}$$

$$\underline{C_P = 179 \text{ pF}}$$

$$b. \quad \tau_S = (R_S + R_P)C_S$$

$$\tau_S = (1 \times 10^3 + 8.17 \times 10^3)(0.174 \times 10^{-6})$$

$$\underline{\tau_S = 1.60 \text{ ms open-circuit time-constant}}$$

$$\tau_P = (R_S || R_P)C_P$$

$$\tau_P = (1 || 8.17) \times 10^3 (179 \times 10^{-12})$$

$$\underline{\tau_P = 0.160 \text{ }\mu\text{s short-circuit time-constant}}$$

E7.6

a. Open-circuit time constant ( $C_L \rightarrow$  open)

$$\tau_S = (R_S + r_\pi)C_C$$

$$= (0.25 + 2) \times 10^3 (2 \times 10^{-6}) = 4.5 \text{ ms}$$

Short-circuit time constant ( $C_C \rightarrow$  short)

$$\tau_P = R_L C_L = (4 \times 10^3)(50 \times 10^{-12})$$

$$\underline{\tau_P = 0.2 \text{ }\mu\text{s}}$$

b. Midband gain

$$V_o = -g_m V_\pi R_L, \quad V_\pi = \left( \frac{r_\pi}{r_\pi + R_S} \right) V_i$$

$$A_v = \frac{V_o}{V_i} = \frac{-g_m r_\pi R_L}{r_\pi + R_S} = \frac{-(65)(2)(4)}{2 + 0.25}$$

$$\underline{A_v = -231}$$

$$c. \quad f_L = \frac{1}{2\pi\tau_S} = \frac{1}{2\pi(4.5 \times 10^{-3})} \Rightarrow \underline{f_L = 35.4 \text{ Hz}}$$

$$f_H = \frac{1}{2\pi\tau_P} = \frac{1}{2\pi(0.2 \times 10^{-6})} \Rightarrow \underline{f_H = 0.796 \text{ MHz}}$$

E7.7

$$a. \quad \tau_S = (R_1 + R_S)C_C$$

$$b. \quad f = \frac{1}{2\pi\tau_S}$$

$$R_{TH} = R_1 || R_2 = 2.2 || 20 = 1.98 \text{ k}\Omega$$

$$V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right) V_{CC} = \left( \frac{2.2}{2.2 + 20} \right) (10) = 0.991 \text{ V}$$

$$I_{BQ} = \frac{V_{TH} - V_{BE(on)}}{R_{TH} + (1 + \beta)R_E} = \frac{0.991 - 0.7}{1.98 + (201)(0.1)} = 0.0132 \text{ mA}$$

$$I_{CQ} = 2.64 \text{ mA}$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{(200)(0.026)}{2.64} = 1.97 \text{ k}\Omega$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{2.64}{0.026} = 102 \text{ mA/V}$$

$$R_{ib} = r_\pi + (1 + \beta)R_E = 1.97 + (201)(0.1) = 22.1 \text{ k}\Omega$$

$$R_B = R_1 || R_2 = 1.98 \text{ k}\Omega$$

$$R_i = R_B || R_{ib} = 1.98 || 22.1 = 1.82 \text{ k}\Omega$$

$$\tau_S = (R_i + R_S)C_C$$

$$= (1.82 + 0.1)(\times 10^3)(47 \times 10^{-6})$$

$$= 90.24 \text{ ms}$$

$$f = \frac{1}{2\pi(90.24 \times 10^{-3})} \Rightarrow \underline{f = 1.76 \text{ Hz}}$$

Midband Gain

$$A_v = \frac{-\beta R_C}{r_\pi + (1 + \beta)R_E} \cdot \frac{R_i}{R_i + R_S} = \frac{-(200)(2)}{1.97 + (201)(0.1)} \cdot \frac{1.82}{1.82 + 0.1}$$

$$\underline{A_v = -17.2}$$

E7.8

$$I_{DQ} = K_n (V_{GS} - V_{TN})^2$$

a.  $\sqrt{\frac{0.8}{0.5}} + 2 = V_{GS} \Rightarrow V_{GS} = 3.26 \text{ V}$

$$V_S = -3.26 \Rightarrow I_{DQ} = \frac{V_S - (-5)}{R_S}$$

$$R_S = \frac{-3.26 + 5}{0.8} \Rightarrow \underline{R_S = 2.18 \text{ k}\Omega}$$

$$V_D = 0 \Rightarrow R_D = \frac{5}{0.8} \Rightarrow \underline{R_D = 6.25 \text{ k}\Omega}$$

b.  $\tau_S = (R_D + R_L)C_C = (10 + 6.25) \times 10^3 \times C_C$

$$f = \frac{1}{2\pi\tau_S} \Rightarrow C_C = \frac{1}{2\pi f(16.25 \times 10^3)}$$

$$C_C = \frac{1}{2\pi(20)(16.25 \times 10^3)}$$

$$\Rightarrow \underline{C_C = 0.49 \mu\text{F}}$$

E7.9

$$\tau_S = (R_L + R_E \parallel R_O)C_{C2}$$

$$f = \frac{1}{2\pi\tau_S} \Rightarrow C_{C2} = \frac{1}{2\pi f(R_L + R_E \parallel R_O)}$$

$$R_O = r_o \parallel \left\{ \frac{r_\pi + (R_S \parallel R_B)}{1 + \beta} \right\}$$

From Example 7-5,  $R_O = 35.6 \Omega$

$$R_O \parallel R_E = 0.0356 \parallel 10 \approx 0.0356 \text{ k}\Omega$$

$$C_{C2} = \frac{1}{2\pi(10)[10 \times 10^3 + 35.6]}$$

$$\underline{C_{C2} = 1.59 \mu\text{F}}$$

E7.10

a.  $I_{DQ} = K_p (V_{SG} + V_{TP})^2$

$$\sqrt{\frac{1}{0.5}} - (-2) = V_{SG} \Rightarrow V_{SG} = 3.41 \text{ V}$$

$$V_S = 3.41$$

$$R_S = \frac{5 - 3.41}{1} \Rightarrow \underline{R_S = 1.59 \text{ k}\Omega}$$

For  $V_{SDG} = V_{SGQ} \Rightarrow V_D = 0$

$$\Rightarrow R_D = \frac{5}{1} \Rightarrow \underline{R_D = 5 \text{ k}\Omega}$$

b.  $\tau_P = (R_D \parallel R_L)C_L$

$$f = \frac{1}{2\pi\tau_P} \Rightarrow C_L = \frac{1}{2\pi f(R_D \parallel R_L)}$$

$$C_L = \frac{1}{2\pi(10^6)(5 \parallel 10) \times 10^3}$$

$$\Rightarrow \underline{C_L = 47.7 \text{ pF}}$$

E7.11

a.  $I_{BQ} = \frac{0 - 0.7 - (-10)}{0.5 + (101)(4)} = 0.0230 \text{ mA}$

$$I_{CQ} = 2.30 \text{ mA}$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{(100)(0.026)}{2.30} = 1.13 \text{ k}\Omega$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{2.30}{0.026} = 88.5 \text{ mA/V}$$

$$\tau_B = \frac{R_E(R_S + r_\pi)C_E}{R_S + r_\pi + (1 + \beta)R_E} = \frac{(4 \times 10^3)(0.5 + 1.13)C_E}{0.5 + 1.13 + (101)(4)}$$

$$\tau_B = \frac{1}{2\pi f_B} = \frac{1}{2\pi(200)} = 0.796 \text{ ms}$$

$$\tau_B = 16.07 C_E \Rightarrow C_E = \frac{0.796 \times 10^{-3}}{16.07}$$

$$\Rightarrow \underline{C_E = 49.5 \mu\text{F}}$$

b.  $\tau_A = R_E C_E = (4 \times 10^3)(49.5 \times 10^{-6})$

$$\Rightarrow \tau_A = 0.198 \text{ s}$$

$$f_A = \frac{1}{2\pi\tau_A} = \frac{1}{2\pi(0.198)} \Rightarrow \underline{f_A = 0.80 \text{ Hz}}$$

E7.14

$$r_\pi = \frac{\beta_0 V_T}{I_{CQ}} = \frac{(150)(0.026)}{0.5} = 7.8 \text{ k}\Omega$$

$$f_\beta = \frac{1}{2\pi r_\pi (C_\pi + C_\mu)}$$

$$= \frac{1}{2\pi(7.8 \times 10^3)(2 + 0.3) \times 10^{-12}}$$

$$\Rightarrow \underline{f_\beta = 8.87 \text{ MHz}}$$

E7.15

$$r_\pi = \frac{\beta_0 V_T}{I_{CQ}} = \frac{(100)(0.026)}{0.25} = 10.4 \text{ k}\Omega$$

$$f_\beta = \frac{1}{2\pi r_\pi (C_\pi + C_\mu)}$$

$$C_\pi + C_\mu = \frac{1}{2\pi f_\beta r_\pi} = \frac{1}{2\pi(11.5 \times 10^6)(10.4 \times 10^3)}$$

$$C_\pi + C_\mu = 1.33 \text{ pF}$$

$$C_\mu = 0.1 \text{ pF}$$

$$\Rightarrow \underline{C_\pi = 1.23 \text{ pF}}$$

E7.16

$$h_{fe} = \frac{\beta_0}{1 + j(f/f_\beta)}$$

$$f_\beta = 5 \text{ MHz}, \beta_0 = 100$$

At  $f = 50 \text{ MHz}$

$$|h_{fe}| = \frac{100}{\sqrt{1 + \left(\frac{50}{5}\right)^2}} \Rightarrow |h_{fe}| = 9.95$$

$$\text{Phase} = -\tan^{-1}\left(\frac{50}{5}\right) \Rightarrow \underline{\text{Phase} = -84.3^\circ}$$

E7.17

$$f_{\beta} = \frac{f_T}{\beta_0} = \frac{500}{120} \Rightarrow f_{\beta} = 4.17 \text{ MHz}$$

$$f_{\beta} = \frac{1}{2\pi r_{\pi}(C_{\pi} + C_{\mu})}$$

$$C_{\pi} + C_{\mu} = \frac{1}{2\pi f_{\beta} r_{\pi}} = \frac{1}{2\pi(4.17 \times 10^6)(5 \times 10^3)}$$

$$C_{\pi} + C_{\mu} = 7.63 \text{ pF}$$

$$C_{\mu} = 0.2 \text{ pF}$$

$$\Rightarrow C_{\pi} = 7.43 \text{ pF}$$

E7.18

$$r_{\pi} = \frac{\beta_0 V_T}{I_{CQ}} = \frac{(150)(0.026)}{1} \Rightarrow r_{\pi} = 3.9 \text{ k}\Omega$$

$$f_{\beta} = \frac{1}{2\pi r_{\pi}(C_{\pi} + C_{\mu})}$$

$$= \frac{1}{2\pi(3.9 \times 10^3)(4 + 0.5)(10^{-12})}$$

$$\Rightarrow f_{\beta} = 9.07 \text{ MHz}$$

$$f_T = \beta_0 f_{\beta} = (150)(9.07)$$

$$\Rightarrow f_T = 1.36 \text{ GHz}$$

E7.19

$$R_{TH} = R_1 || R_2 = 200 || 220 = 105 \text{ k}\Omega$$

$$V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right) V_{CC} = \left( \frac{220}{200 + 220} \right) (5)$$

$$= 2.62 \text{ V}$$

$$I_{BQ} = \frac{2.62 - 0.7}{105 + (101)(1)} = 0.00932 \text{ mA}$$

$$I_{CQ} = 0.932 \text{ mA}$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.932}{0.026} \Rightarrow g_m = 35.8 \text{ mA/V}$$

$$r_{\pi} = \frac{\beta V_T}{I_{CQ}} = \frac{(100)(0.026)}{0.932} \Rightarrow r_{\pi} = 2.79 \text{ k}\Omega$$

a.  $C_M = C_{\mu}[1 + g_m(R_C || R_L)]$

$$C_M = (2)[1 + (35.8)(2.2 || 4.7)]$$

$$\Rightarrow C_M = 109 \text{ pF}$$

b.  $R_B = r_S || R_1 || R_2 = 100 || 200 || 220 = 51.2 \text{ k}\Omega$

$$f_{3dB} = \frac{1}{2\pi(R_B || r_{\pi})(C_{\pi} + C_{\mu})}$$

$$= \frac{1}{2\pi[51.2 || 2.79] \times 10^3 \times (10 + 109) \times 10^{-12}}$$

$$\Rightarrow f_{3dB} = 0.505 \text{ MHz}$$

E7.20

(a)  $g_m = 2K_n(V_{GS} - V_{TN}) = 2(0.4)(3 - 1)$

$$\Rightarrow g_m = 1.6 \text{ mA/V}$$

$$g'_m = 80\% \text{ of } g_m = 1.28 \text{ mA/V}$$

$$g'_m = \frac{g_m}{1 + g_m r_S}$$

$$1 + g_m r_S = \frac{g_m}{g'_m}$$

$$r_S = \frac{1}{g_m} \left( \frac{g_m}{g'_m} - 1 \right) = \frac{1}{1.6} \left( \frac{1.6}{1.28} - 1 \right)$$

$$r_S = 0.156 \text{ k}\Omega \Rightarrow r_S = 156 \text{ ohms}$$

(b)  $g_m = 2K_n(V_{GS} - V_{TN}) = 2(0.4)(5 - 1)$

$$\Rightarrow g_m = 3.2 \text{ mA/V}$$

$$g'_m = \frac{g_m}{1 + g_m r_S} = \frac{3.2}{1 + (3.2)(0.156)} = 2.13$$

$$\frac{\Delta g_m}{g_m} = \frac{3.2 - 2.13}{3.2} \Rightarrow \text{A } 33.4\% \text{ reduction}$$

E7.21

$$f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$

$$I_{DQ} = K_n(V_{GS} - V_{TN})^2$$

$$0.4 = 0.2(V_{GS} - 1)^2 \Rightarrow V_{GS} = 2.41 \text{ V}$$

$$g_m = 2K_n(V_{GS} - V_{TN}) = 2(0.2)(2.41 - 1)$$

$$= 0.564 \text{ mA/V}$$

$$f_T = \frac{0.564 \times 10^{-3}}{2\pi(0.25 + 0.02) \times 10^{-12}} \Rightarrow$$

$$f_T = 332 \text{ MHz}$$

E7.22

$$f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$

$$= \frac{g_m}{2\pi(C_{gs} + C_{gsP} + C_{gdP})}$$

$$C_{gs} = \frac{g_m}{2\pi f_T} - C_{gsP} - C_{gdP}$$

$$= \frac{0.5 \times 10^{-3}}{2\pi(500 \times 10^6)} - (0.01 + 0.01) \times 10^{-12}$$

$$\Rightarrow C_{gs} = 0.139 \text{ pF}$$

E7.23

$$f_T = \frac{g_m}{2\pi(C_{gs} + C_{gsp} + C_{gd})}$$

$$C_{gsp} = C_{gd}$$

$$2C_{gsp} = \frac{g_m}{2\pi f_T} - C_{gs} = \frac{1 \times 10^{-3}}{2\pi(350 \times 10^6)} - 0.4 \times 10^{-12}$$

$$2C_{gsp} = 0.0547 \text{ pF}$$

$$\Rightarrow C_{gsp} = C_{gd} \approx 0.0274 \text{ pF}$$

E7.24

dc analysis

$$V_G = \left(\frac{R_2}{R_1 + R_2}\right)V_{DD} = \left(\frac{166}{166 + 234}\right)(10) = 4.15 \text{ V}$$

$$I_D = \frac{V_S}{R_S} \text{ and } V_S = V_G - V_{GS}$$

$$K_n(V_{GS} - V_{TN})^2 = \frac{V_G - V_{GS}}{R_S}$$


$$(0.5)(0.5)(V_{GS}^2 - 4V_{GS} + 4) = 4.15 - V_{GS}$$

$$0.25V_{GS}^2 - 3.15 = 0 \Rightarrow V_{GS} = 3.55 \text{ V}$$

$$g_m = 2K_n(V_{GS} - V_{TN}) = 2(0.5)(2.55 - 2)$$

$$= 1.55 \text{ mA/V}$$

Small-signal equivalent circuit.

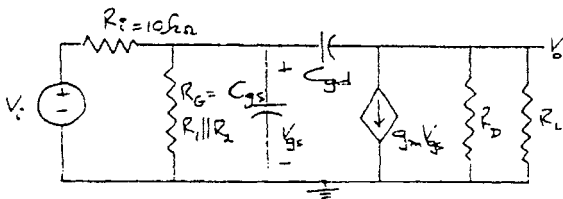

a.  $C_M = C_{gd}(1 + g_m(R_D || R_L))$

$$C_M = (0.1)[1 + (1.55)(4 || 20)]$$

$$\Rightarrow C_M = 0.617 \text{ pF}$$

b.  $f_H = \frac{1}{2\pi\tau_P}$

$$\tau_P = (R_G || R_i)(C_{gs} + C_M)$$

$$R_G = R_1 || R_2 = 234 || 166 = 97.1 \text{ k}\Omega$$

$$R_G || R_i = 97.1 || 10 = 9.07 \text{ k}\Omega$$

$$\tau_P = (9.07 \times 10^3)(1 + 0.617) \times 10^{-12} = 14.7 \text{ ns}$$

$$f_H = \frac{1}{2\pi(14.7 \times 10^{-9})} \Rightarrow f_H = 10.9 \text{ MHz}$$

E7.25

dc analysis

$$V_{TH} = 0, R_{TH} = 10 \text{ k}\Omega$$

$$I_{BQ} = \frac{0 - 0.7 - (-5)}{10 + (126)(5)} = 0.00672 \text{ mA}$$


$$I_{CQ} = 0.840 \text{ mA}$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{(125)(0.026)}{0.840} = 3.87 \text{ k}\Omega$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.840}{0.026} = 32.3 \text{ mA/V}$$

$$r_o = \frac{V_A}{I_{CQ}} = \frac{200}{0.84} = 238 \text{ k}\Omega$$

High-frequency equivalent circuit

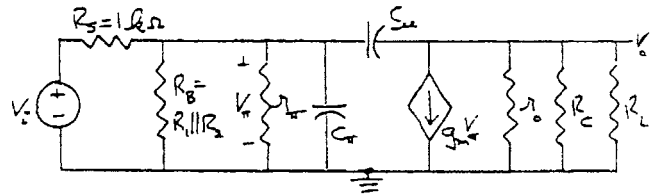

a. Miller capacitance

$$C_M = C_\mu(1 + g_m R'_L)$$

$$R'_L = r_o || R_C || R_L$$

$$R'_L = 238 || 2.3 || 5 = 1.57 \text{ k}\Omega$$

$$C_M = (3)[1 + (32.3)(1.57)] \Rightarrow C_M = 155 \text{ pF}$$

b.  $R_{eq} = R_S || R_B || r_\pi = R_S || R_1 || R_2 || r_\pi$

$$R_{eq} = 1 || 20 || 20 || 3.87 = 0.736 \text{ k}\Omega$$

$$\tau_P = R_{eq}(C_\pi + C_M)$$

$$= (0.736 \times 10^3)(24 + 155) \times 10^{-12}$$

$$= 1.32 \times 10^{-7}$$

$$f_H = \frac{1}{2\pi(1.32 \times 10^{-7})} \Rightarrow f_H = 1.21 \text{ MHz}$$

c.  $(A_v)_M = -g_m R'_L \left[ \frac{R_B || r_\pi}{R_B || r_\pi + R_S} \right]$

$$(A_v)_M = -(32.3)(1.57) \left[ \frac{10 || 3.87}{10 || 3.87 + 1} \right]$$

$$\Rightarrow (A_v)_M = -37.3$$

E7.26

dc analysis

$$V_G = \left( \frac{50}{50 + 150} \right) (10) - 5 = -2.5$$

$$V_S = V_G - V_{GS}. \quad I_D = \frac{V_S - (-5)}{R_S}$$

$$K_n (V_{GS} - V_{TN})^2 = \frac{V_G - V_{GS} + 5}{R_S}$$

$$(1)(2) [V_{GS}^2 - 1.6V_{GS} + 0.64] = -2.5 - V_{GS} + 5$$

$$2V_{GS}^2 - 2.2V_{GS} - 1.22 = 0$$


$$V_{GS} = \frac{2.2 \pm \sqrt{(2.2)^2 + 4(2)(1.22)}}{2(2)}$$

$$\Rightarrow V_{GS} = 1.51 \text{ V}$$

$$g_m = 2K_n (V_{GS} - V_{TN}) = 2(1)(1.51 - 0.8)$$

$$= 1.42 \text{ mA/V}$$

Equivalent circuit

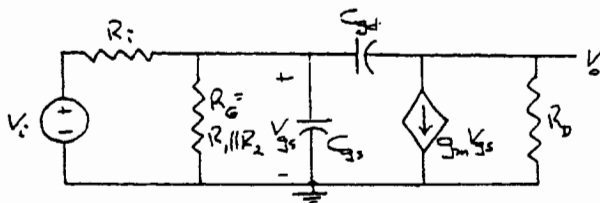

$$(a) \quad C_M = C_{gd} (1 + g_m R_D) = (0.2) [1 + (1.42)(5)] \Rightarrow$$

$$C_M = 1.62 \text{ pF}$$

$$(b) \quad \tau_P = (R_S \parallel R_G) (C_M + C_M)$$

$$\tau_P = [20 \parallel 50 \parallel 150] \times 10^3 \times (2 + 1.62) \times 10^{-12}$$

$$= (13 \times 10^3) (3.62 \times 10^{-12}) = 4.71 \times 10^{-8} \text{ s}$$

$$f_H = \frac{1}{2\pi\tau_P} = \frac{1}{2\pi(4.7 \times 10^{-8})}$$

$$\Rightarrow \underline{f_H = 3.38 \text{ MHz}}$$

$$c. \quad (A_v)_M = -g_m R_D \left( \frac{R_G}{R_G + R_S} \right)$$

$$(A_v)_M = -(1.42)(5) \left( \frac{37.5}{37.5 + 20} \right)$$

$$\Rightarrow \underline{(A_v)_M = -4.63}$$

E7.27

The dc analysis

$$I_{BQ} = \frac{10 - 0.7}{100 + (101)(10)} = 0.00838 \text{ mA}$$

$$I_{CQ} = 0.838 \text{ mA}$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{(100)(0.026)}{0.838} = 3.10 \text{ k}\Omega$$

$$g_m = \frac{I_{CQ}}{V_T} = 32.2 \text{ mA/V}$$

For the input

$$\tau_{P\pi} = \left[ \left( \frac{r_\pi}{1 + \beta} \right) \parallel R_E \parallel R_S \right] C_\pi$$

$$= \left[ \frac{3.10}{101} \parallel 10 \parallel 1 \right] \times 10^3 \times 24 \times 10^{-12}$$

$$= 7.13 \times 10^{-10} \text{ s}$$

$$f_{H\pi} = \frac{1}{2\pi\tau_{P\pi}} = \frac{1}{2\pi(7.13 \times 10^{-10})}$$

$$\Rightarrow \underline{f_{H\pi} = 223 \text{ MHz}}$$

For the output

$$\tau_{P\mu} = [R_C \parallel R_L] C_\mu = (10 \parallel 1) \times 10^3 \times 3 \times 10^{-12}$$

$$= 2.73 \times 10^{-9}$$

$$f_{H\mu} = \frac{1}{2\pi\tau_{P\mu}} = \frac{1}{2\pi(2.73 \times 10^{-9})}$$

$$\Rightarrow \underline{f_{H\mu} = 58.3 \text{ MHz}}$$

$$(A_v)_M = g_m (R_C \parallel R_L) \left[ \frac{R_E \parallel \left( \frac{r_\pi}{1 + \beta} \right)}{R_E \parallel \left( \frac{r_\pi}{1 + \beta} \right) + R_S} \right]$$

$$= (32.2)(10 \parallel 1) \left[ \frac{10 \parallel \left( \frac{3.1}{101} \right)}{10 \parallel \left( \frac{3.1}{101} \right) + 1} \right]$$

$$\Rightarrow \underline{(A_v)_M = 0.869}$$

## Chapter 7


### Problem Solutions

7.1

a.  $T(s) = \frac{V_0(s)}{V_i(s)} = \frac{1/(sC_1)}{[1/(sC_1)] + R_1}$

$$T(s) = \frac{1}{1 + sR_1C_1}$$

b.

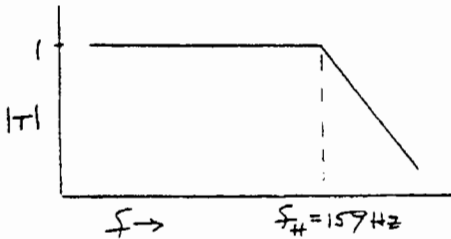

$$f_H = \frac{1}{2\pi R_1 C_1} = \frac{1}{2\pi(10^3)(10^{-6})}$$

$$\Rightarrow f_H = 159 \text{ Hz}$$

c.  $V_0(s) = V_i(s) \cdot \frac{1}{1 + sR_1C_1}$

For a step function  $V_i(s) = \frac{1}{s}$

$$V_0(s) = \frac{1}{s} \cdot \frac{1}{1 + sR_1C_1} = \frac{K_1}{s} + \frac{K_2}{1 + sR_1C_1}$$

$$= \frac{K_1(1 + sR_1C_1) + K_2s}{s(1 + sR_1C_1)}$$

$$= \frac{K_1 + s(K_1R_1C_1 + K_2)}{s(1 + sR_1C_1)}$$

$$K_2 = -K_1R_1C_1 \text{ and } K_1 = 1$$

$$V_0(s) = \frac{1}{s} + \frac{-R_1C_1}{1 + sR_1C_1}$$

$$= \frac{1}{s} - \frac{1}{\frac{1}{R_1C_1} + s}$$


$$v_0(t) = 1 - e^{-t/R_1C_1}$$

7.2

a.  $T(s) = \frac{V_0(s)}{V_i(s)} = \frac{R_2}{R_2 + [1/(sC_2)]}$

$$T(s) = \frac{sR_2C_2}{1 + sR_2C_2}$$

b.

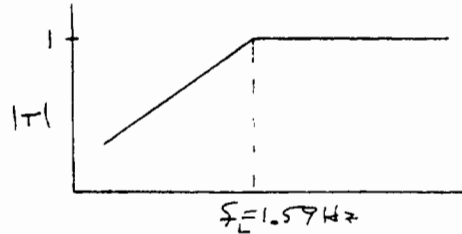

$$f_L = \frac{1}{2\pi R_2 C_2} = \frac{1}{2\pi(10^4)(10 \times 10^{-6})}$$

$$\Rightarrow f_L = 1.59 \text{ kHz}$$

c.  $V_0(s) = V_i(s) \cdot \frac{sR_2C_2}{1 + sR_2C_2}$

$$V_i(s) = \frac{1}{s}$$

$$V_0(s) = \frac{R_2C_2}{1 + sR_2C_2} = \frac{1}{s + \frac{1}{R_2C_2}}$$

$$v_0(t) = e^{-t/R_2C_2}$$

7.3

a.  $T(s) = \frac{V_0(s)}{V_i(s)} = \frac{R_P \parallel \frac{1}{sC_P}}{R_P \parallel \frac{1}{sC_P} + \left(R_S + \frac{1}{sC_S}\right)}$

$$R_P \parallel \frac{1}{sC_P} = \frac{R_P \cdot \frac{1}{sC_P}}{R_P + \frac{1}{sC_P}} = \frac{R_P}{1 + sR_P C_P}$$

Then

$$T(s) = \frac{R_P}{R_P + \left(R_S + \frac{1}{sC_S}\right)(1 + sR_P C_P)}$$

$$= \frac{R_P}{R_P + R_S + \frac{R_P C_P}{C_S} + \frac{1}{sC_S} + sR_S R_P C_P}$$

$T(s)$

$$= \left(\frac{R_P}{R_P + R_S}\right) \times \left(1 / \left[1 + \frac{R_P}{R_P + R_S} \cdot \frac{C_P}{C_S} + \frac{1}{s(R_S + R_P)C_S} + \frac{sR_P R_S}{R_S + R_P} \cdot C_P\right]\right)$$

b.

$$T(s) = \left( \frac{10}{10+10} \right) \times \left( 1 / \left[ 1 + \frac{10}{20} \cdot \frac{10^{-11}}{10^{-6}} + \frac{1}{s(2 \times 10^4) \cdot 10^{-6}} + s(5 \times 10^3) \cdot 10^{-11} \right] \right)$$

$$\approx \frac{1}{2} \cdot \frac{1}{1 + \frac{1}{s(0.02)} + s(5 \times 10^{-6})}$$

$s = j\omega$

$$T(j\omega) = \frac{1}{2} \cdot \frac{1}{1 + j \left[ \omega(5 \times 10^{-6}) - \frac{1}{\omega(0.02)} \right]}$$

For  $\omega_L = \frac{1}{(R_S + R_P)C_S} = \frac{1}{(2 \times 10^4)(10^{-6})} = 50$

$$T(j\omega) = \frac{1}{2} \cdot \frac{1}{1 + j \left[ (50)(5 \times 10^{-6}) - \frac{1}{(50)(0.02)} \right]}$$

$$\approx \frac{1}{2} \cdot \frac{1}{1-j} \Rightarrow |T(j\omega)| = \frac{1}{2} \cdot \frac{1}{\sqrt{2}}$$

For

$$\omega_H = \frac{1}{(R_S \parallel R_P)C_P} = \frac{1}{(5 \times 10^3)(10^{-11})} = 2 \times 10^7$$

$$T(j\omega) = \frac{1}{2} \cdot \frac{1}{1 + j \left[ (2 \times 10^7)(5 \times 10^{-6}) - \frac{1}{(2 \times 10^7)(0.02)} \right]}$$

$$T(j\omega) \approx \frac{1}{2} \cdot \frac{1}{1+j} \Rightarrow |T(j\omega)| = \frac{1}{2} \cdot \frac{1}{\sqrt{2}}$$

In each case,  $|T(j\omega)| = \frac{1}{\sqrt{2}} \cdot \frac{R_P}{R_P + R_S}$

c.  $R_S = R_P = 10 \text{ k}\Omega$ ,  $C_S = C_P = 0.1 \text{ }\mu\text{F}$

$$T(s) = \frac{1}{2} \cdot \left( 1 / \left[ 1 + \frac{1}{2} \cdot \frac{1}{1} + \frac{1}{s(2 \times 10^4)(10^{-7})} + s(5 \times 10^3)(10^{-7}) \right] \right)$$

$s = j\omega$

$$T(j\omega) = \frac{1}{2} \cdot \frac{1}{1 + \frac{1}{2} + j \left[ \omega(5 \times 10^{-4}) - \frac{1}{\omega(2 \times 10^{-3})} \right]}$$

For  $\omega = \frac{1}{(2 \times 10^4)(10^{-7})} = 500$

$$T(j\omega) = \frac{1}{2} \cdot \frac{1}{1.5 + j \left[ (500)(5 \times 10^{-4}) - \frac{1}{(500)(2 \times 10^{-3})} \right]}$$

$$= \frac{1}{2} \cdot \frac{1}{1.5 - j(0.75)} \Rightarrow |T(j\omega)| = 0.298$$

For  $\omega = \frac{1}{(5 \times 10^3)(10^{-7})} = 2 \times 10^3$

$$T(j\omega) = \frac{1}{2} \cdot \left\{ 1 / \left( 1.5 + j \left[ (2 \times 10^3)(5 \times 10^{-4}) - \frac{1}{(2 \times 10^3)(2 \times 10^{-3})} \right] \right) \right\}$$

$$= \frac{1}{2} \cdot \frac{1}{1.5 + j(0.75)} \Rightarrow |T(j\omega)| = 0.298$$

In each case,  $|T(j\omega)| < \frac{1}{\sqrt{2}} \cdot \frac{R_P}{R_P + R_S}$

7.4

Circuit (a):

$$T = \frac{V_o}{V_i} = \frac{R_2}{R_2 + R_1 \parallel \frac{1}{sC_1}} = \frac{R_2}{R_2 + \frac{R_1(1/sC_1)}{R_1 + (1/sC_1)}}$$

$$= \frac{R_2}{R_2 + \frac{R_1}{1 + sR_1C_1}} = \frac{R_2(1 + sR_1C_1)}{R_2 + sR_1R_2C_1 + R_1}$$

or

$$\frac{V_o}{V_i} = \frac{R_2}{R_1 + R_2} \cdot \frac{(1 + sR_1C_1)}{1 + sR_1 \parallel R_2 C_1}$$

Low frequency:

$$\left| \frac{V_o}{V_i} \right| = \frac{R_2}{R_1 + R_2} = \frac{20}{10 + 20} = \frac{2}{3}$$

High frequency:

$$\left| \frac{V_o}{V_i} \right| = 1$$


$$\tau_1 = R_1C_1 = (10^4)(10 \times 10^{-6}) = 0.10 \Rightarrow$$

$$f_1 = \frac{1}{2\pi\tau_1} = 159 \text{ Hz}$$

$$\tau_2 = (R_1 \parallel R_2)C_1 = (10 \parallel 20) \times 10^3 \times (10 \times 10^{-6}) \Rightarrow$$

$$\tau_2 = 0.0667 \Rightarrow$$
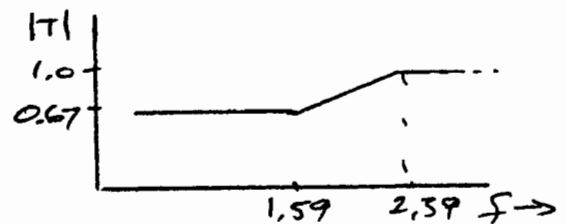
$$f_2 = \frac{1}{2\pi\tau_2} = 2.39 \text{ Hz}$$



Circuit (b):

$$T = \frac{V_o}{V_i} = \frac{R_2 \parallel \frac{1}{sC_2}}{R_2 \parallel \frac{1}{sC_2} + R_1} = \frac{\frac{R_2}{1 + sR_2C_2}}{\frac{R_2}{1 + sR_2C_2} + R_1}$$


$$= \left( \frac{R_2}{R_1 + R_2} \right) \left( \frac{1}{1 + s(R_1 \parallel R_2)C_2} \right)$$

Low frequency:

$$\left| \frac{V_o}{V_i} \right| = \frac{R_2}{R_1 + R_2} = \frac{20}{20 + 10} = \frac{2}{3}$$

$$\tau = (R_1 \parallel R_2)C_2 = (10 \parallel 20) \times 10^3 \times 10 \times 10^{-6} = 0.0667$$
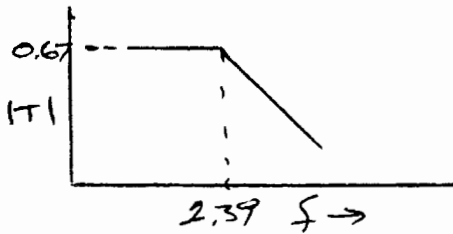
$$f = \frac{1}{2\pi\tau} = 2.39 \text{ Hz}$$



7.5

a.  $\tau_S = (R_i + R_P)C_S = [30 + 10] \times 10^3 \times 10 \times 10^{-6}$

$\Rightarrow \tau_S = 0.40 \text{ s}$

$\tau_P = (R_i \parallel R_P)C_P = [30 \parallel 10] \times 10^3 \times 50 \times 10^{-12}$

$\Rightarrow \tau_P = 0.375 \mu\text{s}$

b.  $f_L = \frac{1}{2\pi\tau_S} = \frac{1}{2\pi(0.4)} \Rightarrow f_L = 0.398 \text{ Hz}$


$f_H = \frac{1}{2\pi\tau_P} = \frac{1}{2\pi(0.375 \times 10^{-6})} \Rightarrow f_H = 424 \text{ kHz}$

At midband.  $C_S \rightarrow$  short,  $C_P \rightarrow$  open

$V_o = I_i(R_i \parallel R_P)$

$T(s) = R_i \parallel R_P = 30 \parallel 10 \Rightarrow T(s) = 7.5 \text{ k}\Omega$

c.

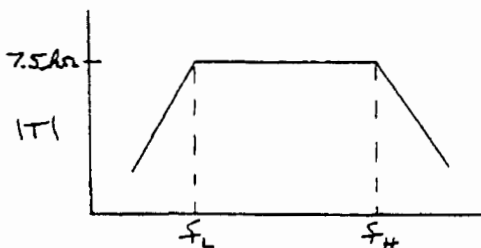

7.6

(a)  $T = \frac{1}{(1 + j2\pi f\tau)^2} \Rightarrow$

$$|T| = \frac{1}{(\sqrt{1 + (2\pi f\tau)^2})^2} = \frac{1}{1 + (2\pi f\tau)^2}$$

$|T|_{\max} = 1$

At  $f = \frac{1}{2\pi\tau} \Rightarrow |T| = \frac{1}{1 + (1)^2} = \frac{1}{2}$

$|T|_{dB} = 20 \log_{10}\left(\frac{1}{2}\right) \Rightarrow |T|_{dB} \approx -6 \text{ dB}$

Phase =  $2 \tan^{-1}(2\pi f\tau) = -2 \tan^{-1}(1) = -2(45^\circ) \Rightarrow$

Phase =  $-90^\circ$

(b) Slope

$= -2(6 \text{ dB/oct}) =$

$-12 \text{ dB/oct} = -40 \text{ dB/decade}$


Phase =  $-2(90^\circ) \Rightarrow$  Phase =  $-180^\circ$

7.7

(a)  $T(j\omega) = \frac{-10(j\omega)}{20\left(1 + \frac{j\omega}{20}\right)(2000)\left(1 + \frac{j\omega}{2000}\right)}$


$$= \frac{2.5 \times 10^{-4}(j\omega)}{\left(1 + \frac{j\omega}{20}\right)\left(1 + \frac{j\omega}{2000}\right)}$$

$$|T| = \frac{2.5 \times 10^{-4}(\omega)}{\sqrt{1 + \left(\frac{\omega}{20}\right)^2} \cdot \sqrt{1 + \left(\frac{\omega}{2000}\right)^2}}$$

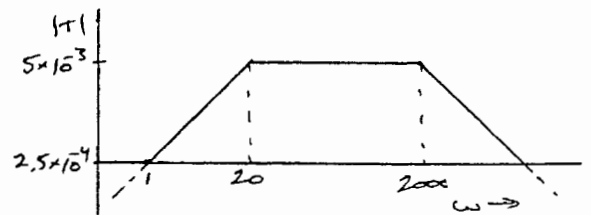

(b)  $T(j\omega) = \frac{(10)(10)\left(1 + \frac{j\omega}{10}\right)}{1000\left(1 + \frac{j\omega}{1000}\right)}$

$$|T| = \frac{(0.10)\sqrt{1 + \left(\frac{\omega}{10}\right)^2}}{\sqrt{1 + \left(\frac{\omega}{1000}\right)^2}}$$

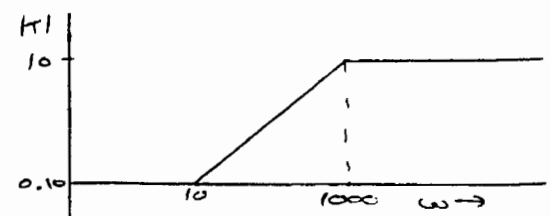

7.8

a.  $V_0 = -g_m V_\pi R_L$   $V_\pi = \left( \frac{r_\pi}{r_\pi + R_S} \right) V_i$

$|T| = g_m R_L \left( \frac{r_\pi}{r_\pi + R_S} \right) = (29)(6) \left( \frac{5.2}{5.2 + 0.5} \right)$

$|T_{midband}| = 159$

b.  $\tau_S = (R_S + r_\pi) C_C$

$f_L = \frac{1}{2\pi\tau_S} \Rightarrow \tau_S = \frac{1}{2\pi f_L} = \frac{1}{2\pi(30)}$

$\Rightarrow \tau_S = 5.31 \text{ ms}$  Open-circuit

$\tau_P = \frac{1}{2\pi f_H} = \frac{1}{2\pi(480 \times 10^3)}$

$\Rightarrow \tau_P = 0.332 \text{ } \mu\text{s}$  Short-circuit

c.  $C_C = \frac{\tau_S}{(R_S + r_\pi)} = \frac{5.31 \times 10^{-3}}{(0.5 + 5.2) \times 10^3}$

$\Rightarrow C_C = 0.932 \text{ } \mu\text{F}$

$\tau_P = R_L C_L$

$C_L = \frac{\tau_P}{R_L} = \frac{0.332 \times 10^{-6}}{6 \times 10^3} \Rightarrow C_L = 55.3 \text{ pF}$

7.11

a.  $R_{TH} = R_1 \parallel R_2 = 10 \parallel 1.5 = 1.30 \text{ k}\Omega$

$V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right) V_{CC} = \left( \frac{1.5}{1.5 + 10} \right) (12)$   
 $= 1.565 \text{ V}$

$I_{BQ} = \frac{1.565 - 0.7}{1.30 + (101)(0.1)} = 0.0759 \text{ mA}$

$I_{CQ} = 7.59 \text{ mA}$

$r_\pi = \frac{(100)(0.026)}{7.59} = 0.343 \text{ k}\Omega$


$g_m = \frac{7.59}{0.026} = 292 \text{ mA/V}$

$R_i = R_1 \parallel R_2 \parallel [r_\pi + (1 + \beta)R_E]$   
 $= 10 \parallel 1.5 \parallel [0.343 + (101)(0.1)]$   
 $= 1.30 \parallel 10.4 \Rightarrow R_i = 1.16 \text{ k}\Omega$

$\tau = (R_S + R_i) C_C = [0.5 + 1.16] \times 10^3 \times 0.1 \times 10^{-6}$   
 $\tau = 1.66 \times 10^{-4}$

$f_L = \frac{1}{2\pi\tau} = \frac{1}{2\pi(1.66 \times 10^{-4})} \Rightarrow f_L = 959 \text{ Hz}$

b.

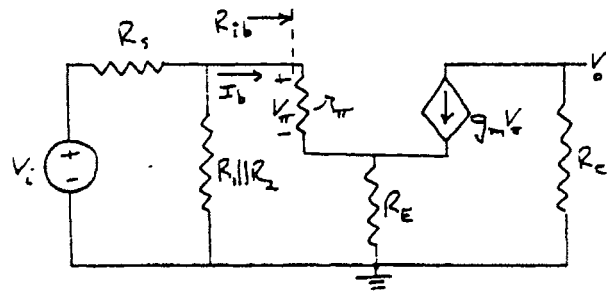

$V_0 = -(\beta I_b) R_C$

$R_{i,b} = r_\pi + (1 + \beta) R_E$   
 $= 0.343 + (101)(0.1) = 10.4 \text{ k}\Omega$

$I_b = \left( \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_{i,b}} \right) I_i$   
 $= \left( \frac{1.30}{1.30 + 10.4} \right) I_i = (0.111) I_i$


$I_i = \frac{V_i}{R_S + R_1 \parallel R_2 \parallel R_{i,b}}$   
 $= \frac{V_i}{0.5 + (1.3) \parallel (10.4)}$

$I_i = \frac{V_i}{1.656}$

$\left| \frac{V_0}{V_i} \right| = \frac{\beta R_C (0.111)}{1.656}$   
 $\Rightarrow \left| \frac{V_0}{V_i} \right|_{midband} = \frac{(100)(1)(0.111)}{1.656}$

$\Rightarrow \left| \frac{V_0}{V_i} \right|_{midband} = 6.70$

c.

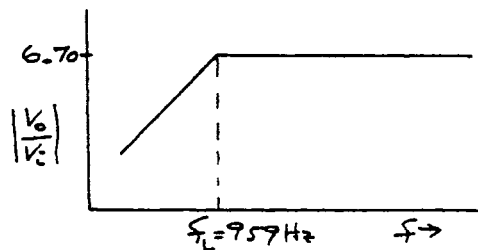

7.12

$I_{DQ} = 0.5 \text{ mA} \Rightarrow V_S = (0.5)(0.5) = 0.25 \text{ V}$

$I_{DQ} = K_n (V_{GS} - V_{TN})^2$

$\Rightarrow V_{GS} = \sqrt{\frac{0.5}{0.2}} + 1.5 = 3.08 \text{ V}$

$V_G = V_{GS} + V_S = 3.08 + 0.25 \Rightarrow V_G = 3.33 \text{ V}$

$V_G = \left( \frac{R_2}{R_1 + R_2} \right) V_{DD} \Rightarrow 3.33 = \frac{1}{R_1} \cdot R_{in} \cdot V_{DD}$

$$3.33 = \frac{1}{R_1}(200)(9) \Rightarrow R_1 = 541 \text{ k}\Omega$$

$$\frac{541R_2}{541 + R_2} = 200 \Rightarrow R_2 = 317 \text{ k}\Omega$$

$$V_D = V_{DSQ} + V_S = 4.5 + 0.25 = 4.75$$

$$R_D = \frac{9 - 4.75}{0.5} \Rightarrow R_D = 8.5 \text{ k}\Omega$$

$$f_L = \frac{1}{2\pi\tau_L} \Rightarrow \tau_L = \frac{1}{2\pi f_L} = \frac{1}{2\pi(20)} = 7.96 \text{ ms}$$



$$\tau_L = R_{in} \cdot C_C \Rightarrow C_C = \frac{\tau_L}{R_{in}} = \frac{7.96 \times 10^{-3}}{200 \times 10^3}$$

$$\Rightarrow C_C = 0.0398 \text{ }\mu\text{F}$$

$$g_m = 2(0.2)(3.08 - 1.5) = 0.632 \text{ mA/V}$$

$$|A_v|_{\text{midband}} = \frac{g_m R_D}{1 + g_m R_S} = \frac{(0.632)(8.5)}{1 + (0.632)(0.5)}$$

$$\Rightarrow |A_v| = 4.08$$

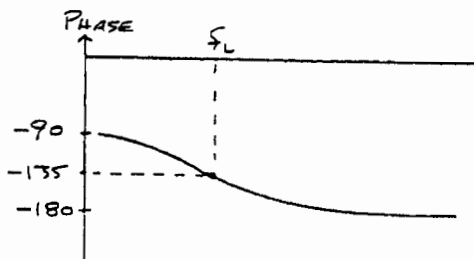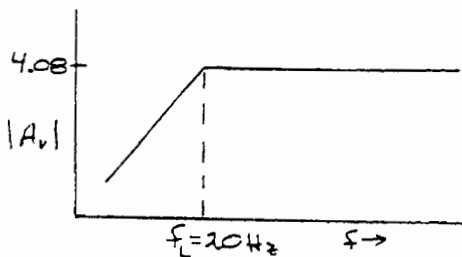

7.13

$$I_{DQ} = K_n(V_{GS} - V_{TN})^2$$

$$\Rightarrow V_{GS} = \sqrt{\frac{I_{DQ}}{K_n}} + V_{TN} = \sqrt{\frac{1}{0.5}} + 1 = 2.41 \text{ V}$$


$$V_S = -2.41 \text{ V}$$

$$R_S = \frac{-2.41 - (-5)}{1} \Rightarrow R_S = 2.59 \text{ k}\Omega$$

$$V_D = V_{DSQ} + V_S = 3 - 2.41 = 0.59 \text{ V}$$

$$R_D = \frac{5 - 0.59}{1} \Rightarrow R_D = 4.4 \text{ k}\Omega$$

b.

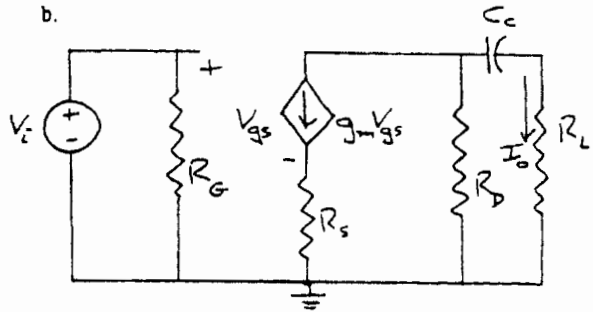

$$I_o = -(g_m V_{gs}) \left( \frac{R_D}{R_D + R_L + \frac{1}{sC_C}} \right)$$

$$V_{gs} = \frac{V_i}{1 + g_m R_S}$$

$$\frac{I_o(s)}{V_i(s)} = \frac{-g_m}{1 + g_m R_S} \cdot R_D \left[ \frac{sC_C}{1 + s(R_D + R_L)C_C} \right]$$

$$T(s) = \frac{I_o(s)}{V_i(s)}$$

$$= \frac{-g_m R_D}{1 + g_m R_S} \cdot \frac{1}{R_D + R_L} \cdot \frac{s(R_D + R_L)C_C}{1 + s(R_D + R_L)C_C}$$

c.  $f_L = \frac{1}{2\pi\tau_L} \rightarrow \tau_L = \frac{1}{2\pi f_L} = \frac{1}{2\pi(10)} = 15.9 \text{ ms}$

$$\tau_L = (R_D + R_L)C_C$$

$$\Rightarrow C_C = \frac{\tau_L}{R_D + R_L} = \frac{15.9 \times 10^{-3}}{(4.41 + 4) \times 10^3}$$

$$\Rightarrow C_C = 1.89 \text{ }\mu\text{F}$$

7.14

a.  $\frac{9 - V_{SG}}{R_S} = I_D = K_p(V_{SG} + V_{TP})^2$

$$9 - V_{SG} = (0.5)(12)(V_{SG}^2 - 4V_{SG} + 4)$$

$$6V_{SG}^2 - 23V_{SG} + 15 = 0$$

$$V_{SG} = \frac{23 \pm \sqrt{(23)^2 - 4(6)(15)}}{2(6)} \Rightarrow V_{SG} = 3 \text{ V}$$

$$g_m = 2K_p(V_{SG} + V_{TP}) = 2(0.5)(3 - 2)$$

$$\Rightarrow g_m = 1 \text{ mA/V}$$

$$R_o = \frac{1}{g_m} \parallel R_S = 1 \parallel 12 \Rightarrow R_o = 0.923 \text{ k}\Omega$$

b.  $\tau = (R_o + R_L)C_C$

c.  $f_L = \frac{1}{2\pi\tau} \Rightarrow \tau = \frac{1}{2\pi f_L} = \frac{1}{2\pi(20)} = 7.96 \text{ ms}$

$$C_C = \frac{\tau}{R_o + R_L} = \frac{7.96 \times 10^{-3}}{(0.923 + 10) \times 10^3}$$

$$\Rightarrow C_C = 0.729 \text{ }\mu\text{F}$$

7.15

a.  $I_{CQ} = 1 \text{ mA}$ ,  $I_{BQ} = \frac{1}{120} = 0.00833 \text{ mA}$

$$R_1 \parallel R_2 = (0.1)(1 + \beta)(R_E) = (0.1)(121)(4) = 48.4 \text{ k}\Omega$$

$$V_{TH} = I_{BQ}R_{TH} + V_{BE(ON)} + (1 + \beta)I_{BQ}R_E$$

$$\frac{1}{R_1} \cdot R_{TH} \cdot V_{CC} = (0.00833)(48.4) + 0.7 + (121)(0.00833)(4)$$

$$\frac{1}{R_1}(48.4)(12) = 5.13$$

$$R_1 = 113 \text{ k}\Omega$$

$$\frac{113R_2}{113 + R_2} = 48.4 \Rightarrow R_2 = 84.7 \text{ k}\Omega$$

b.  $R_o = \frac{r_\pi}{1 + \beta} \parallel R_E \parallel r_o$

$$r_\pi = \frac{(120)(0.026)}{1} = 3.12 \text{ k}\Omega$$

$$r_o = \frac{80}{1} = 80 \text{ k}\Omega$$

$$R_o = \frac{3.12}{121} \parallel 4 \parallel 80 = 0.0258 \parallel 4 \parallel 80$$

$$\Rightarrow R_o = 25.6 \Omega$$

c.  $\tau = (R_o + R_L)C_{C2}$

$$\tau = (0.0256 + 4) \times 10^3 \times 2 \times 10^{-6} = 8.05 \times 10^{-3} \text{ s}$$

$$f = \frac{1}{2\pi\tau} = \frac{1}{2\pi(8.05 \times 10^{-3})} \Rightarrow f = 19.8 \text{ Hz}$$

7.16

(a)  $\frac{5 - V_{SG}}{R_1} = K_p(V_{SG} + V_{TP})^2$

$$5 - V_{SG} = (1)(1.2)(V_{SG} - 1.5)^2 = (1.2)(V_{SG}^2 - 3V_{SG} + 2.25)$$

$$1.2V_{SG}^2 - 2.6V_{SG} - 2.3 = 0 \Rightarrow V_{SG} = 2.84 \text{ V}$$

$$I_{DQ} = 1.8 \text{ mA}$$

$$V_{SDQ} = 10 - (1.8)(1.2 + 1.2) \Rightarrow V_{SDQ} = 5.68 \text{ V}$$

$$g_m = 2\sqrt{K_p I_{DQ}} = 2\sqrt{(1)(1.8)} = 2.68 \text{ mA/V}$$

$$r_o = \infty$$

(b)  $R_{ib} = \frac{1}{g_m} = \frac{1}{2.68} = 0.373 \text{ k}\Omega$

$$R_i = 1.2 \parallel 0.373 = 0.285 \text{ k}\Omega$$

For  $C_{C1}$ ,  $\tau_{11} = (285 + 200)(4.7 \times 10^{-6}) = 2.28 \text{ ms}$

For  $C_{C2}$ ,  $\tau_{12} = (1.2 \times 10^3 + 50 \times 10^3)(10^{-6}) = 51.2 \text{ ms}$

(c)  $C_{C2}$  dominates,

$$f_{3-dB} = \frac{1}{2\pi\tau_{12}} = \frac{1}{2\pi(51.2 \times 10^{-3})} = 3.1 \text{ Hz}$$

7.17

Assume  $V_{TN} = 1 \text{ V}$ ,  $k'_n = 80 \mu\text{A/V}^2$ ,  $\lambda = 0$

Neglecting  $R_{S1} = 200 \Omega$ , Midband gain is:

$$|A_v| = g_m R_D$$

Let  $I_{DQ} = 0.2 \text{ mA}$ ,  $V_{DSQ} = 5 \text{ V}$

$$\text{Then } R_D = \frac{9 - 5}{0.2} \Rightarrow R_D = 20 \text{ k}\Omega$$

We need

$$g_m = \frac{|A_v|}{R_D} = \frac{10}{20} = 0.5 \text{ mA/V}^2$$

and

$$g_m = 2\sqrt{K_n I_{DQ}} = 2\sqrt{\left(\frac{k'_n}{2}\right)\left(\frac{W}{L}\right)I_{DQ}}$$

or

$$0.5 = 2\sqrt{\left(\frac{0.080}{2}\right)\left(\frac{W}{L}\right)(0.2)} \Rightarrow \frac{W}{L} = 7.81$$

$$\text{Let } R_1 + R_2 = \frac{9}{(0.2)I_{DQ}} = \frac{9}{(0.2)(0.2)} = 225 \text{ k}\Omega$$

$$I_{DQ} = 0.2 = \left(\frac{0.080}{2}\right)(7.81)(V_{GS} - 1)^2$$

$$\Rightarrow V_{GS} = 1.80 = \left(\frac{R_2}{R_1 + R_2}\right)(9) = \left(\frac{R_2}{225}\right)(9) \Rightarrow$$

$$R_2 = 45 \text{ k}\Omega, R_1 = 180 \text{ k}\Omega$$

$$R_{TH} = R_1 \parallel R_2 = 180 \parallel 45 = 36 \text{ k}\Omega$$

$$\tau_1 = \frac{1}{2\pi f_1} = \frac{1}{2\pi(200)} = 7.96 \times 10^{-4} \text{ s} = (R_{S1} + R_{TH})C_C$$

or

$$C_C = \frac{7.96 \times 10^{-4}}{(200 + 36 \times 10^3)} \Rightarrow C_C = 220 \mu\text{F}$$

$$\tau_2 = \frac{1}{2\pi f_2} = \frac{1}{2\pi(3 \times 10^3)} = 5.31 \times 10^{-5} \text{ s} = R_D C_L$$

or


$$C_L = \frac{5.31 \times 10^{-5}}{20 \times 10^3} \Rightarrow C_L = 2.66 \text{ nF}$$

7.18

a.  $T(s) = \frac{R_2 + (1/s)C}{R_2 + (1/s)C + R_1}$

$$T(s) = \frac{1 + sR_2C}{1 + s(R_1 + R_2)C}$$

$$\tau_A = R_2C, \tau_B = (R_1 + R_2)C$$

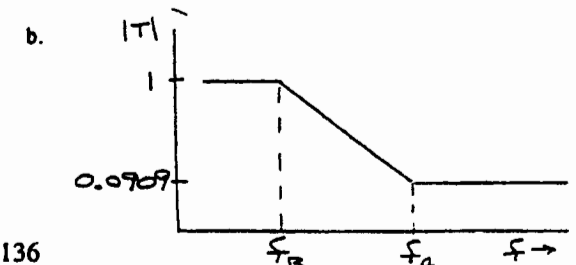

c.  $\tau_A = R_2 C = (10^3)(100 \times 10^{-12}) = 10^{-7} \text{ s} = \tau_A$

$\tau_B = (R_1 + R_2)C = [10 + 1] \times 10^3 \times 100 \times 10^{-12}$   
 $= 1.1 \times 10^{-6} \text{ s} = \tau_B$

$f_A \approx \frac{1}{2\pi\tau_A} = \frac{1}{2\pi(10^{-7})} \Rightarrow f_A = 1.59 \text{ MHz}$

$f_B \approx \frac{1}{2\pi\tau_B} = \frac{1}{2\pi(1.1 \times 10^{-6})}$   
 $\Rightarrow f_B = 0.145 \text{ MHz}$

7.19

$I_{BQ} = \frac{10 - 0.7}{430 + (201)(2.5)} = 0.00997 \text{ mA}$

$I_{CQ} = (200)I_{BQ} = 1.99 \text{ mA}$

$r_\pi = \frac{(200)(0.026)}{1.99} = 2.61 \text{ k}\Omega$

$R_{ib} = 2.61 + (201)(2.5) = 505 \text{ k}\Omega$

$\tau_s = \frac{1}{2\pi f_L} = \frac{1}{2\pi(15)} = 0.0106 \text{ s}$

$= R_{eq} C_C = (0.5 + 505 \parallel 430) \times 10^3 C_C = 232.7 \times 10^3 C_C$

Or

$C_C = 4.56 \times 10^{-8} \text{ F} \Rightarrow 45.6 \text{ nF}$

7.20

$R_{TH} = R_1 \parallel R_2 = 1.2 \parallel 1.2 = 0.6 \text{ k}\Omega$

$V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right) (V_{CC}) = \left( \frac{1.2}{1.2 + 1.2} \right) (5) = 2.5 \text{ V}$

$I_{BQ} = \frac{2.5 - 0.7}{0.6 + (101)(0.05)} = 0.319 \text{ mA}$

$I_{CQ} = 31.9 \text{ mA}$

$r_\pi = \frac{(100)(0.026)}{31.9} = 0.0815 \text{ k}\Omega$

$\tau_{C_{C1}} \gg \tau_{C_{C2}}$  and  $f = \frac{1}{2\pi\tau}$  so that

$f_{3-dB}(C_{C1}) \ll f_{3-dB}(C_{C2})$

Then, for  $f_{3-dB}(C_{C1}) \Rightarrow C_{C2}$  acts as an open and for

$f_{3-dB}(C_{C2}) \Rightarrow C_{C1}$  acts as a short circuit.

$f_{3-dB}(C_{C2}) = 25 \text{ Hz} = \frac{1}{2\pi\tau_2}$ , so that

$\tau_2 = \frac{1}{2\pi(25)} = 0.00637 \text{ s} = R_{eq} C_{C2}$

where  $R_{eq} = R_L + R_E \left\| \left( \frac{r_\pi + R_1 \parallel R_2 \parallel R_3}{1 + \beta} \right) \right\|$

$= 10 + 50 \left\| \left( \frac{815 + 600 \parallel 300}{101} \right) \right\| = 10 + 50 \parallel 2.79 \Rightarrow$

$R_{eq} = 12.6 \Omega \Rightarrow C_{C2} = \frac{0.00637}{12.6} \Rightarrow C_{C2} = 506 \mu\text{F}$

$R_{ib} = r_\pi + (1 + \beta)R_E$  Assume  $C_{C2}$  an open

$R_{ib} = 815 + (101)(50) = 5132 \Omega$

$\tau_1 = (100)\tau_2 = (100)(0.00637) = 0.637 \text{ s} = R_{eq1} C_{C1}$

$R_{eq1} = R_S + R_{TH} \parallel R_{ib} = 300 + 600 \parallel 5132 = 837 \Omega$

So  $C_{C1} = \frac{0.637}{837} \Rightarrow C_{C1} = 761 \mu\text{F}$

7.21

a.  $I_D = K_n (V_{GS} - V_{TN})^2$

$V_{GS} = \sqrt{\frac{I_D}{K_n}} + V_{TN} = \sqrt{\frac{0.5}{0.5}} + 0.8 = 1.8 \text{ V}$

$R_S = \frac{-V_{GS} - (-5)}{0.5} = \frac{5 - 1.8}{0.5} \Rightarrow R_S = 6.4 \text{ k}\Omega$

$V_D = V_{DSQ} + V_S = 4 - 1.8 = 2.2 \text{ V}$

$R_D = \frac{5 - 2.2}{0.5} \Rightarrow R_D = 5.6 \text{ k}\Omega$

(b)  $g_m = 2\sqrt{K_n I_D} = 2\sqrt{(0.5)(0.5)} = 1 \text{ mA/V}$

From Problem 7.20,

$\tau_A = R_S C_S = (6.4 \times 10^3)(5 \times 10^{-6})$   
 $= 3.2 \times 10^{-2} \text{ s}$

$f_A = \frac{1}{2\pi\tau_A} = \frac{1}{2\pi(3.2 \times 10^{-2})} \Rightarrow f_A = 4.97 \text{ Hz}$

$\tau_B = \left( \frac{R_S}{1 + g_m R_S} \right) C_S = \left[ \frac{6.4 \times 10^3}{1 + (1)(6.4)} \right] (5 \times 10^{-6})$   
 $= 4.32 \times 10^{-3} \text{ s}$

$f_B = \frac{1}{2\pi\tau_B} = \frac{1}{2\pi(4.32 \times 10^{-3})} \Rightarrow f_B = 36.8 \text{ Hz}$

c.

$|A_v| = \frac{g_m R_D (1 + s R_S C_S)}{(1 + g_m R_S) \left[ 1 + s \left( \frac{R_S}{1 + g_m R_S} \right) C_S \right]}$

As  $R_S$  becomes large

$|A_v| \rightarrow \frac{g_m R_D (s R_S C_S)}{(g_m R_S) \left[ 1 + s \left( \frac{R_S}{g_m R_S} \right) C_S \right]}$

$A_v = \frac{(g_m R_D) \left[ s \left( \frac{1}{g_m} \right) C_S \right]}{1 + s \left( \frac{1}{g_m} \right) C_S}$

The corner frequency  $f_B = \frac{1}{2\pi(1/g_m)C_S}$  and the

corresponding  $f_A \rightarrow 0$

$$g_m = 2\sqrt{K_n I_D} = 2\sqrt{(0.5)(0.5)} = 1 \text{ mA/V}$$

$$f_B = \frac{1}{2\pi\left(\frac{1}{10^{-3}}\right)(5 \times 10^{-6})} \Rightarrow f_B = 31.8 \text{ Hz}$$

7.22

a.  $f_B = \frac{1}{2\pi\tau_B}$

and  $\tau_B = \frac{R_E(R_S + r_\pi)C_E}{R_S + r_\pi + (1 + \beta)R_E}$

For  $R_S = 0$   $\tau_B = \frac{R_E r_\pi C_E}{r_\pi + (1 + \beta)R_E}$

$$I_{EQ} = \frac{-0.7 - (-10)}{5} = 1.86 \text{ mA}$$

$$\beta = 75 \Rightarrow I_{CQ} = 1.84 \text{ mA}$$

$$\beta = 125 \Rightarrow I_{CQ} = 1.85 \text{ mA}$$

For  $f_B \leq 200 \text{ Hz}$

$$\Rightarrow \tau_B \geq \frac{1}{2\pi(200)} = 0.796 \text{ ms}$$

$r_\pi \propto \beta$  so smallest  $\tau_B$  will occur for smallest  $\beta$ .

$$\beta = 75; r_\pi = \frac{(75)(0.026)}{1.84} = 1.06 \text{ k}\Omega$$

$$0.796 \times 10^{-3} = \frac{(5 \times 10^3)(1.06)C_E}{1.06 + (76)(5)}$$

$$\Rightarrow C_E = 57.2 \text{ }\mu\text{F}$$

b. For  $\beta = 125$ ;  $r_\pi = \frac{(125)(0.026)}{1.85} = 1.76 \text{ k}\Omega$

$$\tau_B = \frac{(5 \times 10^3)(1.76)(57.2 \times 10^{-6})}{1.76 + (126)(5)} = 0.797 \text{ ms}$$

$$f_B = \frac{1}{2\pi\tau_B} = \frac{1}{2\pi(0.797 \times 10^{-3})}$$

$$\Rightarrow f_B = 199.7 \text{ Hz Essentially independent of } \beta.$$

$$\tau_A = R_E C_E = (5 \times 10^3)(57.2 \times 10^{-6}) = 0.286 \text{ sec}$$

$$f_A = \frac{1}{2\pi\tau_A} = \frac{1}{2\pi(0.286)}$$

$$\Rightarrow f_A = 0.556 \text{ Hz Independent of } \beta.$$

7.23

a. Expression for the voltage gain is the same as Equation (7.58) with  $R_S = 0$ .

b.  $\tau_A = R_E C_E$

$$\tau_B = \frac{R_E r_\pi C_E}{r_\pi + (1 + \beta)R_E}$$

7.24

$$\tau_H = (R_L \parallel R_C)C_L = (10 \parallel 5) \times 10^3 \times 15 \times 10^{-12}$$

$$\tau_H = 5 \times 10^{-8} \text{ s}$$

$$f_H = \frac{1}{2\pi\tau_H} = \frac{1}{2\pi(5 \times 10^{-8})} \Rightarrow f_H = 3.18 \text{ MHz}$$

$$I_{EQ} = \frac{10 - 0.7}{10} = 0.93 \text{ mA}, I_{CQ} = 0.921 \text{ mA}$$

$$g_m = \frac{0.921}{0.026} = 35.4 \text{ mA/V}$$

$$A_v = g_m(R_C \parallel R_L) = 35.4(5 \parallel 10) \Rightarrow A_v = 118$$

7.25

$$V_G = \left(\frac{R_2}{R_1 + R_2}\right)V_{DD} = \left(\frac{166}{166 + 234}\right)(10) = 4.15 \text{ V}$$

$$I_D = \frac{V_G - V_{GS}}{R_S} = K_n(V_{GS} - V_{TN})^2$$

$$4.15 - V_{GS} = (0.5)(0.5)(V_{GS}^2 - 4V_{GS} + 4)$$

$$0.25V_{GS}^2 - 3.15 = 0 \Rightarrow V_{GS} = 3.55 \text{ V}$$

$$g_m = 2K_n(V_{GS} - V_{TN}) = 2(0.5)(3.55 - 2)$$

$$g_m = 1.55 \text{ mA/V}$$

$$R_0 = R_S \parallel \frac{1}{g_m} = 0.5 \parallel \frac{1}{1.55} = 0.5 \parallel 0.645$$

$$R_0 = 0.282 \text{ k}\Omega$$

$$\tau = (R_0 \parallel R_L)C_L \text{ and } f_H = \frac{1}{2\pi\tau}$$

$$\beta\omega \approx f_H = 5 \text{ MHz}$$


$$\Rightarrow \tau = \frac{1}{2\pi(5 \times 10^6)} = 3.18 \times 10^{-8} \text{ s}$$

$$C_L = \frac{\tau}{R_0 \parallel R_L} = \frac{3.18 \times 10^{-8}}{(0.282 \parallel 4) \times 10^3}$$


$$\Rightarrow C_L = 121 \text{ pF}$$

7.26


(a) Low-frequency

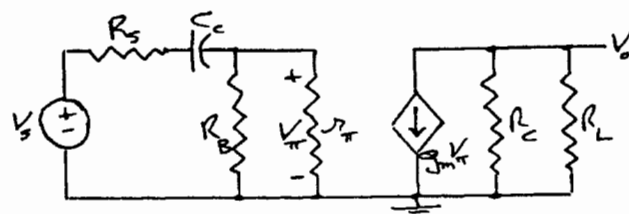


Mid-Band

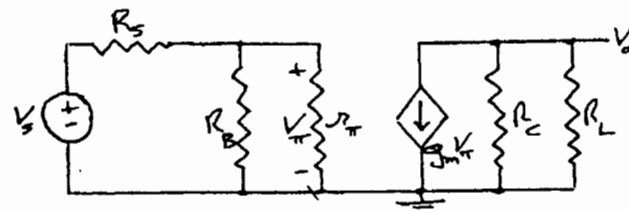

High-frequency

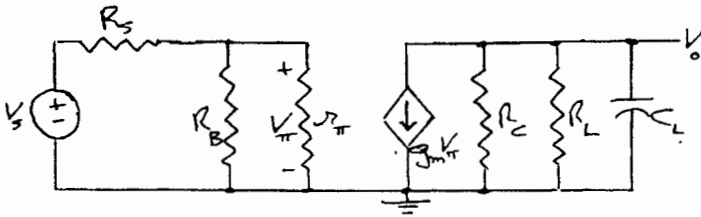

(b)

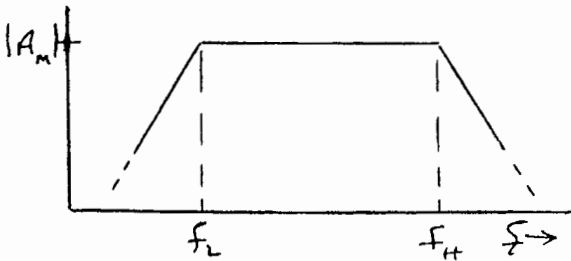

$$(c) I_{BQ} = \frac{12 - 0.7}{1 \text{ M}\Omega} = 11.3 \mu\text{A}$$

$$I_{CQ} = 1.13 \text{ mA}$$

$$r_x = \frac{(100)(0.026)}{1.13} = 2.3 \text{ k}\Omega$$

$$g_m = \frac{1.13}{0.026} = 43.46 \text{ mA/V}$$

$$A_m = \frac{V_o}{V_i} (\text{midband}) = -g_m (R_C \parallel R_L) \left( \frac{R_B \parallel r_x}{R_B \parallel r_x + R_s} \right)$$

$$= -(43.46)(5.1 \parallel 500) \left( \frac{1000 \parallel 2.3}{1000 \parallel 2.3 + 1} \right)$$

$$= -(43.46)(5.05) \left( \frac{2.29}{2.29 + 1} \right) \Rightarrow |A_m| = 153$$

$$|A_m|_{dB} = 43.7 \text{ dB}$$

$$f_L = \frac{1}{2\pi\tau_L}, \quad \tau_L = (R_s + R_B \parallel r_x)C_C$$

or

$$\tau_L = (1 + 1000 \parallel 2.3) \times 10^3 (10 \times 10^{-6}) \Rightarrow$$


$$\tau_L = 3.29 \times 10^{-2} \text{ s} \Rightarrow f_L = 4.84 \text{ Hz}$$

$$f_H = \frac{1}{2\pi\tau_H}, \quad \tau_H = (R_C \parallel R_L)C_L \Rightarrow$$

$$\tau_H = (5.1 \parallel 500) \times 10^3 (10 \times 10^{-12}) = 5.05 \times 10^{-8} \text{ s}$$

$$\Rightarrow f_H = 3.15 \text{ MHz}$$

7.27

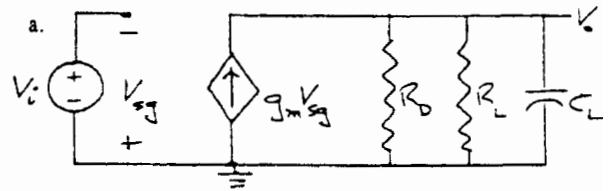

$$V_o = (g_m V_{be}) \left( R_C \parallel R_L \parallel \frac{1}{sC_L} \right)$$

$$V_{be} = -V_i$$

$$A_v(s) = \frac{V_o(s)}{V_i(s)} = -g_m \left( R_C \parallel R_L \parallel \frac{1}{sC_L} \right)$$

$$= -g_m \left[ \frac{R_C \parallel R_L \cdot \frac{1}{sC_L}}{R_C \parallel R_L + \frac{1}{sC_L}} \right]$$

$$A_v(s) = -g_m (R_C \parallel R_L) \cdot \frac{1}{1 + s(R_C \parallel R_L)C_L}$$

b.  $\tau = (R_C \parallel R_L)C_L$

c.  $\tau = (10 \parallel 20) \times 10^3 \times 10 \times 10^{-12}$

$$\Rightarrow \tau = 6.67 \times 10^{-8} \text{ s}$$

$$f_H = \frac{1}{2\pi\tau} = \frac{1}{2\pi(6.67 \times 10^{-8})}$$

$$\Rightarrow f_H = 2.39 \text{ MHz}$$

From Example 7.6,  $g_m = 0.705 \text{ mA/V}$

$$|A_v| = g_m (R_C \parallel R_L) = (0.705)(10 \parallel 20)$$

$$\Rightarrow |A_v| = 4.7$$

7.31

$$f_T = \frac{g_m}{2\pi(C_\pi + C_\mu)}$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{1}{0.026} = 38.5 \text{ mA/V}$$

$$f_T = \frac{38.5 \times 10^{-3}}{2\pi(10 + 2) \times 10^{-12}}$$

$$f_T = 511 \text{ MHz}$$

$$f_\beta = \frac{f_T}{\beta} = \frac{511}{120} \Rightarrow f_\beta = 4.26 \text{ MHz}$$

7.32

$$f_\beta = \frac{f_T}{\beta} = \frac{5000 \text{ MHz}}{150} \Rightarrow f_\beta = 33.3 \text{ MHz}$$

$$f_T = \frac{g_m}{2\pi(C_\pi + C_\mu)}$$

$$g_m = \frac{0.5}{0.026} = 19.2 \text{ mA/V}$$

$$5 \times 10^9 = \frac{19.2 \times 10^3}{2\pi(C_\pi + 0.15) \times 10^{-12}}$$

$$C_\pi + 0.15 = \frac{19.2 \times 10^3}{2\pi(10^{-12})(5 \times 10^9)} = 0.611 \text{ pF}$$

$$C_\pi = 0.461 \text{ pF}$$

7.33

a.  $f_\beta = \frac{f_T}{\beta} = \frac{2000 \text{ MHz}}{150} = 13.3 \text{ MHz} = f_\beta$

b.  $h_{fe} = \frac{150}{1 + j(f/f_\beta)}$

$$|h_{fe}| = \frac{150}{\sqrt{1 + (f/f_\beta)^2}} = 10$$

$$1 + \left(\frac{f}{f_\beta}\right)^2 = \left(\frac{150}{10}\right)^2 = 225$$

$$f = f_\beta \cdot \sqrt{224} = (13.3)\sqrt{224}$$

$$\Rightarrow f = 199 \text{ MHz}$$

7.34

(a)  $V_o = -g_m V_\pi R_L$  where

$$V_\pi = \frac{r_\pi \parallel \frac{1}{sC_1}}{r_\pi \parallel \frac{1}{sC_1} + r_b} \cdot V_i = \frac{\frac{r_\pi}{1 + sr_\pi C_1}}{\frac{r_\pi}{1 + sr_\pi C_1} + r_b} \cdot V_i$$

$$= \frac{r_\pi}{r_\pi + r_b + sr_\pi r_b C_1} \cdot V_i = \left(\frac{r_\pi}{r_\pi + r_b}\right) \left(\frac{1}{1 + s(r_b \parallel r_\pi)C_1}\right) \cdot V_i$$

So

$$A_v(s) = \frac{V_o(s)}{V_i(s)} = -g_m R_L \left(\frac{r_\pi}{r_\pi + r_b}\right) \left(\frac{1}{1 + s(r_b \parallel r_\pi)C_1}\right)$$

(b) Midband gain:

$$r_\pi = \frac{(100)(0.026)}{1} = 2.6 \text{ k}\Omega$$

$$g_m = \frac{1}{0.026} = 38.46 \text{ mA/V}$$

(i) For  $r_b = 100 \Omega$

$$A_{v1} = -(38.46)(4) \left(\frac{2.6}{2.6 + 0.1}\right) \Rightarrow A_{v1} = -148.1$$

(ii) For  $r_b = 500 \Omega$

$$A_{v2} = -(38.46)(4) \left(\frac{2.6}{2.6 + 0.5}\right) \Rightarrow A_{v2} = -129.0$$

(c)  $f_{3-dB} = \frac{1}{2\pi\tau}$ ,  $\tau = (r_b \parallel r_\pi)C_1$

(i) For  $r_b = 100 \Omega$

$$\tau_1 = (0.1 \parallel 2.6) \times 10^3 (2.2 \times 10^{-12}) = 2.12 \times 10^{-10} \text{ s}$$

$$\Rightarrow f_{3-dB} = 751 \text{ MHz}$$

(ii) For  $r_b = 500 \Omega$


$$\tau_2 = (0.5 \parallel 2.3) \times 10^3 (2.2 \times 10^{-12}) = 9.04 \times 10^{-10} \text{ s}$$

$$f_{3-dB} = 176 \text{ MHz}$$

7.35

a.  $C_M = C_\mu(1 + g_m R_L)$

b.

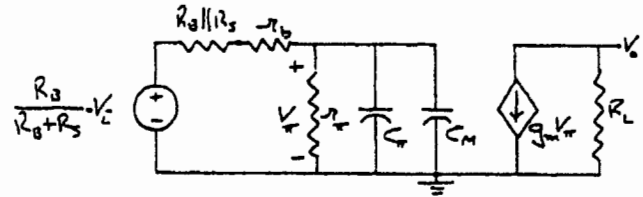

$$V_o = -g_m V_\pi R_L \quad \text{Let } C_\pi + C_M = C_i$$

$$V_\pi = \frac{r_\pi \parallel \frac{1}{sC_i}}{r_\pi \parallel \frac{1}{sC_i} + R_B \parallel R_S + r_b} \cdot \left(\frac{R_B}{R_B + R_S}\right) V_i$$

$$A_v(s) = \frac{V_o(s)}{V_i(s)}$$

$$= -g_m R_L \left(\frac{R_B}{R_B + R_S}\right) \left[ \frac{\frac{r_\pi \parallel \frac{1}{sC_i}}{r_\pi + \frac{1}{sC_i}}}{\frac{r_\pi \parallel \frac{1}{sC_i}}{r_\pi + \frac{1}{sC_i}} + R_B \parallel R_S + r_b} \right]$$

$$= -g_m R_L \left(\frac{R_B}{R_B + R_S}\right) \times \left[ \frac{r_\pi}{r_\pi + (1 + sr_\pi C_i)(R_B \parallel R_S + r_b)} \right]$$

$$\text{Let } R_{eq} = (R_B \parallel R_S + r_b)$$

$$A_v(s) = -\beta R_L \left(\frac{R_B}{R_B + R_S}\right)$$


$$\times \left[ \frac{1}{(r_\pi + R_{eq})[1 + s(r_\pi \parallel R_{eq})C_i]} \right]$$

$$A_v(s) = \frac{-\beta R_L}{r_\pi + R_{eq}} \cdot \left(\frac{R_B}{R_B + R_S}\right) \cdot \frac{1}{1 + s(r_\pi \parallel R_{eq})C_i}$$

c.  $f_H = \frac{1}{2\pi(r_\pi \parallel R_{eq})C_i}$

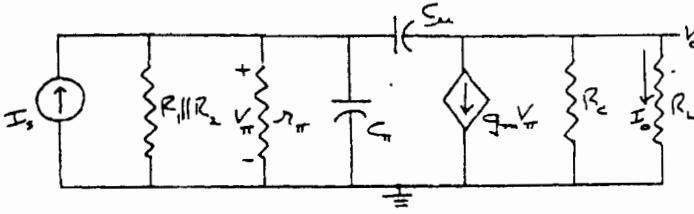7.36

High Freq.  $\Rightarrow C_{C1}, C_{C2}, C_E \rightarrow$  short circuits



$$g_m = \frac{I_{CQ}}{V_T} = \frac{5}{0.026} = 192 \text{ mA/V}$$

$$f_T = \frac{g_m}{2\pi(C_\pi + C_\mu)} \Rightarrow 250 \times 10^6 = \frac{192 \times 10^{-3}}{2\pi(C_\pi + C_\mu)}$$

$$C_\pi + C_\mu = 122 \text{ pF} \Rightarrow C_\mu = 5 \text{ pF}, C_\pi = 117 \text{ pF}$$

$$C_M = C_\mu(1 + g_m(R_C \parallel R_L))$$

$$= 5[1 + (192)(1 \parallel 1)] \Rightarrow C_M = 485 \text{ pF}$$

$$C_i = C_\pi + C_M = 117 + 485 = 602 \text{ pF}$$

$$r_\pi = \frac{(200)(0.026)}{5} = 1.04 \text{ k}\Omega$$

$$R_{eq} = R_1 \parallel R_2 \parallel r_\pi = 5 \parallel 1.04 = 0.861 \text{ k}\Omega$$

$$\tau = R_{eq} \cdot C_i = (0.861 \times 10^3)(602 \times 10^{-12}) = 5.18 \times 10^{-7} \text{ s}$$

$$f = \frac{1}{2\pi\tau} = \frac{1}{2\pi(5.18 \times 10^{-7})} \Rightarrow f = 307 \text{ kHz}$$

7.37

$$R_{TH} = R_1 \parallel R_2 = 60 \parallel 5.5 = 5.04 \text{ k}\Omega$$

$$V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right) V_{CC} = \left( \frac{5.5}{5.5 + 60} \right) (15) = 1.26 \text{ V}$$

$$I_{BQ} = \frac{1.26 - 0.7}{5.04 + (101)(0.2)} = 0.0222 \text{ mA}$$

$$I_{CQ} = 2.22 \text{ mA}$$

$$r_\pi = \frac{(100)(0.026)}{2.22} = 1.17 \text{ k}\Omega$$

$$g_m = \frac{2.22}{0.026} = 85.4 \text{ mA/V}$$

Lower 3 - dB frequency:

$$\tau_L = R_{eq} \cdot C_{C1}$$

$$R_{eq} = R_S + R_1 \parallel R_2 \parallel r_\pi$$

$$= 2 + 60 \parallel 5.5 \parallel 1.17 = 2.95 \text{ k}\Omega$$

$$\tau_L = (2.95 \times 10^3)(0.1 \times 10^{-6}) = 2.95 \times 10^{-4} \text{ s}$$

$$f_L = \frac{1}{2\pi\tau_L} = \frac{1}{2\pi(2.95 \times 10^{-4})} \Rightarrow f_L = 540 \text{ Hz}$$

Upper 3 - dB frequency:

$$f_T = \frac{g_m}{2\pi(C_\pi + C_\mu)} \Rightarrow 400 \times 10^6 = \frac{85.4 \times 10^{-3}}{2\pi(C_\pi + C_\mu)}$$

$$C_\pi + C_\mu = 34 \text{ pF}; C_\mu = 2 \text{ pF} \Rightarrow C_\pi = 32 \text{ pF}$$

$$C_M = C_\mu(1 + g_m R_C) = 2(1 + (85.4)(4))$$

$$\Rightarrow C_M = 685 \text{ pF}$$

$$C_i = C_\pi + C_M = 32 + 685 = 717 \text{ pF}$$

$$R_{eq} = R_S \parallel R_1 \parallel R_2 \parallel r_\pi = 2 \parallel 60 \parallel 5.5 \parallel 1.17 = 0.644 \text{ k}\Omega$$

$$\tau = R_{eq} \cdot C_i = (0.644 \times 10^3)(717 \times 10^{-12}) = 4.62 \times 10^{-7} \text{ s}$$

$$f_H = \frac{1}{2\pi\tau} \Rightarrow f_H = 344 \text{ kHz}$$

7.38

$$f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$

$$g_m = 2\sqrt{K_n I_D}, K_n = (15) \left( \frac{40}{10} \right) = 60 \mu\text{A/V}^2$$

$$g_m = 2\sqrt{(60)(100)} = 155 \mu\text{A/V}^2$$

$$f_T = \frac{155 \times 10^{-6}}{2\pi(0.5 + 0.05) \times 10^{-12}} \Rightarrow f_T = 44.9 \text{ MHz}$$

7.39

a.  $C_M = C_{gs} (1 + g_m(\tau_o \parallel R_D))$

$$C_M = 5[1 + (3)(15 \parallel 10)] \Rightarrow C_M = 95 \text{ pF}$$

b.  $\tau = (\tau_o)(C_{gs} + C_M)$

$$\tau = (10 \times 10^3)(50 + 95) \times 10^{-12} = 1.45 \times 10^{-6} \text{ s}$$

$$f = \frac{1}{2\pi\tau} = \frac{1}{2\pi(1.45 \times 10^{-6})}$$

$$\Rightarrow f = 110 \text{ kHz}$$

7.40

$$f_T = \frac{g_m}{2\pi(C_{gsT} + C_{gdT})} \quad (\text{Eq. 7.90})$$

Let  $C_{gdT} = 0$  and  $C_{gsT} = \left( \frac{2}{3} \right) (WLC_{ox})$

$$g_m = 2\sqrt{K_n I_D} = 2\sqrt{\left( \frac{\mu_n C_{ox}}{2} \right) \left( \frac{W}{L} \right) I_D}$$

$$\text{So } f_T = \frac{2\sqrt{\left(\frac{1}{2}\mu_n C_{ox}\right)\left(\frac{W}{L}\right)I_D}}{2\pi\left(\frac{2}{3}\right)(WLC_{ox})}$$

$$= \frac{3}{2\pi L} \sqrt{\left(\frac{1}{2}\mu_n C_{ox}\right)\left(\frac{W}{L}\right)I_D}$$

$$f_T = \frac{3}{2\pi L} \sqrt{\frac{\mu_n I_D}{2WC_{ox}L}}$$

7.41

(a)  $g'_m = \frac{g_m}{1 + g_m r_s}$

$g_m = 2K_n(V_{GS} - V_{TN})$

$K_n = \left(\frac{\mu_n C_{ox}}{2}\right)\left(\frac{W}{L}\right) = \left(\frac{(400)(7.25 \times 10^{-8})}{2}\right)$  (10)

$K_n = 1.45 \times 10^{-4} \text{ mA/V}^2$

For  $V_{GS} = 5 \text{ V}$

$g_m = 2(1.45 \times 10^{-4})(5 - 0.65) = 1.26 \times 10^{-3}$

$g'_m = (0.80)g_m = 1.01 \times 10^{-3}$

$1.01 \times 10^{-3} = \frac{1.26 \times 10^{-3}}{1 + (1.26 \times 10^{-3})r_s}$

$1 + (1.26 \times 10^{-3})r_s = 1.25$

$\Rightarrow r_s = 198 \Omega$

b. For  $V_{GS} = 3 \text{ V}$

$g_m = 2(1.45 \times 10^{-4})(3 - 0.65) = 0.6815 \times 10^{-3}$


$g'_m = \frac{0.6815 \times 10^{-3}}{1 + (0.6815 \times 10^{-3})(198)}$

$g'_m = 0.60 \times 10^{-3} \text{ A/V}$

Reduced by  $\approx 12\%$

7.42

a.

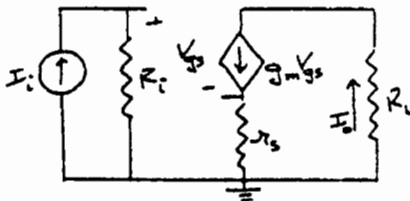


$I_o = g_m V_{gs}$  and  $V_{gs} = I_i R_i - g_m V_{gs} r_s$

so  $V_{gs} = \frac{I_i R_i}{1 + g_m r_s}$

Then  $A_i = \frac{I_o}{I_i} = \frac{g_m R_i}{1 + g_m r_s}$

b. As an approximation, consider

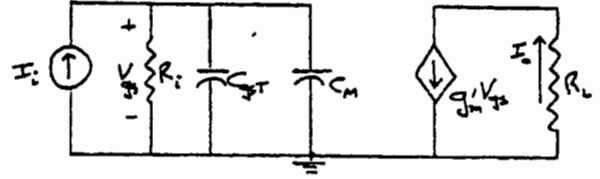

In this case

$A_i = \frac{I_o}{I_i} = g'_m R_i \cdot \frac{1}{1 + sR_i(C_{gsT} + C_M)}$

where  $C_M = C_{gdT}(1 + g'_m R_L)$  and  $g'_m = \frac{g_m}{1 + g_m r_s}$

c. As  $r_s$  increases,  $C_M$  decreases, so the bandwidth increases, but the current gain magnitude decreases.

7.43


$V_{GS} = \left(\frac{R_2}{R_1 + R_2}\right)V_{DD} = \left(\frac{225}{225 + 500}\right)$  (10)

$V_{GS} = 3.10 \text{ V}$

$g_m = 2K_n(V_{GS} - V_{TN}) = 2(1)(3.10 - 2)$

$g_m = 2.2 \text{ mA/V}$

a.

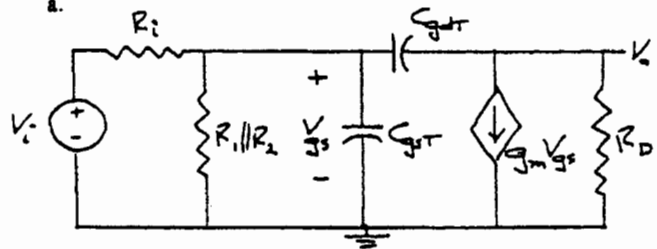

b.  $C_M = C_{gdT}(1 + g_m R_D) = (1)[1 + (2.2)(5)]$

$C_M = 12 \text{ pF}$

c.  $\tau = (R_i \parallel R_1 \parallel R_2)(C_{gsT} + C_M)$

$R_i \parallel R_1 \parallel R_2 = 1 \parallel 500 \parallel 225 = 1 \parallel 155 = 0.994 \text{ k}\Omega$

$\tau = (0.994 \times 10^3)(5 + 12) \times 10^{-12} = 1.69 \times 10^{-8} \text{ s}$

$f_H = \frac{1}{2\pi\tau} = \frac{1}{2\pi(1.69 \times 10^{-8})} \Rightarrow f_H = 9.42 \text{ MHz}$

$A_v = \frac{-g_m V_{gs} R_D}{V_i}$  and

$V_{gs} = \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_i} \cdot V_i = \frac{155}{155 + 1} \cdot V_i = 0.994 V_i$

$A_v = -(2.2)(5)(0.994) \Rightarrow A_v = -10.9$

7.44

$$R_{TH} = R_1 \parallel R_2 = 33 \parallel 22 = 13.2 \text{ k}\Omega$$

$$V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right) (5) = \left( \frac{22}{22 + 33} \right) (5) = 2 \text{ V}$$

$$I_{BQ} = \frac{2 - 0.7}{13.2 + (121)(4)} = 0.00261 \text{ mA}$$

$$I_{CQ} = 0.314 \text{ mA}$$

$$r_\pi = \frac{(120)(0.026)}{0.314} = 9.94 \text{ k}\Omega$$

$$g_m = \frac{0.314}{0.026} = 12.1 \text{ mA/V}$$

$$r_o = \frac{100}{0.314} = 318 \text{ k}\Omega$$

$$a. \quad f_T = \frac{g_m}{2\pi(C_\pi + C_\mu)}$$

$$C_\pi + C_\mu = \frac{g_m}{2\pi f_T} = \frac{12.1 \times 10^{-3}}{2\pi(600 \times 10^6)}$$

$$C_\pi + C_\mu = 3.21 \text{ pF}; \quad C_\mu = 1 \text{ pF} \Rightarrow C_\pi = 2.21 \text{ pF}$$

$$C_M = C_\mu [1 + g_m(r_o \parallel R_C \parallel R_L)]$$

$$= (1)[1 + (12.1)(318 \parallel 4 \parallel 5)]$$

$$C_M = 27.7 \text{ pF}$$

$$b. \quad \tau = R_{eq}(C_\pi + C_M)$$

$$R_{eq} = R_1 \parallel R_2 \parallel R_S \parallel r_\pi = 33 \parallel 22 \parallel 2 \parallel r_\pi$$

$$= 1.74 \parallel 9.94 \text{ k}\Omega \Rightarrow R_{eq} = 1.48 \text{ k}\Omega$$

$$\tau = (1.48 \times 10^3)(2.21 + 27.7) \times 10^{-12}$$

$$\tau = 4.43 \times 10^{-8} \text{ s}$$

$$f_H = \frac{1}{2\pi\tau} = \frac{1}{2\pi(4.43 \times 10^{-8})}$$

$$\Rightarrow \underline{f_H = 3.59 \text{ MHz}}$$

$$V_o = -g_m V_\pi (r_o \parallel R_C \parallel R_L)$$

$$V_\pi = \left( \frac{R_1 \parallel R_2 \parallel r_\pi}{R_1 \parallel R_2 \parallel r_\pi + R_S} \right) V_i$$

$$R_1 \parallel R_2 \parallel r_\pi = 33 \parallel 22 \parallel 9.94 = 5.67 \text{ k}\Omega$$

$$V_\pi = \left( \frac{5.67}{5.67 + 2} \right) V_i = 0.739 V_i$$

$$r_o \parallel R_C \parallel R_L = 318 \parallel 4 \parallel 5 = 2.18 \text{ k}\Omega$$

$$A_v = -(12.1)(0.739)(2.18)$$

$$\underline{A_v = -19.5}$$

7.45

$$R_{TH} = R_1 \parallel R_2 = 40 \parallel 5 = 4.44 \text{ k}\Omega$$

$$V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right) V_{CC} = \left( \frac{5}{5 + 40} \right) (10) = 1.11 \text{ V}$$

$$I_{BQ} = \frac{1.11 - 0.7}{4.44 + (121)(0.5)} = 0.00631 \text{ mA}$$

$$I_{CQ} = 0.758 \text{ mA}$$

$$r_\pi = \frac{(120)(0.026)}{0.758} = 4.12 \text{ k}\Omega$$

$$g_m = \frac{0.758}{0.026} = 29.2 \text{ mA/V}$$

$$r_o = \infty$$

$$f_T = \frac{g_m}{2\pi(C_\pi + C_\mu)}$$

$$C_\pi + C_\mu = \frac{g_m}{2\pi f_T} = \frac{29.2 \times 10^{-3}}{2\pi(250 \times 10^6)}$$

$$C_\pi + C_\mu = 18.6 \text{ pF}; \quad C_\mu = 3 \text{ pF} \Rightarrow C_\pi = 15.6 \text{ pF}$$

$$a. \quad C_M = C_\mu [1 + g_m(R_C \parallel R_L)]$$

$$C_M = 3[1 + (29.2)(5 \parallel 2.5)] \Rightarrow C_M = 149 \text{ pF}$$

For upper frequency:

$$\tau_H = R_{eq}(C_\pi + C_M)$$

$$R_{eq} = r_\pi \parallel R_1 \parallel R_2 \parallel R_S = 4.12 \parallel 40 \parallel 5 \parallel 0.5$$

$$R_{eq} = 0.405 \text{ k}\Omega$$

$$\tau_H = (0.405 \times 10^3)(15.6 + 149) \times 10^{-12}$$

$$= 6.67 \times 10^{-8} \text{ s}$$

$$f_H = \frac{1}{2\pi\tau_H} \Rightarrow \underline{f_H = 2.39 \text{ MHz}}$$

For lower frequency:


$$\tau_L = R_{eq} C_{C1}$$

$$R_{eq} = R_S + R_1 \parallel R_2 \parallel r_\pi = 0.5 + 40 \parallel 5 \parallel 4.12$$

$$R_{eq} = 2.64 \text{ k}\Omega$$

$$\tau_L = (2.64 \times 10^3)(4.7 \times 10^{-6}) = 1.24 \times 10^{-2} \text{ s}$$
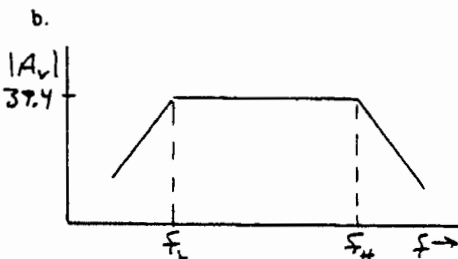
$$f_L = \frac{1}{2\pi\tau_L} \Rightarrow \underline{f_L = 12.8 \text{ Hz}}$$



$$V_o = -g_m V_\pi (R_C \parallel R_L)$$

$$V_\pi = \left( \frac{R_1 \parallel R_2 \parallel r_\pi}{R_1 \parallel R_2 \parallel r_\pi + R_S} \right) V_i$$

$$V_\pi = \left( \frac{2.14}{2.14 + 0.5} \right) V_i = 0.8106 V_i$$

$$|A_v| = (29.2)(0.8106)(5 \parallel 2.5)$$

$$\underline{|A_v| = 39.4}$$

7.46

$$I_D = K_p(V_{SG} + V_{TP})^2 = \frac{9 - V_{SG}}{R_S}$$

$$(2)(1.2)(V_{SG}^2 - 4V_{SG} + 4) = 9 - V_{SG}$$

$$2.4V_{SG}^2 - 8.6V_{SG} + 0.6 = 0$$

$$V_{SG} = \frac{8.6 \pm \sqrt{(8.6)^2 - 4(2.4)(0.6)}}{2(2.4)}$$

$$V_{SG} = 3.51 \text{ V}$$

$$g_m = 2K_p(V_{SG} + V_{TP}) = 2(2)(3.51 - 2)$$

$$g_m = 6.04 \text{ mA/V}$$

$$I_D = (2)(3.51 - 2)^2 = 4.56 \text{ mA}$$

$$r_o = \frac{1}{\lambda I_D} = \frac{1}{(0.01)(4.56)} \Rightarrow r_o = 21.9 \text{ k}\Omega$$

a.  $C_M = C_{gdT}(1 + g_m(r_o \parallel R_D))$   
 $C_M = (1)[1 + (6.04)(21.9 \parallel 1)] \Rightarrow C_M = 6.78 \text{ pF}$

b.  $\tau_H = (R_i \parallel R_G)(C_{gsT} + C_M)$   
 $\tau_H = (2 \parallel 100) \times 10^3(10 + 6.78) \times 10^{-12}$   
 $\tau_H = 3.29 \times 10^{-8} \text{ s}$   
 $f_H = \frac{1}{2\pi\tau_H} \Rightarrow f_H = 4.84 \text{ MHz}$

$$V_o = -g_m(r_o \parallel R_D) \cdot V_{gs}$$

$$V_{gs} = \left(\frac{R_G}{R_G + R_i}\right) V_i = \left(\frac{100}{102}\right) V_i$$

$$A_v = -(6.04) \left(\frac{100}{102}\right) (21.9 \parallel 1)$$

$$\underline{A_v = -5.66}$$

7.47

$$V_G = \left(\frac{R_2}{R_1 + R_2}\right)(20) - 10 = \left(\frac{22}{22 + 8}\right)(20) - 10$$

$$V_G = 4.67 \text{ V}$$

$$I_D = \frac{10 - V_{SG} - 4.67}{R_S} = K_p(V_{SG} + V_{TP})^2$$

$$5.33 - V_{SG} = (1)(0.5)(V_{SG}^2 - 4V_{SG} + 4)$$

$$0.5V_{SG}^2 - V_{SG} - 3.33 = 0$$

$$V_{SG} = \frac{1 \pm \sqrt{1 + 4(0.5)(3.33)}}{2(0.5)} \Rightarrow V_{SG} = 3.77 \text{ V}$$

$$g_m = 2K_p(V_{SG} + V_{TP}) = 2(1)(3.77 - 2)$$

$$g_m = 3.54 \text{ mA/V}$$

b.  $C_M = C_{gdT}(1 + g_m(R_D \parallel R_L))$

$$C_M = (3)[1 + (3.54)(2 \parallel 5)] \Rightarrow C_M = 18.2 \text{ pF}$$

a.  $\tau = R_{eq}(C_{gsT} + C_M)$

$$R_{eq} = R_i \parallel R_1 \parallel R_2 = 0.5 \parallel 8 \parallel 22 = 0.461 \text{ k}\Omega$$

$$\tau = (0.461 \times 10^3)(15 + 18.2) \times 10^{-12}$$

$$= 1.53 \times 10^{-8} \text{ s}$$

$$f_H = \frac{1}{2\pi\tau} \Rightarrow f_H = 10.4 \text{ MHz}$$

c.  $V_o = -g_m V_{gs}(R_D \parallel R_L)$

$$V_{gs} = \left(\frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_i}\right) V_i = \left(\frac{5.87}{5.87 + 0.5}\right) V_i$$

$$\Rightarrow V_{gs} = (0.9215) V_i$$

$$A_v = -(3.54)(0.9215)(2 \parallel 5)$$

$$\Rightarrow \underline{A_v = -4.66}$$

7.48

$$I_E = 0.5 \text{ mA} \Rightarrow I_{CQ} = \left(\frac{100}{101}\right)(0.5) = 0.495 \text{ mA}$$

$$g_m = \frac{0.495}{0.026} = 19.0 \text{ mA/V}$$

$$\tau_\pi = \frac{(100)(0.026)}{0.495} = 5.25 \text{ k}\Omega$$

a. Input: From Eq. 7.107b

$$\tau_{P\pi} = \left[\frac{\tau_\pi}{1 + \beta} \parallel R_E \parallel R_S\right] C_\pi$$

$$= \left[\frac{5.25}{101} \parallel 0.5 \parallel 0.05\right] \times 10^3 \times 10 \times 10^{-12}$$

$$= 2.43 \times 10^{-10} \text{ s}$$

$$f_{H\pi} = \frac{1}{2\pi\tau_{P\pi}} \Rightarrow f_{H\pi} = 656 \text{ MHz}$$


Output: From Eq. 7.108b

$$\tau_{P\mu} = (R_B \parallel R_L) C_\mu = (100 \parallel 1) \times 10^3 \times 10^{-12}$$

$$= 9.90 \times 10^{-10} \text{ s}$$

$$f_{H\mu} = \frac{1}{2\pi\tau_{P\mu}} \Rightarrow f_{H\mu} = 161 \text{ MHz}$$

b.

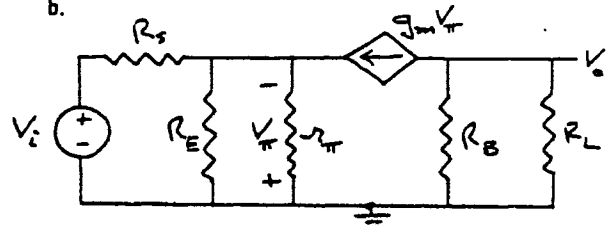

$$V_0 = -g_m V_\pi (R_B \parallel R_L)$$

$$g_m V_\pi + \frac{V_\pi}{r_\pi} + \frac{V_\pi}{R_E} + \frac{V_i - (-V_\pi)}{R_S} = 0$$

$$V_\pi \left[ g_m + \frac{1}{r_\pi} + \frac{1}{R_E} + \frac{1}{R_S} \right] = \frac{-V_i}{R_S}$$

$$V_\pi \left[ 19 + \frac{1}{5.25} + \frac{1}{0.5} + \frac{1}{0.05} \right] = \frac{-V_i}{0.05}$$

$$V_\pi (41.19) = -V_i (20)$$

$$V_\pi = -(0.4856)V_i$$

$$\frac{V_0}{V_i} = -(19)(-0.4856)(100 \parallel 1)$$

$$\underline{A_v = 9.14}$$

c.  $\tau = C_L (R_L \parallel R_B) = (15 \times 10^{-12})(1 \parallel 100) \times 10^3$

$$\tau = 1.485 \times 10^{-8} \text{ s}$$

$$f = \frac{1}{2\pi\tau} \rightarrow f = 10.7 \text{ MHz}$$

Since  $f < f_{H\mu} \Rightarrow 3\text{dB freq. dominated by } C_L$ .

7.49

$$I_{EQ} = \frac{20 - 0.7}{10} = 1.93 \text{ mA}$$

$$I_{CQ} = \left( \frac{100}{101} \right) (1.93) = 1.91 \text{ mA}$$

$$g_m = \frac{1.91}{0.026} = 73.5 \text{ mA/V}$$

$$\tau_\pi = \frac{(100)(0.026)}{1.91} = 1.36 \text{ k}\Omega$$

a. Input:

$$\tau_{P\pi} = \left[ \frac{\tau_\pi}{1 + \beta} \parallel R_E \parallel R_S \right] \cdot C_\pi$$

$$= \left[ \frac{1.36}{101} \parallel 10 \parallel 1 \right] \times 10^3 \times 10 \times 10^{-12}$$

$$\tau_{P\pi} = 1.327 \times 10^{-10} \text{ s}$$

$$f_{P\pi} = \frac{1}{2\pi\tau_{P\pi}} \Rightarrow \underline{f_{P\pi} = 1.20 \text{ GHz}}$$

output:

$$\tau_{P\mu} = (R_C \parallel R_L) C_\mu = (6.5 \parallel 5) \times 10^3 \times 10^{-12}$$

$$\tau_{P\mu} = 2.826 \times 10^{-9} \text{ s}$$

$$f_{P\mu} = \frac{1}{2\pi\tau_{P\mu}} \rightarrow \underline{f_{P\mu} = 56.3 \text{ MHz}}$$

b.  $V_0 = -g_m V_\pi (R_C \parallel R_L)$

$$g_m V_\pi + \frac{V_\pi}{r_\pi} + \frac{V_\pi}{R_E} + \frac{V_i - (-V_\pi)}{R_S} = 0$$

$$V_\pi \left( g_m + \frac{1}{r_\pi} + \frac{1}{R_E} + \frac{1}{R_S} \right) = -\frac{V_i}{R_S}$$

$$V_\pi \left[ 73.5 + \frac{1}{1.36} + \frac{1}{10} + \frac{1}{1} \right] = \frac{-V_i}{(1)}$$

$$V_\pi (75.34) = -V_i \Rightarrow V_\pi = -(0.01327)V_i$$

$$V_0 = -(73.5)(-0.01327)(6.5 \parallel 5)V_i$$

$$\underline{A_v = 2.76}$$

c.  $\tau = C_L (R_L \parallel R_C) = (15 \times 10^{-12})(6.5 \parallel 5) \times 10^3$

$$\tau = 4.24 \times 10^{-8} \text{ s}$$

$$f = \frac{1}{2\pi\tau} \rightarrow f = 3.75 \text{ MHz}$$

Since  $f < f_{P\mu}$ , 3dB frequency is dominated by  $C_L$ .

7.50

$$V_{GS} + I_D R_S = 5$$

$$I_D = \frac{5 - V_{GS}}{R_S} = K_n (V_{GS} - V_{TN})^2$$

$$5 - V_{GS} = (3)(10)(V_{GS}^2 - 2V_{GS} + 1)$$

$$30V_{GS}^2 - 59V_{GS} + 25 = 0$$

$$V_{GS} = \frac{59 \pm \sqrt{(59)^2 - 4(30)(25)}}{2(30)} \Rightarrow V_{GS} = 1.35 \text{ V}$$

$$g_m = 2K_n (V_{GS} - V_{TN}) = 2(3)(1.35 - 1)$$


$$g_m = 2.1 \text{ mA/V}$$

On the output:

$$\tau_{P\mu} = (R_D \parallel R_L) C_{gdT} = (5 \parallel 4) \times 10^3 \times 4 \times 10^{-12}$$

$$\tau_{P\mu} = 8.89 \times 10^{-9} \text{ s}$$
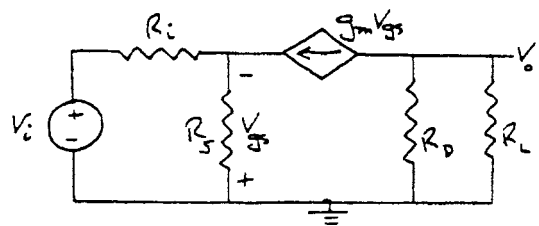
$$f_{P\mu} = \frac{1}{2\pi\tau_{P\mu}} \rightarrow \underline{f_{P\mu} = 17.9 \text{ MHz}}$$



$$V_0 = -g_m V_{gs} (R_D \parallel R_L)$$

$$g_m V_{gs} + \frac{V_{gs}}{R_S} + \frac{V_i - (-V_{gs})}{R_i} = 0$$

$$V_{gs} \left( g_m + \frac{1}{R_S} + \frac{1}{R_i} \right) = -\frac{V_i}{R_i}$$

$$V_{gs} \left( 2.1 + \frac{1}{10} + \frac{1}{2} \right) = -\frac{V_i}{2}$$

$$V_{gs} = -(0.185)V_i$$

$$A_v = \frac{V_0}{V_i} = (2.1)(0.185)(5 \parallel 4)$$

$$\underline{A_v = 0.863}$$

7.51

dc analysis

$$I_D = \frac{V^+ - V_{SG}}{R_S} = K_p(V_{SG} + V_{TP})^2$$

$$5 - V_{SG} = (1)(4)(V_{SG} - 0.8)^2$$


$$= 4(V_{SG}^2 - 1.6V_{SG} + 0.64)$$

$$4V_{SG}^2 - 5.4V_{SG} - 2.44 = 0$$

$$V_{SG} = \frac{5.4 \pm \sqrt{(5.4)^2 + 4(4)(2.44)}}{2(4)} = 1.707$$

$$g_m = 2K_p(V_{SG} + V_{TP}) = 2(1)(1.707 - 0.8)$$

$$g_m = 1.81 \text{ mA/V}$$

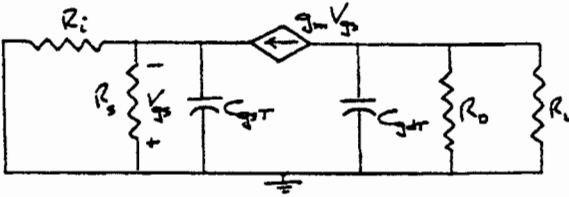

3 - dB frequency due to  $C_{gsT}$ :  $R_{eq} = \frac{1}{g_m} \parallel R_S \parallel R_i$

$$f_A = \frac{1}{2\pi R_{eq} \cdot C_{gsT}}$$

$$R_{eq} = \frac{1}{1.81} \parallel 4 \parallel 0.5 = 0.246 \text{ k}\Omega$$

$$f_A = \frac{1}{2\pi(246)(4 \times 10^{-12})} = 162 \text{ MHz}$$


3 - dB frequency due to  $C_{gdT}$

$$f_B = \frac{1}{2\pi(R_D \parallel R_L)C_{gdT}}$$

$$= \frac{1}{2\pi(2 \parallel 4) \times 10^3 \times 10^{-12}}$$

$$f = 119 \text{ MHz}$$

Midband gain

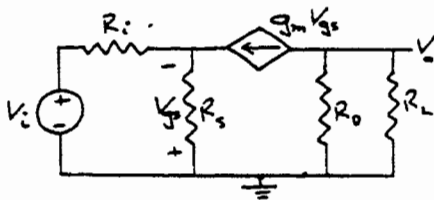

$$V_{gs} = \frac{-\frac{1}{g_m} \parallel R_S}{\frac{1}{g_m} \parallel R_S + R_i} \cdot V_i = \frac{-\frac{1}{1.81} \parallel 4}{\frac{1}{1.81} \parallel 4 + 0.5} \cdot V_i$$

$$= -0.492V_i$$

$$V_o = -g_m V_{gs} (R_D \parallel R_L)$$

$$A_v = (0.492)(1.81)(4 \parallel 2) \Rightarrow A_v = 1.19$$

7.52

$$r_\pi = \frac{(120)(0.026)}{1.02} = 3.06 \text{ k}\Omega$$

$$g_m = 39.2 \text{ mA/V}$$

a. Input:  $f_{H\pi} = \frac{1}{2\pi\tau_\pi}$

$$\tau_\pi = [R_S \parallel R_2 \parallel R_3 \parallel r_\pi](C_\pi + 2C_\mu)$$

$$= 0.1 \parallel 20.5 \parallel 28.3 \parallel 3.06 = 0.096 \text{ k}\Omega$$

$$\tau_\pi = (96)(12 + 2(2)) \times 10^{-12} = 1.536 \times 10^{-9} \text{ s}$$

$$f_{H\pi} = \frac{1}{2\pi(1.536 \times 10^{-9})} = 103.6 \text{ MHz}$$

Output:  $f_{H\mu} = \frac{1}{2\pi\tau_\mu}$

$$\tau_\mu = (R_C \parallel R_L)C_\mu$$

$$= (5 \parallel 10) \times 10^3 \times 2 \times 10^{-12}$$

$$= 6.67 \times 10^{-9}$$

$$f_{H\mu} = \frac{1}{2\pi(6.67 \times 10^{-9})} = 23.9 \text{ MHz}$$

b.  $A = g_m(R_C \parallel R_L) \left[ \frac{R_2 \parallel R_3 \parallel r_\pi}{R_2 \parallel R_3 \parallel r_\pi + R_S} \right]$

$$R_2 \parallel R_3 \parallel r_\pi = 20.5 \parallel 28.3 \parallel 3.06 = 2.43 \text{ k}\Omega$$

$$A = (39.2)(5 \parallel 10) \left[ \frac{2.43}{2.43 + 0.1} \right] \Rightarrow A = 125.5$$

c.  $C_L = 15 \text{ pF} > C_\mu \Rightarrow C_L$  dominates frequency response.

## Chapter 8

### Exercise Solutions

E8.1

For  $V_{DS} = 0$ ,  $I_D(\max) = \frac{24}{20} = 1.2 \text{ A} = I_D(\max)$

For  $I_D = 0 \Rightarrow V_{DS}(\max) = 24 \text{ V}$


Maximum power when

$$V_{DS} = \frac{V_{DS}(\max)}{2} = 12 \text{ V and}$$

$$I_D = \frac{I_D(\max)}{2} = 0.6 \text{ A}$$

$$\Rightarrow P_D(\max) = (12)(0.6) = 7.2 \text{ Watts}$$

E8.2

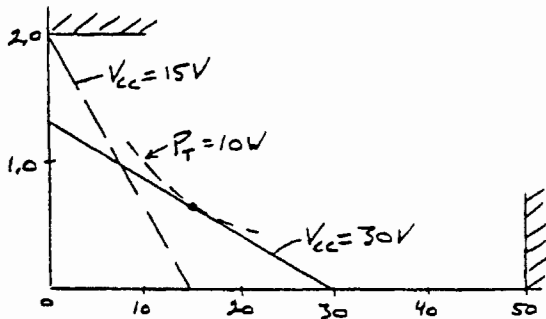

a.  $V_{CC} = 30 \text{ V}$ ,  $V_{CE} = 30 - I_C R_C$ ,  $I_C V_{CE} = 10$

Maximum power at  $V_{CE} = \frac{1}{2} V_{CC} = 15$

$$I_C = \frac{10}{V_{CE}} = \frac{10}{15} = \frac{2}{3}$$

So  $15 = 30 - \frac{2}{3} R_L \Rightarrow R_L = 22.5 \Omega$

$$\Rightarrow \text{Maximum Power} = 10 \text{ W}$$


b.  $V_{CC} = 15 \text{ V}$ ,  $I_{C,\max} = 2 \text{ A}$

$$V_{CE} = 15 - I_C R_L$$

$$0 = 15 - 2R_L \Rightarrow R_L = 7.5 \Omega$$

$$\Rightarrow \text{Maximum Power} = (1)(7.5) = 7.5 \text{ W}$$

E8.3

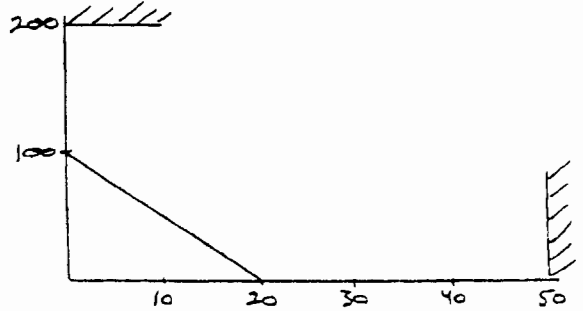

Maximum power at center of load line

$$P_{\max} = (0.05)(10) \Rightarrow P_{\max} = 0.5 \text{ W}$$

E8.4

Power =  $i_D \cdot v_{DS} = (1)(12) = 12 \text{ watts}$

c.  $T_{\text{sink}} = T_{\text{amb}} + P \cdot \theta_{\text{sink-amb}}$

$$T_{\text{sink}} = 25 + (12)(4) \Rightarrow T_{\text{sink}} = 73^\circ\text{C}$$

b.  $T_{\text{case}} = T_{\text{sink}} + P \cdot \theta_{\text{case-sink}}$

$$T_{\text{case}} = 73 + (12)(1) \Rightarrow T_{\text{case}} = 85^\circ\text{C}$$

a.  $T_{\text{dev}} = T_{\text{case}} + P \cdot \theta_{\text{dev-case}}$

$$T_{\text{dev}} = 85 + (12)(3) \Rightarrow T_{\text{dev}} = 121^\circ\text{C}$$

E8.5

$$\theta_{\text{dev-case}} = \frac{T_{j,\max} - T_{\text{amb}}}{P_{D,\text{rated}}} = \frac{200 - 25}{50} = 3.5^\circ\text{C/W}$$

$$P_{D,\max} = \frac{T_{j,\max} - T_{\text{amb}}}{\theta_{\text{dev-case}} + \theta_{\text{case-sink}} + \theta_{\text{sink-amb}}} = \frac{200 - 25}{3.5 + 0.5 + 2} \Rightarrow P_{D,\max} = 29.2 \text{ W}$$

$$T_{\text{case}} = T_{\text{amb}} + P_{D,\max}(\theta_{\text{case-sink}} + \theta_{\text{sink-amb}})$$

$$= 25 + (29.2)(0.5 + 2)$$

$$\Rightarrow T_{\text{case}} = 98^\circ\text{C}$$

E8.6

a.  $P_Q = V_{CEQ} \cdot I_{CQ} = (7.5)(7.5)$

$P_Q = 56.3 \text{ mW}$

b.  $\overline{P}_L = \frac{1}{2} \cdot \frac{V_P^2}{R_L} = \frac{1}{2} \cdot \frac{(6.5)^2}{1} \Rightarrow \overline{P}_L = 21.1 \text{ mW}$

$\overline{P}_S = (15)(7.5) \Rightarrow \overline{P}_S = 113 \text{ mW}$


$\eta = \frac{\overline{P}_L}{\overline{P}_S} = \frac{21.1}{113} \Rightarrow \eta = 18.7\%$

$\overline{P}_Q = 56.3 - 21.1 = 35.2 \text{ mW}$

E8.7

a.  $I_{DQ} = \frac{10 - 4}{0.1} \Rightarrow I_{DQ} = 60 \text{ mA}$

b.

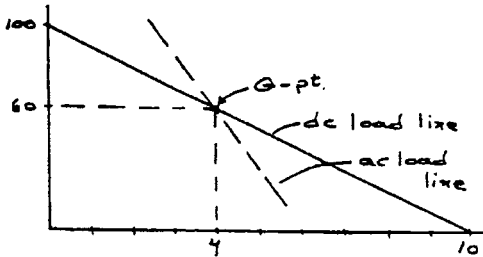

$v_{ds} = -\left(\frac{9}{10}\right)(60)(0.050) = -2.7 \text{ V}$   
 $\Rightarrow v_{DS}(\text{min}) = 4 - 2.7 = 1.3 \text{ V}$

So maximum swing is determined by drain-to-source voltage.

$V_{PP} = 2 \times (2.5) = 5.0 \text{ V}$

c.  $\overline{P}_L = \frac{1}{2} \cdot \frac{V_P^2}{R_L} = \frac{1}{2} \cdot \frac{(2.5)^2}{0.1} \Rightarrow \overline{P}_L = 31.25 \text{ mW}$

$\overline{P}_S = V_{DD} \cdot I_{DQ} = (10)(60) = 600 \text{ mW}$

$\eta = \frac{\overline{P}_L}{\overline{P}_S} = \frac{31.25}{600} \Rightarrow \eta = 5.2\%$

E8.8

a.  $\overline{P}_L = \frac{1}{2} \cdot \frac{V_P^2}{R_L}$   
 $\Rightarrow V_P = \sqrt{2R_L \overline{P}_L} = \sqrt{2(8)(25)} \Rightarrow V_P = 20 \text{ V}$   
 $\Rightarrow V_{CC} = \frac{20}{0.8} \Rightarrow V_{CC} = 25 \text{ V}$

b.  $I_P = \frac{V_P}{R_L} = \frac{20}{8} \Rightarrow I_P = 2.5 \text{ A}$

c.  $\overline{P}_Q = \frac{V_{CC}V_P}{\pi R_L} - \frac{V_P^2}{4R_L}$

$\overline{P}_Q = \frac{(25)(20)}{\pi(8)} - \frac{(20)^2}{4(8)} = 19.9 - 12.5$   
 $\Rightarrow \overline{P}_Q = 7.4 \text{ W}$

d.  $\eta = \frac{\pi V_P}{4V_{CC}} = \frac{\pi}{4} \cdot \frac{20}{25} \Rightarrow \eta = 62.8\%$

E8.9

a.  $\overline{P}_L = \frac{1}{2} \cdot \frac{V_P^2}{R_L} = \frac{(4)^2}{2(0.1)} \Rightarrow \overline{P}_L = 80 \text{ mW}$

b.  $I_P = \frac{V_P}{R_L} = \frac{4}{0.1} \Rightarrow I_P = 40 \text{ mA}$

c.  $\overline{P}_Q = \frac{V_{CC}V_P}{\pi R_L} - \frac{V_P^2}{4R_L}$

$\overline{P}_Q = \frac{(5)(4)}{\pi(0.1)} - \frac{(4)^2}{4(0.1)} = 63.7 - 40$   
 $\Rightarrow \overline{P}_Q = 23.7 \text{ mW}$

d.  $\eta = \frac{\pi V_P}{4V_{CC}} = \frac{\pi}{4} \cdot \frac{4}{5} \Rightarrow \eta = 62.8\%$

E8.10

a.  $v_I = v_o + v_{GSn} - \frac{V_{BB}}{2}$

$\frac{dv_I}{dv_o} = 1 + \frac{dv_{GSn}}{dv_o}$

$i_{Dn} = K_n(v_{GSn} - V_{TN})^2$

$v_{GSn} = \sqrt{\frac{i_{Dn}}{K_n}} + V_{TN}$

$\frac{dv_{GSn}}{dv_o} = \frac{dv_{GSn}}{di_{Dn}} \cdot \frac{di_{Dn}}{dv_o}$

So  $\frac{dv_{GSn}}{di_{Dn}} = \frac{1}{\sqrt{K_n}} \cdot \frac{1}{2} \cdot \frac{1}{\sqrt{i_{Dn}}}$

At  $v_o = 0$ ,  $i_{Dn} = 0.050 \text{ A}$

So  $\frac{dv_{GSn}}{di_{Dn}} = \frac{1}{\sqrt{0.2}} \cdot \frac{1}{2} \cdot \frac{1}{\sqrt{0.050}} = 5$

$i_{Dn} = i_L + i_{Dp}$

For a small change in  $v_o \rightarrow \Delta i_L = \Delta i_{Dn} - (-\Delta i_{Dp})$

So  $\Delta i_{Dn} = \frac{1}{2} \Delta i_L$

or

$\frac{di_{Dn}}{dv_o} = \frac{1}{2} \cdot \frac{di_L}{dv_o} = \frac{1}{2} \cdot \frac{1}{R_L} = \frac{1}{2} \cdot \frac{1}{20} = 0.025$

Then  $\frac{dv_{GSn}}{dv_o} = (5)(0.025) = 0.125$

Then  $\frac{dv_I}{dv_o} = 1 + 0.125 = 1.125$

and  $A_v = \frac{dv_o}{dv_I} = \frac{1}{1.125} \Rightarrow A_v = 0.889$

b. For  $v_o = 5 \text{ V}$ ,  $i_L = 0.25 \text{ A} = i_{Dn}$ , and  $i_{Dp} = 0$

$$\frac{dv_{GSn}}{dv_0} = \frac{dv_{GSn}}{di_{Dn}} \cdot \frac{di_{Dn}}{dv_0}$$

$$\frac{dv_{GSn}}{di_{Dn}} = \frac{1}{\sqrt{K_n}} \cdot \frac{1}{2} \cdot \frac{1}{\sqrt{i_{Dn}}} = \frac{1}{\sqrt{0.2}} \cdot \frac{1}{2} \cdot \frac{1}{\sqrt{0.25}} = 2.24$$

$$\frac{di_{Dn}}{dv_0} = \frac{di_L}{dv_0} = \frac{1}{20} = 0.05$$

$$\frac{dv_{GSn}}{dv_0} = (2.24)(0.05) = 0.112$$

$$\frac{dv_I}{dv_0} = 1 + 0.112 = 1.112$$

$$A_v = \frac{dv_0}{dv_I} = \frac{1}{1.112} \Rightarrow A_v = 0.899$$

E8.11

$$a. \quad I_{CQ} \approx \frac{1}{2} \cdot \left( \frac{2V_{CC}}{R_L} \right) = \frac{V_{CC}}{R_L} = \frac{12}{1.5} = 8 \text{ mA}$$

$$R_{TH} = R_1 \parallel R_2$$

$$V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right) V_{CC} = \frac{1}{R_1} \cdot R_{TH} \cdot V_{CC}$$

$$I_{BQ} = \frac{I_{CQ}}{\beta} = \frac{8}{75} = 0.107 \text{ mA} = \frac{V_{TH} - V_{BE}}{R_{TH} + (1 + \beta)R_E}$$

$$\text{Let } R_{TH} = (1 + \beta)R_E = (76)(0.1) = 7.6 \text{ k}\Omega$$

$$0.107 = \frac{\frac{1}{R_1} \cdot (7.6)(12) - 0.7}{7.6 + 7.6}$$

$$\frac{1}{R_1} \cdot (91.2) = 2.33 \Rightarrow R_1 = 39.1 \text{ k}\Omega$$

$$\frac{39.1R_2}{39.1 + R_2} = 7.6 \Rightarrow (39.1 - 7.6)R_2 = (7.6)(39.1)$$

$$\Rightarrow R_2 = 9.43 \text{ k}\Omega$$

$$b. \quad \overline{P_L} = \frac{1}{2} \cdot (0.9I_{CQ})^2 R_L = \frac{1}{2} [(0.9)(8)]^2 (1.5)$$

$$\Rightarrow \overline{P_L} = 38.9 \text{ mW}$$

$$\overline{P_S} = V_{CC}I_{CQ} = (12)(8) = 96 \text{ mW}$$

$$\overline{P_Q} = \overline{P_S} - \overline{P_L} = 96 - 38.9 \Rightarrow \overline{P_Q} = 57.1 \text{ mW}$$

$$\eta = \frac{\overline{P_L}}{\overline{P_S}} = \frac{38.9}{96} \Rightarrow \eta = 40.5\%$$

E8.12

$$a. \quad R_b = r_\pi + (1 + \beta)R'_E$$

$$\text{and } R'_E = a^2 R_L = (10)^2 (8) = 800 \Omega$$

$$R_i = 1.5 \text{ k}\Omega = R_{TH} \parallel R_b$$

$$I_Q = \frac{V_{CC}}{a^2 R_L} = \frac{18}{(10)^2 (8)} = 22.5 \text{ mA}$$

$$r_\pi = \frac{(100)(0.026)}{22.5} = 0.116 \text{ k}\Omega$$

$$R_b = 0.116 + (101)(0.8) = 80.9 \text{ k}\Omega$$

$$1.5 = R_{TH} \parallel 80.9 = \frac{R_{TH}(80.9)}{R_{TH} + (80.9)}$$

$$\Rightarrow (80.9 - 1.5)R_{TH} = (1.5)(80.9)$$

$$\Rightarrow R_{TH} = 1.53 \text{ k}\Omega$$

$$V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right) V_{CC} = \frac{1}{R_1} \cdot R_{TH} \cdot V_{CC}$$

$$I_{BQ} = \frac{I_Q}{\beta} = \frac{22.5}{100} = 0.225 \text{ mA}$$

$$I_{BQ} = \frac{V_{TH} - 0.7}{R_{TH}}$$

$$\Rightarrow \frac{1}{R_1} (1.53)(18) = (0.225)(1.53) + 0.7$$

$$\Rightarrow R_1 = 26.4 \text{ k}\Omega$$

$$\frac{26.4R_2}{26.4 + R_2} = 1.53$$

$$(26.4 - 1.53)R_2 = (1.53)(26.4)$$

$$\Rightarrow R_2 = 1.62 \text{ k}\Omega$$

$$b. \quad v_E = 0.9V_{CC} = (0.9)(18) = 16.2 \text{ V}$$

$$i_E = 0.9I_{CQ} = (0.9)(22.5) = 20.25 \text{ mA}$$

$$v_0 = \frac{v_E}{a} = \frac{16.2}{10} \Rightarrow v_P = 1.62 \text{ V}$$

$$i_0 = a i_E = (10)(20.25) \Rightarrow i_P = 203 \text{ mA}$$

$$\overline{P_L} = \frac{1}{2} (1.62)(0.203) \Rightarrow \overline{P_L} = 0.164 \text{ W}$$

E8.13

$$a. \quad I_C = I_{SQ} \exp\left(\frac{V_{BE}}{V_T}\right) \Rightarrow V_{BE} = V_T \ln\left(\frac{I_C}{I_{SQ}}\right)$$

$$V_{BE} = (0.026) \ln\left(\frac{5 \times 10^{-3}}{2 \times 10^{-13}}\right) = 0.6225 \text{ V}$$

$$\Rightarrow V_{D1} = V_{D2} = 0.6225$$

$$I_{Bias} = I_D = I_{SD} \exp\left(\frac{0.6225}{0.026}\right)$$

$$= 5 \times 10^{-13} \exp\left(\frac{0.6225}{0.026}\right)$$

$$\underline{I_{Bias} = 12.5 \text{ mA}}$$

$$\text{b. } V_0 = 2 \text{ V, } i_L = \frac{2}{0.075} = 26.7 \text{ mA}$$

1st approximation:

$$i_{Cn} \approx 26.7 \text{ mA, } i_{Bn} = 0.444 \text{ mA}$$

$$V_{BE} = (0.026) \ln \left( \frac{26.7 \times 10^{-3}}{2 \times 10^{-13}} \right) = 0.6661$$

$$I_D = 12.5 - 0.444 = 12.056 \text{ mA}$$

$$V_D = (0.026) \ln \left( \frac{12.056 \times 10^{-3}}{5 \times 10^{-13}} \right) = 0.6216$$

$$2V_D = 1.243 \text{ V}$$

$$V_{EB} = 2V_D - V_{BE} = 0.5769$$

$$i_{Cp} = 2 \times 10^{-13} \exp \left( \frac{0.5769}{0.026} \right) = 0.866 \text{ mA}$$

2nd approximation:

$$i_{En} = i_L + i_{Cp} = 26.7 + 0.866 \approx \underline{27.6 \text{ mA} = i_{En}}$$

$$i_{Cn} = \left( \frac{60}{61} \right) (27.6) \Rightarrow \underline{i_{Cn} = 27.1 \text{ mA}}$$

$$i_{Bn} = 0.452 \text{ mA}$$

$$I_D = 12.5 - 0.452 \Rightarrow \underline{I_D = 12.05 \text{ mA}}$$

$$V_{BE_n} = (0.026) \ln \left( \frac{27.1 \times 10^{-3}}{2 \times 10^{-13}} \right)$$

$$\Rightarrow \underline{V_{BE_n} = 0.6664 \text{ V}}$$

$$V_D = (0.026) \ln \left( \frac{12.05 \times 10^{-3}}{5 \times 10^{-13}} \right) = 0.6215 \text{ V}$$

$$2V_{DD} = 1.243 \text{ V}$$

$$V_{EB} = 1.243 - 0.6664 \Rightarrow \underline{V_{EBp} = 0.5766 \text{ V}}$$

$$i_{Cp} = 2 \times 10^{-13} \exp \left( \frac{0.5766}{0.026} \right) \Rightarrow \underline{i_{Cp} = 0.856 \text{ mA}}$$

$$\text{c. } V_0 = 10 \text{ V, } i_L = \frac{10}{0.075} = 133 \text{ mA}$$

$$i_{En} \approx i_L = 133 \text{ mA} \Rightarrow \underline{i_{Cn} = 131 \text{ mA}}$$

$$i_{Bn} = 2.18 \text{ mA} \Rightarrow I_D = 12.5 - 2.18$$

$$\Rightarrow \underline{I_D = 10.3 \text{ mA}}$$

$$V_D = (0.026) \ln \left( \frac{10.3 \times 10^{-3}}{5 \times 10^{-13}} \right) = 0.6175$$

$$2V_{DD} = 1.235 \text{ V}$$

$$V_{BE_n} = (0.026) \ln \left( \frac{131 \times 10^{-3}}{2 \times 10^{-13}} \right)$$

$$\Rightarrow \underline{V_{BE_n} = 0.7074 \text{ V}}$$

$$V_{EBp} = 1.235 - 0.7074 \Rightarrow \underline{V_{EBp} = 0.5276 \text{ V}}$$

$$i_{Cp} = 2 \times 10^{-13} \exp \left( \frac{0.5276}{0.026} \right)$$

$$\Rightarrow \underline{i_{Cp} = 0.130 \text{ mA}}$$

E8.14

$$\text{a. } v_I = 0 = v_0, v_{B3} = 0.7 \text{ V}$$

$$I_{R1} = \frac{12 - 0.7}{R_1} = \frac{11.3}{0.25} \Rightarrow I_{R1} = 45.2 \text{ mA}$$

If transistors are matched, then

$$i_{E1} = i_{E3}$$

$$i_{R1} = i_{E1} + i_{B3} = i_{E1} + \frac{i_{E3}}{1 + \beta}$$

$$i_{R1} = i_{E1} \left( 1 + \frac{1}{1 + \beta} \right) = i_{E1} \left( 1 + \frac{1}{41} \right)$$

$$i_{E1} = \frac{45.2}{1.024} \Rightarrow \underline{i_{E1} = i_{E2} = 44.1 \text{ mA}}$$

$$i_{B1} = i_{B2} = \frac{i_{E1}}{1 + \beta} = \frac{44.1}{41}$$

$$\Rightarrow \underline{i_{B1} = i_{B2} = 1.08 \text{ mA}}$$

$$\text{b. For } v_I = 5 \text{ V} \Rightarrow v_0 = 5 \text{ V}$$

$$i_0 = \frac{5}{8} \Rightarrow \underline{i_0 = 0.625 \text{ A}}$$

$$i_{E3} \approx 0.625 \text{ A, } i_{B3} = \frac{0.625}{41} \Rightarrow i_{B3} = 15.2 \text{ mA}$$

$$v_{B3} = 5.7 \text{ V} \Rightarrow i_{R1} = \frac{12 - 5.7}{0.25} = 25.2 \text{ mA}$$

$$i_{E1} = 25.2 - 15.2 \Rightarrow \underline{i_{E1} = 10.0 \text{ mA}}$$

$$\Rightarrow \underline{i_{B1} = \frac{10}{41} = 0.244 \text{ mA}}$$

$$v_{B4} = 5 - 0.7 = 4.3 \text{ V.}$$

$$I_{R2} = \frac{4.3 - (-12)}{0.25} = 65.2 \text{ mA} \approx i_{E2}$$

$$\underline{i_{B2} = \frac{65.2}{41} = 1.59 \text{ mA}}$$


$$i_I = i_{B2} - i_{B1} = 1.59 - 0.244 \Rightarrow \underline{i_I = 1.35 \text{ mA}}$$

$$\text{c. } A_I = \frac{i_0}{i_I} = \frac{625}{1.35} \Rightarrow \underline{A_I = 463}$$

From Equation (8.54)

$$A_I = \frac{(1 + \beta)R}{2R_L} = \frac{(41)(250)}{2(8)} = \underline{641}$$

E8.15

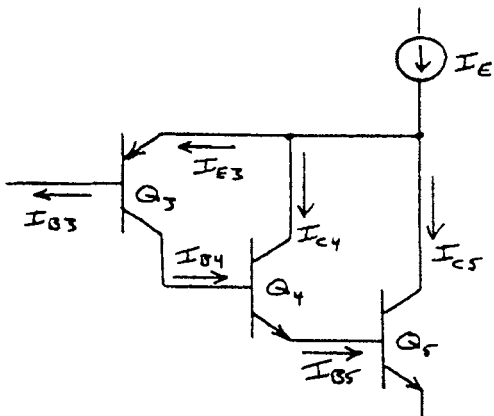

$$\begin{aligned}
 I_E &= I_{E3} + I_{C4} + I_{C5} \\
 &= I_{E3} + I_{C4} + \beta_5 I_{B5} \\
 &= I_{E3} + \beta_4 I_{B4} + \beta_5 (1 + \beta_4) I_{B4} \\
 I_E &= (1 + \beta_3) I_{B3} + \beta_4 \beta_3 I_{B3} + \beta_5 (1 + \beta_4) \beta_3 I_{B3}
 \end{aligned}$$

If  $\beta_4$  and  $\beta_5$  are large, then

$$I_E \approx \beta_3 \beta_4 \beta_5 I_{B3}$$

So that composite current gain is

$$\beta \approx \beta_3 \beta_4 \beta_5$$





## Chapter 8

### Problem Solutions

8.1


a.

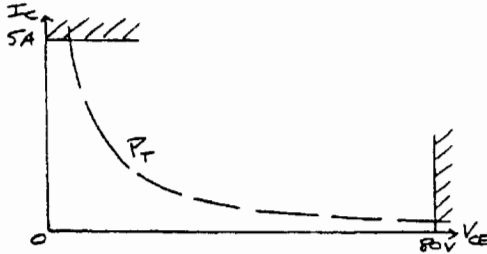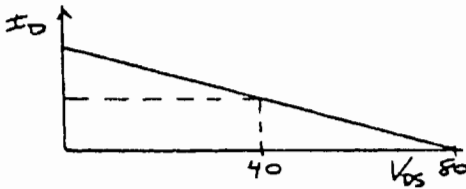
 b. i.  $V_{DD} = 80 \text{ V}$ 


Maximum power at  $V_{DS} = \frac{V_{DD}}{2} = 40 \text{ V}$

$$I_D = \frac{P_T}{V_{DS}} = \frac{25}{40} = 0.625 \text{ A}$$

$$R_D = \frac{80 - 40}{0.625} \Rightarrow \underline{R_D = 64 \Omega}$$

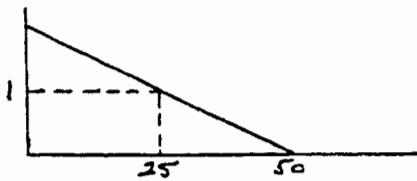 ii.  $V_{DD} = 50 \text{ V}$ 


Maximum power at  $V_{DS} = \frac{V_{DD}}{2} = 25 \text{ V}$

$$I_D = \frac{P_T}{V_{DS}} = \frac{25}{25} = 1 \text{ A}$$

$$R_D = \frac{50 - 25}{1} \Rightarrow \underline{R_D = 25 \Omega}$$

8.2

a.  $P_Q(\text{max}) = I_{CQ} \cdot \frac{V_{CC}}{2}$

So  $I_{CQ} = \frac{2P_Q(\text{max})}{V_{CC}} = \frac{2(20)}{24} = 1.67 \text{ A}$

$$R_L = \frac{V_{CC} - (V_{CC}/2)}{I_{CQ}} = \frac{24 - 12}{1.67} \Rightarrow \underline{R_L = 7.2 \Omega}$$

$$I_B = \frac{I_{CQ}}{\beta} = \frac{1.67}{80} \Rightarrow 20.8 \text{ mA}$$

$$R_B = \frac{24 - 0.7}{20.8} \Rightarrow \underline{R_B = 1.12 \text{ k}\Omega}$$

b.  $|A_v| = g_m R_L = \frac{I_{CQ} \cdot R_L}{V_T} = \frac{(1.67)(7.2)}{0.026} = 462$

$$V_O(\text{max}) = 12 \text{ V} \Rightarrow V_P = \frac{V_O(\text{max})}{A_v} = \frac{12}{462}$$

$$\Rightarrow \underline{V_P \approx 26 \text{ mV}}$$

8.3

a. For maximum power delivered to the load, set

$$V_{CEQ} = \frac{V_{CC}}{2}$$

Set  $V_{CC} = 25 \text{ V} = V_{CE(\text{sat})}$

Then  $I_{Cm} = \frac{V_{CC}}{R_L} = \frac{25}{0.1}$

$$I_{Cm} = 250 \text{ mA} < I_{C,\text{max}}$$

$$I_{CQ} = \frac{25 - 12.5}{0.1} = 125 \text{ mA}$$

$$P_Q(\text{max}) = I_{CQ} \cdot \frac{V_{CC}}{2} = (0.125)(12.5)$$

$$= 1.56 \text{ W} < P_{D,\text{max}}$$


$$I_{BQ} = \frac{125}{100} = 1.25 \text{ mA}$$

$$R_B = \frac{25 - 0.7}{1.25} \Rightarrow \underline{R_B = 19.4 \text{ k}\Omega}$$

b.  $P_L(\text{max}) = \frac{1}{2} \cdot I_{CQ}^2 \cdot R_L = \frac{1}{2}(0.125)^2(100)$

$$\Rightarrow \underline{P_L(\text{max}) = 0.781 \text{ W}}$$

8.4

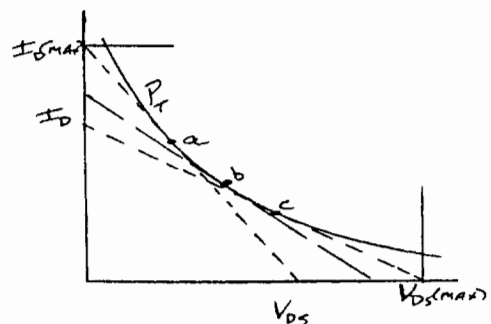


Point (b): Maximum power delivered to load.

Point (a): Will obtain maximum signal current output.

Point (c): Will obtain maximum signal voltage output.

8.5

a.

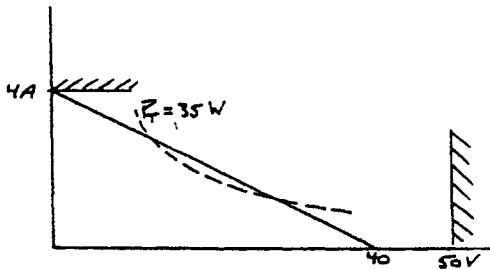

b.  $V_{GG} = 5\text{ V}, I_D = 0.25(5 - 4)^2 = 0.25\text{ A},$   
 $V_{DS} = 37.5\text{ V}, P = 9.375\text{ W}$   
 $V_{GG} = 6\text{ V}, I_D = 0.25(6 - 4)^2 = 1.0\text{ A},$   
 $V_{DS} = 30\text{ V}, P = 30\text{ W}$   
 $V_{GG} = 7\text{ V}, I_D = 0.25(7 - 4)^2 = 2.25\text{ A},$   
 $V_{DS} = 17.5\text{ V}, P = 39.375\text{ W}$

$V_{GG} = 8\text{ V}, I_D = 0.25[2(8 - 4)V_{DS} - V_{DS}^2]$   
 $= \frac{40 - V_{DS}}{10} \Rightarrow V_{DS} = 2.92$   
 $I_D = 3.71\text{ A}, P = 10.8\text{ W}$

$V_{GG} = 9\text{ V}, I_D = 0.25[2(9 - 4)V_{DS} - V_{DS}^2]$   
 $= \frac{40 - V_{DS}}{10} \Rightarrow V_{DS} = 1.88\text{ V}$   
 $I_D = 3.81\text{ A}, P = 7.16\text{ W}$

c. Yes, at  $V_{GG} = 7\text{ V}, P = 39.375\text{ W} > P_{D,max} = 35\text{ W}$

8.6

a. Set  $V_{DSQ} = \frac{V_{DD}}{2} = 25\text{ V}$

$I_{DQ} = \frac{50 - 25}{20} = 1.25\text{ A}$

$I_{DQ} = K_n(V_{GS} - V_{TN})^2$

$\sqrt{\frac{1.25}{0.2}} + 4 = V_{GS} = 6.5\text{ V}$

$V_{GS} = \left(\frac{R_2}{R_1 + R_2}\right)V_{DD}$

Let  $R_1 + R_2 = 100\text{ k}\Omega$

$6.5 = \left(\frac{R_2}{100}\right)(50) \Rightarrow R_2 = 13\text{ k}\Omega$

$R_1 = 87\text{ k}\Omega$

b.  $P_D = I_{DQ}V_{DSQ} = (1.25)(25) \Rightarrow P_D = 31.25\text{ W}$

c.  $I_{D,max} = 2I_{DQ} \Rightarrow I_{D,max} = 2.5\text{ A}$

$V_{DS,max} = V_{DD} \Rightarrow V_{DS,max} = 50\text{ V}$

$P_{D,max} = 31.25\text{ W}$

d.  $\left|\frac{V_o}{V_i}\right| = g_m R_L$

$g_m = 2\sqrt{K_n I_{DQ}} = 2\sqrt{(0.2)(1.25)} = 1\text{ A/V}$


$|V_o| = (1)(20)(0.5) = 10\text{ V}$

$\overline{P_L} = \frac{1}{2} \cdot \frac{V_o^2}{R_L} = \frac{1}{2} \cdot \frac{(10)^2}{20} \Rightarrow \overline{P_L} = 2.5\text{ W}$

$\overline{P_Q} = 31.25 - 2.5 \Rightarrow \overline{P_Q} = 28.75\text{ W}$

8.7

(a)

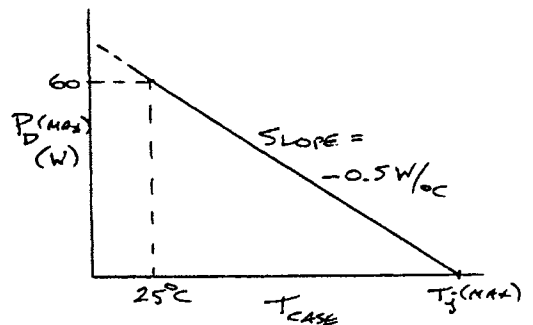

(b)  $P_D = P_{D,max} - (\text{Slope})(T_j - 25)$

At  $P_D = 0, T_{j,max} = \frac{60}{0.5} + 25 \Rightarrow T_{j,max} = 145^\circ\text{C}$

(c)  $P_{D,max} = \frac{T_{j,max} - T_{case}}{\theta_{dev-amb}}$

or

$\theta_{dev-amb} = \frac{145 - 25}{60} \Rightarrow \theta_{dev-amb} = 2^\circ\text{C/W}$

8.8

$P_{D,rated} = \frac{T_{j,max} - T_{amb}}{\theta_{dev-case}}$

or

$\theta_{dev-case} = \frac{T_{j,max} - T_{amb}}{P_{D,rated}}$

$= \frac{150 - 25}{50} = 2.5^\circ\text{C/W}$

Then

$T_{dev} - T_{amb} = P_D(\theta_{dev-case} + \theta_{case-amb})$

$150 - 25 = P_D(2.5 + \theta_{case-amb})$

$\Rightarrow 125 = P_D(2.5 + \theta_{case-amb})$

8.9

$$P_D = I_D \cdot V_{DS} = (4)(5) = 20 \text{ W}$$

$$T_{dev} - T_{amb} = P_D(\theta_{dev-case} + \theta_{case-snk} + \theta_{snk-amb})$$

$$T_{dev} - 25 = 20(1.75 + 0.8 + 3) = 111$$

$$\Rightarrow T_{dev} = 136^\circ\text{C}$$

$$T_{dev} - T_{case} = P_D \cdot \theta_{dev-case} = (20)(1.75) = 35$$

$$T_{case} = T_{dev} - 35 = 136 - 35 \Rightarrow T_{case} = 101^\circ\text{C}$$

$$T_{case} - T_{snk} = P_D \cdot \theta_{case-snk} = (20)(0.8) = 16^\circ\text{C}$$

$$T_{snk} = T_{case} - 16 = 101 - 16 \Rightarrow T_{snk} = 85^\circ\text{C}$$

8.10

$$T_{dev} - T_{amb} = P_D(\theta_{dev-case} + \theta_{case-amb})$$

$$200 - 25 = 25(3 + \theta_{case-amb})$$

$$\Rightarrow \theta_{case-amb} = 4^\circ\text{C/W}$$

8.11

$$\theta_{dev-case} = \frac{T_{j,max} - T_{amb}}{P_{D,rated}} = \frac{175 - 25}{15} = 10^\circ\text{C/W}$$

$$P_D = \frac{T_{j,max} - T_{amb}}{\theta_{dev-case} + \theta_{case-snk} + \theta_{snk-amb}}$$

$$= \frac{175 - 25}{10 + 1 + 4} \Rightarrow P_D = 10 \text{ W}$$

8.12

$$\eta = \frac{\overline{P}_L}{\overline{P}_S}$$

$$\overline{P}_S = V_{CC} \cdot I_Q$$

$$\overline{P}_L = V_P \cdot I_P = \left(\frac{V_{CC}}{2}\right)(I_Q)$$

$$\eta = \frac{\frac{1}{2} \cdot V_{CC} \cdot I_Q}{V_{CC} \cdot I_Q} \Rightarrow \eta = 50\%$$

8.13

a. Neglect base currents.

$$v_o(\max) = V^+ - V_{CE}(\text{sat}) = 10 - 0.2 = 9.8 \text{ V}$$

$$i_L(\max) = I_Q = \frac{9.8}{R_L} = \frac{9.8}{1} \Rightarrow I_Q = 9.8 \text{ mA}$$

$$R = \frac{0 - 0.7 - (-10)}{9.8} \Rightarrow R = 949 \Omega$$

$$i_{E1}(\max) = 2I_Q \Rightarrow i_{E1}(\max) = 19.6 \text{ mA}$$

$$i_{E1}(\min) = 0$$

$$i_L(\max) = I_Q = 9.8 \text{ mA}$$

$$i_L(\min) = -I_Q = -9.8 \text{ mA}$$

$$b. \overline{P}_L = \frac{1}{2}(i_L(\max))^2 R_L = \frac{1}{2}(9.8)^2(1)$$

$$\Rightarrow \overline{P}_L = 48.02 \text{ mW}$$

$$\overline{P}_S = I_Q(V^+ - V^-) + I_Q(0 - V^-)$$

$$= 9.8(20) + 9.8(10) \Rightarrow \overline{P}_S = 294 \text{ mW}$$

$$\eta = \frac{\overline{P}_L}{\overline{P}_S} = \frac{48.02}{294} \Rightarrow \eta = 16.3\%$$

8.14

$$a. I_Q(\min) = \frac{v_o(\max)}{R_L} = \frac{10}{0.1} \Rightarrow I_Q(\min) = 100 \text{ mA}$$

$$R = \frac{0 - 0.7 - (-12)}{100} \Rightarrow R = 113 \Omega$$

$$b. P_{Q1} = I_Q \cdot V_{CE1} = (100)(12) \Rightarrow P_{Q1} = 1.2 \text{ W}$$

$$P(\text{source}) = 2I_Q(12) = 2.4 \text{ W}$$

$$c. \overline{P}_L = \frac{1}{2} \cdot \frac{V_P^2}{R_L} = \frac{(10)^2}{2(100)} = 0.5 \text{ W}$$

$$\overline{P}_S = 1.2 + 2.4 = 3.6 \text{ W}$$

$$\eta = \frac{\overline{P}_L}{\overline{P}_S} = \frac{0.5}{3.6} \Rightarrow \eta = 13.9\%$$

8.15

$$\overline{P}_L = \frac{V_P^2}{R_L} = \frac{(V^+)^2}{R_L}$$

$$\overline{P}_S = \frac{1}{2} \cdot \frac{(V^+)^2}{R_L} + \frac{1}{2} \cdot \frac{(V^-)^2}{R_L}, \quad V^- = -V^+$$

$$\text{So } \overline{P}_S = \frac{(V^+)^2}{R_L}$$

$$\eta = \frac{\overline{P}_L}{\overline{P}_S} \Rightarrow \eta = 100\%$$

8.16

$$(a) V_{DS} \geq V_{DS}(\text{sat}) = V_{GS} - V_{TN} = V_{GS}$$

$$V_{DS} = 10 - V_o(\max) \text{ and } I_D = I_L = K_n(V_{GS})^2$$

$$\frac{V_o(\max)}{R_L} = K_n(V_{GS})^2$$

$$V_{GS} = \sqrt{\frac{V_o(\max)}{R_L \cdot K_n}}$$

So

$$10 - V_o(\max) = \sqrt{\frac{V_o(\max)}{R_L \cdot K_n}} = \sqrt{\frac{V_o(\max)}{(5)(0.4)}}$$

$$[10 - V_o(\max)]^2 = \frac{V_o(\max)}{2}$$

$$100 - 20V_o(\max) + V_o^2(\max) = \frac{V_o(\max)}{2}$$

$$V_0^2(\max) - 20.5V_0(\max) + 100 = 0$$

$$V_0(\max) = \frac{20.5 \pm \sqrt{(20.5)^2 - 4(100)}}{2}$$

$$\Rightarrow \underline{V_0(\max) = 8 \text{ V}}$$

$$i_L = \frac{8}{5} \Rightarrow \underline{i_L = 1.6 \text{ mA}}$$

$$V_{GS} = \sqrt{\frac{i_L}{K_n}} = \sqrt{\frac{1.6}{0.4}} = 2 \text{ V}$$

$$\Rightarrow \underline{v_I = 10 \text{ V}}$$

$$\text{b. } \overline{P_L} = \frac{1}{2} \cdot \frac{(8)^2}{5} = 6.4 \text{ mW}$$

$$\overline{P_S} = \frac{20(1.6)}{\pi} = 10.2 \text{ mW}$$

$$\eta = \frac{\overline{P_L}}{\overline{P_S}} = \frac{6.4}{10.2} \Rightarrow \underline{\eta = 62.7\%}$$

8.17

$$v_o = i_L R_L \text{ and } i_L = i_D = K_n(v_{GS} - V_{TN})^2$$

$$\text{or } i_L = K_n(v_{GS})^2 \text{ and } v_{GS} = v_I - v_o$$

Then

$$v_o = K_n R_L (v_I - v_o)^2 \text{ or } v_o = 2(v_I - v_o)^2$$

$$\frac{dv_o}{dv_I} = 2.2(v_I - v_o) \left(1 - \frac{dv_o}{dv_I}\right)$$

$$\frac{dv_o}{dv_I} [1 + 4(v_I - v_o)] = 4(v_I - v_o)$$

$$\text{or } \frac{dv_o}{dv_I} = \frac{4(v_I - v_o)}{1 + 4(v_I - v_o)}$$

$$\text{For } v_I = 10 \text{ V, } v_o = 8 \text{ V} \Rightarrow \frac{dv_o}{dv_I} = \frac{4(10 - 8)}{1 + 4(10 - 8)}$$

$$\Rightarrow \underline{\frac{dv_o}{dv_I} = 0.889}$$

$$\text{At } v_I = 0, v_o = 0 \Rightarrow \frac{dv_o}{dv_I} = 0$$

$$\text{At } v_I = 1, v_o = 0.5 \Rightarrow \frac{dv_o}{dv_I} = 0.667$$

8.18

$$\text{a. } V_{BE} = V_T \ln \left( \frac{i_C}{I_S} \right) = (0.026) \ln \left( \frac{5 \times 10^{-3}}{5 \times 10^{-13}} \right)$$

$$V_{BE} = \frac{V_{BB}}{2} = 0.5987 \text{ V}$$

$$\Rightarrow \underline{V_{BB} = 1.1973 \text{ V}}$$

$$P_Q = i_C \cdot v_{CE} = (5)(10) \Rightarrow \underline{P_Q = 50 \text{ mW}}$$

$$\text{b. } v_o = -8 \text{ V}$$

$$i_L = \frac{-8}{0.1} \Rightarrow \underline{i_L = -80 \text{ mA}}$$

$$\underline{i_{C_P} \approx 80 \text{ mA}}$$

$$v_{EB} = V_T \ln \left( \frac{i_{C_P}}{I_S} \right) = (0.026) \ln \left( \frac{80 \times 10^{-3}}{5 \times 10^{-13}} \right)$$

$$v_{EB} = 0.6708 \text{ V}$$

$$v_I = \frac{V_{BB}}{2} - v_{EB} + v_o = 0.5987 - 0.6708 - 8$$

$$\Rightarrow \underline{v_I = -8.072 \text{ V}}$$

$$v_{BE} = V_{BB} - v_{EB} = 1.1973 - 0.6708 = 0.5265 \text{ V}$$

$$i_{C_n} = I_S \exp \left( \frac{v_{BE}}{V_T} \right) = 5 \times 10^{-13} \exp \left( \frac{0.5265}{0.026} \right)$$

$$\Rightarrow \underline{i_{C_n} = 0.311 \text{ mA}}$$

$$P_L = i_L^2 R_L = (80)^2 (0.1) \Rightarrow \underline{P_L = 640 \text{ mW}}$$

$$P_{Q_n} = i_{C_n} \cdot v_{CE} = (0.311)(10 - (-8))$$

$$\Rightarrow \underline{P_{Q_n} = 5.60 \text{ mW}}$$

$$P_{Q_P} = i_{C_P} \cdot v_{EC} = (80)(2) \Rightarrow \underline{P_{Q_P} = 160 \text{ mW}}$$

8.19

$$\text{(a) } i_{D_n} = K_n (v_{GS_n} - V_{TN})^2$$

$$\sqrt{\frac{0.5}{2}} + 2 = v_{GS_n} = 2.5 \text{ V} = \frac{V_{BB}}{2}$$

$$\Rightarrow \underline{V_{BB} = 5.0 \text{ V}}$$

$$P_n = (0.5)(10) \Rightarrow \underline{P_n = P_p = 5 \text{ mW}}$$

$$\text{(b) } V_{DS} = V_{GS} - \widehat{V_{TN}} \Rightarrow V_{DS} = V_{GS} - 2$$

$$V_{DS} = 10 - v_o(\max)$$

and

$$V_{GS} = \sqrt{\frac{i_L}{K_n}} + V_{TN} = \sqrt{\frac{v_o(\max)}{R_L K_n}} + 2$$

$$= \sqrt{\frac{v_o(\max)}{(2)(1)}} + 2$$

so

$$10 - v_o(\max) = \sqrt{\frac{v_o(\max)}{2}} + 2 - 2 = \sqrt{\frac{v_o(\max)}{2}}$$

$$\text{so } \underline{v_o(\max) = 8 \text{ V}}$$

$$i_{D_n} = i_L = \frac{8}{1} \Rightarrow \underline{i_{D_n} = i_L = 8 \text{ mA}}$$

$$V_{GS} = \sqrt{\frac{8}{2}} + 2 \Rightarrow \underline{V_{GS} = 4 \text{ V}}$$

$$\text{Then } v_I = v_o + V_{GS} - \frac{V_{BB}}{2} = 8 + 4 - 2.5$$

$$\Rightarrow \underline{v_I = 9.5 \text{ V}}$$

$$v_{SG_P} = v_o - \left( v_I - \frac{V_{BB}}{2} \right) = 8 - (9.5 - 2.5)$$

$$v_{SG_P} = 1 \text{ V} \Rightarrow \underline{M_P \text{ cutoff}} \Rightarrow \underline{i_{D_P} = 0}$$

$$P_L = i_L^2 R_L = (8)^2(1) \Rightarrow \underline{P_L = 64 \text{ mW}}$$

$$P_{Mn} = i_{Dn} \cdot v_{DS} = (8)(10 - 8) \Rightarrow \underline{P_{Mn} = 16 \text{ mW}}$$

$$P_{Mp} = i_{Dp} \cdot v_{SD} \Rightarrow \underline{P_{Mp} = 0}$$

8.20

$$a. \quad v_0 = 24 \text{ V} \Rightarrow i_L = \frac{24}{8} \Rightarrow \underline{i_L \approx i_N = 3 \text{ A}}$$

$$i_{Bn} = \frac{3}{41} \Rightarrow i_{Bn} = 73.2 \text{ mA}$$

$$\text{For } i_D = 25 \text{ mA} \Rightarrow i_{R1} = 25 + 73.2 = 98.2 \text{ mA}$$

$$V_{BE} = V_T \ln \left( \frac{i_N}{I_S} \right) = (0.026) \ln \left( \frac{3}{6 \times 10^{-12}} \right)$$

$$= 0.7004 \text{ V}$$

$$\text{Then } 98.2 = \frac{30 - (24 + 0.7)}{R_1} \Rightarrow R_1 = \frac{5.3}{98.2}$$

$$\Rightarrow \underline{R_1 = 53.97 \Omega}$$

$$V_D = (0.026) \ln \left( \frac{25 \times 10^{-3}}{6 \times 10^{-12}} \right) = 0.5759 \text{ V}$$

$$V_{EB} = 2V_D - V_{BE} = 2(0.5759) - 0.7004$$

$$= 0.4514 \text{ V}$$

$$i_P = I_S \exp \left( \frac{V_{EB}}{V_T} \right) = (6 \times 10^{-12}) \exp \left( \frac{0.4514}{0.026} \right)$$

$$\Rightarrow \underline{i_P = 0.208 \text{ mA}}$$

b. Neglecting base current

$$i_D \approx \frac{30 - 0.6}{R_1} = \frac{30 - 0.6}{53.97} \Rightarrow \underline{i_D \approx 545 \text{ mA}}$$

$$V_D = (0.026) \ln \left( \frac{0.545}{6 \times 10^{-12}} \right) = 0.656 \text{ V}$$

 Approximation for  $i_D$  is okay.

$$\text{Diodes and transistors matched} \Rightarrow \underline{i_N = i_P = 545 \text{ mA}}$$

8.21

$$(a) \quad I_{D1} = K_1(V_{GS1} - V_{TN})^2$$

$$V_{GS1} = \sqrt{\frac{5}{K_1}} + 1 = 2 \text{ V}$$

$$I_{D3} = K_3(V_{GS3} - V_{TN})^2$$

$$200 = K_3(2 - 1)^2 \Rightarrow \underline{K_{n3} = K_{p4} = 200 \mu\text{A}/\text{V}^2}$$

$$(b) \quad v_i + V_{SG4} + V_{GS3} - V_{GS1} = v_o$$

$$\text{For } v_o \text{ large, } i_L = i_i = K_{n1}(V_{GS1} - V_{TN})^2$$

$$V_{GS1} = \sqrt{\frac{i_L}{K_{n1}}} + V_{TN} = \sqrt{\frac{v_o}{R_L K_{n1}}} + V_{TN}$$

$$\text{So } v_i + 2 + 2 - \left( \sqrt{\frac{v_o}{(0.5)(5)}} + 1 \right) = v_o$$

$$v_i = v_o + \sqrt{\frac{v_o}{2.5}} - 3$$

$$\frac{dv_i}{dv_i} = 1 = \frac{dv_o}{dv_i} + \frac{1}{2} \cdot \frac{1}{\sqrt{2.5v_o}} \cdot \frac{dv_o}{dv_i}$$

$$1 = \frac{dv_o}{dv_i} \left[ 1 + \frac{1}{2\sqrt{2.5v_o}} \right]$$

 For  $v_o = 5 \text{ V}$ :

$$1 = \frac{dv_o}{dv_i} \left[ 1 + \frac{1}{2\sqrt{2.5(5)}} \right] = \frac{dv_o}{dv_i} (1.1414)$$

$$\Rightarrow \underline{\frac{dv_o}{dv_i} = 0.876}$$

8.22

$$v_o = v_i + \frac{V_{BB}}{2} - V_{GS} \quad \text{and} \quad V_{GS} = \sqrt{\frac{I_{Dn}}{K_n}} + V_{TN}$$

$$\text{For } v_o \approx 0, \quad I_{Dn} = I_{DQ} + i_L = I_{DQ} + \frac{v_o}{R_L}$$

Then

$$v_o = v_i + \frac{V_{BB}}{2} - V_{TN} - \sqrt{\frac{I_{DQ} + (v_o/R_L)}{K_n}}$$

or

$$v_o = v_i + \frac{V_{BB}}{2} - V_{TN} - \sqrt{\frac{I_{DQ}}{K_n}} \cdot \sqrt{1 + \frac{v_o}{I_{DQ}R_L}}$$

 For  $v_o$  small,

$$v_o \approx v_i + \frac{V_{BB}}{2} - V_{TN} - \sqrt{\frac{I_{DQ}}{K_n}} \cdot \left( 1 + \frac{1}{2} \cdot \frac{v_o}{I_{DQ}R_L} \right)$$

$$v_o \left[ 1 + \frac{1}{2} \cdot \frac{\sqrt{I_{DQ}}}{\sqrt{K_n}} \cdot \frac{1}{I_{DQ}R_L} \right]$$

$$= v_i + \frac{V_{BB}}{2} - V_{TN} - \sqrt{\frac{I_{DQ}}{K_n}}$$

Now

$$\frac{dv_o}{dv_i} = \frac{1}{\left[ 1 + \frac{1}{2} \cdot \frac{\sqrt{I_{DQ}}}{\sqrt{K_n}} \cdot \frac{1}{I_{DQ}R_L} \right]} = 0.95$$

$$\text{So } \frac{1}{2} \cdot \frac{\sqrt{I_{DQ}}}{\sqrt{K_n}} \cdot \frac{1}{I_{DQ}R_L} = \frac{1}{0.95} - 1 = 0.0526$$

$$\text{For } R_L = 0.1 \text{ k}\Omega, \text{ then } \frac{1}{\sqrt{K_n I_{DQ}}} = 0.01052$$

$$\text{Or } \sqrt{K_n I_{DQ}} = 95.1$$

We can write

$$g_m = 2\sqrt{K_n I_{DQ}} = 190 \text{ mA/V}$$

This is the required transconductance for the output transistor. This implies a very large transistor.

8.23

$$A_v = -g_m R_L$$

$$\text{So } -12 = -g_m(2) \Rightarrow g_m = 6 \text{ mA/V} = \frac{I_{CQ}}{V_T}$$

$$I_{CQ} = (6)(0.026) \Rightarrow I_{CQ} = 0.156 \text{ mA}$$

But for maximum symmetrical swing, set

$$I_{CQ} = \frac{V_{CC}}{R_L} = \frac{10}{2} = 5 \text{ mA} \Rightarrow |A_v| > 12$$

Maximum power to the load:

$$\overline{P_L}(\text{max}) = \frac{1}{2} \cdot \frac{V_{CC}^2}{R_L} = \frac{(10)^2}{2(2)} \Rightarrow \overline{P_L}(\text{max}) = 25 \text{ mW}$$

$$\overline{P_S} = V_{CC} \cdot I_{CQ} = (10)(5) = 50 \text{ mW}$$

$$\text{So } \underline{\eta = 50\%}$$

$$I_{BQ} = \frac{I_{CQ}}{\beta} = \frac{5}{180} = 0.0278 \text{ mA}$$

$$R_1 = R_{TH} = 6 \text{ k}\Omega$$

$$V_{TH} = I_{BQ} R_{TH} + V_{BE(\text{on})} + (1 + \beta) I_{BQ} R_E$$

$$\text{Set } R_E = 20 \Omega$$

$$V_{TH} = (0.0278)(6) + 0.7 + (181)(0.0278)(0.020)$$

$$V_{TH} = 0.967 \text{ V}$$

$$V_{TH} = \frac{1}{R_1} \cdot R_{TH} \cdot V_{CC}$$

$$0.967 = \frac{1}{R_1}(6)(10) \Rightarrow \underline{R_1 = 62.0 \text{ k}\Omega}$$

$$\underline{R_2 = 6.64 \text{ k}\Omega}$$

8.24

$$I_{CQ} = \frac{V_{CC}}{R_L} = \frac{15}{1} = 15 \text{ mA}$$

$$I_{BQ} = \frac{15}{100} = 0.15 \text{ mA}$$

$$\overline{P_L}(\text{max}) = \frac{1}{2} \cdot \frac{V_{CC}^2}{R_L} = \frac{(15)^2}{2(1)} \Rightarrow \overline{P_L}(\text{max}) = 112.5 \text{ mW}$$

$$\text{Let } R_{TH} = 10 \text{ k}\Omega$$

$$V_{TH} = I_{BQ} R_{TH} + V_{BE} + (1 + \beta) I_{BQ} R_E$$

$$= (0.15)(10) + 0.7 + (101)(0.15)(0.1)$$

$$V_{TH} = 3.715 = \frac{1}{R_1} \cdot R_{TH} \cdot V_{CC} = \frac{1}{R_1} \cdot (10)(15)$$

$$\underline{R_1 = 40.4 \text{ k}\Omega}$$

$$\underline{R_2 = 13.3 \text{ k}\Omega}$$

8.25

$$V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right) V_{CC} = \left( \frac{1.55}{1.55 + 0.73} \right) (10) = 6.80 \text{ V}$$

$$R_{TH} = R_1 \parallel R_2 = 0.73 \parallel 1.55 = 0.496 \text{ k}\Omega$$

$$I_{BQ} = \frac{V_{TH} - V_{BE}}{R_{TH} + (1 + \beta) R_E} = \frac{6.80 - 0.70}{0.496 + (26)(0.02)}$$

$$I_{BQ} = 6.0 \text{ mA}, I_{CQ} = 150 \text{ mA}$$

$$A_v = -g_m R'_L \text{ and } R'_L = a^2 R_L = (3)^2 (8) = 72 \Omega$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{150}{0.026} \Rightarrow 5.77 \text{ A/V}$$

$$A_v = -(5.77)(72) = -415$$

$$|V_o'| = |A_v| \cdot V_i = (415)(0.017) = 7.06 \text{ V}$$

$$V_o = \frac{7.06}{3} = 2.35 \text{ V}$$

$$\overline{P_L} = \frac{1}{2} \cdot \frac{V_o'^2}{R_L} = \frac{(2.35)^2}{2(8)} \Rightarrow \overline{P_L} = 345 \text{ mW}$$

$$\overline{P_S} = I_{CQ} \cdot V_{CC} = (0.15)(10) = 1.5 \text{ W}$$

$$\eta = \frac{\overline{P_L}}{\overline{P_S}} = \frac{0.345}{1.5} \Rightarrow \underline{\eta = 23\%}$$

8.26

a. Assuming the maximum power is being delivered, then

$$V_o'(\text{peak}) = 36 \text{ V} \Rightarrow V_o = \frac{36}{4} = 9 \text{ V}$$

$$\Rightarrow V_{\text{rms}} = \frac{9}{\sqrt{2}} \Rightarrow \underline{V_{\text{rms}} = 6.36 \text{ V}}$$

$$\text{b. } V_o = \frac{36}{\sqrt{2}} \Rightarrow \underline{V_o = 25.5 \text{ V}}$$

$$\text{c. Secondary } I_{\text{rms}} = \frac{R_L}{V_{\text{rms}}} = \frac{2}{6.36} \Rightarrow \underline{I_{\text{rms}} = 0.314 \text{ A}}$$


$$\text{Primary } I_P = \frac{0.314}{4} \Rightarrow \underline{I_P = 78.6 \text{ mA}}$$

$$\text{d. } \overline{P_S} = I_{CQ} \cdot V_{CC} = (0.15)(36) = 5.4 \text{ W}$$

$$\eta = \frac{2}{5.4} \Rightarrow \underline{\eta = 37\%}$$

8.27

a.

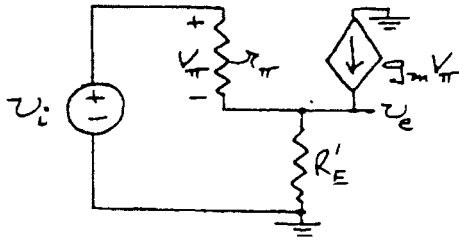

$$\begin{aligned} v_e &= \left( \frac{V_{\pi}}{r_{\pi}} + g_m V_{\pi} \right) R'_E = V_{\pi} \left( \frac{1}{r_{\pi}} + g_m \right) R'_E \\ &= V_{\pi} \left( \frac{1 + \beta}{r_{\pi}} \right) R'_E \end{aligned}$$

$$v_i = V_{\pi} + v_e \Rightarrow V_{\pi} = v_i - v_e$$

$$v_e = (v_i - v_e) \left( \frac{1 + \beta}{r_{\pi}} \right) R'_E$$

$$\frac{v_e}{v_i} = \frac{\frac{1 + \beta}{r_{\pi}} \cdot R'_E}{1 + \frac{1 + \beta}{r_{\pi}} \cdot R'_E} = \frac{(1 + \beta) R'_E}{r_{\pi} + (1 + \beta) R'_E} = \frac{v_e}{v_i}$$

$$\text{where } R'_E = \left( \frac{n_1}{n_2} \right)^2 R_L$$

$$v_o = \frac{v_e}{\left( \frac{n_1}{n_2} \right)} \text{ so } v_e = v_o \left( \frac{n_1}{n_2} \right)$$

$$\text{so } \frac{v_o}{v_i} = \frac{1}{\left( \frac{n_1}{n_2} \right)} \cdot \frac{(1 + \beta) R'_E}{r_{\pi} + (1 + \beta) R'_E}$$

b.  $\overline{P}_L = \frac{1}{2} \cdot I_P^2 R_L$ ,  $a = \frac{n_1}{n_2}$ ,  $I_{CQ} = \frac{I_P}{a}$

$$\text{so } \overline{P}_L = \frac{1}{2} \cdot a^2 I_{CQ}^2 R_L$$

$$\overline{P}_S = I_{CQ} \cdot V_{CC}$$

For  $\eta = 50\%$  :


$$\frac{\overline{P}_L}{\overline{P}_S} = 0.5 = \frac{\frac{1}{2} \cdot a^2 I_{CQ}^2 R_L}{I_{CQ} \cdot V_{CC}} = \frac{a^2 I_{CQ} R_L}{2 V_{CC}}$$

$$\text{so } a^2 = \frac{V_{CC}}{I_{CQ} \cdot R_L} = \frac{V_{CC}}{(0.1)(50)} \Rightarrow a^2 = \frac{V_{CC}}{5}$$

c.  $R_o = \frac{r_{\pi}}{1 + \beta} = \frac{\beta V_T}{(1 + \beta) I_{CQ}} = \frac{49(0.026)}{(50)(0.1)}$   
 $\Rightarrow R_o = 0.255 \Omega$

8.28

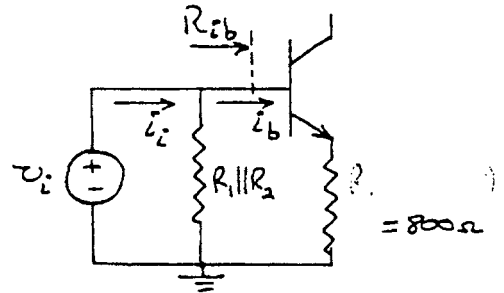a. With a 10:1 transformer ratio, we need a current gain of 8 through the transistor.



$$i_e = (1 + \beta) i_b \text{ and } i_b = \left( \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_{i_b}} \right) i_i$$

so we need

$$\frac{i_e}{i_i} = 8 = (1 + \beta) \left( \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_{i_b}} \right)$$

where

$$\begin{aligned} R_{i_b} &= r_{\pi} + (1 + \beta) R'_L \approx (1 + \beta) R'_L \\ &= (101)(0.8) = 80.8 \end{aligned}$$

$$\text{Then } 8 = (101) \left( \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + 80.8} \right)$$

$$\frac{R_1 \parallel R_2}{R_1 \parallel R_2 + 80.8} = 0.0792 \text{ or } R_1 \parallel R_2 = 6.95 \text{ k}\Omega$$

Set

$$\frac{2V_{CC}}{2I_{CQ}} = R'_L \Rightarrow I_{CQ} = \frac{V_{CC}}{R'_L} = \frac{12}{0.8} = 15 \text{ mA}$$

$$I_{BQ} = \frac{15}{100} = 0.15 \text{ mA}$$

$$V_{TH} = I_{BQ} R_{TH} + V_{BE}$$

$$\frac{1}{R_1} \cdot R_{TH} \cdot V_{CC} = I_{BQ} R_{TH} + V_{BE}$$

$$\frac{1}{R_1} (6.95)(12) = (0.15)(6.95) + 0.7$$

$$\Rightarrow R_1 = 47.9 \text{ k}\Omega \text{ then } R_2 = 8.13 \text{ k}\Omega$$

b.  $I_e = 0.9 I_{CQ} = 13.5 \text{ mA} = \frac{I_L}{a} \Rightarrow I_L = 135 \text{ mA}$

$$\overline{P}_L = \frac{1}{2} (0.135)^2 (8) \Rightarrow \overline{P}_L = 72.9 \text{ mW}$$

$$\overline{P}_S = V_{CC} I_{CQ} = (12)(15) \Rightarrow \overline{P}_S = 180 \text{ mW}$$

$$\eta = \frac{\overline{P}_L}{\overline{P}_S} \Rightarrow \eta = 40.5\%$$

8.29

a.  $V_P = \sqrt{2R_L \overline{P_L}}$   
 $V_P = \sqrt{2(8)(1)} = 5.66 \text{ V} = \text{peak output voltage}$   
 $I_P = \frac{V_P}{R_L} = \frac{5.66}{8} = 0.708 \text{ A} = \text{peak output current}$

Set  $V_e = 0.9V_{CC} = aV_P$  to minimize distortion

Then  $a = \frac{(0.9)(18)}{5.66} \Rightarrow a = 2.86$

b. Now


$I_{CQ} = \frac{1}{0.9} \left( \frac{I_P}{a} \right) = \frac{1}{0.9} \left( \frac{0.708}{2.86} \right) \Rightarrow I_{CQ} = 0.275 \text{ A}$

Then  $P_Q = V_{CC} I_{CQ} = (18)(0.275)$

$\Rightarrow P_Q = 4.95 \text{ W}$  Power rating of transistor

8.30

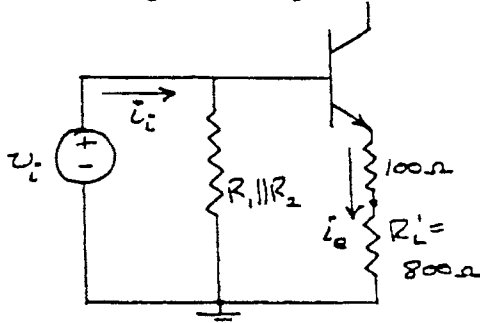a. Need a current gain of 8 through the transistor.



$\frac{i_b}{i_i} = 8 = (1 + \beta) \left( \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_{i_b}} \right)$

where  $R_{i_b} \approx (1 + \beta)(0.9) = 90.9 \text{ k}\Omega$

$\frac{8}{101} = \left( \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + 90.9} \right) = 0.0792$

or  $R_1 \parallel R_2 = 7.82 \text{ k}\Omega$

Set

$\frac{2V_{CC}}{2I_{CQ}} = 0.9 \text{ k}\Omega \Rightarrow I_{CQ} = \frac{12}{0.9} = 13.3 \text{ mA}$

$I_{BQ} = \frac{13.3}{100} = 0.133 \text{ mA}$

Then

$\frac{1}{R_1} (7.82)(12) = (0.133)(7.82) + 0.7$

$\Rightarrow R_1 = 53.9 \text{ k}\Omega$  and  $R_2 = 9.15 \text{ k}\Omega$

b.  $I_e = (0.9)I_{CQ} = 12 \text{ mA} = \frac{I_L}{a} \Rightarrow I_L = 120 \text{ mA}$

$\overline{P_L} = \frac{1}{2} (0.12)^2 (8) \Rightarrow \overline{P_L} = 57.6 \text{ mW}$

$\overline{P_S} = V_{CC} I_{CQ} = (12)(13.3) \Rightarrow \overline{P_S} = 159.6 \text{ mW}$

$\eta = \frac{\overline{P_L}}{\overline{P_S}} = \frac{57.6}{159.6} \Rightarrow \eta = 36.1\%$

8.31

a. All transistors are matched.

$3 \text{ mA} = i_{E1} + i_{E3} = \left( \frac{1 + \beta}{\beta} \right) i_C + \frac{i_C}{\beta}$

$3 = \left( \frac{61}{60} + \frac{1}{60} \right) i_C \Rightarrow i_C = 2.90 \text{ mA}$

b. For  $v_o = 6 \text{ V}$ , let  $R_L = 200 \Omega$ .

$i_o = \frac{6}{200} = 0.03 \text{ A} = 30 \text{ mA} \approx i_{E3}$

$i_{B3} = \frac{30}{61} = 0.492 \text{ mA}$

$i_{E1} = 3 - 0.492 = 2.508 \text{ mA}$

$i_{B1} = \frac{2.508}{61} \Rightarrow i_{B1} = 41.11 \mu\text{A}$

$i_{E2} \approx 3 \text{ mA} \Rightarrow i_{B2} = \frac{3}{61} \Rightarrow 49.18 \mu\text{A}$

$i_I = i_{B2} - i_{B1} = 49.18 - 41.11 \Rightarrow i_I = 8.07 \mu\text{A}$

Current gain

$A_i = \frac{30 \times 10^{-3}}{8.07 \times 10^{-6}} \Rightarrow A_i = 3.72 \times 10^3$

$V_{BE3} = V_T \ln \left( \frac{i_{E3}}{I_S} \right) = (0.026) \ln \left( \frac{30 \times 10^{-3}}{5 \times 10^{-13}} \right)$

$V_{BE3} = 0.6453 \text{ V}$

$V_{BE1} = V_T \ln \left( \frac{i_{E1}}{I_S} \right) = (0.026) \ln \left( \frac{2.508 \times 10^{-3}}{5 \times 10^{-13}} \right)$

$V_{BE1} = 0.5807 \text{ V}$

$v_I = v_o + V_{BE3} - V_{BE1} = 6 + 0.6453 - 0.5807$

$v_I = 6.0646 \text{ V}$

Voltage gain

$A_v = \frac{v_o}{v_I} = \frac{6}{6.0646} \Rightarrow A_v = 0.989$

8.32

a. For  $i_o = 1 \text{ A}$ ,  $I_{B3} \approx \frac{1}{50} \Rightarrow 20 \text{ mA}$

We can then write

$$\frac{10 - V_{EB1}}{R_1} = 2 \left[ \frac{10 - (\nu_{o,\max} + V_{BE3})}{R_1} - 20 \right]$$

If, for simplicity, we assume  $V_{EB1} = V_{BE3} = 0.7 \text{ V}$ , then

$$\frac{10 - V_{BE}}{R_1} = \frac{2\nu_{o,\max}}{R_1} + 40$$

If we assume  $\nu_{o,\max} = 4 \text{ V}$ , then

$$\frac{9.3}{R_1} = \frac{2(4)}{R_1} + 40$$

which yields  $R_1 = R_2 = 32.5 \Omega$

b. For  $\nu_I = 0$ ,

$$I_{E1} = \frac{9.3}{32.5} \Rightarrow I_{E1} = 0.286 \text{ A} = I_{E2}$$

Since  $I_{S3,4} = 10I_{S1,2}$ , then

$$I_{E3} = I_{E4} = 2.86 \text{ A}$$

c. We can write

$$R_o = \frac{1}{2} \left\{ \frac{r_{\pi 3} + R_1 \parallel \frac{r_{\pi 1}}{1 + \beta_1}}{1 + \beta_3} \right\}$$

Now  $r_{\pi 3} = \frac{\beta_3 V_T}{I_{C3}} = \frac{(50)(0.026)}{2.86} = 0.4545 \Omega$

$$r_{\pi 1} = \frac{\beta_1 V_T}{I_{C1}} = \frac{(120)(0.026)}{0.286} = 10.91 \Omega$$

So

$$R_o = \frac{1}{2} \left\{ \frac{0.4545 + 32.5 \parallel \frac{10.91}{121}}{51} \right\}$$

$$32.5 \parallel \frac{10.91}{121} = 32.5 \parallel 0.0902 = 0.0900$$

Then

$$R_o = \frac{1}{2} \left\{ \frac{0.4545 + 0.0900}{51} \right\} \text{ or } R_o = 0.00534 \Omega$$

8.33

$$R_i = \frac{1}{2} \{ r_{\pi 1} + (1 + \beta) [R_1 \parallel (r_{\pi 3} + (1 + \beta) R_L)] \}$$

$$i_{C1} \approx 7.2 \text{ mA and } i_{C3} \approx 7.2 \text{ mA}$$

$$\text{Then } r_{\pi} = \frac{(60)(0.026)}{7.2} = 0.217 \text{ k}\Omega$$

So

$$R_i = \frac{1}{2} \{ 0.217 + (61) [2 \parallel (0.217 + (61)(0.1))] \}$$


$$= \frac{1}{2} \{ 0.217 + 61 [2 \parallel 6.32] \}$$

or

$$R_i = 46.4 \text{ k}\Omega$$

8.34

a.

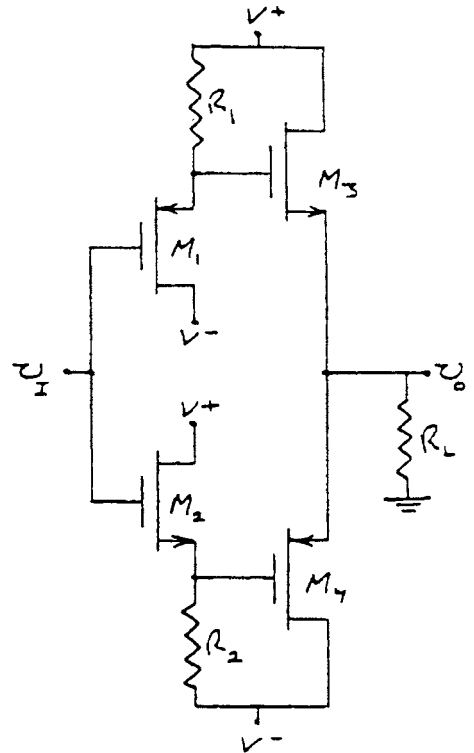

b.  $I_1 = K_1 (V_{SG} + V_{TP})^2 = \frac{V^+ - V_{SG}}{R_1}$

$$5 = 10(V_{SG} - 2)^2 \Rightarrow V_{SG} = 2.707 \text{ V}$$

$$5 = \frac{10 - 2.707}{R_1} \Rightarrow R_1 = R_2 = 1.46 \text{ k}\Omega$$

c.  $R_L = 100 \Omega$  For a sinusoidal output signal:

$$\overline{P_L} = \frac{1}{2} \cdot \frac{(\nu_o)^2}{R_L} = \frac{1}{2} \cdot \frac{(5)^2}{0.1} \Rightarrow \overline{P_L} = 125 \text{ mW}$$

$$i_{D3} \approx \frac{(\nu_o)}{R_L} = \frac{(5)}{0.1} \Rightarrow i_{D3} = 50 \text{ mA}$$

$$V_{GS3} = \sqrt{\frac{50}{10}} + 2 = 4.236 \text{ V}$$

$$I_1 = \frac{10 - (4.236 + 5)}{1.46} \Rightarrow I_{D1} = 0.523 \text{ mA}$$

$$V_{SG1} = \sqrt{\frac{0.523}{10}} + 2 = 2.229 \text{ V}$$

$$\nu_I = 5 + 4.236 - 2.229 \Rightarrow \nu_I = 7.007 \text{ V}$$

$$I_{D2} = \frac{(\nu_I - V_{SG}) - (-10)}{1.46} = 10(V_{SG} - 2)^2$$

$$\frac{17.007 - V_{SG}}{1.46} = 10(V_{SG}^2 - 4V_{SG} + 4)$$

$$14.6V_{SG}^2 - 57.4V_{SG} + 41.4 = 0$$

$$V_{SG} = \frac{57.4 \pm \sqrt{(57.4)^2 - 4(14.6)(41.4)}}{2(14.6)}$$

$$V_{SG2} = 2.98 \text{ V}$$

$$I_{D2} = 10(2.98 - 2)^2 \Rightarrow I_{D2} = 9.60 \text{ mA}$$


$$V_{G4} = \nu_I - V_{GS2} = 7 - 2.98 = 4.02 \text{ V}$$

$$V_{SG4} = 5 - 4.02 = 0.98 \text{ V} \Rightarrow I_{D4} = 0$$

$$I_{E1} = 1.692 \mu\text{A} \Rightarrow I_{C1} = 1.534 \mu\text{A}$$

$$I_{C2} = (50) \left( \frac{10}{11} \right) (1.692) \Rightarrow I_{C2} = 76.9 \mu\text{A}$$
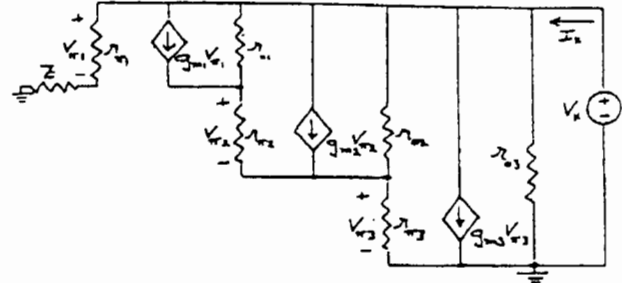
$$I_{C3} = (51)(50) \left( \frac{10}{11} \right) (1.692) \Rightarrow I_{C3} = 3.92 \text{ mA}$$



Because of  $r_{\pi 1}$  and  $Z$ , neglect effect of  $r_o$ . Then neglecting  $r_{o1}$ ,  $r_{o2}$ , and  $r_{o3}$ , we find

$$I_X = g_{m3} V_{\pi 3} + g_{m2} V_{\pi 2} + g_{m1} V_{\pi 1} + \frac{V_X}{r_{\pi 1} + Z}$$

Now

$$V_{\pi 1} = \left( \frac{r_{\pi 1}}{r_{\pi 1} + Z} \right) V_X, \quad V_{\pi 2} \approx g_{m1} V_{\pi 1} r_{\pi 2}$$

and

$$V_{\pi 3} = (g_{m1} V_{\pi 1} + g_{m2} V_{\pi 2}) r_{\pi 3} \\ = [g_{m1} V_{\pi 1} + g_{m2} (g_{m1} V_{\pi 1} r_{\pi 2})] r_{\pi 3}$$

$$V_{\pi 3} = \left( \frac{r_{\pi 1}}{r_{\pi 1} + Z} \right) [g_{m1} + g_{m1} g_{m2} r_{\pi 2}] r_{\pi 3} \cdot V_X$$

$$V_{\pi 3} = \frac{(\beta_1 + \beta_1 \beta_2) r_{\pi 3}}{r_{\pi 1} + Z} \cdot V_X$$

and

$$V_{\pi 2} = g_{m1} \left( \frac{r_{\pi 1}}{r_{\pi 1} + Z} \right) r_{\pi 2} V_X = \left( \frac{\beta_1 r_{\pi 2}}{r_{\pi 1} + Z} \right) V_X$$

Then

$$I_X = \frac{(\beta_1 + \beta_1 \beta_2) \beta_3}{r_{\pi 1} + Z} \cdot V_X + \frac{\beta_1 \beta_2}{r_{\pi 1} + Z} \cdot V_X \\ + \frac{\beta_1}{r_{\pi 1} + Z} \cdot V_X + \frac{V_X}{r_{\pi 1} + Z}$$

Then

$$R_o = \frac{V_X}{I_X} = \frac{r_{\pi 1} + Z}{1 + \beta_1 + \beta_1 \beta_2 + (\beta_1 + \beta_1 \beta_2) \beta_3}$$

$$r_{\pi 1} = \frac{(10)(0.026)}{1.534} = 0.169 \text{ M}\Omega$$

$$Z = 25 \text{ k}\Omega$$

8.35

For  $\nu_o = 0$

$$I_Q = I_{C3} + I_{C2} + I_{E1}$$

$$I_{B3} = I_{E2} = \left( \frac{1 + \beta_n}{\beta_n} \right) I_{C2} = \frac{I_{C3}}{\beta_n}$$

$$I_{C3} = (1 + \beta_n) I_{C2}$$

$$I_{B2} = I_{C1} = \left( \frac{\beta_p}{1 + \beta_p} \right) I_{E1} = \frac{I_{C2}}{\beta_n}$$

$$I_{C2} = \beta_n \left( \frac{\beta_p}{1 + \beta_p} \right) I_{E1}$$

$$I_{C3} = (1 + \beta_n) \beta_n \left( \frac{\beta_p}{1 + \beta_p} \right) I_{E1}$$

$$I_Q = (1 + \beta_n) \beta_n \left( \frac{\beta_p}{1 + \beta_p} \right) I_{E1} \\ + \beta_n \left( \frac{\beta_p}{1 + \beta_p} \right) I_{E1} + I_{E1}$$

$$= (51)(50) \left( \frac{10}{11} \right) I_{E1} + (50) \left( \frac{10}{11} \right) I_{E1} + I_{E1}$$

$$I_Q = 2318.18 I_{E1} + 45.45 I_{E1} + I_{E1}$$

Then

$$R_0 = \frac{169 + 25}{1 + (10) + (10)(50) + [10 + (10)(50)](50)}$$

$$R_0 = \frac{194}{26,011} = 0.00746 \text{ k}\Omega$$

$$\text{or } \underline{R_0 = 7.46 \Omega}$$

8.36

a. Neglect base currents.

$$\begin{aligned} V_{BB} &= 2V_D = 2V_T \ln \left( \frac{I_{B1+s}}{I_S} \right) \\ &= 2(0.026) \ln \left( \frac{5 \times 10^{-3}}{10^{-13}} \right) \\ \Rightarrow \underline{V_{BB} = 1.281 \text{ V}} \end{aligned}$$

$$V_{BE1} + V_{EB3} = V_{BB}$$

$$I_{E1} = I_{E3} + I_{C2}$$

$$I_{B2} = I_{C3} = \left( \frac{\beta_p}{1 + \beta_p} \right) I_{E3}$$

$$I_{C2} = \beta_n I_{B2} = \beta_n \left( \frac{\beta_p}{1 + \beta_p} \right) I_{E3}$$

$$I_{E1} = I_{E3} + \beta_n \left( \frac{\beta_p}{1 + \beta_p} \right) I_{E3}$$

$$I_{E1} = I_{E3} \left[ 1 + \beta_n \left( \frac{\beta_p}{1 + \beta_p} \right) \right]$$

$$\left( \frac{1 + \beta_n}{\beta_n} \right) I_{C1} = \left( \frac{1 + \beta_p}{\beta_p} \right) I_{C3} \left[ 1 + \beta_n \left( \frac{\beta_p}{1 + \beta_p} \right) \right]$$

$$V_{BE1} = V_T \ln \left[ \frac{I_{C1}}{I_S} \right], \quad V_{EB3} = V_T \ln \left[ \frac{I_{C3}}{I_S} \right]$$

$$\begin{aligned} (1.01)I_{C1} &= \left( \frac{21}{20} \right) I_{C3} \left[ 1 + (100) \left( \frac{20}{21} \right) \right] \\ &= I_{C3} \left[ \frac{21}{20} + 100 \right] = 101.05 I_{C3} \end{aligned}$$

$$I_{C1} = 100.05 I_{C3}$$

$$V_T \ln \left( \frac{100.05 I_{C3}}{I_S} \right) + V_T \ln \left( \frac{I_{C3}}{I_S} \right) = V_{BB}$$

$$V_T \ln \left( \frac{100.05 I_{C3}^2}{I_S^2} \right) = V_{BB}$$

$$\frac{100.05 I_{C3}^2}{I_S^2} = \exp \left( \frac{V_{BB}}{V_T} \right)$$

$$I_{C3} = \frac{I_S}{\sqrt{100.05}} \sqrt{\exp \left( \frac{V_{BB}}{V_T} \right)} = \underline{0.4997 \text{ mA} = I_{C3}}$$

$$\text{Then } I_{E3} = 0.5247 \text{ mA}$$

Now

$$I_{C1} = 100.05 I_{C3} = \underline{50 \text{ mA} = I_{C1}}$$

$$I_{C2} = (100) \left( \frac{20}{21} \right) (0.5247) = \underline{49.97 \text{ mA} = I_{C2}}$$

$$\text{b. } v_0 = 10 \text{ V} \Rightarrow i_{E1} \approx \frac{10}{100} = 0.10 \text{ A} = i_{C1}$$

$$i_{B1} = \frac{100}{100} = 1 \text{ mA}$$

$$V_{BB} = 2(0.026) \ln \left( \frac{4 \times 10^{-3}}{10^{-13}} \right) = 1.269 \text{ V}$$

$$V_{BE1} = (0.026) \ln \left( \frac{0.1}{10^{-13}} \right) = 0.7184$$

$$V_{EB3} = 1.269 - 0.7184 = 0.5506 \text{ V}$$

$$I_{C3} = 10^{-13} \exp \left( \frac{0.5506}{0.026} \right) = 0.157 \text{ mA}$$

$$\overline{P_L} = \frac{v_0^2}{R_L} = \frac{(10)^2}{100} \Rightarrow \underline{\overline{P_L} = 1 \text{ W}}$$

$$P_{Q1} = i_{C1} \cdot v_{CE1} = (0.1)(12 - 10) \Rightarrow \underline{P_{Q1} = 0.2 \text{ W}}$$

$$\begin{aligned} P_{Q3} &= i_{C3} \cdot v_{EC3} = (0.157)(10 - [0.7 - 12]) \\ &\Rightarrow \underline{P_{Q3} = 3.34 \text{ mW}} \end{aligned}$$

$$i_{C2} = (100)(i_{C3}) = (100)(0.157) = 15.7 \text{ mA}$$

$$\begin{aligned} P_{Q2} &= i_{C2} \cdot v_{CE2} = (15.7)(10 - [-12]) \\ &\Rightarrow \underline{P_{Q2} = 0.345 \text{ W}} \end{aligned}$$

8.37

$$\begin{aligned} \text{a. } V_{BB} &= 3(0.026) \ln \left( \frac{10 \times 10^{-3}}{2 \times 10^{-12}} \right) \\ &\Rightarrow \underline{V_{BB} = 1.74195 \text{ V}} \end{aligned}$$

$$V_{BE1} + V_{BE2} + V_{EB3} = V_{BB}$$

$$I_{C1} \approx \frac{I_{C2}}{\beta_n}, \quad I_{C3} \approx \frac{I_{C2}}{\beta_n^2}$$

$$V_T \ln \left( \frac{I_{C1}}{I_S} \right) + V_T \ln \left( \frac{I_{C2}}{I_S} \right) + V_T \ln \left( \frac{I_{C3}}{I_S} \right) = V_{BB}$$

$$V_T \ln \left[ \frac{I_{C2}^3}{\beta_n^3 I_S^3} \right] = V_{BB}$$

$$\begin{aligned} I_{C2} &= \beta_n I_S \sqrt[3]{\exp \left( \frac{V_{BB}}{V_T} \right)} \\ &= (20)(2 \times 10^{-12}) \sqrt[3]{\exp \left( \frac{1.74195}{0.026} \right)} \end{aligned}$$

$$I_{C2} = 0.20 \text{ A}, \quad I_{C1} \approx 10 \text{ mA}, \quad I_{C3} \approx 0.5 \text{ mA}$$

$$\begin{aligned} V_{BE1} &= (0.026) \ln \left( \frac{10 \times 10^{-3}}{2 \times 10^{-12}} \right) \\ &\Rightarrow \underline{V_{BE1} = 0.58065 \text{ V}} \end{aligned}$$

$$V_{BE2} = (0.026) \ln \left( \frac{0.2}{2 \times 10^{-12}} \right)$$

$$\Rightarrow V_{BE2} = 0.6585 \text{ V}$$

$$V_{EB3} = (0.026) \ln \left( \frac{0.5 \times 10^{-3}}{2 \times 10^{-12}} \right)$$

$$\Rightarrow V_{EB3} = 0.50276 \text{ V}$$

$$\text{b. } \overline{P_L} = 10 \text{ W} = \frac{1}{2} \cdot \frac{V_o^2}{R_L} = \frac{1}{2} \cdot \frac{V_o^2}{20}$$

$$\Rightarrow V_o(\text{max}) = 20 \text{ V}$$

For  $v_o(\text{max})$  :

$$P_L = \frac{v_o^2}{R_L} = \frac{(20)^2}{20} \Rightarrow \underline{P_L = 20 \text{ W}}$$

$$i_o(\text{max}) = -\frac{20}{20} = -1 \text{ A}$$

$$i_{C3} + i_{C4} + i_{E3} = -i_o(\text{max}) = 1 \text{ A}$$

$$i_{C3} + \frac{i_{C3}}{\beta_n} \cdot \left( \frac{1 + \beta_p}{\beta_p} \right) + \frac{i_{C4}}{\beta_n} \cdot \left( \frac{1 + \beta_p}{\beta_p} \right) = 1$$

$$i_{C3} \left[ 1 + \frac{1}{\beta_n} \cdot \left( \frac{1 + \beta_p}{\beta_p} \right) + \left\{ \frac{1}{\beta_n} \cdot \left( \frac{1 + \beta_p}{\beta_p} \right) \right\}^2 \right] = 1$$

$$i_{C3} \left[ 1 + \frac{1}{20} \cdot \left( \frac{6}{5} \right) + \left( \frac{1}{20} \cdot \frac{6}{5} \right)^2 \right]$$

$$i_{C3} [1 + 0.06 + 0.0036] = 1 \Rightarrow \underline{i_{C3} = 0.940 \text{ A}}$$

$$\underline{i_{C4} = 0.0564 \text{ A}}$$

$$\underline{i_{E3} = 3.38 \text{ mA}}$$

$$i_{C2} = 2.82 \text{ mA}$$

$$V_{EB3} = (0.026) \ln \left( \frac{2.82 \times 10^{-3}}{2 \times 10^{-12}} \right) = 0.5477 \text{ V}$$

$$V_{BE1} + V_{BE2} = 1.74195 - 0.5477 = 1.1942$$

$$V_T \ln \left( \frac{I_{C2}}{\beta_n I_S} \right) + V_T \ln \left( \frac{I_{C2}}{I_S} \right) = 1.1942$$

$$I_{C2} = \sqrt{\beta_n} \cdot I_S \sqrt{\exp \left( \frac{1.1942}{0.026} \right)}$$

$$= \sqrt{20} (18.83) \text{ mA}$$

$$I_{C2} = 84.2 \text{ mA}$$

## Chapter 9

## Exercise Solutions

E9.1

$$A_{CL} = -\frac{R_2}{R_1} = \frac{-100 \text{ k}\Omega}{10 \text{ k}\Omega} \Rightarrow \underline{A_{CL} = -10}$$

$$v_I = 0.25 \text{ V} \Rightarrow \underline{v_O = -2.5 \text{ V}}$$

$$i_1 = \frac{v_I}{R_1} = \frac{0.25}{10 \text{ k}\Omega} = 0.025 \text{ mA} \Rightarrow \underline{i_1 = 25 \mu\text{A}}$$

$$\underline{i_2 = i_1 = 25 \mu\text{A}}$$

$$\underline{R_1 = R_1 = 10 \text{ k}\Omega}$$

E9.2

$$A_{CL} = -\frac{R_2}{R_1} = -15$$

$$R_1 = \underline{R_1 = 20 \text{ k}\Omega} \Rightarrow R_2 = (15)(20 \text{ k}\Omega)$$

$$\underline{R_2 = 300 \text{ k}\Omega}$$

E9.3

(a)  $A_v = \frac{-R_2}{R_1 + R_3}$

$$A_v(\text{min}) = \frac{-100}{19 + 1.3} = -4.926$$

$$A_v(\text{max}) = \frac{-100}{19 + 0.7} = -5.076$$

so  $\underline{4.926 \leq |A_v| \leq 5.076}$

(b)  $i_1(\text{max}) = \frac{0.1}{19 + 0.7} = 5.076 \mu\text{A}$

$$i_1(\text{min}) = \frac{0.1}{19 + 1.3} = 4.926 \mu\text{A}$$

so  $\underline{4.926 \leq i_1 \leq 5.076 \mu\text{A}}$

(c) Maximum current specification is violated.

E9.4

We can write

$$A_{CL} = -\frac{R_2}{R_1} \left(1 + \frac{R_3}{R_4}\right) - \frac{R_3}{R_1}$$

$$R_1 = \underline{R_1 = 10 \text{ k}\Omega}$$

Want  $A_{CL} = -50$  Set  $\underline{R_2 = R_3 = 50 \text{ k}\Omega}$


$$A_{CL} = -50 = -5 \left(1 + \frac{R_3}{R_4}\right) - 5$$

$$1 + \frac{R_3}{R_4} = 9 \Rightarrow \frac{R_3}{R_4} = 8 = \frac{50}{R_4}$$

$$\underline{R_4 = 6.25 \text{ k}\Omega}$$

E9.5
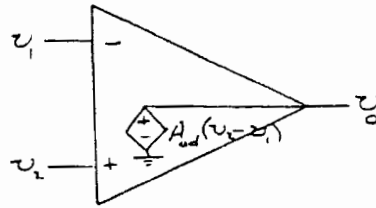
$$v_O = A_d(v_2 - v_1) \quad A_d = 10^3$$



a.  $v_2 = 0, v_O = 5$

$$v_1 = -\frac{v_O}{A_d} = -\frac{5}{10^3} \Rightarrow \underline{v_1 = -5 \text{ mV}}$$

b.  $v_1 = 5, v_O = -10$

$$\frac{v_O}{A_d} = v_2 - v_1$$

$$\frac{-10}{10^3} = v_2 - 5 \Rightarrow \underline{v_2 = 4.99 \text{ V}}$$

c.  $v_1 = 0.001, v_2 = -0.001$

$$v_O = 10^3(-0.001 - 0.001)$$

$$\underline{v_O = -2 \text{ V}}$$

d.  $v_2 = 3, v_O = 3$

$$v_O = A_d(v_2 - v_1)$$

$$\frac{v_O}{A_d} = v_2 - v_1$$

$$\frac{3}{10^3} = 3 - v_1 \Rightarrow \underline{v_1 = 2.997 \text{ V}}$$

E9.6

We have

$$A_{CL} = -\frac{R_2}{R_1} \cdot \frac{1}{\left[1 + \frac{1}{A_d} \left(1 + \frac{R_2}{R_1}\right)\right]}$$

$$\underline{R_1 = R_1 = 25 \text{ k}\Omega} \quad \text{Let } \frac{R_2}{R_1} = x$$

$$-12 = -\frac{x}{1 + \frac{1}{5 \times 10^3}(1 + x)}$$

$$= \frac{-x}{1.0002 + \frac{x}{5 \times 10^3}}$$

$$12 \left(1.0002 + \frac{x}{5 \times 10^3}\right) = x$$

$$12.0024 = x - (2.4 \times 10^{-3})x$$

$$x = \frac{12.0024}{0.9976} = 12.0313 = \frac{R_2}{25 \text{ k}\Omega}$$


$$\underline{R_2 = 300.78 \text{ k}\Omega}$$

E9.7

$$\begin{aligned} v_o &= -\left(\frac{R_4}{R_1}v_{I1} + \frac{R_4}{R_2}v_{I2} + \frac{R_4}{R_3}v_{I3}\right) \\ v_o &= -\left[\left(\frac{40}{10}\right)(250) + \left(\frac{40}{20}\right)(200) + \left(\frac{40}{30}\right)(75)\right] \\ v_o &= -[1000 + 400 + 100] \\ v_o &= -1500 \mu\text{V} = -1.5 \text{ mV} \end{aligned}$$

E9.8
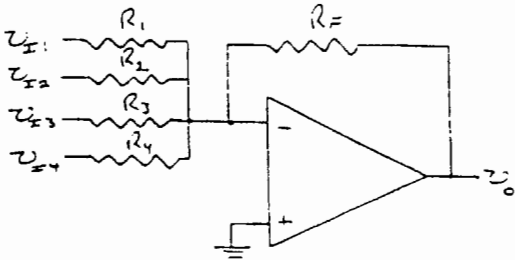
$$v_o = -\left(\frac{R_F}{R_1}v_{I1} + \frac{R_F}{R_2}v_{I2} + \frac{R_F}{R_3}v_{I3} + \frac{R_F}{R_4}v_{I4}\right)$$



We need

$$\frac{R_F}{R_1} = 7, \frac{R_F}{R_2} = 14, \frac{R_F}{R_3} = 3.5, \frac{R_F}{R_4} = 10$$

Set  $R_F = 280 \text{ k}\Omega$

$$\text{Then } R_1 = \frac{280}{7} = 40 \text{ k}\Omega$$

$$R_2 = \frac{280}{14} = 20 \text{ k}\Omega$$

$$R_3 = \frac{280}{3.5} = 80 \text{ k}\Omega$$

$$R_4 = \frac{280}{10} = 28 \text{ k}\Omega$$

E9.9

$$|v_o| = \frac{v_{I1} + v_{I2} + v_{I3}}{3} = \frac{R_F}{R}(v_{I1} + v_{I2} + v_{I3})$$

$$\frac{R_F}{R} = \frac{1}{3} \Rightarrow R_1 = R_2 = R_3 = R = 1 \text{ M}\Omega$$

$$\text{Then } R_F = \frac{1}{3} \text{ M}\Omega = 333 \text{ k}\Omega$$

E9.10

$$A_v = \frac{v_o}{v_I} = \left(1 + \frac{R_2}{R_1}\right) = 5$$

$$\text{so that } \frac{R_2}{R_1} = 4$$


For  $v_o = 10 \text{ V}$ ,  $v_I = 2 \text{ V}$

$$\text{Then } i_1 = \frac{2}{R_1} = 50 \mu\text{A} \Rightarrow R_1 = 40 \text{ k}\Omega$$

Then  $R_2 = 160 \text{ k}\Omega$  we find

$$i_2 = \frac{v_o - v_I}{R_2} = \frac{10 - 2}{160} = 50 \mu\text{A}$$

E9.11

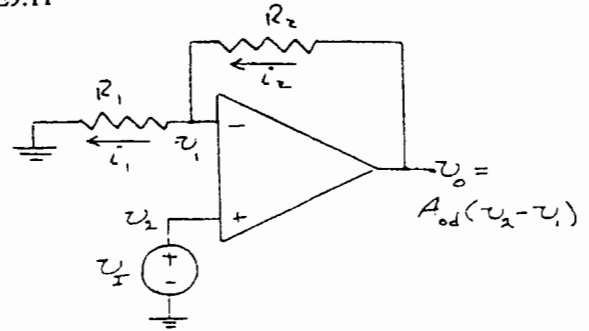

$$v_o = A_{od}(v_2 - v_1) = A_{od}(v_I - v_1)$$

$$\frac{v_o}{A_{od}} - v_I = -v_1 \text{ or } v_1 = v_I - \frac{v_o}{A_{od}}$$

$$i_1 = \frac{v_1}{R_1} = i_2 \text{ and } i_2 = \frac{v_o - v_1}{R_2}$$

$$\text{Then } v_1 \left(\frac{1}{R_1}\right) = \frac{v_o - v_1}{R_2}$$

$$v_1 \left(\frac{1}{R_1} + \frac{1}{R_2}\right) = \frac{v_o}{R_2}$$

$$v_o \left(1 + \frac{R_2}{R_1}\right) v_1 = \left(1 + \frac{R_2}{R_1}\right) \left(v_I - \frac{v_o}{A_{od}}\right)$$

$$\text{So } A_v = \frac{v_o}{v_I} = \frac{\left(1 + \frac{R_2}{R_1}\right)}{1 + \frac{1}{A_{od}} \left(1 + \frac{R_2}{R_1}\right)}$$

E9.12

$$\text{For } v_{I2} = 0, v_2 = \left(\frac{R_b}{R_b + R_a}\right)v_{I1} \text{ and}$$

$$v_o(v_{I1}) = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_b}{R_b + R_a}\right)v_{I1}$$

$$= \left(1 + \frac{70}{5}\right) \left(\frac{50}{50 + 25}\right)v_{I1}$$

$$= 10v_{I1}$$

For  $v_{I1} = 0$ ,

$$v_2 = \left(\frac{R_a}{R_b + R_a}\right)v_{I2}$$

$$v_o(v_{I2}) = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_a}{R_b + R_a}\right)v_{I2}$$

$$= \left(1 + \frac{70}{5}\right) \left(\frac{25}{25 + 50}\right)v_{I2}$$


$$= 5v_{I2}$$

Then

$$v_o = v_o(v_{I1}) + v_o(v_{I2})$$

$$v_o = 10v_{I1} + 5v_{I2}$$

E9.13

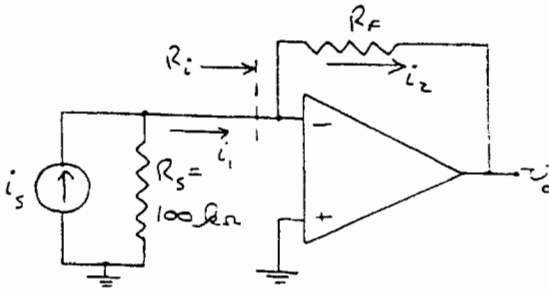

$$R_S \gg R_i \text{ so } i_1 = i_2 = i_S = 100 \mu\text{A}$$

$$v_o = -i_S R_F$$

$$\text{We want } -10 = -(100 \times 10^{-6}) R_F$$

$$\Rightarrow R_F = 100 \text{ k}\Omega$$

E9.14

We may note that

$$\frac{R_3}{R_2} = \frac{3}{1.5} = 2 \text{ and } \frac{R_F}{R_1} = \frac{20}{10} = 2$$

so that

$$\frac{R_3}{R_2} = \frac{R_F}{R_1}$$

Then

$$i_L = \frac{-v_I}{R_2} = \frac{-(-3)}{1.5 \text{ k}\Omega}$$

$$\Rightarrow i_L = 2 \text{ mA}$$

$$v_L = i_L Z_L = (2 \times 10^{-3})(200) = 0.4 \text{ V}$$

$$i_4 = \frac{v_L}{R_2} = \frac{0.4}{1.5 \text{ k}\Omega} = 0.267 \text{ mA}$$

$$i_3 = i_4 + i_L = 0.267 + 2 = 2.267 \text{ mA}$$

$$v_o = i_3 R_3 + v_L = (2.267 \times 10^{-3})(3 \times 10^3) - 0.4$$

$$\Rightarrow v_o = 7.2 \text{ V}$$

E9.15

We want  $i_L = 1 \text{ mA}$  when  $v_I = -5 \text{ V}$

$$i_L = \frac{-v_I}{R_2} \Rightarrow R_2 = \frac{-v_I}{i_L} = \frac{-(-5)}{10^{-3}}$$

$$\Rightarrow R_2 = 5 \text{ k}\Omega$$

$$v_L = i_L Z_L = (10^{-3})(500)$$

$$\Rightarrow v_L = 0.5 \text{ V}$$

$$i_4 = \frac{v_L}{R_2} = \frac{0.5}{5 \text{ k}\Omega} \Rightarrow i_4 = 0.1 \text{ mA}$$

$$i_3 = i_4 + i_L = 0.1 + 1 = 1.1 \text{ mA}$$

If op-amp is biased at  $\pm 10 \text{ V}$ , output must be limited to  $\approx 8 \text{ V}$ .

$$\text{So } v_o = i_3 R_3 + v_L$$

$$8 = (1.1 \times 10^{-3}) R_3 + 0.5$$

$$\Rightarrow R_3 = 6.82 \text{ k}\Omega$$

$$\text{Let } R_3 = 7.0 \text{ k}\Omega$$

Then we want

$$\frac{R_3}{R_2} = \frac{R_F}{R_1} = \frac{7}{5} = 1.4$$

$$\text{Can choose } R_1 = 10 \text{ k}\Omega \text{ and } R_F = 14 \text{ k}\Omega$$

E9.16

Refer to Fig. 9.24

$$R_1 = 2R_2 = 5 \text{ k}\Omega$$

$$\text{Let } R_1 = R_3 = 2.5 \text{ k}\Omega$$

$$\text{Set } R_2 = R_4$$

$$\text{Differential Gain} = \frac{v_o}{v_i} = \frac{R_2}{R_1} = 100 = \frac{R_2}{2.5 \text{ k}\Omega}$$

$$\Rightarrow R_2 = R_4 = 250 \text{ k}\Omega$$

E9.17

We have the general relation that

$$v_o = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{[R_4/R_3]}{1 + [R_4/R_3]}\right) v_{I2} - \frac{R_2}{R_1} v_{I1}$$

$$R_1 = R_3 = 10 \text{ k}\Omega, R_2 = 20 \text{ k}\Omega, R_4 = 21 \text{ k}\Omega$$

$$v_o = \left(1 + \frac{20}{10}\right) \left(\frac{[21/10]}{1 + [21/10]}\right) v_{I2} - \left(\frac{20}{10}\right) v_{I1}$$

$$v_o = 2.0323 v_{I2} - 2.0 v_{I1}$$

a.  $v_{I1} = 1, v_{I2} = -1$

$$v_o = -2.0323 - 2.0 \Rightarrow v_o = -4.032 \text{ V}$$

b.  $v_{I1} = v_{I2} = 1 \text{ V}$

$$v_o = 2.0323 - 2.0 \Rightarrow v_o = 0.0323 \text{ V}$$

c.  $v_{cm} = v_{I1} = v_{I2}$  so common-mode gain

$$A_{cm} = \frac{v_o}{v_{cm}} = 0.0323$$

d.  $CMRR_{dB} = 20 \log_{10} \left(\frac{A_d}{A_{cm}}\right)$

$$A_d = \frac{2.0323}{2} - (2.0) \left(-\frac{1}{2}\right) = 2.016$$

$$CMRR_{dB} = 20 \log_{10} \left(\frac{2.016}{0.0323}\right) = 35.9 \text{ dB}$$

E9.18

$$v_o = -\frac{R_4}{R_3} \left( 1 + \frac{2R_2}{R_1} \right) (v_{I1} - v_{I2})$$

$$\text{Differential gain (magnitude)} = \frac{R_4}{R_3} \left( 1 + \frac{2R_2}{R_1} \right)$$

Minimum Gain  $\Rightarrow$  Maximum  $R_1 = 1 + 50 = 51 \text{ k}\Omega$

$$\text{So } A_d = \frac{20}{20} \left( 1 + \frac{2(100)}{51} \right) \Rightarrow A_d = 4.92$$

Maximum Gain  $\Rightarrow$  Minimum  $R_1 = 1 \text{ k}\Omega$

$$A_d = \frac{20}{20} \left( 1 + \frac{2(100)}{1} \right) \Rightarrow A_d = 201$$

Range of Differential Gain = 4.92-201

Maximum Gain  $\Rightarrow$  Minimum  $R_1$

$$\text{So } \left( 1 + \frac{2R_2}{R_1(\text{min})} \right) = 1000 \text{ or } 2R_2 = 999R_1(\text{min})$$

If  $R_2 = 50 \text{ k}\Omega$ , let  $R_1(\text{min}) = 100 \Omega$  fixed resistor

$$\text{and let } R_1(\text{max}) = \frac{100 \text{ k}\Omega}{\text{pot}} + 100 \Omega = 100.1$$

Then actual differential gain is in the range of

$$\underline{1.999 - 1001}$$

E9.21


$$\begin{aligned} \text{Time constant} = \tau &= R_1 C_2 = (10^4)(0.1 \times 10^{-6}) \\ &= 1 \text{ m sec} \end{aligned}$$

$$0 \leq t \leq 1 \Rightarrow v_o = \frac{-1}{R_1 C_2} \times t$$

$$\text{At } t = 1 \text{ m sec} \Rightarrow v_o = -1 \text{ V}$$

$$0 \leq t \leq 2 \Rightarrow v_o = -1 + \frac{1}{R_1 C_2} \times (t - 1)$$
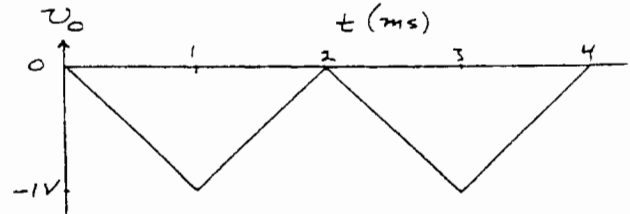
$$\text{At } t = 2 \text{ m sec} \Rightarrow v_o = -1 + \frac{(2 - 1)}{1} = 0$$



E9.22

End of 1st pulse:

$$v_o = \frac{-1}{\tau} \times t \Big|_0^{10 \mu\text{sec}} = \frac{-10 \times 10^{-6}}{\tau}$$

After 10 pulses:

$$v_o = -5 = \frac{-(10)(10 \times 10^{-6})}{\tau}$$

$$\text{So } \tau = \frac{100 \times 10^{-6}}{5} = 20 \mu\text{sec} = \tau$$

$$\tau = R_1 C_2 = 20 \mu\text{sec} = 20 \times 10^{-6}$$

For example,

$$\underline{C_2 = 0.01 \times 10^{-6} = 0.01 \mu\text{F} \Rightarrow R_1 = 2 \text{ k}\Omega}$$

E9.19

$$\text{a. } i_1 = \frac{v_{I1} - v_{I2}}{R_1}$$

$$v_{o1} = v_{I1} + i_1 R_2', \quad v_{o2} = v_{I2} - i_1 R_2 \text{ and}$$

$$v_o = \frac{R_4}{R_3} (v_{o2} - v_{o1})$$

$$v_o = \frac{R_4}{R_3} [v_{I2} - i_1 R_2 - v_{I1} - i_1 R_2']$$

$$v_o = \frac{R_4}{R_3} [(v_{I2} - v_{I1}) - i_1 (R_2 + R_2')]$$

$$v_o = \frac{R_4}{R_3} \left[ (v_{I2} - v_{I1}) - \left( \frac{v_{I2} - v_{I1}}{R_1} \right) (R_2 + R_2') \right]$$

For common-mode input  $v_{I2} = v_{I1}$

$$\Rightarrow v_o = 0 \Rightarrow \underline{\text{Common Gain} = 0, \text{ CMRR} = \infty}$$

b.  $A_d(\text{min}) \Rightarrow R_2' \text{ min}, R_1 \text{ max}$

$$A_d = \left( \frac{20}{20} \right) \left[ 1 + \frac{100 + 95}{51} \right] = 4.82$$

$$A_d(\text{max}) = \left( \frac{20}{20} \right) \left[ 1 + \frac{100 + 105}{1} \right] = 206$$

$$\text{c. } \text{CMRR} = \left| \frac{A_d}{A_{cm}} \right|$$

$$A_{cm} = 0 \Rightarrow \underline{\text{CMRR} = \infty}$$

E9.20

$$\text{Differential Gain} = \frac{R_4}{R_3} \left( 1 + \frac{2R_2}{R_1} \right)$$

Let  $R_3 = R_4$  so the difference amplifier gain is unity.

Minimum Gain  $\Rightarrow$  Maximum  $R_1$

$$\text{So } \left( 1 + \frac{2R_2}{R_1(\text{max})} \right) = 2$$

We want  $2R_2 = R_1(\text{max})$

E9.23

$$v_o = v_{I1} + 10v_{I2} - 25v_{I3} - 80v_{I4}$$

From Figure 9.37,  $v_{I3}$  input to  $R_1$ ,  $v_{I4}$  input to  $R_2$ ,  $v_{I1}$  input to  $R_A$ , and  $v_{I2}$  input to  $R_B$ .

From Equation (9.87)

$$\frac{R_F}{R_1} = 25 \text{ and } \frac{R_F}{R_2} = 80$$

Set  $R_F = 500 \text{ k}\Omega$ , then  $R_1 = 20 \text{ k}\Omega$ , and

$$R_2 = 6.25 \text{ k}\Omega.$$

$$\text{Also } \left(1 + \frac{R_F}{R_N}\right) \left(\frac{R_P}{R_A}\right) = 1$$

$$\text{and } \left(1 + \frac{R_F}{R_N}\right) \left(\frac{R_P}{R_B}\right) = 10$$

where  $R_N = R_1 \parallel R_2 = 20 \parallel 6.25 = 4.76 \text{ k}\Omega$

and  $R_P = R_A \parallel R_B \parallel R_C$

We find that  $\frac{R_A}{R_B} = 10$

Let  $R_A = 200 \text{ k}\Omega$ ,  $R_B = 20 \text{ k}\Omega$

$$\text{Now } \left(1 + \frac{500}{4.76}\right) \left(\frac{R_P}{R_A}\right) = 1 = (106) \left(\frac{R_P}{200}\right)$$

Then  $R_P = 1.89 \text{ k}\Omega$

$$R_A \parallel R_B = 200 \parallel 20 = 18.2 \text{ k}\Omega$$

$$\text{So } R_P = 1.89 = \frac{18.2 R_C}{18.2 + R_C} \Rightarrow R_C = 2.11 \text{ k}\Omega$$

E9.25

$$\begin{aligned} v_{o1} &= \left[ \frac{R - \Delta R}{(R - \Delta R) + (R + \Delta R)} \right. \\ &\quad \left. - \frac{R + \Delta R}{(R + \Delta R) + (R - \Delta R)} \right] V^+ \\ &= \left[ \frac{R - \Delta R}{2R} - \frac{R + \Delta R}{2R} \right] V^+ \\ &= \left( \frac{R - \Delta R - R - \Delta R}{2R} \right) V^+ \end{aligned}$$

$$v_{o1} = -\left(\frac{\Delta R}{R}\right) V^+$$

For  $V^+ = 3.5 \text{ V}$ ,  $\Delta R = 50$ ,  $R = 10 \times 10^3$

$$v_{o1} = -\left(\frac{50}{10^4}\right)(3.5) = -1.75 \times 10^{-2}$$

Need an amplifier with a gain of

$$A_d = \frac{v_o}{v_i} = \frac{5}{-1.75 \times 10^{-2}} \Rightarrow A_d = -285.7$$

Use instrumentation amplifier, Fig. 9-25.

Connect  $v_{o1}$  to  $v_{I1}$  and  $(-v_{o1})$  to  $v_{I2}$ .

$$|A_d| = \left(\frac{R_4}{R_3}\right) \left(1 + \frac{2R_2}{R_1}\right) = 285.7$$

Let  $R_4 = 150 \text{ k}\Omega$ ,  $R_3 = 10 \text{ k}\Omega$  Then  $\frac{R_2}{R_1} = 9.02$

Let  $R_2 = 100 \text{ k}\Omega$ ,  $R_1 = 11.1 \text{ k}\Omega$

E9.26

$$\begin{aligned} v_{o1} &= \left[ \frac{1}{2} - \frac{R}{R + R(1 + \delta)} \right] V^+ \\ &= \left[ \frac{R + R(1 + \delta) - 2R}{2(R + R(1 + \delta))} \right] V^+ \\ &= \frac{R\delta}{2R(2 + \delta)} \times V^+ \end{aligned}$$

$$v_{o1} \approx \left(\frac{\delta}{4}\right) V^+$$

$V^+ = 5$  For  $\delta = 0.01$

$$v_{o1} = \left(\frac{0.01}{4}\right)(5) = 0.0125$$

Need a gain

$$A_d = \frac{v_o}{v_{o1}} = \frac{5}{0.0125} = 400$$

Use an instrumentation amplifier

$$A_d = 400 = \left(\frac{R_4}{R_3}\right) \left(1 + \frac{2R_2}{R_1}\right)$$

Let  $R_4 = 150 \text{ k}\Omega$ ,  $R_3 = 10 \text{ k}\Omega$ , then  $\frac{R_2}{R_1} = 12.8$

Let  $R_2 = 150 \text{ k}\Omega$ ,  $R_1 = 11.7 \text{ k}\Omega$



## Chapter 9

## Problem Solutions

9.1

$$\left. \begin{array}{l} A_v = -\frac{200}{20} = -10 \\ \text{and} \\ R_1 = 20 \text{ k}\Omega \end{array} \right\} \text{for each case}$$

9.2

$$\text{a. } A_v = -\frac{100}{10} = -10$$

$$R_1 = R_2 = 10 \text{ k}\Omega$$

$$\text{b. } A_v = -\frac{100 \parallel 100}{10} = -5$$

$$R_1 = R_2 = 10 \text{ k}\Omega$$

$$\text{c. } A_v = -\frac{100}{10 \parallel 10} = -20$$

$$R_1 = 10 \parallel 10 = 5 \text{ k}\Omega$$

9.3

$$A_v = -\frac{R_2}{R_1} = -12 \Rightarrow R_2 = 12R_1$$

$$R_1 = R_2 = 25 \text{ k}\Omega$$

$$\Rightarrow R_2 = (12)(25) = 300 \text{ k}\Omega$$

9.4

$$A_v = -\frac{R_2}{R_1} = -8 \Rightarrow R_2 = 8R_1$$

$$\text{For } \nu_f = -1, i_1 = \frac{1}{R_1} = 15 \mu\text{A} \Rightarrow R_1 = 66.7 \text{ k}\Omega$$

$$\Rightarrow R_2 = 533.3 \text{ k}\Omega$$

9.5

$$A_v = -\frac{R_2}{R_1} = -30 \Rightarrow R_2 = 30R_1$$

$$\text{Set } R_2 = 1 \text{ M}\Omega$$

$$\Rightarrow R_1 = 33.3 \text{ k}\Omega$$

9.6

$$\text{a. } A_v = \frac{R_2}{R_1} \Rightarrow \frac{1.05R_2}{0.95R_1} = 1.105 \left( \frac{R_2}{R_1} \right)$$

$$\frac{0.95R_2}{1.05R_1} = 0.905 \left( \frac{R_2}{R_1} \right)$$

Deviation in gain is +10.5% and -9.5%

$$\text{b. } A_v \Rightarrow \frac{1.01R_2}{0.99R_1} = 1.02 \left( \frac{R_2}{R_1} \right)$$

$$\Rightarrow \frac{0.99R_2}{1.01R_1} = 0.98 \left( \frac{R_2}{R_1} \right)$$

Deviation in gain =  $\pm 2\%$

9.7

$$\text{(a) } A_v = \frac{\nu_o}{\nu_i} = \frac{-15}{1} = -15$$

$$\nu_o = -15\nu_i \Rightarrow \nu_o = -150 \sin \alpha \text{ (mV)}$$

$$\text{(b) } i_2 = i_1 = \frac{\nu_i}{R_1} = 10 \sin \alpha \text{ (}\mu\text{A)}$$

$$i_L = \frac{\nu_o}{R_L} \Rightarrow i_L = -37.5 \sin \alpha \text{ (}\mu\text{A)}$$

$$i_o = i_L - i_2$$

$$i_o = -47.5 \sin \alpha \text{ (}\mu\text{A)}$$

9.8

$$A_v = -\frac{R_2}{R_1 + R_3}$$

$$A_v = -30 \pm 2.5\% \Rightarrow 29.25 \leq |A_v| \leq 30.75$$

$$\text{So } \frac{R_2}{R_1 + 2} = 29.25 \text{ and } \frac{R_2}{R_1 + 1} = 30.75$$

$$\text{We have } 29.25(R_1 + 2) = 30.75(R_1 + 1)$$

$$\text{Which yields } R_1 = 18.5 \text{ k}\Omega \text{ and } R_2 = 599.6 \text{ k}\Omega$$

For  $\nu_i = 25 \text{ mV}$ , then

$$0.731 \leq |\nu_o| \leq 0.769 \text{ V}$$

9.9

$$\nu_{o1} = -\left(\frac{50}{10}\right)\nu_i = (-5)(0.15) \Rightarrow \nu_{o1} = -0.75 \text{ V}$$

$$\nu_o = -\frac{150}{25} \cdot \nu_{o1} = (-6)(-0.75) \Rightarrow \nu_o = 4.5 \text{ V}$$

$$i_1 = i_2 = \frac{0.15}{10} \Rightarrow i_1 = i_2 = 15 \mu\text{A}$$

$$i_3 = i_4 = \frac{\nu_{o1}}{R_3} = -\frac{0.75}{25} \Rightarrow i_3 = i_4 = -30 \mu\text{A}$$

First op-amp must sink  $15 + 30 = 45 \mu\text{A}$

9.10

(a)  $A_v = -\frac{R_2}{R_1} = -\frac{22}{1} \Rightarrow A_v = -22$

(b)  $A_v = -\frac{R_2}{R_1} \cdot \frac{1}{\left[1 + \frac{1}{A_{nd}} \left(1 + \frac{R_2}{R_1}\right)\right]}$   
 $= -\frac{22}{1} \cdot \frac{1}{\left[1 + \frac{1}{1.5 \times 10^5} \left(1 + \frac{22}{1}\right)\right]} = -\frac{22}{1} \cdot \frac{1}{1.000153} \Rightarrow$

$A_v = -21.99663$

(c)  $|A_v| = 22 - 1\% = 22 - 0.22 = 21.78$

Then  $21.78 = \frac{22}{1} \cdot \frac{1}{\left[1 + \frac{1}{A_{nd}} (23)\right]} \Rightarrow A_{nd} = 2277$

9.11

$A_v = -\frac{R_2}{R_1} \left(1 + \frac{R_3}{R_4} + \frac{R_3}{R_2}\right)$

a.  $-10 = -\frac{R_2}{100} \left(1 + \frac{100}{100} + \frac{100}{R_2}\right)$

$10 = \frac{2R_2}{100} + 1 \Rightarrow R_2 = 450 \text{ k}\Omega$

b.  $100 = \frac{2R_2}{100} + 1 \Rightarrow R_2 = 4.95 \text{ M}\Omega$

9.12

a.  $A_v = -\frac{R_2}{R_1} \left(1 + \frac{R_3}{R_4} + \frac{R_3}{R_2}\right)$

$R_1 = 500 \text{ k}\Omega$

$80 = \frac{R_2}{500} \left(1 + \frac{R_3}{R_4} + \frac{R_3}{R_2}\right)$

Set  $R_2 = R_3 = 500 \text{ k}\Omega$

$80 = 1 \left(1 + \frac{500}{R_4} + 1\right) = 2 + \frac{500}{R_4}$

$\Rightarrow R_4 = 6.41 \text{ k}\Omega$

b. For  $v_I = -0.05 \text{ V}$


$i_1 = i_2 = \frac{-0.05}{500 \text{ k}\Omega} \Rightarrow i_1 = i_2 = -0.1 \mu\text{A}$

$v_X = -i_2 R_2 = -(-0.1 \times 10^{-6})(500 \times 10^3)$   
 $= 0.05$

$i_4 = -\frac{v_X}{R_4} = -\frac{0.05}{6.41} \Rightarrow i_4 = -7.80 \mu\text{A}$

$i_3 = i_2 + i_4 = -0.1 - 7.80 \Rightarrow i_3 = -7.90 \mu\text{A}$

9.13

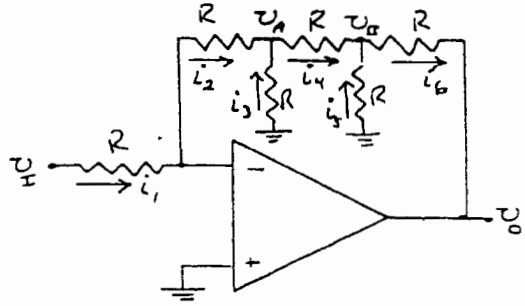

$i_1 = \frac{v_I}{R} = i_2$

$v_A = -i_2 R = -\left(\frac{v_I}{R}\right) R = -v_I$

$i_3 = -\frac{v_A}{R} = \frac{v_I}{R}$

$i_4 = i_2 + i_3 = -\frac{v_A}{R} - \frac{v_A}{R} = -\frac{2v_A}{R} = \frac{2v_I}{R}$

$v_B = v_A - i_4 R = -v_I - \left(\frac{2v_I}{R}\right) (R) = -3v_I$

$i_5 = -\frac{v_B}{R} = -\frac{(-3v_I)}{R} = \frac{3v_I}{R}$

$i_6 = i_4 + i_5 = \frac{2v_I}{R} + \frac{3v_I}{R} = \frac{5v_I}{R}$

$v_O = v_B - i_6 R = -3v_I - \left(\frac{5v_I}{R}\right) R$

$\Rightarrow \frac{v_O}{v_I} = -8$

From Figure 9.11  $\Rightarrow A_v = -3$

9.14

(a)  $A_v = -\frac{R_2}{R_1} \cdot \frac{1}{\left[1 + \frac{1}{A_{nd}} \left(1 + \frac{R_2}{R_1}\right)\right]}$   
 $= -\frac{50}{10} \cdot \frac{1}{\left[1 + \frac{1}{2 \times 10^5} \left(1 + \frac{50}{10}\right)\right]} \Rightarrow A_v = -4.99985$

(b)  $v_O = -(4.99985)(100 \times 10^{-3}) \Rightarrow$   
 $v_O = -499.985 \text{ mV}$

(c) Error =  $\frac{0.5 - 0.499985}{0.5} \times 100\% \Rightarrow 0.003\%$

9.15

a. From Equation (9.23)


$$A_v = -\frac{R_2}{R_1} \cdot \frac{1}{\left[1 + \frac{1}{A_{od}} \left(1 + \frac{R_2}{R_1}\right)\right]}$$

$$= -\frac{100}{100} \cdot \frac{1}{\left[1 + \frac{1}{10^3} \left(1 + \frac{100}{100}\right)\right]} = -0.9980$$

$$\text{Then } v_o = A_v \cdot v_I = (-0.9980)(2)$$

$$\Rightarrow v_o = -1.9960$$

b.

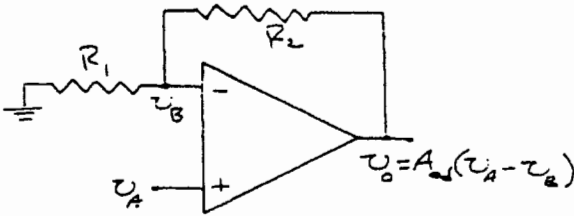

$$v_o = A_{od}(v_A - v_B)$$

$$\frac{v_B}{R_1} = \frac{v_o - v_B}{R_2} \Rightarrow v_B \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{v_o}{R_2}$$

$$v_B = \frac{v_o}{\left(1 + \frac{R_2}{R_1}\right)}$$

$$\text{Then } v_o = A_{od}v_A - \frac{A_{od}v_o}{\left(1 + \frac{R_2}{R_1}\right)}$$

$$v_o \left[ 1 + \frac{A_{od}}{\left(1 + \frac{R_2}{R_1}\right)} \right] = A_{od}v_A$$

$$v_o \left[ \frac{\left(1 + \frac{R_2}{R_1}\right) + A_{od}}{\left(1 + \frac{R_2}{R_1}\right)} \right] = A_{od}v_A$$

$$v_o = \frac{A_{od} \left(1 + \frac{R_2}{R_1}\right) v_A}{A_{od} + \left(1 + \frac{R_2}{R_1}\right)}$$

$$v_o = \frac{\left(1 + \frac{R_2}{R_1}\right) v_A}{1 + \frac{1}{A_{od}} \left(1 + \frac{R_2}{R_1}\right)}$$

So

$$v_o = \frac{\left(1 + \frac{10}{10}\right) \left(\frac{v_I}{2}\right)}{1 + \frac{1}{10^3} \left(1 + \frac{10}{10}\right)} = 0.9980v_I$$

$$\text{For } v_I = 2 \text{ V}$$

$$v_o = 1.9960 \text{ V}$$

9.16

$$(a) i_i = \frac{v_I}{R_1} = i_2 = -\frac{v_o}{R_2} \Rightarrow \frac{v_o}{v_I} = -\frac{R_2}{R_1}$$

$$(b) i_2 = i_1 = \frac{v_I}{R_1} = i_3 + \frac{v_o}{R_L} = i_3 + \frac{1}{R_L} \left( -\frac{R_2}{R_1} v_I \right)$$

$$\text{Then } i_3 = \frac{v_I}{R_1} \left( 1 + \frac{R_2}{R_L} \right)$$

9.17

$$V_{x,\max} = \left( \frac{R_3 \parallel R_1}{R_3 \parallel R_1 + R_4} \right) \cdot V^* = \left( \frac{0.1 \parallel 1}{0.1 \parallel 1 + 10} \right) (10) \Rightarrow$$

$$V_{x,\max} = 0.09008 \text{ V}$$

$$|v_o| = \frac{R_2}{R_1} \cdot V_{x,\max}$$

$$10 = \frac{R_2}{R_1} (0.09008) \Rightarrow \frac{R_2}{R_1} = 111$$

$$\text{So } R_2 = 111 \text{ k}\Omega$$

9.18

$$v_o = A_{oL}(v_2 - v_1)$$

$$a. A_{oL} = \frac{1}{[1 - (-1)] \times 10^{-3}} \Rightarrow A_{oL} = 500$$

$$b. 1 = 500(v_2 - 1 \times 10^{-3}) \Rightarrow v_2 = 3 \text{ mV}$$

$$c. 5 = 500(1 - v_1) \Rightarrow v_1 = 0.99 \text{ V}$$

$$d. v_o = 500(-1 - (-1)) \Rightarrow v_o = 0$$

$$e. -3 = 500(v_2 - (-0.5)) \Rightarrow v_2 = -0.506 \text{ V}$$

9.19

$$a. v_o = -\frac{R_F}{R_1} \cdot v_{I1} - \frac{R_F}{R_2} \cdot v_{I2} - \frac{R_F}{R_3} \cdot v_{I3}$$

$$v_o = -\frac{80}{20}(0.5) - \frac{80}{40}(-1) - \frac{80}{60}(2)$$

$$= -4(0.5) - 2(-1) - 1.33(2)$$

$$v_o = -2.667 \text{ V}$$

$$b. -6.2 = -4(1) - 2(0.25) - 1.33v_{I3}$$

$$v_{I3} = 0.525$$

9.20

$$v_o = -8v_{I1} - 2v_{I2} - 5v_{I3}$$

$$= -\frac{R_F}{R_1}v_{I1} - \frac{R_F}{R_2}v_{I2} - \frac{R_F}{R_3}v_{I3}$$

$$\frac{R_F}{R_1} = 8 \quad \frac{R_F}{R_2} = 2 \quad \frac{R_F}{R_3} = 5$$

Let  $R_F = 500 \text{ k}\Omega \Rightarrow R_1 = 62.5 \text{ k}\Omega$   
 $R_2 = 250 \text{ k}\Omega$   
 $R_3 = 100 \text{ k}\Omega$

9.21

$$v_o = -4v_{I1} - 0.5v_{I2} = -\frac{R_F}{R_1}v_{I1} - \frac{R_F}{R_2}v_{I2}$$

$$\frac{R_F}{R_1} = 4 \quad \frac{R_F}{R_2} = 0.5$$

$\Rightarrow R_1$  is the smallest resistor

$$|i| = 100 \mu\text{A} = \frac{v_I}{R_1} = \frac{2}{R_1} \Rightarrow R_1 = 20 \text{ k}\Omega$$

$$\Rightarrow R_F = 80 \text{ k}\Omega$$

$$\Rightarrow R_2 = 160 \text{ k}\Omega$$

9.22

$$v_{I1} = (0.05)\sqrt{2} \sin(2\pi ft) = 0.0707 \sin(2\pi ft)$$


$$f = 1 \text{ kHz} \Rightarrow T = \frac{1}{10^3} \Rightarrow 1 \text{ ms}$$

$$v_{I2} \Rightarrow T_2 = \frac{1}{100} \Rightarrow 10 \text{ ms}$$

$$v_o = -\frac{R_F}{R_1}v_{I1} - \frac{R_F}{R_2}v_{I2} = -\frac{10}{1}v_{I1} - \frac{10}{5}v_{I2}$$

$$v_o = -(10)(0.0707 \sin(2\pi ft)) - (2)(\pm 1 \text{ V})$$
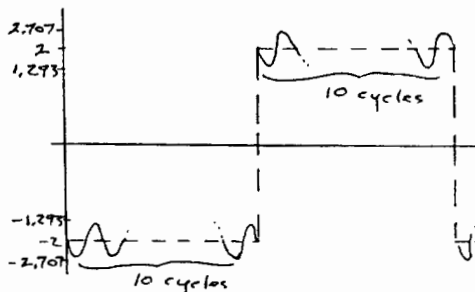
$$v_o = -0.707 \sin(2\pi ft) - (\pm 2 \text{ V})$$



9.23

$$v_o = -\frac{R_F}{R_1}v_{I1} - \frac{R_F}{R_2}v_{I2} - \frac{R_F}{R_3}v_{I3}$$

$$v_o = -\frac{20}{10}v_{I1} - \frac{20}{5}v_{I2} - \frac{20}{2}v_{I3}$$

$$K \sin \alpha x = -2v_{I1} - 4[2 + 100 \sin \alpha x] - 30$$

Set  $v_{I1} = -4$

9.24

a.

$$v_o = -\frac{R_F}{R_3} \cdot a_3(-5) - \frac{R_F}{R_2} \cdot a_2(-5) - \frac{R_F}{R_1} \cdot a_1(-5) - \frac{R_F}{R_o} \cdot a_o(-5)$$

So  $v_o = \frac{R_F}{10} \left[ \frac{a_3}{2} + \frac{a_2}{4} + \frac{a_1}{8} + \frac{a_o}{16} \right] (5)$

b.  $v_o = 2.5 = \frac{R_F}{10} \cdot \frac{1}{2} \cdot 5 \Rightarrow R_F = 10 \text{ k}\Omega$

c. i.  $v_o = \frac{10}{10} \cdot \frac{1}{16} \cdot 5 \Rightarrow v_o = 0.3125 \text{ V}$

ii.  $v_o = \frac{10}{10} \left[ \frac{1}{2} + \frac{1}{4} + \frac{1}{8} + \frac{1}{16} \right] (5)$   
 $\Rightarrow v_o = 4.6875 \text{ V}$


9.25

(a)  $v_{o1} = -\frac{10}{1}v_{I1}$   
 $v_o = -\frac{20}{1}v_{o1} - \frac{20}{1}v_{I2} = -(20)(-10)v_{I1} - (20)v_{I2}$   
 $v_o = 200v_{I1} - 20v_{I2}$

(b)  $v_{I1} = 1 + 2 \sin \alpha x \text{ (mV)}$   
 $v_{I2} = -10 \text{ mV}$   
 Then  $v_o = 200(1 + 2 \sin \alpha x) - 20(-10)$   
 So  $v_o = 0.4 + 0.4 \sin \alpha x \text{ (V)}$

9.26

For one-input

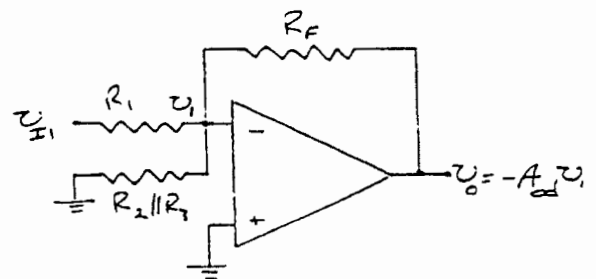

$$v_i = -\frac{v_o}{A_{od}}$$

$$\frac{v_{I1} - v_i}{R_1} = \frac{v_i}{R_2 \parallel R_3} + \frac{v_i - v_o}{R_F}$$

$$\frac{v_{I1}}{R_1} = v_i \left[ \frac{1}{R_1} + \frac{1}{R_2 \parallel R_3} + \frac{1}{R_F} \right] - \frac{v_o}{R_F}$$

$$= -\frac{v_o}{A_{od}} \left[ \frac{1}{R_1} + \frac{1}{R_2 \parallel R_3} + \frac{1}{R_F} \right] - \frac{v_o}{R_F}$$

$$= -v_o \left\{ \frac{1}{A_{od} R_F} + \frac{1}{R_F} + \frac{1}{A_{od}} \left( \frac{1}{R_1} + \frac{1}{R_2 \parallel R_3} \right) \right\}$$

$$= -\frac{v_o}{R_F} \left\{ \frac{1}{A_{od}} + 1 + \frac{1}{A_{od}} \cdot \frac{R_F}{R_1 \parallel R_2 \parallel R_3} \right\}$$

$$v_o = -\frac{R_F}{R_1} \cdot v_{I1} \cdot \left\{ \frac{1}{1 + \frac{1}{A_{od}} \left( 1 + \frac{R_F}{R_P} \right)} \right\}$$

where  $R_P = R_1 \parallel R_2 \parallel R_3$

Therefore, for three-inputs

$$v_o = \frac{-1}{1 + \frac{1}{A_{od}} \left( 1 + \frac{R_F}{R_P} \right)} \times \left( \frac{R_F}{R_1} \cdot v_{I1} + \frac{R_F}{R_2} \cdot v_{I2} + \frac{R_F}{R_3} \cdot v_{I3} \right)$$

9.27


$$A_v = \left( 1 + \frac{R_2}{R_1} \right) = 10$$

$$\frac{R_2}{R_1} = 9$$

$$|i| = \frac{v_I}{R_1} = \frac{0.8}{R_1} = 100 \mu A$$

$$\Rightarrow \underline{R_1 = 8 \text{ k}\Omega, R_2 = 72 \text{ k}\Omega}$$

9.28

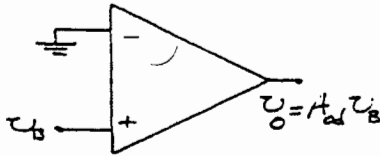

$$v_B = \left( \frac{1}{1 + 500} \right) v_I. \quad v_o = A_{od} \left( \frac{1}{501} \right) v_I$$

a.  $2.5 = A_{od} \left( \frac{1}{501} \right) (5) \Rightarrow \underline{A_{od} = 250.5}$

b.  $v_o = 5000 \left( \frac{1}{501} \right) (5) \Rightarrow \underline{v_o = 49.9 \text{ V}}$

9.29

$$v_o = \left( 1 + \frac{50}{50} \right) \left[ \left( \frac{20}{20 + 40} \right) v_{I2} + \left( \frac{40}{20 + 40} \right) v_{I1} \right]$$

$$\underline{v_o = 1.33 v_{I1} + 0.667 v_{I2}}$$


9.30

$$v_o = \left( 1 + \frac{100}{50} \right) \times \left[ \left( \frac{10 \parallel 40}{10 \parallel 40 + 20} \right) v_{I1} + \left( \frac{10 \parallel 20}{10 \parallel 20 + 40} \right) v_{I2} \right]$$

$$v_o = 3 \left[ \left( \frac{8}{8 + 20} \right) v_{I1} + \left( \frac{6.67}{6.67 + 40} \right) v_{I2} \right]$$

$$\underline{v_o = 0.857 v_{I1} + 0.429 v_{I2}}$$

9.31

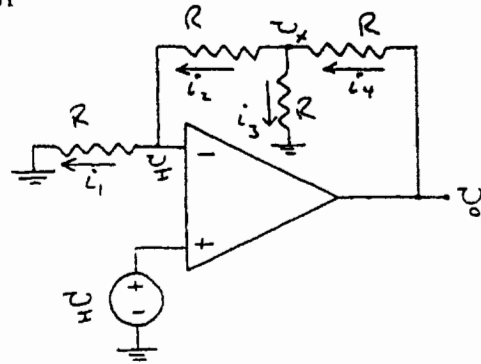

$$i_1 = \frac{v_I}{R} = i_2$$

$$v_x = i_2 R + v_I = \left( \frac{v_I}{R} \right) R + v_I = 2v_I$$

$$i_3 = \frac{v_x}{R} = \frac{2v_I}{R}$$

$$i_4 = i_2 + i_3 = \frac{v_I}{R} + \frac{2v_I}{R} = \frac{3v_I}{R}$$

$$v_o = i_4 R + v_x = \left( \frac{3v_I}{R} \right) R + 2v_I$$

$$\underline{\frac{v_o}{v_I} = 5}$$

9.32

(a)  $\frac{v_o}{v_I} = 1$

(b) From Exercise 9.11


$$\frac{v_o}{v_I} = \frac{\left( 1 + \frac{R_2}{R_1} \right)}{\left[ 1 + \frac{1}{A_{od}} \left( 1 + \frac{R_2}{R_1} \right) \right]}$$

But  $R_2 = 0, R_1 = \infty$

$$\frac{v_o}{v_I} = \frac{1}{1 + \frac{1}{A_{od}}} = \frac{1}{1 + \frac{1}{15 \times 10^5}} \Rightarrow \underline{\frac{v_o}{v_I} = 0.99999}$$

(b) Want  $\frac{v_o}{v_I} = 0.990 = \frac{1}{1 + \frac{1}{A_{od}}} \Rightarrow \underline{A_{od} = 99}$

9.33

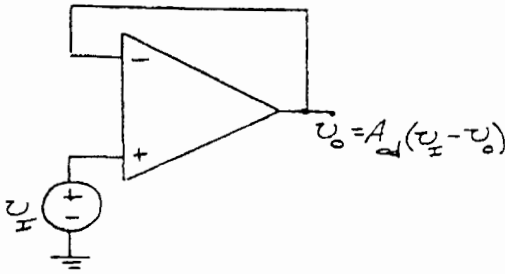

$$v_o = A_{od}(v_I - v_o)$$

$$\left(\frac{1}{A_{od}} + 1\right)v_o = v_I$$

$$v_o = \frac{v_I}{\left(1 + \frac{1}{A_{od}}\right)}$$

$$A_{od} = 10^4; \frac{v_o}{v_I} = 0.99990$$

$$A_{od} = 10^3; \frac{v_o}{v_I} = 0.9990$$

$$A_{od} = 10^2; \frac{v_o}{v_I} = 0.990$$

$$A_{od} = 10; \frac{v_o}{v_I} = 0.909$$

9.34

$$v_{o1} = \left(1 + \frac{R_2}{R_1}\right)v_I$$

$$v_{o1} = \left(1 + \frac{R_2}{R_1}\right)v_I, \quad v_{o2} = -\left(1 + \frac{R_2}{R_1}\right)v_I$$

So  $v_{o1} = -v_{o2}$

9.35

(a)  $i_L = \frac{v_I}{R_1}$

(b)  $v_{o1} = i_L R_L + v_I = i_L R_L + i_L R_1$   
 $v_{o1}(\max) \cong 8V = i_L(1+9) = 10i_L$   
 So  $i_L(\max) \cong 0.8\text{ mA}$   
 Then  $v_I(\max) \cong i_L R_1 = (0.8)(9) \Rightarrow v_I(\max) \cong 7.2V$

9.36

(a)  $v_x = \left(\frac{20}{20+40}\right)v_I = \left(\frac{20}{60}\right)(6) = 2$   
 $v_o = 2V$

(b) Same as (a)

(c)  $v_x = \left(\frac{6}{6+48}\right)(6) = 0.666V$   
 $v_o = \left(1 + \frac{10}{10}\right)v_x \Rightarrow v_o = 1.33V$

9.37

a.  $R_{in} = \frac{v_1}{i_1}$  and  $\frac{v_1 - v_o}{R_F} = i_1$  and  $v_o = -A_{od}v_1$

So  $i_1 = \frac{v_1 - (-A_{od}v_1)}{R_F} = \frac{v_1(1 + A_{od})}{R_F}$

Then  $R_{in} = \frac{v_1}{i_1} = \frac{R_F}{1 + A_{od}}$

b.  $i_1 = \left(\frac{R_S}{R_S + R_{in}}\right)i_S$  and  $v_o = -A_{od} \cdot \frac{R_F}{1 + A_{od}} \cdot i_1$

So  $v_o = -R_F \left(\frac{A_{od}}{1 + A_{od}}\right) \left(\frac{R_S}{R_S + R_{in}}\right)i_S$


$R_{in} = \frac{R_F}{1 + A_{od}} = \frac{10}{1001} = 0.009990$

$v_o = -R_F \left(\frac{1000}{1001}\right) \left(\frac{R_S}{R_S + 0.009990}\right)i_S$

Want  $\left(\frac{1000}{1001}\right) \left(\frac{R_S}{R_S + 0.009990}\right) \geq 0.990$

which yields  $R_S \geq 1.099\text{ k}\Omega$

9.38

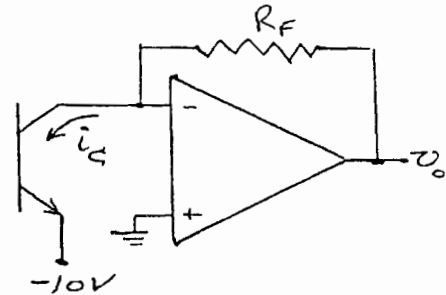

$v_o = i_c R_F, \quad 0 \leq i_c \leq 8\text{ mA}$   
 For  $v_o(\max) = 8V$ , Then  
 $R_F = 1\text{ k}\Omega$

9.39

$i = \frac{v_I}{R}$  so  $1 = \frac{10}{R} \Rightarrow R = 10\text{ k}\Omega$

In the ideal op-amp,  $R_1$  has no influence.

Output voltage:  $v_o = \left(1 + \frac{R_2}{R}\right)v_I$

$v_o$  must remain within the bias voltages of the op-amp; the larger the  $R_2$ , the smaller the range of input voltage  $v_I$  in which the output is valid.

9.40

$$i_L = \frac{-v_I}{R_2} \Rightarrow 10 = -\frac{(-10)}{R_2} \Rightarrow R_2 = 1 \text{ k}\Omega$$

$$i_4 = \frac{v_L}{R_2} \text{ and } v_L = i_L Z_L = (0.010)(100) = 1 \text{ V}$$

$$i_4 = \frac{1}{1 \text{ k}\Omega} = 1 \text{ mA}$$

$$i_3 = i_4 + i_L = 1 + 10 = 11 \text{ mA}$$

$$\text{For } v_0(\text{max}) \approx 12 \text{ V} = i_3 R_3 + v_L = (11)R_3 + 1$$

$$\Rightarrow R_3 = 1 \text{ k}\Omega$$

We need

$$\frac{R_3}{R_2} = \frac{R_F}{R_1} = \frac{1 \text{ k}\Omega}{1 \text{ k}\Omega} \Rightarrow R_1 = R_F$$

9.41

$$(a) i_1 = i_2 \text{ and } i_2 = \frac{v_x}{R_2} + i_D, \quad v_x = -i_2 R_F$$

$$\text{Then } i_1 = -i_1 \left( \frac{R_F}{R_2} \right) + i_D$$

$$\text{Or } i_D = i_1 \left( 1 + \frac{R_F}{R_2} \right)$$

$$(b) R_1 = \frac{v_L}{i_1} = \frac{5}{1} \Rightarrow R_1 = 5 \text{ k}\Omega$$

$$12 = (1) \left( 1 + \frac{R_F}{R_2} \right) \Rightarrow \frac{R_F}{R_2} = 11$$

$$\text{For example, } R_2 = 5 \text{ k}\Omega, \quad R_F = 55 \text{ k}\Omega$$

9.42

$$(1) I_x = \frac{V_x}{R_2} + \frac{V_x - v_o}{R_3}$$

$$(2) \frac{V_x}{R_1} + \frac{V_x - v_o}{R_F} = 0$$

$$\text{From (2) } v_o = V_x \left( 1 + \frac{R_F}{R_1} \right)$$

$$\text{Then (1) } I_x = V_x \left( \frac{1}{R_2} + \frac{1}{R_3} \right) - \frac{1}{R_3} \cdot V_x \left( 1 + \frac{R_F}{R_1} \right)$$

$$\frac{I_x}{V_x} = \frac{1}{R_2} + \frac{1}{R_3} - \frac{1}{R_3} \cdot \frac{R_F}{R_1} = \frac{1}{R_2} - \frac{R_F}{R_1 R_3}$$

$$= \frac{R_1 R_3 - R_2 R_F}{R_1 R_2 R_3}$$

or

$$R_s = \frac{R_1 R_2 R_3}{R_1 R_3 - R_2 R_F}$$

$$\text{Note: If } \frac{R_F}{R_1 R_3} = \frac{1}{R_2} \Rightarrow R_2 R_F = R_1 R_3$$

then  $R_s = \infty$ , which corresponds to an ideal current source.

9.43

$$A_d = \frac{R_2}{R_1} = \frac{R_4}{R_3} = 5$$

Minimum resistance seen by  $v_{I1}$  is  $R_1$ .

$$\text{Set } R_1 = R_3 = 25 \text{ k}\Omega \text{ Then } R_2 = R_4 = 125 \text{ k}\Omega$$

$$i_L = \frac{v_o}{R_L} \Rightarrow v_o = i_L R_L = (0.5)(5) = 2.5 \text{ V}$$

$$v_o = 5(v_{I2} - v_{I1})$$

$$2.5 = 5(v_{I2} - 2) \Rightarrow v_{I2} = 2.5 \text{ V}$$

9.44

a. From superposition:

$$v_{o1} = -\frac{R_2}{R_1} \cdot v_{I1}$$

$$v_{o2} = \left( 1 + \frac{R_2}{R_1} \right) \left( \frac{R_4}{R_3 + R_4} \right) v_{I2}$$

Setting  $v_{I1} = v_{I2} = v_{cm}$

$$v_o = v_{o1} + v_{o2} = \left[ \left( 1 + \frac{R_2}{R_1} \right) \left( \frac{1}{1 + \frac{R_3}{R_4}} \right) - \frac{R_2}{R_1} \right] v_{cm}$$

$$A_{cm} = \frac{v_o}{v_{cm}} = \frac{R_4}{R_3} \cdot \left( 1 + \frac{R_2}{R_1} \right) \left( \frac{1}{1 + \frac{R_3}{R_4}} \right) - \frac{R_2}{R_1}$$

$$= \frac{\frac{R_4}{R_3} \left( 1 + \frac{R_2}{R_1} \right) - \frac{R_2}{R_1} \left( 1 + \frac{R_4}{R_3} \right)}{\left( 1 + \frac{R_4}{R_3} \right)}$$


$$A_{cm} = \frac{\frac{R_4}{R_3} - \frac{R_2}{R_1}}{\left( 1 + \frac{R_4}{R_3} \right)}$$

b. Max  $|A_{cm}| \Rightarrow$  Min  $\frac{R_4}{R_3}$  and Max  $\frac{R_2}{R_1}$

$$\text{Max } |A_{cm}| = \frac{47.5 - 52.5}{10.5 - 9.5} = \frac{4.5238 - 5.5263}{1 + 4.5238}$$

$$\Rightarrow |A_{cm}|_{\text{max}} = 0.1815$$

9.45

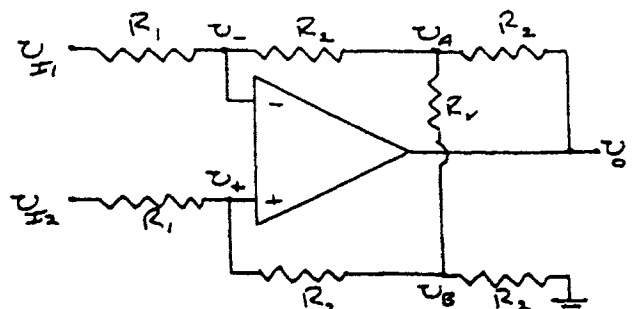

$$\frac{v_{I1} - v_A}{R_1 + R_2} = \frac{v_A - v_B}{R_V} + \frac{v_A - v_0}{R_2} \quad (1)$$

$$\frac{v_{I2} - v_B}{R_1 + R_2} = \frac{v_B - v_A}{R_V} + \frac{v_B}{R_2} \quad (2)$$

$$v_- = \left( \frac{R_1}{R_1 + R_2} \right) v_A + \left( \frac{R_2}{R_1 + R_2} \right) v_{I1} \quad (3)$$

$$v_+ = \left( \frac{R_1}{R_1 + R_2} \right) v_B + \left( \frac{R_2}{R_1 + R_2} \right) v_{I2} \quad (4)$$

Now  $v_- = v_+ \Rightarrow R_1 v_A + R_2 v_{I1} = R_1 v_B + R_2 v_{I2}$

So that  $v_A = v_B + \frac{R_2}{R_1} (v_{I2} - v_{I1})$

$$\frac{v_{I1}}{R_1 + R_2} = v_A \left( \frac{1}{R_1 + R_2} + \frac{1}{R_V} + \frac{1}{R_2} \right) - \frac{v_B}{R_V} - \frac{v_0}{R_2} \quad (1)$$

$$\frac{v_{I2}}{R_1 + R_2} = v_B \left( \frac{1}{R_1 + R_2} + \frac{1}{R_V} + \frac{1}{R_2} \right) - \frac{v_A}{R_V} \quad (2)$$

Then

$$\begin{aligned} \frac{v_{I1}}{R_1 + R_2} &= v_B \left( \frac{1}{R_1 + R_2} + \frac{1}{R_V} + \frac{1}{R_2} \right) - \frac{v_B}{R_V} - \frac{v_0}{R_2} \\ &+ \left( \frac{R_2}{R_1} \right) \left( \frac{1}{R_1 + R_2} + \frac{1}{R_V} + \frac{1}{R_2} \right) (v_{I2} - v_{I1}) \end{aligned} \quad (1)$$

$$\begin{aligned} \frac{v_{I2}}{R_1 + R_2} &= v_B \left( \frac{1}{R_1 + R_2} + \frac{1}{R_V} + \frac{1}{R_2} \right) \\ &- \frac{1}{R_V} \left[ v_B + \frac{R_2}{R_1} (v_{I2} - v_{I1}) \right] \end{aligned} \quad (2)$$

Substitute (1)-(2)

$$\begin{aligned} \frac{1}{R_1 + R_2} (v_{I1} - v_{I2}) &= \left( \frac{R_2}{R_1} \right) \left( \frac{1}{R_1 + R_2} + \frac{1}{R_V} + \frac{1}{R_2} \right) (v_{I2} - v_{I1}) \\ &- \frac{v_0}{R_2} + \frac{1}{R_V} \cdot \frac{R_2}{R_1} (v_{I2} - v_{I1}) \end{aligned}$$

$$\frac{v_0}{R_2} = (v_{I2} - v_{I1}) \left\{ \left( \frac{R_2}{R_1} \right) \left( \frac{1}{R_1 + R_2} + \frac{1}{R_V} + \frac{1}{R_2} \right) + \frac{1}{R_1 + R_2} + \frac{1}{R_V} \cdot \frac{R_2}{R_1} \right\}$$

$$v_0 = (v_{I2} - v_{I1}) \left( \frac{R_2}{R_1} \right) \left\{ \frac{R_2}{R_1 + R_2} + \frac{R_2}{R_V} + 1 + \frac{R_1}{R_1 + R_2} + \frac{R_2}{R_V} \right\}$$

$$v_0 = \frac{2R_2}{R_1} \left( 1 + \frac{R_2}{R_V} \right) (v_{I2} - v_{I1})$$

9.46

$$\begin{aligned} v_{01} &= \left( 1 + \frac{R_2}{R_1} \right) v_{I1} - \frac{R_2}{R_1} \cdot v_{I2} \\ &= \left( 1 + \frac{50}{10} \right) (-25 \sin \omega t) - \frac{50}{10} (25 \sin \omega t) \end{aligned}$$

$$v_{01} = -275 \sin \omega t \text{ mV}$$

$$\begin{aligned} v_{02} &= \left( 1 + \frac{R_2}{R_1} \right) v_{I2} - \frac{R_2}{R_1} \cdot v_{I1} \\ &= \left( 1 + \frac{50}{10} \right) (25 \sin \omega t) - \frac{50}{10} (-25 \sin \omega t) \end{aligned}$$

$$v_{02} = 275 \sin \omega t \text{ mV}$$

$$\begin{aligned} v_0 &= \frac{R_4}{R_3} \left( 1 + \frac{2R_2}{R_1} \right) (v_{I2} - v_{I1}) \\ &= \frac{30}{20} \left( 1 + 2 \left[ \frac{50}{10} \right] \right) (25 - [-25]) \sin \omega t \end{aligned}$$

$$v_0 = 825 \sin \omega t \text{ mV}$$

Current in  $R_1$  and  $R_2$ :

$$i_1 = \frac{v_{I1} - v_{I2}}{R_1} = \frac{(-25 - 25) \sin \omega t \text{ mV}}{10 \text{ k}\Omega}$$

$$|i_1| = 5 \sin \omega t \text{ }\mu\text{A}$$

Current in bottom  $R_3$  and  $R_4$ :

$$i_3 = \frac{v_{02}}{R_3 + R_4} = \frac{275 \sin \omega t \text{ mV}}{(20 + 30) \text{ k}\Omega}$$

$$|i_3| = 5.5 \sin \omega t \text{ }\mu\text{A}$$

Current in top  $R_3$  and  $R_4$ :

$$\begin{aligned} i'_3 &= \frac{v_{01} - \left( \frac{R_4}{R_3 + R_4} \right) v_{02}}{R_3} \\ &= \frac{[-275 - \left( \frac{30}{30 + 20} \right) (275)] \sin \omega t \text{ mV}}{20 \text{ k}\Omega} \end{aligned}$$

$$|i'_3| = 22 \sin \omega t \text{ }\mu\text{A}$$

9.47

$$v_0 = \frac{30}{20} \left( 1 + \frac{2(50)}{R_1} \right) (25 - (-25)) \sin \omega t \text{ mV}$$

$$|v_0| = (1.5)(50) \left( 1 + \frac{100}{R_1} \right) \text{ mV}$$

For

$$|v_0| = 0.1 \text{ V} = (1.5)(0.050) \left( 1 + \frac{100}{R_1} \right)$$

$$\Rightarrow \underline{R_1 = 300 \text{ k}\Omega}$$

For

$$|v_o| = 5 \text{ V} = (1.5)(0.050) \left(1 + \frac{100}{R_1}\right)$$

$$\Rightarrow R_1 = 1.52 \text{ k}\Omega$$

So  $R_{if} = 1.52 \text{ k}\Omega \Rightarrow$  Potentiometer  $\approx 300 \text{ k}\Omega$ 

9.48

$$A_d = \frac{R_4}{R_3} \left(1 + \frac{2R_2}{R_1}\right)$$

For  $A_d(\text{max})$ ,  $R_1 = R_1(\text{min}) = R_{if}$ 

$$200 = \frac{R_4}{R_3} \left(1 + \frac{2R_2}{R_{if}}\right)$$

For  $A_d(\text{min})$ ,  $R_1 = R_1(\text{max}) \approx 50 \text{ k}\Omega$ 

$$0.5 = \frac{R_4}{R_3} \left(1 + \frac{2R_2}{50}\right)$$

$$\text{Let } \frac{R_4}{R_3} = 0.4$$

$$\text{Then } 0.5 = 0.4 \left(1 + \frac{2R_2}{50}\right) \Rightarrow R_2 = 6.25 \text{ k}\Omega$$

and

$$200 = (0.4) \left(1 + \frac{2(6.25)}{R_{if}}\right) \Rightarrow R_{if} = 25.05 \text{ }\Omega$$

9.49

For a common-mode gain,  $v_{cm} = v_{I1} = v_{I2}$ 

Then

$$v_{o1} = \left(1 + \frac{R_2}{R_1}\right)v_{cm} - \frac{R_2}{R_1}v_{cm} = v_{cm}$$

$$v_{o2} = \left(1 + \frac{R_2}{R_1}\right)v_{cm} - \frac{R_2}{R_1}v_{cm} = v_{cm}$$

From Problem 9.41, we can write

$$A_{cm} = \frac{\frac{R_4}{R_3} - \frac{R_4}{R_3'}}{\left(1 + \frac{R_4}{R_3}\right)}$$

 $R_3 = R_4 = 20 \text{ k}\Omega$ ,  $R_3' = 20 \text{ k}\Omega \pm 5\%$ 

$$A_{cm} = \frac{1 - \frac{20}{R_3'}}{(1 + 1)} = \frac{1}{2} \left(1 - \frac{20}{R_3'}\right)$$

For  $R_3' = 20 \text{ k}\Omega - 5\% = 19 \text{ k}\Omega$ 

$$A_{cm} = \frac{1}{2} \left(1 - \frac{20}{19}\right) = -0.0263$$

For  $R_3' = 20 \text{ k}\Omega + 5\% = 21 \text{ k}\Omega$ 

$$A_{cm} = \frac{1}{2} \left(1 - \frac{20}{21}\right) = 0.0238$$

So  $|A_{cm}|_{\text{max}} = 0.0263$ 

9.50

$$\text{a. } v_o = \frac{1}{R_1 C_2} \int v_I(t') dt'$$

$$\int 0.5 \sin \omega t dt = -\frac{0.5}{\omega} \cos \omega t$$

$$|v_o| = 0.5 = \frac{1}{R_1 C_2} \cdot \frac{(0.5)}{\omega} = \frac{0.5}{2\pi R_1 C_2 f}$$

$$f = \frac{1}{2\pi R_1 C_2} = \frac{1}{2\pi(50 \times 10^3)(0.1 \times 10^{-6})}$$

$$\Rightarrow f = 31.8 \text{ Hz}$$

Output signal lags input signal by  $90^\circ$ 

$$\text{b. i. } f = \frac{0.5}{2\pi(50 \times 10^3)(0.1 \times 10^{-6})} \Rightarrow f = 15.9 \text{ Hz}$$

$$\text{ii. } f = \frac{0.5}{(0.1)(2\pi)(50 \times 10^3)(0.1 \times 10^{-6})}$$

$$\Rightarrow f = 159 \text{ Hz}$$

9.51

$$\text{(a) } v_o = -\frac{1}{RC} \int v_I(t') dt'$$

$$v_o = -\frac{1}{0.2} (0.5)(2) \Rightarrow v_o = -5 \text{ V}$$

$$\text{(b) } -15 = -\frac{1}{0.2} (0.5)t \Rightarrow t = 6 \text{ s}$$

9.52

$$\text{a. } \frac{v_o}{v_I} = \frac{-R_2 \parallel \frac{1}{j\omega C_2}}{R_1} = -\frac{R_2 \cdot \frac{1}{j\omega C_2}}{R_1 \left(R_2 + \frac{1}{j\omega C_2}\right)}$$

$$\frac{v_o}{v_I} = -\frac{R_2}{R_1} \cdot \frac{1}{1 + j\omega R_2 C_2}$$

$$\text{b. } \frac{v_o}{v_I} = -\frac{R_2}{R_1}$$

$$\text{c. } f = \frac{1}{2\pi R_2 C_2}$$

9.53

$$\text{a. } \frac{v_o}{v_I} = \frac{-R_2}{R_1 + \frac{1}{j\omega C_1}} = -\frac{R_2(j\omega C_1)}{1 + j\omega R_1 C_1}$$

$$\frac{v_o}{v_I} = -\frac{R_2}{R_1} \cdot \frac{j\omega R_1 C_1}{1 + j\omega R_1 C_1}$$

$$\text{b. } \frac{v_o}{v_I} = -\frac{R_2}{R_1}$$

$$\text{c. } f = \frac{1}{2\pi R_1 C_1}$$

9.54

Assuming the Zener diode is in breakdown,

$$v_o = -\frac{R_2}{R_1} \cdot V_Z = -\frac{1}{1}(6.8) \Rightarrow v_o = -6.8 \text{ V}$$

$$i_2 = \frac{0 - v_o}{R_2} = \frac{0 - (-6.8)}{1} \Rightarrow i_2 = 6.8 \text{ mA}$$

$$i_z = \frac{10 - V_Z}{R_s} - i_2 = \frac{10 - 6.8}{5.6} - 6.8 \Rightarrow i_z = -6.2 \text{ mA!!!}$$

Circuit is not in breakdown. Now

$$\frac{10 - 0}{R_s + R_1} = i_2 = \frac{10}{5.6 + 1} \Rightarrow i_2 = 1.52 \text{ mA}$$

$$v_o = -i_2 R_2 = -(1.52)(1) \Rightarrow v_o = -1.52 \text{ V}$$

$$i_z = 0$$


9.55

$$v_o = -V_T \ln\left(\frac{v_i}{I_s R_1}\right) = -(0.026) \ln\left[\frac{v_i}{(10^{-14})(10^4)}\right] \Rightarrow$$

$$v_o = -0.026 \ln\left(\frac{v_i}{10^{-10}}\right)$$

For  $v_i = 20 \text{ mV}$ ,  $|v_o| = 0.497 \text{ V}$

For  $v_i = 2 \text{ V}$ ,  $|v_o| = 0.617 \text{ V}$

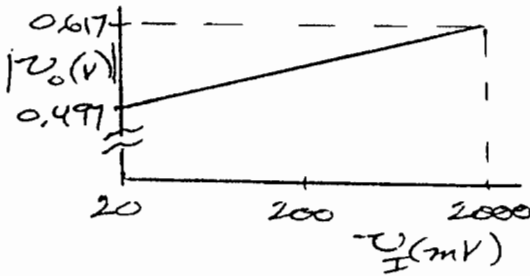

$$\ln(x) = \log_e(x) = [\log_{10}(x)] \cdot [\log_e(10)]$$

$$= 2.3026 \log_{10}(x)$$

Then

$$v_o \approx (1.0) \log_{10}\left(\frac{v_2}{v_1} \cdot \frac{R_1}{R_2}\right)$$


9.57

$$v_o = -I_s R(e^{v_i/N_T}) = -(10^{-14})(10^4)e^{v_i/N_T}$$

$$|v_o| = (10^{-10})e^{v_i/0.026}$$

For  $v_i = 0.30 \text{ V}$ ,  $|v_o| = 1.03 \times 10^{-5} \text{ V}$


For  $v_i = 0.60 \text{ V}$ ,  $|v_o| = 1.05 \text{ V}$

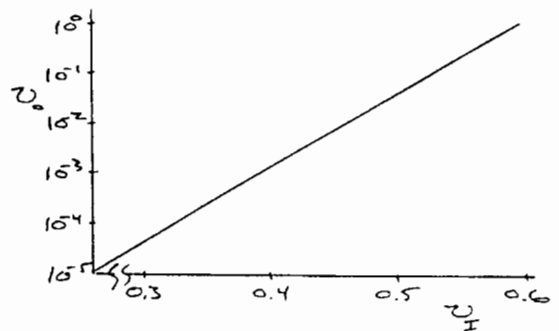

9.58

$$v_o = 2v_{i1} - 10v_{i2} + 3v_{i3} - v_{i4}$$

From Figure 9.37

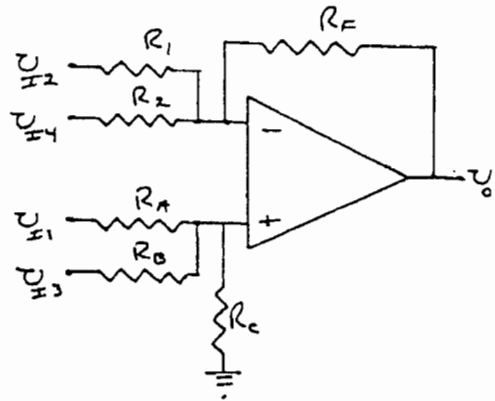

From Equation (9.110), we can write

$$v_o = -\frac{R_F}{R_1} \cdot v_{i2} - \frac{R_F}{R_2} \cdot v_{i4}$$

$$+ \left(1 + \frac{R_F}{R_N}\right) \left[\frac{R_F}{R_A} \cdot v_{i1} + \frac{R_F}{R_B} \cdot v_{i3}\right]$$

where  $R_N = R_1 \parallel R_2$ ,  $R_P = R_A \parallel R_B \parallel R_C$

Then  $\frac{R_F}{R_1} = 10$ ;  $\frac{R_F}{R_2} = 1$

9.56

$$v_o = \left(\frac{333}{20}\right)(v_{o1} - v_{o2}) = 16.65(v_{o1} - v_{o2})$$

$$v_{o1} = -v_{BE1} = -V_T \ln\left(\frac{i_{C1}}{I_s}\right)$$

$$v_{o2} = -v_{BE2} = -V_T \ln\left(\frac{i_{C2}}{I_s}\right)$$

$$v_{o1} - v_{o2} = -V_T \ln\left(\frac{i_{C1}}{i_{C2}}\right) = V_T \ln\left(\frac{i_{C2}}{i_{C1}}\right)$$

$$i_{C2} = \frac{v_2}{R_2}, \quad i_{C1} = \frac{v_1}{R_1}$$

$$\text{So } v_{o1} - v_{o2} = V_T \ln\left(\frac{v_2}{R_2} \cdot \frac{R_1}{v_1}\right)$$

Then

$$v_o = (16.65)(0.026) \ln\left(\frac{v_2}{v_1} \cdot \frac{R_1}{R_2}\right)$$

$$v_o = 0.4329 \ln\left(\frac{v_2}{v_1} \cdot \frac{R_1}{R_2}\right)$$

Set  $R_F = 500 \text{ k}\Omega$ , then  $R_1 = 50 \text{ k}\Omega$ ,  $R_2 = 500 \text{ k}\Omega$

Now  $R_N = R_1 \parallel R_2 = 50 \parallel 500 = 45.45 \text{ k}\Omega$

$$\left(1 + \frac{R_F}{R_N}\right) = \left(1 + \frac{500}{45.45}\right) = 12$$

Then (12)  $\left(\frac{R_F}{R_A}\right) = 2$ ; (12)  $\left(\frac{R_F}{R_B}\right) = 3$

Now  $\frac{12(R_F/R_A)}{12(R_F/R_B)} = \frac{2}{3} = \frac{R_B}{R_A}$

$R_A$  is the largest resistor

Set  $R_A = 500 \text{ k}\Omega$ , then  $R_B = 333.3 \text{ k}\Omega$

Then  $\frac{12R_F}{R_A} = 2 = \frac{12R_F}{500} = 2 \Rightarrow R_F = 83.33 \text{ k}\Omega$


$R_F = R_A \parallel R_B \parallel R_C$  and  $R_A \parallel R_B = 500 \parallel 333.3$   
 $= 200 \text{ k}\Omega$

Then  $200 \parallel R_C = 83.33$  so  $R_C = 142.8 \text{ k}\Omega$

9.59

$$v_O = 6v_{I1} + 3v_{I2} + 5v_{I3} - v_{I4} - 2v_{I5}$$

From Figure 9.37

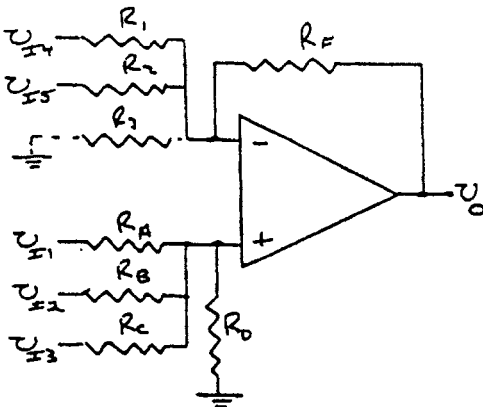

$$v_O = -\frac{R_F}{R_1} \cdot v_{I4} - \frac{R_F}{R_2} \cdot v_{I5} + \left(1 + \frac{R_F}{R_N}\right) \left[ \frac{R_F}{R_A} \cdot v_{I1} + \frac{R_F}{R_B} \cdot v_{I2} + \frac{R_F}{R_C} \cdot v_{I3} \right]$$

where

$$R_N = R_1 \parallel R_2, \quad R_P = R_A \parallel R_B \parallel R_C \parallel R_D$$

Then  $\frac{R_F}{R_1} = 1$ ;  $\frac{R_F}{R_2} = 2$

Let  $R_F = 250 \text{ k}\Omega$ , then  $R_1 = 250 \text{ k}\Omega$ ,  $R_2 = 125 \text{ k}\Omega$

Then  $R_N = R_1 \parallel R_2 = 250 \parallel 125 = 83.33 \text{ k}\Omega$

$$\left(1 + \frac{R_F}{R_N}\right) = \left(1 + \frac{250}{83.33}\right) = 4$$

Now  $4\left(\frac{R_F}{R_A}\right) = 6$ ;  $4\left(\frac{R_F}{R_B}\right) = 3$ ;  $4\left(\frac{R_F}{R_C}\right) = 5$

$$\frac{4(R_F/R_A)}{4(R_F/R_B)} = \frac{6}{3} = 2 = \frac{R_B}{R_A}$$

$$\frac{4(R_F/R_C)}{4(R_F/R_B)} = \frac{5}{3} = 1.667 = \frac{R_B}{R_C}$$

Set  $R_B = 250 \text{ k}\Omega$ , then

$$R_A = 125 \text{ k}\Omega, \quad R_C = 150 \text{ k}\Omega$$

Then  $\frac{4R_F}{R_A} = 6 = \frac{4R_F}{125} = 6 \Rightarrow R_F = 187.5 \text{ k}\Omega$

$\Rightarrow$  won't work since

$$R_F = R_A \parallel R_B \parallel R_C \parallel R_D > R_A \text{ and } R_C$$

Add a resistor  $R_3$  in parallel with  $R_1$  and  $R_2$  to decrease  $R_N$  (but with zero input to  $R_3$ ).

Set  $R_D = \infty \Rightarrow R_F = R_A \parallel R_B \parallel R_C = 53.57 \text{ k}\Omega$

Then

$$\left(1 + \frac{R_F}{R_N}\right) \cdot \frac{R_F}{R_A} = 6 = \left(1 + \frac{R_F}{R_N}\right) \cdot \left(\frac{53.57}{125}\right)$$

$$\Rightarrow \frac{R_F}{R_N} = 13.0$$

So

$$R_N = \frac{250}{13} = 19.23 = R_1 \parallel R_2 \parallel R_3 = 83.33 \parallel R_3$$

So  $R_3 = 25 \text{ k}\Omega$


9.60

$$\frac{V_O}{V_Z} = \left(1 + \frac{R_2}{R_1}\right)$$

$$\frac{9}{5.6} = 1 + \frac{R_2}{R_1} \Rightarrow \frac{R_2}{R_1} = 0.607$$

$$I_F = \frac{V_O - V_Z}{R_F}$$

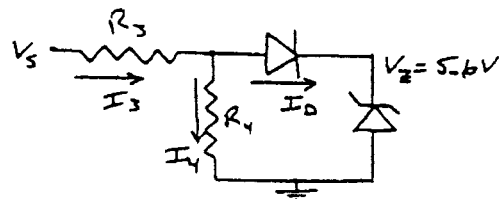Set  $I_F = 0.8 \text{ mA} = \frac{9 - 5.6}{R_F} \Rightarrow R_F = 4.25 \text{ k}\Omega$



$$V_2' = 5.6 + 0.7 = 6.3 \text{ V}$$

$$I_4 = \frac{V_2'}{R_4} = \frac{6.3}{R_4}, \quad I_3 = \frac{V_S - V_2'}{R_3}$$

If  $V_S = 10 \text{ V}$ ,  $I_3 = \frac{10 - 6.3}{R_3} = \frac{3.7}{R_3}$

Want  $I_{D1} = 0.1 \text{ mA}$ ; if we set  $I_4 = 0.1 \text{ mA} = \frac{6.3}{R_4}$

$$\Rightarrow R_4 = 63 \text{ k}\Omega$$

Then  $I_3 = 0.2 \text{ mA} = \frac{3.7}{R_3} \Rightarrow R_3 = 18.5 \text{ k}\Omega$

9.61

For  $I_Z = 1 \text{ mA}$ 

$$I_Z = \frac{V_0 - V_Z}{R_1} = \frac{10 - 5.6}{R_1} = 1 \text{ mA} \Rightarrow R_1 = 4.4 \text{ k}\Omega$$

$$V_Z = \left( \frac{R_3}{R_2 + R_3} \right) \cdot V_0 \Rightarrow 5.6 = \frac{R_3}{R_2 + R_3} \cdot 10$$

$$= \frac{10}{\left( 1 + \frac{R_2}{R_3} \right)}$$

$$1 + \frac{R_2}{R_3} = \frac{10}{5.6} \Rightarrow \frac{R_2}{R_3} = 0.786$$

$$\text{Let } \frac{V_0}{R_2 + R_3} = 1 \text{ mA} = \frac{10}{R_2 + R_3} = 1 \text{ mA}$$

$$\Rightarrow R_2 + R_3 = 10 \text{ k}\Omega$$

$$R_2 = 0.786 R_3 \Rightarrow 0.786 R_3 + R_3 = 10$$

$$\Rightarrow R_3 = 5.6 \text{ k}\Omega, R_2 = 4.4 \text{ k}\Omega$$

$$\text{Let } \frac{V_{in} - V_0}{R_4} = 2 \text{ mA} = \frac{12 - 10}{R_4} \Rightarrow R_4 = 1 \text{ k}\Omega$$

In this case, the op-amp must supply the load current.

9.62

For  $\nu_{01} - \nu_{02} = 0$  at  $T = 250^\circ \text{ K}$ , set

$$R_1 = R_2 = R_3 = R_T @ 250^\circ \text{ K} = 12 \text{ k}\Omega$$

Assuming  $\nu_{01}$  and  $\nu_{02}$  look into an open circuit.

$$\nu_{02} = \left( \frac{R_T}{R_T + R_2} \right) V^+ \text{ and}$$

$$\nu_{01} = \left( \frac{R_3}{R_1 + R_3} \right) \cdot V^+ = \frac{V^+}{2}$$

As temperature increases,  $R_T$  decreases. Let  $R_T = 12(1 - \delta)$  where  $\delta$  is positive.

$$R_T = 10 \text{ k}\Omega @ 300^\circ \Rightarrow \delta = 0.1667$$

$$\nu_{02} = \left( \frac{12(1 - \delta)}{12(1 - \delta) + 12} \right) V^+$$

Consider

$$\nu_{02} - \nu_{01} = \left( \frac{12(1 - \delta)}{12(1 - \delta) + 12} - \frac{1}{2} \right) (10)$$

$$= \left( \frac{12(1 - \delta) - 6[(1 - \delta) + 1]}{12[(1 - \delta) + 1]} \right) (10)$$

$$= \left( \frac{6(1 - \delta) - 6}{12[(1 - \delta) + 1]} \right) (10) = \frac{60\delta}{12[(1 - \delta) + 1]}$$

$$\text{Now consider } \nu_{01} - \nu_{02} = \frac{5\delta}{2 - \delta} \approx \frac{5}{2} \cdot \delta$$

Connect  $\nu_{01}$  to the  $\nu_{I2}$  terminal of the instrumentation amplifier and  $\nu_{02}$  to the  $\nu_{I1}$  terminal.

$$\text{Now } \nu_0 = \frac{R_4}{R_3} \left( 1 + \frac{2R_2}{R_1} \right) \left( \frac{5}{2} \right) \cdot \delta$$

For  $\delta = 0.1667$ ,  $\nu_0 = 5$ 

$$\frac{5}{0.1667} = 30 = \frac{R_4}{R_3} \left( 1 + \frac{2R_2}{R_1} \right) \left( \frac{5}{2} \right) \text{ or}$$

$$\frac{R_4}{R_3} \left( 1 + \frac{2R_2}{R_1} \right) = 12$$

Set  $\frac{R_4}{R_3} = 4$  Then  $\frac{2R_2}{R_1} = 3$  If  $R_2 = 30 \text{ k}\Omega$ 

$$R_1 = 20 \text{ k}\Omega$$

Resistor  $R_1$  can be a fixed resistor in series with a potentiometer for more precise control.

9.63

Using the bridge circuit shown in Figure 9.44

$$\nu_{01} = \left[ \frac{1}{2} - \frac{R}{R + R(1 + \delta)} \right] V^+ = \left[ \frac{1}{2} - \frac{1}{2 + \delta} \right] (10)$$

$$= \left( \frac{2 + \delta - 2}{2(2 + \delta)} \right) (10)$$

$$\Rightarrow \nu_{01} \approx \frac{10\delta}{4} = 2.5\delta$$

Connect  $\nu_{01}$  to an instrumentation amplifier.

$$\nu_0 = \frac{R_4}{R_3} \left( 1 + \frac{2R_2}{R_1} \right) (2.5\delta)$$

When  $\delta = 0.02$ ,  $\nu_0 = 5$ 

$$\frac{5}{(2.5)(0.02)} = 100 = \frac{R_4}{R_3} \left( 1 + \frac{2R_2}{R_1} \right)$$

Set  $\frac{R_4}{R_3} = 10$  Then  $\frac{2R_2}{R_1} = 9$

## Chapter 10

## Exercise Solutions

E10.1

$$I_{REF} = \frac{V^+ - V_{BE(on)}}{R_1} = \frac{10 - 0.7}{15}$$

$$I_{REF} = 0.62 \text{ mA}$$

$$I_0 = \frac{I_{REF}}{1 + \frac{2}{\beta}} = \frac{0.62}{1 + \frac{2}{75}}$$

$$I_0 = 0.604 \text{ mA}$$

E10.2

For  $I_0 = 0.75 \text{ mA}$ 

$$I_{REF} = I_0 \left(1 + \frac{2}{\beta}\right) = (0.75) \left(1 + \frac{2}{100}\right)$$

$$I_{REF} = 0.765 \text{ mA}$$

$$I_{REF} = \frac{V^+ - V_{BE(on)} - V^-}{R_1}$$

$$R_1 = \frac{5 - 0.7 - (-5)}{0.765}$$

$$R_1 = 12.2 \text{ k}\Omega$$

E10.3

$$I_{REF} = \frac{V^+ - V_{BE(on)} - V^-}{R_1} = \frac{5 - 0.7 - (-5)}{12}$$

$$I_{REF} = 0.775 \text{ mA}$$

$$I_0 = \frac{I_{REF}}{1 + \frac{2}{\beta}} = \frac{0.775}{1 + \frac{2}{75}} = 0.754 \text{ mA}$$

$$\Delta I_0 = (0.02)(0.754) = 0.0151 \text{ mA}$$

$$\text{and } \Delta I_0 = \frac{1}{r_0} \Delta V_{CE2} \Rightarrow r_0 = \frac{\Delta V_{CE2}}{\Delta I_0}$$

$$r_0 = \frac{4}{0.0151} = 265 \text{ k}\Omega = \frac{V_A}{I_0}$$

$$\Rightarrow V_A = (265)(0.754) \Rightarrow V_A \approx 200 \text{ V}$$

E10.4

$$I_{REF} = \frac{V^+ - 2V_{BE(on)}}{R_1} = \frac{9 - 2(0.7)}{12}$$

$$I_{REF} = 0.6333 \text{ mA}$$

$$I_0 = \frac{I_{REF}}{1 + \frac{2}{\beta(1+\beta)}} = \frac{0.6333}{1 + \frac{2}{75(76)}} = 0.6331 \text{ mA}$$

$$I_0 = 0.6331 \text{ mA} = I_{C1}$$

$$I_{B1} = I_{B2} = \frac{I_0}{\beta} \Rightarrow I_{B1} = I_{B2} = 8.44 \text{ }\mu\text{A}$$

$$I_{E3} = I_{B1} + I_{B2} \Rightarrow I_{E3} = 16.88 \text{ }\mu\text{A}$$

$$I_{B3} = \frac{I_{E3}}{1 + \beta} \Rightarrow I_{B3} = 0.222 \text{ }\mu\text{A}$$

E10.5

$$I_{REF} = \frac{10 - (0.7)(2)}{12} = 0.717 \text{ mA}$$

$$I_0 \approx I_{REF} = 0.717$$

$$r_0 = \frac{V_A}{I_0} = \frac{100}{0.717} \Rightarrow r_0 = 139 \text{ k}\Omega$$

$$\Delta I_0 = \frac{1}{r_0} \Delta V_{CE2} = \frac{4}{139}$$

$$\Rightarrow \Delta I_0 = 0.0288 \text{ mA}$$

E10.6

$$I_0 = I_{REF} \cdot \frac{1}{\left(1 + \frac{2}{\beta(1+\beta)}\right)} = \frac{0.50}{\left(1 + \frac{2}{50(51)}\right)}$$

$$\Rightarrow I_0 = 0.4996 \text{ mA}$$

$$I_{B3} = \frac{I_0}{\beta} \Rightarrow I_{B3} = 9.99 \text{ }\mu\text{A}$$

$$I_{E3} = \left(\frac{1+\beta}{\beta}\right) I_{C3} \Rightarrow I_{E3} = 0.5096 \text{ mA}$$

$$I_{C2} = \frac{I_{E3}}{\left(1 + \frac{2}{\beta}\right)} = \frac{0.5096}{\left(1 + \frac{2}{50}\right)}$$

$$\Rightarrow I_{C2} = 0.490 \text{ mA} = I_{C1}$$

$$I_{B1} = I_{B2} = \frac{I_{C2}}{\beta} \Rightarrow I_{B1} = I_{B2} = 9.80 \text{ }\mu\text{A}$$

E10.7

$$I_0 R_E = V_T \ln \left(\frac{I_{REF}}{I_0}\right)$$

$$R_E = \frac{V_T}{I_0} \ln \left(\frac{I_{REF}}{I_0}\right) = \frac{0.026}{0.025} \ln \left(\frac{0.75}{0.025}\right)$$

$$\Rightarrow R_E = 3.54 \text{ k}\Omega$$

$$R_1 = \frac{5 - 0.7}{0.75} \Rightarrow R_1 = 5.73 \text{ k}\Omega$$

$$V_{BE1} - V_{BE2} = I_0 R_E = (0.025)(3.54)$$

$$\Rightarrow V_{BE1} - V_{BE2} = 88.5 \text{ mV}$$

E10.8

$$I_{REF} = \frac{5 - 0.7 - (-5)}{12} \Rightarrow I_{REF} = 0.775 \text{ mA}$$

$$I_0 R_E = V_T \ln \left(\frac{I_{REF}}{I_0}\right)$$

$$I_0(6) = (0.026) \ln \left(\frac{0.775}{I_0}\right)$$

$$\Rightarrow I_0 \approx 16.6 \text{ }\mu\text{A}$$

E10.9

$$I_0 R_E = V_T \ln \left( \frac{I_{REF}}{I_0} \right)$$

$$R_E = \frac{0.026}{0.025} \ln \left( \frac{0.70}{0.025} \right) \Rightarrow R_E = 3.47 \text{ k}\Omega$$

$$g_{m2} = \frac{I_0}{V_T} = \frac{0.025}{0.026} \Rightarrow g_{m2} = 0.962 \text{ mA/V}$$

$$r_{\pi 2} = \frac{\beta V_T}{I_0} = \frac{(150)(0.026)}{0.025} = 156 \text{ k}\Omega$$

$$r_{o2} = \frac{V_A}{I_0} = \frac{100}{0.025} = 4000 \text{ k}\Omega$$

$$R'_E = R_E \parallel r_{\pi 2} = 3.47 \parallel 156 = 3.39 \text{ k}\Omega$$

$$R_o = r_{o2} (1 + g_{m2} R'_E) = 4000 [1 + (0.962)(3.39)]$$

$$R_o = 17,045 \text{ k}\Omega$$

$$dI_0 = \frac{1}{R_o} \cdot dV_{C2} = \frac{3}{17,045}$$

$$\Rightarrow dI_0 = 0.176 \text{ }\mu\text{A}$$

E10.10

$$I_{REF} = I_R + I_{BR} + I_{B1} + \dots + I_{BN}$$

$$I_R = I_{O1} = I_{O2} = \dots = I_{ON}$$

$$\text{and } I_{BR} = I_{B1} = I_{B2} = \dots = I_{BN} = \frac{I_{O1}}{\beta}$$

$$I_{REF} = I_{O1} + (N+1) \left( \frac{I_{O1}}{\beta} \right) = I_{O1} \left( 1 + \frac{N+1}{\beta} \right)$$

$$\text{So } I_{O1} = I_{O2} = \dots = I_{ON} = \frac{I_{REF}}{1 + \frac{N+1}{\beta}}$$

$$\frac{I_{O1}}{I_{REF}} = 0.90 = \frac{1}{1 + \frac{N+1}{50}}$$

$$1 + \frac{N+1}{50} = \frac{1}{0.9}$$

$$N+1 = \left( \frac{1}{0.9} - 1 \right) (50)$$

$$N = \left( \frac{1}{0.9} - 1 \right) (50) - 1$$

$$N = 4.55 \Rightarrow \underline{N = 4}$$

E10.11

a. From Equation (10.52),

$$V_{GS1} = \frac{\sqrt{\frac{3}{12}}}{1 + \sqrt{\frac{3}{12}}} \times 10 + \left( \frac{1 - \sqrt{\frac{3}{12}}}{1 + \sqrt{\frac{3}{12}}} \right) \times (1.8)$$

$$V_{GS1} = \left( \frac{0.5}{1 + 0.5} \right) (10) + \left( \frac{1 - 0.5}{1 + 0.5} \right) \times (1.8)$$

$$V_{GS1} = 3.93 \text{ V also } V_{DS1} = 3.93 \text{ V}$$

$$I_{REF} = (12)(0.020)[3.93 - 1.8]^2 [1 + (0.01)(3.93)]$$

$$\Rightarrow \underline{I_{REF} = 1.13 \text{ mA}}$$

$$b. I_0 = I_{REF} \times \frac{(W/L)_2}{(W/L)_1} \times \frac{(1 + \lambda V_{DS2})}{(1 + \lambda V_{DS1})}$$

$$I_0 = (1.13) \times \left( \frac{6}{12} \right) \times \frac{[1 + (0.01)(2)]}{[1 + (0.01)(3.93)]}$$

$$\Rightarrow \underline{I_0 = 0.555 \text{ mA}}$$

c. For  $V_{DS2} = 6 \text{ V}$ 

$$\Rightarrow \underline{I_0 = 0.576 \text{ mA}}$$

E10.12

$$K_{n1}(V_{GS1} - V_{TN})^2 = K_{n3}(V_{GS3} - V_{TN})^2$$

$$V_{GS1} - 2 = \left( \sqrt{\frac{0.10}{0.25}} \right) (V_{GS3} - 2)$$

$$V_{GS1} - 2 = (0.632)(V_{GS3} - 2)$$

$$V_{GS3} = 10 - V_{GS1}$$

$$V_{GS1} - 2 = (0.632)(10 - V_{GS1}) - (0.632)(2)$$

$$1.632V_{GS1} = 7.056 \Rightarrow V_{GS1} = 4.32 \text{ V}$$

$$I_{REF} = K_{n1}(V_{GS1} - V_{TN})^2 = (0.25)(4.32 - 2)^2 \Rightarrow$$

$$\underline{I_{REF} = 1.35 \text{ mA}}$$

$$I_0 = 3K_{n2}(V_{GS1} - V_{TN})^2 = 3(0.25)(4.32 - 2)^2$$

$$I_0 = 3I_{REF} \Rightarrow \underline{I_0 = 4.04 \text{ mA}}$$

E10.13

$$V_{DS}(\text{sat}) = 1 \text{ V} = V_{GS2} - V_{TN} = V_{GS2} - 2$$

$$\Rightarrow V_{GS2} = 3 \text{ V}$$

$$I_0 = K_{n2}(V_{GS2} - V_{TN})^2 = \left( \frac{\mu_n C_{ox}}{2} \right) \left( \frac{W}{L} \right)_2 (V_{GS2} - V_{TN})^2$$

$$0.20 = (0.020) \left( \frac{W}{L} \right)_2 (3 - 2)^2 \Rightarrow \left( \frac{W}{L} \right)_2 = 10$$

$$I_{REF} = \left( \frac{\mu_n C_{ox}}{2} \right) \left( \frac{W}{L} \right)_1 (V_{GS1} - V_{TN})^2$$

$$V_{GS1} = V_{GS2}$$

$$0.5 = (0.020) \left( \frac{W}{L} \right)_1 (3 - 2)^2 \Rightarrow \left( \frac{W}{L} \right)_1 = 25$$

$$V_{GS3} = V^* - V_{GS1} = 10 - 3 = 7 \text{ V}$$

$$I_{REF} = \left( \frac{\mu_n C_{ox}}{2} \right) \left( \frac{W}{L} \right)_3 (V_{GS3} - V_{TN})^2$$

$$0.5 = (0.020) \left( \frac{W}{L} \right)_3 (7 - 2)^2 \Rightarrow \left( \frac{W}{L} \right)_3 = 1$$

E10.14

$$a. I_{REF} = K_n (V_{GS} - V_{TN})^2$$

$$0.020 = 0.080 (V_{GS} - 1)^2$$

$$\underline{V_{GS} = 1.5 \text{ V all transistors}}$$

b.  $V_{G4} = V_{GS3} + V_{GS1} + V^- = 1.5 + 1.5 - 5 = -2 \text{ V}$

$V_{S4} = V_{G4} - V_{GS4} = -2 - 1.5 = -3.5 \text{ V}$

$V_{D4}(\text{min}) = V_{S4} + V_{DS4}(\text{sat})$

and  $V_{DS4}(\text{sat}) = V_{GS4} - V_{TN} = 1.5 - 1 = 0.5 \text{ V}$

So  $V_{D4}(\text{min}) = -3.5 + 0.5$

$\Rightarrow \underline{V_{D4}(\text{min}) = -3.0 \text{ V}}$

c.  $R_o = r_{o4} + r_{o2}(1 + g_m r_{o4})$

$r_{o2} = r_{o4} = \frac{1}{\lambda I_o} = \frac{1}{(0.02)(0.020)} = 2500 \text{ k}\Omega$

$g_m = 2K_n(V_{GS} - V_{TN}) = 2(0.080)(1.5 - 1) \Rightarrow$

$g_m = 0.080 \text{ mA/V}$

$R_o = 2500 + 2500(1 + (0.080)(2500))$

$\Rightarrow \underline{R_o = 505 \text{ M}\Omega}$

E10.15

$I_{REF} = 0.20 = K_{n1}(V_{GS1} - V_{TN})^2 = 0.15(V_{GS1} - 1)^2$

$\Rightarrow \underline{V_{GS1} = V_{GS2} = 2.15 \text{ V}}$

$I_o = K_{n2}(V_{GS2} - V_{TN})^2 = \frac{0.15}{2}(2.15 - 1)^2 \Rightarrow$

$\underline{I_o = 0.10 \text{ mA}}$

$I_o = K_{n3}(V_{GS3} - V_{TN})^2$

$0.10 = 0.15(V_{GS3} - 1)^2 \Rightarrow \underline{V_{GS3} = 1.82 \text{ V}}$

E10.16

All transistors are identical

$\Rightarrow \underline{I_o = I_{REF} = 250 \mu\text{A}}$

$I_{REF} = K_n(V_{GS} - V_{TN})^2$

$0.25 = 0.20(V_{GS} - 1)^2$

$\Rightarrow \underline{V_{GS} = 2.12 \text{ V}}$

E10.17

For  $Q_2$ :  $v_{DS}(\text{min}) = |V_P| = 2 \text{ V}$

$\Rightarrow V_S(\text{min}) = v_{DS}(\text{min}) - 5 = 2 - 5$

$\Rightarrow \underline{V_S(\text{min}) = -3 \text{ V}}$

$I_o = I_{DSS2}(1 + \lambda v_{DS2}) = 0.5(1 + (0.15)(2))$

$\Rightarrow \underline{I_o = 0.65 \text{ mA}}$


$I_o = I_{DSS1} \left(1 - \frac{v_{GS1}}{V_{P1}}\right)^2$

$0.65 = 0.80 \left(1 - \frac{v_{GS1}}{-2}\right)^2$


$\frac{v_{GS1}}{-2} = 0.0986 \Rightarrow v_{GS1} = -0.197 \text{ V}$

$v_{GS1} = V_I - V_S$

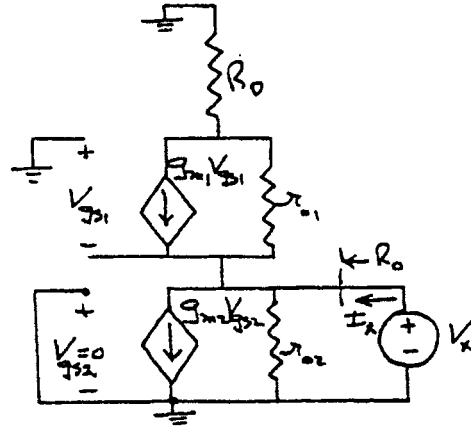$-0.197 = V_I - (-3) \Rightarrow \underline{V_I(\text{min}) = -3.2 \text{ V}}$



$V_{gs2} = 0, V_{gs1} = -V_x$

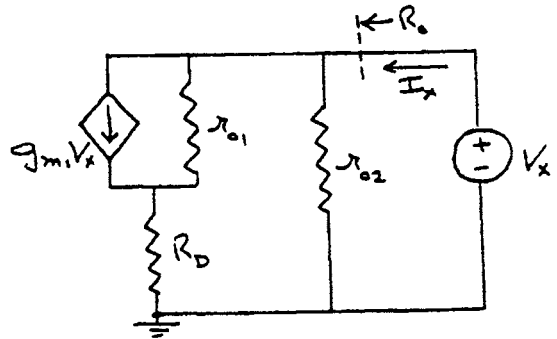

$I_x = \frac{V_x}{r_{o2}} + \frac{V_x - V_1}{r_{o1}} + g_{m1} V_x \quad (1)$

$\frac{V_1}{R_D} + \frac{V_1 - V_x}{r_{o1}} = g_{m1} V_x \quad (2)$

$V_1 = \frac{V_x \left( \frac{1}{r_{o1}} + g_{m1} \right)}{\frac{1}{R_D} + \frac{1}{r_{o1}}}$

$$\begin{aligned} \frac{I_x}{V_x} &= \frac{1}{R_o} = \frac{1}{r_{o2}} + \frac{1}{r_{o1}} + g_{m1} - \frac{\frac{1}{r_{o1}} \left( \frac{1}{r_{o1}} + g_{m1} \right)}{\frac{1}{R_D} + \frac{1}{r_{o1}}} \\ &= \frac{1}{r_{o2}} + \left( \frac{1}{r_{o1}} + g_{m1} \right) \left[ 1 - \frac{\frac{1}{r_{o1}}}{\frac{1}{R_D} + \frac{1}{r_{o1}}} \right] \\ &= \frac{1}{r_{o2}} + \left( \frac{1}{r_{o1}} + g_{m1} \right) \left( \frac{\frac{1}{R_D}}{\frac{1}{R_D} + \frac{1}{r_{o1}}} \right) \end{aligned}$$

For  $R_D \ll r_{o1}$

$$\Rightarrow \frac{1}{R_0} \approx \frac{1}{r_{o2}} + \left( \frac{1}{r_{o1}} + g_{m1} \right)$$

For  $Q_1$ :

$$g_{m1} = \frac{2I_{DSS1}}{|V_P|} \left( 1 - \frac{V_{GS1}}{V_P} \right) = \frac{2(0.8)}{2} \left( 1 - \frac{-0.197}{-2} \right)$$

$$g_{m1} = 0.721 \text{ mA/V}$$

$$r_o = \frac{1}{\lambda I_0} = \frac{1}{(0.15)(0.65)} = 10.3 \text{ k}\Omega$$

$$\frac{1}{R_0} = \frac{1}{10.3} + \frac{1}{10.3} + 0.721 = 0.915$$

$$\Rightarrow \underline{R_0 = 1.09 \text{ k}\Omega}$$

E10.18

For  $Q_1$ :  $i_D = I_{DSS1}(1 + \lambda v_{DS1})$

For  $Q_2$ :  $i_D = I_{DSS2} \left( 1 - \frac{v_{GS2}}{V_P} \right)^2 (1 + \lambda v_{DS2})$

$$v_{GS2} = -v_{DS1}$$

$$\text{and } v_{DS2} = V_{DS} - v_{DS1}$$

So

$$I_{DSS1}(1 + \lambda v_{DS1}) = I_{DSS2} \left[ 1 - \frac{-v_{DS1}}{V_P} \right]^2 [1 + \lambda(V_{DS} - v_{DS1})]$$

$$I_{DSS1} = I_{DSS2}$$

$$[1 + (0.1)v_{DS1}]$$

$$= \left[ 1 - \frac{v_{DS1}}{2} \right]^2 [1 + (0.1)(3) - (0.1)v_{DS1}]$$

$$1 + 0.1v_{DS1} = (1 - v_{DS1} + 0.25v_{DS1}^2)(1.3 - 0.1v_{DS1})$$

This becomes

$$0.025v_{DS1}^3 - 0.425v_{DS1}^2 + 1.5v_{DS1} - 0.3 = 0$$

We find  $v_{DS1} = 0.212 \text{ V}$ ,  $v_{DS2} = 2.79 \text{ V}$ ,

$$v_{GS2} = -0.212 \text{ V}$$

$$i_D = I_{DSS1}(1 + \lambda v_{DS1}) = 2[1 + (0.1)(0.212)]$$

$$\underline{i_D = 2.04 \text{ mA}}$$

$$R_0 = r_{o2} + r_{o1}(1 + g_{m2}r_{o2})$$

$$g_m = \frac{2I_{DSS}}{-V_P} \left( 1 - \frac{v_{GS2}}{V_P} \right) = \frac{2(2)}{2} \left( 1 - \frac{-0.212}{-2} \right)$$

$$g_m = 1.79 \text{ mA/V}$$

$$r_{o2} = r_{o4} = \frac{1}{\lambda I_{DSS}} = \frac{1}{(0.1)(2)} = 5 \text{ k}\Omega$$

$$R_0 = 5 + 5[1 + (1.79)(5)]$$

$$\Rightarrow \underline{R_0 = 54.8 \text{ k}\Omega}$$

E10.19

a.  $I_{REF} = I_S \exp\left(\frac{V_{EB2}}{V_T}\right)$

$$V_{EB2} = V_T \ln\left(\frac{I_{REF}}{I_S}\right) = (0.026) \ln\left(\frac{0.5 \times 10^{-3}}{10^{-12}}\right)$$

$$\Rightarrow \underline{V_{EB2} = 0.521 \text{ V}}$$

b.  $R_1 = \frac{5 - 0.521}{0.5} \Rightarrow \underline{R_1 = 8.96 \text{ k}\Omega}$

c. From Equation (10.72)

$$I_{S0} \left[ \exp\left(\frac{V_I}{V_T}\right) \right] \left( 1 + \frac{V_{CE0}}{V_{AN}} \right) = I_{REF} \times \frac{\left( 1 + \frac{V_{EC2}}{V_{AP}} \right)}{\left( 1 + \frac{V_{EB2}}{V_{AP}} \right)}$$

$$10^{-12} \left[ \exp\left(\frac{V_I}{V_T}\right) \right] \left( 1 + \frac{2.5}{100} \right) = (0.5 \times 10^{-3}) \frac{\left( 1 + \frac{2.5}{100} \right)}{\left( 1 + \frac{0.521}{100} \right)}$$

$$1.03 \times 10^{-12} \exp\left(\frac{V_I}{V_T}\right) = 5.125 \times 10^{-4}$$

$$\exp\left(\frac{V_I}{V_T}\right) = 4.976 \times 10^8$$

$$\Rightarrow \underline{V_I = 0.521 \text{ V}}$$

d.

$$A_v = \frac{-\left(\frac{1}{V_T}\right)}{\frac{1}{V_{AN}} + \frac{1}{V_{AP}}} = \frac{-\frac{1}{0.026}}{\frac{1}{100} + \frac{1}{100}} = \frac{-38.46}{0.01 + 0.01}$$

$$\Rightarrow \underline{A_v = -1923}$$

E10.20

a.  $V_{EB2} = (0.026) \ln\left(\frac{0.1 \times 10^{-3}}{5 \times 10^{-14}}\right)$

$$\Rightarrow \underline{V_{EB2} = 0.557 \text{ V}}$$

b.  $R_1 = \frac{5 - 0.557}{0.1} \Rightarrow \underline{R_1 = 44.4 \text{ k}\Omega}$

c.  $I_{S0} \left[ \exp\left(\frac{V_I}{V_T}\right) \right] \left( 1 + \frac{V_{CE0}}{V_{AN}} \right) = I_{REF} \times \frac{\left( 1 + \frac{V_{EC2}}{V_{AP}} \right)}{\left( 1 + \frac{V_{EB2}}{V_{AP}} \right)}$

$$= I_{REF} \times \frac{\left( 1 + \frac{V_{EC2}}{V_{AP}} \right)}{\left( 1 + \frac{V_{EB2}}{V_{AP}} \right)}$$

$$5 \times 10^{-14} \left[ \exp \left( \frac{V_I}{V_T} \right) \right] \left( 1 + \frac{2.5}{100} \right) = (0.1 \times 10^{-3}) \left( \frac{1 + \frac{2.5}{100}}{1 + \frac{0.557}{100}} \right)$$

$$(5.125 \times 10^{-14}) \exp \left( \frac{V_I}{V_T} \right) = 1.019 \times 10^{-4}$$

$$\exp \left( \frac{V_I}{V_T} \right) = 1.988 \times 10^9$$

$$\Rightarrow \underline{V_I = 0.557 \text{ V}}$$

$$d. \quad A_v = \frac{-\frac{1}{0.026}}{\frac{1}{100} + \frac{1}{100}} \Rightarrow \underline{A_v = -1923}$$

E10.21

$$a. \quad I_{REF} = K_{p1}(V_{SG} + V_{TP})^2$$

$$0.25 = 0.20(V_{SG} - 1)^2$$

$$\Rightarrow \underline{V_{SG} = 2.12 \text{ V}}$$

b. From Equation (10.89)

$$V_{DSO} = V_o = \frac{[1 + \lambda_p(V^+ - V_{SG})]}{\lambda_n + \lambda_p} \cdot \frac{K_n(V_I - V_{TN})^2}{I_{REF}(\lambda_n + \lambda_p)}$$

$$5 = \frac{1 + (0.015)(10 - 2.12)}{0.030} - \frac{(0.2)(V_I - 1)^2}{0.25(0.030)}$$

$$0.15 = 1.12 - 0.8(V_I - 1)^2$$

$$\Rightarrow \underline{V_I = 2.10 \text{ V}}$$

$$c. \quad A_v = \frac{-2K_n(V_I - V_{TN})}{I_{REF}(\lambda_n + \lambda_p)}$$

$$A_v = -\frac{2(0.2)(2.10 - 1.0)}{0.25(0.030)}$$

$$\Rightarrow \underline{A_v = -58.7}$$

E10.22

$$(a) \quad I_{REF} = K_{p1}(V_{SG} + V_{TP})^2$$

$$80 = 50(V_{SG} - 1)^2 \Rightarrow \underline{V_{SG} = 2.26 \text{ V}}$$

$$(b) \quad V_{DSO} = V_o = \frac{[1 + \lambda_p(V^+ - V_{SG})]}{\lambda_n + \lambda_p} \cdot \frac{K_n(V_I - V_{TN})^2}{I_{REF}(\lambda_n + \lambda_p)}$$

$$5 = \frac{[1 + (0.015)(10 - 2.26)]}{0.030} - \frac{(50)(V_I - 1)^2}{(80)(0.030)}$$

$$20.83(V_I - 1)^2 = 32.2 \Rightarrow \underline{V_I = 2.24 \text{ V}}$$

$$(c) \quad A_v = \frac{-2K_n(V_I - V_{TN})}{I_{REF}(\lambda_n + \lambda_p)} = \frac{-2(50)(2.24 - 1)}{(80)(0.030)} \Rightarrow$$

$$\underline{A_v = -51.7}$$

E10.23

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.8}{0.026} = 30.8 \text{ mA/V}$$

$$r_o = r_{o2} = \frac{V_A}{I_{CQ}} = \frac{80}{0.8} = 100 \text{ k}\Omega$$

$$a. \quad V_o = -g_m V_{\pi 1}(r_o || r_{o2}), \quad V_{\pi 1} = V_i$$

$$A_v = -g_m(r_o || r_{o2}) = -(30.8)[100 || 100]$$

$$\Rightarrow \underline{A_v = -1540}$$

$$b. \quad A_v = -g_m(r_o || r_{o2} || R_L)$$

$$A_v = -\frac{1540}{2} = -770$$

$$-770 = -(30.8)(50 || R_L) \Rightarrow (50 || R_L) = 25$$

$$\Rightarrow \underline{R_L = 50 \text{ k}\Omega}$$

E10.24

$$a. \quad g_m = \frac{I_{CQ}}{V_T} = \frac{0.5}{0.026} \Rightarrow \underline{g_m = 19.2 \text{ mA/V}}$$

$$r_o = \frac{V_{AN}}{I_{CQ}} = \frac{120}{0.5} \Rightarrow \underline{r_o = 240 \text{ k}\Omega}$$

$$r_{o2} = \frac{V_{AP}}{I_{CQ}} = \frac{80}{0.5} \Rightarrow \underline{r_{o2} = 160 \text{ k}\Omega}$$

$$b. \quad A_v = -g_m(r_o || r_{o2} || R_L) = -(19.2)[240 || 160 || 50]$$

$$\Rightarrow \underline{A_v = -631}$$

## E10.25

(a) Neglecting effect of  $\lambda$  and  $R_L$ 

$$I_O = I_{REF} = K_n (V_{I_Q} - V_{TN})^2$$

$$0.40 = 0.25(V_{I_Q} - 1)^2$$

$$\text{Then } \underline{V_{I_Q} = 2.26 \text{ V}}$$

$$\text{b. } r_o = r_{o2} = \frac{1}{\lambda I_O} = \frac{1}{(0.02)(0.4)} = 125 \text{ k}\Omega$$

$$g_m = 2K_n(V_{I_Q} - V_{TN}) = 2(0.25)(2.26 - 1) \\ = 0.63 \text{ mA/V}$$

$$A_v = -g_m(r_o \parallel r_{o2}) = -(0.63)(125 \parallel 125)$$

$$\Rightarrow \underline{A_v = -39.4}$$

$$\text{c. } A_v = -g_m(r_o \parallel r_{o2} \parallel R_L)$$

$$-\frac{39.4}{2} = -(0.63)(62.5 \parallel R_L)$$

$$\Rightarrow 62.5 \parallel R_L = 31.25 \Rightarrow \underline{R_L = 62.5 \text{ k}\Omega}$$

## E10.26

 $M_1$  and  $M_2$  identical  $\Rightarrow I_O = I_{REF}$ 

$$\text{a. } I_O = K_n (V_I - V_{TN})^2$$

$$0.25 = 0.2(V_I - 1)^2$$

$$V_I = 2.12 \text{ V}$$

$$g_m = 2K_n(V_I - V_{TN}) = 2(0.2)(2.12 - 1)$$

$$\Rightarrow \underline{g_m = 0.448 \text{ mA/V}}$$

$$r_{on} = \frac{1}{\lambda_n I_O} = \frac{1}{(0.01)(0.25)} \Rightarrow \underline{r_{on} = 400 \text{ k}\Omega}$$

$$r_{op} = \frac{1}{\lambda_p I_O} = \frac{1}{(0.02)(0.25)} \Rightarrow \underline{r_{op} = 200 \text{ k}\Omega}$$

$$\text{b. } A_v = -g_m(r_o \parallel r_{o2} \parallel R_L)$$

$$A_v = -(0.448)[400 \parallel 200 \parallel 100]$$

$$\Rightarrow \underline{A_v = -25.6}$$

## Chapter 10

## Problem Solutions

10.1

$$a. \quad I_1 = I_2 = \frac{0 - 2V_\gamma - V^-}{R_1 + R_2}$$

$$2V_\gamma + I_2 R_2 = V_{BE} + I_C R_3$$

$$2V_\gamma + \frac{R_2}{R_1 + R_2}(-2V_\gamma - V^-) = V_{BE} + I_C R_3$$

$$I_C = \frac{1}{R_3} \left\{ 2V_\gamma - (2V_\gamma + V^-) \left( \frac{R_2}{R_1 + R_2} \right) - V_{BE} \right\}$$

$$b. \quad V_\gamma = V_{BE} \text{ and } R_1 = R_2$$

$$I_C = \frac{1}{R_3} \left\{ 2V_\gamma - \frac{1}{2}(2V_\gamma + V^-) - V_{BE} \right\}$$

$$\text{or } I_C = \frac{-V^-}{2R_3}$$

$$c. \quad I_C = 2 \text{ mA} = \frac{-(-10)}{2R_3} \Rightarrow R_3 = 2.5 \text{ k}\Omega$$

$$I_1 = I_2 = 2 \text{ mA} = \frac{-2(0.7) - (-10)}{R_1 + R_2}$$

$$\Rightarrow R_1 + R_2 = 4.3 \text{ k}\Omega$$

$$\Rightarrow R_1 = R_2 = 2.15 \text{ k}\Omega$$

10.2

$$I_{C2} = \frac{I_{REF}}{1 + \frac{2}{\beta}} = \frac{1}{1 + \frac{2}{50}}$$

$$I_{C1} = I_{C2} = 0.962 \text{ mA}$$

$$I_{B1} = I_{B2} = \frac{I_{C2}}{\beta} \Rightarrow I_{B1} = I_{B2} = 0.0192 \text{ mA}$$

10.3

$$(a) \quad I_{REF} = \frac{V^+ - V_{BE(on)} - V^-}{R_1}$$

or

$$R_1 = \frac{15 - 0.7 - (-15)}{0.5} \Rightarrow R_1 = 58.6 \text{ k}\Omega$$

$$(b) \quad R_1 = \frac{V^+ - V_{BE(on)} - V^-}{I_{REF}} = \frac{0 - 0.7 - (-15)}{0.5} \Rightarrow$$

$$R_1 = 28.6 \text{ k}\Omega$$

Advantage: Requires smaller resistance.

(c) For part (a):

$$I_o(\text{max}) = \frac{29.3}{(58.6)(0.95)} = 0.526 \text{ mA}$$

$$I_o(\text{min}) = \frac{29.3}{(58.6)(1.05)} = 0.476 \text{ mA}$$

$$\Delta I_o = 0.526 - 0.476 = 0.05 \text{ mA} \Rightarrow \pm 5\%$$

$$\text{For part (b): } I_o(\text{max}) = \frac{14.3}{(28.6)(0.95)} = 0.526 \text{ mA}$$

$$I_o(\text{min}) = \frac{14.3}{(28.6)(1.05)} = 0.476 \text{ mA}$$

$$\Delta I_o = 0.05 \text{ mA} \Rightarrow \pm 5\%$$

10.4

$$a. \quad I_{REF} = I_o \left( 1 + \frac{2}{\beta} \right) = 2 \left( 1 + \frac{2}{100} \right)$$

$$\text{or } I_{REF} = 2.04 \text{ mA}$$

$$R_1 = \frac{15 - 0.7}{2.04} \Rightarrow R_1 = 7.01 \text{ k}\Omega$$

$$b. \quad r_o = \frac{V_A}{I_o} = \frac{80}{2} = 40 \text{ k}\Omega$$

$$\frac{\Delta I_o}{\Delta V_{CE}} = \frac{1}{r_o} \Rightarrow \Delta I_o = \left( \frac{1}{40} \right) (9.3) = 0.2325 \text{ mA}$$

$$\frac{\Delta I_o}{I_o} = \frac{0.2325}{2} \Rightarrow \frac{\Delta I_o}{I_o} = 11.6\%$$

10.5

$$I_{REF} = I_o \left( 1 + \frac{2}{\beta} \right) = (0.5) \left( 1 + \frac{2}{25} \right)$$

$$= 0.54 \text{ mA} = I_{REF}$$

$$R_1 = \frac{5 - 0.7}{0.54} \Rightarrow R_1 = 7.96 \text{ k}\Omega$$

10.6

$$a. \quad I_{REF} = \frac{5 - 0.7}{18} = 0.239 \text{ mA}$$

$$I_o = \frac{0.239}{1 + \frac{2}{50}} \Rightarrow I_o = 0.230 \text{ mA}$$

$$b. \quad r_o = \frac{V_A}{I_o} = \frac{50}{0.230} = 217 \text{ k}\Omega$$

$$\Delta I_o = \frac{1}{r_o} \cdot \Delta V_{EC} = \left( \frac{1}{217} \right) (1.3) = 0.00599 \text{ mA}$$

$$\Rightarrow I_o = 0.236 \text{ mA}$$

$$c. \quad \Delta I_o = \left( \frac{1}{217} \right) (3.3) = 0.0152 \text{ mA}$$

$$\Rightarrow I_o = 0.245 \text{ mA}$$

10.7

$$a. \quad I_{REF} = 1 = \frac{5 - 0.7 - (-5)}{R_1}$$

$$\Rightarrow R_1 = 9.3 \text{ k}\Omega$$

$$b. \quad I_0 = 2I_{REF} \Rightarrow I_0 = 2 \text{ mA}$$

$$c. \quad \text{For } V_{EC2}(\text{min}) = 0.7 \Rightarrow R_{C2} = \frac{5 - 0.7}{2}$$

$$\Rightarrow R_{C2} = 2.15 \text{ k}\Omega$$

10.8

$$I_0 = nI_{C1}$$

$$I_{REF} = I_{C1} + I_{B1} + I_{B2} = I_{C1} + \frac{I_{C1}}{\beta} + \frac{I_0}{\beta}$$

$$I_{REF} = I_{C1} \left( 1 + \frac{1}{\beta} + \frac{n}{\beta} \right) = I_{C1} \left( 1 + \frac{1+n}{\beta} \right)$$

$$= \frac{I_0}{n} \left( 1 + \frac{1+n}{\beta} \right)$$

$$\text{or } I_0 = \frac{nI_{REF}}{\left( 1 + \frac{1+n}{\beta} \right)}$$

10.9

Using the results of Problem 10-8.

$$2 = \frac{2I_{REF}}{3} \Rightarrow I_{REF} = 1.06 \text{ mA}$$

$$R_1 = \frac{5 - 0.7}{1.06} \Rightarrow R_1 = 4.06 \text{ k}\Omega$$

10.10

First approximation - BE area of  $Q_2$  is 3 times that of  $Q_1$ .

$$R_1 \cong \frac{5 - 0.7 - (-5)}{0.5} \Rightarrow R_1 = 18.6 \text{ k}\Omega$$

Second approximation - take into account  $I_C$  vs  $V_{BE}$  variation.For  $Q_1$ :

$$\frac{I_{C1}}{I_{C2}} = \exp\left(\frac{V_{BE1} - V_{BE2}}{V_T}\right)$$

or

$$V_{BE1} - V_{BE2} = V_T \ln\left(\frac{I_{C1}}{I_{C2}}\right)$$

$$0.7 - V_{BE2} = 0.026 \ln\left(\frac{1}{0.5}\right) \Rightarrow V_{BE2} = 0.682 \text{ V for}$$

$$I_C = 0.5 \text{ mA}$$

Then

$$R_1 = \frac{5 - 0.682 - (-5)}{0.5} \Rightarrow R_1 = 18.64 \text{ k}\Omega$$

Now

$$I_{S1} = \frac{I_C}{\exp\left(\frac{V_{BE}}{V_T}\right)} = \frac{1 \times 10^{-3}}{\exp\left(\frac{0.7}{0.026}\right)} \Rightarrow I_{S1} = 2.03 \times 10^{-15} \text{ A}$$

For  $Q_2$ :

$$I_{S2} = \frac{I_{C2}}{\exp\left(\frac{V_{BE2}}{V_T}\right)} = \frac{1.5 \times 10^{-3}}{\exp\left(\frac{0.682}{0.026}\right)} = 6.09 \times 10^{-15} \text{ A}$$

10.11

$$I_2 = 2I_1 \text{ and } I_3 = 3I_1$$

$$(a) \quad I_2 = 1.0 \text{ mA}, I_3 = 1.5 \text{ mA}$$

$$(b) \quad I_1 = 0.25 \text{ mA}, I_3 = 0.75 \text{ mA}$$

$$(c) \quad I_1 = 0.167 \text{ mA}, I_2 = 0.333 \text{ mA}$$

10.12

$$a. \quad I_0 = I_{C1} \text{ and } I_{REF} = I_{C1} + I_{B3} = I_{C1} + \frac{I_{E3}}{1 + \beta}$$

$$I_{E3} = I_{B1} + I_{B2} + \frac{V_{BE}}{R_2} = \frac{2I_{C1}}{\beta} + \frac{V_{BE}}{R_2}$$

$$I_{REF} = I_{C1} + \frac{2I_{C1}}{\beta(1 + \beta)} + \frac{V_{BE}}{(1 + \beta)R_2}$$

$$I_{REF} - \frac{V_{BE}}{(1 + \beta)R_2} = I_0 \left( 1 + \frac{2}{\beta(1 + \beta)} \right)$$

$$I_0 = \frac{I_{REF} - \frac{V_{BE}}{(1 + \beta)R_2}}{\left( 1 + \frac{2}{\beta(1 + \beta)} \right)}$$

$$b. \quad I_{REF} = (0.70) \left( 1 + \frac{2}{(80)(81)} \right) + \frac{0.7}{(81)(10)}$$

$$I_{REF} = 0.700216 + 0.000864$$

$$I_{REF} = 0.7011 \text{ mA} = \frac{10 - 2(0.7)}{R_1}$$

$$\Rightarrow R_1 = 12.27 \text{ k}\Omega$$

10.13

$$a. \quad I_{0i} = I_{CR} \text{ and } I_{REF} = I_{CR} + I_{BS} = I_{CR} + \frac{I_{ES}}{1 + \beta}$$

$$I_{ES} = I_{BR} + I_{B1} + I_{B2} + \dots + I_{BN} = (1 + N)I_{BR}$$

$$= \frac{(1 + N)I_{CR}}{\beta}$$

$$\text{Then } I_{REF} = I_{CR} + \frac{(1 + N)I_{CR}}{\beta(1 + \beta)}$$


$$\text{or } I_{0i} = \frac{I_{REF}}{\left( 1 + \frac{(1 + N)}{\beta(1 + \beta)} \right)}$$

$$b. \quad I_{REF} = (0.5) \left[ 1 + \frac{6}{(50)(51)} \right] = 0.5012 \text{ mA}$$

$$R_1 = \frac{5 - 2(0.7) - (-5)}{0.5012}$$

$$\Rightarrow R_1 = 17.16 \text{ k}\Omega$$

10.14

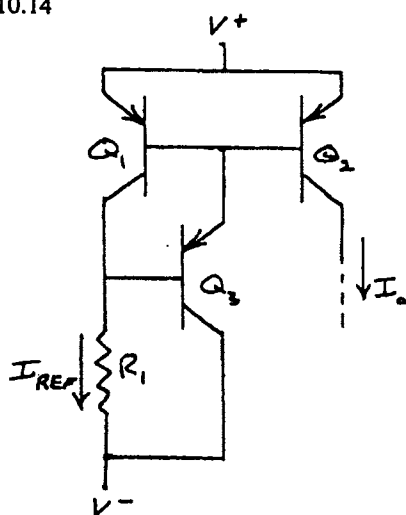


$$I_{REF} = I_0 \left( 1 + \frac{2}{\beta(1+\beta)} \right) = (0.5) \left[ 1 + \frac{2}{(50)(51)} \right]$$

$$\Rightarrow I_{REF} = 0.5004 \text{ mA}$$

$$R_1 = \frac{5 - 2(0.7) - (-5)}{0.5004} \Rightarrow R_1 = 17.19 \text{ k}\Omega$$

10.15

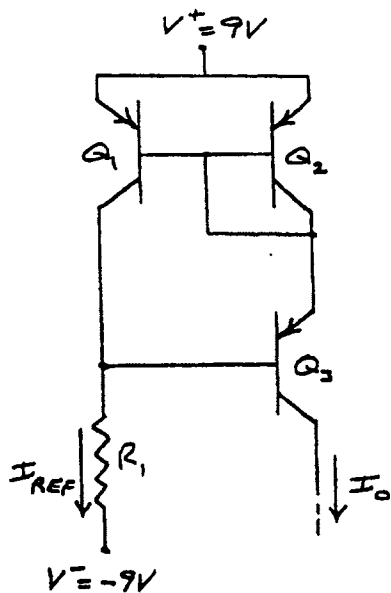

$$I_0 = I_{REF} \cdot \frac{1}{\left( 1 + \frac{2}{\beta(2+\beta)} \right)}$$

For  $I_0 = 0.8 \text{ mA}$

$$I_{REF} = (0.8) \left( 1 + \frac{2}{25(27)} \right)$$

$$\Rightarrow I_{REF} = 0.8024 \text{ mA}$$

$$R_1 = \frac{18 - 2(0.7)}{0.8024} \Rightarrow R_1 = 20.69 \text{ k}\Omega$$

10.16

The analysis is exactly the same as in the text. We have

$$I_0 = I_{REF} \cdot \frac{1}{\left( 1 + \frac{2}{\beta(2+\beta)} \right)}$$

10.17

$$I_0 = 2 \text{ mA}, I_{B2} = \frac{2}{75} = 0.0267 \text{ mA}$$

$$I_{C1} = 1 \text{ mA}, I_{B1} = \frac{1}{75} = 0.0133 \text{ mA}$$

$$I_{E3} = I_{B1} + I_{B2} = 0.0133 + 0.0267 = 0.04 \text{ mA}$$

$$I_{B3} = \frac{I_{E3}}{1+\beta} = \frac{0.04}{76} = 0.000526 \text{ mA}$$

$$I_{REF} = I_{C1} + I_{B3} \Rightarrow I_{REF} = 1.000526 \approx 1 \text{ mA}$$

$$R_1 = \frac{10 - 2(0.7)}{I_{REF}} = \frac{8.6}{1} \Rightarrow R_1 = 8.6 \text{ k}\Omega$$

10.18

a. We have

$$R_0 \approx \frac{\beta r_{o3}}{2}$$

$$r_{o3} = \frac{V_A}{I_0} \approx \frac{V_A}{I_{REF}} = \frac{80}{0.5} = 160 \text{ k}\Omega$$

Then

$$R_0 \approx \frac{(80)(160)}{2} \Rightarrow R_0 \approx 6.4 \text{ M}\Omega$$

$$b. \Delta I_0 = \frac{1}{R_0} \cdot \Delta V_C = \frac{5}{6.4} \Rightarrow \Delta I_0 = 0.781 \mu\text{A}$$

10.19

$$V_{BE} = V_T \ln \left( \frac{I_{REF}}{I_S} \right)$$

$$0.7 = (0.026) \ln \left( \frac{10^{-3}}{I_S} \right) \Rightarrow I_S = 2.03 \times 10^{-15} \text{ A}$$

$$\text{At } 2 \text{ mA}, V_{BE} = (0.026) \ln \left( \frac{2 \times 10^{-3}}{2.03 \times 10^{-15}} \right) \\ = 0.718 \text{ V}$$

$$R_1 = \frac{15 - 0.718}{2} \Rightarrow R_1 = 7.14 \text{ k}\Omega$$

$$R_E = \frac{V_T}{I_0} \ln \left( \frac{I_{REF}}{I_0} \right) = \frac{0.026}{0.050} \cdot \ln \left( \frac{2}{0.050} \right) \\ \Rightarrow R_E = 1.92 \text{ k}\Omega$$

10.20

$$a. \quad I_{REF} \approx \frac{10 - 0.7}{20} = 0.465 \text{ mA}$$

Let  $V^- = 0$

$$V_{BE} \approx V_T \ln \left( \frac{I_{REF}}{I_S} \right)$$

$$0.7 = (0.026) \ln \left( \frac{10^{-3}}{I_S} \right) \Rightarrow I_S = 2.03 \times 10^{-15} \text{ A}$$

Then

$$V_{BE} \approx (0.026) \ln \left( \frac{0.465 \times 10^{-3}}{2.03 \times 10^{-15}} \right) = 0.680 \text{ V}$$

Then

$$I_{REF} \approx \frac{10 - 0.680}{20} \Rightarrow \underline{I_{REF} = 0.466 \text{ mA}}$$

$$b. \quad R_E = \frac{V_T}{I_0} \ln \left( \frac{I_{REF}}{I_0} \right) = \frac{0.026}{0.10} \cdot \ln \left( \frac{0.466}{0.10} \right)$$

$$\Rightarrow \underline{R_E = 400 \Omega}$$

10.21

$$(a) \quad I_{REF} = \frac{V^+ - V_{BE1} - V^-}{R_1} = \frac{5 - 0.7 - (-5)}{100} \Rightarrow$$

$$\underline{I_{REF} = 93 \mu\text{A}}$$

$$I_0 R_E = V_T \ln \left( \frac{I_{REF}}{I_0} \right) \Rightarrow I_0(10) = 0.026 \ln \left( \frac{93 \times 10^{-3} \text{ mA}}{I_0} \right)$$

By trial and error,  $\underline{I_0 \approx 6.8 \mu\text{A}}$

$$R_o = r_{o2}(1 + g_{m2} R'_E)$$

Now

$$r_{o2} = \frac{30}{6.8} = 4.41 \text{ M}\Omega$$

$$g_{m2} = \frac{0.0068}{0.026} = 0.262 \text{ mA/V}$$

$$r_{\pi 2} = \frac{(100)(0.026)}{0.0068} = 382 \text{ k}\Omega$$

So

$$R'_E = r_{\pi 2} \parallel R_E = 382 \parallel 10 = 9.74 \text{ k}\Omega$$

Then

$$R_o = 4.41 [1 + (0.262)(9.74)] \Rightarrow \underline{R_o = 15.7 \text{ M}\Omega}$$

$$(d) \quad V_{BE1} - V_{BE2} = I_0 R_E = (0.0068)(10) \Rightarrow$$

$$\underline{V_{BE1} - V_{BE2} = 0.068 \text{ V}}$$

10.22

$$\Delta I_0 = \frac{1}{R_o} \cdot \Delta V_C$$

$$R_o = r_{o2}(1 + g_{m2} R'_E)$$

$$r_{o2} = \frac{V_A}{I_0} = \frac{80}{17.4} = 4.6 \text{ M}\Omega$$

$$g_{m2} = \frac{I_0}{V_T} = \frac{0.0174}{0.026} = 0.669 \text{ mA/V}$$

$$r_{\pi 2} = \frac{(80)(0.026)}{0.0174} = 119.5 \text{ k}\Omega$$

$$R'_E = R_E \parallel r_{\pi 2} = 7 \parallel 119.5$$

$$R'_E = 6.61 \text{ k}\Omega$$

$$R_o = (4.6)[1 + (0.669)(6.61)] \Rightarrow R_o = 24.9 \text{ M}\Omega$$

Now

$$\Delta I_0 = \left( \frac{1}{24.9} \right) (5) \Rightarrow \underline{\Delta I_0 = 0.201 \mu\text{A}}$$

10.23

$$R_o = r_{o2}(1 + g_{m2} R'_E) \text{ where } R'_E = R_E \parallel r_{\pi 2}$$

$$r_{o2} = \frac{V_A}{I_0} = \frac{75}{25} = 3 \text{ M}\Omega$$

$$g_{m2} = \frac{I_0}{V_T} = \frac{0.025}{0.026} = 0.962 \text{ mA/V}$$

$$r_{\pi 2} = \frac{\beta V_T}{I_0} = \frac{(80)(0.026)}{0.025} = 83.2 \text{ k}\Omega$$

$$R_E = \frac{V_T}{I_0} \ln \left( \frac{I_{REF}}{I_0} \right) = \frac{0.026}{0.025} \cdot \ln \left( \frac{0.75}{0.025} \right)$$

$$= 3.54 \text{ k}\Omega$$

$$R'_E = 3.54 \parallel 83.2 = 3.40 \text{ k}\Omega$$

$$R_o = 3[1 + (0.962)(3.4)] = 12.8 \text{ M}\Omega$$

$$\Delta I_0 = \frac{1}{R_o} \cdot \Delta V_{C2} = \frac{3}{12.8} = 0.234 \mu\text{A}$$

So

$$\frac{\Delta I_0}{I_0} = \frac{0.234}{25} \Rightarrow \underline{0.936\%}$$

10.24

Let  $R_1 = 5 \text{ k}\Omega$ , Then

$$I_{REF} = \frac{12 - 0.7 - (-12)}{5} \Rightarrow \underline{I_{REF} = 4.66 \text{ mA}}$$

Now

$$I_0 R_E = V_T \ln \left( \frac{I_{REF}}{I_0} \right) \Rightarrow$$

$$R_E = \frac{0.026}{0.10} \ln \left( \frac{4.66}{0.10} \right) \Rightarrow \underline{R_E \approx 1 \text{ k}\Omega}$$

10.25

$$I_{REF} \approx \frac{10 - 0.7 - (-10)}{40} = 0.4825 \text{ mA}$$

$$V_{BE} \approx V_T \ln \left( \frac{I_{REF}}{I_S} \right)$$

$$0.7 = (0.026) \ln \left( \frac{10^{-3}}{I_S} \right) \Rightarrow I_S = 2.03 \times 10^{-15} \text{ A}$$

Now

$$V_{BE} = (0.026) \ln \left( \frac{0.4825 \times 10^{-3}}{2.03 \times 10^{-15}} \right) = 0.681 \text{ V}$$

$$V_{BE1} = 0.681 \text{ V}$$

So

$$I_{REF} \approx \frac{10 - 0.681 - (-10)}{40}$$

$$\Rightarrow I_{REF} = 0.483 \text{ mA}$$

$$I_0 R_E = V_T \ln \left( \frac{I_{REF}}{I_0} \right)$$

$$I_0(12) = (0.026) \ln \left( \frac{0.483}{I_0} \right)$$

By trial and error,

$$\Rightarrow I_0 \approx 8.7 \mu\text{A}$$

$$V_{BE2} = V_{BE1} - I_0 R_E = 0.681 - (0.0087)(12)$$

$$\Rightarrow V_{BE2} = 0.5766 \text{ V}$$

10.26

$$V_{BE1} + I_{REF} R_{E1} = V_{BE2} + I_0 R_{E2}$$

$$V_{BE1} - V_{BE2} = I_0 R_{E2} - I_{REF} R_{E1}$$

For matched transistors

$$V_{BE1} = V_T \ln \left( \frac{I_{REF}}{I_S} \right)$$

$$V_{BE2} = V_T \ln \left( \frac{I_0}{I_S} \right)$$


Then

$$V_T \ln \left( \frac{I_{REF}}{I_0} \right) = I_0 R_{E2} - I_{REF} R_{E1}$$

Output resistance looking into the collector of  $Q_2$  is increased.

10.27

a.

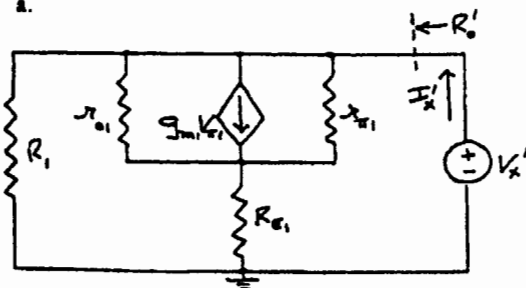

$$I_x' = \frac{V_{\pi 1}}{r_{\pi 1}} + g_{m1} V_{\pi 1} + \frac{V_{\pi 1}}{r_{o1}} + \frac{V_x'}{R_i} \quad (1)$$

$$V_x' = V_{\pi 1} + \left( \frac{V_{\pi 1}}{r_{\pi 1}} + g_{m1} V_{\pi 1} + \frac{V_{\pi 1}}{r_{o1}} \right) R_{E1} \quad (2)$$

$$V_x' = V_{\pi 1} \left[ 1 + \left( \frac{1}{r_{\pi 1}} + g_{m1} + \frac{1}{r_{o1}} \right) R_{E1} \right]$$

$$I_{REF} \approx \frac{10 - 0.7}{13.6 + 5} = 0.5 \text{ mA}$$

$$r_{\pi 1} = \frac{(50)(0.026)}{0.5} = 2.6 \text{ k}\Omega$$

$$r_{o1} = \frac{75}{0.5} = 150 \text{ k}\Omega$$

$$g_{m1} = \frac{0.5}{0.026} = 19.23 \text{ mA/V}$$


$$V_x' = V_{\pi 1} \left[ 1 + \left( \frac{1}{2.6} + 19.23 + \frac{1}{150} \right) (5) \right]$$

$$\Rightarrow V_{\pi 1} = V_x' (0.01009)$$

$$\text{Then } I_x' = V_x' (0.01009) \left[ \frac{1}{2.6} + 19.23 + \frac{1}{150} \right] + \frac{V_x'}{13.6}$$

$$I_x' = V_x' (0.1980) + V_x' (0.0735)$$
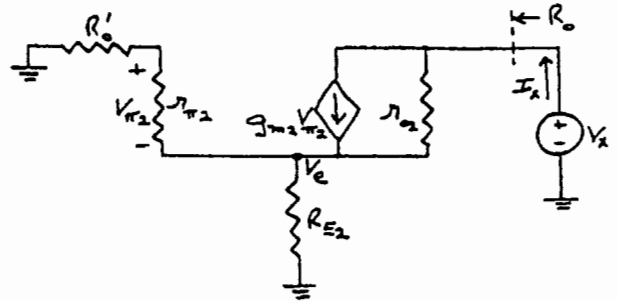
$$\Rightarrow R_o' = \frac{V_x'}{I_x'} = 3.683 \text{ k}\Omega$$



$$I_x = \frac{V_x - V_e}{r_{o2}} + g_{m2} V_{\pi 2}$$

$$V_e = I_x [R_{E2} \parallel (r_{\pi 2} + R_o')]$$

$$V_{\pi 2} = - \left( \frac{r_{\pi 2}}{r_{\pi 2} + R_o'} \right) V_e$$

Then

$$I_x = \frac{V_x}{r_{o2}} - \frac{I_x}{r_{o2}} [R_{E2} \parallel (r_{\pi 2} + R_o')] - g_{m2} \left( \frac{r_{\pi 2}}{r_{\pi 2} + R_o'} \right) (I_x) [R_{E2} \parallel (r_{\pi 2} + R_o')]$$

$$R_{E1} = R_{E2} \Rightarrow I_{REF} = I_0 \Rightarrow r_{\pi 2} = 2.6 \text{ k}\Omega$$

$$r_{o2} = 150 \text{ k}\Omega$$

$$g_{m2} = 19.23 \text{ mA/V}$$

$$I_X = \frac{V_X}{150} - \frac{I_X}{150} [5 \parallel (2.6 + 3.68)]$$

$$- (19.23) \left( \frac{2.6}{2.6 + 3.68} \right) (I_X) [5 \parallel (2.6 + 3.68)]$$

$$I_X = V_X (0.00666) - I_X (0.01853) - I_X (22.13)$$

$$I_X (23.148) = V_X (0.00666)$$

$$\Rightarrow R_0 = \frac{V_X}{I_X} = 3.48 \text{ M}\Omega$$

b. When  $R_{E1} = R_{E2} = 0$

$$R_0 \approx r_{o2} = 150 \text{ k}\Omega$$

10.28

Assume all transistors are matched.

a.

$$2V_{BE1} = V_{BE3} + I_0 R_E$$

$$V_{BE1} = V_T \ln \left( \frac{I_{REF}}{I_S} \right)$$

$$V_{BE3} = V_T \ln \left( \frac{I_0}{I_S} \right)$$

$$2V_T \ln \left( \frac{I_{REF}}{I_S} \right) - V_T \ln \left( \frac{I_0}{I_S} \right) = I_0 R_E$$

$$V_T \left[ \ln \left( \frac{I_{REF}}{I_S} \right)^2 - \ln \left( \frac{I_0}{I_S} \right) \right] = I_0 R_E$$

$$V_T \ln \left( \frac{I_{REF}^2}{I_0 I_S} \right) = I_0 R_E$$

b.  $V_{BE} = 0.7 \text{ V at } 1 \text{ mA} \Rightarrow 10^{-3} = I_S \exp \left( \frac{0.7}{0.026} \right)$

or  $I_S = 2.03 \times 10^{-15} \text{ A}$

$V_{BE}$  at  $0.1 \text{ mA}$

$$\Rightarrow V_{BE} = (0.026) \ln \left( \frac{0.1 \times 10^{-3}}{2.03 \times 10^{-15}} \right) = 0.640 \text{ V}$$

Since  $I_0 = I_{REF}$ , then

$$V_{BE} = I_0 R_E \Rightarrow R_E = \frac{0.640}{0.1}$$

or  $R_E = 6.4 \text{ k}\Omega$

10.29

$$I_{REF} = \frac{10 - 0.7}{R_1} = 0.5 \Rightarrow R_1 = 18.6 \text{ k}\Omega$$

$$I_{02} R_{E2} = V_T \ln \left( \frac{I_{REF}}{I_{01}} \right)$$

$$R_{E2} = \frac{0.026}{0.010} \cdot \ln \left( \frac{0.50}{0.01} \right) \Rightarrow R_{E2} = 10.17 \text{ k}\Omega$$

$$R_{E3} = \frac{0.026}{0.030} \cdot \ln \left( \frac{0.50}{0.03} \right) \Rightarrow R_{E3} = 2.438 \text{ k}\Omega$$

$$V_{BE2} = 0.7 - I_{02} R_{E2} = 0.7 - (0.01)(10.17)$$

$$\Rightarrow V_{BE2} = 0.598 \text{ V}$$

$$V_{BE3} = 0.7 - I_{03} R_{E3} = 0.7 - (0.03)(2.438)$$

$$\Rightarrow V_{BE3} = 0.627 \text{ V}$$

10.30

(a)  $V_{BE1} = V_{BE2}$

$$I_{REF} = \frac{V^+ - 2V_{BE1} - V^-}{R_1 + R_2}$$

Now

$$2V_{BE1} + I_{REF} R_2 = V_{BE3} + I_0 R_E$$

or

$$I_0 R_E = 2V_{BE1} - V_{BE3} + I_{REF} R_2$$

We have

$$V_{BE1} = V_T \ln \left( \frac{I_{REF}}{I_S} \right) \text{ and } V_{BE3} = V_T \ln \left( \frac{I_0}{I_S} \right)$$

(b) Let  $R_1 = R_2$  and  $I_0 = I_{REF} \Rightarrow V_{BE1} = V_{BE3} \equiv V_{BE}$

Then

$$V_{BE} = I_0 R_E - I_{REF} R_2 = I_0 (R_E - R_2)$$

so

$$I_{REF} = I_0 = \frac{V^+ - V^- - 2I_0 (R_E - R_2)}{2R_2}$$

$$= \frac{V^+ - V^-}{2R_2} - I_0 \left( \frac{R_E}{R_2} \right) + I_0$$

Then

$$I_0 = \frac{V^+ - V^-}{2R_E}$$

(c) Want  $I_0 = 0.5 \text{ mA}$

$$\text{So } R_E = \frac{5 - (-5)}{2(0.5)} \Rightarrow R_E = 10 \text{ k}\Omega$$

$$2R_2 = \frac{5 - 2(0.7) - (-5)}{0.5} = 17.2 \text{ k}\Omega$$

Then  $R_1 = R_2 = 8.6 \text{ k}\Omega$

10.31

a.  $I_{REF} = \frac{20 - 0.7 - 0.7}{12} = 1.55 \text{ mA}$

$$I_{01} = 2I_{REF} = 3.1 \text{ mA}$$

$$I_{02} = I_{REF} = 1.55 \text{ mA}$$

$$I_{03} = 3I_{REF} = 4.65 \text{ mA}$$

b.  $V_{CE1} = -I_{01} R_{C1} - (-10) = -(3.1)(2) + 10$

$$\Rightarrow V_{CE1} = 3.8 \text{ V}$$

$$V_{EC2} = 10 - I_{02} R_{C2} = 10 - (1.55)(3)$$

$$\Rightarrow V_{EC2} = 5.35 \text{ V}$$

$$V_{EC3} = 10 - I_{03} R_{C3} = 10 - (4.65)(1)$$

$$\Rightarrow V_{EC3} = 5.35 \text{ V}$$

10.32

a. 1st approximation

$$I_{REF} \approx \frac{20 - 1.4}{8} = 2.325 \text{ mA}$$

$$\text{Now } V_{BE} - 0.7 = (0.026) \ln \left( \frac{2.32}{1} \right)$$

$$\Rightarrow V_{BE} = V_{EB} = 0.722 \text{ V}$$

Then 2nd approximation

$$I_{REF} \approx \frac{20 - 2(0.722)}{8} = 2.32 \text{ mA}$$

$$I_{01} = 2I_{REF} = 4.64 \text{ mA}$$

$$I_{02} = I_{REF} = 2.32 \text{ mA}$$

$$I_{03} = 3I_{REF} = 6.96 \text{ mA}$$

b. At the edge of saturation,  $V_{CE} = V_{BE} = 0.722 \text{ V}$

$$R_{C1} = \frac{0 - 0.722 - (-10)}{4.64} \Rightarrow \underline{R_{C1} = 2.0 \text{ k}\Omega}$$

$$R_{C2} = \frac{10 - 0.722}{2.32} \Rightarrow \underline{R_{C2} = 4.0 \text{ k}\Omega}$$

$$R_{C3} = \frac{10 - 0.722}{6.96} \Rightarrow \underline{R_{C3} = 1.33 \text{ k}\Omega}$$

10.33

1st approximation

$$I_{REF} = \frac{10 - 0.7}{6.3 + 3} = 1 \text{ mA}$$

$$\Rightarrow V_B = 0.7 \text{ V as assumed}$$

$$V_{RE1} = I_{REF} \cdot R_{E1} = (1)(3) = 3 \text{ V}$$

$$V_{RE1} = 3 \text{ V} \Rightarrow R_{E1} = \frac{V_{RE1}}{I_{01}} = \frac{3}{1} \Rightarrow \underline{R_{E1} = 3 \text{ k}\Omega}$$

$$V_{RE2} = 3 \text{ V} \Rightarrow R_{E2} = \frac{V_{RE2}}{I_{02}} = \frac{3}{2} \Rightarrow \underline{R_{E2} = 1.5 \text{ k}\Omega}$$

$$V_{RE3} = 3 \text{ V} \Rightarrow R_{E3} = \frac{V_{RE3}}{I_{03}} = \frac{3}{4} \Rightarrow \underline{R_{E3} = 0.75 \text{ k}\Omega}$$

$$I_{01} = 1 \text{ mA}$$

$$I_{02} = 2 \text{ mA}$$

$$I_{03} = 4 \text{ mA}$$

10.34

$$V_{GS} = V_{TN1} + \sqrt{\frac{I_{REF}}{K_{n1}}} = 1 + \sqrt{\frac{200}{250}} = 1.89 \text{ V} = V_{DS1}$$

$$\frac{I_0}{I_{REF}} = \frac{1 + \lambda V_{DS2}}{1 + \lambda V_{DS1}}$$

a.  $V_{DS2} = 2 \text{ V}$

$$I_0 = (200) \left[ \frac{1 + (0.02)(2)}{1 + (0.02)(1.89)} \right] \Rightarrow \underline{I_0 \approx 200 \mu\text{A}}$$

b.  $V_{DS2} = 4 \text{ V}$

$$I_0 = (200) \left[ \frac{1 + (0.02)(4)}{1 + (0.02)(1.89)} \right] \Rightarrow \underline{I_0 \approx 208 \mu\text{A}}$$

c.  $V_{DS2} = 6 \text{ V}$

$$I_0 = (200) \left[ \frac{1 + (0.02)(6)}{1 + (0.02)(1.89)} \right] \Rightarrow \underline{I_0 \approx 216 \mu\text{A}}$$

10.35

$$(a) V_{GS} = V_{TN1} + \sqrt{\frac{I_{REF}}{K_{n1}}} = 1 + \sqrt{\frac{0.5}{0.5}} = 2 \text{ V}$$

$$I_0 = K_{n2} \left( \sqrt{\frac{I_{REF}}{K_{n1}}} \right)^2 = K_{n2} \left( \frac{I_{REF}}{K_{n1}} \right)$$

$$I_0(\text{max}) = (0.5)(1.05) \left( \frac{0.5}{0.5} \right) \Rightarrow I_0(\text{max}) = 0.525 \text{ mA}$$

$$I_0(\text{min}) = (0.5)(0.95) \left( \frac{0.5}{0.5} \right) \Rightarrow I_0(\text{min}) = 0.475 \text{ mA}$$

So

$$0.475 \leq I_0 \leq 0.525 \text{ mA}$$

$$(b) I_0 = K_{n2} \left[ \sqrt{\frac{I_{REF}}{K_{n1}}} + V_{TN1} - V_{TN2} \right]^2$$

$$I_0(\text{min}) = (0.5) \left[ \sqrt{\frac{0.5}{0.5}} + 1 - 1.05 \right]^2$$

$$\Rightarrow I_0(\text{min}) = 0.451 \text{ mA}$$


$$I_0(\text{max}) = (0.5) \left[ \sqrt{\frac{0.5}{0.5}} + 1 - 0.95 \right]^2$$

$$\Rightarrow I_0(\text{max}) = 0.551 \text{ mA}$$

So

$$0.451 \leq I_0 \leq 0.551 \text{ mA}$$

10.36

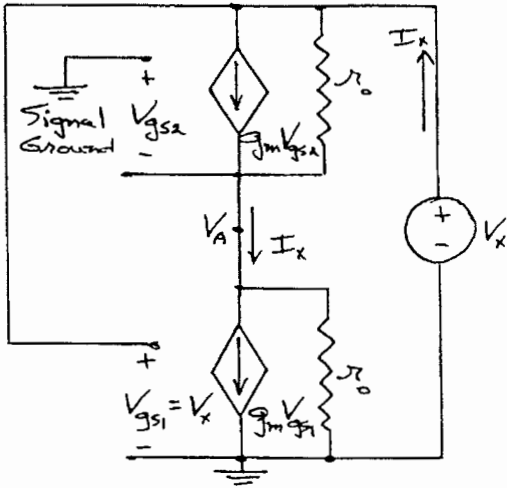

$$(1) I_x = \frac{V_x - V_A}{r_o} + g_m V_{gs2}$$

$$(2) I_x = \frac{V_A}{r_o} + g_m V_{gs1}$$

$$V_{gs1} = V_x, \quad V_{gs2} = -V_A$$

So

$$(1) I_x = \frac{V_x}{r_o} - V_A \left( \frac{1}{r_o} + g_m \right)$$

$$(2) I_x = \frac{V_A}{r_o} + g_m V_x \Rightarrow V_A = r_o [I_x - g_m V_x]$$

Then

$$I_x = \frac{V_x}{r_o} - r_o (I_x - g_m V_x) \left( \frac{1}{r_o} + g_m \right)$$

$$I_x = \frac{V_x}{r_o} - r_o \left[ \frac{I_x}{r_o} + g_m I_x - \frac{g_m}{r_o} V_x - g_m^2 V_x \right]$$

$$I_x = \frac{V_x}{r_o} - I_x - g_m r_o I_x + g_m V_x + g_m^2 r_o V_x$$

$$I_x [2 + g_m r_o] = V_x \left[ \frac{1}{r_o} + g_m + g_m^2 r_o \right]$$

Since  $g_m \gg \frac{1}{r_o}$

$$I_x [2 + g_m r_o] \cong V_x (g_m) (1 + g_m r_o)$$

Then

$$\frac{V_x}{I_x} = R_o = \frac{2 + g_m r_o}{g_m (1 + g_m r_o)}$$

Usually,  $g_m r_o \gg 2$ , so that

$$R_o \cong \frac{1}{g_m}$$

10.37

(a)  $V_{Ds}(\text{sat}) = V_{GS} - V_{TN}$

or  $V_{GS} = V_{Ds}(\text{sat}) + V_{TN} = 0.2 + 0.8 = 1.0$

$$I_D = \frac{k'_n}{2} \left( \frac{W}{L} \right) (V_{GS} - V_{TN})^2$$

$$50 = 48 \left( \frac{W}{L} \right) (0.2)^2 \Rightarrow \left( \frac{W}{L} \right) = 26$$

(b)  $V_{GS5} - V_{TN} = 2(V_{GS} - V_{TN})$

$$V_{GS5} = 0.8 + 2(0.2) \Rightarrow V_{GS5} = 1.2 \text{ V}$$

(c)  $V_{D1}(\text{min}) = 2V_{Ds}(\text{sat}) = 2(0.2) \Rightarrow$

$$V_{D1}(\text{min}) = 0.4 \text{ V}$$

10.38

$$V_{Ds2}(\text{sat}) = 2 \text{ V} = V_{GS2} - V_{TN2} = V_{GS2} - 1.5 \Rightarrow$$

$$V_{GS2} = 3.5 \text{ V}$$

$$I_O = \left( \frac{1}{2} \mu_n C_{ox} \right) \left( \frac{W}{L} \right)_2 (V_{GS2} - V_{TN2})^2$$

$$250 = (20) \left( \frac{W}{L} \right)_2 (3.5 - 1.5)^2 \Rightarrow$$

$$\left( \frac{W}{L} \right)_2 = 3.125$$

$$I_{REF} = \left( \frac{1}{2} \mu_n C_{ox} \right) \left( \frac{W}{L} \right)_1 (V_{GS2} - V_{TN1})$$

$$100 = (20) \left( \frac{W}{L} \right)_2 (3.5 - 1.5)^2 \Rightarrow$$

$$\left( \frac{W}{L} \right)_1 = 1.25$$

Now  $V_{GS3} = 10 - V_{GS2} = 10 - 3.5 = 6.5 \text{ V}$

$$\text{So } 100 = (20) \left( \frac{W}{L} \right)_3 (6.5 - 1.5)^2 \Rightarrow$$

$$\left( \frac{W}{L} \right)_3 = 0.2$$

10.39

a. From Equation (10.50),

$$V_{GS1} = V_{GS2} = \left( \frac{\sqrt{\frac{5}{25}}}{1 + \sqrt{\frac{5}{25}}} \right) (5) + \left( \frac{1 - \sqrt{\frac{5}{25}}}{1 + \sqrt{\frac{5}{25}}} \right) (0.5)$$

$$= \left( \frac{0.447}{1 + 0.447} \right) (5) + \left( \frac{1 - 0.447}{1 + 0.447} \right) (0.5)$$

$$V_{GS1} = V_{GS2} = 1.74 \text{ V}$$

$$I_{REF} \cong K_{n1}(V_{GS1} - V_{TN})^2 = (18)(25)(1.74 - 0.5)^2 \Rightarrow I_{REF} = 0.692 \text{ mA}$$

$$b. \quad I_O = \left( \frac{1}{2} \mu_n C_{ox} \right) \left( \frac{W}{L} \right)_2 (V_{GS2} - V_{TN})^2 (1 + \lambda V_{DS2})$$

$$I_O = (18)(15)(1.74 - 0.5)^2 [1 + (0.02)(2)] = (415)(104) \Rightarrow I_O = 0.432 \text{ mA}$$

$$c. \quad I_O = (415)[1 + (0.02)(4)] \Rightarrow I_O = 0.448 \text{ mA}$$

10.40

$$(a) \quad I_{REF} = \left( \frac{k'_p}{2} \right) \left( \frac{W}{L} \right)_1 (V_{SG1} + V_{TP})^2 = \left( \frac{k'_p}{2} \right) \left( \frac{W}{L} \right)_3 (V_{SG3} + V_{TP})^2$$

$$\text{But } V_{SG3} = 3 - V_{SG1}$$

So

$$25(V_{SG1} - 0.4)^2 = 5(3 - V_{SG1} - 0.4)^2$$

which yields  $V_{SG1} = 1.08 \text{ V}$  and  $V_{SG3} = 1.92 \text{ V}$

$$I_{REF} = 20(25)(1.08 - 0.4)^2 \Rightarrow I_{REF} = 231 \mu\text{A}$$

$$\frac{I_O}{I_{REF}} = \frac{(W/L)_2}{(W/L)_1} = \frac{15}{25} = 0.6$$

$$\text{Then } I_O = (0.6)(231) = 139 \mu\text{A}$$

$$(b) \quad V_{DS2}(\text{sat}) = 1.08 - 0.4 = 0.68 \text{ V}$$

$$V_R = 3 - 0.68 = 2.32 = I_O R$$

then

$$R = \frac{2.32}{0.139} \Rightarrow R = 16.7 \text{ k}\Omega$$

10.41

$$V_{SD2}(\text{sat}) = 0.25 = V_{SG} + V_{TP} = V_{SG} - 0.4 \Rightarrow$$

$$V_{SG2} = 0.65 \text{ V}$$

$$I_O = \frac{k'_p}{2} \left( \frac{W}{L} \right)_2 (V_{SG2} + V_{TP})^2$$

$$25 = \frac{40}{2} \left( \frac{W}{L} \right)_2 (0.65 - 0.4)^2 \Rightarrow \left( \frac{W}{L} \right)_2 = 20$$

$$I_{REF} = 75 \mu\text{A} = \frac{(W/L)_1}{(W/L)_2} \cdot I_O \Rightarrow \left( \frac{W}{L} \right)_1 = 60$$

$$I_{REF} = \frac{k'_p}{2} \left( \frac{W}{L} \right)_3 (V_{SG3} + V_{TP})^2$$

$$V_{SG3} = 3 - 0.65 = 2.35 \text{ V}$$

Then

$$75 = \frac{40}{2} \left( \frac{W}{L} \right)_3 (2.35 - 0.4)^2 \Rightarrow \left( \frac{W}{L} \right)_3 = 0.986$$

10.42

$$a. \quad I_{REF} = K_n (V_{GS} - V_{TN})^2$$

$$100 = 100(V_{GS} - 2)^2 \Rightarrow V_{GS} = 3 \text{ V}$$

$$\text{For } V_{D4} = -3 \text{ V, } I_O \approx 100 \mu\text{A}$$

$$b. \quad R_O = r_{o4} + r_{o2}(1 + g_m r_{o4})$$

$$r_{o2} = r_{o4} = \frac{1}{\lambda I_O} = \frac{1}{(0.02)(0.1)} = 500 \text{ k}\Omega$$


$$g_m = 2K_n(V_{GS} - V_{TN}) = 2(0.1)(3 - 2) = 0.2 \text{ mA/V}$$

$$R_O = 500 + 500[1 + (0.2)(500)]$$

$$R_O = 51 \text{ M}\Omega$$

$$\Delta I_O = \frac{1}{R_O} \cdot \Delta V_{D4} = \frac{6}{51} \Rightarrow \Delta I_O = 0.118 \mu\text{A}$$

10.43

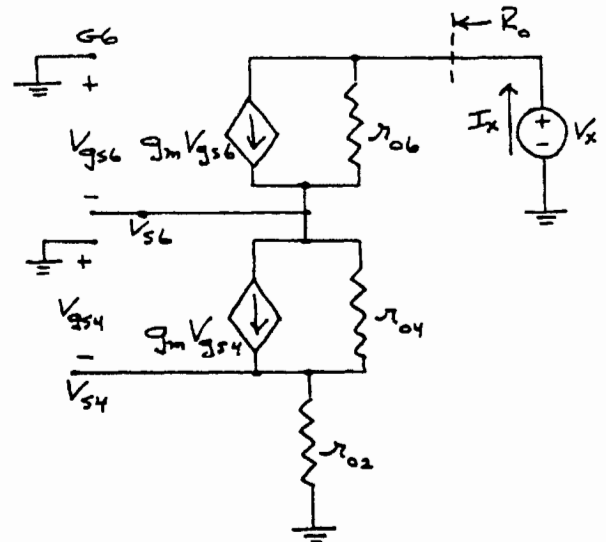

$$V_{gs4} = -I_X r_{o2}$$

$$V_{S6} = (I_X - g_m V_{gs4})r_{o4} + I_X r_{o2}$$

$$= (I_X + g_m I_X r_{o2})r_{o4} + I_X r_{o2}$$

$$V_{S6} = I_X [r_{o2} + (1 + g_m r_{o2})r_{o4}] = -V_{gs6}$$

$$I_X = g_m V_{gs6} + \frac{V_X - V_{SG}}{r_{o6}} = \frac{V_X}{r_{o6}} - V_{S6} \left( g_m + \frac{1}{r_{o6}} \right)$$

$$I_X = \frac{V_X}{r_{o6}} - I_X \left( g_m + \frac{1}{r_{o6}} \right) [r_{o2} + (1 + g_m r_{o2})r_{o4}]$$

$$I_X \left\{ 1 + \left( g_m + \frac{1}{r_{o6}} \right) [r_{o2} + (1 + g_m r_{o2})r_{o4}] \right\} = \frac{V_X}{r_{o6}}$$

$$\frac{V_X}{I_X} = R_O = r_{o6} + (1 + g_m r_{o6}) [r_{o2} + (1 + g_m r_{o2})r_{o4}]$$

$$I_O \approx I_{REF} = 0.2 \text{ mA} = 0.2(V_{GS} - 1)^2$$

$$V_{GS} = 2 \text{ V}$$

$$g_m = 2K_n(V_{GS} - V_{TN}) = 2(0.2)(2 - 1) = 0.4 \text{ mA/V}$$

$$r_{o2} = r_{o4} = r_{o6} = \frac{1}{\lambda I_0} = \frac{1}{(0.02)(0.2)} = 250 \text{ k}\Omega$$

$$R_o = 250 + [1 + (0.4)(250)] \times \{250 + [1 + (0.4)(250)](250)\}$$

$$R_o = 2575750 \text{ k}\Omega$$

$$\Rightarrow R_o = 2.58 \times 10^9 \Omega$$

10.44

$$\frac{k'_n}{2} \left(\frac{W}{L}\right)_1 (V_{GS1} - V_{TN})^2 = \frac{k'_n}{2} \left(\frac{W}{L}\right)_3 (V_{GS3} - V_{TN})^2$$

$$= \frac{k'_p}{2} \left(\frac{W}{L}\right)_4 (V_{SG4} + V_{TP})^2$$

$$(1) 50(20)(V_{GS1} - 0.5)^2 = 50(5)(V_{GS3} - 0.5)^2$$

$$(2) 50(20)(V_{GS1} - 0.5)^2 = 20(10)(V_{SG4} - 0.5)^2$$

$$(3) V_{SG4} + V_{GS3} + V_{GS1} = 6$$

$$\text{From (1)} 4(V_{GS1} - 0.5)^2 = (V_{GS3} - 0.5)^2 \Rightarrow$$

$$V_{GS3} = 2(V_{GS1} - 0.5) + 0.5$$

$$\text{From (2)} 5(V_{GS1} - 0.5)^2 = (V_{SG4} - 0.5)^2 \Rightarrow$$

$$V_{SG4} = \sqrt{5}(V_{GS1} - 0.5) + 0.5$$

Then (3) becomes

$$\sqrt{5}(V_{GS1} - 0.5) + 0.5 + 2(V_{GS1} - 0.5) + 0.5 + V_{GS1} = 6$$

which yields  $V_{GS1} = 1.36 \text{ V}$  and

$$V_{GS3} = 2.22 \text{ V}, \quad V_{SG4} = 2.42 \text{ V}$$

Then

$$I_{REF} = \frac{k'_n}{2} \left(\frac{W}{L}\right)_1 (V_{GS1} - V_{TN})^2 = 50(20)(1.36 - 0.5)^2$$

$$\text{or } I_{REF} = I_o = 0.740 \text{ mA}$$

$$V_{GS1} = V_{GS2} = 1.36 \text{ V}$$

$$V_{DS2}(\text{sat}) = V_{GS2} - V_{TN} = 1.36 - 0.5 \Rightarrow$$

$$V_{DS2}(\text{sat}) = 0.86 \text{ V}$$

10.45

$$V_{DS2}(\text{sat}) = 0.5 \text{ V} = V_{GS2} - V_{TN} = V_{GS2} - 0.5 \Rightarrow$$

$$V_{GS2} = 1 \text{ V}$$

$$I_o = 50 \mu\text{A} = \frac{k'_n}{2} \left(\frac{W}{L}\right)_2 (V_{GS2} - V_{TN})^2$$

$$= 50 \left(\frac{W}{L}\right)_2 (1 - 0.5)^2 \Rightarrow \left(\frac{W}{L}\right)_2 = 4$$

$$V_{GS1} = V_{GS2} = 1 \text{ V} \Rightarrow$$

$$I_{REF} = 150 = \frac{k'_n}{2} \left(\frac{W}{L}\right)_1 (V_{GS1} - V_{TN})^2$$

$$= 50 \left(\frac{W}{L}\right)_1 (1 - 0.5)^2 \Rightarrow \left(\frac{W}{L}\right)_1 = 12$$

$$V_{GS3} + V_{SG4} + V_{GS1} = 6$$

$$2V_{GS3} = 6 - 1 = 5 \text{ V} \Rightarrow V_{GS3} = 2.5 \text{ V}$$

$$I_{REF} = 150 = 50 \left(\frac{W}{L}\right)_3 (2.5 - 0.5)^2 \Rightarrow \left(\frac{W}{L}\right)_3 = 0.75$$

$$I_{REF} = \frac{k'_p}{2} \left(\frac{W}{L}\right)_4 (V_{SG4} + V_{TP})^2$$

$$150 = 20 \left(\frac{W}{L}\right)_4 (2.5 - 0.5)^2 \Rightarrow \left(\frac{W}{L}\right)_4 = 1.88$$

10.46

a. As a first approximation

$$I_{REF} = 80 = 80(V_{GS1} - 1)^2 \Rightarrow V_{GS1} = 2 \text{ V}$$

$$\text{Then } V_{DS1} \approx 2(2) = 4 \text{ V}$$

The second approximation

$$80 = 80(V_{GS1} - 1)^2 [1 + (0.02)(4)]$$

$$\text{Or } \frac{80}{86.4} = (V_{GS1} - 1)^2 \Rightarrow V_{GS1} = 1.962$$

Then

$$I_o = K_n(V_{GS1} - V_{TN})^2 (1 + \lambda_n V_{GS1})$$

$$= 80(1.962 - 1)^2 [1 + (0.02)(1.962)]$$

$$\text{Or } I_o = 76.94 \mu\text{A}$$

b. From a PSpice analysis,  $I_o = 77.09 \mu\text{A}$  for  $V_{D3} = -1 \text{ V}$  and  $I_o = 77.14 \mu\text{A}$  for  $V_{D3} = 3 \text{ V}$ . The change is  $\Delta I_o \approx 0.05 \mu\text{A}$  or 0.065%.

10.47

a. For a first approximation,

$$I_{REF} = 80 = 80(V_{GS4} - 1)^2 \Rightarrow V_{GS4} = 2 \text{ V}$$

As a second approximation

$$I_{REF} = 80 = 80(V_{GS4} - 1)^2 [1 + (0.02)(2)]$$

$$\text{Or } V_{GS4} = 1.98 \text{ V} = V_{GS1}$$

$$I_o = K_n(V_{GS2} - V_{TN})^2 (1 + \lambda V_{GS2})$$

To a very good approximation

$$I_o = 80 \mu\text{A}$$

b. From a PSpice analysis,  $I_o = 80.00 \mu\text{A}$  for  $V_{D3} = -1 \text{ V}$  and the output resistance is  $R_o = 76.9 \text{ M}\Omega$ . Then

$$\Delta I_o = \frac{1}{R_o} \cdot V_{D3} = \frac{4}{76.9} = 0.052 \mu\text{A}$$

or a change of 0.065%.

10.48

$$(a) K_{n1} = \frac{k'_n}{2} \left( \frac{W}{L} \right)_1 = 50(5) = 250 \mu\text{A}/\text{V}^2$$

$$R = \frac{1}{\sqrt{K_{n1} I_{D1}}} \left( 1 - \sqrt{\frac{(W/L)_1}{(W/L)_2}} \right)$$

$$= \frac{1}{\sqrt{(0.25)(0.05)}} \left( 1 - \sqrt{\frac{5}{50}} \right) = (8.94)(0.684)$$

$$R = 6.11 \text{ k}\Omega$$

$$(b) V^+ - V^- = V_{SD3}(\text{sat}) + V_{GS1}$$

$$V_{SD3}(\text{sat}) = V_{SG3} + V_{TP}$$

$$I_{D1} = 50 = 20(5)(V_{SG3} - 0.5)^2 \Rightarrow V_{SG3} = 1.21 \text{ V}$$

Then

$$V_{SD3}(\text{sat}) = 1.21 - 0.5 = 0.71 \text{ V}$$

Also

$$I_{D1} = 50 = 50(5)(V_{GS1} - 0.5)^2 \Rightarrow V_{GS1} = 0.947 \text{ V}$$

Then

$$(V^+ - V^-)_{\min} = 0.71 + 0.947 = 1.66 \text{ V}$$

$$(c) I_{O1} = 25 = 50 \left( \frac{W}{L} \right)_5 (0.947 - 0.5)^2 \Rightarrow \left( \frac{W}{L} \right)_5 = 2.5$$

$$I_{O2} = 75 = 20 \left( \frac{W}{L} \right)_6 (1.21 - 0.5)^2 \Rightarrow \left( \frac{W}{L} \right)_6 = 7.44$$

10.49

$$V_{GS3} = \frac{1}{3}(5) = 1.667 \text{ V}$$

$$I_{REF} = \left( \frac{1}{2} \mu_n C_{ox} \right) \left( \frac{W}{L} \right)_3 (V_{GS3} - V_{TN})^2$$

$$100 = (20) \left( \frac{W}{L} \right)_3 (1.667 - 1)^2$$

$$\Rightarrow \left( \frac{W}{L} \right)_3 = \left( \frac{W}{L} \right)_4 = \left( \frac{W}{L} \right)_5 = 11.2$$

$$I_{O1} = \left( \frac{1}{2} \mu_n C_{ox} \right) \left( \frac{W}{L} \right)_1 (V_{GS3} - V_{TN})^2$$

$$\text{Or } \frac{I_{REF}}{I_{O1}} = \left( \frac{W}{L} \right)_3$$

$$\left( \frac{W}{L} \right)_1 = \left( \frac{I_{O1}}{I_{REF}} \right) \left( \frac{W}{L} \right)_3 = \left( \frac{0.2}{0.1} \right) (11.2)$$

$$\Rightarrow \left( \frac{W}{L} \right)_1 = 22.4$$

$$\text{And } \left( \frac{W}{L} \right)_2 = \left( \frac{I_{O2}}{I_{REF}} \right) \left( \frac{W}{L} \right)_3 = \left( \frac{0.3}{0.1} \right) (11.2)$$

$$\Rightarrow \left( \frac{W}{L} \right)_2 = 33.6$$

10.50

$$I_{REF} = \frac{24 - V_{SGP} - V_{GSN}}{R}$$

Also

$$I_{REF} = 40(1)(V_{GSN} - 1.2)^2$$

$$I_{REF} = 18(1)(V_{SGP} - 1.2)^2$$

Then

$$\sqrt{40}(V_{GSN} - 1.2) = \sqrt{18}(V_{SGP} - 1.2)$$

which yields

$$V_{SGP} = \frac{6.325}{4.243}(V_{GSN} - 1.2) + 1.2$$

Then

$$\left[ 0.040(V_{GSN} - 1.2)^2 \right] \cdot R = 24 - V_{GSN} - 1.49(V_{GSN} - 1.2) - 1.2$$

which yields

$$V_{GSN} = 2.69 \text{ V and } V_{SGP} = 3.42 \text{ V}$$

Now

$$I_{REF} = \frac{24 - 3.42 - 2.69}{200} \Rightarrow I_{REF} = 89.5 \mu\text{A}$$

$$I_1 = \frac{89.5}{5} = 17.9 \mu\text{A}$$

$$I_2 = (1.25)(89.5) = 112 \mu\text{A}$$

$$I_3 = (0.8)(89.5) = 71.6 \mu\text{A}$$

$$I_4 = 4(89.5) = 358 \mu\text{A}$$

10.51

 We have  $V_{GSN} = 2.69 \text{ V}$  and  $V_{SGP} = 3.42 \text{ V}$ 

So

$$I_{REF} = \frac{10 - 2.69 - 3.42}{R} = \frac{3.89}{200} \Rightarrow I_{REF} = 19.45 \mu\text{A}$$

Then

$$I_1 = (0.2)(19.45) = 3.89 \mu\text{A}$$

$$I_2 = (1.25)(19.45) = 24.3 \mu\text{A}$$

$$I_3 = (0.8)(19.45) = 15.56 \mu\text{A}$$

$$I_4 = 4(19.45) = 77.8 \mu\text{A}$$

10.52

 For  $v_{GS} = 0$ ,  $i_D = I_{DSS}(1 + \lambda v_{DS})$ 

$$a. V_D = -5 \text{ V, } v_{DS} = 5$$

$$i_D = (2)[1 + (0.05)(5)]$$

$$\Rightarrow \underline{i_D = 2.5 \text{ mA}}$$

$$b. V_D = 0, v_{DS} = 10$$

$$i_D = (2)[1 + (0.05)(10)]$$

$$\Rightarrow \underline{i_D = 3 \text{ mA}}$$

$$c. V_D = 5 \text{ V, } v_{DS} = 15 \text{ V}$$

$$i_D = (2)[1 + (0.05)(15)]$$

$$\Rightarrow \underline{i_D = 3.5 \text{ mA}}$$

10.54

$$I_0 = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$2 = 4 \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$\frac{V_{GS}}{V_P} = 1 - \sqrt{\frac{2}{4}} = 0.293$$

$$\text{So } V_{GS} = (0.293)(-4) = -1.17 \text{ V}$$

$$\text{Then } I_0 = \frac{V_S}{R} \text{ and } V_S = -V_{GS}$$

$$R = \frac{-V_{GS}}{I_0} = \frac{-(-1.17)}{2} \Rightarrow R = 0.585 \text{ k}\Omega$$

10.55

$$\text{a. } I_{REF} = I_{S1} \exp\left(\frac{V_{EB1}}{V_T}\right)$$

$$\text{or } V_{EB1} = V_T \ln\left(\frac{I_{REF}}{I_{S1}}\right) = (0.026) \ln\left(\frac{1 \times 10^{-3}}{5 \times 10^{-13}}\right)$$

$$\Rightarrow V_{EB1} = 0.5568$$

$$\text{b. } R_1 = \frac{5 - 0.5568}{1} \Rightarrow R_1 = 4.44 \text{ k}\Omega$$

c. From Equation (10.72) and letting  $V_{CE0} = V_{EC2} = 2.5 \text{ V}$

$$10^{-12} \exp\left(\frac{V_I}{V_T}\right) \left[1 + \frac{2.5}{120}\right] = 10^{-3} \left(\frac{1 + \frac{2.5}{80}}{1 + \frac{0.5568}{80}}\right)$$

$$1.0208 \times 10^{-12} \exp\left(\frac{V_I}{V_T}\right) = (10^{-3}) \left(\frac{1.03125}{1.00696}\right)$$

Then

$$V_I = 0.026 \ln(1.003613 \times 10^9)$$

$$\text{So } V_I = 0.5389 \text{ V}$$

$$\text{d. } A_v = \frac{-(1/V_T)}{(1/V_{AN}) + (1/V_{AP})}$$

$$A_v = \frac{-\frac{1}{0.026}}{\frac{1}{120} + \frac{1}{80}} = \frac{-38.46}{0.00833 + 0.0125}$$

$$A_v = -1846$$

10.56

$$\text{a. } V_{BE} = V_T \ln\left(\frac{I_{REF}}{I_{S1}}\right) = (0.026) \ln\left(\frac{0.5 \times 10^{-3}}{10^{-12}}\right)$$

$$\Rightarrow V_{BE} = 0.5208$$

$$\text{b. } R_1 = \frac{5 - 0.5208}{0.5} \Rightarrow R_1 = 8.96 \text{ k}\Omega$$

c. From Equation (10.72) applies with slight modifications

$$I_{S0} \exp\left(\frac{V_{EB0}}{V_T}\right) \left[1 + \frac{V_{EC0}}{V_{AP}}\right] = I_{REF} \cdot \left(\frac{1 + \frac{V_{CE2}}{V_{AN}}}{1 + \frac{V_{BE2}}{V_{AN}}}\right)$$

$$(5 \times 10^{-13}) \left[\exp\left(\frac{V_{EB0}}{V_T}\right)\right] \left(1 + \frac{2.5}{80}\right)$$

$$= (0.5 \times 10^{-3}) \cdot \left(\frac{1 + \frac{2.5}{120}}{1 + \frac{0.5208}{120}}\right)$$

$$5.15625 \times 10^{-13} \exp\left(\frac{V_{EB0}}{V_T}\right) = (0.5 \times 10^{-3}) \cdot \frac{1.02083}{1.00434}$$

$$V_{EB0} = 0.5384 \Rightarrow V_I = 5 - 0.5384$$

$$\Rightarrow V_I = 4.462 \text{ V}$$

$$\text{d. } A_v = \frac{-(1/V_T)}{(1/V_{AN}) + (1/V_{AP})}$$

$$A_v = \frac{-\frac{1}{0.026}}{\frac{1}{120} + \frac{1}{80}} = \frac{-38.46}{0.00833 + 0.0125}$$

$$A_v = -1846$$

10.57

Ignore  $(W/L)_3 = 5$  specification

a.  $M_1$  and  $M_2$  matched, so we must have

$$V_{SD2} = V_{SG} = V_{SG3} = V_{DS0} = 2.5 \text{ V}$$

For  $M_1$  and  $M_3$ :

$$I_{REF} = \left(\frac{1}{2} \mu_p C_{ox}\right) \left(\frac{W}{L}\right)_1 (V_{SG} + V_{TP})^2 (1 + \lambda_p V_{SD})$$

$$100 = 10 \left(\frac{W}{L}\right)_1 (2.5 - 1)^2 [1 + (0.02)(2.5)]$$

$$\Rightarrow \left(\frac{W}{L}\right)_1 = 4.23 = \left(\frac{W}{L}\right)_3 = \left(\frac{W}{L}\right)_2$$

For  $M_0$ :

$$I_0 = \left(\frac{1}{2} \mu_n C_{ox}\right) \left(\frac{W}{L}\right)_0 (V_{GS} - V_{TN})^2 (1 + \lambda_n V_{DS})$$

$$100 = 20 \left(\frac{W}{L}\right)_0 (2 - 1)^2 [1 + (0.02)(2.5)]$$

$$\Rightarrow \left(\frac{W}{L}\right)_0 = 4.76$$

$$\text{b. } r_{on} = r_{op} = \frac{1}{\lambda I_0} = \frac{1}{(0.02)(0.1)} = 500 \text{ k}\Omega$$

$$g_m = 2\sqrt{K_n I_0} = 2\sqrt{\left(\frac{1}{2}\mu_n C_{ox}\right)\left(\frac{W}{L}\right) I_0}$$

$$= 2\sqrt{(0.02)(4.76)(0.1)}$$

$$g_m = 0.195 \text{ mA/V}$$

$$A_v = -g_m(r_{on} \parallel r_{op}) = -(0.195)(500 \parallel 500)$$

$$\Rightarrow A_v = -48.75$$

10.58

$$\text{a. } I_{REF} = K_{p1}(V_{SG} + V_{TP})^2$$

$$100 = 100(V_{SG} - 1)^2 \Rightarrow V_{SG} = 2 \text{ V}$$

$$\text{b. } V_{DS0} = V_{DS2} = 5 \text{ V}$$

From Equation (10.87)

$$100(V_I - 1)^2 = 100[1 + (0.02)(5)]$$

$$\times [1 - (0.02)(2)][1 - (0.02)(5)]$$

$$(V_I - 1)^2 = (1.1)(0.96)(0.90) = 0.9504$$

$$\Rightarrow V_I = 1.975 \text{ V}$$

$$\text{c. } A_v = -g_m(r_{on} \parallel r_{op})$$

$$r_{on} = r_{op} = \frac{1}{\lambda I_{REF}} = \frac{1}{(0.02)(0.1)} = 500 \text{ k}\Omega$$

$$g_m = 2\sqrt{K_n I_{REF}} = 2\sqrt{(0.1)(0.1)} = 0.2 \text{ mA/V}$$

$$A_v = -(0.2)(500 \parallel 500)$$

$$\Rightarrow A_v = -50$$

10.59

- a. Using the results of problem 10.27, we find the resistance looking into the collector of  $Q_2$  to be

$$R_0 = r_{o2} \left[ 1 + \frac{R_E \parallel (\tau_{\pi 2} + R'_0)}{r_{o2}} \right]$$

$$+ g_{m2} \left( \frac{\tau_{\pi 2}}{\tau_{\pi 2} + R'_0} \right) [R_E \parallel (\tau_{\pi 2} + R'_0)]$$

where  $R'_0$  is the resistance from the base of  $Q_2$  toward  $Q_1$ . We found

$$\frac{1}{R'_0} = \frac{1}{R_1} + \frac{\frac{1}{r_{\pi 1}} + g_{m1} + \frac{1}{r_{o1}}}{1 + \left( \frac{1}{r_{\pi 1}} + g_{m1} + \frac{1}{r_{o1}} \right) (R_E)}$$

$$\text{b. } A_v = -g_{m0}(r_{o0} \parallel R_L \parallel R_0)$$

10.60

Output resistance of Wilson source

$$R_0 \approx \frac{\beta r_{o3}}{2}$$

Then

$$A_v = -g_m(r_0 \parallel R_0)$$

$$r_{o3} = \frac{V_{AP}}{I_{REF}} = \frac{80}{0.2} = 400 \text{ k}\Omega$$

$$r_0 = \frac{V_{AN}}{I_{REF}} = \frac{120}{0.2} = 600 \text{ k}\Omega$$

$$g_m = \frac{I_{REF}}{V_T} = \frac{0.2}{0.026} = 7.69 \text{ mA/V}$$

$$A_v = -7.69 \left[ 600 \parallel \left( \frac{(80)(400)}{2} \right) \right] = -7.69[600 \parallel 16,000]$$

$$\Rightarrow A_v = -4447$$

10.61

$$\text{a. } g_m(M_v) = 2\sqrt{K_n I_{REF}}$$

$$g_m(M_0) = 2\sqrt{(0.25)(0.2)}$$

$$\Rightarrow g_m(M_0) = 0.447 \text{ mA/V}$$

$$r_{on} = \frac{1}{\lambda_n I_{REF}} = \frac{1}{(0.02)(0.2)} \Rightarrow r_{on} = 250 \text{ k}\Omega$$


$$r_{op} = \frac{1}{\lambda_p I_{REF}} = \frac{1}{(0.03)(0.2)} \Rightarrow r_{op} = 167 \text{ k}\Omega$$

$$\text{b. } A_v = -g_m(r_{on} \parallel r_{op}) = -(0.447)(250 \parallel 167)$$


$$\Rightarrow A_v = -44.8$$

$$\text{c. } R_L = 250 \parallel 167 = r_{on} \parallel r_{op} \text{ or } R_L = 100 \text{ k}\Omega$$

10.62

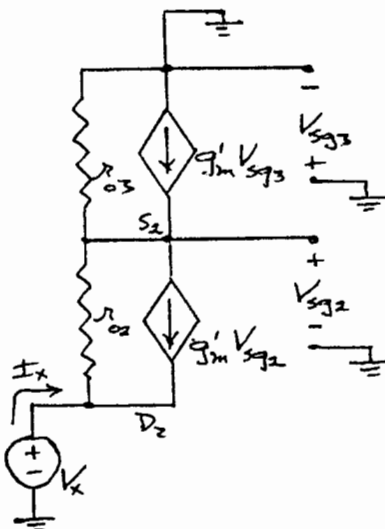

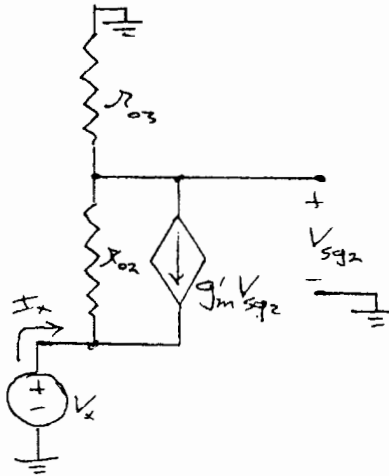Since  $V_{sg3} = 0$ , the circuit becomes



10.63

$$A_v = -g_{m1}(R_{o2} \parallel R_{o3})$$

From the results of JFETs:

$$R_{o2} = r_{o1} + r_{o2}(1 + g_m' r_{o1})$$

From results of Problem 10.62

$$R_{o3} = r_{o3} + r_{o4}(1 + g_m' r_{o3})$$

We find

$$g_{m1} = 2\sqrt{(0.05)(20)(0.08)} = 0.566 \text{ mA/V}$$

$$r_{o1} = r_{o2} = \frac{1}{\lambda_n I_{DQ}} = \frac{1}{(0.02)(0.08)} = 625 \text{ k}\Omega$$

$$r_{o3} = r_{o4} = \frac{1}{\lambda_p I_{DQ}} = \frac{1}{(0.02)(0.08)} = 625 \text{ k}\Omega$$

$$g_m' = 2\sqrt{(0.02)(40)(0.08)} = 0.506 \text{ mA/V}$$

Then

$$R_{o2} = 625 + 625[1 + (0.506)(625)] \Rightarrow 199 \text{ M}\Omega$$

$$R_{o3} = 625 + 625[1 + (0.506)(625)] \Rightarrow 199 \text{ M}\Omega$$

Then

$$A_v = -(0.566)[199000 \parallel 199000] \Rightarrow \underline{A_v = -56,317}$$

$$I_x = -g_m' V_{sg2} + \frac{V_x - V_{sg2}}{r_{o2}} \text{ and } V_{sg2} = I_x r_{o3}$$

Then

$$I_x \left( 1 + g_m' r_{o3} + \frac{r_{o3}}{r_{o2}} \right) = \frac{V_x}{r_{o2}}$$

so that

$$\frac{V_x}{I_x} = R_o = r_{o2} \left( 1 + g_m' r_{o3} + \frac{r_{o3}}{r_{o2}} \right)$$

or

$$R_o = r_{o2} + r_{o3}(1 + g_m' r_{o2})$$

$$A_v = \frac{v_o}{v_i} = -g_{m1}(r_{o1} \parallel R_o)$$

Now

$$g_{m1} = 2\sqrt{(0.050)(20)(0.10)} = 0.632 \text{ mA/V}$$

$$r_{o1} = \frac{1}{\lambda_n I_{DQ}} = \frac{1}{(0.02)(0.10)} = 500 \text{ k}\Omega$$

$$g_m' = 2\sqrt{K_p I_{DQ}} = 2\sqrt{(0.020)(80)(0.1)} = 0.80 \text{ mA/V}$$

$$r_{o2} = r_{o3} = \frac{1}{\lambda_p I_{DQ}} = \frac{1}{(0.020)(0.1)} = 500 \text{ k}\Omega$$

Then

$$R_o = 500 + 500[1 + (0.8)(500)] \Rightarrow 201 \text{ M}\Omega$$

$$A_v = -(0.632)(500 \parallel 201000) \Rightarrow \underline{A_v = -315}$$

## Chapter 11

## Exercise Solutions

E11.1

$$\begin{aligned} V_d &= V_1 - V_2 \\ &= 2 + 0.005 \sin \omega t - (0.5 - 0.005 \sin \omega t) \\ \Rightarrow V_d &= 1.5 + 0.010 \sin \omega t \text{ (V)} \\ V_{cm} &= \frac{V_1 + V_2}{2} \\ &= \frac{2 + 0.005 \sin \omega t + 0.5 - 0.005 \sin \omega t}{2} \\ \Rightarrow V_{cm} &= 1.25 \text{ V} \end{aligned}$$

E11.2

$$\begin{aligned} v_E &= -V_{BE(\text{on})} \Rightarrow \underline{v_E = -0.7 \text{ V}} \\ I_{C1} &= I_{C2} = 0.5 \text{ mA} \\ v_{C1} &= v_{C2} = 10 - (0.5)(10) \\ \Rightarrow \underline{v_{C1} = v_{C2} = 5 \text{ V}} \end{aligned}$$

E11.3

$$\begin{aligned} \text{For } v_1 &= v_2 = +4 \text{ V} \\ \Rightarrow \text{Minimum } v_{C1} &= v_{C2} = 4 \text{ V} \\ I_{C1} &= I_{C2} = \frac{I_Q}{2} = 1 \text{ mA} \\ R_C &= \frac{10 - 4}{1} \Rightarrow \underline{R_C = 6 \text{ k}\Omega} \end{aligned}$$

E11.4

$$\begin{aligned} \frac{i_{C2}}{I_Q} &= \frac{1}{1 + \exp\left(\frac{v_d}{V_T}\right)} = 0.99 \\ 1 + \exp\left(\frac{v_d}{V_T}\right) &= \frac{1}{0.99} \\ \exp\left(\frac{v_d}{V_T}\right) &= \frac{1}{0.99} - 1 \\ v_d &= V_T \ln\left[\frac{1}{0.99} - 1\right] \\ \Rightarrow \underline{v_d = -119.5 \text{ mV}} \end{aligned}$$

E11.6

$$\begin{aligned} \text{a. } v_1 &= v_2 = 0 \Rightarrow \underline{v_E = 0.7 \text{ V}} \\ \Delta V_{RC} &= (0.25)(8) = 2 \text{ V} \\ \Rightarrow v_{C1} &= v_{C2} = -3 \text{ V} \\ \Rightarrow \underline{v_{EC1} = 3.7 \text{ V}} \end{aligned}$$

$$\begin{aligned} \text{b. } v_1 &= v_2 = 2.5 \text{ V} \Rightarrow \underline{v_E = 3.2 \text{ V}} \\ \Rightarrow \underline{v_{EC1} = 6.2 \text{ V}} \end{aligned}$$

$$\begin{aligned} \text{c. } v_1 &= v_2 = -2.5 \text{ V} \Rightarrow \underline{v_E = -1.8 \text{ V}} \\ \Rightarrow \underline{v_{EC1} = 1.2 \text{ V}} \end{aligned}$$

E11.7

$$\text{Let } I_Q = 1 \text{ mA, then } I_{CQ1} = I_{CQ2} = 0.5 \text{ mA}$$

$$g_{m1} = g_{m2} = \frac{0.5}{0.026} = 19.23 \text{ mA/V}$$

At  $v_{C2}$ ,

$$A_d = \frac{v_{c2}}{v_d} = \frac{1}{2} g_m R_{C2}$$

$$\text{So, } 150 = \frac{1}{2} (19.23) R_{C2} \Rightarrow \underline{R_{C2} = 15.6 \text{ k}\Omega}$$

At  $v_{C1}$ ,

$$A_d = \frac{v_{c1}}{v_d} = -\frac{1}{2} g_m R_{C1}$$

$$\text{So, } -100 = -\frac{1}{2} (19.23) R_{C1} \Rightarrow \underline{R_{C1} = 10.4 \text{ k}\Omega}$$

If  $V^+ = +10 \text{ V}$  and  $V^- = -10 \text{ V}$ , dc biasing is OK.

E11.8

$$\text{a. Diff. Gain } A_d = \frac{I_Q R_C}{4V_T}$$

For  $v_1 = v_2 = 5 \text{ V} \Rightarrow$  Minimum collector voltage  $v_{C2} = 5 \text{ V}$ 

$$\Rightarrow \frac{I_Q}{2} \cdot R_C = 15 - 5 = 10 \text{ V}$$

or  $\underline{I_Q R_C = 20 \text{ V}}$  for max.  $A_d$ 

Then

$$A_d = \frac{20}{2(0.026)} \Rightarrow \underline{A_d(\text{max}) = 192}$$

b. If  $I_Q = 0.5 \text{ mA}$ ,  $R_C = 40 \text{ k}\Omega$ 

$$A_{cm} = \frac{-\left(\frac{I_Q R_C}{2V_T}\right)}{\left[1 + \frac{(1 + \beta)I_Q R_O}{V_T \beta}\right]}$$

$$\text{Then } A_{cm} = \frac{-\left(\frac{20}{2(0.026)}\right)}{\left[1 + \frac{(201)(0.5)(100)}{(0.026)(200)}\right]}$$

$$\Rightarrow \underline{A_{cm} = -0.199}$$

$$\text{and } CMRR_{dB} = 20 \log_{10} \left(\frac{192}{0.199}\right)$$

$$\Rightarrow \underline{CMRR_{dB} = 59.7 \text{ dB}}$$

E11.9

For  $v_1 = v_2 = 5 \text{ V} \Rightarrow \min v_{C1} = v_{C2} = 5 \text{ V}$

So  $I_{C1}R_C = 10 - 5 = 0.25R_C \Rightarrow R_C = 20 \text{ k}\Omega$

$$A_d = \frac{I_Q R_C}{4V_T} = \frac{(0.5)(20)}{4(0.026)} \Rightarrow A_d = 96.2 \quad \text{Let } I_Q = 0.5 \text{ mA}$$

$CMRR_{dB} = 95 \text{ dB} \Rightarrow CMRR = 5.62 \times 10^4$

$$\Rightarrow A_{cm} = \frac{96.2}{5.62 \times 10^4} \Rightarrow |A_{cm}| = 1.71 \times 10^{-3}$$

$$|A_{cm}| = \frac{\left(\frac{I_Q R_C}{2V_T}\right)}{\left[1 + \frac{(1 + \beta)I_Q R_0}{V_T \beta}\right]} = 1.71 \times 10^{-3}$$

$$\frac{\left[\frac{(0.5)(20)}{2(0.026)}\right]}{\left[1 + \frac{(201)(0.5)R_0}{(0.026)(200)}\right]} = 1.71 \times 10^{-3}$$

$$1 + 19.3R_0 = 1.12 \times 10^5 \Rightarrow R_0 = 5.83 \times 10^3 \text{ k}\Omega = 5.83 \text{ M}\Omega$$

We have  $R_0 = r_{o4}[1 + g_{m2}(R_2 || r_{\pi 2})]$

$$r_{o4} = \frac{V_A}{I_Q} = \frac{125}{0.5} = 250 \text{ k}\Omega$$

$$g_{m2} = \frac{I_Q}{V_T} = \frac{0.5}{0.026} = 19.2 \text{ mA/V}$$

$$r_{\pi 2} = \frac{\beta V_T}{I_Q} = \frac{(200)(0.026)}{0.5} = 10.4 \text{ k}\Omega$$

$$5830 = 250[1 + g_{m2}(R_2 || r_{\pi 2})]$$

$$19.2(R_2 || r_{\pi 2}) = 22.3$$

$$(R_2 || r_{\pi 2}) = 1.16 \text{ k}\Omega$$

$$\frac{R_2(10.4)}{R_2 + 10.4} = 1.16$$

$$R_2(10.4 - 1.16) = (1.16)(10.4)$$

$$\Rightarrow R_2 = 1.31 \text{ k}\Omega$$

$$I_Q R_2 - I_1 R_3 = V_T \ln\left(\frac{I_1}{I_Q}\right) \quad \text{Let } I_1 = 1 \text{ mA}$$

$$(0.5)(1.31) - (1)R_3 = (0.026) \ln\left(\frac{1}{0.5}\right)$$

$$\Rightarrow R_3 = 0.637 \text{ k}\Omega$$

If  $V_{BE}(Q_3) \approx 0.7 \text{ V}$

$$R_1 + R_3 = \frac{10 - 0.7 - (-10)}{1} = 19.3$$

$$\Rightarrow R_1 \approx 18.7 \text{ k}\Omega$$

E11.10

a.  $v_o = A_d v_d + A_{cm} v_{cm}$

$$v_d = v_1 - v_2 = 0.505 \sin \omega t - 0.495 \sin \omega t = 0.01 \sin \omega t$$

$$v_{cm} = \frac{v_1 + v_2}{2} = \frac{0.505 \sin \omega t + 0.495 \sin \omega t}{2} = 0.50 \sin \omega t$$

$$v_o = (60)(0.01 \sin \omega t) + (0.5)(0.5 \sin \omega t)$$

$$\Rightarrow v_o = 0.85 \sin \omega t \text{ (V)}$$

b.

$$v_d = v_1 - v_2$$

$$= 0.5 + 0.005 \sin \omega t - (0.5 - 0.005 \sin \omega t)$$

$$= 0.01 \sin \omega t$$

$$v_{cm} = \frac{v_1 + v_2}{2}$$

$$= \frac{0.5 + 0.005 \sin \omega t + 0.5 - 0.005 \sin \omega t}{2}$$

$$= 0.5$$

$$v_o = (60)(0.01 \sin \omega t) + (0.5)(0.5)$$

$$\Rightarrow v_o = 0.25 + 0.6 \sin \omega t \text{ (V)}$$

E11.11

a.  $I_{B1} = I_{B2} = \frac{I_Q/2}{(1 + \beta)} = \frac{1}{151}$

$$\Rightarrow I_{B1} = I_{B2} = 6.62 \text{ }\mu\text{A}$$

b.  $r_{\pi} = \frac{\beta V_T}{I_{CQ}} = \frac{(150)(0.026)}{1} = 3.9 \text{ k}\Omega$

$$R_{1,d} = 2r_{\pi} = 2(3.9) = 7.8 \text{ k}\Omega$$

$$I_b = \frac{V_d}{R_{1,d}} = \frac{10 \sin \omega t \text{ (mV)}}{7.8 \text{ k}\Omega}$$

$$\Rightarrow I_b = 1.28 \sin \omega t \text{ (}\mu\text{A)}$$

c.  $R_{1,cm} \approx 2(1 + \beta)R_0 = 2(151)(50) \Rightarrow 15.1 \text{ M}\Omega$

$$I_b = \frac{V_{cm}}{R_{1,cm}} = \frac{3 \sin \omega t}{15.1 \text{ M}\Omega} \Rightarrow I_b = 0.199 \sin \omega t \text{ (}\mu\text{A)}$$

E11.12

$$\frac{i_{D1}}{I_Q} = \frac{1}{2} + \sqrt{\frac{K_n}{2I_Q}} \cdot v_d \sqrt{1 - \left(\frac{K_n}{2I_Q}\right) v_d^2}$$

Using the parameters in Example 11.11,

$K_n = 0.5 \text{ mA/V}^2$ ,  $I_Q = 1 \text{ mA}$ , then

$$\frac{i_{D1}}{I_Q} = 0.90 = \frac{1}{2} + \sqrt{\frac{0.5}{2(1)}} \cdot v_d \sqrt{1 - \left(\frac{0.5}{2(1)}\right) v_d^2}$$

By trial and error,  
 $v_d = 0.894 \text{ V}$

E11.13

$$I_1 = \frac{10 - V_{GS4}}{R_1} = K_{n3}(V_{GS4} - V_{TN})^2$$

$$10 - V_{GS4} = (0.1)(80)(V_{GS4} - 0.8)^2$$

$$10 - V_{GS4} = 8(V_{GS4}^2 - 1.6V_{GS4} + 0.64)$$

$$8V_{GS4}^2 - 11.8V_{GS4} - 4.88 = 0$$

$$V_{GS4} = \frac{11.8 \pm \sqrt{(11.8)^2 + 4(8)(4.88)}}{2(8)} = 1.81 \text{ V}$$

$$I_1 = I_Q = \frac{10 - 1.81}{80} = 0.102 \text{ mA}$$

$$I_{D1} = I_{D2} = \frac{0.102}{2} = 0.051 \text{ mA}$$

$$= K_n(V_{GS1} - V_{TN})^2$$

$$0.051 = 0.050(V_{GS1} - 0.8)^2 \Rightarrow V_{GS1} = 1.81 \text{ V}$$

$$v_{o1} = v_{o2} = 5 - (0.051)(40) = 2.96 \text{ V}$$

Max  $v_{cm}$ :  $V_{DS1}(sat) = V_{GS1} - V_{TN}$

$$= 1.81 - 0.8 = 1.01 \text{ V}$$

$$v_{cm}(\max) = v_{o1} - V_{DS1}(sat) + V_{GS1}$$

$$= 2.96 - 1.01 + 1.81$$

$$v_{cm}(\max) = 3.76 \text{ V}$$

Min  $v_{cm}$ :  $V_{DS4}(sat) = V_{GS4} - V_{TN}$

$$= 1.81 - 0.8 = 1.01 \text{ V}$$

$$v_{cm}(\min) = V_{GS1} + V_{DS4}(sat) - 5$$

$$= 1.81 + 1.01 - 5$$

$$v_{cm}(\min) = -2.18 \text{ V}$$

$$\underline{-2.18 < v_{cm} < 3.76 \text{ V}}$$

E11.14

$$g_f(\max) = \sqrt{\frac{K_n I_Q}{2}} = \sqrt{\frac{(1)(2)}{(2)}} \Rightarrow$$

$$g_f(\max) = 1 \text{ mA/V}$$

$$A_d = g_f R_D = (1)(5) \Rightarrow \underline{A_d = 5}$$

E11.15

$$A_d = g_f R_D$$

$$8 = g_f(4) \Rightarrow g_f(\max) = 2 \text{ mA/V}$$

$$g_f(\max) = \sqrt{\frac{K_n I_Q}{2}}$$

$$(2)^2 = K_n \left(\frac{4}{2}\right) \Rightarrow \underline{K_n = 2 \text{ mA/V}^2}$$

E11.16

From Example 11-10,  $I_Q = 0.588 \text{ mA}$

$$A_d = \sqrt{\frac{K_n I_Q}{2}} \cdot R_D = \sqrt{\frac{(0.1)(0.588)}{2}} \cdot (16)$$

$$\Rightarrow \underline{A_d = 2.74}$$

For  $M_A$ ,  $R_o = \frac{1}{\lambda_4 I_Q} = \frac{1}{(0.02)(0.588)} \Rightarrow R_o = 85 \text{ k}\Omega$

$$g_m = 2K_n(V_{GS2} - V_{TN}) = 2(0.1)(2.71 - 1)$$

$$= 0.342 \text{ mA/V}$$

$$A_{cm} = \frac{-g_m R_D}{1 + 2g_m R_o} = \frac{-(0.342)(16)}{1 + 2(0.342)(85)}$$

$$\Rightarrow \underline{A_{cm} = -0.0925}$$

$$CMRR_{dB} = 20 \log_{10} \left( \frac{2.74}{0.0925} \right)$$

$$\Rightarrow \underline{CMRR_{dB} = 29.4 \text{ dB}}$$

E11.17

$$CMRR = \frac{1}{2} [1 + 2\sqrt{2K_n I_Q} \cdot R_o]$$

$$CMRR_{dB} = 60 \text{ dB} \Rightarrow CMRR = 1000$$

$$1000 = \frac{1}{2} [1 + 2\sqrt{2(0.1)(0.2)} \cdot R_o]$$

$$2000 = 1 + 0.4R_o$$

$$\Rightarrow \underline{R_o \approx 5 \text{ M}\Omega}$$

E11.18

$$R_o = r_{o4} + r_{o2}(1 + g_{m4} r_{o4})$$

Assume  $I_{REF} = I_O = 100 \mu\text{A}$  and  $\lambda = 0.01 \text{ V}^{-1}$

$$r_{o2} = r_{o4} = \frac{1}{\lambda I_D} = \frac{1}{(0.01)(0.1)} \Rightarrow 1 \text{ M}\Omega$$

Let  $K_n$  (all devices) =  $0.1 \text{ mA/V}^2$

Then

$$g_{m4} = 2\sqrt{K_n I_D} = 2\sqrt{(0.1)(0.1)} = 0.2 \text{ mA/V}$$

$$R_o = 1000 + 1000(1 + (0.2)(1000)) \Rightarrow 202 \text{ M}\Omega$$

Now

$$V_{GS1} = V_{GS2} = \sqrt{\frac{I_D}{K_n}} + V_{TN} = \sqrt{\frac{0.05}{0.1}} + 1 = 1.71 \text{ V}$$

$$V_{DS1}(sat) = V_{GS1} - V_{TN} = 1.71 - 1 = 0.71 \text{ V}$$

So

$$v_{o1}(\min) = +4 - V_{GS1} + V_{DS1}(sat) = 4 - 1.71 + 0.71$$

$$v_{o1}(\min) = 3 \text{ V} = 10 - I_D R_D = 10 - (0.05)R_D \Rightarrow$$

$$\underline{R_D = 140 \text{ k}\Omega}$$

For a one-sided output, the differential gain is:

$$A_d = \frac{1}{2} g_{m1} R_D \text{ where } g_{m1} = 2\sqrt{K_n I_D}$$

$$= 2\sqrt{(0.1)(0.05)} = 0.141 \text{ mA/V}$$

$$A_d = \frac{1}{2} (0.141)(140) \Rightarrow \underline{A_d = 9.87}$$

The common-mode gain is:

$$A_{cm} = \frac{\sqrt{2K_n I_Q} \cdot R_D}{1 + 2\sqrt{2K_n I_Q} \cdot R_o} = \frac{\sqrt{2(0.1)(0.1)} \cdot (140)}{1 + 2\sqrt{2(0.1)(0.1)} \cdot (202000)}$$

$$\Rightarrow \underline{A_{cm} = 0.000347}$$

Then

$$CMRR_{dB} = 20 \log_{10} \left| \frac{A_d}{A_{cm}} \right| \Rightarrow \underline{CMRR_{dB} = 89.1 \text{ dB}}$$

E11.19

$$a. \quad I_{B5} = \frac{I_Q}{\beta(1+\beta)} = \frac{0.5}{(180)(181)} \Rightarrow 15.3 \text{ nA}$$

$$\text{So } I_0 = 15.3 \text{ nA}$$

b. For a balanced condition

$$V_{EC4} = V_{EC3} = V_{EB3} \Rightarrow V_{EC4} = 0.7 \text{ V}$$

$$V_{CE2} = V_{C2} - V_{E2} = (10 - 0.7) - (-0.7)$$

$$\Rightarrow V_{CE2} = 10 \text{ V}$$

$$r_{o2} = \frac{V_{A2}}{I_{C2}} = \frac{125}{0.05} \Rightarrow 2.5 \text{ M}\Omega$$

$$r_{o4} = \frac{V_{A4}}{I_{C4}} = \frac{85}{0.05} \Rightarrow 1.7 \text{ M}\Omega$$

$$g_m = \frac{0.05}{0.026} = 1.923 \text{ mA/V}$$

$$A_d = g_m(r_{o2} \parallel r_{o4} \parallel R_L) = (1.923)(2500 \parallel 1700 \parallel 90) \Rightarrow$$

$$A_d = 159$$

E11.20

$$a. \quad g_f = \frac{I_Q}{4V_T} = \frac{0.5}{4(0.026)} = 4.81 \text{ mA/V}$$

$$r_{o2} = \frac{V_{A2}}{I_{C2}} = \frac{125}{0.25} = 500 \text{ k}\Omega$$

$$r_{o4} = \frac{V_{A4}}{I_{C4}} = \frac{85}{0.25} = 340 \text{ k}\Omega$$

$$A_d = 2g_f(r_{o2} \parallel r_{o4}) = 2(4.81)(500 \parallel 340)$$

$$\Rightarrow A_d = 1947$$

$$b. \quad A_d = 2g_f(r_{o2} \parallel r_{o4} \parallel R_L)$$

$$A_d = 2(4.81)(500 \parallel 340 \parallel 100)$$

$$\Rightarrow A_d = 644$$

$$c. \quad r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{(150)(0.026)}{0.25} = 15.6 \text{ k}\Omega$$

$$R_{i,d} = 2r_\pi \Rightarrow R_{i,d} = 31.2 \text{ k}\Omega$$

$$d. \quad R_o = r_{o2} \parallel r_{o4} = 500 \parallel 340 \Rightarrow R_o = 202 \text{ k}\Omega$$

E11.21

$$A_d = 2g_f(r_{o2} \parallel r_{o4})$$

$$g_f = \frac{I_Q}{4V_T} = \frac{0.2}{4(0.026)} = 1.92 \text{ mA/V}$$

$$r_{o2} = \frac{V_{A2}}{I_{C2}} = \frac{120}{0.1} = 1200 \text{ k}\Omega$$

$$r_{o4} = \frac{V_{A4}}{I_{C4}} = \frac{80}{0.1} = 800 \text{ k}\Omega$$

$$A_d = 2(1.92)(1200 \parallel 800) \Rightarrow A_d = 1843$$

E11.22

$$P = (I_Q + I_{REF})(5 - (-5))$$

$$10 = (0.1 + I_{REF})(10) \Rightarrow I_{REF} = 0.9 \text{ mA}$$

$$R_1 = \frac{5 - 0.7 - (-5)}{I_{REF}} = \frac{9.3}{0.9} \Rightarrow R_1 = 10.3 \text{ k}\Omega$$

$$I_Q R_E = V_T \ln\left(\frac{I_{REF}}{I_Q}\right)$$

$$R_E = \frac{0.026}{0.1} \ln\left(\frac{0.9}{0.1}\right) \Rightarrow R_E = 0.571 \text{ k}\Omega$$

E11.23

$$a. \quad R_o = r_{o2} \parallel r_{o4}$$

$$r_{o2} = \frac{120}{0.1} = 1.2 \text{ M}\Omega$$

$$r_{o4} = \frac{80}{0.1} = 0.8 \text{ M}\Omega$$

$$R_o = 1.2 \parallel 0.8 \Rightarrow R_o = 0.48 \text{ M}\Omega$$

$$b. \quad A_d(\text{open circuit}) = 2g_f(r_{o2} \parallel r_{o4})$$

$$A_d(\text{with load}) = 2g_f(r_{o2} \parallel r_{o4} \parallel R_L)$$

$$\text{For } A_d(\text{with load}) = \frac{1}{2} A_d(\text{open circuit})$$

$$\Rightarrow R_L = (r_{o2} \parallel r_{o4}) \Rightarrow R_L = 0.48 \text{ M}\Omega$$

E11.24

$$A_d = 2 \sqrt{\frac{2K_n}{I_Q}} \cdot \frac{1}{(\lambda_2 + \lambda_4)}$$

$$= 2 \sqrt{\frac{2(0.1)}{0.1}} \cdot \frac{1}{(0.01 + 0.015)} \Rightarrow$$

$$A_d = 113$$

E11.25

 For the MOSFET,  $I_D = 25 \mu\text{A}$ 

$$25 = 20(V_{GS} - 1)^2 \Rightarrow V_{GS} = 2.12 \text{ V}$$

$$g_{m1} = 2K_{n1}(V_{GS} - V_{TN}) = 2(20)(2.12 - 1)$$

$$\Rightarrow g_{m1} = 44.8 \mu\text{A/V}, \quad r_{o1} = \infty$$

 For the Bipolar,  $I_Q = 100 - 25 = 75 \mu\text{A}$ 

$$r_{\pi 2} = \frac{\beta V_T}{I_{CQ}} = \frac{(100)(0.026)}{0.075} \Rightarrow r_{\pi 2} = 34.7 \text{ k}\Omega$$

$$g_{m2} = \frac{I_{CQ}}{V_T} = \frac{75}{0.026}$$

$$\Rightarrow g_{m2} = 2.88 \text{ mA/V}, \quad r_{o2} = \infty$$

$$g_m^C = \frac{g_{m1}(1 + g_{m2}r_\pi)}{(1 + g_{m1}r_\pi)}$$

$$= \frac{(44.8)[1 + (2.88)(34.7)]}{1 + (0.0448)(34.7)}$$

$$= \frac{(44.8)(100.9)}{2.55}$$

$$\Rightarrow g_m^C = 1.77 \text{ mA/V}$$

E11.26

From Figure 11.41

$$r_{o4} = \frac{80}{0.5} = 160 \text{ k}\Omega$$

$$R_o \approx \beta r_{o4} = (150)(160) \text{ k}\Omega \Rightarrow \underline{R_o = 24 \text{ M}\Omega}$$

From Figure 11.42

$$r_{o6} = \frac{1}{\lambda I_D} = \frac{1}{(0.0125)(0.5)} \Rightarrow \underline{r_{o6} = 160 \text{ k}\Omega}$$

$$0.5 = 0.5(V_{GS} - 1)^2 \Rightarrow V_{GS} = 2 \text{ V}$$

$$g_{m6} = 2K_n(V_{GS} - V_{TN}) = 2(0.5)(2 - 1) = 1 \text{ mA/V}$$

$$r_{o4} = 160 \text{ k}\Omega$$

$$R_o = (g_{m6})(r_{o6})(\beta r_{o4}) = (1)(160)(150)(160)$$

$$\Rightarrow \underline{R_o = 3.840 \text{ M}\Omega}$$

E11.27

From Equation (11.103)

$$R_i = \frac{2(1 + \beta)\beta V_T}{I_Q} = \frac{2(121)(120)(0.026)}{0.5}$$

$$\Rightarrow \underline{R_i = 1.51 \text{ M}\Omega}$$

$$r_{\pi 11} = \frac{\beta V_T}{I_Q} = \frac{(120)(0.026)}{0.5} = 6.24 \text{ k}\Omega$$

$$R'_E = r_{\pi 11} \parallel R_3 = 6.24 \parallel 0.1 = 0.0984 \text{ k}\Omega$$

$$g_{m11} = \frac{I_Q}{V_T} = \frac{0.5}{0.026} = 19.23 \text{ mA/V}$$

$$r_{o11} = \frac{V_A}{I_Q} = \frac{120}{0.5} = 240 \text{ k}\Omega$$

Then

$$R_{C11} = r_{o11} (1 + g_{m11} R'_E)$$

$$= 240[1 + (19.23)(0.0984)]$$

$$= 694 \text{ k}\Omega$$

$$r_{\pi 8} = \frac{\beta V_T}{I_{C8}} = \frac{(120)(0.026)}{2} = 1.56 \text{ k}\Omega$$

$$R_{b8} = r_{\pi 8} + (1 + \beta)R_4 = 1.56 + (121)(5) = 607 \text{ k}\Omega$$

Then

$$R_{L7} = R_{C11} \parallel R_{b8} = 694 \parallel 607 = 324 \text{ k}\Omega$$

Then

$$A_v = \left( \frac{I_Q}{2V_T} \right) R_{L7} = \left[ \frac{0.5}{2(0.026)} \right] (324)$$

$$\Rightarrow \underline{A_v = 3115}$$

$$R_o = R_4 \parallel \left( \frac{r_{\pi 8} + Z}{1 + \beta} \right)$$

$$Z = R_{C11} \parallel R_{C7}$$

$$R_{C7} = \frac{V_A}{I_Q} = \frac{120}{0.5} = 240 \text{ k}\Omega$$

$$Z = 694 \parallel 240 = 178 \text{ k}\Omega$$

$$R_o = 5 \parallel \left( \frac{1.56 + 178}{121} \right) = 5 \parallel 1.48$$

$$\Rightarrow \underline{R_o = 1.14 \text{ k}\Omega}$$

E11.28

$$A_v = \left( \frac{I_Q}{2V_T} \right) R_{L7}$$

$$10^3 = \left( \frac{0.5}{2(0.026)} \right) R_{L7}$$

$$\Rightarrow \underline{R_{L7} = 104 \text{ k}\Omega}$$

E11.29

$$a. \quad R_1 = \frac{10 - 0.7 - (-10)}{I_1} = \frac{19.3}{0.6} \Rightarrow \underline{R_1 = 32.2 \text{ k}\Omega}$$

$$I_{C1} = I_{C2} = 0.1 \text{ mA} \Rightarrow I_Q \approx 0.2 \text{ mA}$$

$$R_2 = \frac{V_T}{I_Q} \cdot \ln\left(\frac{I_1}{I_Q}\right) = \frac{0.026}{0.2} \cdot \ln\left(\frac{0.6}{0.2}\right)$$

$$\Rightarrow \underline{R_2 = 143 \Omega}$$

$$I_{R6} = I_1 = 0.6 \text{ mA} \Rightarrow \underline{R_3 = 0}$$

$$V_{O2} = V_{CE2} + V_E = 4 - 0.7 = 3.3 \text{ V}$$

$$R_C = \frac{10 - 3.3}{I_{C2}} = \frac{6.7}{0.1} \Rightarrow \underline{R_C = 67 \text{ k}\Omega}$$

$$V_{E4} = V_{O2} - 2V_{BE} = 3.3 - 2(0.7) = 1.9 \text{ V}$$

$$R_4 = \frac{1.9}{I_{R4}} = \frac{1.9}{0.6} \Rightarrow \underline{R_4 = 3.17 \text{ k}\Omega}$$

$$V_{O3} = V_{CE4} + V_{E4} = 3 + 1.9 = 4.9$$

$$R_5 = \frac{10 - 4.9}{I_{R4}} = \frac{5.1}{0.6} \Rightarrow \underline{R_5 = 8.5 \text{ k}\Omega}$$

$$V_{E5} = V_{O3} - V_{BE} = 4.9 - 0.7 = 4.2$$

$$R_6 = \frac{4.2 - 0.7}{I_{R6}} = \frac{3.5}{0.6} \Rightarrow \underline{R_6 = 5.83 \text{ k}\Omega}$$

$$R_7 = \frac{0 - (-10)}{I_{R7}} = \frac{10}{5} \Rightarrow \underline{R_7 = 2 \text{ k}\Omega}$$

$$b. \quad R_{i2} = r_{\pi 3} + (1 + \beta)r_{\pi 4}$$

$$r_{\pi 4} = \frac{\beta V_T}{I_{R4}} = \frac{(100)(0.026)}{0.6} = 4.33 \text{ k}\Omega$$

$$r_{\pi 3} \approx \frac{\beta^2 V_T}{I_{R4}} = \frac{(100)^2(0.026)}{0.6} = 433 \text{ k}\Omega$$

$$R_{i2} = 433 + (101)(4.33) \Rightarrow \underline{R_{i2} = 870 \text{ k}\Omega}$$

$$R_{i3} = r_{\pi 5} + (1 + \beta)[R_6 + r_{\pi 6} + (1 + \beta)R_7]$$

$$r_{\pi 5} = \frac{\beta V_T}{I_{R6}} = \frac{(100)(0.026)}{0.6} = 4.33 \text{ k}\Omega$$

$$r_{\pi 6} = \frac{\beta V_T}{I_{R7}} = \frac{(100)(0.026)}{5} = 0.52 \text{ k}\Omega$$

$$R_{i3} = 4.33 + (101)[5.83 + 0.52 + (101)(2)]$$

$$\Rightarrow \underline{R_{i3} = 21.0 \text{ M}\Omega}$$

$$c. \quad A_d = A_{d1} \cdot A_2 \cdot A_3$$

$$A_{d1} = g_f(R_C \parallel R_{i2})$$

$$g_f = \frac{I_Q}{4V_T} = \frac{0.2}{4(0.026)} = 1.92 \text{ mA/V}$$

$$A_{d1} = (1.92)(67 \parallel 870) = 119$$

$$A_2 = \left(\frac{I_{R4}}{2V_T}\right) R_5 = \frac{0.6}{2(0.026)}(8.5) = 98.1$$

$$A_3 \approx 1$$

$$A_d = (119)(98.1)(1)$$

$$\Rightarrow \underline{A_d = 11,674}$$

## Chapter 11

## Problem Solutions

11.1

$$a. \quad I_E = I_{C1} + I_{C2} = 4 \text{ mA} = \frac{-0.7 - (-8.7)}{R_E}$$

$$\text{So } R_E = \frac{8.0}{4} = \underline{2 \text{ k}\Omega = R_E}$$

Then


$$R_C = \frac{16 - V_{O2}}{I_{C2}} = \frac{16 - 8}{2} \Rightarrow \underline{R_C = 4 \text{ k}\Omega}$$

b. Neglecting base currents

$$16 = I_C R_C + V_{CE2} + 2I_C R_E - 8.7$$

$$V_{CE2} = 24.7 - I_C(R_C + 2R_E) = 24.7 - I_C(8)$$
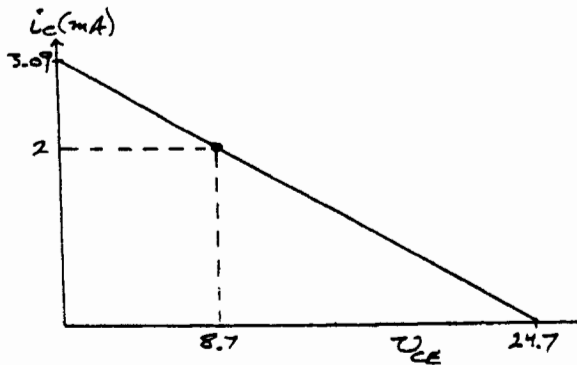
$$\text{For } I_C = 2 \text{ mA, } V_{CEQ} = 8.7 \text{ V}$$



$$c. \quad v_{cm}(\text{max}) \text{ for } V_{CB} = 0 \Rightarrow \underline{v_{cm}(\text{max}) = 8 \text{ V}}$$

$$v_{cm}(\text{min}) \text{ for } Q_1 \text{ and } Q_2 \text{ at edge of cutoff}$$

$$\Rightarrow \underline{v_{cm}(\text{min}) = -8 \text{ V}}$$

11.2

$$P = (I_1 + I_{C4})(V^+ - V^-)$$

$$I_1 \cong I_{C4} \text{ so}$$

$$1.2 = 2I_1(6) \Rightarrow \underline{I_1 = I_{C4} = 0.1 \text{ mA}}$$

$$R_1 = \frac{3 - 0.7 - (-3)}{0.1} \Rightarrow \underline{R_1 = 53 \text{ k}\Omega}$$

$$\text{For } v_{CM} = +1 \text{ V} \Rightarrow V_{C1} = V_{C2} = 1 \text{ V} \Rightarrow$$

$$R_C = \frac{3 - 1}{0.05} \Rightarrow \underline{R_C = 40 \text{ k}\Omega}$$

One-sided output

$$A_d = \frac{1}{2} g_m R_C \text{ where } g_m = \frac{0.05}{0.026} = 1.923 \text{ mA/V}$$

Then

$$A_d = \frac{1}{2} (1.923)(40) \Rightarrow \underline{A_d = 38.5}$$

11.3

$$a. \quad I_1 = \frac{10 - 2(0.7)}{8.5} \Rightarrow \underline{I_1 = 1.01 \text{ mA}}$$

$$I_{C2} = \frac{I_1}{1 + \frac{2}{\beta(1+\beta)}} = \frac{1.01}{1 + \frac{2}{(100)(101)}}$$

$$\Rightarrow \underline{I_{C2} \cong 1.01 \text{ mA}}$$

$$I_{C4} = \left(\frac{100}{101}\right) \left(\frac{1.01}{2}\right) \Rightarrow \underline{I_{C4} \cong 0.50 \text{ mA}}$$

$$V_{CE2} = (0 - 0.7) - (-5) \Rightarrow \underline{V_{CE2} = 4.3 \text{ V}}$$

$$V_{CE4} = [5 - (0.5)(2)] - (-0.7) \Rightarrow \underline{V_{CE4} = 4.7 \text{ V}}$$

$$b. \quad \text{For } V_{CE4} = 2.5 \text{ V} \Rightarrow V_{C4} = -0.7 + 2.5 = 1.8 \text{ V}$$

$$I_{C4} = \frac{5 - 1.8}{2} \Rightarrow \underline{I_{C4} = 1.6 \text{ mA}}$$

$$I_{C2} + \left(\frac{1+\beta}{\beta}\right) (2I_{C4}) = \left(\frac{101}{100}\right) (2)(1.6)$$

$$\Rightarrow \underline{I_{C2} = 3.23 \text{ mA}}$$

$$\underline{I_1 \cong I_{C2} = 3.23 \text{ mA}}$$

$$R_1 = \frac{10 - 2(0.7)}{3.23} \Rightarrow \underline{R_1 = 2.66 \text{ k}\Omega}$$

11.4

$$a. \quad 0 = 0.7 + \frac{I_E}{2}(2) + I_E(85) - 5$$

$$I_E = \frac{5 - 0.7}{85 + 1} \Rightarrow \underline{I_E = 0.050 \text{ mA}}$$

$$I_{C1} = I_{C2} = \left(\frac{\beta}{1+\beta}\right) \left(\frac{I_E}{2}\right) = \left(\frac{100}{101}\right) \left(\frac{0.050}{2}\right)$$

$$\text{Or } \underline{I_{C1} = I_{C2} = 0.0248 \text{ mA}}$$

$$V_{CE1} = V_{CE2} = [5 - I_{C1}(100)] - (-0.7)$$

$$\text{So } \underline{V_{CE1} = V_{CE2} = 3.22 \text{ V}}$$

$$b. \quad v_{cm}(\text{max}) \text{ for } V_{CB} = 0 \text{ and}$$

$$V_C = 5 - I_{C1}(100) = 2.52 \text{ V}$$

$$\text{So } \underline{v_{cm}(\text{max}) = 2.52 \text{ V}}$$

$$v_{cm}(\text{min}) \text{ for } Q_1 \text{ and } Q_2 \text{ at the edge of cutoff}$$

$$\Rightarrow \underline{v_{cm}(\text{min}) = -4.3 \text{ V}}$$

(c) Differential-mode half circuits

$$-\frac{v_d}{2} = V_\pi + \left(\frac{V_\pi}{r_\pi} + g_m V_\pi\right) \cdot R_E$$

$$= V_\pi \left[1 + \frac{(1+\beta) R_E}{r_\pi}\right]$$

Then

$$V_x = \frac{-(v_d/2)}{\left[1 + \frac{(1+\beta)R_B}{r_x}\right]}$$

$$v_o = -g_m V_x R_C \Rightarrow A_d = \frac{1}{2} \frac{\beta R_C}{r_x + (1+\beta)R_B}$$

$$r_x = \frac{\beta V_T}{I_{CQ}} = \frac{(100)(0.026)}{0.0248} = 105 \text{ k}\Omega$$

Then

$$A_d = \frac{1}{2} \frac{(100)(100)}{105 + (101)(2)} \Rightarrow A_d = 16.3$$

11.5

a. i.  $(v_{o1} - v_{o2}) = 0$

ii.  $I_{C1} = I_{C2} = 1 \text{ mA}$

$$\begin{aligned} v_{o1} - v_{o2} &= [V^+ - I_{C1}R_{C1}] - [V^+ - I_{C2}R_{C2}] \\ &= I_C(R_{C2} - R_{C1}) = (1)(7.9 - 8) \\ \Rightarrow v_{o1} - v_{o2} &= -0.1 \text{ V} \end{aligned}$$

b.  $I_0 = (I_{S1} + I_{S2}) \exp\left(\frac{v_{BE}}{V_T}\right)$

$$\begin{aligned} \text{So } \exp\left(\frac{v_{BE}}{V_T}\right) &= \frac{2 \times 10^{-3}}{10^{-13} + 1.1 \times 10^{-13}} \\ &= 9.524 \times 10^9 \end{aligned}$$

$$I_{C1} = I_{S1} \exp\left(\frac{v_{BE}}{V_T}\right) = (10^{-13})(9.524 \times 10^9)$$

$$\Rightarrow I_{C1} = 0.952 \text{ mA}$$

$$I_{C2} = (1.1 \times 10^{-13})(9.524 \times 10^9)$$

$$\Rightarrow I_{C2} = 1.048 \text{ mA}$$

i.  $v_{o1} - v_{o2} = I_{C2}R_{C2} - I_{C1}R_{C1}$

$$\Rightarrow v_{o1} - v_{o2} = (1.048 - 0.952)(8)$$

$$\Rightarrow v_{o1} - v_{o2} = 0.768 \text{ V}$$

ii.  $v_{o1} - v_{o2} = (1.048)(7.9) - (0.952)(8)$

$$v_{o1} - v_{o2} = 8.279 - 7.616$$

$$\Rightarrow v_{o1} - v_{o2} = 0.663 \text{ V}$$

11.6

From Equation (11.12(b))

$$i_{C2} = \frac{I_Q}{1 + e^{v_d/V_T}}$$

$$0.90 = \frac{1}{1 + e^{v_d/V_T}}$$

$$\text{So } e^{v_d/V_T} = \frac{1}{0.90} - 1 = 0.111$$

$$v_d = V_T \ln(0.111) = (0.026) \ln(0.111)$$

$$\Rightarrow v_d = -0.0571 \text{ V}$$

11.7

For  $v_{CM} = 3.5 \text{ V}$  and a maximum peak-to-peak swing in the output voltage of  $2 \text{ V}$ , we need the quiescent collector voltage to be

$$V_C = 3.5 + 1 = 4.5 \text{ V}$$

Assume the bias is  $\pm 10 \text{ V}$ , and  $I_Q = 0.5 \text{ mA}$ .

Then  $I_C = 0.25 \text{ mA}$

$$\text{Now } R_C = \frac{10 - 4.5}{0.25} \Rightarrow R_C = 22 \text{ k}\Omega$$

$$\text{In this case, } r_x = \frac{(100)(0.026)}{0.25} = 10.4 \text{ k}\Omega$$

Then

$$A_d = \frac{(100)(22)}{2(10.4 + 0.5)} = 101 \text{ So gain specification is met.}$$

For  $CMRR_{dB} = 80 \text{ dB} \Rightarrow$

$$\begin{aligned} CMRR &= 10^4 = \frac{1}{2} \left[ 1 + \frac{(1+\beta)I_Q R_o}{V_T \beta} \right] \\ &= \frac{1}{2} \left[ 1 + \frac{(101)(0.5)R_o}{(0.026)(100)} \right] \Rightarrow \end{aligned}$$

$$R_o = 1.03 \text{ M}\Omega$$

Need to use a Modified Widlar current source.

$$R_o = r_o \left[ 1 + g_m (R_{E1} \parallel r_x) \right]$$

$$\text{If } V_A = 100 \text{ V, then } r_o = \frac{100}{0.5} = 200 \text{ k}\Omega$$

$$r_x = \frac{(100)(0.026)}{0.5} = 5.2 \text{ k}\Omega$$

$$g_m = \frac{0.5}{0.026} = 19.23 \text{ mA/V}$$

Then

$$1030 = 200 \left[ 1 + (19.23)(R_{E1} \parallel r_x) \right] \Rightarrow$$

$$R_{E1} \parallel r_x = 0.216 \text{ k}\Omega = R_{E1} \parallel 5.2 \Rightarrow$$

$$R_{E1} = 225 \Omega$$

Also let  $R_{E2} = 225 \Omega$  and  $I_{RBF} \cong 0.5 \text{ mA}$

11.8

a. For  $v_1 = v_2 = 0$  and neglecting base currents

$$R_E = \frac{-0.7 - (-10)}{0.15} \Rightarrow R_E = 62 \text{ k}\Omega$$

b. Using the small-signal equivalent circuit shown in Figure 11.8, but including the  $R_B$  resistors, we have

$$\frac{V_{\pi 1}}{r_{\pi}} + g_m V_{\pi 1} + g_m V_{\pi 2} + \frac{V_{\pi 2}}{r_{\pi}} = \frac{V_e}{R_E}$$

$$(V_{\pi 1} + V_{\pi 2}) \left( \frac{1 + \beta}{r_{\pi}} \right) = \frac{V_e}{R_E}$$

$$\text{Now } \frac{v_1 - V_e}{R_B + r_{\pi}} = \frac{V_{\pi 1}}{r_{\pi}} \text{ and } \frac{v_2 - V_e}{R_B + r_{\pi}} = \frac{V_{\pi 2}}{r_{\pi}}$$

Then

$$V_{\pi 1} = \left( \frac{r_{\pi}}{R_B + r_{\pi}} \right) (v_1 - V_e)$$

$$\text{and } V_{\pi 2} = \left( \frac{r_{\pi}}{R_B + r_{\pi}} \right) (v_2 - V_e)$$

Substituting, we find

$$(v_1 + v_2 - 2V_e) \left( \frac{r_{\pi}}{R_B + r_{\pi}} \right) \left( \frac{1 + \beta}{r_{\pi}} \right) = \frac{V_e}{R_E}$$

or

$$(v_1 + v_2 - 2V_e) \left( \frac{1 + \beta}{R_B + r_{\pi}} \right) = \frac{V_e}{R_E}$$

Solving for  $V_e$ ,

$$V_e = \frac{v_1 + v_2}{2 + \frac{(1 + \beta)R_E}{R_B + r_{\pi}}}$$

Now  $v_{o2} = -g_m V_{\pi 2} R_C$

$$= -g_m R_C \left( \frac{r_{\pi}}{R_B + r_{\pi}} \right) (v_2 - V_e)$$

Substituting for  $V_e$ ,

$$v_{o2} = \frac{-\beta R_C}{R_B + r_{\pi}} \left[ v_2 - \frac{v_1 + v_2}{2 + \frac{(1 + \beta)R_E}{R_B + r_{\pi}}} \right]$$

$$= \frac{-\beta R_C}{R_B + r_{\pi}} \left[ \frac{v_2 \left( 1 + \frac{R_B + r_{\pi}}{(1 + \beta)R_E} \right) - v_1}{2 + \frac{(1 + \beta)R_E}{R_B + r_{\pi}}} \right]$$

$$\text{Now } v_1 = v_{cm} + \frac{v_d}{2}$$

$$v_2 = v_{cm} - \frac{v_d}{2}$$

Substituting and rearranging terms, we obtain

$$v_{o2} = \frac{-\beta R_C}{R_B + r_{\pi}} \left\{ \frac{v_d}{2} - v_{cm} \left[ \frac{1}{1 + \frac{2R_E(1 + \beta)}{R_B + r_{\pi}}} \right] \right\}$$

$$A_d = \frac{v_{o2}}{v_d} = \frac{\beta R_C}{2(r_{\pi} + R_B)}$$

$$r_{\pi} = \frac{\beta V_T}{I_{CQ}} = \frac{(100)(0.026)}{0.075} = 34.7 \text{ k}\Omega$$

$$A_d = \frac{(100)(50)}{2(34.7 + 0.5)} \Rightarrow A_d = 71.0$$

$$A_{cm} = -\frac{\beta R_C}{r_{\pi} + R_B} \left[ \frac{1}{1 + \frac{2R_E(1 + \beta)}{r_{\pi} + R_B}} \right]$$

$$= -\frac{(100)(50)}{34.7 + 0.5} \left[ \frac{1}{1 + \frac{2(62)(101)}{34.7 + 0.5}} \right]$$

$$\Rightarrow A_{cm} = -0.398$$

$$CMRR_{dB} = 20 \log_{10} \left| \frac{71.0}{0.398} \right| \Rightarrow CMRR_{dB} = 45.0 \text{ dB}$$

c.  $R_{i,d} = 2(r_{\pi} + R_B)$

$$R_{i,d} = 2(34.7 + 0.5) \Rightarrow R_{i,d} = 70.4 \text{ k}\Omega$$

Common-mode input resistance


$$R_{i,cm} = \frac{1}{2} [r_{\pi} + R_B + 2(1 + \beta)R_E]$$

$$= \frac{1}{2} [34.7 + 0.5 + 2(101)(62)]$$

$$\Rightarrow R_{i,cm} = 6.28 \text{ M}\Omega$$

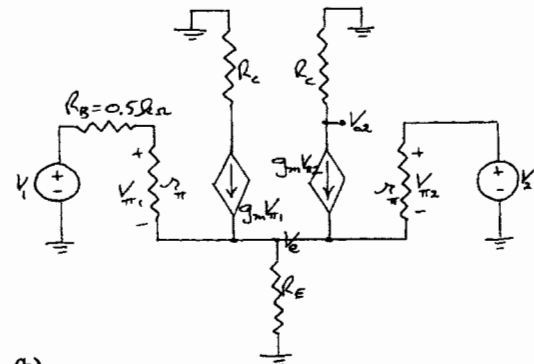11.9

$$(a) R_g = \frac{-0.7 - (-10)}{0.25} \Rightarrow R_g = 37.2 \text{ k}\Omega$$



(b)

$$\frac{V_{\pi 1}}{r_{\pi}} + g_m V_{\pi 1} + \frac{V_{\pi 2}}{r_{\pi}} + g_m V_{\pi 2} = \frac{V_e}{R_E}$$

$$\text{or (1) } \left( \frac{1 + \beta}{r_{\pi}} \right) (V_{\pi 1} + V_{\pi 2}) = \frac{V_e}{R_E}$$

$$\frac{V_{\pi 1}}{r_{\pi}} = \frac{V_1 - V_e}{R_B + r_{\pi}} \Rightarrow V_{\pi 1} = \left( \frac{r_{\pi}}{r_{\pi} + R_B} \right) (V_1 - V_e)$$

$$V_{\pi 2} = V_2 - V_e$$

Then

$$(1) \left( \frac{1+\beta}{r_{\pi}} \right) \left[ \frac{r_{\pi}}{r_{\pi} + R_B} (V_1 - V_e) + (V_2 - V_e) \right] = \frac{V_e}{R_E}$$

From this, we find

$$V_e = \frac{V_1 + \frac{r_{\pi} + R_B}{r_{\pi}} V_2}{\left[ \frac{r_{\pi} + R_B}{R_E(1+\beta)} + 1 + \frac{r_{\pi} + R_B}{r_{\pi}} \right]}$$

Now

$$V_o = -g_m V_{\pi 2} R_C = -g_m R_C (V_2 - V_e)$$

We have

$$r_{\pi} = \frac{(120)(0.026)}{0.125} \approx 25 \text{ k}\Omega, \quad g_m = \frac{0.125}{0.026} = 4.81 \text{ mA/V}$$

(i) Set  $V_1 = \frac{V_d}{2}$  and  $V_2 = -\frac{V_d}{2}$

Then

$$V_e = \frac{\frac{V_d}{2} \left( 1 - \left( \frac{25+0.5}{25} \right) \right)}{\left[ \frac{25+0.5}{(37.2)(121)} + 1 + \frac{25+0.5}{25} \right]} = \frac{V_d}{2} \frac{(-0.02)}{2.026}$$

So

$$V_e = -0.00494 V_d$$

Now

$$V_o = -(4.81)(50) \left( -\frac{V_d}{2} - (-0.00494) V_d \right) \Rightarrow$$

$$A_d = \frac{V_o}{V_d} = 119$$

(ii) Set  $V_1 = V_2 = V_{cm}$

Then

$$V_e = \frac{V_{cm} \left( 1 + \frac{25+0.5}{25} \right)}{\left[ \frac{25+0.5}{(37.2)(121)} + 1 + \frac{25+0.5}{25} \right]} = \frac{V_{cm}(2.02)}{2.02567}$$

$$V_e = V_{cm}(0.9972)$$

Then

$$V_o = -(4.81)(50) [V_{cm} - V_{cm}(0.9972)]$$

or

$$A_{cm} = \frac{V_o}{V_{cm}} = -0.673$$

11.10

a. Neglecting base currents

$$I_1 = I_3 = 400 \mu\text{A} \Rightarrow R_1 = \frac{30 - 0.7}{0.4}$$

$$\Rightarrow R_1 = 73.25 \text{ k}\Omega$$

$$V_{CE1} = 10 \text{ V} \Rightarrow V_{C1} = 9.3 \text{ V}$$

$$R_C = \frac{15 - 9.3}{0.2} \Rightarrow R_C = 28.5 \text{ k}\Omega$$

b.  $r_{\pi} = \frac{(100)(0.026)}{0.2} = 13 \text{ k}\Omega$

$$r_o(Q_3) = \frac{50}{0.4} = 125 \text{ k}\Omega$$

Using the results from problem 11.9, we have

$$A_d = \frac{\beta R_C}{2(r_{\pi} + R_B)} = \frac{(100)(28.5)}{2(13 + 10)} \Rightarrow A_d = 62$$

$$A_{cm} = -\frac{\beta R_C}{r_{\pi} + R_B} \left\{ \frac{1}{1 + \frac{2r_o(1+\beta)}{r_{\pi} + R_B}} \right\}$$

$$= -\frac{(100)(28.5)}{13 + 10} \left\{ \frac{1}{1 + \frac{2(125)(101)}{13 + 10}} \right\}$$

$$\Rightarrow A_{cm} = -0.113$$

$$CMRR_{dB} = 20 \log_{10} \left( \frac{62}{0.113} \right)$$

$$\Rightarrow CMRR_{dB} = 54.8 \text{ dB}$$

c.  $R_{id} = 2(r_{\pi} + R_B) = 2(13 + 10) \Rightarrow R_{id} = 46 \text{ k}\Omega$

$$R_{icm} = \frac{1}{2} [r_{\pi} + R_B + 2(1 + \beta)r_o]$$

$$= \frac{1}{2} [13 + 10 + 2(101)(125)]$$

$$\Rightarrow R_{icm} = 12.6 \text{ M}\Omega$$

11.11

From Equation (11.18)

$$v_o = v_{C2} - v_{C1} = g_m R_C v_d$$

$$g_m = \frac{I_{CQ}}{V_T}$$

For  $I_Q = 2 \text{ mA}$ ,  $I_{CQ} = 1 \text{ mA}$

$$\text{Then } g_m = \frac{1}{0.026} = 38.46 \text{ mA/V}$$

Now

$$2 = (38.46) R_C (0.015)$$


So  $R_C = 3.47 \text{ k}\Omega$

$$\text{Now } V_C = V^+ - I_C R_C = 10 - (1)(3.47) = 6.53 \text{ V}$$

For  $V_{CB} = 0 \Rightarrow v_{cm}(\text{max}) = 6.53 \text{ V}$

11.12

The small-signal equivalent circuit is

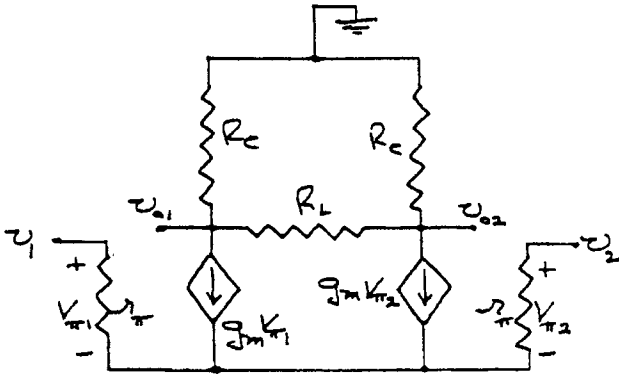

A KVL equation:  $v_1 = V_{\pi 1} - V_{\pi 2} + v_2$   
 $v_1 - v_2 = V_{\pi 1} - V_{\pi 2}$

A KCL equation

$$\frac{V_{\pi 1}}{r_{\pi}} + g_m V_{\pi 1} + \frac{V_{\pi 2}}{r_{\pi}} + g_m V_{\pi 2} = 0$$

$$(V_{\pi 1} + V_{\pi 2}) \left( \frac{1}{r_{\pi}} + g_m \right) = 0 \Rightarrow V_{\pi 1} = -V_{\pi 2}$$

Then  $v_1 - v_2 = 2V_{\pi 1} \Rightarrow V_{\pi 1} = \frac{1}{2}(v_1 - v_2)$

and  $V_{\pi 2} = -\frac{1}{2}(v_1 - v_2)$

At the  $v_{01}$  node:

$$\frac{v_{01}}{R_C} + \frac{v_{01} - v_{02}}{R_L} + g_m V_{\pi 1} = 0$$

$$v_{01} \left( \frac{1}{R_C} + \frac{1}{R_L} \right) - v_{02} \left( \frac{1}{R_L} \right) = \frac{1}{2} g_m (v_2 - v_1) \quad (1)$$

At the  $v_{02}$  node:

$$\frac{v_{02}}{R_C} + \frac{v_{02} - v_{01}}{R_L} + g_m V_{\pi 2} = 0$$

$$v_{02} \left( \frac{1}{R_C} + \frac{1}{R_L} \right) - v_{01} \left( \frac{1}{R_L} \right) = \frac{1}{2} g_m (v_1 - v_2) \quad (2)$$

From (1):

$$v_{02} = v_{01} \left( 1 + \frac{R_L}{R_C} \right) - \frac{1}{2} g_m R_L (v_2 - v_1)$$

Substituting into (2)

$$v_{01} \left( 1 + \frac{R_L}{R_C} \right) \left( \frac{1}{R_C} + \frac{1}{R_L} \right) - \frac{1}{2} g_m R_L (v_2 - v_1) \left( \frac{1}{R_C} + \frac{1}{R_L} \right) - v_{01} \left( \frac{1}{R_L} \right) = \frac{1}{2} g_m (v_1 - v_2)$$

$$v_{01} \left( \frac{1}{R_C} + \frac{R_L}{R_C^2} + \frac{1}{R_C} \right) = \frac{1}{2} g_m (v_1 - v_2) \left[ 1 - \left( \frac{R_L}{R_C} + 1 \right) \right]$$

$$\frac{v_{01}}{R_C} \left( 2 + \frac{R_L}{R_C} \right) = -\frac{1}{2} g_m \left( \frac{R_L}{R_C} \right) (v_1 - v_2)$$

For  $v_1 - v_2 = v_d$


$$A_{v1} = \frac{v_{01}}{v_d} = \frac{-\frac{1}{2} g_m R_L}{\left( 2 + \frac{R_L}{R_C} \right)}$$

From symmetry:  $A_{v2} = \frac{v_{02}}{v_d} = \frac{\frac{1}{2} g_m R_L}{\left( 2 + \frac{R_L}{R_C} \right)}$

Then  $A_v = \frac{v_{02} - v_{01}}{v_d} = \frac{g_m R_L}{\left( 2 + \frac{R_L}{R_C} \right)}$

11.13

The small-signal equivalent circuit is

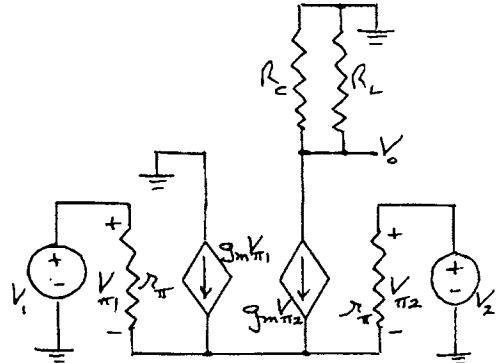

KVL equation:  $v_1 = V_{\pi 1} - V_{\pi 2} + v_2$  or  
 $v_1 - v_2 = V_{\pi 1} - V_{\pi 2}$

KCL equation:

$$\frac{V_{\pi 1}}{r_{\pi}} + g_m V_{\pi 1} + g_m V_{\pi 2} + \frac{V_{\pi 2}}{r_{\pi}} = 0$$

$$(V_{\pi 1} + V_{\pi 2}) \left( \frac{1}{r_{\pi}} + g_m \right) = 0 \Rightarrow V_{\pi 1} = -V_{\pi 2}$$

Then  $v_1 - v_2 = -2V_{\pi 2}$  or  $V_{\pi 2} = -\frac{1}{2}(v_1 - v_2)$

Now  $v_0 = -g_m V_{\pi 2} (R_C \parallel R_L)$   
 $= \frac{1}{2} g_m (R_C \parallel R_L) (v_1 - v_2)$

For  $v_1 - v_2 \equiv v_d$

$\Rightarrow A_d = \frac{v_0}{v_d} = \frac{1}{2} g_m (R_C \parallel R_L)$

11.14

We have

$$V_{C2} = -g_m V_{\pi 2} R_C = -g_m (V_{b2} - V_e) R_C$$

and

$$V_{C1} = -g_m V_{\pi 1} R_C = -g_m (V_{b1} - V_e) R_C$$

Then

$$\begin{aligned} V_0 &= V_{C2} - V_{C1} \\ &= -g_m (V_{b2} - V_e) R_C - [-g_m (V_{b1} - V_e) R_C] \\ &= g_m R_C (V_{b1} - V_{b2}) \end{aligned}$$

Differential gain

$$A_d = \frac{V_0}{V_{b1} - V_{b2}} = g_m R_C$$

Common-mode gain

$$A_{cm} = 0$$

11.15

(a)  $v_{cm} = 3V \Rightarrow V_{C1} = V_{C2} = 3V$

Then  $R_C = \frac{10-3}{0.1} \Rightarrow R_C = 70 \text{ k}\Omega$

(b)  $CMRR_{dB} = 75 \text{ dB} \Rightarrow CMRR = 5623$

Now

$$\begin{aligned} CMRR &= \frac{1}{2} \left[ 1 + \frac{(1+\beta)I_Q R_o}{\beta V_T} \right] \\ 5623 &= \frac{1}{2} \left[ 1 + \frac{(151)(0.2)R_o}{(150)(0.026)} \right] \Rightarrow R_o = 1.45 \text{ M}\Omega \end{aligned}$$

Use a Widlar current source.

$$R_o = r_o [1 + g_m R'_E]$$

Let  $V_A$  of current source transistor be  $100V$ .

Then

$$r_o = \frac{100}{0.2} = 500 \text{ k}\Omega, \quad g_m = \frac{0.2}{0.026} = 7.69 \text{ mA/V}$$

$$r_\pi = \frac{(150)(0.026)}{0.2} = 19.5 \text{ k}\Omega$$

So

$$1450 = 500 [1 + (7.69)R'_E] \Rightarrow R'_E = 0.247 \text{ k}\Omega$$

Now

$$R'_E = R_E \parallel r_\pi \Rightarrow 0.247 = R_E \parallel 19.5 \Rightarrow R_E = 250 \Omega$$

Then

$$I_Q R_E = V_T \ln \left( \frac{I_{REF}}{I_Q} \right)$$

$$(0.2)(0.250) = (0.026) \ln \left( \frac{I_{REF}}{0.2} \right) \Rightarrow I_{REF} = 1.37 \text{ mA}$$

Then

$$R_1 = \frac{10 - 0.7 - (-10)}{1.37} \Rightarrow R_1 = 14.1 \text{ k}\Omega$$

11.16

$$A_d = 180, \quad CMRR_{dB} = 85 \text{ dB}$$

$$CMRR = 17,783 = \left| \frac{A_d}{A_{cm}} \right| = \frac{180}{A_{cm}}$$

$$\Rightarrow |A_{cm}| = 0.01012$$

Assume the common-mode gain is negative.

$$v_0 = A_d v_d + A_{cm} v_{cm}$$

$$= 180 v_d - 0.01012 v_{cm}$$

$$v_0 = 180(2 \sin \omega t) \text{ mV} - (0.01012)(2 \sin \omega t) \text{ V}$$

$$v_0 = 0.36 \sin \omega t - 0.02024 \sin \omega t$$

Ideal Output:  $v_0 = 0.360 \sin \omega t \text{ (V)}$

Actual Output:  $v_0 = 0.340 \sin \omega t \text{ (V)}$

11.17

At terminal A.

$$R_{THA} = R_A \parallel R = \frac{R(1+\delta) \cdot R}{R(1+\delta) + R} = \frac{R(1+\delta)}{2+\delta} \cong \frac{R}{2} = 5 \text{ k}\Omega$$

Variation in  $R_{TH}$  is not significant

$$V_{THA} = \left( \frac{R_A}{R_A + R} \right) V^+ = \frac{R(1+\delta)(5)}{R(1+\delta) + R} = \frac{5(1+\delta)}{2+\delta}$$

At terminal B.

$$R_{THB} = R \parallel R = \frac{R}{2} = 5 \text{ k}\Omega$$

$$V_{THB} = \left( \frac{R}{R + R} \right) V^+ = 2.5V$$

From Eq. (11.27)

$$V_o = \frac{-\beta R_C (V_2 - V_1)}{2(r_\pi + R_B)} \text{ where } V_2 = V_{THB} \text{ and } V_1 = V_{THA}$$

$$R_B = 5 \text{ k}\Omega, \quad r_\pi = \frac{(120)(0.026)}{0.25} = 12.5 \text{ k}\Omega$$

So

$$V_o = \frac{-(120)(3)(V_2 - V_1)}{2(12.5 + 5)} = -10.3(V_2 - V_1)$$

We can find  $V_2 - V_1 = V_{THB} - V_{THA}$

$$\begin{aligned} V_{THB} - V_{THA} &= 2.5 - \left[ \frac{5(1+\delta)}{2+\delta} \right] \\ &= \frac{2.5(2+\delta) - 5(1+\delta)}{2+\delta} = \frac{2.5\delta - 5\delta}{2+\delta} \\ &= \frac{-2.5\delta}{2} = -1.25\delta \end{aligned}$$

Then

$$V_o = -(10.3)(-1.25)\delta = 12.9\delta$$

So for  $-0.01 \leq \delta \leq 0.01$

We have

$$-0.129 \leq V_{o2} \leq 0.129V$$

11.18

a.  $R_{id} = 2r_{\pi}$

$$r_{\pi} = \frac{(180)(0.026)}{0.2} = 23.4 \text{ k}\Omega$$

So

$$\underline{R_{id} = 46.8 \text{ k}\Omega}$$

b. Assuming  $r_{\mu} \rightarrow \infty$ , then

$$R_{icm} \cong [(1 + \beta)R_0] \parallel \left[ (1 + \beta) \left( \frac{r_o}{2} \right) \right]$$

$$r_o = \frac{125}{0.2} = 625 \text{ k}\Omega$$

$$R_{icm} = [(181)(1)] \parallel [(181)(0.3125)]$$

$$= 181 \parallel 56.56$$

$$\Rightarrow \underline{R_{icm} = 43.1 \text{ M}\Omega}$$

11.19

a. For  $I_1 = 1 \text{ mA}$ ,  $V_{BE3} = 0.7 \text{ V}$

$$R_1 = \frac{20 - 0.7}{1} \Rightarrow \underline{R_1 = 19.3 \text{ k}\Omega}$$

$$R_2 = \frac{V_T}{I_Q} \cdot \ln \left( \frac{I_1}{I_Q} \right) = \frac{0.026}{0.1} \cdot \ln \left( \frac{1}{0.1} \right)$$

$$\Rightarrow \underline{R_2 = 0.599 \text{ k}\Omega}$$

b.  $r_{\pi 4} = \frac{(180)(0.026)}{0.1} = 46.8 \text{ k}\Omega$

$$g_m = \frac{0.1}{0.026} = 3.846 \text{ mA/V}$$

$$r_{o4} = \frac{100}{0.1} \Rightarrow 1 \text{ M}\Omega$$

From Chapter 10

$$R_0 = r_{o4} [1 + g_m (R_E \parallel r_{\pi 4})]$$

$$R_E \parallel r_{\pi 4} = 0.599 \parallel 46.8 = 0.591$$

$$R_0 = (1) [1 + (3.846)(0.591)] = 3.27 \text{ M}\Omega$$

$$r_{o1} = \frac{100}{0.05} \Rightarrow 2 \text{ M}\Omega$$

$$R_{icm} \cong [(1 + \beta)R_0] \parallel \left[ (1 + \beta) \left( \frac{r_{o1}}{2} \right) \right]$$

$$= [(181)(3.27)] \parallel [(181)(1)]$$

$$= 592 \parallel 181$$

$$\Rightarrow \underline{R_{icm} = 139 \text{ M}\Omega}$$

(c) From Eq. (11.32(b))

$$A_{cm} = \frac{-g_m R_C}{1 + \frac{2(1 + \beta)R_o}{r_{\pi} + R_B}}$$

$$g_m = \frac{0.05}{0.026} = 1.923 \text{ mA/V}$$

$$r_{\pi} = \frac{(180)(0.026)}{0.05} = 93.6 \text{ k}\Omega$$

$$R_B = 0$$

Then

$$A_{cm} = \frac{-(1.923)(50)}{1 + \frac{2(181)(3270)}{93.6}} \Rightarrow \underline{A_{cm} = -0.00760}$$

11.20

$$A_{d1} = g_{m1} (R_1 \parallel r_{\pi 3})$$

$$g_{m1} = \frac{I_{Q1}/2}{V_T} = 19.23 I_{Q1}$$

$$r_{\pi 3} = \frac{\beta V_T}{I_{Q2}/2} = \frac{2(100)(0.026)}{I_{Q2}} = \frac{5.2}{I_{Q2}}$$

$$A_{d2} = \frac{g_{m3} R_2}{2}, \quad g_{m3} = \frac{I_{Q2}/2}{V_T} = 19.23 I_{Q2}$$

Then

$$30 = \frac{(19.23)I_{Q2}}{2} \cdot R_2 \Rightarrow I_{Q2} R_2 = 3.12 \text{ V}$$

Maximum  $v_{o2} - v_{o1} = \pm 18 \text{ mV}$  for linearity

$$v_{o3}(\text{max}) = (\pm 18)(30) \text{ mV} \Rightarrow \pm 0.54 \text{ V}$$

so  $I_{Q2} R_2 = 3.12 \text{ V}$  is OK.

From  $A_{d1}$ :

$$20 = 19.23 I_{Q1} (R_1 \parallel r_{\pi 3})$$

$$= 19.23 I_{Q1} \left( \frac{R_1 \left( \frac{5.2}{I_{Q2}} \right)}{R_1 + \left( \frac{5.2}{I_{Q2}} \right)} \right)$$

$$20 = \frac{19.23 I_{Q1} R_1 (5.2)}{I_{Q2} R_1 + 5.2}$$

$$\text{Let } \frac{I_{Q1}}{2} \cdot R_1 = 5 \text{ V} \Rightarrow I_{Q1} R_1 = 10 \text{ V}$$

Then

$$20 = \frac{19.23(10)(5.2)}{I_{Q2} R_1 + 5.2} \Rightarrow I_{Q2} R_1 = 44.8 \text{ V}$$

Now

$$I_{Q1} R_1 = 10 \Rightarrow R_1 = \frac{10}{I_{Q1}}$$

So

$$I_{Q2} \left( \frac{10}{I_{Q1}} \right) = 44.8 \Rightarrow \frac{I_{Q2}}{I_{Q1}} = 4.48$$

$$\text{Let } I_{Q1} = 100 \mu\text{A}, \quad I_{Q2} = 448 \mu\text{A}$$

Then

$$I_{Q2} R_2 = 3.12 \Rightarrow \underline{R_2 = 6.96 \text{ k}\Omega}$$

$$I_{Q1} R_1 = 10 \Rightarrow \underline{R_1 = 100 \text{ k}\Omega}$$

11.21

a.  $I_1 = \frac{20 - V_{GS3}}{50} = 0.25(V_{GS3} - 2)^2$

$20 - V_{GS3} = 12.5(V_{GS3}^2 - 4V_{GS3} + 4)$

$12.5V_{GS3}^2 - 49V_{GS3} + 30 = 0$

$V_{GS3} = \frac{49 \pm \sqrt{(49)^2 - 4(12.5)(30)}}{2(12.5)}$

$\Rightarrow V_{GS3} = 3.16 \text{ V}$

$I_1 = \frac{20 - 3.16}{50} \Rightarrow I_1 = I_Q = 0.337 \text{ mA}$

$I_{D1} = \frac{I_Q}{2} \Rightarrow I_{D1} = 0.168 \text{ mA}$


$0.168 = 0.25(V_{GS1} - 2)^2 \Rightarrow V_{GS1} = 2.82 \text{ V}$

$V_{DS4} = -2.82 - (-10) \Rightarrow V_{DS4} = 7.18 \text{ V}$

$V_{D1} = 10 - (0.168)(24) = 5.97 \text{ V}$

$V_{DS1} = 5.97 - (-2.82) \Rightarrow V_{DS1} = 8.79 \text{ V}$

(b)

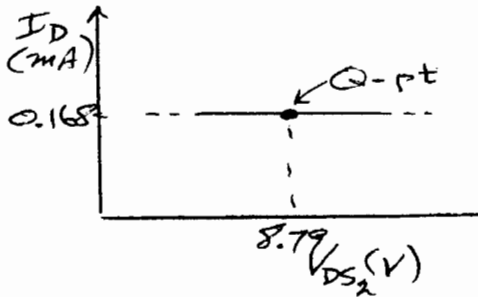

(c) Max  $v_{CM} \Rightarrow V_{DS1} = V_{DS2} = V_{DS}(\text{sat}) = V_{GS1} - V_{TN}$   
 $2.82 - 2 = 0.82 \text{ V}$

Now  $V_{D1} = 10 - (0.168)(24) = 5.97 \text{ V}$

$V_{S}(\text{max}) = 5.97 - V_{DS1}(\text{sat}) = 5.97 - 0.82$

$V_{S}(\text{max}) = 5.15 \text{ V}$

$v_{CM}(\text{max}) = V_{S}(\text{max}) + V_{GS1} = 5.15 + 2.82$

$v_{CM}(\text{max}) = 7.97 \text{ V}$

$v_{CM}(\text{min}) = V^- + V_{DS4}(\text{sat}) + V_{GS1}$

$V_{DS4}(\text{sat}) = V_{GS4} - V_{TN} = 3.16 - 2 = 1.16 \text{ V}$

Then

$v_{CM}(\text{min}) = -10 + 1.16 + 2.82 \Rightarrow$

$v_{CM}(\text{min}) = -6.02 \text{ V}$

11.22

a.  $I_{D1} = I_{D2} = 120 \mu\text{A} = 100(V_{GS1} - 1.2)^2$

$\Rightarrow V_{GS1} = V_{GS2} = 2.30 \text{ V}$

For  $v_1 = v_2 = -5.4 \text{ V}$  and  $V_{DS1} = V_{DS2} = 12 \text{ V}$

$\Rightarrow V_0 = -5.4 - 2.30 + 12 = 4.3 \text{ V}$

$R_D = \frac{10 - 4.3}{0.12} \Rightarrow R_D = 47.5 \text{ k}\Omega$

$I_Q = I_{D1} + I_{D2} \Rightarrow I_Q = I_1 = 240 \mu\text{A}$

$I_1 = 240 = 200(V_{GS3} - 1.2)^2 \Rightarrow V_{GS3} = 2.30 \text{ V}$

$R_1 = \frac{20 - 2.3}{0.24} \Rightarrow R_1 = 73.75 \text{ k}\Omega$

b.  $r_{o4} = \frac{1}{\lambda I_Q} = \frac{1}{(0.01)(0.24)} = 416.7 \text{ k}\Omega$

$\Delta I_Q = \frac{1}{r_{o4}} \cdot \Delta V_{DS} = \frac{5.4}{416.7} \Rightarrow \Delta I_Q \approx 13 \mu\text{A}$

11.23

a.  $R_D = \frac{10 - 7}{0.5} \Rightarrow R_D = 6 \text{ k}\Omega$


$I_Q = I_{D1} + I_{D2} \Rightarrow I_Q = 1 \text{ mA}$

b.  $10 = I_D(6) + V_{DS} - V_{GS}$

and  $V_{GS} = \sqrt{\frac{I_D}{K_n}} + V_{TN}$

For  $I_D = 0.5 \text{ mA}$ ,  $V_{GS} = \sqrt{\frac{0.5}{0.4}} + 2 = 3.12 \text{ V}$

and  $V_{DS} = 10.12$

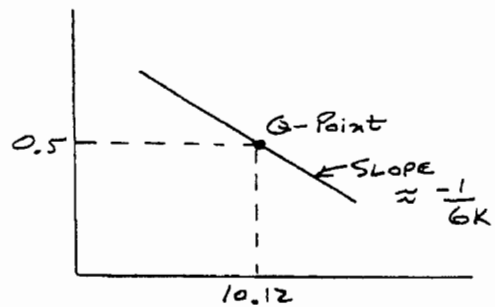

Load line is actually nonlinear.

c. Maximum common-mode voltage when  $M_1$  and  $M_2$  reach the transition point, or

$V_{DS}(\text{sat}) = V_{GS} - V_{TN} = 3.12 - 2 = 1.12 \text{ V}$

Then

$v_{cm} = v_{o2} - v_{DS}(\text{sat}) + V_{GS} = 7 - 1.12 + 3.12$

Or  $v_{cm}(\text{max}) = 9 \text{ V}$

Minimum common-mode voltage, voltage across  $I_Q$  becomes zero.

So  $v_{cm}(\text{min}) = -10 + 3.12$

$\Rightarrow v_{cm}(\text{min}) = -6.88 \text{ V}$

11.24

a.  $I_{D1} = I_{D2} = 0.5 \text{ mA}$

$v_{o1} - v_{o2} = [V^+ - I_{D1}R_{D1}] - [V^+ - I_{D2}R_{D2}]$

$v_{o1} - v_{o2} = I_{D2}R_{D2} - I_{D1}R_{D1} = I_D(R_{D2} - R_{D1})$

i.  $R_{D1} - R_{D2} = 6 \text{ k}\Omega$ ,  $v_{O1} - v_{O2} = 0$

ii.  $R_{D1} = 6 \text{ k}\Omega$ ,  $R_{D2} = 5.9 \text{ k}\Omega$

$$v_{O1} - v_{O2} = (0.5)(5.9 - 6)$$

$$\Rightarrow v_{O1} - v_{O2} = -0.05 \text{ V}$$

b.  $K_{n1} = 0.4 \text{ mA/V}^2$ ,  $K_{n2} = 0.44 \text{ mA/V}^2$

$$V_{GS1} = V_{GS2}$$

$$I_Q = (K_{n1} + K_{n2})(V_{GS} - V_{TN})^2$$

$$1 = (0.4 + 0.44)(V_{GS} - V_{TN})^2$$

$$\Rightarrow (V_{GS} - V_{TN})^2 = 1.19$$

$$I_{D1} = (0.4)(1.19) = 0.476 \text{ mA}$$

$$I_{D2} = (0.44)(1.19) = 0.524 \text{ mA}$$

i.  $R_{D1} = R_{D2} = 6 \text{ k}\Omega$

$$v_{O1} - v_{O2} = (0.524 - 0.476)(6)$$

$$\Rightarrow v_{O1} - v_{O2} = 0.288 \text{ V}$$

ii.  $R_{D1} = 6 \text{ k}\Omega$ ,  $R_{D2} = 5.9 \text{ k}\Omega$

$$v_{O1} - v_{O2} = (0.524)(5.9) - (0.476)(6)$$

$$= 3.0916 - 2.856$$

$$\Rightarrow v_{O1} - v_{O2} = 0.236 \text{ V}$$

11.25

(a) From Equation (11.51)

$$\frac{i_{D2}}{I_Q} = \frac{1}{2} - \sqrt{\frac{K_n}{2I_Q} \cdot v_d} \sqrt{1 - \left(\frac{K_n}{2I_Q}\right) v_d^2}$$

$$0.90 = 0.50 - \sqrt{\frac{0.1}{2(0.25)}} \cdot v_d \sqrt{1 - \left[\frac{0.1}{2(0.25)}\right] v_d^2}$$

$$-0.40 = -(0.4472)v_d \sqrt{1 - (0.2)v_d^2}$$

$$0.8945 = v_d \sqrt{1 - (0.2)v_d^2}$$

Square both sides

$$0.80 = v_d^2(1 - [0.2]v_d^2)$$

$$(0.2)(v_d^2)^2 - v_d^2 + 0.80 = 0$$

$$v_d^2 = \frac{1 \pm \sqrt{1 - 4(0.2)(0.80)}}{2(0.2)} = 4V^2 \text{ or } 1V^2$$

 Then  $v_d = 2 \text{ V}$  or  $1 \text{ V}$ 

$$\text{But } |v_d|_{\max} = \sqrt{\frac{I_Q}{k_n}} = \sqrt{\frac{0.25}{0.1}} = 1.58$$

 So  $v_d = 1 \text{ V}$ 

 b. From part (a),  $v_{d,\max} = 1.58 \text{ V}$ 

11.26

$$A_d = \frac{g_m R_D}{2}$$

 For  $v_{CM} = 2.5 \text{ V}$ 

$$I_{D1} = I_{D2} = \frac{I_Q}{2} = 0.25 \text{ mA}$$

$$\text{Let } V_{D1} = V_{D2} = 3 \text{ V, then } R_D = \frac{10 - 3}{0.25} \Rightarrow$$

$$R_D = 28 \text{ k}\Omega$$

$$\text{Then } 100 = \frac{g_m(28)}{2} \Rightarrow g_m = 7.14 \text{ mA/V}$$

$$\text{And } g_m = 2 \sqrt{\frac{k'_n}{2} \left(\frac{W}{L}\right) I_D}$$

$$7.14 = 2 \sqrt{\left(\frac{0.080}{2}\right) \left(\frac{W}{L}\right) (0.25)} \Rightarrow$$

$$\left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2 = 1274 \text{ (Extremely large transistors to meet the gain requirement.)}$$

 Need  $|A_{CM}| = 0.10$ 

From Eq.(11.64(b))

$$|A_{CM}| = \frac{g_m R_o}{1 + 2g_m R_o}$$

$$\text{So } 0.10 = \frac{(7.14)(28)}{1 + 2(7.14)R_o} \Rightarrow R_o = 140 \text{ k}\Omega$$

For the basic 2-transistor current source

$$R_o = r_o = \frac{1}{\lambda I_Q} = \frac{1}{(0.01)(0.5)} = 200 \text{ k}\Omega$$

This current source is adequate to meet common-mode gain requirement.

11.27

a.  $I_S = \frac{-V_{GS1} - (-5)}{R_S}$

and  $I_S = 2I_D = 2K_n(V_{GS1} - V_{TN})^2$

$$\frac{5 - V_{GS1}}{20} = 2(0.050)(V_{GS1} - 1)^2$$

$$5 - V_{GS1} = 2(V_{GS1}^2 - 2V_{GS1} + 1)$$

$$2V_{GS1}^2 - 3V_{GS1} - 3 = 0$$


$$V_{GS1} = \frac{3 \pm \sqrt{(3)^2 + 4(2)(3)}}{2(2)} \Rightarrow V_{GS1} = 2.186 \text{ V}$$

$$I_S = \frac{5 - 2.186}{20} \Rightarrow I_S = 0.141 \text{ mA}$$

$$I_{D1} = I_{D2} = \frac{I_S}{2} \Rightarrow I_{D1} = I_{D2} = 0.0704 \text{ mA}$$

$$v_{O2} = 5 - (0.0704)(25) \Rightarrow v_{O2} = 3.24 \text{ V}$$

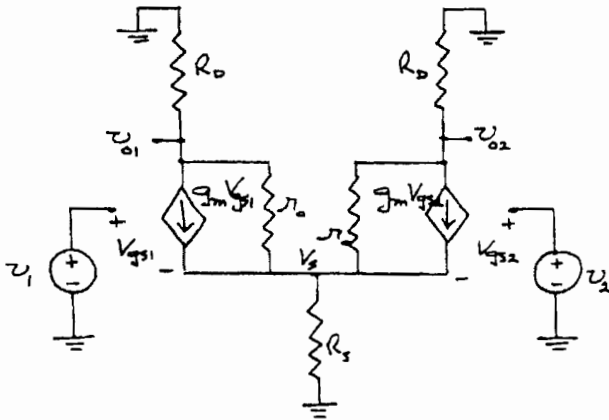b.  $g_m = 2K_n(V_{GS} - V_{TN}) = 2(0.05)(2.186 - 1)$   
 $g_m = 0.119 \text{ mA/V}$   
 $r_o = \frac{1}{\lambda I_{DQ}} = \frac{1}{(0.02)(0.0704)} = 710 \text{ k}\Omega$



$V_{gs1} = v_1 - V_S, V_{gs2} = v_2 - V_S$

$\frac{v_{01}}{R_D} + g_m V_{gs1} + \frac{v_{01} - V_S}{r_o} = 0$

$v_{01} \left( \frac{1}{R_D} + \frac{1}{r_o} \right) + g_m(v_1 - V_S) - \frac{V_S}{r_o} = 0$  (1)

$\frac{v_{02}}{R_D} + g_m V_{gs2} + \frac{v_{02} - V_S}{r_o} = 0$

$v_{02} \left( \frac{1}{R_D} + \frac{1}{r_o} \right) + g_m(v_2 - V_S) - \frac{V_S}{r_o} = 0$  (2)

$g_m V_{gs1} + \frac{v_{01} - V_S}{r_o} + \frac{v_{02} - V_S}{r_o} + g_m V_{gs2} = \frac{V_S}{R_S}$

$g_m(v_1 - V_S) + \frac{v_{01}}{r_o} + \frac{v_{02}}{r_o} - \frac{2V_S}{r_o} + g_m(v_2 - V_S) = \frac{V_S}{R_S}$

$g_m(v_1 + v_2) + \frac{v_{01}}{r_o} + \frac{v_{02}}{r_o} = V_S \left\{ 2g_m + \frac{2}{r_o} + \frac{1}{R_S} \right\}$  (3)

From (1)

$v_{01} = \frac{V_S \left( g_m + \frac{1}{r_o} \right) - g_m v_1}{\left( \frac{1}{R_D} + \frac{1}{r_o} \right)}$

Then

$g_m(v_1 + v_2) + \frac{V_S \left( g_m + \frac{1}{r_o} \right) - g_m v_1}{r_o \left( \frac{1}{R_D} + \frac{1}{r_o} \right)} + \frac{v_{02}}{r_o}$  (3)  
 $= V_S \left\{ 2g_m + \frac{2}{r_o} + \frac{1}{R_S} \right\}$

$g_m(v_1 + v_2)r_o \left( \frac{1}{R_D} + \frac{1}{r_o} \right) + V_S \left( g_m + \frac{1}{r_o} \right)$   
 $- g_m v_1 + v_{02} \left( \frac{1}{R_D} + \frac{1}{r_o} \right)$   
 $= V_S \left\{ 2g_m + \frac{2}{r_o} + \frac{1}{R_S} \right\} \cdot r_o \left( \frac{1}{R_D} + \frac{1}{r_o} \right)$

$g_m(v_1 + v_2) \left( 1 + \frac{r_o}{R_D} \right) - g_m v_1 + v_{02} \left( \frac{1}{R_D} + \frac{1}{r_o} \right)$   
 $= V_S \left\{ \left( 2g_m + \frac{2}{r_o} + \frac{1}{R_S} \right) \left( 1 + \frac{r_o}{R_D} \right) - \left( g_m + \frac{1}{r_o} \right) \right\}$

$g_m \left( v_1 \cdot \frac{r_o}{R_D} + v_2 + v_2 \cdot \frac{r_o}{R_D} \right) + v_{02} \left( \frac{1}{R_D} + \frac{1}{r_o} \right)$   
 $= V_S \left\{ 2g_m + \frac{2}{r_o} + \frac{1}{R_S} + 2g_m \cdot \frac{r_o}{R_D} + \frac{2}{R_D} \right.$   
 $\left. + \frac{r_o}{R_S R_D} - g_m - \frac{1}{r_o} \right\}$

$g_m \left( v_1 \cdot \frac{r_o}{R_D} + v_2 + v_2 \cdot \frac{r_o}{R_D} \right) + v_{02} \left( \frac{1}{R_D} + \frac{1}{r_o} \right)$   
 $= V_S \left\{ 2g_m + \frac{1}{r_o} + \frac{1}{R_S} \left( 1 + \frac{r_o}{R_D} \right) \right.$  (4)  
 $\left. + \frac{2}{R_D} (1 + g_m r_o) \right\}$

Then substituting into (2),

$v_{02} \left( \frac{1}{R_D} + \frac{1}{r_o} \right) + g_m v_2 = V_S \left( g_m + \frac{1}{r_o} \right)$

Substitute numbers:

$(0.119) \left[ v_1 \frac{710}{25} + v_2 + v_2 \frac{710}{25} \right] + v_{02} \left[ \frac{1}{25} + \frac{1}{710} \right]$   
 $= V_S \left\{ 0.119 + \frac{1}{710} + \frac{1}{20} \left( 1 + \frac{710}{25} \right) \right.$  (4)  
 $\left. + \frac{2}{25} [1 + (0.119)(710)] \right\}$

$(0.119)[28.4v_1 + 29.4v_2] + (0.0414)v_{02}$   
 $= V_S \{ 0.1204 + 1.470 + 6.8392 \}$   
 $= V_S (8.4296)$

or

$V_S = 0.4010v_1 + 0.4150v_2 + 0.00491v_{02}$

Then

$v_{02} \left( \frac{1}{25} + \frac{1}{710} \right) + (0.119)v_2 = V_S \left( 0.119 + \frac{1}{710} \right)$  (2)

$v_{02}(0.0414) + v_2(0.119)$   
 $= (0.1204)[0.401v_1 + 0.4150v_2 + 0.00491v_{02}]$

$v_{02}(0.0408) = (0.04828)v_1 - (0.0690)v_2$

$v_{02} = (1.183)v_1 - (1.691)v_2$

Now  $v_1 = v_{cm} + \frac{v_d}{2}$   
 $v_2 = v_{cm} - \frac{v_d}{2}$

So  $v_{o2} = (1.183)(v_{cm} + \frac{v_d}{2}) - (1.691)(v_{cm} - \frac{v_d}{2})$


Or  $v_{o2} = 1.437v_d - 0.508v_{cm}$

$\Rightarrow A_d = 1.437, A_{cm} = -0.508$

$CMRR_{dB} = 20 \log_{10} \left( \frac{1.437}{0.508} \right)$

$\Rightarrow CMRR_{dB} = 9.03 \text{ dB}$

11.28

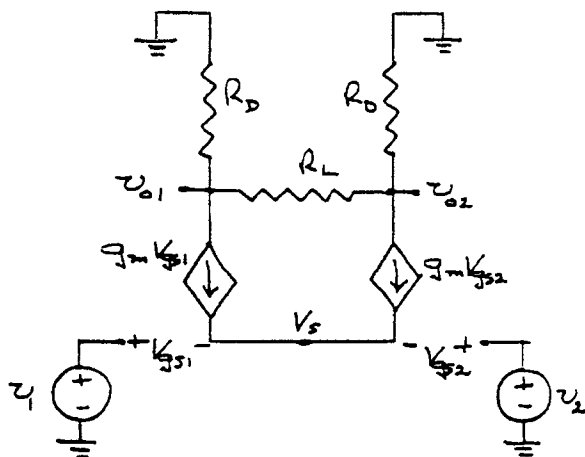

KVL:

$v_1 = V_{gs1} - V_{gs2} + v_2$

So  $v_1 - v_2 = V_{gs1} - V_{gs2}$

KCL:

$g_m V_{gs1} + g_m V_{gs2} = 0 \Rightarrow V_{gs1} = -V_{gs2}$

So  $V_{gs1} = \frac{1}{2}(v_1 - v_2), V_{gs2} = -\frac{1}{2}(v_1 - v_2)$

Now

$$\frac{v_{o2}}{R_D} + \frac{v_{o2} - v_{o1}}{R_L} = -g_m V_{gs2}$$

$$= v_{o2} \left( \frac{1}{R_D} + \frac{1}{R_L} \right) - \frac{v_{o1}}{R_L}$$

$$\frac{v_{o1}}{R_D} + \frac{v_{o1} - v_{o2}}{R_L} = -g_m V_{gs1}$$

$$= v_{o1} \left( \frac{1}{R_D} + \frac{1}{R_L} \right) - \frac{v_{o2}}{R_L}$$

From (1):  $v_{o1} = v_{o2} \left( 1 + \frac{R_L}{R_D} \right) + g_m R_L V_{gs2}$

Substitute into (2):

$$-g_m V_{gs1} = v_{o2} \left( 1 + \frac{R_L}{R_D} \right) \left( \frac{1}{R_D} + \frac{1}{R_L} \right) + g_m R_L \left( \frac{1}{R_D} + \frac{1}{R_L} \right) V_{gs2} - \frac{v_{o2}}{R_L}$$

$$-g_m (v_1 - v_2) + g_m \left( 1 + \frac{R_L}{R_D} \right) \left( \frac{1}{2} \right) (v_1 - v_2) = v_{o2} \left( \frac{1}{R_D} + \frac{R_L}{R_D^2} + \frac{1}{R_D} \right)$$

$$\frac{1}{2} g_m \left( \frac{R_L}{R_D} \right) (v_1 - v_2) = \frac{v_{o2}}{R_D} \left( 2 + \frac{R_L}{R_D} \right)$$

$$\Rightarrow A_{d2} = \frac{v_{o2}}{v_1 - v_2} = \frac{\frac{1}{2} g_m R_L}{\left( 2 + \frac{R_L}{R_D} \right)}$$


From symmetry

$$A_{d1} = \frac{v_{o1}}{v_1 - v_2} = \frac{-\frac{1}{2} g_m R_L}{\left( 2 + \frac{R_L}{R_D} \right)}$$

Then

$$A_v = \frac{v_{o2} - v_{o1}}{v_1 - v_2} = \frac{g_m R_L}{\left( 2 + \frac{R_L}{R_D} \right)}$$

11.29

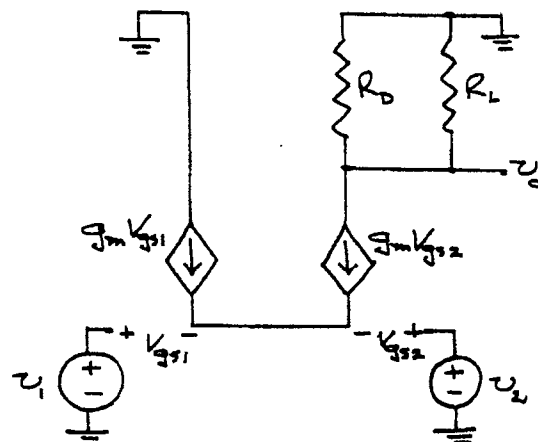

(1)

$v_1 - v_2 = V_{gs1} - V_{gs2}$

(2)

and  $g_m V_{gs1} + g_m V_{gs2} = 0 \Rightarrow V_{gs1} = -V_{gs2}$

Then  $v_1 - v_2 = -2V_{gs2}$

Or  $V_{gs2} = -\frac{1}{2}(v_1 - v_2)$

$$v_o = -g_m V_{gs2} (R_D \parallel R_L) = \frac{g_m}{2} (R_D \parallel R_L) (v_1 - v_2)$$

Or  $A_d = \frac{g_m}{2} (R_D \parallel R_L)$

11.30

From Equation (11.64(a)),  $A_d = \sqrt{\frac{K_n I_Q}{2}} \cdot R_D$

We need  $A_d = \frac{2}{0.2} = 10$

Then  $10 = \sqrt{\frac{K_n (0.5)}{2}} \cdot R_D$  or  $\sqrt{K_n} \cdot R_D = 20$

If we set  $R_D = 20 \text{ k}\Omega$ , then  $K_n = 1 \text{ mA/V}^2$

For this case  $V_D = 10 - (0.25)(20) = 5 \text{ V}$

$$V_{GS} = \sqrt{\frac{0.25}{1}} + 1 = 1.5 \text{ V}$$

$$V_{DS}(\text{sat}) = V_{GS} - V_{TN} = 1.5 - 1 = 0.5 \text{ V}$$

Then  $v_{cm}(\text{max}) = V_D - V_{DS}(\text{sat}) + V_{GS}$   
 $= 5 - 0.5 + 1.5$

Or  $v_{cm}(\text{max}) = 6 \text{ V}$

11.31

$$V_{d1} = -g_m V_{gs1} R_D = -g_m R_D (V_1 - V_s)$$

$$V_{d2} = -g_m V_{gs2} R_D = -g_m R_D (V_2 - V_s)$$

Now

$$V_o = V_{d2} - V_{d1} = -g_m R_D (V_2 - V_s) - (-g_m R_D (V_1 - V_s))$$

$$V_o = g_m R_D (V_1 - V_2)$$

Define  $V_1 - V_2 \equiv V_d$

Then

$$A_d = \frac{V_o}{V_d} = g_m R_D$$

and

$$A_{cm} = 0$$

11.32

(a)  $K_{n1} = K_{n2} = \left(\frac{k'_n}{2}\right) \left(\frac{W}{L}\right) = \left(\frac{0.080}{2}\right) (10) = 0.40 \text{ mA/V}^2$

$$V_{GS1} = V_{GS2} = \sqrt{\frac{I_D}{K_n}} + V_{TN} = \sqrt{\frac{0.1}{0.4}} + 1 = 1.5 \text{ V}$$

$$V_{DS1}(\text{sat}) = 1.5 - 1 = 0.5 \text{ V}$$

For  $v_{CM} = +3 \text{ V} \Rightarrow V_{D1} = V_{D2} = v_{CM} - V_{GS1} + V_{DS1}(\text{sat})$   
 $= 3 - 1.5 + 0.5 \Rightarrow V_{D1} = V_{D2} = 2 \text{ V}$

$$R_D = \frac{10 - 2}{0.1} \Rightarrow R_D = 80 \text{ k}\Omega$$

(b)  $A_d = \frac{1}{2} g_m R_D$  and  $g_m = 2\sqrt{(0.4)(0.1)} = 0.4 \text{ mA/V}$

Then  $A_d = \frac{1}{2} (0.4)(80) = 16$

$$CMRR_{dB} = 45 \Rightarrow CMRR = 177.8 = \frac{16}{A_{cm}}$$

So  $|A_{cm}| = 0.090$

$$|A_{cm}| = \frac{g_m R_D}{1 + 2g_m R_o}$$

$$0.090 = \frac{(0.4)(80)}{1 + 2(0.4)R_o} \Rightarrow R_o = 443 \text{ k}\Omega$$

If we assume  $\lambda = 0.01 \text{ V}^{-1}$  for the current source transistor, then

$$r_o = \frac{1}{\lambda I_Q} = \frac{1}{(0.01)(0.2)} = 500 \text{ k}\Omega$$

So the CMRR specification can be met by a 2-transistor current source.

Let  $\left(\frac{W}{L}\right)_3 = \left(\frac{W}{L}\right)_4 = 1$

Then  $K_{n3} = K_{n4} = \left(\frac{0.080}{2}\right) (1) = 0.040 \text{ mA/V}^2$

and  $V_{GS3} = \sqrt{\frac{I_Q}{K_{n3}}} + V_{TN} = \sqrt{\frac{0.2}{0.04}} + 1 = 3.24 \text{ V}$

For  $v_{CM} = -3 \text{ V}$ ,  $V_{D3} = -3 - V_{GS1} = -3 - 1.5 = -4.5 \text{ V}$   
 $\Rightarrow V_{DS3}(\text{min}) = -4.5 - (-10) = 5.5 \text{ V} > V_{DS3}(\text{sat})$


So design is OK.

On reference side: For  $\left(\frac{W}{L}\right) \geq 1$ ,  $V_{GS}(\text{max}) = 3.24 \text{ V}$

$$20 - V_{GS3} = 20 - 3.24 = 16.76 \text{ V}$$

Then
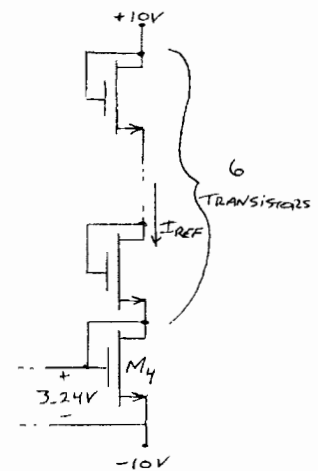
$$\frac{16.67}{3.24} = 5.17 \Rightarrow \text{We need six transistors in series.}$$




$$V_{GS} = \frac{20 - 3.24}{6} = 2.793 \text{ V}$$

$$I_{REF} = \left(\frac{k'_n}{2}\right) \left(\frac{W}{L}\right) (V_{GS} - V_{TN})^2$$

$$0.2 = \left(\frac{0.080}{2}\right) \left(\frac{W}{L}\right) (2.793 - 1)^2 \Rightarrow$$

$$\left(\frac{W}{L}\right) = 1.56 \text{ for each of the 6 transistors.}$$

11.33

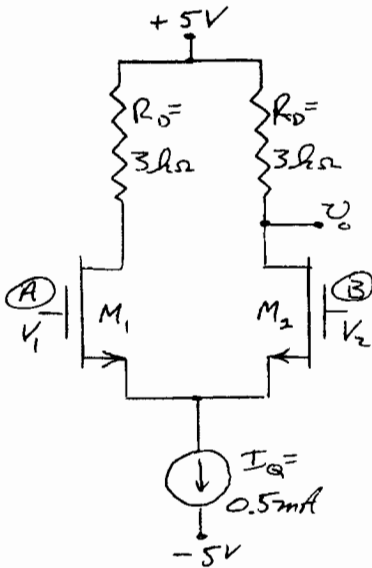

$$A_d = \frac{1}{2} g_m R_D$$

$$g_m = 2\sqrt{K_n I_D} = 2\sqrt{(0.25)(0.25)} = 0.50 \text{ mA/V}$$

$$A_d = \frac{1}{2} (0.50)(3) = 0.75$$

From Problem 11.17

$$V_1 = V_A = \frac{5(1+\delta)}{2+\delta}, \quad V_2 = V_B = 2.5 \text{ V}$$

$$\text{and } V_1 - V_2 = 1.25\delta$$

Then

$$V_{o2} = A_d (V_1 - V_2) = (0.75)(1.25\delta) = 0.9375\delta$$

$$\text{So for } -0.01 \leq \delta \leq 0.01$$

$$-9.375 \leq V_{o2} \leq 9.375 \text{ mV}$$

11.34

From previous results

$$A_{d1} = \frac{v_{o2} - v_{o1}}{v_1 - v_2} = g_{m1} R_1 = \sqrt{2K_{n1} I_{Q1}} \cdot R_1 = 20$$

and

$$A_{d2} = \frac{v_{o2}}{v_{o2} - v_{o1}} = \frac{1}{2} g_{m3} R_2 = \frac{1}{2} \sqrt{2K_{n3} I_{Q2}} \cdot R_2 = 30$$

$$\text{Set } \frac{I_{Q1} R_1}{2} = 5 \text{ V and } \frac{I_{Q2} R_2}{2} = 2.5 \text{ V}$$

$$\text{Let } I_{Q1} = I_{Q2} = 0.1 \text{ mA}$$

$$\text{Then } R_1 = 100 \text{ k}\Omega, \quad R_2 = 50 \text{ k}\Omega$$

Then

$$2 \left( \frac{0.06}{2} \right) \left( \frac{W}{L} \right)_1 (0.1) = \left( \frac{20}{100} \right)^2 \Rightarrow$$

$$\left( \frac{W}{L} \right)_1 = \left( \frac{W}{L} \right)_2 = 6.67$$

and

$$2 \left( \frac{0.060}{2} \right) \left( \frac{W}{L} \right)_3 (0.1) = \left( \frac{2(30)}{50} \right)^2 \Rightarrow$$

$$\left( \frac{W}{L} \right)_3 = \left( \frac{W}{L} \right)_4 = 240$$

11.35

$$\text{a. } i_{D1} = I_{DSS} \left( 1 - \frac{v_{GS1}}{V_P} \right)^2$$

$$i_{D2} = I_{DSS} \left( 1 - \frac{v_{GS2}}{V_P} \right)^2$$

$$\sqrt{i_{D1}} - \sqrt{i_{D2}}$$

$$= \sqrt{I_{DSS}} \left( 1 - \frac{v_{GS1}}{V_P} \right) - \sqrt{I_{DSS}} \left( 1 - \frac{v_{GS2}}{V_P} \right)$$

$$= \frac{\sqrt{I_{DSS}}}{V_P} (v_{GS2} - v_{GS1})$$

$$= -\frac{\sqrt{I_{DSS}}}{V_P} \cdot v_d = \frac{\sqrt{I_{DSS}}}{(-V_P)} \cdot v_d$$

$$i_{D1} + i_{D2} = I_Q \Rightarrow i_{D2} = I_Q - i_{D1}$$

$$\left( \sqrt{i_{D1}} - \sqrt{I_Q - i_{D1}} \right)^2 = \frac{I_{DSS}}{(-V_P)^2} \cdot v_d^2$$

$$i_{D1} - 2\sqrt{i_{D1}(I_Q - i_{D1})} + (I_Q - i_{D1}) = \frac{I_{DSS}}{(-V_P)^2} \cdot v_d^2$$

Then

$$\sqrt{i_{D1}(I_Q - i_{D1})} = \frac{1}{2} \left[ I_Q - \frac{I_{DSS}}{(-V_P)^2} \cdot v_d^2 \right]$$

Square both sides

$$i_{D1}^2 - i_{D1} I_Q + \frac{1}{4} \left[ I_Q - \frac{I_{DSS}}{(-V_P)^2} \cdot v_d^2 \right]^2 = 0$$

$$i_{D1} = \frac{I_Q \pm \sqrt{I_Q^2 - 4 \left( \frac{1}{4} \right) \left[ I_Q - \frac{I_{DSS}}{(-V_P)^2} \cdot v_d^2 \right]^2}}{2}$$

$$i_{D1} =$$

$$\frac{I_Q}{2} \pm \frac{1}{2} \sqrt{I_Q^2 - \left[ I_Q^2 - \frac{2I_Q I_{DSS} v_d^2}{(-V_P)^2} + \left( \frac{I_{DSS} v_d^2}{(-V_P)^2} \right)^2 \right]}$$

Use + sign

$$i_{D1} = \frac{I_Q}{2} + \frac{1}{2} \sqrt{\frac{2I_Q I_{DSS}}{(-V_P)^2} \cdot v_d^2 - \left( \frac{I_{DSS}}{(-V_P)^2} \cdot v_d^2 \right)^2}$$

$$i_{D1} = \frac{I_Q}{2} + \frac{1}{2} \frac{I_Q}{(-V_P)} v_d \sqrt{\frac{2I_{DSS}}{I_Q} - \left( \frac{I_{DSS}}{I_Q} \right)^2 \left( \frac{v_d}{V_P} \right)^2}$$

Or

$$\frac{i_{D1}}{I_Q} = \frac{1}{2} + \left( \frac{1}{-2V_P} \right) \cdot v_d \sqrt{\frac{2I_{DSS}}{I_Q} - \left( \frac{I_{DSS}}{I_Q} \right)^2 \left( \frac{v_d}{V_P} \right)^2}$$

We had

$$i_{D2} = I_Q - i_{D1}$$

Then

$$\frac{i_{D2}}{I_Q} = \frac{1}{2} - \left(\frac{1}{-2V_P}\right) \cdot \nu_d \sqrt{\frac{2I_{DSS}}{I_Q} - \left(\frac{I_{DSS}}{I_Q}\right)^2 \left(\frac{\nu_d}{V_P}\right)^2}$$

b. If  $i_{D1} = I_Q$ , then

$$1 = \frac{1}{2} + \left(\frac{1}{-2V_P}\right) \cdot \nu_d \sqrt{\frac{2I_{DSS}}{I_Q} - \left(\frac{I_{DSS}}{I_Q}\right)^2 \left(\frac{\nu_d}{V_P}\right)^2}$$

$$|V_P| = \nu_d \sqrt{\frac{2I_{DSS}}{I_Q} - \left(\frac{I_{DSS}}{I_Q}\right)^2 \left(\frac{\nu_d}{V_P}\right)^2}$$

Square both sides

$$|V_P|^2 = \nu_d^2 \left[ \frac{2I_{DSS}}{I_Q} - \left(\frac{I_{DSS}}{I_Q}\right)^2 \left(\frac{\nu_d}{V_P}\right)^2 \right]$$

$$\left(\frac{I_{DSS}}{I_Q}\right)^2 \left(\frac{1}{V_P}\right)^2 (\nu_d^2)^2 - \frac{2I_{DSS}}{I_Q} \cdot \nu_d^2 + |V_P|^2 = 0$$

$$\nu_d^2 =$$

$$\frac{\frac{2I_{DSS}}{I_Q} \pm \sqrt{\left(\frac{2I_{DSS}}{I_Q}\right)^2 - 4\left(\frac{I_{DSS}}{I_Q}\right)^2 \left(\frac{1}{V_P}\right)^2 (V_P)^2}}{2\left(\frac{I_{DSS}}{I_Q}\right)^2 \left(\frac{1}{V_P}\right)^2}$$

$$\nu_d^2 = (V_P)^2 \left(\frac{I_Q}{I_{DSS}}\right)$$

$$\text{Or } |\nu_d| = |V_P| \left(\frac{I_Q}{I_{DSS}}\right)^{1/2}$$

c. For  $\nu_d$  small,

$$i_{D1} \approx \frac{I_Q}{2} + \frac{1}{2} \cdot \frac{I_Q}{(-V_P)} \cdot \nu_d \sqrt{\frac{2I_{DSS}}{I_Q}}$$

$$g_f = \left. \frac{di_{D1}}{d\nu_d} \right|_{\nu_d=0} = \frac{1}{2} \cdot \frac{I_Q}{(-V_P)} \cdot \sqrt{\frac{2I_{DSS}}{I_Q}}$$

Or

$$\Rightarrow g_f(\text{max}) = \left(\frac{1}{-V_P}\right) \sqrt{\frac{I_Q I_{DSS}}{2}}$$

11.36

a.  $I_Q = I_{D1} + I_{D2} \Rightarrow I_Q = 1 \text{ mA}$   
 $\nu_0 = 7 = 10 - (0.5)R_D \Rightarrow R_D = 6 \text{ k}\Omega$

b.  $g_f(\text{max}) = \left(\frac{1}{-V_P}\right) \sqrt{\frac{I_Q \cdot I_{DSS}}{2}}$

$$g_f(\text{max}) = \left(\frac{1}{4}\right) \sqrt{\frac{(1)(2)}{2}}$$

$$\Rightarrow g_f(\text{max}) = 0.25 \text{ mA/V}$$

c.  $A_d = \frac{g_m R_D}{2} = g_f(\text{max}) \cdot R_D$

$$A_d = (0.25)(6) \Rightarrow A_d = 1.5$$

11.37

a.  $I_S = \frac{-V_{GS} - (-5)}{R_S} = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$

$$5 - V_{GS} = (0.8)(20) \left(1 - \frac{V_{GS}}{-2}\right)^2$$

$$5 - V_{GS} = 16 \left(1 + V_{GS} + \frac{1}{4}V_{GS}^2\right)$$

$$4V_{GS}^2 + 17V_{GS} + 11 = 0$$

$$V_{GS} = \frac{-17 \pm \sqrt{(17)^2 - 4(4)(11)}}{2(4)}$$

$$V_{GS} = -0.796 \text{ V}$$

$$I_S = \frac{5 - (-0.796)}{20} \Rightarrow I_S = 0.290 \text{ mA}$$

$$I_{D1} = I_{D2} = \frac{I_S}{2} \Rightarrow I_{D1} = I_{D2} = 0.145 \text{ mA}$$

$$\nu_{02} = 5 - (0.145)(25) \Rightarrow \nu_{02} = 1.375 \text{ V}$$

b. Taking into account the  $r_o$  parameters of  $Q_1$  and  $Q_2$ , the analysis is identical to that in problem 11.34.

11.38

Equivalent circuit and analysis is identical to that in problem 11.36.

$$A_{d2} = \frac{\frac{1}{2} \cdot g_m R_L}{\left(2 + \frac{R_L}{R_D}\right)}$$

$$A_{d1} = \frac{-\frac{1}{2} \cdot g_m R_L}{\left(2 + \frac{R_L}{R_D}\right)}$$

$$A_v = \frac{\nu_{02} - \nu_{01}}{\nu_d} = \frac{g_m R_L}{\left(2 + \frac{R_L}{R_D}\right)}$$

11.39

a. Using the results of problem 10.59, the resistance from the base of  $Q_4$  looking toward  $Q_3$ :

$$\frac{1}{R'_0} = \frac{1}{r_{01}} + \frac{\left(\frac{1}{r_{\pi 3}} + g_{m3} + \frac{1}{r_{03}}\right)}{\left[1 + \left(\frac{1}{r_{\pi 3}} + g_{m3} + \frac{1}{r_{03}}\right) R_E\right]}$$

$$r_{01} = \frac{120}{0.1} = 1200 \text{ k}\Omega, \quad r_{03} = \frac{80}{0.1} = 800 \text{ k}\Omega$$

Assume  $\beta = 100$

$$r_{\pi 3} = \frac{(100)(0.026)}{0.1} = 26 \text{ k}\Omega$$

$$g_{m3} = \frac{0.1}{0.026} = 3.846 \text{ mA/V}$$

$$\frac{1}{R'_o} = \frac{1}{1200} + \frac{\left(\frac{1}{26} + 3.846 + \frac{1}{800}\right)}{\left[1 + \left(\frac{1}{26} + 3.846 + \frac{1}{800}\right)(1)\right]}$$

$$= \frac{1}{1200} + \frac{3.886}{1 + (3.886)(1)} \Rightarrow R'_o = 1.256 \text{ k}\Omega$$

$$R_o = r_{o2} \left[ 1 + \frac{R_E \parallel (r_{\pi 2} + R'_o)}{r_{o2}} + g_{m2} \left( \frac{r_{\pi 2}}{r_{\pi 2} + R'_o} \right) \{ R_E \parallel (r_{\pi 2} + R'_o) \} \right]$$

$$R_E \parallel (r_{\pi 2} + R'_o) = (1) \parallel (26 + 1.256)$$

$$= (1) \parallel (27.256)$$

$$= 0.965 \text{ k}\Omega$$

$$R_o = 1200 \left[ 1 + \frac{0.965}{1200} + (3.846) \left( \frac{26}{26 + 1.256} \right) (0.965) \right]$$

$$\Rightarrow R_o = 5.45 \text{ M}\Omega$$

Then

$$A_v = -g_m(r_{o2} \parallel R_o)$$

$$r_{o2} = \frac{120}{0.1} = 1200 \text{ k}\Omega$$

$$g_m = \frac{0.1}{0.026} = 3.846 \text{ mA/V}$$

$$A_v = -(3.846)[1200 \parallel 5450]$$

$$\Rightarrow \underline{A_v = -3782}$$

b. For  $R = 0$ ,  $r_{o4} = \frac{80}{0.1} = 800 \text{ k}\Omega$

$$A_v = -g_m(r_{o2} \parallel r_{o4})$$

$$= -(3.846)[1200 \parallel 800]$$

$$\Rightarrow \underline{A_v = -1846}$$

(c) For part (a),  $R_o = (5.45 \parallel 1.2) = 0.983 \text{ M}\Omega$

For part (b),  $R_o = (1.2 \parallel 0.8) = 0.48 \text{ M}\Omega$

11.40

$$I_{B5} = \frac{I_{E5}}{1 + \beta} = \frac{I_{B3} + I_{B4}}{1 + \beta} = \frac{I_{C3} + I_{C4}}{\beta(1 + \beta)}$$

Now  $I_{C3} + I_{C4} \approx I_Q$

$$\text{So } I_{B5} \approx \frac{I_Q}{\beta(1 + \beta)}$$

$$I_{B6} = \frac{I_{E6}}{1 + \beta} = \frac{I_{Q1}}{\beta(1 + \beta)}$$

For balance, we want  $I_{B6} = I_{B5}$

So that  $\underline{I_{Q1} = I_Q}$

11.41

a.  $A_d = g_m(r_{o2} \parallel r_{o4})$

$$r_{o2} = \frac{V_{A2}}{I_{C2}} = \frac{150}{0.4} = 375 \text{ k}\Omega$$

$$r_{o4} = \frac{V_{A4}}{I_{C4}} = \frac{100}{0.4} = 250 \text{ k}\Omega$$

$$g_m = \frac{I_{C2}}{V_T} = \frac{0.4}{0.026} = 15.38 \text{ mA/V}$$

$$A_d = (15.38)(375 \parallel 250)$$


$$\Rightarrow \underline{A_d = 2307}$$

b.  $R_L = r_{o2} \parallel r_{o4} = 375 \parallel 250$

$$\Rightarrow \underline{R_L = 150 \text{ k}\Omega}$$

11.42

(a) For  $Q_2, Q_4$

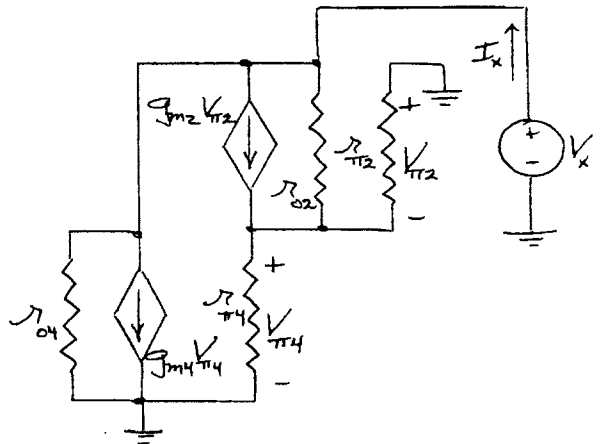

$$(1) I_x = \frac{V_x - V_{x4}}{r_{o2}} + g_{m2}V_{x2} + g_{m4}V_{x4} + \frac{V_x}{r_{o4}}$$

$$(2) g_{m2}V_{x2} + \frac{V_x - V_{x4}}{r_{o2}} = \frac{V_{x4}}{r_{x4} \parallel r_{x2}}$$

$$(3) V_{x4} = -V_{x2}$$

From (2)

$$\frac{V_x}{r_{o2}} = V_{x4} \left[ \frac{1}{r_{x4} \parallel r_{x2}} + \frac{1}{r_{o2}} + g_{m2} \right]$$

Now

$$I_{C4} = \left( \frac{\beta}{1 + \beta} \right) \left( \frac{I_Q}{2} \right) = \left( \frac{120}{121} \right) (0.5) = 0.496 \text{ mA}$$

$$I_{C2} = \left( \frac{I_Q}{2} \right) \left( \frac{1}{1 + \beta} \right) \left( \frac{\beta}{1 + \beta} \right) = (0.5) \left( \frac{120}{(121)^2} \right) \Rightarrow$$

$$I_{C2} = 0.0041 \text{ mA}$$

So

$$r_{\pi 2} = \frac{(120)(0.026)}{0.0041} = 761 \text{ k}\Omega$$

$$g_{m2} = \frac{0.0041}{0.026} = 0.158 \text{ mA/V}$$

$$r_{o2} = \frac{100}{0.0041} \Rightarrow 24.4 \text{ M}\Omega$$

$$r_{\pi 4} = \frac{(120)(0.026)}{0.496} = 6.29 \text{ k}\Omega$$

$$g_{m4} = \frac{0.496}{0.026} = 19.08 \text{ mA/V}$$

$$r_{o4} = \frac{100}{0.496} = 202 \text{ k}\Omega$$

Now

$$\frac{V_x}{r_{o2}} = V_{\pi 4} \left[ \frac{1}{6.29 \parallel 761} + \frac{1}{24400} + 0.158 \right] \Rightarrow$$

which yields

$$V_{\pi 4} = \frac{V_x}{(0.318)r_{o2}}$$

From (1),

$$I_x = \frac{V_x}{r_{o2}} + \frac{V_x}{r_{o4}} + V_{\pi 4} \left( g_{m4} - g_{m2} - \frac{1}{r_{o2}} \right)$$

$$\frac{I_x}{V_x} = \left[ \frac{1}{24400} + \frac{1}{202} + \frac{(19.08 - 0.158 - \frac{1}{24400})}{(0.318)(24400)} \right]$$

which yields

$$R_{o2} = \frac{V_x}{I_x} = 135 \text{ k}\Omega$$


Now

$$r_{o6} = \frac{80}{0.5} = 160 \text{ k}\Omega$$

Then

$$R_o = R_{o2} \parallel r_{o6} = 135 \parallel 160 \Rightarrow R_o = 73.2 \text{ k}\Omega$$

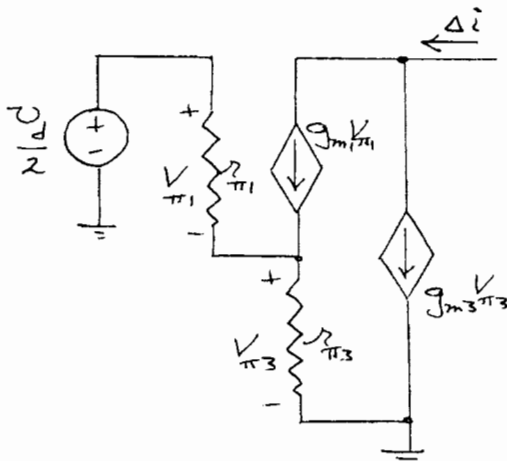(b)  $A_d = g_m^c R_o$  where  $g_m^c = \frac{\Delta i}{v_d/2}$



$$\Delta i = g_{m1}V_{\pi 1} + g_{m3}V_{\pi 3} \text{ and } V_{\pi 1} + V_{\pi 3} = \frac{v_d}{2}$$

$$\text{Also } \left( \frac{V_{\pi 1}}{r_{\pi 1}} + g_{m1}V_{\pi 1} \right) r_{\pi 3} = V_{\pi 3}$$

$$\text{So } V_{\pi 1} \left( \frac{1+\beta}{r_{\pi 1}} \right) r_{\pi 3} = V_{\pi 3}$$

Or

$$V_{\pi 1} \left( \frac{121}{761} \right) (6.29) = V_{\pi 3} \cong V_{\pi 1}$$

$$\text{Then } 2V_{\pi 1} = \frac{v_d}{2} \Rightarrow V_{\pi 1} = \frac{v_d}{4}$$

So

$$\Delta i = (g_{m1} + g_{m3})V_{\pi 1} = (0.158 + 19.08) \left( \frac{v_d}{4} \right) = 9.62 \left( \frac{v_d}{2} \right)$$

So

$$g_m^c = \frac{\Delta i}{v_d/2} = 9.62 \Rightarrow A_d = (9.62)(73.2) \Rightarrow$$

$$A_d = 704$$

Now


$$R_{id} = 2R_i \text{ where } R_i = r_{\pi 1} + (1+\beta)r_{\pi 3}$$

$$R_i = 761 + (121)(6.29) = 1522 \text{ k}\Omega$$

Then

$$R_{id} = 3.044 \text{ M}\Omega$$

11.43

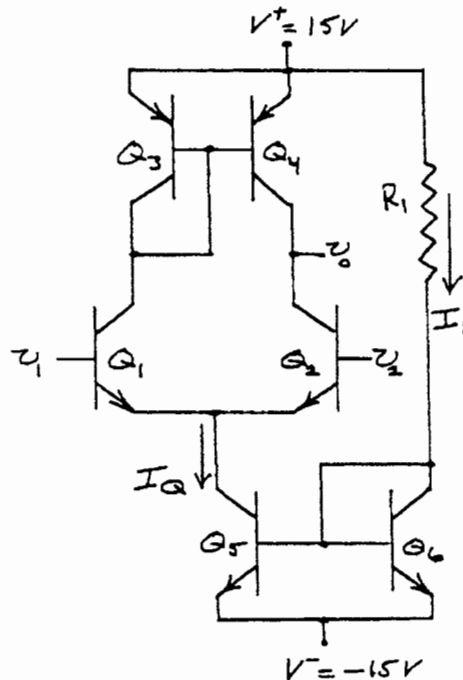

a.  $g_f = \frac{I_Q}{4V_T} \Rightarrow I_Q = g_f(4V_T) = (8)(4)(0.026)$   
 $\Rightarrow I_Q = 0.832 \text{ mA}$

Neglecting base currents,

$$R_1 = \frac{30 - 0.7}{0.832} \Rightarrow \underline{R_1 = 35.2 \text{ k}\Omega}$$

$$\text{b. } r_{o4} = r_{o2} = \frac{V_A}{I_{CQ}} = \frac{100}{0.416} = 240 \text{ k}\Omega$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.416}{0.026} = 16 \text{ mA/V}$$

$$A_d = g_m(r_{o2} \parallel r_{o4}) = 16(240 \parallel 240)$$

$$\Rightarrow \underline{A_d = 1920}$$

$$R_{id} = 2r_{\pi}, \quad r_{\pi} = \frac{(180)(0.026)}{0.416} = 11.25 \text{ k}\Omega$$

$$\Rightarrow \underline{R_{id} = 22.5 \text{ k}\Omega}$$

$$R_o = r_{o2} \parallel r_{o4} \Rightarrow \underline{R_o = 120 \text{ k}\Omega}$$

c. Max. common-mode voltage when

$$V_{CB} = 0 \text{ for } Q_1 \text{ and } Q_2.$$

Therefore

$$v_{cm}(\text{max}) = V^+ - V_{EB}(Q_3) = 15 - 0.7$$

$$v_{cm}(\text{max}) = 14.3 \text{ V}$$

Min. common-mode voltage when

$$V_{CB} = 0 \text{ for } Q_3.$$

Therefore

$$v_{cm}(\text{min}) = 0.7 + 0.7 + (-15) = -13.6 \text{ V}$$

$$\text{So } \underline{-13.6 < v_{cm} < 14.3 \text{ V}}$$

$$R_{icm} \approx \frac{1}{2}(1 + \beta)(2R_o)$$

$$R_o = \frac{V_A}{I_Q} = \frac{100}{0.832} = 120 \text{ k}\Omega$$

$$R_{icm} = (181)(120) \Rightarrow \underline{R_{icm} = 21.7 \text{ M}\Omega}$$

11.44

$$\text{a. } I_o = I_{B3} + I_{B4} \approx 2 \left( \frac{I_Q}{2} \right) \left( \frac{1}{\beta} \right)$$

$$I_o = \frac{I_Q}{\beta} = \frac{0.2}{100} \Rightarrow \underline{I_o = 2 \mu\text{A}}$$

$$\text{b. } r_{o2} = r_{o4} = \frac{V_A}{I_{CQ}} = \frac{100}{0.1} = 1000 \text{ k}\Omega$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.1}{0.026} = 3.846 \text{ mA/V}$$

$$A_d = g_m(r_{o2} \parallel r_{o4}) = (3.846)(1000 \parallel 1000)$$

$$\Rightarrow \underline{A_d = 1923}$$


$$\text{c. } A_d = g_m(r_{o2} \parallel r_{o4} \parallel R_L)$$

$$A_d = (3.846)(1000 \parallel 1000 \parallel 250)$$

$$\Rightarrow \underline{A_d = 641}$$

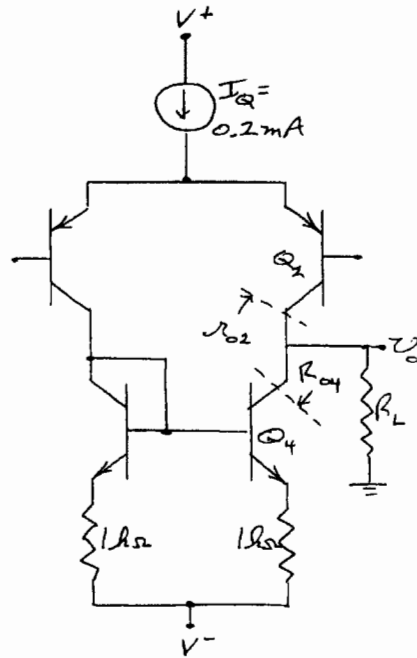11.45

Let  $\beta = 100$ ,  $V_A = 100 \text{ V}$



$$r_{o2} = \frac{V_A}{I_{CQ}} = \frac{100}{0.1} = 1000 \text{ k}\Omega$$

$$R_{o4} = r_{o4}[1 + g_m R'_E] \text{ where } R'_E = r_{\pi} \parallel R_E$$

Now

$$r_{\pi} = \frac{(100)(0.026)}{0.1} = 26 \text{ k}\Omega$$

$$g_m = \frac{0.1}{0.026} = 3.846 \text{ mA/V}$$

$$R'_E = 26 \parallel 1 = 0.963 \text{ k}\Omega$$

Then

$$R_{o4} = 1000[1 + (3.846)(0.963)] = 4704 \text{ k}\Omega$$

$$A_d = g_m(r_{o2} \parallel R_{o4}) = 3.846(1000 \parallel 4704) \Rightarrow$$

$$\underline{A_d = 3172}$$

11.46

$$\text{a. } A_d = g_m(r_{o2} \parallel r_{o4} \parallel R_L)$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{I_Q}{2V_T}$$

$$r_{o2} = \frac{V_{A2}}{I_{CQ}} = \frac{125}{I_{CQ}}$$

$$r_{o4} = \frac{V_{A4}}{I_{CQ}} = \frac{80}{I_{CQ}}$$

If  $I_Q = 2 \text{ mA}$ , then  $g_m = 38.46 \text{ mA/V}$

$$r_{o2} = 125 \text{ k}\Omega, r_{o4} = 80 \text{ k}\Omega$$

$$\text{So } A_d = 38.46[125 \parallel 80 \parallel 200]$$

$$\text{Or } A_d = 1508$$

For each gain of 1000, lower the current level

For  $I_Q = 0.60 \text{ mA}$ ,  $I_{CQ} = 0.30 \text{ mA}$

$$g_m = \frac{0.3}{0.026} = 11.54 \text{ mA/V}$$

$$r_{o2} = \frac{125}{0.3} = 417 \text{ k}\Omega$$

$$r_{o4} = \frac{80}{0.3} = 267 \text{ k}\Omega$$

$$A_d = 11.54[417 \parallel 267 \parallel 200] = 1036$$

So  $I_Q = 0.60 \text{ mA}$  is adequate

b. For  $V^+ = 10 \text{ V}$ ,  $V_{BE} = V_{EB} = 0.6 \text{ V}$

For  $V_{CB} = 0$ ,

$$v_{cm}(\text{max}) = V^+ - 2V_{BE} = 10 - 2(0.6)$$

$$\text{Or } v_{cm}(\text{max}) = 8.8 \text{ V}$$

11.48

a. From symmetry,

$$V_{GS3} = V_{GS4} = V_{DS3} = V_{DS4} = \sqrt{\frac{0.1}{0.1}} + 1$$

$$\text{Or } V_{DS3} = V_{DS4} = 2 \text{ V}$$

$$V_{SG1} = V_{SG2} = \sqrt{\frac{0.1}{0.1}} + 1 = 2 \text{ V}$$

$$V_{SD1} = V_{SD2} = V_{SG1} - (V_{DS3} - 10) = 2 - (2 - 10)$$

$$\text{Or } V_{SD1} = V_{SD2} = 10 \text{ V}$$

$$\text{b. } r_{on} = \frac{1}{\lambda_n I_{DQ}} = \frac{1}{(0.01)(0.1)} \Rightarrow 1 \text{ M}\Omega$$

$$r_{op} = \frac{1}{\lambda_p I_{DQ}} = \frac{1}{(0.015)(0.1)} \Rightarrow 0.667 \text{ M}\Omega$$

$$g_m = 2K_p(V_{so} + V_{TP}) = 2(0.1)(2 - 1) = 0.2 \text{ mA/V}$$

$$A_d = g_m(r_{on} \parallel r_{op}) = (0.2)(1000 \parallel 667) \Rightarrow A_d = 80$$

$$\text{(c) } I_{D2} = I_{D1} = \frac{I_Q}{2} = 0.1 \text{ mA}$$

$$r_{o4} = \frac{1}{\lambda_n I_{D4}} = \frac{1}{(0.01)(0.1)} = 1000 \text{ k}\Omega$$

$$r_{o2} = \frac{1}{\lambda_p I_{D2}} = \frac{1}{(0.015)(0.1)} = 667 \text{ k}\Omega$$

$$R_o = r_{o2} \parallel r_{o4} = 667 \parallel 1000 = 400 \text{ k}\Omega$$

11.49

$$A_d = g_m(r_{o2} \parallel r_{o4})$$

$$g_m = 2\sqrt{k_n I_{DQ}} = 2\sqrt{(0.12)(0.075)} = 0.1897 \text{ mA/V}$$

$$r_{o2} = \frac{1}{\lambda_n I_{DQ}} = \frac{1}{(0.015)(0.075)} = 889 \text{ k}\Omega$$


$$r_{o4} = \frac{1}{\lambda_p I_{DQ}} = \frac{1}{(0.02)(0.075)} = 667 \text{ k}\Omega$$

$$A_d = (0.1897)(889 \parallel 667)$$

$$\Rightarrow A_d = 72.3$$

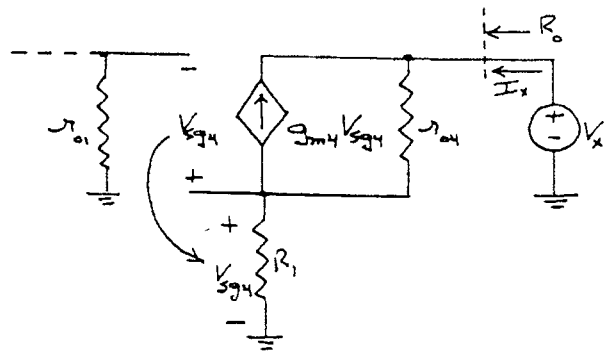11.50

Resistance looking into drain of  $M_4$ .



$$V_{sg4} = I_x R_1$$

$$I_x = g_{m4} V_{sg4} = \frac{V_x - V_{sg4}}{r_{o4}}$$

$$I_x \left[ 1 + g_{m4} R_1 + \frac{R_1}{r_{o4}} \right] = \frac{V_x}{r_{o4}}$$

$$\text{Or } R_o = r_{o4} \left[ 1 + g_{m4} R_1 + \frac{R_1}{r_{o4}} \right]$$

$$\text{a. } A_d = g_{m2}(r_{o2} \parallel R_o)$$

$$g_{m2} = 2\sqrt{K_n I_{DQ}} = 2\sqrt{(0.080)(0.1)} = 0.179 \text{ mA/V}$$

$$r_{o2} = \frac{1}{\lambda_n I_{DQ}} = \frac{1}{(0.015)(0.1)} = 667 \text{ k}\Omega$$

$$g_{m4} = 2\sqrt{K_p I_{DQ}} = 2\sqrt{(0.080)(0.1)} = 0.179 \text{ mA/V}$$

$$r_{o4} = \frac{1}{\lambda_p I_{DQ}} = \frac{1}{(0.02)(0.1)} = 500 \text{ k}\Omega$$

$$R_o = 500 \left[ 1 + (0.179)(1) + \frac{1}{500} \right] = 590.5 \text{ k}\Omega$$

$$A_d = (0.179)[667 \parallel 590.5]$$

$$\Rightarrow A_d = 56.06$$

b. When  $R_1 = 0$ ,  $R_o = r_{o4} = 500 \text{ k}\Omega$

$$A_d = (0.179)[667 \parallel 500]$$

$$\Rightarrow A_d = 51.15$$

(c) For part (a),  $R_o = r_{o2} \parallel R_o = 667 \parallel 590.5 \Rightarrow$

$$R_o = 313 \text{ k}\Omega$$

For part (b),  $R_o = r_{o2} \parallel r_{o4} = 667 \parallel 500 \Rightarrow$

$$R_o = 286 \text{ k}\Omega$$

11.51

$$(a) A_d = 100 = g_m(r_{o2} \parallel r_{o4})$$

$$\text{Let } I_Q = 0.5 \text{ mA}$$

$$r_{o2} = \frac{1}{\lambda_n I_D} = \frac{1}{(0.02)(0.25)} = 200 \text{ k}\Omega$$

$$r_{o4} = \frac{1}{\lambda_p I_D} = \frac{1}{(0.025)(0.25)} = 160 \text{ k}\Omega$$

Then

$$100 = g_m(200 \parallel 160) \Rightarrow g_m = 1.125 \text{ mA/V}$$

$$g_m = 2 \sqrt{\left(\frac{k'_n}{2}\right) \left(\frac{W}{L}\right) I_D}$$

$$1.125 = 2 \sqrt{\left(\frac{0.080}{2}\right) \left(\frac{W}{L}\right) (0.25)} \Rightarrow \left(\frac{W}{L}\right)_n = 31.6$$

Now  $\left(\frac{W}{L}\right)_p$  somewhat arbitrary. Let  $\left(\frac{W}{L}\right)_p = 31.6$

11.52

$$A_d = g_m(r_{o2} \parallel r_{o4})$$

$$P = (I_Q + I_{REF})(V^+ - V^-)$$

$$\text{Let } I_Q = I_{REF}$$

$$\text{Then } 0.5 = 2I_Q(3 - (-3)) \Rightarrow I_Q = I_{REF} = 0.0417 \text{ mA}$$

$$r_{o2} = \frac{1}{\lambda_n I_D} = \frac{1}{(0.015)(0.0208)} = 3205 \text{ k}\Omega$$

$$r_{o4} = \frac{1}{\lambda_p I_D} = \frac{1}{(0.02)(0.0208)} = 2404 \text{ k}\Omega$$

Then

$$A_d = 80 = g_m(3205 \parallel 2404) \Rightarrow g_m = 0.0582 \text{ mA/V}$$

$$g_m = 2 \sqrt{\left(\frac{k'_n}{2}\right) \left(\frac{W}{L}\right) I_D}$$

$$0.0582 = 2 \sqrt{\left(\frac{0.080}{2}\right) \left(\frac{W}{L}\right) (0.0208)} \Rightarrow$$

$$\left(\frac{W}{L}\right)_n = 1.02$$

11.53

$$A_d = g_m(r_{o2} \parallel R_o)$$

$$\text{Want } A_d = 400$$

From Example 11.15,  $r_{o2} = 1 \text{ M}\Omega$

Assuming that  $g_m = 0.283 \text{ mA/V}$  for the PMOS from Example 11.15, then  $R_o = 285 \text{ M}\Omega$ .

So

$$400 = g_m(1000 \parallel 285000) \Rightarrow$$

$$g_m = 0.4014 \text{ mA/V} = 2 \sqrt{\left(\frac{k'_n}{2}\right) \left(\frac{W}{L}\right) I_{DQ}}$$

$$0.4014 = \left(\frac{0.080}{2}\right) \left(\frac{W}{L}\right) (0.1) \Rightarrow$$

$$\left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2 = 10.1$$

11.54

$$A_d = g_m(R_{o4} \parallel R_{o6})$$

where

$$R_{o4} = r_{o4} + r_{o2}[1 + g_{m4}r_{o4}]$$

$$R_{o6} = r_{o6} + r_{o8}[1 + g_{m6}r_{o6}]$$

We have

$$r_{o2} = r_{o4} = \frac{1}{(0.015)(0.040)} = 1667 \text{ k}\Omega$$

$$r_{o6} = r_{o8} = \frac{1}{(0.02)(0.040)} = 1250 \text{ k}\Omega$$

$$g_{m4} = 2 \sqrt{\left(\frac{0.060}{2}\right) (15)(0.040)} = 0.268 \text{ mA/V}$$

$$g_{m6} = 2 \sqrt{\left(\frac{0.025}{2}\right) (10)(0.040)} = 0.141 \text{ mA/V}$$

Then

$$R_{o4} = 1667 + 1667[1 + (0.268)(1667)] \Rightarrow 748 \text{ M}\Omega$$

$$R_{o6} = 1250 + 1250[1 + (0.141)(1250)] \Rightarrow 222.8 \text{ M}\Omega$$

(a)

$$R_o = R_{o4} \parallel R_{o6} = 748 \parallel 222.8 \Rightarrow R_o = 172 \text{ M}\Omega$$

(b)

$$A_d = g_{m4}(R_{o4} \parallel R_{o6}) = (0.268)(172000) \Rightarrow$$

$$A_d = 46096$$


11.55

$$g_{m1} = 2 \sqrt{K_n I_{Bias1}} = 2 \sqrt{(0.2)(0.25)}$$

$$= 0.447 \text{ mA/V}$$

$$g_{m2} = \frac{I_{CQ}}{V_T} = \frac{0.75}{0.026} = 28.85 \text{ mA/V}$$
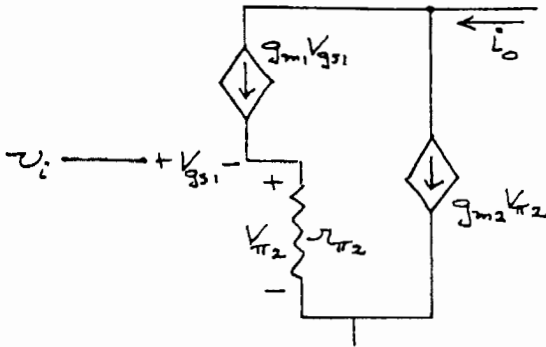
$$r_{\pi 2} = \frac{\beta V_T}{I_{CQ}} = \frac{(120)(0.026)}{0.75} = 4.16 \text{ k}\Omega$$



$$i_o = g_{m1}V_{gs1} + g_{m2}V_{\pi 2}$$

$$V_{\pi 2} = g_{m1}V_{gs1}r_{\pi 2} \text{ and } v_i = V_{gs1} + V_{\pi 2}$$

$$i_o = V_{gs1}(g_{m1} + g_{m2} \cdot g_{m1}r_{\pi 2})$$

$$v_i = V_{gs1} + g_{m1}V_{gs1}r_{\pi 2}$$

and  $V_{gs1} = \frac{v_i}{1 + g_{m1}r_{\pi 2}}$

$$i_o = v_i \cdot \frac{g_{m1}(1 + \beta)}{1 + g_{m1}r_{\pi 2}}$$

$$g_m^C = \frac{i_o}{v_i} = \frac{g_{m1}(1 + \beta)}{1 + g_{m1}r_{\pi 2}}$$

$$= \frac{(0.447)(121)}{1 + (0.447)(4.16)}$$

$$\Rightarrow \underline{g_m^C = 18.9 \text{ mA/V}}$$

11.56

$$r_o(M_2) = \frac{1}{\lambda_n I_{DQ}} = \frac{1}{(0.01)(0.2)} = 500 \text{ k}\Omega$$

$$r_o(Q_2) = \frac{V_A}{I_{CQ}} = \frac{80}{0.2} = 400 \text{ k}\Omega$$

$$g_m(M_2) = 2\sqrt{K_n I_{DQ}} = 2\sqrt{(0.2)(0.2)}$$

$$= 0.4 \text{ mA/V}$$


$$A_d = g_m(M_2)[r_o(M_2) \parallel r_o(Q_2)]$$

$$= 0.4[500 \parallel 400]$$

$$\Rightarrow \underline{A_d = 88.9}$$

If the  $I_Q$  current source is ideal,  
 $A_{cm} = 0$  and  $CMRR_{dB} = \infty$

11.57

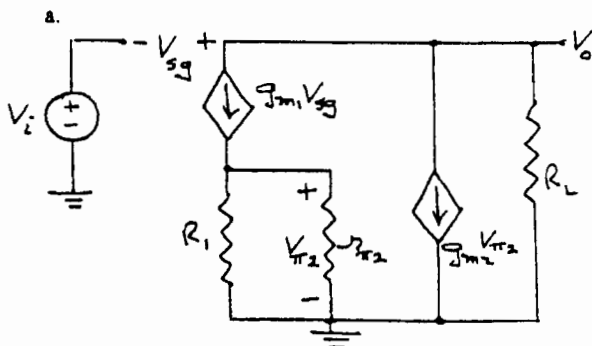

b. Assume  $R_L$  is capacitively coupled. Then

$$I_{CQ} + I_{DQ} = I_Q$$

$$I_{DQ} = \frac{V_{BE}}{R_1} = \frac{0.7}{8} = 0.0875 \text{ mA}$$

$$I_{CQ} = 0.9 - 0.0875 = 0.8125 \text{ mA}$$

$$g_{m1} = 2\sqrt{K_p I_{DQ}} = 2\sqrt{(1)(0.0875)}$$

$$\Rightarrow \underline{g_{m1} = 0.592 \text{ mA/V}}$$

$$g_{m2} = \frac{I_{CQ}}{V_T} = \frac{0.8125}{0.026} \Rightarrow \underline{g_{m2} = 31.25 \text{ mA/V}}$$

$$r_{\pi 2} = \frac{\beta V_T}{I_{CQ}} = \frac{(100)(0.026)}{0.8125} \Rightarrow \underline{r_{\pi 2} = 3.2 \text{ k}\Omega}$$

c.  $V_o = (-g_{m1}V_{sg} - g_{m2}V_{\pi 2})R_L$

$$V_i + V_{sg} = V_o \Rightarrow V_{sg} = V_o - V_i$$

$$V_{\pi 2} = (g_{m1}V_{sg})(R_1 \parallel r_{\pi 2})$$

$$V_o = -[g_{m1}V_{sg} + g_{m2}g_{m1}V_{sg}(R_1 \parallel r_{\pi 2})]R_L$$

$$V_o = -(V_o - V_i)[g_{m1} + g_{m2}g_{m1}(R_1 \parallel r_{\pi 2})]R_L$$

$$A_v = \frac{V_o}{V_i} = \frac{[g_{m1} + g_{m2}g_{m1}(R_1 \parallel r_{\pi 2})]R_L}{1 + [g_{m1} + g_{m2}g_{m1}(R_1 \parallel r_{\pi 2})]R_L}$$

We find

$$g_{m1} + g_{m2}g_{m1}(R_1 \parallel r_{\pi 2})$$

$$= 0.592 + (31.25)(0.592)(8 \parallel 3.2)$$

$$= 42.88$$

$$\text{Then } A_v = \frac{(42.88)(R_L)}{1 + (42.88)(R_L)}$$

11.58

a. Assume  $R_L$  is capacitively coupled.

$$I_{DQ} = \frac{0.7}{8} = 0.0875 \text{ mA}$$

$$I_{CQ} = 1.2 - 0.0875 = 1.11 \text{ mA}$$


$$g_{m1} = 2\sqrt{K_p I_{DQ}} = 2\sqrt{(1)(0.0875)}$$

$$\Rightarrow \underline{g_{m1} = 0.592 \text{ mA/V}}$$

$$g_{m2} = \frac{I_{CQ}}{V_T} = \frac{1.11}{0.026} \Rightarrow \underline{g_{m2} = 42.7 \text{ mA/V}}$$

$$r_{\pi 2} = \frac{\beta V_T}{I_{CQ}} = \frac{(100)(0.026)}{1.11} \Rightarrow \underline{r_{\pi 2} = 2.34 \text{ k}\Omega}$$

b.

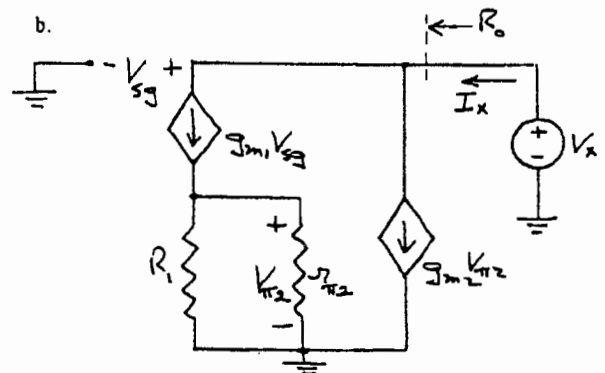

$$V_{ig} = V_X$$

$$I_X = g_{m2}V_{\pi 2} + g_{m1}V_{ig}$$

$$(g_{m1}V_{ig})(R_1 \parallel r_{\pi 2}) = V_{\pi 2}$$

$$I_X = V_X [g_{m1} + g_{m2}g_{m1}(R_1 \parallel r_{\pi 2})]$$


$$R_o = \frac{V_X}{I_X} = \frac{1}{g_{m1} + g_{m2}g_{m1}(R_1 \parallel r_{\pi 2})}$$

$$= \frac{1}{0.592 + (0.592)(42.7)(8 \parallel 2.34)}$$

$$\Rightarrow R_o = 21.6 \Omega$$

11.59

(a)

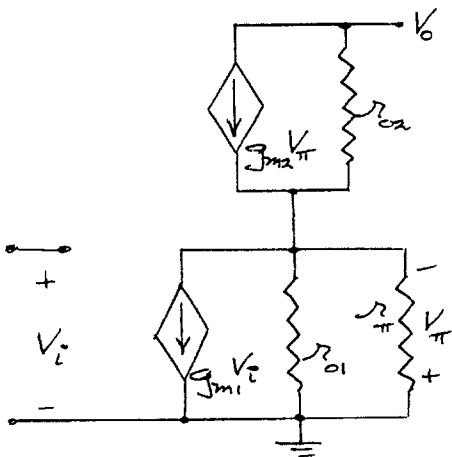

$$(1) g_{m2}V_{\pi} + \frac{V_o - (-V_{\pi})}{r_{o2}} = 0$$

$$(2) g_{m2}V_{\pi} + \frac{V_o - (-V_{\pi})}{r_{o2}} = g_{m1}V_i + \frac{-V_{\pi}}{r_{o1}} + \frac{-V_{\pi}}{r_{\pi}}$$

or

$$0 = g_{m1}V_i - V_{\pi} \left( \frac{1}{r_{o1}} + \frac{1}{r_{\pi}} \right)$$

Then

$$V_{\pi} = \frac{g_{m1}V_i}{\left( \frac{1}{r_{o1}} + \frac{1}{r_{\pi}} \right)}$$

From (1)

$$\left( g_{m2} + \frac{1}{r_{o2}} \right) V_{\pi} + \frac{V_o}{r_{o2}} = 0$$

$$V_o = -r_{o2} \left( g_{m2} + \frac{1}{r_{o2}} \right) V_{\pi} = -r_{o2} g_{m1} V_i \frac{\left( g_{m2} + \frac{1}{r_{o2}} \right)}{\left( \frac{1}{r_{o1}} + \frac{1}{r_{\pi}} \right)}$$

$$A_v = \frac{V_o}{V_i} = \frac{-g_{m1}r_{o2} \left( g_{m2} + \frac{1}{r_{o2}} \right)}{\left( \frac{1}{r_{o1}} + \frac{1}{r_{\pi}} \right)}$$

Now

$$g_{m1} = 2\sqrt{K_n I_Q} = 2\sqrt{(0.25)(0.025)} = 0.158 \text{ mA/V}$$

$$g_{m2} = \frac{I_Q}{V_T} = \frac{0.025}{0.026} = 0.9615 \text{ mA/V}$$

$$r_{o1} = \frac{1}{\lambda I_Q} = \frac{1}{(0.02)(0.025)} = 2000 \text{ k}\Omega$$

$$r_{o2} = \frac{V_A}{I_Q} = \frac{50}{0.025} = 2000 \text{ k}\Omega$$


$$r_{\pi} = \frac{\beta V_T}{I_Q} = \frac{(100)(0.026)}{0.025} = 104 \text{ k}\Omega$$

Then

$$A_v = \frac{-(0.158)(2000) \left( 0.9615 + \frac{1}{2000} \right)}{\left( \frac{1}{2000} + \frac{1}{104} \right)} \Rightarrow$$

$$A_v = -30039$$

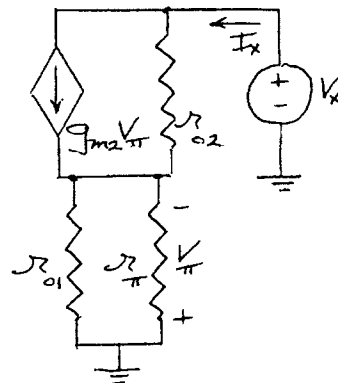To find  $R_o$ ; set  $V_i = 0 \Rightarrow g_{m1}V_i = 0$



$$I_x = g_{m2}V_{\pi} + \frac{V_x - (-V_{\pi})}{r_{o2}}$$

$$V_{\pi} = -I_x(r_{o1} \parallel r_{\pi})$$

Then

$$I_x = \left( g_{m2} + \frac{1}{r_{o2}} \right) (-I_x)(r_{o1} \parallel r_{\pi}) + \frac{V_x}{r_{o2}}$$


Combining terms,

$$R_o = \frac{V_x}{I_x} = r_{o2} \left[ 1 + (r_{o1} \parallel r_{\pi}) \left( g_{m2} + \frac{1}{r_{o2}} \right) \right]$$

$$= 2000 \left[ 1 + (2000 \parallel 104) \left( 0.9615 + \frac{1}{2000} \right) \right] \Rightarrow$$

$$R_o = 192.2 \text{ M}\Omega$$

(b)

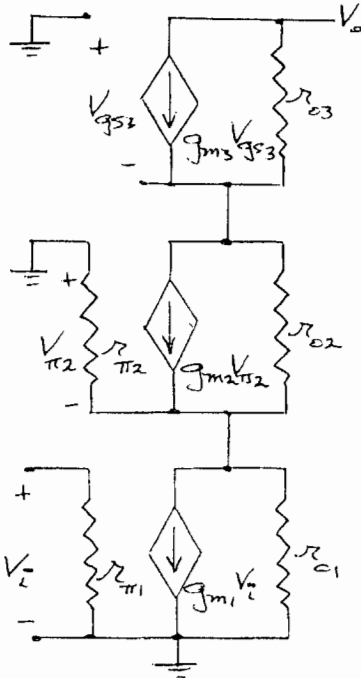

$$(1) g_{m3}V_{gs3} + \frac{V_o - (-V_{gs3})}{r_{o3}} = 0$$

$$(2) g_{m3}V_{gs3} + \frac{V_o - (-V_{gs3})}{r_{o3}} = g_{m2}V_{gs2} + \frac{-V_{gs3} - (-V_{gs2})}{r_{o2}}$$

or

$$0 = V_{gs2} \left( g_{m2} + \frac{1}{r_{o2}} \right) - \frac{V_{gs3}}{r_{o2}}$$

$$(3) \frac{V_{gs2}}{r_{gs2}} + g_{m2}V_{gs2} + \frac{-V_{gs3} - (-V_{gs2})}{r_{o2}} = g_{m1}V_i + \frac{(-V_{gs2})}{r_{o1}}$$

$$\text{From (2), } V_{gs2} = \frac{V_{gs3}}{r_{o2} \left( g_{m2} + \frac{1}{r_{o2}} \right)}$$

Then

$$(3) V_{gs2} \left( \frac{1}{r_{gs2}} + g_{m2} + \frac{1}{r_{o2}} + \frac{1}{r_{o1}} \right) = g_{m1}V_i + \frac{V_{gs3}}{r_{o2}}$$

or

$$\frac{V_{gs3}}{r_{o2} \left( g_{m2} + \frac{1}{r_{o2}} \right)} \left[ \frac{1}{r_{gs2}} + g_{m2} + \frac{1}{r_{o2}} + \frac{1}{r_{o1}} \right] = g_{m1}V_i + \frac{V_{gs3}}{r_{o2}}$$

$$\frac{V_{gs3}}{2000 \left( 0.9615 + \frac{1}{2000} \right)} \left[ \frac{1}{104} + 0.9615 + \frac{1}{2000} + \frac{1}{2000} \right] = 0.9615V_i + \frac{V_{gs3}}{2000}$$

$$\text{Then } V_{gs3} = 1.83 \times 10^5 V_i$$


From (1),

$$\left( g_{m3} + \frac{1}{r_{o3}} \right) V_{gs3} = \frac{-V_o}{r_{o3}}$$

or

$$V_o = -2000 \left( 0.158 + \frac{1}{2000} \right) (1.83 \times 10^5) V_i$$
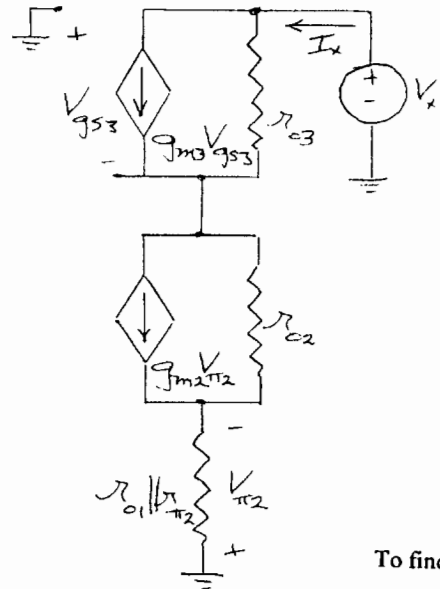
$$A_v = \frac{V_o}{V_i} = -5.80 \times 10^7$$



To find  $R_o$

$$(1) I_x = g_{m3}V_{gs3} + \frac{V_x - (-V_{gs3})}{r_{o3}}$$

$$(2) g_{m3}V_{gs3} + \frac{V_x - (-V_{gs3})}{r_{o3}} = g_{m2}V_{gs2} + \frac{-V_{gs3} - (-V_{gs2})}{r_{o2}}$$

$$(3) V_{gs2} = -I_x(r_{o1} \parallel r_{gs2})$$

$$\text{From (1) } I_x = V_{gs3} \left( g_{m3} + \frac{1}{r_{o3}} \right) + \frac{V_x}{r_{o3}}$$

$$I_x = V_{gs3} \left( 0.158 + \frac{1}{2000} \right) + \frac{V_x}{2000}$$

So

$$V_{gs3} = \frac{I_x - \frac{V_x}{2000}}{0.1585}$$

From (2),

$$V_{gs3} \left[ g_{m3} + \frac{1}{r_{o3}} + \frac{1}{r_{o2}} \right] + \frac{V_x}{r_{o3}} = V_{gs2} \left( g_{m2} + \frac{1}{r_{o2}} \right)$$

$$V_{gs3} \left[ 0.158 + \frac{1}{2000} + \frac{1}{2000} \right] + \frac{V_x}{2000} = V_{gs2} \left( 0.9615 + \frac{1}{2000} \right)$$

Then

$$\left[ \frac{I_x - V_x/2000}{0.1585} \right] (0.159) + \frac{V_x}{2000} = -I_x (2000 \parallel 104) (0.962)$$

We find

$$R_o = \frac{V_x}{I_x} = 6.09 \times 10^{10} \Omega$$

11.60

Assume emitter of  $Q_1$  is capacitively coupled to signal ground.

$$I_{CQ} = 0.2 \left( \frac{80}{81} \right) = 0.1975 \text{ mA}$$


$$I_{DQ} = \frac{0.2}{81} = 0.00247 \text{ mA}$$

$$r_\pi = \frac{(80)(0.026)}{0.1975} = 10.5 \text{ k}\Omega$$

$$g_m(Q_1) = \frac{0.1975}{0.026} = 7.60 \text{ mA/V}$$

$$g_m(M_1) = 2\sqrt{K_n I_D} = 2\sqrt{(0.2)(0.00247)}$$

$$g_m(M_1) = 0.0445 \text{ mA/V}$$

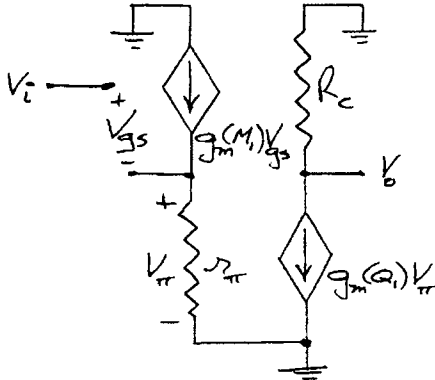

$$V_i = V_{gs} + V_\pi \text{ and } V_\pi = g_m(M_1) V_{gs} r_\pi$$

or

$$V_{gs} = \frac{V_\pi}{g_m(M_1) r_\pi}$$

Then

$$V_i = V_\pi \left( 1 + \frac{1}{g_m(M_1) r_\pi} \right)$$

or

$$V_\pi = \frac{V_i}{\left( 1 + \frac{1}{g_m(M_1) r_\pi} \right)}$$

$$V_o = -g_m(Q_1) V_\pi R_c \Rightarrow$$

$$A_v = \frac{V_o}{V_i} = \frac{-g_m(Q_1) R_c}{\left( 1 + \frac{1}{g_m(M_1) r_\pi} \right)}$$

Then

$$A_v = \frac{-(7.60)(20)}{\left( 1 + \frac{1}{(0.0445)(10.5)} \right)} \Rightarrow$$

$$A_v = -48.4$$

11.61

Using the results from Chapter 4 for the emitter-follower:

$$R_o = R_A \parallel \left[ \frac{r_{\pi 8} + \frac{r_{\pi 9} + r_{o7} + R_{o11}}{1 + \beta}}{1 + \beta} \right]$$

$$r_{\pi 8} = \frac{\beta V_T}{I_{C8}} = \frac{(100)(0.026)}{1} = 2.6 \text{ k}\Omega$$

$$I_{C9} \approx \frac{I_{C8}}{\beta} = \frac{1}{100} = 0.01 \text{ mA}$$

$$r_{\pi 9} = \frac{(100)(0.026)}{0.01} = 260 \text{ k}\Omega$$

$$r_{o7} = \frac{V_A}{I_Q} = \frac{100}{0.2} = 500 \text{ k}\Omega$$

$$r_{o11} = \frac{V_A}{I_Q} = \frac{100}{0.2} = 500 \text{ k}\Omega$$

$$R_{o11} = r_{o11} [1 + g_m R'_E], \quad g_m = \frac{0.2}{0.026} = 7.69$$

$$r_{\pi 11} = \frac{(100)(0.026)}{0.2} = 13 \text{ k}\Omega$$

$$R'_E = 0.2 \parallel 13 = 0.197 \text{ k}\Omega$$

$$R_{o11} = 500 [1 + (7.69)(0.197)] = 1257 \text{ k}\Omega$$

Then

$$R_o = 5 \parallel \left[ \frac{2.6 + \frac{260 + 500 + 1257}{101}}{101} \right]$$

$$= 5 \parallel 0.223$$

$$\Rightarrow R_o = 0.213 \text{ k}\Omega$$

11.62

$$R_i = r_{\pi 1} + (1 + \beta) r_{\pi 2}$$


$$r_{\pi 2} = \frac{(100)(0.026)}{0.5} = 5.2 \text{ k}\Omega$$

$$r_{\pi 1} = \frac{(100)(0.026)}{(0.5/100)} = \frac{(100)^2(0.026)}{0.5} = 520 \text{ k}\Omega$$

$$R_i = 520 + (101)(5.2) \Rightarrow R_i \approx 1.05 \text{ M}\Omega$$

$$R_o = 5 \parallel \frac{r_{\pi 3} + 50}{101}, \quad r_{\pi 3} = \frac{(100)(0.026)}{1} = 2.6 \text{ k}\Omega$$
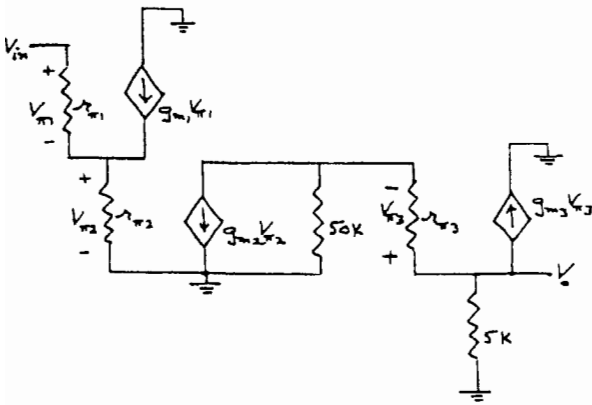
$$R_o = 5 \parallel \frac{2.6 + 50}{101} = 5 \parallel 0.521 \Rightarrow R_o = 0.472 \text{ k}\Omega$$



$$V_o = -\left(\frac{V_{\pi3}}{r_{\pi3}} + g_{m3}V_{\pi3}\right) (5) \quad (1)$$

$$V_o = -V_{\pi3} \left(\frac{1 + \beta}{r_{\pi3}}\right) (5) \quad (2)$$

$$\frac{V_{\pi3}}{r_{\pi3}} = g_{m2}V_{\pi2} + \frac{(V_o - V_{\pi3})}{50} \quad (3)$$

$$g_{m2}V_{\pi2} = V_{\pi3} \left(\frac{1}{r_{\pi3}} + \frac{1}{50}\right) - \frac{V_o}{50} \quad (4)$$

$$V_{\pi2} = \left(\frac{V_{\pi1}}{r_{\pi1}} + g_{m1}V_{\pi1}\right) r_{\pi2} = V_{\pi1} \left(\frac{1 + \beta}{r_{\pi1}}\right) r_{\pi2} \quad (5)$$

and

$$V_{in} = V_{\pi1} + V_{\pi2} \quad (6)$$

$$g_{m2} = \frac{0.5}{0.026} = 19.23 \text{ mA/V} \quad (7)$$

Then

$$V_o = -V_{\pi3} \left(\frac{101}{2.6}\right) (5) \quad (8)$$

$$\Rightarrow V_{\pi3} = -V_o(0.005149) \quad (9)$$

And

$$19.23V_{\pi2} = -V_o(0.005149) \left(\frac{1}{2.6} + \frac{1}{50}\right) - \frac{V_o}{50} = -V_o(0.02208) \quad (10)$$

$$\text{Or } V_{\pi2} = -V_o(0.001148) \quad (11)$$

And

$$V_{\pi1} = V_{in} - V_{\pi2} = V_{in} + V_o(0.001148) \quad (12)$$

So

$$-V_o(0.001148)$$

$$= [V_{in} + V_o(0.001148)] \left(\frac{101}{520}\right) (5.2) \quad (13)$$

$$-V_o(0.001148) - V_o(0.001159) = V_{in}(1.01)$$


$$\Rightarrow A_v = \frac{V_o}{V_{in}} = -438$$

11.63

$$I_2 = \frac{5}{5} = 1 \text{ mA}$$

$$V_{GS2} = \sqrt{\frac{1}{0.5}} + 0.8 = 2.21 \text{ V}$$
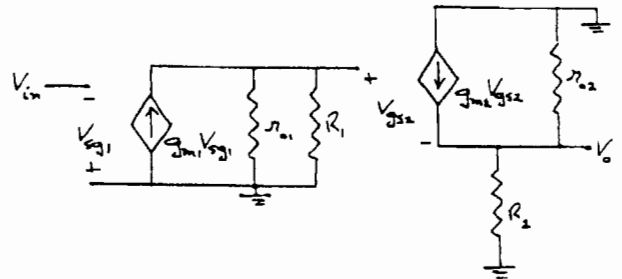
$$I_1 = \frac{2.21 - (-5)}{35} = 0.206 \text{ mA}$$



$$V_o = (g_{m2}V_{gs2})(R_2 \parallel r_{o2})$$

$$V_{gs2} = (g_{m1}V_{gs1})(r_{o1} \parallel R_1) - V_o$$

$$\text{and } V_{gs1} = -V_{in} \quad (1)$$

So

$$V_{gs2} = -(g_{m1}V_{in})(r_{o1} \parallel R_1) - V_o$$

Then

$$V_o = g_{m2}(R_2 \parallel r_{o2})[-(g_{m1}V_{in})(r_{o1} \parallel R_1) - V_o]$$

$$A_v = \frac{V_o}{V_{in}} = \frac{-g_{m2}(R_2 \parallel r_{o2})g_{m1}(r_{o1} \parallel R_1)}{1 + g_{m2}(R_2 \parallel r_{o2})}$$

$$g_{m2} = 2\sqrt{K_{n2}I_{D2}} = 2\sqrt{(0.5)(1)} = 1.414 \text{ mA/V}$$

$$g_{m1} = 2\sqrt{K_{p1}I_{D1}} = 2\sqrt{(0.2)(0.206)} = 0.406 \text{ mA/V}$$

$$r_{o1} = \frac{1}{\lambda_1 I_{D1}} = \frac{1}{(0.01)(0.206)} = 485 \text{ k}\Omega$$

$$r_{o2} = \frac{1}{\lambda_2 I_{D2}} = \frac{1}{(0.01)(1)} = 100 \text{ k}\Omega$$

$$R_2 \parallel r_{o2} = 5 \parallel 100 = 4.76 \text{ k}\Omega$$

$$R_1 \parallel r_{o1} = 35 \parallel 485 = 32.6 \text{ k}\Omega$$

Then

$$A_v = \frac{-(1.414)(4.76)(0.406)(32.6)}{1 + (1.414)(4.76)}$$

So

$$\Rightarrow A_v = -11.5$$

Output Resistance—From the results for a source follower in Chapter 6.

$$R_o = \frac{1}{g_{m2}} \parallel R_2 \parallel r_{o2} = \frac{1}{1.414} \parallel 5 \parallel 100$$

$$= 0.707 \parallel 4.76$$

So  $R_o = 0.616 \text{ k}\Omega$


11.64

a.  $R_2 = \frac{5}{0.5} \Rightarrow R_2 = 10 \text{ k}\Omega$

$$V_{sg2} = \sqrt{\frac{I_{D2}}{K_{p2}}} - V_{TP2} = \sqrt{\frac{0.5}{0.25}} + 1 = 2.41 \text{ V}$$

$$R_1 = \frac{5 - (-2.41)}{0.1} \Rightarrow R_1 = 74.1 \text{ k}\Omega$$

b.

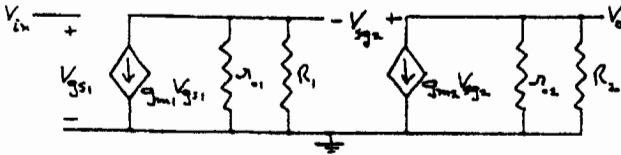

$$V_o = -(g_{m2} V_{sg2})(r_{o2} \parallel R_2)$$

$$V_{sg2} = V_o - [-(g_{m1} V_{gs1})(r_{o1} \parallel R_1)]$$

and  $V_{gs1} = V_{in}$

$$A_v = \frac{V_o}{V_{in}} = \frac{-(g_{m2})(r_{o2} \parallel R_2)(g_{m1})(r_{o1} \parallel R_1)}{1 + (g_{m2})(r_{o2} \parallel R_2)}$$

$$g_{m1} = 2\sqrt{K_{n1}I_{D1}} = 2\sqrt{(0.1)(0.1)} = 0.2 \text{ mA/V}$$

$$g_{m2} = 2\sqrt{K_{p2}I_{D2}} = 2\sqrt{(0.25)(0.5)} = 0.707 \text{ mA/V}$$

$$r_{o1} = \frac{1}{\lambda_1 I_{D1}} = \frac{1}{(0.01)(0.1)} = 1000 \text{ k}\Omega$$

$$r_{o2} = \frac{1}{\lambda_2 I_{D2}} = \frac{1}{(0.01)(0.5)} = 200 \text{ k}\Omega$$

$$r_{o2} \parallel R_2 = 200 \parallel 10 = 9.52 \text{ k}\Omega$$

$$r_{o1} \parallel R_1 = 1000 \parallel 74.1 = 69.0 \text{ k}\Omega$$

Then

$$A_v = \frac{-(0.707)(9.52)(0.2)(69)}{1 + (0.707)(9.52)}$$

So

$$\Rightarrow A_v = -12.0$$

$$R_o = \frac{1}{g_{m2}} \parallel R_2 \parallel r_{o2} = \frac{1}{0.707} \parallel 10 \parallel 200$$

$$= 1.414 \parallel 9.52$$

Or  $R_o = 1.23 \text{ k}\Omega$

11.65

a.  $I_{C2} = 0.25 \text{ mA}$

$$R = \frac{5 - 2}{0.25} \Rightarrow R = 12 \text{ k}\Omega$$

$$I_{C3} = \frac{v_{o2} - V_{BE(on)}}{R_{E1}} \Rightarrow R_{E1} = \frac{2 - 0.7}{0.5}$$

$$\Rightarrow R_{E1} = 2.6 \text{ k}\Omega$$

$$R_C = \frac{5 - v_{o3}}{I_{C3}} = \frac{5 - 3}{0.5} \Rightarrow R_C = 4 \text{ k}\Omega$$

$$I_{C4} = \frac{[v_{o3} - V_{BE(on)}] - (-5)}{R_{E2}}$$

$$R_{E2} = \frac{3 - 0.7 + 5}{3} \Rightarrow R_{E2} = 2.43 \text{ k}\Omega$$

b. Input resistance to base of  $Q_3$ .

$$R_{i3} = r_{\pi 3} + (1 + \beta)R_{E1}$$

$$r_{\pi 3} = \frac{(100)(0.026)}{0.5} = 5.2 \text{ k}\Omega$$

$$R_{i3} = 5.2 + (101)(2.6) = 267.8 \text{ k}\Omega$$

$$A_{d1} = \frac{v_{o2}}{v_d} = \frac{1}{2}g_{m2}(R \parallel R_{i3})$$

$$g_{m2} = \frac{0.25}{0.026} = 9.62 \text{ mA/V}$$

$$A_{d1} = \frac{1}{2}(9.62)(12 \parallel 267.8) \Rightarrow A_{d1} = 55.2$$

$$\text{Now } \frac{v_{o3}}{v_{o2}} = \frac{-\beta(R_C \parallel R_{i4})}{r_{\pi 3} + (1 + \beta)R_{E1}}$$

where  $R_{i4} = r_{\pi 4} + (1 + \beta)R_{E2}$

$$\text{and } \frac{v_o}{v_{o3}} = \frac{(1 + \beta)R_{E2}}{r_{\pi 4} + (1 + \beta)R_{E2}}$$

$$r_{\pi 4} = \frac{(100)(0.026)}{3} = 0.867 \text{ k}\Omega$$

$$\frac{v_o}{v_{o3}} = \frac{(101)(2.43)}{0.867 + (101)(2.43)} = 0.9965$$

$$R_{i4} = 0.867 + (101)(2.43) = 246.3 \text{ k}\Omega$$

$$r_{\pi 3} = 5.2 \text{ k}\Omega$$

So

$$\frac{v_{o3}}{v_{o2}} = \frac{-(100)(4 \parallel 246.3)}{5.2 + (101)(2.6)} = -1.47$$

So

$$A_d = \frac{v_o}{v_d} = (55.2)(0.9965)(-1.47)$$

$$\Rightarrow A_d = -80.9$$

c. Using Equation (11.32b)

$$A_{cm1} = \frac{-g_{m2}(R \parallel R_{i3})}{1 + \frac{2(1 + \beta)R_o}{r_{\pi 2}}}$$

$$r_{\pi 2} = \frac{(100)(0.026)}{0.25} = 10.4 \text{ k}\Omega$$

$$A_{cm1} = \frac{-(9.62)(12 \parallel 267.8)}{1 + \frac{2(101)(100)}{10.4}} = -0.0569 = A_{cm1}$$

Then

$$A_{cm} = \left( \frac{v_0}{v_{03}} \right) \left( \frac{v_{03}}{v_{02}} \right) \cdot A_{cm1}$$

$$= (0.9965)(-1.47)(-0.0569)$$

$$\Rightarrow \underline{A_{cm} = 0.08335}$$

$$CMRR_{dB} = 20 \log_{10} \left( \frac{80.9}{0.08335} \right)$$

$$\Rightarrow \underline{CMRR_{dB} = 59.7 \text{ dB}}$$

11.66

a.  $R_{C1} = \frac{10 - v_{01}}{I_{C1}} = \frac{10 - 2}{0.1} \Rightarrow \underline{R_{C1} = 80 \text{ k}\Omega}$

$$R_{C2} = \frac{10 - v_{04}}{I_{C4}} = \frac{10 - 6}{0.2} \Rightarrow \underline{R_{C2} = 20 \text{ k}\Omega}$$

b.  $A_{d1} = \frac{v_{01} - v_{02}}{v_d} = -g_{m1}(R_{C1} \parallel r_{\pi3})$

$$g_{m1} = \frac{0.1}{0.026} = 3.846 \text{ mA/V}$$

$$r_{\pi3} = \frac{(180)(0.026)}{0.2} = 23.4 \text{ k}\Omega$$

$$A_{d1} = -(3.846)(80 \parallel 23.4) \Rightarrow \underline{A_{d1} = -69.6}$$

$$A_{d2} = \frac{v_{04}}{v_{01} - v_{02}} = \frac{1}{2} g_{m4} R_{C2}$$

$$g_{m4} = \frac{0.2}{0.026} = 7.692 \text{ mA/V}$$

$$A_{d2} = \frac{1}{2}(7.692)(20) = 76.9$$

Then  $A_d = (76.9)(-69.6)$

$$\Rightarrow \underline{A_d = -5352}$$

11.67

a. Neglect the effect of  $r_0$  in determining the differential-mode gain.

$$A_{d1} = \frac{v_{02}}{v_d} = \frac{1}{2} g_{m2}(R_C \parallel R_{i3})$$

where  $R_{i3} = r_{\pi3} + (1 + \beta)R_E$

$$A_2 = \frac{-\beta R_{C2}}{r_{\pi3} + (1 + \beta)R_E}$$

$$I_1 = \frac{12 - 0.7 - (-12)}{R_1} = \frac{23.3}{12} = 1.94 \text{ mA} \approx I_{C3}$$

$$g_{m2} = \frac{\frac{1}{2}(1.94)}{0.026} = 37.3 \text{ mA/V}$$

$$r_{\pi3} = \frac{(200)(0.026)}{I_{C3}}$$

$$v_{02} = 12 - \frac{1}{2}(1.94)(8) = 4.24 \text{ V}$$

$$I_{C3} = \frac{4.24 - 0.7}{3.3} = 1.07 \text{ mA}$$

$$r_{\pi3} = \frac{(200)(0.026)}{1.07} = 4.86 \text{ k}\Omega$$

$$R_{i3} = 4.86 + (201)(3.3) = 668 \text{ k}\Omega$$

$$A_{d1} = \frac{1}{2}(37.3)[8 \parallel 668] = 147.4$$

$$A_2 = \frac{-(200)(4)}{4.86 + (201)(3.3)} = -1.197$$

Then

$$A_d = A_{d1} \cdot A_2 = (147.4)(-1.197) \Rightarrow \underline{A_d = -176}$$

$$R_0 = r_{05} = \frac{V_A}{I_{C5}} = \frac{80}{1.94} = 41.2 \text{ k}\Omega$$

$$A_{cm1} = \frac{-g_{m2}(R_C \parallel R_{i3})}{1 + \frac{2(1 + \beta)R_0}{r_{\pi2}}}$$

$$r_{\pi2} = \frac{(200)(0.026)}{\frac{1}{2}(1.94)} = 5.36 \text{ k}\Omega$$

$$A_{cm1} = \frac{-(37.3)(8 \parallel 668)}{1 + \frac{2(201)(41.2)}{5.36}} = -0.09539$$

$$A_2 = -1.197$$

$$A_{cm} = (-0.09539)(-1.197) \Rightarrow \underline{A_{cm} = 0.114}$$

b.  $v_d = v_1 - v_2 = 2.015 \sin \omega t - 1.985 \sin \omega t$

$$v_d = 0.03 \sin \omega t \text{ (V)}$$

$$v_{cm} = \frac{v_1 + v_2}{2} = 2.0 \sin \omega t$$

$$v_{03} = A_d v_d + A_{cm} v_{cm}$$

$$= (-176)(0.03) + (0.114)(2)$$

Or

$$\underline{v_{03} = -5.052 \sin \omega t}$$

Ideal,  $A_{cm} = 0$

So

$$v_{03} = A_d v_d = (-176)(0.03)$$

$$\underline{v_{03} = -5.28 \sin \omega t}$$

c.  $R_{id} = 2r_{\pi2} = 2(5.36) \Rightarrow \underline{R_{id} = 10.72 \text{ k}\Omega}$

$$2R_{icm} \approx 2(1 + \beta)R_0 \parallel (1 + \beta)r_0$$

$$r_0 = \frac{V_A}{I_{C2}} = \frac{80}{\frac{1}{2}(1.94)} = 82.5 \text{ k}\Omega$$

$$2R_{icm} = [2(201)(41.2)] \parallel [(201)(82.5)]$$

$$= 16.6 \text{ M}\Omega \parallel 16.6 \text{ M}\Omega$$

So

$$\Rightarrow \underline{R_{icm} = 4.15 \text{ M}\Omega}$$

11.68

$$a. \quad I_1 = \frac{24 - V_{GS4}}{R_1} = k_n(V_{GS4} - V_{TN})^2$$

$$24 - V_{GS4} = (55)(0.2)(V_{GS4} - 2)^2$$

$$24 - V_{GS4} = 11(V_{GS4}^2 - 4V_{GS4} + 4)$$

$$11V_{GS4}^2 - 43V_{GS4} + 20 = 0$$

$$V_{GS4} = \frac{43 \pm \sqrt{(43)^2 - 4(11)(20)}}{2(11)} = 3.37 \text{ V}$$

$$I_1 = \frac{24 - 3.37}{55} = 0.375 \text{ mA} = I_Q$$

$$v_{o2} = 12 - \left(\frac{0.375}{2}\right)(40) = 4.5 \text{ V}$$

$$\frac{v_{o2} - V_{GS3}}{R_5} = I_{D3} = k_n(V_{GS3} - V_{TN})^2$$

$$4.5 - V_{GS3} = (0.2)(6)(V_{GS3}^2 - 4V_{GS3} + 4)$$

$$1.2V_{GS3}^2 - 3.8V_{GS3} + 0.3 = 0$$

$$V_{GS3} = \frac{3.8 \pm \sqrt{(3.8)^2 - 4(1.2)(0.3)}}{2(1.2)} = 3.09 \text{ V}$$

$$I_{D3} = \frac{4.5 - 3.09}{6} = 0.235 \text{ mA}$$

$$g_{m2} = 2\sqrt{K_n I_{D2}} = 2\sqrt{(0.2)\left(\frac{0.375}{2}\right)}$$

$$= 0.387 \text{ mA/V}$$

$$A_{d1} = \frac{1}{2}g_{m2}R_D = \frac{1}{2}(0.387)(40)$$

$$\Rightarrow A_{d1} = 7.74$$

$$A_2 = \frac{-g_{m3}R_{D2}}{1 + g_{m3}R_5}$$

$$g_{m3} = 2\sqrt{K_n I_{D3}} = 2\sqrt{(0.2)(0.235)}$$

$$= 0.434 \text{ mA/V}$$

$$A_2 = \frac{-(0.434)(4)}{1 + (0.434)(6)} = -0.482$$

$$\text{So } A_d = A_{d1} \cdot A_2 = (7.74)(-0.482)$$

$$\Rightarrow A_d = -3.73$$

$$R_o = r_{o3} = \frac{1}{\lambda I_Q} = \frac{1}{(0.02)(0.375)} = 133 \text{ k}\Omega$$

$$A_{cm1} = \frac{-g_{m2}R_D}{1 + 2g_{m2}R_o} = \frac{-(0.387)(40)}{1 + 2(0.387)(133)}$$

$$= -0.149$$

$$A_{cm} = (-0.149)(-0.482) \Rightarrow A_{cm} = 0.0718$$

$$b. \quad v_d = v_1 - v_2 = 0.3 \sin \omega t$$

$$v_{cm} = \frac{v_1 + v_2}{2} = 2 \sin \omega t$$

$$v_{o3} = A_d v_d + A_{cm} v_{cm}$$

$$= (-3.73)(0.3) + (0.0718)(2)$$

$$\Rightarrow v_{o3} = -0.975 \sin \omega t \text{ (V)}$$

Ideal,  $A_{cm} = 0$ 

$$v_{o3} = A_d v_d = (-3.73)(0.3)$$

Or

$$\Rightarrow v_{o3} = -1.12 \sin \omega t \text{ (V)}$$

11.69

The low-frequency, one-sided differential gain is

$$A_{v2} = \frac{v_{o2}}{v_d} = \frac{1}{2}g_m R_C \left( \frac{r_\pi}{r_\pi + R_B} \right)$$

$$= \frac{\frac{1}{2} \cdot \beta R_C}{r_\pi + R_B}$$

$$r_\pi = \frac{(100)(0.026)}{0.5} = 5.2 \text{ k}\Omega$$

$$A_{v2} = \frac{\frac{1}{2} \cdot (100)(10)}{5.2 + 0.5} \Rightarrow A_{v2} = 87.7$$

$$C_M = C_\mu(1 + g_m R_C)$$

$$g_m = \frac{0.5}{0.026} = 19.23 \text{ mA/V}$$

$$C_M = 2[1 + (19.23)(10)] \Rightarrow C_M = 387 \text{ pF}$$

$$f_H = \frac{1}{2\pi[r_\pi \| R_B](C_\pi + C_M)}$$

$$= \frac{1}{2\pi[5.2 \| 0.5] \times 10^3 \times (8 + 387) \times 10^{-12}}$$

So

$$\Rightarrow f_H = 883 \text{ kHz}$$

11.70

a. From Equation (11.117),

$$f_Z = \frac{1}{2\pi R_o C_o} = \frac{1}{2\pi(5 \times 10^6)(0.8 \times 10^{-12})}$$

$$\text{Or } f_Z = 39.8 \text{ kHz}$$

b. From Problem 11.69,  $f_H = 883 \text{ kHz}$ . From Equation (11.116(b)), the low-frequency common-mode gain is

$$A_{cm} = \frac{-g_m R_C}{\left[ \left(1 + \frac{R_B}{r_\pi}\right) + \frac{2(1 + \beta)R_o}{r_\pi} \right]}$$

$$r_\pi = 5.2 \text{ k}\Omega, g_m = 19.23 \text{ mA/V}$$

So



$$A_{cm} = \frac{-(19.23)(10)}{\left[ \left(1 + \frac{0.5}{5.2}\right) + \frac{2(101)(5 \times 10^6)}{5.2 \times 10^3} \right]}$$

$$= -9.9 \times 10^{-4}$$

$$CMRR_{dB} = 20 \log_{10} \left( \frac{87.7}{9.9 \times 10^{-4}} \right) = 98.9 \text{ dB}$$

11.72

The differential-mode half circuit is:

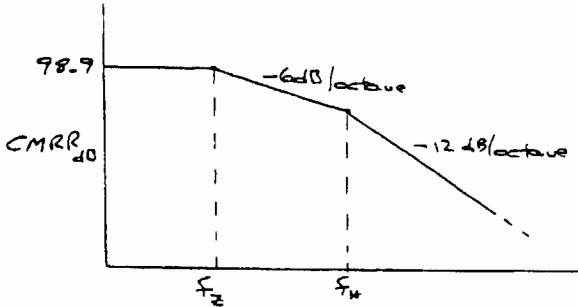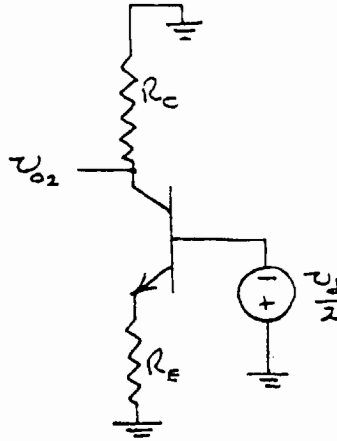

11.71

a. From Equation (7.72),

$$f_T = \frac{g_m}{2\pi(C_\pi + C_\mu)}$$

$$g_m = \frac{1}{0.026} = 38.46 \text{ mA/V}$$

Then

$$800 \times 10^6 = \frac{38.46 \times 10^{-3}}{2\pi(C_\pi + C_\mu)}$$

Or

$$C_\pi + C_\mu = 7.65 \times 10^{-12} \text{ F} = 7.65 \text{ pF}$$

And  $C_\pi = 6.65 \text{ pF}$

$$C_M = C_\mu(1 + g_m R_C) = 1[1 + (38.46)(10)]$$

$$= 386 \text{ pF}$$

$$f_H = \frac{1}{2\pi[r_\pi || R_B](C_\pi + C_M)}$$

$$r_\pi = \frac{(120)(0.026)}{1} = 3.12 \text{ k}\Omega$$

$$f_H = \frac{1}{2\pi[3.12 || 1] \times 10^3 \times (6.65 + 386) \times 10^{-12}}$$

Or

$$f_H = 535 \text{ kHz}$$

b. From Equation (11.117),

$$f_z = \frac{1}{2\pi R_0 C_0} = \frac{1}{2\pi(10 \times 10^6)(10^{-12})}$$

Or

$$f_z = 15.9 \text{ kHz}$$

$$v_{o2} = \frac{g_m \left(\frac{v_d}{2}\right) R_C}{1 + \left(\frac{1 + \beta}{r_\pi}\right) R_E} \text{ or } A_v = \frac{\left(\frac{1}{2}\right) \beta R_C}{r_\pi + (1 + \beta) R_E}$$

$$r_\pi = \frac{(100)(0.026)}{0.5} = 5.2 \text{ k}\Omega$$

$$A_v = \frac{\left(\frac{1}{2}\right)(100)(10)}{5.2 + (101)R_E} = \frac{500}{5.2 + (101)R_E}$$

- a. For  $R_E = 0.1 \text{ k}\Omega$  :  $A_v = 32.7$
- b. For  $R_E = 0.25 \text{ k}\Omega$  :  $A_v = 16.4$

## Chapter 12

## Exercise Solutions

E12.1

$$a. \quad A_f = \frac{A}{1 + A\beta}$$

$$1 + A\beta = \frac{A}{A_f} \Rightarrow A\beta = \frac{A}{A_f} - 1$$

$$\beta = \frac{1}{A_f} - \frac{1}{A} = \frac{1}{20} - \frac{1}{10^4} = 0.05 - 0.0001$$

$$\Rightarrow \beta = 0.0499$$

$$b. \quad \frac{A_f}{(1/\beta)} = \frac{20}{(1/0.0499)} = \frac{20}{20.040} = 0.998$$

E12.2

$$A_f = \frac{A}{1 + A\beta}$$

$$A_f + A_f A\beta = A$$

$$A_f = A(1 - A_f\beta)$$

$$A = \frac{A_f}{1 - A_f\beta} = \frac{80}{1 - (80)(0.0120)}$$

$$\underline{A = 2000}$$

E12.3

$$A_f = \frac{A}{1 + A\beta}$$

$$\beta = \frac{1}{A_f} - \frac{1}{A} = \frac{1}{100} - \frac{1}{10^6} = 0.01 - 10^{-6}$$

$$\beta = 0.009999$$

$$\frac{dA_f}{A_f} = \frac{1}{(1 + \beta A)} \cdot \frac{dA}{A} = \left(\frac{A_f}{A}\right) \cdot \frac{dA}{A}$$

$$\frac{dA_f}{A_f} = \left(\frac{100}{10^6}\right)(20)\%$$

$$\Rightarrow \frac{dA_f}{A_f} = 0.002\%$$

E12.4

$$\frac{dA_f}{A_f} = \frac{1}{(1 + \beta A)} \cdot \frac{dA}{A} = \left(\frac{A_f}{A}\right) \cdot \frac{dA}{A}$$

$$\frac{dA}{A} = \frac{dA_f}{A_f} \cdot \left(\frac{A}{A_f}\right) = (0.001) \left(\frac{5 \times 10^5}{100}\right)$$

$$\Rightarrow \frac{dA}{A} = \pm 5\%$$

E12.5

$$\text{Bandwidth} = \omega_H(1 + \beta A_0)$$

$$= \omega_H \left(\frac{A_0}{A_f}\right) = (2\pi)(10) \left(\frac{10^5}{100}\right)$$

$$\omega = (2\pi)(10^4) \text{ rad/sec} \Rightarrow f = 10 \text{ kHz}$$

E12.6

$$A_f \cdot f_H = A_0 \cdot f_i$$

$$A_f = \frac{A_0 \cdot f_i}{f_H} = \frac{(10^6)(8)}{250 \times 10^3}$$

$$\Rightarrow \underline{A_f(0) = 32}$$

E12.7

$$a. \quad V_e = V_S - V_{fb} = 100 - 99 = 1 \text{ mV}$$

$$V_0 = A_v V_e \Rightarrow A_v = \frac{5}{0.001} \Rightarrow \underline{A_v = 5000 \text{ V/V}}$$

$$V_{fb} = \beta V_0 \Rightarrow \beta = \frac{V_{fb}}{V_0} = \frac{0.099}{5} \Rightarrow \underline{\beta = 0.0198 \text{ V/V}}$$

$$A_{vf} = \frac{A_v}{1 + \beta A_v} = \frac{5000}{1 + (0.0198)(5000)}$$

$$\Rightarrow \underline{A_{vf} = 50 \text{ V/V}}$$

$$b. \quad R_{if} = R_i(1 + \beta A_v) = (5)[1 + (0.0198)(5000)]$$

$$\Rightarrow \underline{R_{if} = 500 \text{ k}\Omega}$$

$$R_{of} = \frac{R_o}{1 + \beta A_v} = \frac{4}{1 + (0.0198)(5000)}$$

$$\Rightarrow \underline{R_{of} = 40 \Omega}$$

E12.8

$$a. \quad I_e = I_S - I_{fb} = 100 - 99 = 1 \mu\text{A}$$

$$A_i = \frac{I_o}{I_e} = \frac{5}{0.001} \Rightarrow \underline{A_i = 5000 \text{ A/A}}$$

$$\beta = \frac{I_{fb}}{I_o} = \frac{0.099}{5} \Rightarrow \underline{\beta = 0.0198 \text{ A/A}}$$

$$A_{if} = \frac{A_i}{1 + A_i\beta} = \frac{5000}{1 + (5000)(0.0198)}$$

$$\Rightarrow \underline{A_{if} = 50 \text{ A/A}}$$

$$b. \quad R_{if} = \frac{R_i}{1 + \beta A_i} = \frac{5}{1 + (0.0198)(5000)}$$

$$\Rightarrow \underline{R_{if} = 50 \Omega}$$

$$R_{of} = (1 + \beta A_i)R_o = [1 + (0.0198)(5000)](4)$$

$$\Rightarrow \underline{R_{of} = 400 \text{ k}\Omega}$$

E12.9

$$V_e = V_S - V_{fb} = 100 - 99 = 1 \text{ mV}$$

$$A_g = \frac{I_o}{V_e} = \frac{5 \text{ mA}}{1 \text{ mV}} \Rightarrow \underline{A_g = 5 \text{ A/V}}$$

$$\beta = \frac{V_{fb}}{I_o} = \frac{99 \text{ mV}}{5 \text{ mA}} \Rightarrow \underline{\beta = 19.8 \text{ V/A}}$$

$$A_{gf} = \frac{A_g}{1 + \beta A_g} = \frac{5}{1 + (19.8)(5)}$$

$$\Rightarrow \underline{A_{gf} = 0.05 \text{ A/V} = 50 \text{ mA/V}}$$

E12.10

$$I_e = I_S - I_{fb} = 100 - 99 = 1 \mu\text{A}$$

$$A_z = \frac{V_0}{I_e} = \frac{5 \text{ V}}{1 \mu\text{A}} \Rightarrow A_z = 5 \times 10^6 \text{ V/A}$$

$$\beta = \frac{I_{fb}}{V_0} = \frac{99 \mu\text{A}}{5 \text{ V}} \Rightarrow \beta = 1.98 \times 10^{-5} \text{ A/V}$$

$$A_{zf} = \frac{A_z}{1 + \beta A_z} = \frac{5 \times 10^6}{1 + (1.98 \times 10^{-5})(5 \times 10^6)} \Rightarrow A_{zf} = 5 \times 10^4 \text{ V/A} = 50 \text{ V/mA}$$

E12.11

$$A_{vf} = \frac{A_v}{1 + \frac{A_v}{1 + (R_2/R_1)}} = \frac{10^4}{1 + \frac{10^4}{1 + (30/10)}} \Rightarrow A_{vf} = 3.9984$$

$$A_{vf} = \frac{10^5}{1 + \frac{10^5}{1 + (30/10)}} = 3.99984$$

$$\frac{3.99984 - 3.9984}{3.9984} \times 100\% \Rightarrow 0.0360\%$$

E12.12

a.  $r_\pi = \frac{h_{FE} V_T}{I_{CQ}} = \frac{(100)(0.026)}{0.5} = 5.2 \text{ k}\Omega$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.5}{0.026} = 19.23 \text{ mA/V}$$

$$A_{vf} = \frac{\left(\frac{1}{r_\pi} + g_m\right) R_E}{1 + \left(\frac{1}{r_\pi} + g_m\right) R_E} = \frac{\left(\frac{1}{5.2} + 19.23\right)(2)}{1 + \left(\frac{1}{5.2} + 19.23\right)(2)} = \frac{(19.42)(2)}{1 + (19.42)(2)} \Rightarrow A_{vf} = 0.97490$$

$$R_{if} = r_\pi + (1 + h_{FE})R_E = 5.2 + (101)(2) \Rightarrow R_{if} = 207.2 \text{ k}\Omega$$

$$R_{of} = R_E \parallel \frac{r_\pi}{1 + h_{FE}} = 2 \parallel \frac{5.2}{101} \Rightarrow R_{of} = 0.0502 \text{ k}\Omega \Rightarrow 50.2 \Omega$$

b.  $h_{FE} = 150 \Rightarrow r_\pi = 7.8 \text{ k}\Omega, g_m = 19.23 \text{ mA/V}$

$$A_{vf} = \frac{\left(\frac{1}{7.8} + 19.23\right)(2)}{1 + \left(\frac{1}{7.8} + 19.23\right)(2)} = \frac{(19.36)(2)}{1 + (19.36)(2)}$$


$$A_{vf} = 0.97482 \Rightarrow 0.0082\% \text{ change in } A_{vf}$$

$$R_{if} = 7.8 + (101)(2) = 209.8 \text{ k}\Omega \Rightarrow 1.25\% \text{ change in } R_{if}$$

$$R_{of} = R_E \parallel \frac{r_\pi}{1 + h_{FE}} = 2 \parallel \frac{7.8}{151} = 2 \parallel 0.0517$$

$$R_{of} = 50.4 \Omega \Rightarrow 0.397\% \text{ change in } R_{of}$$

E12.13

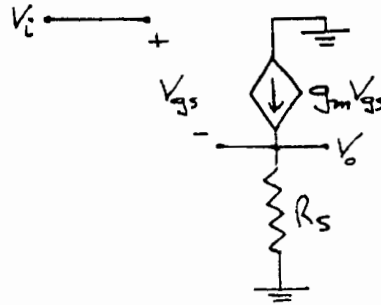

$$V_0 = (g_m V_{gs}) R_S$$

$$V_i = V_{gs} + g_m R_S V_{gs}$$


$$V_{gs} = \frac{V_i}{1 + g_m R_S}$$

$$g_m = 2\sqrt{K_n I_{DQ}} = 2\sqrt{(0.2)(0.25)} = 0.447 \text{ mA/V}$$

$$A_{vf} = \frac{V_0}{V_i} = \frac{g_m R_S}{1 + g_m R_S}$$

$$A_{vf} = \frac{(0.447)(5)}{1 + (0.447)(5)} \Rightarrow A_{vf} = 0.691$$

$$R_{if} = \infty$$

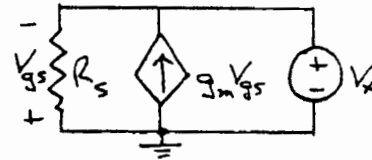

$$I_X = g_m V_{gs} = \frac{V_X}{R_S}$$

$$V_{gs} = -V_X$$

$$I_X = V_X \left( g_m + \frac{1}{R_S} \right)$$

$$R_{of} = \frac{1}{g_m} \parallel R_S = \frac{1}{0.447} \parallel 5$$

$$R_{of} = 1.55 \text{ k}\Omega$$

E12.15

$$i_o = \left( \frac{h_{FE}}{1 + h_{FE}} \right) \left( \frac{R_E}{R_E + \frac{r_\pi}{1 + h_{FE}}} \right) i_i$$

$$r_\pi = \frac{(80)(0.026)}{0.5} = 4.16 \text{ k}\Omega$$

Then

$$\frac{r_\pi}{1 + h_{FE}} = \frac{4.16}{81} = 0.0514 \text{ k}\Omega$$

Then we want



E12.22

dc analysis:

$$\frac{10 - V_0}{4.7} = I_D + \frac{V_0}{47 + 20} \tag{1}$$

$$I_D = K_n(V_{GS} - V_{TN})^2 \tag{2}$$

$$V_{GS} = \left(\frac{20}{20 + 47}\right)V_0 = 0.2985V_0 \tag{3}$$

$$2.13 - V_0(0.213) = I_D + (0.0149)V_0 \tag{1}$$

$$I_D = 2.13 - V_0(0.2279)$$

From (2):

$$2.13 - V_0(0.2279) = 1[(0.2985V_0) - 1.5]^2$$

$$2.13 - V_0(0.2279) = 0.0891V_0^2 - 0.8955V_0 + 2.25$$

$$0.0891V_0^2 - 0.6676V_0 + 0.12 = 0$$

$$V_0 = \frac{0.6676 \pm \sqrt{(0.6676)^2 - 4(0.0891)(0.12)}}{2(0.0891)}$$

$$V_0 = 7.31 \text{ V}$$


$$I_D = \frac{10 - 7.31}{4.7} - \frac{7.31}{67} = 0.572 - 0.109$$

$$I_D = 0.463 \text{ mA}$$

$$V_{GS} = \sqrt{\frac{0.463}{1}} + 1.5 = 2.18$$

a.  $g_m = 2K_n(V_{GS} - V_{TN}) = 2(1)(2.18 - 1.5)$

$$\Rightarrow g_m = 1.36 \text{ mA/V}$$

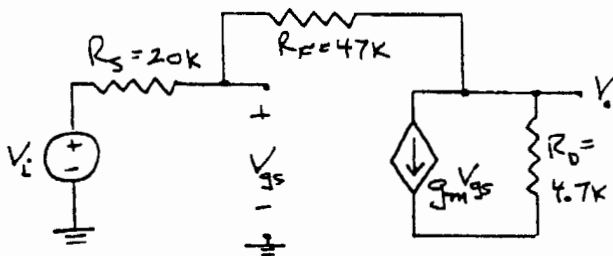

$$\frac{V_0}{R_D} + g_m V_{gs} + \frac{V_0 - V_{gs}}{R_F} = 0 \tag{1}$$

$$\frac{V_{gs} - V_i}{R_S} + \frac{V_{gs} - V_0}{R_F} = 0 \tag{2}$$

$$V_{gs} \left(\frac{1}{R_S} + \frac{1}{R_F}\right) = \frac{V_0}{R_F} + \frac{V_i}{R_S}$$

$$V_{gs} \left(\frac{1}{20} + \frac{1}{47}\right) = \frac{V_0}{47} + \frac{V_i}{20}$$

$$V_{gs}(0.0713) = V_0(0.0213) + V_i(0.050)$$

$$V_{gs} = V_0(0.299) + V_i(0.701)$$

From (1):

$$\frac{V_0}{4.7} + (1.36)V_{gs} + \frac{V_0}{47} - \frac{V_{gs}}{47} = 0$$

$$V_0(0.213) + (1.36)V_{gs}$$

$$+ V_0(0.0213) - V_{gs}(0.0213) = 0$$

$$V_0(0.234) + V_{gs}(1.34) = 0$$

$$V_0(0.234) + (1.34)[V_0(0.299) + V_i(0.701)] = 0$$

$$V_0(0.635) + V_i(0.939) = 0$$

$$\Rightarrow A_{vf} = \frac{V_0}{V_i} = -1.48$$

b. For  $K_n = 1.5 \text{ mA/V}^2$

From dc analysis:

$$2.13 - V_0(0.2279) = 1.5[(0.2985V_0) - 1.5]^2$$

$$= 1.5[0.0891V_0^2 - 0.8955V_0 + 2.25]$$

$$= 0.1337V_0^2 - 1.343V_0 + 3.375$$

$$0.1337V_0^2 - 1.115V_0 + 1.245 = 0$$

$$V_0 = \frac{1.115 \pm \sqrt{(1.115)^2 - 4(0.1337)(1.245)}}{2(0.1337)}$$

$$V_0 = \frac{1.115 \pm 0.7597}{2(0.1337)} \Rightarrow V_0 = 7.01 \text{ V}$$

$$I_D = \frac{10 - 7.01}{4.7} - \frac{7.01}{67} = 0.636 - 0.105$$

$$I_D = 0.531 \text{ mA}$$

$$V_{GS} = \sqrt{\frac{0.531}{1.5}} + 1.5 = 2.09$$

$$g_m = 2K_n(V_{GS} - V_{TN}) = 2(1.5)(2.09 - 1.5)$$

$$= 1.77 \text{ mA/V}$$

From ac analysis:

$$\frac{V_0}{4.7} + (1.77)V_{gs} + \frac{V_0}{47} - \frac{V_{gs}}{47} = 0$$

$$V_0(0.213) + (1.77)V_{gs}$$

$$+ V_0(0.0213) - V_{gs}(0.0213) = 0$$

$$V_0(0.234) + V_{gs}(1.75) = 0$$

$$V_0(0.234) + (1.75)[V_0(0.299) + V_i(0.701)] = 0$$


$$V_0(0.757) + V_i(1.23) = 0$$

$$\Rightarrow A_{vf} = \frac{V_0}{V_i} = -1.62$$

$$\% \text{ change} = \frac{1.62 - 1.48}{1.48} \Rightarrow 9.46\%$$

E12.23

a. Input resistance.

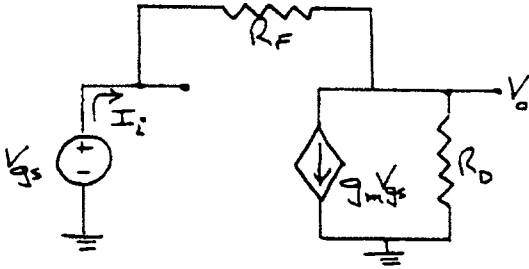

$$\frac{V_o}{R_D} + g_m V_{gs} + \frac{V_o - V_{gs}}{R_F} = 0 \quad (1)$$

$$I_i = \frac{V_{gs} - V_o}{R_F} \quad (2)$$

So  $V_o = V_{gs} - I_i R_F$

$$V_o \left( \frac{1}{R_D} + \frac{1}{R_F} \right) + V_{gs} \left( g_m - \frac{1}{R_F} \right) = 0 \quad (1)$$


$$[V_{gs} - I_i(47)] \left( \frac{1}{4.7} + \frac{1}{47} \right) + V_{gs} \left( 1.36 - \frac{1}{47} \right) = 0$$

$$[V_{gs} - I_i(47)](0.234) + V_{gs}(1.34) = 0$$

$$V_{gs}(1.57) = I_i(11.0)$$

$$\Rightarrow R_{i_f} = \frac{V_{gs}}{I_i} = 7.0 \text{ k}\Omega$$

Output Resistance.

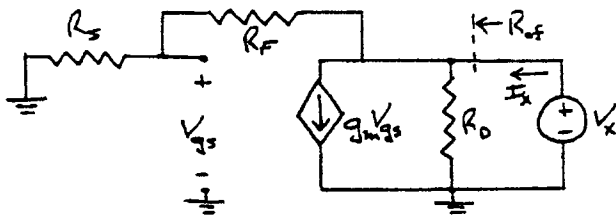

$$I_x = \frac{V_x}{R_D} + g_m V_{gs} + \frac{V_x}{R_S + R_F}$$

$$V_{gs} = \left( \frac{R_S}{R_S + R_F} \right) V_x = \left( \frac{20}{20 + 47} \right) V_x = 0.2985 V_x$$

$$I_x = \frac{V_x}{4.7} + (1.36)(0.2985)V_x + \frac{V_x}{20 + 47}$$

$$I_x = V_x [0.213 + 0.406 + 0.0149]$$

$$R_{o_f} = \frac{V_x}{I_x} = 1.58 \text{ k}\Omega$$

b. From part (a)

$$[V_{gs} - I_i(47)](0.234) + V_{gs} \left( 1.77 - \frac{1}{47} \right) = 0$$

$$V_{gs}(1.98) = I_i(11)$$

$$\Rightarrow R_{i_f} = \frac{V_{gs}}{I_i} = 5.56 \text{ k}\Omega$$

$$I_x = \frac{V_x}{4.7} + (1.77)(0.2985)V_x + \frac{V_x}{20 + 47}$$

$$I_x = V_x [0.213 + 0.528 + 0.0149]$$

$$\Rightarrow R_{o_f} = \frac{V_x}{I_x} = 1.32 \text{ k}\Omega$$

E12.25

$$V_{TH} = \left( \frac{5.5}{5.5 + 51} \right) (10) = 0.973 \text{ V}$$

$$R_{TH} = 5.5 \parallel 51 = 4.96 \text{ k}\Omega$$

$$I_{BQ} = \frac{0.973 - 0.7}{4.96 + (121)(1)} = 0.00217 \text{ mA}$$

$$I_{CQ} = 0.260 \text{ mA}$$

$$r_\pi = 12 \text{ k}\Omega, \quad g_m = 10 \text{ mA/V}$$

$$R_{eq} = R_S \parallel R_1 \parallel R_2 \parallel r_\pi = 10,000 \parallel 51 \parallel 5.5 \parallel 12 = 3.51 \text{ k}\Omega$$


From Equation (12.99(b)):

$$T = (g_m R_C) \left( \frac{R_{eq}}{R_C + R_F + R_{eq}} \right)$$

$$= (10)(10) \left( \frac{3.51}{10 + 82 + 3.51} \right)$$

$$\Rightarrow T = 3.68$$

E12.26

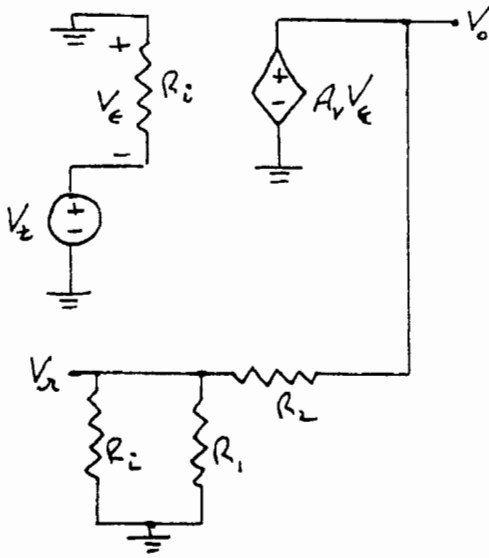

$$V_i = -V_x, \quad V_o = A_v V_i = -A_v V_x$$

$$V_x = \left( \frac{R_1 \parallel R_i}{R_1 \parallel R_i + R_2} \right) V_o = - \left( \frac{R_1 \parallel R_i}{R_1 \parallel R_i + R_2} \right) (A_v V_i)$$

$$T = -\frac{V_o}{V_i} = A_v \left( \frac{R_1 \parallel R_i}{R_1 \parallel R_i + R_2} \right)$$

or

$$T = \frac{A_v}{1 + \frac{R_2}{R_1 \parallel R_i}}$$

E12.27

$$T = A_i \beta = \frac{A_{i0} \beta}{\left(1 + j \cdot \frac{f}{f_1}\right)} = \frac{(10^5)(0.01)}{1 + j \cdot \left(\frac{f}{10}\right)}$$

$$|T(f_1)| = 1 = \frac{10^3}{\sqrt{1 + \left(\frac{f'_E}{10}\right)^2}}$$

$$1 + \left(\frac{f'_E}{10}\right)^2 = 10^6$$

$$f'_E = 10\sqrt{10^6 - 1} \Rightarrow f'_E \approx 10^4 \text{ Hz}$$

$$\begin{aligned} \text{Phase} = \phi &= -\tan^{-1}\left(\frac{f'_E}{10}\right) = -\tan^{-1}\left(\frac{10^4}{10}\right) \\ &= -\tan^{-1}(10^3) \end{aligned}$$

$$\phi \approx 90^\circ$$

$$\text{Phase Margin} = 180 - 90 \Rightarrow \underline{\text{Phase Margin} = 90^\circ}$$

E12.28

$$T = A_i \beta = \frac{A_{i0} \beta}{\left(1 + j \cdot \frac{f}{f_1}\right) \left(1 + j \cdot \frac{f}{f_2}\right)}$$

$$\text{Phase} = -\left[\tan^{-1}\left(\frac{f}{f_1}\right) + \tan^{-1}\left(\frac{f}{f_2}\right)\right]$$

$$\text{Phase Margin} = 60^\circ \Rightarrow \text{Phase} = -120^\circ$$

$$-120^\circ = -\left[\tan^{-1}\left(\frac{f}{10^4}\right) + \tan^{-1}\left(\frac{f}{10^5}\right)\right]$$

$$\text{At } f' = 7.66 \times 10^4 \text{ Hz,}$$

$$\text{Phase} = -\left[\tan^{-1}(7.66) + \tan^{-1}(0.766)\right]$$

$$= -[82.56 + 37.45]$$

$$= -120^\circ$$

$$\begin{aligned} |T(f')| = 1 &= \frac{(10^5) \beta}{\sqrt{1 + (7.66)^2} \times \sqrt{1 + (0.766)^2}} \\ 1 &= \frac{(10^5) \beta}{(7.725)(1.26)} \Rightarrow \underline{\beta = 9.73 \times 10^{-5}} \end{aligned}$$

E12.29

$$\text{Phase} = -180^\circ = -3 \tan^{-1}\left(\frac{f'}{10^5}\right)$$

$$\text{or } \tan^{-1}\left(\frac{f'}{10^5}\right) = 60^\circ \Rightarrow f' = 1.732 \times 10^5 \text{ Hz}$$

$$\begin{aligned} |T(f')| = 1 &= \frac{\beta(100)}{\left[\sqrt{1 + \left(\frac{f'}{10^5}\right)^2}\right]^3} \\ &= \frac{\beta(100)}{\left[\sqrt{1 + (1.732)^2}\right]^3} \\ &\Rightarrow \underline{\beta = 0.08} \end{aligned}$$

E12.30

$$\text{Phase Margin} = 60^\circ \Rightarrow \text{Phase} = -120^\circ$$

$$\text{Phase} = -120^\circ = -3 \tan^{-1}\left(\frac{f'}{10^5}\right)$$

$$\tan^{-1}\left(\frac{f'}{10^5}\right) = 40^\circ \Rightarrow f' = 0.839 \times 10^5 \text{ Hz}$$

$$\begin{aligned} |T(f')| = 1 &= \frac{\beta(100)}{\left[\sqrt{1 + \left(\frac{f'}{10^5}\right)^2}\right]^3} \\ &= \frac{\beta(100)}{\left[\sqrt{1 + (0.839)^2}\right]^3} \\ &\Rightarrow \underline{\beta = 0.0222} \end{aligned}$$

E12.31

The new loop gain function is

$$T'(f) = \frac{10^5}{\left(1 + j \cdot \frac{f}{f_{PD}}\right) \left(1 + j \cdot \frac{f}{5 \times 10^5}\right)} \times \frac{1}{\left(1 + j \cdot \frac{f}{10^7}\right) \left(1 + j \cdot \frac{f}{5 \times 10^8}\right)}$$

$$\text{Phase} = -\left\{ \tan^{-1}\left(\frac{f}{f_{PD}}\right) + \tan^{-1}\left(\frac{f}{5 \times 10^5}\right) + \tan^{-1}\left(\frac{f}{10^7}\right) + \tan^{-1}\left(\frac{f}{5 \times 10^8}\right) \right\}$$

For a phase margin  $45^\circ \Rightarrow \text{Phase} = -135^\circ$ , the poles are far apart so this will occur at approximately  $f' = 5 \times 10^5$  Hz. Then

$$|T'(f)| = 1 = \frac{10^5}{\sqrt{1 + \left(\frac{5 \times 10^5}{f_{PD}}\right)^2} \times \sqrt{1+1} \times \sqrt{1} \times \sqrt{1}}$$

$$1 = \frac{10^5}{(1.414) \sqrt{1 + \left(\frac{5 \times 10^5}{f_{PD}}\right)^2}}$$

$$1 + \left(\frac{5 \times 10^5}{f_{PD}}\right)^2 = 5 \times 10^9$$

$$f_{PD} \approx \frac{5 \times 10^5}{\sqrt{5 \times 10^9}} \Rightarrow \underline{f_{PD} = 7.07 \text{ Hz}}$$

E12.32

Phase Margin =  $45^\circ \Rightarrow \text{Phase} = -135^\circ$

This will occur at approximately  $f' = 10^7$  Hz

$$|T'(f)| = 1 = \frac{10^5}{\sqrt{1 + \left(\frac{10^7}{f_{PD}}\right)^2} \times \sqrt{2} \times \sqrt{1}}$$

$$1 + \left(\frac{10^7}{f_{PD}}\right)^2 = 5 \times 10^9$$

$$f_{PD} \approx \frac{10^7}{\sqrt{5 \times 10^9}} \Rightarrow \underline{f_{PD} = 141 \text{ Hz}}$$

E12.33

$$A_f(0) = \frac{A_0}{1 + \beta A_0} = \frac{2 \times 10^5}{1 + (0.05)(2 \times 10^5)}$$

$$\Rightarrow \underline{A_f(0) \approx 20}$$

$$f_C = f_{PD}(1 + \beta A_0) = 100[1 + (0.05)(2 \times 10^5)]$$

$$\Rightarrow \underline{f_C \approx 1 \text{ MHz}}$$



## Chapter 12

### Problem Solutions

12.1

a.  $A_f = \frac{A}{1 + A\beta}$

$$80 = \frac{10^5}{1 + (10^5)\beta} \Rightarrow 1 + (10^5)\beta = \frac{10^5}{80}$$

$$\Rightarrow \beta = \frac{\frac{10^5}{80} - 1}{10^5} \Rightarrow \underline{\beta = 0.01249}$$

b.  $\frac{dA_f}{A_f} = \left(\frac{A_f}{A}\right) \cdot \frac{dA}{A} = \frac{80}{10^5}(-20)$

or

$$\frac{dA_f}{A_f} = -0.016\%$$

$$A_f = 80 - (0.00016)80 \Rightarrow \underline{A_f \approx 79.99}$$

c.  $80 = \frac{10^3}{1 + (10^3)\beta}$

$$\beta = \frac{\frac{10^3}{80} - 1}{10^3} \Rightarrow \underline{\beta = 0.0115}$$

$$\frac{dA_f}{A_f} = \left(\frac{80}{10^3}\right)(-20) \Rightarrow \frac{dA_f}{A_f} = -1.6\%$$

$$A_f = 80 - (0.016)(80) \Rightarrow \underline{A_f = 78.72}$$

12.2

a.  $A_f = \frac{(A)^3}{1 + (A)^3\beta}$

$$100 = \frac{1000}{1 + (1000)\beta} \Rightarrow \beta = \frac{\frac{1000}{100} - 1}{1000} \Rightarrow \underline{\beta = 0.009}$$

b. A goes from 10 to 11 so

$$A_f = \frac{(11)^3}{1 + (11)^3(0.009)} = \frac{1331}{1 + (1331)(0.009)}$$

or

$$A_f = 102.55$$

so

$$\frac{\Delta A_f}{A_f} = \frac{2.55}{100} \Rightarrow \underline{2.55\% \text{ change}}$$

12.3

(a)  $V_o = (-10)(-15)(-20)V_e = -3000V_e$

$$V_e = \beta V_o + V_s$$

$$\text{So } V_o = -3000(\beta V_o + V_s)$$

We find

$$A_v = \frac{V_o}{V_s} = \frac{-3000}{1 + 3000\beta}$$

For  $A_v = -120 = \frac{-3000}{1 + 3000\beta} \Rightarrow \underline{\beta = 0.008}$


(b) Now  $V_o = (-9)(-13.5)(-18)V_e = -2187V_e$

Then

$$A_v = \frac{-2187}{1 + 2187\beta} = \frac{-2187}{1 + 2187(0.008)} = -118.24$$

$$\% \text{ change} = \frac{120 - 118.24}{120} \times 100 \Rightarrow \underline{1.47\% \text{ change}}$$

12.4

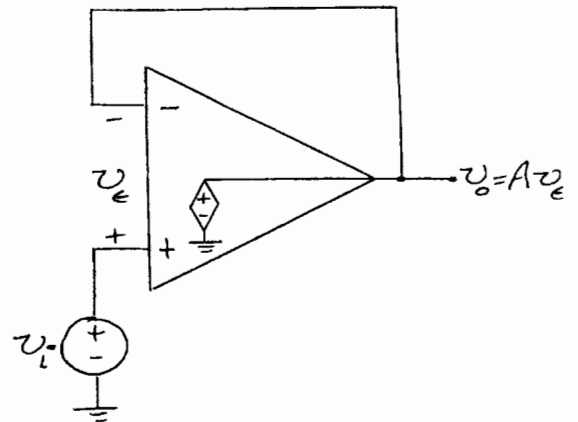

$$v_o = v_i - v_e \Rightarrow v_e = v_i - v_o$$

Then  $v_o = A(v_i - v_o) = Av_i - Av_o$

And

$$v_o(1 + A) = Av_i$$

so

$$\frac{v_o}{v_i} = \frac{A}{1 + A} = 0.9998 \Rightarrow \underline{A = 4999}$$

12.5

$$(10^5)(4) = (50)f_B \Rightarrow \underline{f_B = 8 \text{ kHz}}$$

12.6

(a)  $(50)f_{3-dB} = (10^5)(4) \Rightarrow \underline{f_{3-dB} = 8 \text{ kHz}}$

(b)  $(10)f_{3-dB} = (10^5)(4) \Rightarrow \underline{f_{3-dB} = 40 \text{ kHz}}$

12.7

$$(50)(20 \times 10^3) = 5A_0 \text{ so } \underline{A_0 = 2 \times 10^5}$$




12.8

$$v_o = A_1 A_2 v_i + A_1 v_n$$

$$v_o = (100)v_i + (1)v_n = (100)(10) + (1)(1)$$

$$\Rightarrow \underline{\frac{S_o}{N_o} = \frac{1000}{1} = 1000}$$

12.9

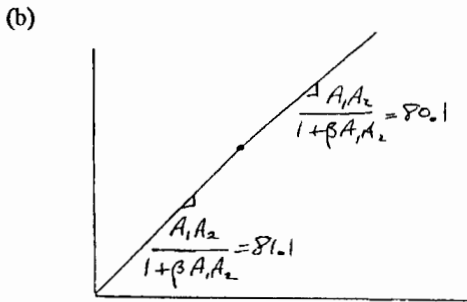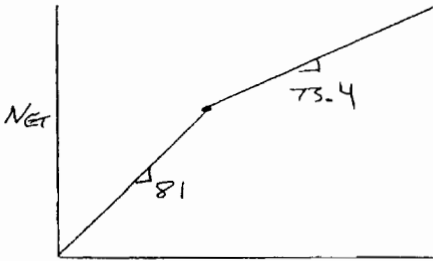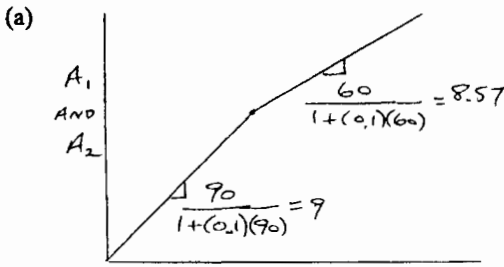

Circuit (b) – less distortion

12.10

- (a) Low input  $R \Rightarrow$  Shunt input  
Low output  $R \Rightarrow$  Shunt output  
Or a Shunt-Shunt circuit
- (b) High input  $R \Rightarrow$  Series input  
High output  $R \Rightarrow$  Series output  
Or a Series-Series circuit
- (c) Shunt-Series circuit
- (d) Series-Shunt circuit

12.11

(a)  $R_i(\max) = R_i(1+T) = 10(1+10^4) \Rightarrow$   
 $R_i(\max) \cong 10^5 \text{ k}\Omega$

$R_i(\min) = \frac{R_i}{1+T} = \frac{10}{1+10^4} \cong 10^{-3} \text{ k}\Omega$   
 Or  $R_i(\min) = 1 \Omega$


(b)  $R_o(\max) = R_o(1+T) = 1(1+10^4) \Rightarrow$   
 $R_o(\max) \cong 10^4 \text{ k}\Omega$

$R_o(\min) = \frac{R_o}{1+T} = \frac{1}{1+10^4} \cong 10^{-4} \text{ k}\Omega$   
 Or  $R_o(\min) = 0.1 \Omega$

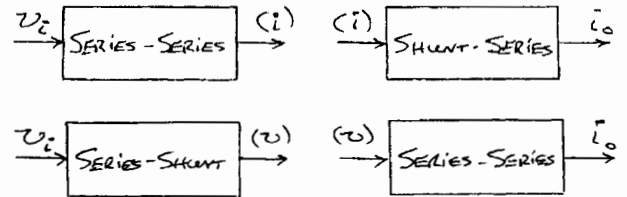12.12


Overall Transconductance Amplifier,  $A_x = \frac{i_o}{v_i}$

Series output = current signal and Shunt input = current signal. Also, Shunt output = voltage signal and Series input = voltage signal. Two possible solutions are shown.



12.13

a.

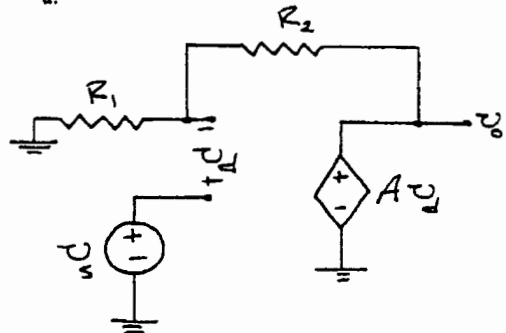

$$\frac{v_s - v_d}{R_1} = \frac{v_o - (v_s - v_d)}{R_2} \text{ and } v_d = \frac{v_o}{A}$$

$$\frac{v_s}{R_1} + \frac{v_s}{R_2} = \frac{v_o}{R_2} + v_d \left( \frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$= \frac{v_o}{R_2} + \frac{v_o}{A} \left( \frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$\nu_S \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{\nu_0}{R_2} \left[ 1 + \frac{1}{A} \left( 1 + \frac{R_2}{R_1} \right) \right]$$

$$\frac{\nu_0}{\nu_S} = \frac{\left( 1 + \frac{R_2}{R_1} \right)}{1 + \frac{1}{A} \left( 1 + \frac{R_2}{R_1} \right)}$$

which can be written as

$$A_{\nu f} = \frac{\nu_0}{\nu_S} = \frac{A}{1 + \left[ \frac{A}{\left( 1 + \frac{R_2}{R_1} \right)} \right]}$$

b.  $\beta = \frac{1}{1 + \frac{R_2}{R_1}}$

c.  $20 = \frac{10^5}{1 + (10^5)\beta}$

So  $\beta = \frac{\frac{10^5}{20} - 1}{10^5} \Rightarrow \beta = 0.04999$


Then  $\frac{R_2}{R_1} = \frac{1}{\beta} - 1 = \frac{1}{0.04999} - 1$   
 $\Rightarrow \frac{R_2}{R_1} = 19.004$

d.  $A \rightarrow 8 \times 10^4$

$$A_f = \frac{8 \times 10^4}{1 + (8 \times 10^4)(0.04999)} = 19.999$$

$$\frac{\Delta A_f}{A_f} = -\frac{0.001}{20} \Rightarrow \frac{\Delta A_f}{A_f} = -0.005\%$$

12.14

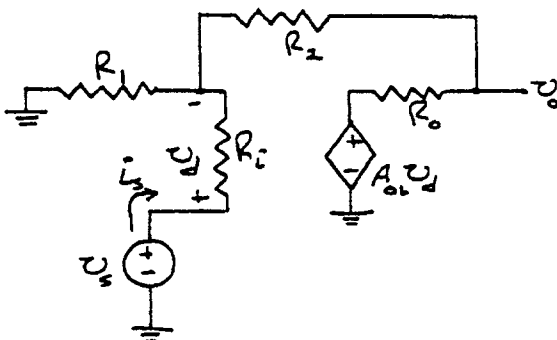

$$A_{\nu f} \approx \left( 1 + \frac{R_2}{R_1} \right) = 20 \Rightarrow \frac{R_2}{R_1} = 19$$

$$\nu_d = i_s R_i$$

$$i_s = \frac{\nu_S - \nu_d}{R_1} + \frac{(\nu_S - \nu_d) - \nu_0}{R_2} \quad (1)$$

$$\frac{\nu_0 - A_0 L \nu_d}{R_0} + \frac{\nu_0 - (\nu_S - \nu_d)}{R_2} = 0 \quad (2)$$

$$\nu_0 \left( \frac{1}{R_0} + \frac{1}{R_2} \right) = \frac{A_0 L \nu_d}{R_0} + \frac{(\nu_S - \nu_d)}{R_2}$$

$$\nu_0 = \frac{\frac{A_0 L \nu_d}{R_0} + \frac{(\nu_S - \nu_d)}{R_2}}{\left( \frac{1}{R_0} + \frac{1}{R_2} \right)}$$

From (1):

$$i_s = \frac{\nu_S - \nu_d}{R_1} + \frac{\nu_S - \nu_d}{R_2} - \frac{\frac{1}{R_2} \left[ \frac{A_0 L \nu_d}{R_0} + \frac{(\nu_S - \nu_d)}{R_2} \right]}{\left( \frac{1}{R_0} + \frac{1}{R_2} \right)}$$

$$i_s = \nu_S \left( \frac{1}{R_1} + \frac{1}{R_2} - \frac{\frac{1}{R_2}}{1 + \frac{R_2}{R_0}} \right) - \nu_d \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{\frac{A_0 L}{R_0} - \frac{1}{R_2}}{1 + \frac{R_2}{R_0}} \right)$$

$$\nu_d = i_s R_i$$

$$i_s \left\{ 1 + \frac{R_i \left[ \left( \frac{1}{R_1} + \frac{1}{R_2} \right) \left( 1 + \frac{R_2}{R_0} \right) + \frac{A_0 L}{R_0} - \frac{1}{R_2} \right]}{1 + \frac{R_2}{R_0}} \right\} = \nu_S \left[ \frac{\left( \frac{1}{R_1} + \frac{1}{R_2} \right) \left( 1 + \frac{R_2}{R_0} \right) - \frac{1}{R_2}}{1 + \frac{R_2}{R_0}} \right]$$

$$i_s \left\{ 1 + \frac{R_2}{R_0} + R_i \left[ \frac{1}{R_1} + \frac{R_2}{R_1} \cdot \frac{1}{R_0} + \frac{1}{R_0} + \frac{A_0 L}{R_0} \right] \right\} = \nu_S \left[ \frac{1}{R_1} + \frac{R_2}{R_1} \cdot \frac{1}{R_0} + \frac{1}{R_0} \right]$$

$$i_s \left\{ R_0 + R_2 + R_i \left[ \frac{R_0}{R_1} + \left( 1 + \frac{R_2}{R_1} \right) + A_0 L \right] \right\} = \nu_S \left[ \frac{R_0}{R_1} + \left( 1 + \frac{R_2}{R_1} \right) \right] \quad (1)$$


Let  $R_2 = 190 \text{ k}\Omega$ ,  $R_1 = 10 \text{ k}\Omega$

$$i_s \left\{ 0.1 + 190 + 100 \cdot \left[ \frac{0.1}{10} + 20 + 10^5 \right] \right\} = \nu_S \left[ \frac{0.1}{10} + 20 \right]$$

$$i_s (1.000219 \times 10^7) = \nu_S (20.01)$$

$$R_{if} = \frac{\nu_S}{i_s} \approx 5 \times 10^5 \text{ k}\Omega \Rightarrow R_{if} \approx 500 \text{ M}\Omega$$

Output Resistance

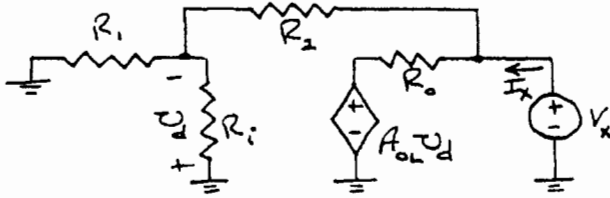

$$I_X = \frac{V_X - A_{OL}v_d}{R_o} + \frac{V_X}{R_2 + R_1 \parallel R_i}$$

$$v_d = \frac{-R_1 \parallel R_i}{R_1 \parallel R_i + R_2} \cdot V_X$$

$$\frac{I_X}{V_X} = \frac{1}{R_{of}} = \frac{1}{R_o} + \frac{A_{OL} \cdot R_1 \parallel R_i}{R_o(R_1 \parallel R_i + R_2)} + \frac{1}{R_2 + R_1 \parallel R_i}$$

$$R_1 \parallel R_i = 10 \parallel 100 = 9.09$$


$$\frac{1}{R_{of}} = \frac{1}{0.1} + \frac{10^5}{0.1} \cdot \left( \frac{9.09}{9.09 + 190} \right) + \frac{1}{190 + 9.09}$$

$$= 10 + 4.566 \times 10^4 + 0.00502$$

$$R_{of} = 2.19 \times 10^{-5} \text{ k}\Omega \Rightarrow R_{of} = 0.0219 \Omega$$

12.15

a.

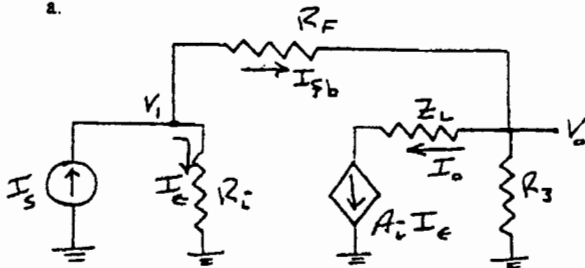

Assume that  $V_1$  is at virtual ground.

$$V_o = -I_{fb} R_F$$

Now

$$I_{fb} = I_o + \frac{V_o}{R_3} = I_o - \frac{I_{fb} R_F}{R_3}$$

$$I_{fb} = I_S - I_e$$

and

$$I_o = A_i I_e \Rightarrow I_e = \frac{I_o}{A_i}$$

so

$$I_{fb} = I_S - \frac{I_o}{A_i}$$

From above

$$I_{fb} \left( 1 + \frac{R_F}{R_3} \right) = I_o$$

$$\left( I_S - \frac{I_o}{A_i} \right) \left( 1 + \frac{R_F}{R_3} \right) = I_o$$

$$I_S \left( 1 + \frac{R_F}{R_3} \right) = I_o \left[ 1 + \frac{1}{A_i} \left( 1 + \frac{R_F}{R_3} \right) \right]$$

or

$$A_{if} = \frac{I_o}{I_S} = \frac{\left( 1 + \frac{R_F}{R_3} \right)}{\left[ 1 + \frac{1}{A_i} \left( 1 + \frac{R_F}{R_3} \right) \right]}$$

$$= \frac{A_i}{1 + \frac{R_F}{R_3}} = A_{if}$$

b.  $\beta_i = \frac{1}{\left( 1 + \frac{R_F}{R_3} \right)}$

c.  $25 = \frac{10^5}{1 + (10^5)\beta_i}$

so  $\beta_i = \frac{\frac{10^5}{25} - 1}{10^5} \Rightarrow \beta_i = 0.03999$


so  $\frac{R_F}{R_3} = \frac{1}{\beta_i} - 1 = \frac{1}{0.03999} - 1 \Rightarrow \frac{R_F}{R_3} = 24.0$

d.  $A_i = 10^5 - (0.15)(10^5) = 8.5 \times 10^4$

so  $A_{if} = \frac{8.5 \times 10^4}{1 + (8.5 \times 10^4)(0.03999)} = 24.9989$

so  $\frac{\Delta A_{if}}{A_{if}} = -\frac{1.10 \times 10^{-3}}{25} = -4.41 \times 10^{-5}$   
 $\Rightarrow -4.41 \times 10^{-3} \%$

12.16

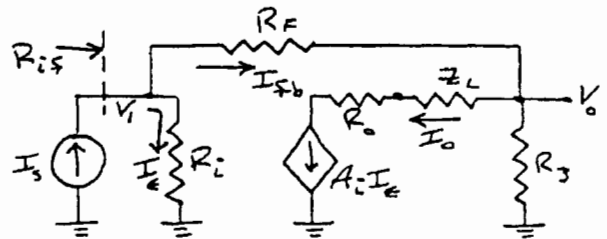

$$I_S = I_e + I_{fb}, \quad V_1 = I_e R_i$$

$$I_{fb} = I_o + \frac{V_o}{R_3} \quad \text{and} \quad V_o = V_1 - I_{fb} R_F$$

$$I_o = A_i I_e \Rightarrow I_e = \frac{I_o}{A_i}$$

Now

$$I_{fb} = A_i I_e + \frac{1}{R_3} (V_1 - I_{fb} R_F)$$

$$I_{fb} \left[ 1 + \frac{R_F}{R_3} \right] = A_i I_e + \frac{V_1}{R_3}$$

$$I_{fb} = I_S - I_e$$

$$(I_S - I_e) \left[ 1 + \frac{R_F}{R_3} \right] = A_i I_e + \frac{V_1}{R_3}$$

$$I_S \left[ 1 + \frac{R_F}{R_3} \right] = I_e \left[ \left( 1 + \frac{R_F}{R_3} \right) + A_i \right] + \frac{V_1}{R_3}$$

$$I_e = \frac{V_1}{R_i}$$

$$I_S \left[ 1 + \frac{R_F}{R_3} \right] = V_1 \left\{ \frac{1}{R_i} \cdot \left[ \left( 1 + \frac{R_F}{R_3} \right) + A_i \right] + \frac{1}{R_3} \right\}$$


$$R_{if} = \frac{V_1}{I_S} = \frac{\left( 1 + \frac{R_F}{R_3} \right)}{\left\{ \frac{1}{R_i} \cdot \left[ \left( 1 + \frac{R_F}{R_3} \right) + A_i \right] + \frac{1}{R_3} \right\}}$$

The  $1/R_3$  term in the denominator will be negligible.  
Using the results of Problem 12.15:

$$R_{if} = \frac{25}{\left\{ \frac{1}{2} [(25) + 10^5] \right\}}$$

$$R_{if} \approx 5 \times 10^{-4} \text{ k}\Omega \Rightarrow R_{if} = 0.5 \Omega$$

Output Resistance (Let  $Z_L = 0$ )

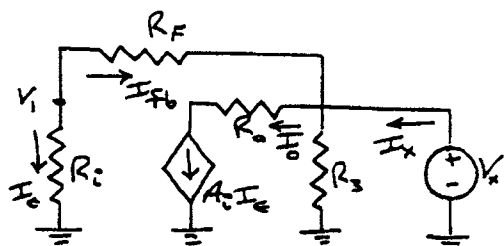

$$I_X = \frac{V_X}{R_3} + A_i I_e + \frac{V_X}{R_F + R_i}$$

$$I_e = \frac{V_X}{R_F + R_i}$$

so

$$\frac{I_X}{V_X} = \frac{1}{R_{of}} = \frac{1}{R_3} + \frac{A_i + 1}{R_F + R_i}, \quad \frac{R_F}{R_3} = 24$$

Let  $R_F = 240 \text{ k}\Omega$ ,  $R_3 = 10 \text{ k}\Omega$


$$\frac{1}{R_{of}} = \frac{1}{10} + \frac{10^5 + 1}{240 + 2}$$

$$\text{so } R_{of} \approx \frac{R_F + R_i}{A_i + 1} = \frac{240 + 2}{10^5 + 1}$$

$$\Rightarrow R_{of} \approx 2.42 \times 10^{-3} \text{ k}\Omega \text{ or } R_{of} \approx 2.42 \Omega$$

12.17

a.

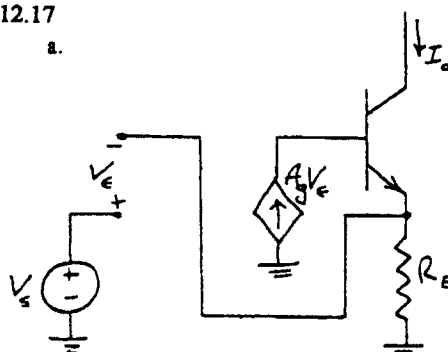

$$I_E = \frac{(1 + h_{FE})}{h_{FE}} \cdot I_o = \frac{V_S - V_e}{R_E}$$

$$\text{Also } I_o = h_{FE} A_g V_e \text{ so } V_e = \frac{I_o}{h_{FE} A_g}$$

Then

$$\frac{1 + h_{FE}}{h_{FE}} \cdot I_o = \frac{V_S}{R_E} - \frac{I_o}{h_{FE} A_g R_E}$$

$$\left[ \frac{1 + h_{FE}}{h_{FE}} + \frac{1}{h_{FE} A_g R_E} \right] I_o = \frac{V_S}{R_E}$$

$$\left[ \frac{A_g (1 + h_{FE}) R_E + 1}{h_{FE} A_g R_E} \right] I_o = \frac{V_S}{R_E}$$

$$\frac{I_o}{V_S} = \frac{1}{R_E} \cdot \left[ \frac{h_{FE} A_g R_E}{1 + A_g (1 + h_{FE}) R_E} \right]$$

$$\Rightarrow \frac{I_o}{V_S} \approx \frac{h_{FE} A_g}{1 + (h_{FE} A_g) R_E}$$

b.  $\beta_z = R_E$

c.  $10 = \frac{5 \times 10^5}{1 + (5 \times 10^5) \beta_z}$


$$\beta_z = \frac{5 \times 10^5 - 1}{5 \times 10^5} \Rightarrow \beta_z = R_E = 0.099998 \text{ k}\Omega$$

d. If  $A_g \rightarrow 5.5 \times 10^5$  then

$$A_{gf} = \frac{5.5 \times 10^5}{1 + (5.5 \times 10^5)(0.099998)} = 10.0000182$$

$$\frac{\Delta A_{gf}}{A_{gf}} = \frac{1.82 \times 10^{-5}}{10} \Rightarrow 1.82 \times 10^{-4} \%$$

12.18

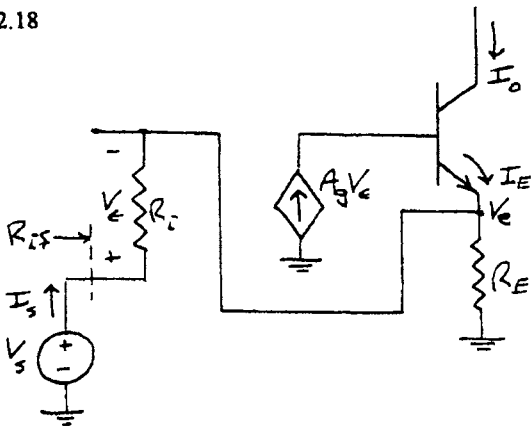

$$I_E = (1 + h_{FE})A_g V_e, I_E = \frac{V_e}{R_E} - I_S \text{ and } V_e = I_S R_i,$$

$$V_e = V_S - V_e = V_S - I_S R_i,$$

$$\text{Now } (1 + h_{FE})A_g I_S R_i = \frac{1}{R_E} (V_S - I_S R_i) - I_S$$

$$\left[ (1 + h_{FE})A_g R_i + \frac{R_i}{R_E} + 1 \right] I_S = \frac{V_S}{R_E}$$

$$R_{if} = \frac{V_S}{I_S} = R_E \left[ (1 + h_{FE})A_g R_i + \frac{R_i}{R_E} + 1 \right]$$


From Problem 12.16:

$$(1 + h_{FE})A_g \approx h_{FE}A_g = 5 \times 10^5 \text{ mS}$$

$$R_E \approx 0.1 \text{ k}\Omega$$

$$\text{so } R_{if} = (0.1) \left[ (5 \times 10^5)(20) + \frac{20}{0.1} + 1 \right]$$
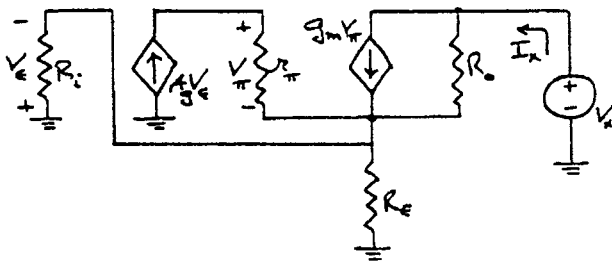
$$\text{or } R_{if} = 10^6 \text{ k}\Omega$$



$$\frac{V_\pi}{r_\pi} = A_g V_e$$

$$I_X = g_m V_\pi + \frac{V_X - (-V_e)}{R_o} \quad (1)$$

$$V_e = -(I_X + A_g V_e)(R_E \parallel R_i) \quad (2)$$

$$\text{or } V_e = [1 + A_g(R_E \parallel R_i)] = -I_X(R_E \parallel R_i)$$

Now

$$I_X = g_m A_g r_\pi V_e + \frac{V_X}{R_o} + \frac{V_e}{R_o} \quad (1)$$

$$I_X = \left( g_m A_g r_\pi + \frac{1}{R_o} \right) \left[ \frac{-I_X(R_E \parallel R_i)}{1 + A_g(R_E \parallel R_i)} \right] + \frac{V_X}{R_o}$$

$$R_{of} = \frac{V_X}{I_X}$$

$$= R_o \left\{ 1 + \left( g_m A_g r_\pi + \frac{1}{R_o} \right) \left[ \frac{(R_E \parallel R_i)}{1 + A_g(R_E \parallel R_i)} \right] \right\}$$

$$g_m r_\pi A_g = h_{FE} A_g = 5 \times 10^5 \text{ mS}$$

$$\text{Let } h_{FE} = 100 \text{ so } A_g = 5 \times 10^3 \text{ mS}$$

$$R_E \parallel R_i = 0.1 \parallel 20 \approx 0.1 \text{ k}\Omega$$


Then

$$R_{of} = 50 \left\{ 1 + \left( 5 \times 10^5 + \frac{1}{50} \right) \left[ \frac{0.1}{1 + (5 \times 10^3)(0.1)} \right] \right\}$$

$$\text{or } R_{of} = 5.04 \text{ M}\Omega$$

12.19

a.

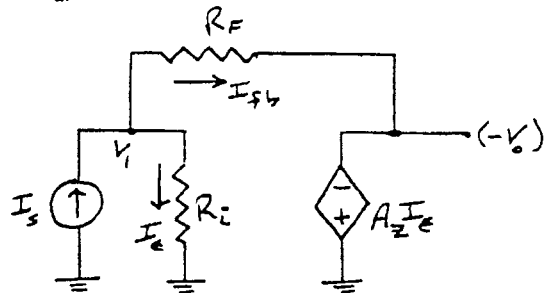

Assuming \$V\_i\$ is at virtual ground

$$(-V_o) = -I_{fb} R_F \text{ and } (-V_o) = -A_z I_e \Rightarrow I_e = \frac{V_o}{A_z}$$

$$I_{fb} = I_S - I_e$$

$$\text{So } V_o = (I_S - I_e) R_F = I_S R_F - \left( \frac{V_o}{A_z} \right) R_F$$

$$V_o \left[ 1 + \frac{R_F}{A_z} \right] = I_S R_F$$

$$\text{so } A_{zf} = \frac{V_o}{I_S} = \frac{R_F}{\left[ 1 + \frac{R_F}{A_z} \right]} = \frac{A_z R_F}{A_z + R_F}$$

$$\text{or } A_{zf} = \frac{A_z}{1 + A_z \left( \frac{1}{R_F} \right)} = \frac{A_z}{1 + A_z \beta_g}$$

$$\text{b. } \beta_g = \frac{1}{R_F}$$

c.  $5 \times 10^4 = \frac{5 \times 10^6}{1 + (5 \times 10^6)\beta_g}$

$\beta_g = \frac{\frac{5 \times 10^6}{5 \times 10^4} - 1}{5 \times 10^6} \Rightarrow \beta_g = 1.98 \times 10^{-5}$


$R_F = \frac{1}{\beta_g} \Rightarrow R_F = 50.5 \text{ k}\Omega$

d.  $A_s = (0.9)(5 \times 10^6) = 4.5 \times 10^6$

$A_{zf} = \frac{4.5 \times 10^6}{1 + (4.5 \times 10^6)(1.98 \times 10^{-5})} = 4.994 \times 10^4$

$\frac{\Delta A_{zf}}{A_{zf}} = -\frac{55.4939}{5 \times 10^4} = -1.11 \times 10^{-3} \Rightarrow -0.111\%$

12.20

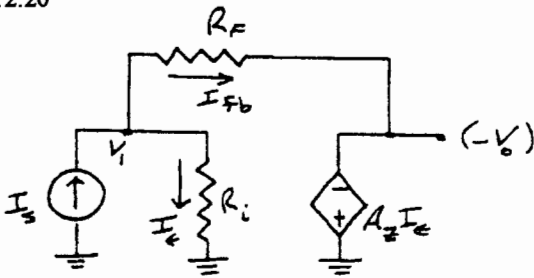

$V_i = I_e R_i, -V_o = -A_z I_e \Rightarrow V_o = A_z I_e$

$I_{fb} = I_s - I_e$  and  $-V_o = V_i - I_{fb} R_F$

$-A_z I_e = V_i - (I_s - I_e) R_F$

$-A_z \left(\frac{V_i}{R_i}\right) = V_i - I_s R_F + \left(\frac{V_i}{R_i}\right) R_F$

$I_s R_F = V_i \left[1 + \frac{A_z}{R_i} + \frac{R_F}{R_i}\right]$

$R_{if} = \frac{V_i}{I_s} = \frac{R_F}{\left[1 + \frac{A_z}{R_i} + \frac{R_F}{R_i}\right]}$


Or, using the results from Problem 12.18,

$R_{if} = \frac{50.5 \times 10^3}{\left[1 + \frac{5 \times 10^6}{10 \times 10^3} + \frac{50.5 \times 10^3}{10 \times 10^3}\right]}$   
 $= \frac{50.5 \times 10^3}{[1 + 500 + 5.05]}$   
 $\Rightarrow R_{if} = 99.79 \Omega$

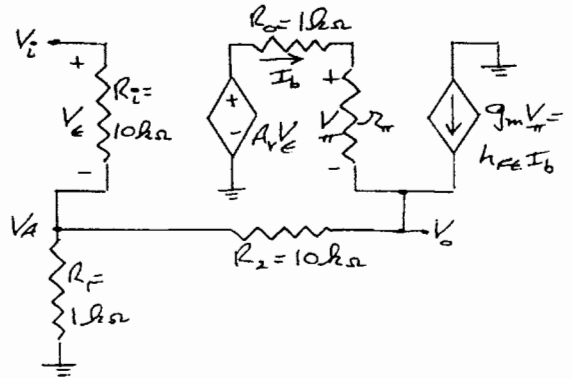12.21

Assume  $I_{CQ} = 0.2 \text{ mA}$

Then  $r_\pi = \frac{(100)(0.026)}{0.2} = 13 \text{ k}\Omega$



(1)  $\frac{V_i - V_A}{R_i} = \frac{V_A}{R_1} + \frac{V_A - V_o}{R_2} \Rightarrow$

$\frac{V_i}{R_i} + \frac{V_o}{R_2} = V_A \left(\frac{1}{R_i} + \frac{1}{R_1} + \frac{1}{R_2}\right)$

Now

$\frac{V_i}{10} + \frac{V_o}{10} = V_A \left(\frac{1}{10} + \frac{1}{1} + \frac{1}{10}\right) \Rightarrow V_i + V_o = V_A (12)$

or  $V_A = \frac{1}{12}(V_i + V_o)$

(2)  $\left(\frac{A_v V_e - V_o}{R_o + r_\pi}\right)(1 + h_{FE}) = \frac{V_o - V_A}{R_2}$

where  $V_e = V_i - V_A$

Then

$\left(\frac{A_v(V_i - V_A) - V_o}{R_o + r_\pi}\right)(1 + h_{FE}) = \frac{V_o - V_A}{R_2}$

we find

$\frac{A_v V_i (1 + h_{FE})}{R_o + r_\pi} - \frac{V_o (1 + h_{FE})}{R_o + r_\pi} - \frac{V_o}{R_2} = \frac{A_v V_A (1 + h_{FE})}{R_o + r_\pi} - \frac{V_A}{R_2}$

Then

$\frac{(5 \times 10^3)(101)V_i}{14} - \frac{V_o(101)}{14} - \frac{V_o}{10} = \frac{A_v V_A (101)}{14} - \frac{V_A}{10}$   
 $= \left(\frac{(5 \times 10^3)(101)}{14} - \frac{1}{10}\right) V_A$

Rearranging terms, we find

$A_v = \frac{V_o}{V_i} = 10.97$


$R_v = \frac{V_i}{I_i} = \frac{V_i}{\left(\frac{V_i - V_A}{R_i}\right)} = \left(\frac{V_i}{V_i - V_A}\right) R_i$

$V_A = \frac{1}{12}(V_i + V_o) = \frac{1}{12}(V_i + 10.97V_i) = 0.9975V_i$

Then

$R_v = \left(\frac{1}{1 - 0.9975}\right)(10 \text{ k}\Omega) \Rightarrow R_v = 4 \text{ M}\Omega$

To find the output resistance:

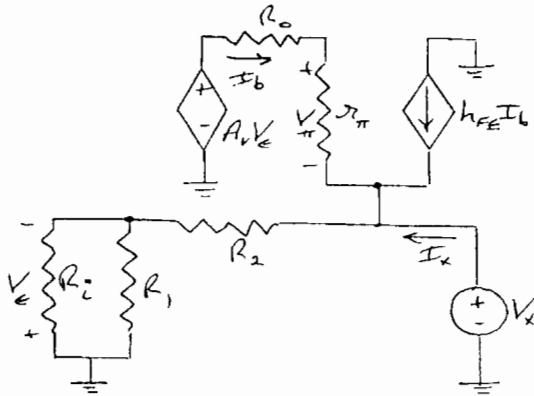

$$I_x + \frac{(A_v V_\epsilon - V_x)(1 + h_{FE})}{R_o + r_x} = \frac{V_x}{R_2 + R_1 \parallel R_i}$$

$$V_\epsilon = -\left(\frac{R_1 \parallel R_i}{R_1 \parallel R_i + R_2}\right) \cdot V_x$$

Now

$$R_1 \parallel R_i = 1 \parallel 10 = 0.909$$

Then

$$V_\epsilon = -0.0833 V_x$$

Now

$$I_x = V_x \left\{ \left[ \frac{(5 \times 10^3)(0.0833) + 1}{1 + 13} \right] (101) + \frac{1}{10 + 0.909} \right\}$$

$$= V_x [3.012 \times 10^3 + 0.0917]$$

Or

$$\frac{V_x}{I_x} = R_{of} = 3.32 \times 10^{-4} \text{ k}\Omega \Rightarrow R_{of} = 0.332 \Omega$$

12.22

a. Neglecting base currents

$$I_{C2} = 0.5 \text{ mA}, V_{C2} = 12 - (0.5)(22.6) = 0.7 \text{ V}$$

$$I_{C1} = 0.5 \text{ mA}$$

$$\Rightarrow v_o = 0$$


$$\text{Then } I_{C3} = 2 \text{ mA}$$

$$b. r_{\pi 1} = r_{\pi 2} = \frac{h_{FE} \cdot V_T}{I_{C1}} = \frac{(100)(0.026)}{0.5} = 5.2 \text{ k}\Omega$$

$$g_{m1} = g_{m2} = \frac{0.5}{0.026} = 19.23 \text{ mA/V}$$

$$r_{\pi 3} = \frac{(100)(0.026)}{2} = 1.3 \text{ k}\Omega$$
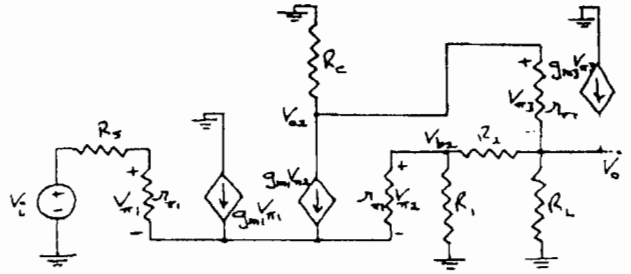
$$g_{m3} = \frac{2}{0.026} = 76.92 \text{ mA/V}$$



$$\frac{V_{\pi 1}}{r_{\pi 1}} + g_{m1} V_{\pi 1} + g_{m1} V_{\pi 2} + \frac{V_{\pi 2}}{r_{\pi 2}} = 0$$

$$(V_{\pi 1} + V_{\pi 2}) \left( \frac{1}{r_{\pi 1}} + g_{m1} \right) = 0$$

$$\Rightarrow V_{\pi 1} = -V_{\pi 2}$$

(1)

$$V_i = \frac{V_{\pi 1}}{r_{\pi 1}} (R_S + r_{\pi 1}) - V_{\pi 2} + V_{b2}$$

or

$$V_i = V_{\pi 1} \left( 1 + \frac{R_S}{r_{\pi 1}} \right) - V_{\pi 2} + V_{b2}$$

$$\text{But } V_{\pi 2} = -V_{\pi 1}$$

so

$$V_i = V_{\pi 1} \left( 2 + \frac{R_S}{r_{\pi 1}} \right) + V_{b2}$$

(2)

$$\frac{V_{o2}}{R_C} + g_{m1} V_{\pi 2} + \frac{V_{o2} - V_0}{r_{\pi 3}} = 0$$

(3)

$$\frac{V_{\pi 3}}{r_{\pi 3}} + g_{m3} V_{\pi 3} = \frac{V_0}{R_L} + \frac{V_0 - V_{b2}}{R_2}$$

$$V_{\pi 3} = V_{o2} - V_0$$

so

$$(V_{o2} - V_0) \left( \frac{1 + h_{FE}}{r_{\pi 3}} \right) = V_0 \left( \frac{1}{R_L} + \frac{1}{R_2} \right) - \frac{V_{b2}}{R_2}$$

(4)

$$\frac{V_{b2} - V_0}{R_2} + \frac{V_{b2}}{R_1} + \frac{V_{\pi 2}}{r_{\pi 1}} = 0$$

(5)

Substitute numbers into (2), (3), (4) and (5):

$$V_i = -V_{\pi 2} \left( 2 + \frac{1}{5.2} \right) + V_{b2}$$

$$V_i = -V_{\pi 2} (2.192) + V_{b2}$$

(2)

$$V_{o2} \left( \frac{1}{22.6} + \frac{1}{1.3} \right) + (19.23) V_{\pi 2} - V_0 \left( \frac{1}{1.3} \right) = 0$$

$$V_{o2} (0.8135) + (19.23) V_{\pi 2} - (0.7692) V_0 = 0$$

(3)

$$V_{O2} \left( \frac{101}{1.3} \right) = V_0 \left( \frac{101}{1.3} + \frac{1}{4} + \frac{1}{50} \right) - V_{b2} \left( \frac{1}{50} \right)$$

$$V_{O2}(77.69) = V_0(77.96) - V_{b2}(0.02) \quad (4)$$

$$V_{b2} \left( \frac{1}{50} + \frac{1}{10} \right) - V_0 \left( \frac{1}{50} \right) + V_{\pi 2} \left( \frac{1}{5.2} \right) = 0$$

$$V_{b2}(0.120) - V_0(0.020) + V_{\pi 2}(0.1923) = 0 \quad (5)$$

From (2):  $V_{b2} = V_i + V_{\pi 2}(2.192)$ . Substitute in (4) and (5) to obtain:

$$V_{O2}(77.69) = V_0(77.96) - [V_i + V_{\pi 2}(2.192)](0.02) \quad (4')$$

$$[V_i + V_{\pi 2}(2.192)](0.120) - V_0(0.020) + V_{\pi 2}(0.1923) = 0 \quad (5')$$

So we now have the following three equations:

$$V_{O2}(0.8135) + (19.23)V_{\pi 2} - (0.7692)V_0 = 0 \quad (3)$$

$$V_{O2}(77.69) = V_0(77.96) - V_i(0.02) - V_{\pi 2}(0.04384) \quad (4')$$

$$(0.120)V_i + V_{\pi 2}(0.4553) - V_0(0.020) = 0 \quad (5')$$

From (3):  $V_{O2} = V_0(0.9455) - V_{\pi 2}(23.64)$ . Substitute for  $V_{O2}$  in (4') to obtain:

$$(77.69)[V_0(0.9455) - V_{\pi 2}(23.64)] = V_0(77.96) - V_i(0.02) - V_{\pi 2}(0.04384)$$

or

$$0 = V_0(4.504) - V_i(0.02) + V_{\pi 2}(1836.5)$$

Next, solve (5') for  $V_{\pi 2}$ :

$$(0.120)V_i + V_{\pi 2}(0.4553) - V_0(0.020) = 0$$

$$V_{\pi 2} = V_0(0.04393) - V_i(0.2636)$$

Finally,

$$0 = V_0(4.504) - V_i(0.02)$$

$$+ (1836.5)[V_0(0.04393) - V_i(0.2636)]$$

$$0 = V_0(85.18) - V_i(484.12)$$

So

$$A_{v_f} = \frac{V_0}{V_i} = \frac{484.12}{85.18} \Rightarrow A_{v_f} = 5.68$$

12.23

a.  $R_{TH} = R_1 \parallel R_2 = 400 \parallel 75 = 63.2 \text{ k}\Omega$

$$V_{TH} = \left( \frac{R_2}{R_1 + R_2} \right) V_{CC} = \left( \frac{75}{75 + 400} \right) (10)$$

$$= 1.579 \text{ V}$$

$$I_{BQ1} = \frac{1.579 - 0.7}{63.2 + (121)(0.5)} = 0.007106 \text{ mA}$$

$$I_{CQ1} = 0.853 \text{ mA}$$

$$V_{C1} = 10 - (0.853)(8.8) = 2.49 \text{ V}$$

$$I_{C2} \approx \frac{2.49 - 0.7}{3.6} = 0.497 \text{ mA}$$

$$V_{C2} = 10 - (0.497)(13) = 3.54 \text{ V}$$

$$I_{C3} \approx \frac{3.54 - 0.7}{1.4} = 2.03 \text{ mA}$$

Then

$$r_{\pi 1} = \frac{(120)(0.026)}{0.853} = 3.66 \text{ k}\Omega$$

$$g_{m1} = \frac{0.853}{0.026} = 32.81 \text{ mA/V}$$


$$r_{\pi 2} = \frac{(120)(0.026)}{0.497} = 6.28 \text{ k}\Omega$$

$$g_{m2} = \frac{0.497}{0.026} = 19.12 \text{ mA/V}$$

$$r_{\pi 3} = \frac{(120)(0.026)}{2.03} = 1.54 \text{ k}\Omega$$

$$g_{m3} = \frac{2.03}{0.026} = 78.08 \text{ mA/V}$$

b.

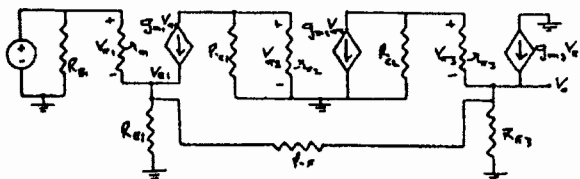

$$V_i = V_{\pi 1} + V_{e1} \Rightarrow V_{e1} = V_i - V_{\pi 1} \quad (1)$$

$$\frac{V_{\pi 1}}{r_{\pi 1}} + g_{m1} V_{\pi 1} = \frac{V_{e1}}{R_{E1}} + \frac{V_{e1} - V_0}{R_F} \quad (2)$$

$$V_{\pi 2} = -(g_{m1} V_{\pi 1})(R_{C1} \parallel R_2) \quad (3)$$

$$g_{m2} V_{\pi 2} + \frac{V_{\pi 3} + V_0}{R_{C2}} + \frac{V_{\pi 3}}{r_{\pi 3}} = 0 \quad (4)$$

$$\frac{V_{\pi 3}}{r_{\pi 3}} + g_{m3} V_{\pi 3} = \frac{V_0}{R_{E3}} + \frac{V_0 - V_{e1}}{R_F} \quad (5)$$

Substitute numbers in (2), (3), (4) and (5):

$$V_{\pi 1} \left( \frac{1}{3.66} + 32.81 \right) = (V_i - V_{\pi 1}) \left( \frac{1}{0.5} + \frac{1}{10} \right) - \frac{V_0}{10}$$

or  $V_{\pi 1}(35.18) = V_i(2.10) - V_0(0.10)$  (2)

$$V_{\pi 2} = -(32.81)V_{\pi 1} (88 \parallel 6.28)$$

or  $V_{\pi 2} = -V_{\pi 1}(120.2)$  (3)

$$(19.12)V_{\pi 2} + \frac{V_{\pi 3}}{13} + \frac{V_0}{13} + \frac{V_{\pi 3}}{1.54} = 0$$

or

$$V_{\pi 2}(19.12) + V_{\pi 3}(0.7263) + V_0(0.07692) = 0$$
 (4)

$$V_{\pi 3} \left( \frac{1}{1.54} + 78.08 \right) = V_0 \left( \frac{1}{1.4} + \frac{1}{10} \right) - \frac{V_i - V_{\pi 1}}{10}$$

or

$$V_{\pi 3}(78.73) = V_0(0.8143) - V_i(0.10) + V_{\pi 1}(0.10)$$
 (5)

Now substituting  $V_{\pi 2} = -V_{\pi 1}(120.2)$  in (4):

$$(19.12)[-V_{\pi 1}(120.2)] + V_{\pi 3}(0.7263) + V_0(0.07692) = 0$$

or

$$-V_{\pi 1}(2298.2) + V_{\pi 3}(0.7263) + V_0(0.07692) = 0$$

Then

$$V_{\pi 3} = V_{\pi 1}(3164.3) - V_0(0.1059)$$

Substituting  $V_{\pi 3} = V_{\pi 1}(3164.3) - V_0(0.1059)$  in (5):

$$(78.73)[V_{\pi 1}(3164.3) - V_0(0.1059)] = V_0(0.8143) - V_i(0.10) + V_{\pi 1}(0.10)$$

or

$$V_{\pi 1}(2.49 \times 10^5) - V_0(9.152) = -V_i(0.10)$$

Then

$$V_{\pi 1} = V_0(3.674 \times 10^{-5}) - V_i(4.014 \times 10^{-7})$$

Now substituting  $V_{\pi 1} = V_0(3.674 \times 10^{-5}) - V_i(4.014 \times 10^{-7})$  in (2):

$$(35.18)[V_0(3.674 \times 10^{-5}) - V_i(4.014 \times 10^{-7})] = V_i(2.10) - V_0(0.10)$$

or  $V_0(0.1013) = V_i(2.10)$

So  $\frac{V_0}{V_i} = 20.7$

c.  $R_{i,f} = \frac{V_i}{I_i}$  and  $I_i = I_{RB1} + I_{b1}$

$$I_{RB1} = \frac{V_i}{R_{B1}}$$

$$I_{b1} = \frac{V_{\pi 1}}{r_{\pi 1}}$$

Now

$$V_{\pi 1} = (20.7V_i)(3.674 \times 10^{-5}) - V_i(4.014 \times 10^{-7})$$

$$V_{\pi 1} = V_i(7.60 \times 10^{-4})$$

Then

$$R_{i,f} = \frac{V_i}{\frac{V_i}{63.2} + \frac{V_i(7.60 \times 10^{-4})}{3.66}}$$

$$= \frac{1}{0.01582 + 2.077 \times 10^{-4}}$$

or  $R_{i,f} = 62.4 \text{ k}\Omega$

d. To determine  $R_{o,f}$ :

Equation (1) is modified to  $V_{\pi 1} + V_{e1} = 0$  ( $V_i = 0$ )  
Equation (5) is modified to:

$$V_{\pi 3}(78.73) + I_X = V_0(0.8143) + V_{\pi 1}(0.10)$$
 (5)

Now

$$V_{\pi 1}(35.18) = -V_0(0.10)$$
 (2)

$$V_{\pi 2} = -V_{\pi 1}(120.2)$$
 (3)

$$V_{\pi 2}(19.12) + V_{\pi 3}(0.7263) + V_0(0.07692) = 0$$
 (4)

Now

$$V_{\pi 1} = -V_0(0.002843)$$

so

$$V_{\pi 2} = -(-V_0)(0.002843)(120.2)$$

$$V_{\pi 2} = V_0(0.3417)$$

Then

$$V_0(0.3417)(19.12) + V_{\pi 3}(0.7263) + V_0(0.07692) = 0$$

or

$$V_{\pi 3} = -V_0(9.101)$$
 (4)

So then

$$-V_0(9.101)(78.73) + I_X = V_0(0.8143) + (0.10)(-V_0)(0.002843)$$

or


$$I_X = V_0(717.3)$$
 (5)

or

$$R_{o,f} = \frac{V_0}{I_X} = 0.00139 \text{ k}\Omega \Rightarrow R_{o,f} = 1.39 \Omega$$

12.24

b.

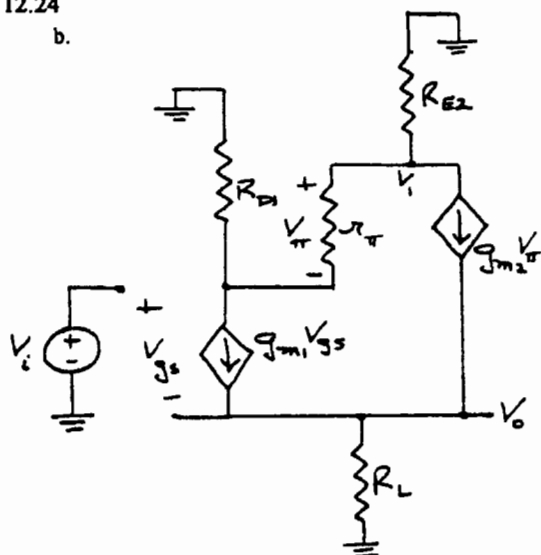

$$V_0 = (g_{m1} V_{gs} + g_{m2} V_{\pi}) R_L \quad (1)$$

$$V_1 = V_{gs} + V_0 \quad (2)$$

$$\begin{aligned} \frac{V_{\pi}}{r_{\pi}} + g_{m2} V_{\pi} + \frac{V_1}{R_{E2}} &= 0 \\ \Rightarrow V_{\pi} \left( \frac{1 + h_{FE}}{r_{\pi}} \right) + \frac{V_1}{R_{E2}} &= 0 \end{aligned} \quad (3)$$

$$\begin{aligned} \frac{V_{\pi}}{r_{\pi}} &= g_{m1} V_{gs} + \frac{V_1 - V_{\pi}}{R_{D1}} = 0 \\ \text{or} \\ V_1 &= R_{D1} \left[ \frac{V_{\pi}}{r_{\pi}} + \frac{V_{\pi}}{R_{D1}} - g_{m1} V_{gs} \right] \end{aligned} \quad (4)$$

Then

$$V_{\pi} \left( \frac{1 + h_{FE}}{r_{\pi}} \right) + \frac{R_{D1}}{R_{E2}} \left[ \frac{V_{\pi}}{r_{\pi}} + \frac{V_{\pi}}{R_{D1}} - g_{m1} V_{gs} \right] = 0 \quad (3)$$

$$V_{\pi} \left\{ \left( \frac{1 + h_{FE}}{r_{\pi}} \right) + \frac{R_{D1}}{R_{E2} r_{\pi}} + \frac{1}{R_{E2}} \right\} = g_{m1} \left( \frac{R_{D1}}{R_{E2}} \right) V_{gs}$$

Let

$$V_{\pi} \cdot \frac{1}{R_{eq}} = g_{m1} \left( \frac{R_{D1}}{R_{E2}} \right) V_{gs}$$

$$\text{so } V_{\pi} = g_{m1} R_{eq} \left( \frac{R_{D1}}{R_{E2}} \right) V_{gs}$$

Then

$$V_0 = \left[ g_{m1} V_{gs} + g_{m1} g_{m2} R_{eq} \left( \frac{R_{D1}}{R_{E2}} \right) V_{gs} \right] R_L \quad (1)$$

so

$$V_0 = g_{m1} R_L \left[ 1 + g_{m2} R_{eq} \left( \frac{R_{D1}}{R_{E2}} \right) \right] (V_i - V_0)$$

so

$$A_v = \frac{V_0}{V_i} = \frac{g_{m1} R_L \left[ 1 + g_{m2} R_{eq} \left( \frac{R_{D1}}{R_{E2}} \right) \right]}{1 + g_{m1} R_L \left[ 1 + g_{m2} R_{eq} \left( \frac{R_{D1}}{R_{E2}} \right) \right]}$$

c. Set  $V_i = 0$

$$I_X + g_{m1} V_{gs} + g_{m2} V_{\pi} = \frac{V_X}{R_L}$$

$$V_{gs} = -V_X$$

From part (b), we have

$$V_{\pi} = g_{m1} R_{eq} \left( \frac{R_{D1}}{R_{E2}} \right) V_{gs} = -g_{m1} R_{eq} \left( \frac{R_{D1}}{R_{E2}} \right) V_X$$

Then


$$\frac{I_X}{V_X} = \frac{1}{R_0} = \frac{1}{R_L} + g_{m1} g_{m2} R_{eq} \left( \frac{R_{D1}}{R_{E2}} \right)$$

or

$$R_0 = R_L \parallel \frac{1}{g_{m1}} \parallel \frac{1}{g_{m1} g_{m2} R_{eq} \left( \frac{R_{D1}}{R_{E2}} \right)}$$

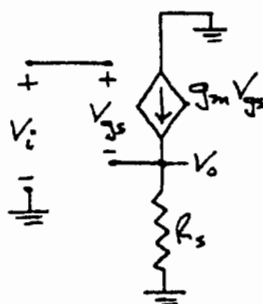12.25

$$\text{a. } g_m = 2\sqrt{K_n I_{DQ}} = 2\sqrt{(0.5)(0.5)} = 1 \text{ mA/V}$$



$$V_0 = (g_m V_{gs}) R_S$$

$$V_i = V_{gs} + V_0 \text{ so } V_{gs} = V_i - V_0$$

Then

$$V_0 = g_m R_S (V_i - V_0)$$

$$A_v = \frac{g_m R_S}{1 + g_m R_S} = \frac{1(2)}{1 + (1)(2)} \Rightarrow A_v = 0.667$$

To determine  $R_{of}$

$$I_X + g_m V_{gs} = \frac{V_X}{R_S} \text{ and } V_{gs} = -V_X$$

$$\frac{I_X}{V_X} = \frac{1}{R_{of}} = g_m + \frac{1}{R_S}$$

$$\text{so } R_{of} = \frac{1}{g_m} \parallel R_S = \frac{1}{1} \parallel 2 \Rightarrow R_{of} = 0.667 \text{ k}\Omega$$

b. For  $K_n = 0.8 \text{ mA/V}^2$

$$g_m = 2\sqrt{(0.8)(0.5)} = 1.265 \text{ mA/V}$$

$$A_v = \frac{(1.265)(2)}{1 + (1.265)(2)} = 0.7167$$

$$\frac{\Delta A_f}{A_f} = \frac{0.7167 - 0.667}{0.667} \Rightarrow 7.45\% \text{ increase}$$

$$R_{of} = \frac{1}{1.265} \parallel 2 = 0.7905 \parallel 2$$

$$R_{of} = 0.5666$$

$$\frac{\Delta R_{of}}{R_{of}} = \frac{0.5666 - 0.667}{0.667} \Rightarrow 15.05\% \text{ decrease}$$

12.26

dc analysis:

$$R_{TH1} = 150 \parallel 47 = 35.8 \text{ k}\Omega,$$

$$V_{TH1} = \left( \frac{47}{47 + 150} \right) (25) = 5.96 \text{ V}$$

$$R_{TH2} = 33 \parallel 47 = 19.4 \text{ k}\Omega,$$

$$V_{TH2} = \left( \frac{33}{33 + 47} \right) (25) = 10.3 \text{ V}$$

$$I_{B1} = \frac{5.96 - 0.7}{35.8 + (51)(4.8)} = 0.0187 \text{ mA}$$

$$I_{C1} = (50)(0.0187) = 0.935 \text{ mA}$$

$$I_{B2} = \frac{10.3 - 0.7}{19.4 + (51)(4.7)} = 0.03705 \text{ mA}$$


$$I_{C2} = (50)(0.03705) = 1.85 \text{ mA}$$

$$r_{\pi 1} = \frac{(50)(0.026)}{0.935} = 1.39 \text{ k}\Omega;$$

$$r_{\pi 2} = \frac{(50)(0.026)}{1.85} = 0.703 \text{ k}\Omega$$

$$g_{m1} = \frac{0.935}{0.026} = 35.96 \text{ mA/V}$$
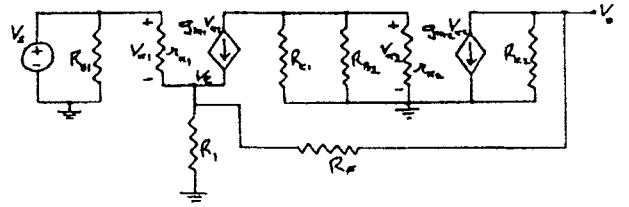
$$g_{m2} = \frac{1.85}{0.026} = 71.15 \text{ mA/V}$$



$$V_S = V_{\pi 1} + V_e \tag{1}$$

$$\frac{V_{\pi 1}}{r_{\pi 1}} + g_{m1} V_{\pi 1} = \frac{V_e}{R_1} + \frac{V_e - V_0}{R_F} \tag{2}$$

$$g_{m1} V_{\pi 1} + \frac{V_{\pi 2}}{R_{C1}} + \frac{V_{\pi 2}}{R_{B2}} + \frac{V_{\pi 2}}{r_{\pi 2}} = 0 \tag{3}$$

$$g_{m2} V_{\pi 2} + \frac{V_0}{R_{C2}} + \frac{V_0 - V_e}{R_F} = 0 \tag{4}$$

Substitute numerical values in (2), (3) and (4):

$$V_e = V_S - V_{\pi 1} \tag{1}$$

$$\frac{V_{\pi 1}}{1.39} + (35.96)V_{\pi 1}$$

$$= (V_S - V_{\pi 1}) \left( \frac{1}{0.1} + \frac{1}{4.7} \right) - V_0 \left( \frac{1}{4.7} \right)$$

or

$$V_{\pi 1}(46.89) = V_S(10.213) - V_0(0.2128) \tag{2}$$

$$(35.96)V_{\pi 1} + V_{\pi 2} \left( \frac{1}{10} + \frac{1}{19.4} + \frac{1}{0.703} \right) = 0$$

or

$$(35.96)V_{\pi 1} + V_{\pi 2}(1.574) = 0 \tag{3}$$

$$(71.15)V_{\pi 2} + V_0 \left( \frac{1}{4.7} + \frac{1}{4.7} \right)$$

$$- (V_S - V_{\pi 1}) \left( \frac{1}{4.7} \right) = 0$$

or

$$(71.15)V_{\pi 2} + V_0(0.4255) - V_S(0.2128) + V_{\pi 1}(0.2128) = 0 \tag{4}$$

$$\text{From (3): } V_{\pi 2} = -V_{\pi 1}(22.85)$$

Then substitute in (4):

$$-(71.15)V_{\pi 1}(22.85) + V_0(0.4255)$$

$$- V_S(0.2128) + V_{\pi 1}(0.2128) = 0$$

or

$$- V_{\pi 1}(1625.6) + V_0(0.4255) - V_S(0.2128) = 0$$

$$\text{From (2): } V_{\pi 1} = V_S(0.2178) - V_0(0.004538)$$

Then

$$-(1625.6)[V_S(0.2178) - V_0(0.004538)]$$

$$+ V_0(0.4255) - V_S(0.2128) = 0$$

or  $-V_S(354.3) + V_O(7.802) = 0$


Finally

$$\Rightarrow \frac{V_O}{V_S} = 45.4$$

12.27

For example, use the circuit shown in Figure 12.23

12.28

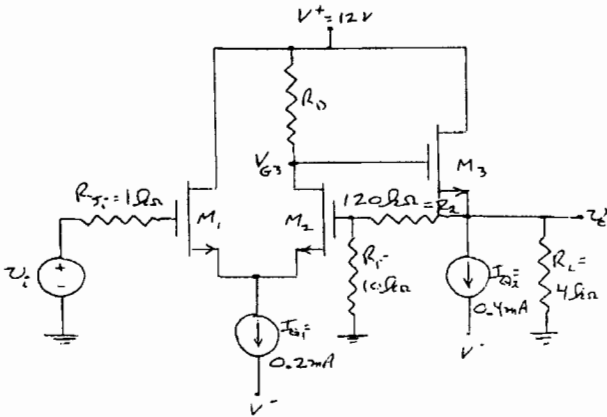

For  $M_3$ :  $K_{n3} = \frac{k'_n}{2} \left(\frac{W}{L}\right)_3$  Let  $\left(\frac{W}{L}\right)_3 = 25$

Then  $K_{n3} = \left(\frac{0.080}{2}\right)(25) = 1 \text{ mA/V}^2$


Want  $v_o = 0$  for  $v_i = 0$ , so that

$$I_{D3} = I_{Q2} = 0.4 = 1 \cdot (V_{GS3} - V_{TN})^2$$

Then  $V_{GS3} = \sqrt{\frac{0.4}{1}} + 2 = 2.63 \text{ V}$

For  $V_{GS3} = 2.63 \text{ V} \Rightarrow V_{G3} = 12 - I_{D2}R_D$

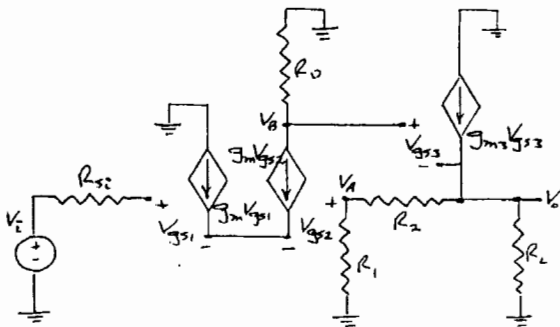Or  $2.63 = 12 - (0.1)R_D \Rightarrow R_D = 93.7 \text{ k}\Omega$



$$g_{m3} = 2\sqrt{K_{n3}I_{D3}} = 2\sqrt{(1)(0.4)} = 1.26 \text{ mA/V}$$

$$V_A = \left(\frac{R_1}{R_1 + R_2}\right)(V_o) = \left(\frac{10}{120 + 10}\right)(V_o) = 0.0769V_o$$

(Small amount of feedback)

(1)  $V_i = V_{gs1} - V_{gs2} + V_A$

(2)  $g_m V_{gs1} + g_m V_{gs2} = 0 \Rightarrow V_{gs1} = -V_{gs2}$

Then

$$V_i = -2V_{gs2} + V_A \Rightarrow V_{gs2} = \frac{1}{2}(V_A - V_i)$$

$$V_{gs2} = 0.03846V_o - 0.5V_i$$

(3)  $V_B = -g_m V_{gs2} R_D = -g_m R_D [0.03846V_o - 0.5V_i]$

(4)  $V_{gs3} = V_B - V_o$  and  $V_o = g_{m3} V_{gs3} [R_L \parallel (R_1 + R_2)]$

So

$$V_o = g_{m3} [R_L \parallel (R_1 + R_2)] (V_B - V_o)$$

Then

$$V_o = g_{m3} [R_L \parallel (R_1 + R_2)] [-g_m R_D (0.03846V_o - 0.5V_i) - V_o]$$

Or

$$V_o [1 + g_{m3} [R_L \parallel (R_1 + R_2)] [g_m R_D (0.03846) + 1]] = g_{m3} [R_L \parallel (R_1 + R_2)] [0.5g_m R_D] \cdot V_i$$

Now

$$R_L \parallel (R_1 + R_2) = 4 \parallel 130 = 3.88$$

So

$$V_o [1 + (1.26)(3.88)[g_m(93.7)(0.03846) + 1]] = (1.26)(3.88)(0.5)g_m(93.7)V_i$$

Rearranging terms, we find

$$\frac{V_o}{V_i} = \frac{229g_m}{5.89 + 17.6g_m} = 10 \Rightarrow g_m = 1.11 \text{ mA/V}$$

We have

$$g_m = 2\sqrt{\left(\frac{k'_n}{2}\right)\left(\frac{W}{L}\right)I_D} \Rightarrow$$

$$1.11 = 2\sqrt{\left(\frac{0.080}{2}\right)\left(\frac{W}{L}\right)(0.1)} \Rightarrow$$

$$\left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2 = 77$$

12.29

Assuming an ideal op-amp, then from Equation (12.58)

$$\frac{I_o}{I_S} = 1 + \frac{R_1}{R_2} = \frac{20}{0.2} = 100$$

Then  $\frac{R_1}{R_2} = 99$

For example, set  $R_2 = 5 \text{ k}\Omega$  and  $R_1 = 495 \text{ k}\Omega$

12.30

(a)  $I_{C1} = \left(\frac{h_{FE}}{1 + h_{FE}}\right) I_{E1} = \left(\frac{100}{101}\right)(0.2) = 0.198 \text{ mA}$

$$V_{C1} = 10 - (0.198)(40) = 2.08 \text{ V}$$

$$I_{E2} = \frac{2.08 - 0.7}{1} = 1.38 \text{ mA}$$

$$I_{C2} = \left(\frac{100}{101}\right)(1.38) = 1.37 \text{ mA}$$

For  $Q_1$ :

$$r_{\pi 1} = \frac{(100)(0.026)}{0.198} = 13.1 \text{ k}\Omega$$


$$g_{m1} = \frac{0.198}{0.026} = 7.62 \text{ mA/V}$$

For  $Q_2$ :

$$r_{\pi 2} = \frac{(100)(0.026)}{1.37} = 1.90 \text{ k}\Omega$$

$$g_{m2} = \frac{1.37}{0.026} = 52.7 \text{ mA/V}$$

(b)

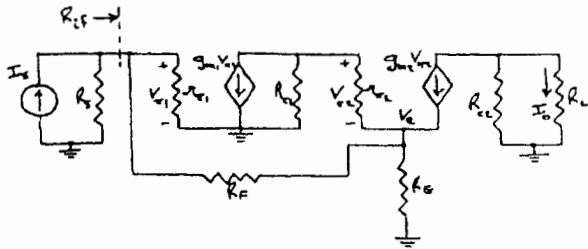

$$I_S = \frac{V_{\pi 1}}{R_S} + \frac{V_{\pi 1}}{r_{\pi 1}} + \frac{V_{\pi 1} - V_c}{R_F} \quad (1)$$

$$g_{m1} V_{\pi 1} + \frac{V_{\pi 2} + V_c}{R_{C1}} + \frac{V_{\pi 2}}{r_{\pi 2}} = 0 \quad (2)$$

$$\frac{V_{\pi 2}}{r_{\pi 2}} + g_{m2} V_{\pi 2} = \frac{V_c}{R_E} + \frac{V_c - V_{\pi 1}}{R_F} \quad (3)$$

Substitute numerical values in (1), (2), and (3):

$$I_S = V_{\pi 1} \left( \frac{1}{10} + \frac{1}{13.1} + \frac{1}{10} \right) - V_c \left( \frac{1}{10} \right)$$

$$I_S = V_{\pi 1} (0.2763) - V_c (0.10) \quad (1)$$

$$(7.62)V_{\pi 1} + V_{\pi 2} \left( \frac{1}{40} + \frac{1}{1.90} \right) + V_c \left( \frac{1}{40} \right) = 0$$

$$(7.62)V_{\pi 1} + V_{\pi 2} (0.5513) + V_c (0.025) = 0 \quad (2)$$

$$V_{\pi 2} \left( \frac{1}{1.90} + 52.7 \right) = V_c \left( \frac{1}{1} + \frac{1}{10} \right) - V_{\pi 1} \left( \frac{1}{10} \right)$$

$$V_{\pi 2} (53.23) = V_c (1.10) - V_{\pi 1} (0.10) \quad (3)$$

From (3),

$$V_c = V_{\pi 2} (48.39) + V_{\pi 1} (0.0909)$$

Substituting into (1),

$$I_S = V_{\pi 1} (0.2763) - (0.10) [V_{\pi 2} (48.39) + V_{\pi 1} (0.0909)]$$

or

$$I_S = V_{\pi 1} (0.2672) - V_{\pi 2} (4.839) \quad (1')$$

and substituting into (2),

$$(7.62)V_{\pi 1} + V_{\pi 2} (0.5513) + (0.025) [V_{\pi 2} (48.39) + V_{\pi 1} (0.0909)] = 0$$

or

$$(7.622)V_{\pi 1} + V_{\pi 2} (1.761) = 0$$

$$\Rightarrow V_{\pi 1} = -V_{\pi 2} (0.2310) \quad (2')$$

Then substituting (2') into (1'), we obtain

$$I_S = (0.2672)(-V_{\pi 2})(0.2310) - V_{\pi 2} (4.839)$$

or

$$I_S = -V_{\pi 2} (4.901)$$

Now

$$I_O = -g_{m2} V_{\pi 2} \left( \frac{R_{C2}}{R_{C2} + R_L} \right)$$

$$= -(52.7) \left( \frac{2}{2+0.5} \right) V_{\pi 2} = -(42.16)V_{\pi 2}$$

Then

$$I_O = -(42.16) \left( \frac{-I_S}{4.901} \right)$$

or

$$A_{ij} = \frac{I_O}{I_S} = 8.60$$

(c)  $R_i = \frac{V_{\pi 1}}{I_S}$  and  $R_i = R_S \parallel R_{if}$

We had

$$V_{\pi 1} = -V_{\pi 2} (0.2310) \text{ and } I_S = -V_{\pi 2} (4.901)$$

so

$$I_S = - \left( \frac{-V_{\pi 1}}{0.2310} \right) (4.901) = V_{\pi 1} (21.22)$$

Then

$$R_i = \frac{V_{\pi 1}}{I_S} = \frac{1}{21.22} = 0.04713$$

Finally

$$0.04713 = \frac{10R_{if}}{10 + R_{if}} \Rightarrow$$

$$R_{if} = 47.4 \Omega$$

### 12.31

(a) Using Figure 12.25

$$I_i = \frac{V_{\pi 1}}{R_S \parallel R_{B1} \parallel \tau_{\pi 1}} + \frac{V_{\pi 1} - V_{c2}}{R_F} \quad (1)$$

$$g_{m1} V_{\pi 1} + \frac{V_{\pi 2}}{R_{C1} \parallel R_{B2}} + \frac{V_{\pi 2}}{\tau_{\pi 2}} = 0$$

$$= g_{m1} V_{\pi 1} + \frac{V_{\pi 2}}{R_{C1} \parallel R_{B2} \parallel \tau_{\pi 2}} \quad (2)$$

$$\frac{V_{\pi 2}}{r_{\pi 2}} + g_{m2} V_{\pi 2} = \frac{V_{e2}}{R_{E2}} + \frac{V_{e2} - V_{\pi 1}}{R_F} \quad (3)$$

$$I_o = -\left(\frac{R_{C2}}{R_{C2} + R_L}\right)(g_{m2} V_{\pi 2}) \quad (4)$$

$$I_i = \frac{V_{\pi 1}}{R_S \parallel R_{B1} \parallel r_{\pi 1} \parallel R_F} - \frac{V_{e2}}{R_F} \quad (1')$$

so that

$$V_{e2} = \left(\frac{R_F}{R_S \parallel R_{B1} \parallel r_{\pi 1} \parallel R_F}\right) V_{\pi 1} - R_F I_i$$

Then

$$V_{\pi 2} \left(\frac{1 + \beta_2}{r_{\pi 2}}\right) = \left(\frac{1}{R_{E2}} + \frac{1}{R_F}\right) \times \left\{ \left(\frac{R_F}{R_S \parallel R_{B1} \parallel r_{\pi 1} \parallel R_F}\right) V_{\pi 1} - R_F I_i \right\} - \frac{V_{\pi 1}}{R_F} \quad (3')$$

From (2):

$$V_{\pi 1} = -\frac{V_{\pi 2}}{g_{m1}} \cdot \frac{1}{(R_{C1} \parallel R_{B2} \parallel r_{\pi 2})}$$

Then

$$V_{\pi 2} \left(\frac{1 + \beta_2}{r_{\pi 2}}\right) = \frac{V_{\pi 2}}{g_{m1} R_F} \cdot \frac{1}{R_{C1} \parallel R_{B2} \parallel r_{\pi 2}} \times \left\{ 1 - \left(1 + \frac{R_F}{R_{E2}}\right) \left(\frac{R_F}{R_S \parallel R_{B1} \parallel r_{\pi 1} \parallel R_F}\right) \right\} - \left(1 + \frac{R_F}{R_{E2}}\right) I_i$$

Solve for  $V_{\pi 2}$  and substitute into Equation 4.

$$(b) R_{TH1} = 20 \parallel 80 = 16 \text{ k}\Omega = R_{B1}$$

$$V_{TH1} = \left(\frac{20}{100}\right)(10) = 2 \text{ V}$$

$$I_{BQ1} = \frac{2 - 0.7}{16 + (101)(1)} = 0.0111 \text{ mA} \Rightarrow$$

$$I_{CQ1} = 1.11 \text{ mA}$$

$$R_{TH2} = 15 \parallel 85 = 12.75 \text{ k}\Omega$$

$$V_{TH2} = \left(\frac{15}{15 + 85}\right)(10) = 1.5 \text{ V}$$

$$I_{BQ2} = \frac{1.5 - 0.7}{12.75 + (101)(0.5)} = 0.0126 \text{ mA} \Rightarrow$$

$$I_{CQ2} = 1.26 \text{ mA}$$

$$g_{m1} = \frac{1.11}{0.026} = 42.69 \text{ mA/V}$$

$$g_{m2} = \frac{1.26}{0.026} = 48.46 \text{ mA/V}$$

$$r_{\pi 1} = \frac{(100)(0.026)}{1.11} = 2.34 \text{ k}\Omega$$

$$r_{\pi 2} = \frac{(100)(0.026)}{1.26} = 2.06 \text{ k}\Omega$$

From part (a)

$$V_{\pi 2} \left(\frac{101}{2.06}\right) = \frac{V_{e2}}{(42.69)(10)} \cdot \frac{1}{2 \parallel 12.75 \parallel 2.06} \times \left\{ 1 - \left(1 + \frac{10}{0.5}\right) \left(\frac{10}{10000 \parallel 16 \parallel 2.34 \parallel 10}\right) \right\} - \left(1 + \frac{10}{0.5}\right) I_i$$

So

$$V_{\pi 2}(49.34) = -(21)I_i$$

or

$$V_{\pi 2} = -0.4256I_i$$

Now

$$I_o = -\left(\frac{4}{4 + 4}\right)(48.46)(-0.4256)I_i$$

or

$$A_i = \frac{I_o}{I_i} = 10.3$$

From Example 12.9, computer analysis showed  $A_i = 9.58$ . The difference in results is usually in the calculation of quiescent currents which leads to slight differences in the small-signal parameter values.

### 12.32

$$a. R_{TH} = 13.5 \parallel 38.3 = 9.98 \text{ k}\Omega$$

$$V_{TH} = \left(\frac{13.5}{13.5 + 38.3}\right)(10) = 2.606 \text{ V}$$

$$I_{C1} = \frac{(120)(2.606 - 0.7)}{9.98 + (121)(1)} = 1.75 \text{ mA}$$

$$V_{C1} = 10 - (1.75)(3) = 4.75 \text{ V}$$

$$I_{C2} \approx \frac{4.75 - 0.7}{8.1} = 0.50 \text{ mA}$$


$$r_{\pi 1} = \frac{(120)(0.026)}{1.75} = 1.78 \text{ k}\Omega$$

$$g_{m1} = \frac{1.75}{0.026} = 67.31 \text{ mA/V}$$

$$r_{\pi 2} = \frac{(120)(0.026)}{0.50} = 6.24 \text{ k}\Omega$$

$$g_{m2} = \frac{0.50}{0.026} = 19.23 \text{ mA/V}$$

b.

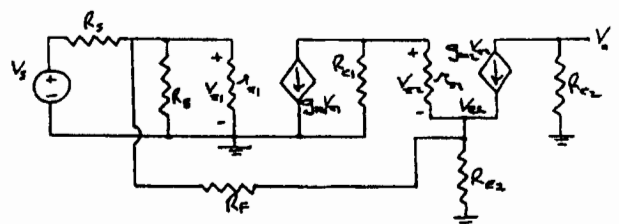

$$\frac{V_S - V_{\pi 1}}{R_S} = \frac{V_{\pi 1}}{R_B \| r_{\pi 1}} + \frac{V_{\pi 1} - V_{e 2}}{R_F} \quad (1)$$

$$g_{m 1} V_{\pi 1} + \frac{V_{\pi 2} + V_{e 2}}{R_{C 1}} + \frac{V_{\pi 2}}{r_{\pi 2}} = 0 \quad (2)$$

$$\frac{V_{\pi 2}}{r_{\pi 2}} + g_{m 2} V_{\pi 2} = \frac{V_{e 2}}{R_{E 2}} + \frac{V_{e 2} - V_{\pi 1}}{R_F} \quad (3)$$

and

$$V_o = -(g_{m 2} V_{\pi 2}) R_{C 2} \quad (4)$$

Substitute numerical values in (1), (2), and (3):

$$\frac{V_S}{0.6} = V_{\pi 1} \left[ \frac{1}{0.6} + \frac{V_{\pi 1}}{9.98 \| 1.78} + \frac{1}{1.2} \right] - \frac{V_{e 2}}{1.2}$$

or

$$V_S(1.667) = V_{\pi 1}(4.011) - V_{e 2}(0.8333) \quad (1)$$

$$(67.31)V_{\pi 1} + V_{\pi 2} \left( \frac{1}{3} + \frac{1}{6.24} \right) + \frac{V_{e 2}}{3} = 0$$

or

$$V_{\pi 1}(67.31) + V_{\pi 2}(0.4936) + V_{e 2}(0.3333) = 0 \quad (2)$$

$$V_{\pi 2} \left( \frac{1}{6.24} + 19.23 \right) = \frac{V_{e 2}}{8.1} + \frac{V_{e 2}}{1.2} - \frac{V_{\pi 1}}{1.2}$$

or

$$V_{\pi 2}(19.39) = V_{e 2}(0.9568) - V_{\pi 1}(0.8333) \quad (3)$$

From (1)

$$V_{e 2} = V_{\pi 1}(4.813) - V_S(2.00)$$

Then

$$V_{\pi 1}(67.31) + V_{\pi 2}(0.4936) + (0.3333)[V_{\pi 1}(4.813) - V_S(2.00)] = 0$$

or

$$V_{\pi 1}(68.91) + V_{\pi 2}(0.4936) - V_S(0.6666) = 0 \quad (2')$$

and

$$V_{\pi 2}(19.39) = (0.9568)[V_{\pi 1}(4.813) - V_S(2.00)] - V_{\pi 1}(0.8333)$$

or

$$V_{\pi 2}(19.39) = V_{\pi 1}(3.772) - V_S(1.914) \quad (3')$$

We find

$$V_{\pi 1} = V_S(0.009673) - V_{\pi 2}(0.007163)$$

Then

$$\begin{aligned} V_{\pi 2}(19.39) &= (3.772)[V_S(0.009673) - V_{\pi 2}(0.007163)] \\ &\quad - V_S(1.914) \end{aligned}$$

$$V_{\pi 2}(19.42) = V_S(-1.878) \text{ or } V_{\pi 2} = -V_S(0.09670)$$

so that

$$V_o = -(19.23)(4)(-V_S)(0.09670)$$

Then

$$\frac{V_o}{V_S} = 1.86$$

### 12.33

Using the circuit from Problem 12.32, we have  $R_V = \frac{V_{e 1}}{I_S}$

$$\text{where } I_S = \frac{V_S - V_{\pi 1}}{R_S}$$

From Problem 12.32

$$\begin{aligned} V_{\pi 1} &= V_S(0.009673) - V_{\pi 2}(0.007163) \\ &= V_S(0.009673) - (0.007163)(-V_S)(0.09670) \\ &= V_S(0.01037) \end{aligned}$$

So

$$R_{i f} = \frac{V_S(0.01037) \cdot (0.6)}{V_S - V_S(0.01037)} = 0.00629 \text{ k}\Omega$$

or

$$\underline{R_{i f} = 6.29 \Omega}$$

### 12.34

$$R_{TH} = 1.4 \| 17.9 = 1.298 \text{ k}\Omega$$

$$V_{TH} = \left( \frac{1.4}{1.4 + 17.9} \right) (10) = 0.7254 \text{ V}$$

$$I_{B 1} = \frac{0.7254 - 0.7}{1.298} = 0.0196 \text{ mA}$$

$$I_{C 1} = (50)(0.0196) = 0.98 \text{ mA}$$

Neglecting dc base currents,

$$V_{B 2} = 10 - (0.98)(7) = 3.14 \text{ V}$$

$$I_{E 2} = \frac{3.14 - 0.7}{0.25 + 0.5} = 3.25 \text{ mA}$$


$$I_{C 2} = \left( \frac{50}{51} \right) (3.25) = 3.19 \text{ mA}$$

$$r_{\pi 1} = \frac{(50)(0.026)}{0.98} = 1.33 \text{ k}\Omega$$

$$g_{m1} = \frac{0.98}{0.026} = 37.7 \text{ mA/V}$$

$$r_{\pi 2} = \frac{(50)(0.026)}{3.19} = 0.408 \text{ k}\Omega$$
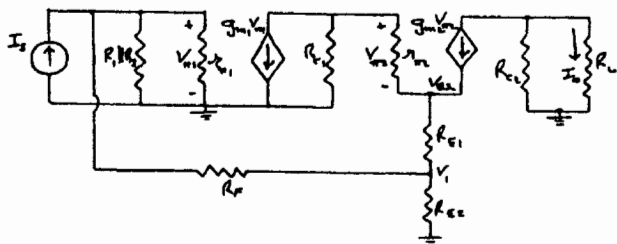
$$g_{m2} = \frac{3.19}{0.026} = 123 \text{ mA/V}$$



$$I_S = \frac{V_{\pi 1}}{R_1 \parallel R_2 \parallel r_{\pi 1}} + \frac{V_{\pi 1} - V_1}{R_F} \quad (1)$$

$$g_{m1} V_{\pi 1} + \frac{V_{\pi 2}}{r_{\pi 2}} + \frac{V_{\pi 2} + V_{e2}}{R_{C1}} = 0 \quad (2)$$

$$\frac{V_{\pi 2}}{r_{\pi 2}} + g_{m2} V_{\pi 2} = \frac{V_{e2} - V_1}{R_{E1}} \quad (3)$$

$$\frac{V_{e2} - V_{\pi 1}}{R_{E1}} = \frac{V_1}{R_{E2}} + \frac{V_1 - V_{\pi 1}}{R_F} \quad (4)$$

Enter numerical values in (1), (2), (3) and (4):

$$I_S = \frac{V_{\pi 1}}{17.9 \parallel 1.4 \parallel 1.33} + \frac{V_{\pi 1} - V_1}{5}$$

or

$$I_S = V_{\pi 1}(1.722) - V_1(0.20) \quad (1)$$

$$(37.7)V_{\pi 1} + \frac{V_{\pi 2}}{0.408} + \frac{V_{\pi 2} + V_{e2}}{7} = 0$$

or

$$V_{\pi 1}(37.7) + V_{\pi 2}(2.594) + V_{e2}(0.1429) = 0 \quad (2)$$

$$\frac{V_{\pi 2}}{0.408} + (123)V_{\pi 2} = \frac{V_{e2} - V_1}{0.25}$$

or

$$V_{\pi 2}(125.5) = V_{e2}(4) - V_1(4) \quad (3)$$

$$\frac{V_{e2} - V_1}{0.25} = \frac{V_1}{0.50} + \frac{V_1 - V_{\pi 1}}{5}$$

or

$$V_{e2}(4) = V_1(6.20) - V_{\pi 1}(0.20) \quad (4)$$

From (4):

$$V_{e2} = V_1(1.55) - V_{\pi 1}(0.05)$$

Then substituting in (3):

$$V_{\pi 2}(125.5) = (4)[V_1(1.55) - V_{\pi 1}(0.05)] - V_1(4)$$

or

$$V_{\pi 2}(125.5) = V_1(2.20) - V_{\pi 1}(0.20) \quad (3')$$

and substituting in (2):

$$V_{\pi 1}(37.7) + V_{\pi 2}(2.594) + (0.1429)[V_1(1.55) - V_{\pi 1}(0.05)] = 0$$

or

$$V_{\pi 1}(37.69) + V_{\pi 2}(2.594) + V_1(0.2215) = 0$$

Now

$$V_1 = -V_{\pi 1}(170.16) - V_{\pi 2}(11.71)$$

Then substituting in (1):

$$I_S = V_{\pi 1}(1.722) - (0.20)[-V_{\pi 1}(170.16) - V_{\pi 2}(11.71)]$$

or

$$I_S = V_{\pi 1}(35.75) + V_{\pi 2}(2.342)$$

and substituting in (3'):

$$V_{\pi 2}(125.5) = (2.20)[-V_{\pi 1}(170.16) - V_{\pi 2}(11.71)] - V_{\pi 1}(0.20)$$

or  $V_{\pi 2}(151.3) = -V_{\pi 1}(374.55)$  so that

$$V_{\pi 1} = -V_{\pi 2}(0.4040)$$

Then

$$I_S = (35.75)[-V_{\pi 2}(0.4040)] + V_{\pi 2}(2.342)$$

$$I_S = -V_{\pi 2}(12.10)$$

$$I_0 = -(g_{m2} V_{\pi 2}) \left( \frac{R_{C2}}{R_{C2} + R_L} \right)$$

$$= -(123) \left( \frac{2.2}{2.2 + 2} \right) V_{\pi 2} = -(64.43)V_{\pi 2}$$

or  $V_{\pi 2} = -(0.01552)I_0$

Then


$$\frac{I_0}{I_S} = \frac{1}{(0.01552)(12.10)} \Rightarrow \frac{I_0}{I_S} = 5.33$$

12.35

For example, use the circuit shown in Figure P12.30

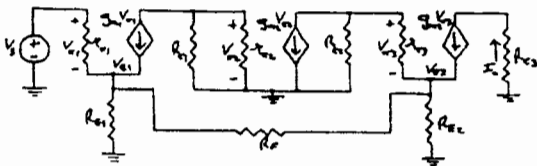12.36

$r_{\pi 1} = 6.24 \text{ k}\Omega$ ,  $r_{\pi 2} = 3.12 \text{ k}\Omega$ ,  $r_{\pi 3} = 1.56 \text{ k}\Omega$   
 $g_{m1} = 19.23 \text{ mA/V}$ ,  $g_{m2} = 38.46 \text{ mA/V}$ ,  
 $g_{m3} = 76.92 \text{ mA/V}$



$$V_S = V_{\pi 1} + V_{e1} \quad (1)$$

$$\frac{V_{\pi 1}}{r_{\pi 1}} + g_{m1} V_{\pi 1} = \frac{V_{e1}}{R_{E1}} + \frac{V_{e1} - V_{e3}}{R_F} \quad (2)$$

$$V_{\pi 2} = -g_{m1} V_{\pi 1} (R_{C1} \parallel r_{\pi 2}) \quad (3)$$

$$g_{m2} V_{\pi 2} + \frac{V_{\pi 3} + V_{e3}}{R_{C2}} + \frac{V_{\pi 3}}{r_{\pi 3}} = 0 \quad (4)$$

$$\frac{V_{\pi 3}}{r_{\pi 3}} + g_{m3} V_{\pi 3} = \frac{V_{e3}}{R_{E2}} + \frac{V_{e3} - V_{e1}}{R_F} \quad (5)$$

Enter numerical values in (2)-(5):

$$\frac{V_{\pi 1}}{6.24} + (19.23)V_{\pi 1} = V_{e1} \left( \frac{1}{0.1} + \frac{1}{0.8} \right) - V_{e3} \left( \frac{1}{0.8} \right)$$

or  
 $V_{\pi 1}(19.39) = V_{e1}(11.25) - V_{e3}(1.25) \quad (2)$

$$V_{\pi 2} = -(19.23)V_{\pi 1}(5 \parallel 3.12) = -(36.94)V_{\pi 1} \quad (3)$$

$$(38.46)V_{\pi 2} + V_{\pi 3} \left( \frac{1}{2} + \frac{1}{1.56} \right) + V_{e3} \left( \frac{1}{2} \right) = 0$$

or  
 $V_{\pi 2}(38.46) + V_{\pi 3}(1.141) + V_{e3}(0.5) = 0 \quad (4)$

$$V_{\pi 3} \left( \frac{1}{1.56} + 76.92 \right) = V_{e3} \left( \frac{1}{0.1} + \frac{1}{0.8} \right) - V_{e3} \left( \frac{1}{0.8} \right)$$

or  
 $V_{\pi 3}(77.56) = V_{e3}(11.25) - V_{e1}(1.25) \quad (5)$

From (1)  $V_{\pi 1} = V_S - V_{e1}$

Then

$$(V_S - V_{e1})(19.39) = V_{e1}(11.25) - V_{e3}(1.25)$$

or

$$V_S(19.39) = V_{e1}(30.64) - V_{e3}(1.25) \quad (2')$$

$$V_{\pi 2} = -V_S(36.94) + V_{e1}(36.94) \quad (3')$$

$$(38.46)[-V_S(36.94) + V_{e1}(36.94)] + V_{\pi 3}(1.141) + V_{e3}(0.5) = 0 \quad (4')$$

From (5):  $V_{e3} = V_{\pi 3}(6.894) + V_{e1}(0.1111)$

Then

$$V_S(19.39) = V_{e1}(30.64) - (1.25)[V_{\pi 3}(6.894) + V_{e1}(0.1111)]$$

or

$$V_S(19.39) = V_{e1}(30.50) - V_{\pi 3}(8.6175) \quad (2'')$$

and

$$-V_S(1420.7) + V_{e1}(1420.7) + V_{\pi 3}(1.141) + (0.5)[V_{\pi 3}(6.894) + V_{e1}(0.1111)] = 0$$

or

$$-V_S(1420.7) + V_{e1}(1420.76) + V_{\pi 3}(4.588) = 0 \quad (4'')$$

From (2''):

$$V_{e1} = V_S(0.6357) + V_{\pi 3}(0.2825)$$

Then substituting in (4''):

$$-V_S(1420.7) + (1420.76)[V_S(0.6357) + V_{\pi 3}(0.2825)] + V_{\pi 3}(4.588) = 0$$

$$-V_S(517.5) + V_{\pi 3}(405.95) = 0$$

Now

$$I_0 = g_{m3} V_{\pi 3} = 76.92 V_{\pi 3} \text{ or } V_{\pi 3} = I_0(0.0130)$$

Then  $-V_S(517.5) + I_0(0.0130)(405.95) = 0$

or

$$\underline{\underline{\frac{I_0}{V_S} = 98.06 \text{ mA/V}}}$$


12.38

$$r_{\pi 1} = r_{\pi 2} = \frac{(100)(0.026)}{0.5} = 5.2 \text{ k}\Omega$$

$$g_{m1} = g_{m2} = \frac{0.5}{0.026} = 19.23 \text{ mA/V}$$

$$r_{\pi 3} = \frac{(100)(0.026)}{2} = 1.3 \text{ k}\Omega$$
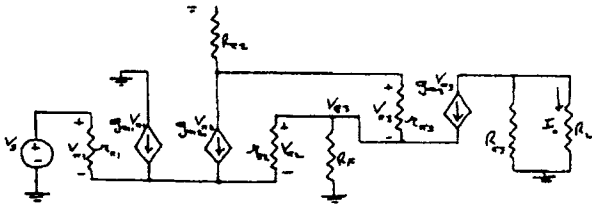
$$g_{m3} = \frac{2}{0.026} = 76.92 \text{ mA/V}$$



$$\frac{V_{\pi 1}}{r_{\pi 1}} + g_{m1} V_{\pi 1} + g_{m2} V_{\pi 2} + \frac{V_{\pi 2}}{r_{\pi 2}} = 0 \quad (1)$$

Since  $r_{\pi 1} = r_{\pi 2}$  and  $g_{m1} = g_{m2}$ , then  $V_{\pi 1} = -V_{\pi 2}$

$$V_S = V_{\pi 1} - V_{\pi 2} + V_{e3} = -2V_{\pi 2} + V_{e3} \quad (2)$$

$$g_{m2} V_{\pi 2} + \frac{V_{\pi 3}}{r_{\pi 3}} + \frac{V_{\pi 3} + V_{e3}}{R_{C2}} = 0 \quad (3)$$

$$\frac{V_{\pi 3}}{r_{\pi 3}} + g_{m3} V_{\pi 3} = \frac{V_{e3}}{R_F} + \frac{V_{\pi 2}}{r_{\pi 2}} \quad (4)$$

$$I_0 = -\left(\frac{R_{C3}}{R_{C3} + R_L}\right)(g_{m3} V_{\pi 3}) \quad (5)$$

From (2):  $V_{e3} = V_S + 2V_{\pi 2}$

$$(19.23)V_{\pi 2} + \frac{V_{\pi 3}}{1.3} + \frac{V_{\pi 3}}{18.6} + \frac{1}{18.6}(V_S + 2V_{\pi 2}) = 0$$

or

$$(19.23)V_{\pi 2} + (0.8230)V_{\pi 3} + (0.05376)V_S = 0 \quad (3')$$

$$V_{\pi 3} \left(\frac{1}{1.3} + 76.92\right) = \left(\frac{1}{10}\right)(V_S + 2V_{\pi 2}) + \frac{V_{\pi 2}}{5.2}$$

or

$$(77.69)V_{\pi 3} = (0.3923)V_{\pi 2} + (0.1)V_S \quad (4')$$

$$I_0 = -\left(\frac{2}{2+1}\right)(76.92)V_{\pi 3} = -(51.28)V_{\pi 3} \quad (5')$$

From (3'):

$$V_{\pi 2} = -(0.04255)V_{\pi 3} - (0.002780)V_S$$

Then

$$(77.69)V_{\pi 3} = (0.3923)[-(0.04255)V_{\pi 3} - (0.002780)V_S] + (0.1)V_S$$

$$(77.71)V_{\pi 3} = (0.0989)V_S$$

or

$$V_{\pi 3} = (0.001273)V_S$$

so that


$$I_0 = -(51.28)(0.001273)V_S$$

or

$$\frac{I_0}{V_S} = -(0.0653) \text{ mA/V}$$

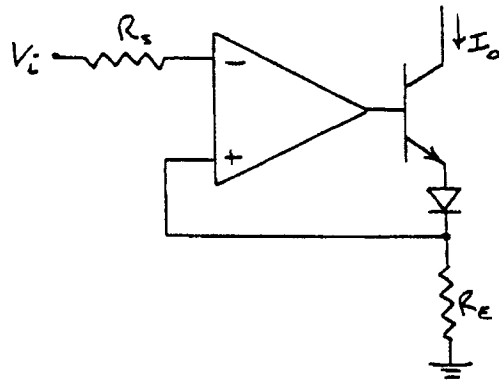12.39

Use the basic circuit shown in Figure 12.27.



For the ideal case

$$\frac{I_0}{V_i} = \frac{1}{R_E}$$

we want

$$\frac{I_0}{V_i} = 10^{-3} \text{ A/V} = 1 \text{ mA/V}$$

Set  $R_E = 1 \text{ k}\Omega$

Since the op-amp has a finite gain, finite input resistance, and finite output resistance, the closed-loop gain is slightly less than the ideal.  $R_E$  will need to be slightly decreased to increase the gain.

12.40

dc analysis


$$I_E R_E + V_{EB}(\text{on}) + I_B R_B + V_{CC} = 0$$

$$I_B = \frac{5 - 0.7}{100 + (51)(0.5)} = 0.0343$$

$$I_C = (50)(0.0343) = 1.71 \text{ mA}$$

$$\text{Then } r_{\pi} = \frac{(50)(0.026)}{1.71} = 0.760 \text{ k}\Omega$$
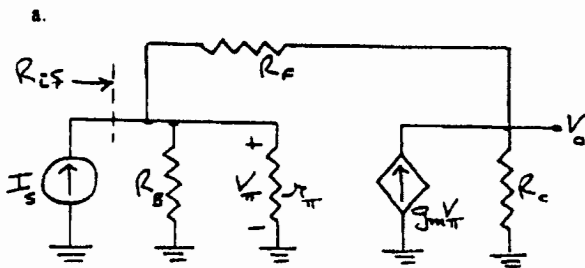
$$g_m = \frac{1.71}{0.026} = 65.77 \text{ mA/V}$$



To determine  $R_o$ :

$$I_S + \frac{V_\pi}{R_B \parallel r_\pi} + \frac{V_o - (-V_\pi)}{R_F} = 0 \quad (1)$$

$$g_m V_\pi = \frac{V_o}{R_C} + \frac{V_o - (-V_\pi)}{R_F} \quad (2)$$

Now from (2):

$$(65.77)V_\pi - \frac{V_\pi}{10} = V_o \left( \frac{1}{1} + \frac{1}{10} \right)$$

$$(65.67)V_\pi = V_o(1.10)$$

or

$$V_o = (59.7)V_\pi$$

and from (1):

$$I_S + \frac{V_\pi}{100 \parallel 0.760} + \frac{V_\pi}{10} + \frac{V_o}{10} = 0$$


$$I_S + V_\pi(0.8543) + (0.1)(59.7)V_\pi = 0$$

$$I_S = -V_\pi(6.824)$$

Now

$$R_{if} = \frac{(-V_\pi)}{I_S} \Rightarrow R_{if} = 147 \Omega$$

To determine  $R_{of}$ :

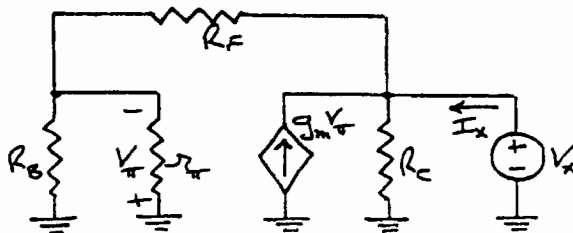

$$I_X = \frac{V_X}{R_C} + \frac{V_X}{R_F + R_B \parallel r_\pi} - g_m V_\pi \quad (3)$$

$$V_\pi = \left( \frac{-(R_B \parallel r_\pi)}{(R_B \parallel r_\pi) + R_F} \right) (V_X) \quad (4)$$

Now

$$V_\pi = \left( \frac{-(100 \parallel 0.760)}{(100 \parallel 0.760) + 10} \right) (V_X) = -(0.07014)V_X$$

so

$$I_X = V_X \left( \frac{1}{1} + \frac{1}{10.754} + (65.77)(0.07014) \right)$$

$$R_{of} = \frac{V_X}{I_X} \Rightarrow R_{of} = 175 \Omega$$

b. From part (a), we find

$$V_\pi = -\frac{I_S}{6.824}$$

then

$$V_o = (59.7) \left( \frac{-I_S}{6.824} \right)$$

or

$$\frac{V_o}{V_S} = -8.75 \text{ k}\Omega$$

c. If capacitance is finite, a phase shift will be introduced.

12.41

dc analysis:  $V_{GS} = V_{DS}$

$$I_D = \frac{V_{DD} - V_{GS}}{R_D} = K_n (V_{GS} - V_{TN})^2$$

$$10 - V_{GS} = (0.20)(8)(V_{GS} - 2)^2$$


$$10 - V_{GS} = 1.6(V_{GS}^2 - 4V_{GS} + 4)$$

$$1.6V_{GS}^2 - 5.4V_{GS} - 3.6 = 0$$

$$V_{GS} = \frac{5.4 \pm \sqrt{(5.4)^2 + 4(1.6)(3.6)}}{2(1.6)} = 3.95 \text{ V}$$

$$I_D = \frac{10 - 3.95}{8} = 0.756 \text{ mA}$$
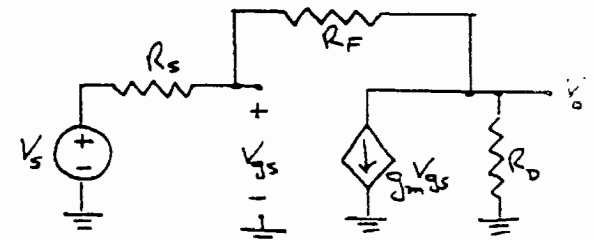
$$g_m = 2\sqrt{K_n I_D} = 2\sqrt{(0.2)(0.756)} \Rightarrow g_m = 0.778 \text{ mA/V}$$



a.

$$\frac{V_{gs} - V_S}{R_S} + \frac{V_{gs} - V_o}{R_F} = 0$$

$$V_{gs} \left( \frac{1}{R_S} + \frac{1}{R_F} \right) = \frac{V_S}{R_S} + \frac{V_o}{R_F} \quad (1)$$

$$\frac{V_0}{R_D} + g_m V_{gs} + \frac{V_0 - V_{gs}}{R_F} = 0$$

$$V_0 \left( \frac{1}{R_D} + \frac{1}{R_F} \right) = V_{gs} \left( \frac{1}{R_F} - g_m \right) \quad (2)$$

So from (1):

$$V_{gs} \left( \frac{1}{10} + \frac{1}{100} \right) = \frac{V_S}{10} + \frac{V_0}{100}$$

or

$$V_{gs}(0.11) = V_S(0.10) + V_0(0.010)$$

$$V_{gs} = V_S(0.909) + V_0(0.0909)$$

Then from (2):

$$V_0 \left( \frac{1}{8} + \frac{1}{100} \right) = V_{gs} \left( \frac{1}{100} - 0.778 \right)$$

$$V_0(0.135) = V_{gs}(-0.768)$$

$$= (-0.768)[V_S(0.909) + V_0(0.0909)]$$

$$V_0(0.2048) = -V_S(0.6981)$$

so

$$A_v = \frac{V_0}{V_S} = -3.41$$

b. We have

$$V_{gs} = V_S(0.909) + V_0(0.0909)$$

$$= V_S(0.909) + (0.0909)(-3.41V_S)$$

$$= 0.599V_S$$

Now

$$A_{zf} = \frac{V_0}{I_S} = \frac{V_0}{\frac{V_S - V_{gs}}{R_S}} = \frac{(-3.41V_S)R_S}{V_S - 0.599V_S}$$


or

$$A_{zf} = \frac{(-3.41)(10)}{0.401} \Rightarrow A_{zf} = -85.0 \text{ V/ma}$$

$$c. R_{if} = \frac{V_{gs}}{I_S} = \frac{V_{gs}}{\frac{V_S - V_{gs}}{R_S}} = \frac{0.599V_S}{0.401V_S} \cdot (10)$$

$$\Rightarrow R_{if} = 14.9 \text{ k}\Omega$$

d.

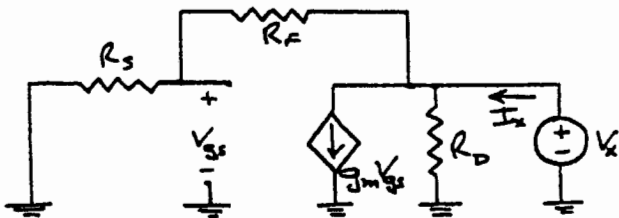

$$I_X = \frac{V_X}{R_D} + g_m V_{gs} + \frac{V_X}{R_S + R_F}$$

$$V_{gs} = \left( \frac{R_S}{R_S + R_F} \right) V_X = \left( \frac{10}{10 + 100} \right) V_X$$

$$= (0.0909)V_X$$

$$I_X = V_X \left[ \frac{1}{8} + (0.778)(0.0909) + \frac{1}{10 + 100} \right]$$

$$\frac{I_X}{V_X} = \frac{1}{R_{of}} = 0.2048 \Rightarrow R_{of} = 4.88 \text{ k}\Omega$$

12.42

$$\text{As } g_m \rightarrow \infty, \frac{V_0}{V_S} = \frac{-R_F}{R_S} = \frac{-100}{10} = -10$$

To be within 10% of ideal,

$$\frac{V_0}{V_S} = -10(0.9) = -9$$

From Problem 12.41, we had

$$V_{gs} = V_S(0.909) + V_0(0.0909)$$

$$= V_S(0.909) + (-9V_S)(0.0909)$$

$$= 0.0909V_S$$

Also from Problem 12.41, we had

$$V_0(0.135) = V_{gs}(0.010 - g_m)$$

or

$$(-9V_S)(0.135) = (0.0909)V_S(0.010 - g_m)$$

$$-1.215 = 0.000909 - 0.0909g_m$$

or

$$g_m = 13.36 \text{ mA/V}$$

12.43

dc analysis

$$R_{TH} = 24 \parallel 150 = 20.7 \text{ k}\Omega$$


$$V_{TH} = \left( \frac{24}{24 + 150} \right) (12) = 1.655 \text{ V}$$

$$I_{BQ} = \frac{1.655 - 0.7}{20.7 + (151)(1)} = 0.00556 \text{ mA}$$

$$\text{so } I_{CQ} = 0.834 \text{ mA}$$

$$r_\pi = \frac{(150)(0.026)}{0.834} = 4.68 \text{ k}\Omega$$
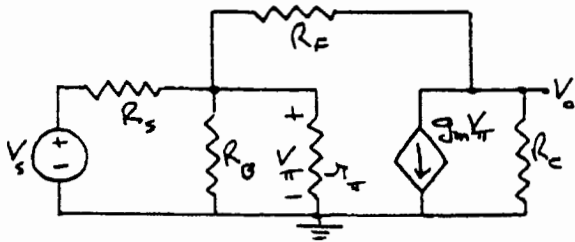
$$g_m = \frac{0.834}{0.026} = 32.08 \text{ mA/V}$$



$$\frac{V_S - V_\pi}{R_S} = \frac{V_\pi}{R_B \parallel r_\pi} + \frac{V_\pi - V_o}{R_F} \quad (1)$$

$$g_m V_\pi + \frac{V_o}{R_C} + \frac{V_o - V_\pi}{R_F} = 0 \quad (2)$$

From (1):

$$\frac{V_S}{5} = V_\pi \left[ \frac{1}{5} + \frac{1}{20.7 \parallel 4.68} + \frac{1}{R_F} \right] - \frac{V_o}{R_F}$$

or

$$V_S(0.20) = V_\pi \left( 0.4620 + \frac{1}{R_F} \right) - \frac{V_o}{R_F}$$

From (2):

$$\left( 32.08 - \frac{1}{R_F} \right) V_\pi + V_o \left( \frac{1}{6} + \frac{1}{R_F} \right) = 0$$

so

$$V_\pi = \frac{-V_o \left( 0.1667 + \frac{1}{R_F} \right)}{\left( 32.08 - \frac{1}{R_F} \right)}$$

Then

$$V_S(0.20) = \left( 0.4620 + \frac{1}{R_F} \right) \left[ \frac{-V_o \left( 0.1667 + \frac{1}{R_F} \right)}{\left( 32.08 - \frac{1}{R_F} \right)} \right] - \frac{V_o}{R_F}$$

Neglect the  $R_F$  in the denominator term. Now

$$\frac{V_o}{V_S} = -5 \Rightarrow V_S = -\frac{V_o}{5} = -V_o(0.20)$$

$$-V_o(0.20)(0.20)R_F = (0.4620R_F + 1) \left[ \frac{-V_o(0.1667R_F + 1)}{32.08R_F} \right] - V_o$$

$$-1.283R_F^2 = -(0.4620R_F + 1)(0.1667R_F + 1) - 32.08R_F$$

$$1.206R_F^2 - 32.71R_F - 1 = 0$$

$$R_F = \frac{32.71 \pm \sqrt{(32.71)^2 + 4(1.206)(1)}}{2(1.206)}$$

so that

$$R_F = 27.2 \text{ k}\Omega$$

12.44

dc analysis

$$R_{TH} = 4 \parallel 15 = 3.16 \text{ k}\Omega = R_B$$


$$V_{TH} = \left( \frac{4}{4 + 15} \right) 12 = 2.526 \text{ V}$$

$$I_{BQ} = \frac{2.526 - 0.7}{3.16 + (181)(4)} = 0.00251$$

$$I_{CQ} = 0.452 \text{ mA}$$

$$r_\pi = \frac{(180)(0.026)}{0.452} = 10.4 \text{ k}\Omega$$
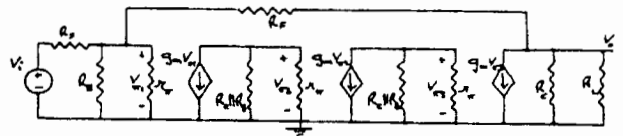
$$g_m = \frac{0.452}{0.026} = 17.4 \text{ mA/V}$$



$$\frac{V_i - V_{\pi 1}}{R_S} = \frac{V_{\pi 1}}{R_B \parallel r_\pi} + \frac{V_{\pi 1} - V_o}{R_F} \quad (1)$$

$$g_m V_{\pi 1} + \frac{V_{\pi 2}}{R_C \parallel R_B \parallel r_\pi} = 0 \quad (2)$$

$$g_m V_{\pi 2} + \frac{V_{\pi 3}}{R_C \parallel R_B \parallel r_\pi} = 0 \quad (3)$$

$$g_m V_{\pi 3} + \frac{V_o}{R_C} + \frac{V_o}{R_L} + \frac{V_o - V_{\pi 3}}{R_F} = 0 \quad (4)$$

Now

$$R_C \parallel R_B \parallel r_\pi = 8 \parallel 3.16 \parallel 10.4 = 1.86 \text{ k}\Omega$$

$$R_B \parallel r_\pi = 3.16 \parallel 10.4 = 2.42 \text{ k}\Omega$$

Now substituting in (2):

$$(17.4)V_{\pi 1} + \frac{V_{\pi 2}}{1.86} = 0 \text{ or } V_{\pi 2} = -(32.36)V_{\pi 1}$$

and substituting in (3):

$$(17.4)V_{\pi 2} + \frac{V_{\pi 3}}{1.86} = 0$$

$$(17.4)[-(32.36)V_{\pi 1}] + \frac{V_{\pi 3}}{1.86} = 0$$

$$\text{or } V_{\pi 3} = (1047.3)V_{\pi 1}$$

Substitute numerical values in (1):

$$\frac{V_i}{10} = V_{\pi 1} \left( \frac{1}{10} + \frac{1}{2.42} + \frac{1}{R_F} \right) - \frac{V_0}{R_F}$$

or

$$V_i(0.10) = V_{\pi 1} \left( 0.513 + \frac{1}{R_F} \right) - \frac{V_0}{R_F}$$

Substitute numerical values in (4):

$$(17.4)(1047.3)V_{\pi 1} + V_0 \left( \frac{1}{8} + \frac{1}{4} + \frac{1}{R_F} \right) - \frac{V_{\pi 1}}{R_F} = 0$$

$$V_{\pi 1} \left( 1.822 \times 10^4 - \frac{1}{R_F} \right) + V_0 \left( 0.375 + \frac{1}{R_F} \right) = 0$$

$$V_{\pi 1} = \frac{-V_0 \left( 0.375 + \frac{1}{R_F} \right)}{1.822 \times 10^4 - \frac{1}{R_F}}$$

so that

$$V_i(0.10)$$

$$= \left( 0.513 + \frac{1}{R_F} \right) \left[ \frac{-V_0 \left( 0.375 + \frac{1}{R_F} \right)}{1.822 \times 10^4 - \frac{1}{R_F}} \right] - \frac{V_0}{R_F}$$

$$\text{We have } \frac{V_0}{V_i} = -80 \text{ or } V_i = -\frac{V_0}{80}$$

$$-\frac{(0.10)}{80}$$

$$= \left( 0.513 + \frac{1}{R_F} \right) \left[ \frac{-\left( 0.375 + \frac{1}{R_F} \right)}{1.822 \times 10^4 - \frac{1}{R_F}} \right] - \frac{1}{R_F}$$

Neglect the  $1/R_F$  term in the denominator.

$$\begin{aligned} - (0.00125 R_F) &= - \frac{(0.513 R_F + 1)(0.375 R_F + 1)}{1.822 \times 10^4 R_F} - 1 \\ 22.775 R_F^2 &= (0.513 R_F + 1)(0.375 R_F + 1) + 1.822 \times 10^4 R_F \end{aligned}$$


We find

$$\begin{aligned} 22.58 R_F^2 - 1.822 \times 10^4 R_F - 1 &= 0 \\ R_F &= \frac{1.822 \times 10^4 \pm \sqrt{(1.822 \times 10^4)^2 + 4(22.58)(1)}}{2(22.58)} \end{aligned}$$

or

$$\underline{R_F = 0.807 \text{ M}\Omega}$$

12.45

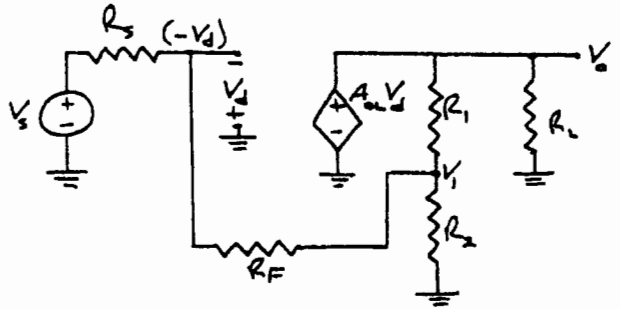

a.

$$\frac{V_S - (-V_d)}{R_S} = \frac{-V_d - V_1}{R_F}$$

or

$$V_d \left( \frac{1}{R_S} + \frac{1}{R_F} \right) + \frac{V_S}{R_S} + \frac{V_1}{R_F} = 0 \quad (1)$$

$$\frac{V_0 - V_1}{R_1} = \frac{V_1}{R_2} + \frac{V_1 - (-V_d)}{R_F}$$

or

$$\frac{V_0}{R_1} = V_1 \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_F} \right) + \frac{V_d}{R_F} \quad (2)$$

$$\text{and } V_0 = A_{oL} V_d \text{ or } V_d = \frac{V_0}{A_{oL}}$$

Substitute numerical values in (1) and (2):

$$\frac{V_0}{10^4} \left( \frac{1}{5} + \frac{1}{10} \right) + \frac{V_S}{5} + \frac{V_1}{10} = 0$$

or

$$V_0(0.3 \times 10^{-4}) + V_S(0.20) + V_1(0.10) = 0 \quad (1)$$

$$\frac{V_0}{50} = V_1 \left( \frac{1}{50} + \frac{1}{10} + \frac{1}{10} \right) + \frac{V_0}{10^4} \left( \frac{1}{10} \right)$$

or

$$V_0(0.02 - 10^{-5}) = V_1(0.22) \quad (2)$$

$$\text{Then } V_1 = V_0 \left( \frac{0.02 - 10^{-5}}{0.22} \right)$$

and

$$V_0(0.3 \times 10^{-4}) + V_S(0.20)$$

$$+ (0.10) \left[ V_0 \left( \frac{0.02 - 10^{-5}}{0.22} \right) \right] = 0$$

$$V_0 [0.3 \times 10^{-4} - 0.4545 \times 10^{-5} + 0.00909] + V_S(0.20) = 0$$

$$\text{Then } \frac{V_0}{V_S} = \frac{-0.20}{9.115 \times 10^{-3}} \Rightarrow \frac{V_0}{V_S} = -21.94$$

$$\text{b. } R_{if} = \frac{-V_d}{V_S - (-V_d)} = \frac{-V_d \cdot R_S}{V_S + V_d}$$

$$\text{Now } V_d = \frac{V_0}{A_{oL}} = \frac{-21.94 V_S}{10^4}$$

$$\text{Then } R_{if} = \frac{(21.94 \times 10^{-4})(5)}{1 - 21.94 \times 10^{-4}}$$

$$\text{or } R_{if} = 1.099 \times 10^{-2} \text{ k}\Omega$$

$$\Rightarrow \underline{R_{if} = 10.99 \Omega}$$

c. Because of the  $A_{oL} V_d$  source,


$$\underline{R_{of} = 0}$$

12.46

For example, use the circuit shown in Figure 12.41

12.47

Break the loop

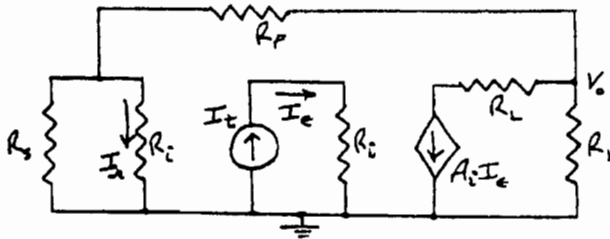

$$I_t = I_e$$

$$\text{Now } A_i I_t + \frac{V_0}{R_1} + \frac{V_0}{R_F + R_S \parallel R_i} = 0$$

$$I_r = \left( \frac{R_S}{R_S + R_i} \right) \cdot \frac{V_0}{R_F + R_S \parallel R_i}$$

$$\text{or } V_0 = I_r \left( \frac{R_S + R_i}{R_S} \right) \cdot (R_F + R_S \parallel R_i)$$


Then

$$A_i I_t + \left( \frac{1}{R_1} + \frac{1}{R_F + R_S \parallel R_i} \right) \times \left[ I_r \left( \frac{R_S + R_i}{R_S} \right) (R_F + R_S \parallel R_i) \right] = 0$$

$$T = -\frac{I_r}{I_t} \Rightarrow$$

$$T = \frac{A_i}{\left[ \frac{1}{R_1} + \frac{1}{R_F + R_S \parallel R_i} \right] \left( \frac{R_S + R_i}{R_S} \right) (R_F + R_S \parallel R_i)}$$

12.48

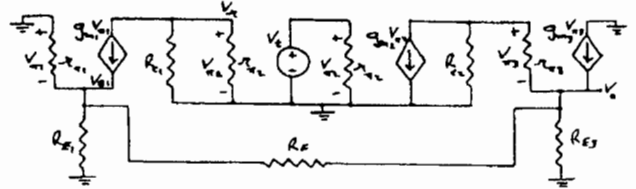

$$\frac{V_{\pi 1}}{r_{\pi 1}} + g_{m1} V_{\pi 1} = \frac{V_{e1}}{R_{E1}} + \frac{V_{e1} - V_0}{R_F} \quad (1)$$

$$g_{m1} V_{\pi 1} + \frac{V_r}{R_{C1} \parallel r_{\pi 2}} = 0$$

$$\Rightarrow V_r = -(g_{m1} V_{\pi 1})(R_{C1} \parallel r_{\pi 2}) \quad (2)$$

$V_{\pi 2} = V_r$  so that

$$g_{m2} V_r + \frac{V_{\pi 3} + V_0}{R_{C2}} + \frac{V_{\pi 3}}{r_{\pi 3}} = 0 \quad (3)$$

$$\frac{V_{\pi 3}}{r_{\pi 3}} + g_{m3} V_{\pi 3} = \frac{V_0}{R_{E3}} + \frac{V_0 - V_{e1}}{R_F} \quad (4)$$

From (4):

$$V_0 \left( \frac{1}{R_{E3}} + \frac{1}{R_F} \right) = V_{\pi 3} \left( \frac{1}{r_{\pi 3}} + g_{m3} \right) + \frac{V_{e1}}{R_F}$$

But  $V_{e1} = -V_{\pi 1}$

$$\text{so } V_0 = \frac{V_{\pi 3} \left( \frac{1}{r_{\pi 3}} + g_{m3} \right) - \frac{V_{\pi 1}}{R_F}}{\left( \frac{1}{R_{E3}} + \frac{1}{R_F} \right)}$$

Then


$$V_{\pi 1} \left[ \left( \frac{1}{r_{\pi 1}} + g_{m1} \right) - \left( \frac{1}{R_{E1}} + \frac{1}{R_F} \right) \right] = \frac{-V_{\pi 3} \left( \frac{1}{r_{\pi 3}} + g_{m3} \right) + \frac{V_{\pi 1}}{R_F}}{R_F \cdot \left( \frac{1}{R_{E3}} + \frac{1}{R_F} \right)} \quad (1')$$

and

$$g_{m2} V_r + V_{\pi 3} \left( \frac{1}{R_{C2}} + \frac{1}{r_{\pi 3}} \right) + \frac{V_{\pi 3} \left( \frac{1}{r_{\pi 3}} + g_{m3} \right) - \frac{V_{\pi 1}}{R_F}}{R_{C2} \cdot \left( \frac{1}{R_{E3}} + \frac{1}{R_F} \right)} = 0 \quad (3')$$

From (3'), solve for  $V_{\pi 3}$  and substitute into (1'). Then from (1'), solve for  $V_{\pi 1}$  and substitute into (2). Then  $T = -\frac{V_r}{V_t}$ .

12.49

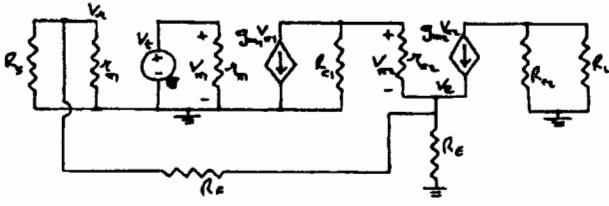

$$\frac{V_r}{R_S} + \frac{V_r}{r_{\pi 1}} + \frac{V_r - V_e}{R_F} = 0 \quad (1)$$

$$g_{m1} V_i + \frac{V_{\pi 2} + V_e}{R_{C1}} + \frac{V_{\pi 2}}{r_{\pi 2}} = 0 \quad (2)$$

$$\frac{V_{\pi 2}}{r_{\pi 2}} + g_{m2} V_{\pi 2} = \frac{V_e}{R_E} + \frac{V_e - V_r}{R_F} \quad (3)$$

Using the parameters from Problem 12.29, we obtain

$$V_r \left( \frac{1}{10} + \frac{1}{15.8} + \frac{1}{10} \right) - \frac{V_e}{10} = 0$$

or

$$V_r(0.2633) = V_e(0.10) \quad (1)$$

$$(7.62)V_i + V_{\pi 2} \left( \frac{1}{40} + \frac{1}{2.28} \right) + \frac{V_e}{40} = 0$$

or

$$V_i(7.62) + V_{\pi 2}(0.4636) + V_e(0.025) = 0 \quad (2)$$

$$V_{\pi 2} \left( \frac{1}{2.28} + 52.7 \right) = V_e \left( \frac{1}{1} + \frac{1}{10} \right) - \frac{V_r}{10}$$

or

$$V_{\pi 2}(53.14) = V_e(1.10) - V_r(0.10)$$

Then

$$V_{\pi 2} = V_e(0.0207) - V_r(0.001882) \quad (3)$$

Substituting in (2):

$$V_i(7.62) + (0.4636)[V_e(0.0207) - V_r(0.001882)] + V_e(0.025) = 0$$

or

$$V_i(7.62) + V_e(0.03460) - V_r(0.0008725) = 0$$

 From (1)  $V_e = V_r(2.633)$ 

Then

$$V_i(7.62) + V_r(2.633)(0.03460) - V_r(0.0008725) = 0$$


$$V_i(7.62) + V_r(0.09023) = 0$$

$$\text{or } \frac{V_r}{V_i} = -84.45$$

Now

$$T = -\frac{V_r}{V_i} \Rightarrow T = 84.45$$

12.50

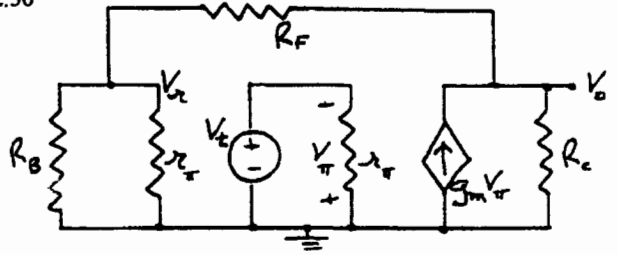

$$V_r = -V_i$$

$$g_m V_r = \frac{V_0}{R_C} + \frac{V_0}{R_F + R_B || r_{\pi}} \quad (1)$$

and

$$V_r = \left( \frac{R_B || r_{\pi}}{R_B || r_{\pi} + R_F} \right) V_0 \quad (2)$$

Now

$$(65.77)V_r = V_0 \left( \frac{1}{1} + \frac{1}{10 + 100 || 0.760} \right)$$

$$\text{or } (65.77)V_r = V_0(1.0930)$$

and

$$V_r = \left( \frac{0.754}{10 + 0.754} \right) V_0 = (0.07011)V_0$$

$$\text{so } V_0 = (14.26)V_r$$

$$\text{Then } (65.77)(-V_i) = (14.26)V_r(1.0930)$$

$$\frac{V_r}{V_i} = -4.22 \text{ so that } T = 4.22$$

12.51

$$\text{a. } \phi = -\tan^{-1} \left( \frac{f}{5 \times 10^2} \right) - 2 \tan^{-1} \left( \frac{f}{10^4} \right)$$

or

$$-180 = -\tan^{-1} \left( \frac{f_{180}}{5 \times 10^2} \right) - 2 \tan^{-1} \left( \frac{f_{180}}{10^4} \right)$$

$$\Rightarrow f_{180} \approx 1.05 \times 10^4 \text{ Hz}$$

b.

$$|T(f_{180})| = 1$$

$$= \frac{\beta(10^5)}{\sqrt{1 + \left( \frac{1.05 \times 10^4}{5 \times 10^2} \right)^2} \left[ 1 + \left( \frac{1.05 \times 10^4}{10^4} \right)^2 \right]}$$

$$1 = \frac{\beta(10^5)}{(21.02)(2.105)} \quad \text{or}$$

$$\beta = 4.42 \times 10^{-4}$$

12.52

$$A = \frac{5 \times 10^3}{\left(1 + j \frac{f}{10^4}\right) \left(1 + j \frac{f}{10^5}\right)^2}$$

$$\text{Phase} = \phi = -\tan^{-1}\left(\frac{f}{10^4}\right) - 2 \tan^{-1}\left(\frac{f}{10^5}\right)$$

By trial and error, when  $f = 1.095 \times 10^5$  Hz,  $\phi \cong 180^\circ$

For  $|T| = 1$  at  $f = 1.095 \times 10^5$  Hz,

$$1 = \frac{\beta(5 \times 10^3)}{\sqrt{1 + \left(\frac{f}{10^4}\right)^2} \cdot \left[1 + \left(\frac{f}{10^5}\right)^2\right]} \Rightarrow$$

$$1 = \frac{\beta(5 \times 10^3)}{(10.996)(2.199)} \Rightarrow \beta = 4.84 \times 10^{-3}$$

12.53

$$\phi = -\tan^{-1}\left(\frac{f}{10^4}\right) - \tan^{-1}\left(\frac{f}{5 \times 10^4}\right) - \tan^{-1}\left(\frac{f}{10^5}\right)$$

At  $f = 8.1 \times 10^4$  Hz,  $\phi = -180.28^\circ$

Determine  $|T(f)|$  at this frequency.

$$\begin{aligned} |T| &= \beta(10^3) \times \frac{1}{\sqrt{1 + \left(\frac{8.1 \times 10^4}{10^4}\right)^2}} \\ &\times \frac{1}{\sqrt{1 + \left(\frac{8.1 \times 10^4}{5 \times 10^4}\right)^2}} \times \frac{1}{\sqrt{1 + \left(\frac{8.1 \times 10^4}{10^5}\right)^2}} \\ &= \frac{\beta(10^3)}{(8.161)(1.904)(1.287)} \end{aligned}$$

a. For  $\beta = 0.005$

$$|T(f)| = 0.250 < 1 \Rightarrow \text{Stable}$$

b. For  $\beta = 0.05$

$$|T(f)| = 2.50 > 1 \Rightarrow \text{Unstable}$$

12.54

(b) Phase margin =  $80^\circ \Rightarrow \phi = -100^\circ$


$$\phi = -100 = -2 \tan^{-1}\left(\frac{f}{10^3}\right) - \tan^{-1}\left(\frac{f}{5 \times 10^4}\right)$$

By trial and error,  $f = 1.16 \times 10^3$  Hz

Then

$$\begin{aligned} |T| = 1 &= \frac{\beta(5 \times 10^3)}{\left(\sqrt{1 + \left(\frac{1.16 \times 10^3}{10^3}\right)^2}\right)^2 \cdot \sqrt{1 + \left(\frac{1.16 \times 10^3}{5 \times 10^4}\right)^2}} \\ &= \frac{\beta(5 \times 10^3)}{(2.35)(1.00)} \Rightarrow \beta = 4.7 \times 10^{-4} \end{aligned}$$

12.55

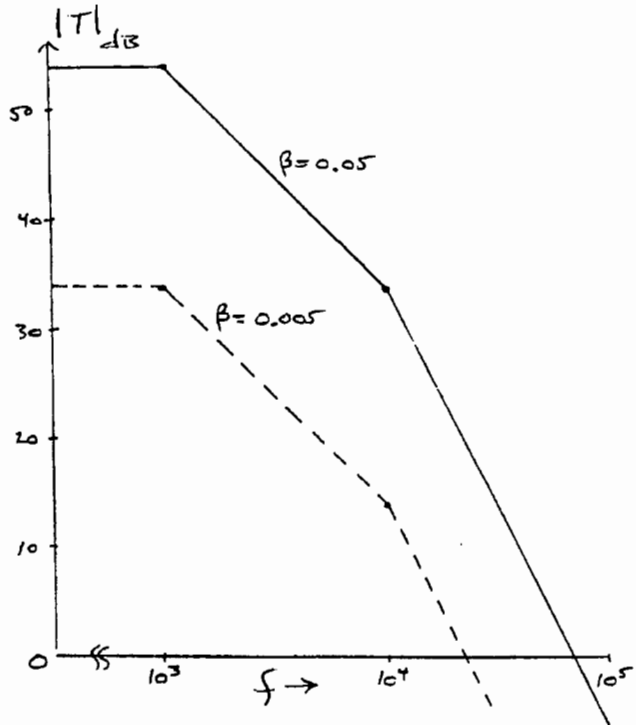

c. For  $\beta = 0.005$ ,

$$|T(f)| = 1 \text{ (0 dB) at } f \approx 2.24 \times 10^4 \text{ Hz}$$

Then

$$\begin{aligned} \phi &= -\tan^{-1}\left(\frac{2.24 \times 10^4}{10^3}\right) - \tan^{-1}\left(\frac{2.24 \times 10^4}{10^4}\right) \\ &\quad - \tan^{-1}\left(\frac{2.24 \times 10^4}{10^5}\right) \\ &= -87.44 - 65.94 - 12.63 \end{aligned}$$

or

$$\phi = -166^\circ \text{ System is stable.}$$

$$\text{Phase margin} = 14^\circ$$

For  $\beta = 0.05$ ,

$$|T(f)| = 1 \text{ (0 dB) at } f \approx 7.08 \times 10^4 \text{ Hz}$$

Then

$$\begin{aligned} \phi &= -\tan^{-1}\left(\frac{7.08 \times 10^4}{10^3}\right) - \tan^{-1}\left(\frac{7.08 \times 10^4}{10^4}\right) \\ &\quad - \tan^{-1}\left(\frac{7.08 \times 10^4}{10^5}\right) \\ &= -89.19 - 81.96 - 35.30 \end{aligned}$$

or

$$\phi = -206.45^\circ \Rightarrow \text{System is unstable.}$$

12.56

$$T = A\beta = \frac{\beta(10^5)}{\left(1 + j\frac{f}{5 \times 10^4}\right)\left(1 + j\frac{f}{10^5}\right)\left(1 + j\frac{f}{5 \times 10^5}\right)}$$

$$\text{Phase Margin} = 60^\circ \Rightarrow \phi = -120^\circ$$

So

$$-120 = -\tan^{-1}\left(\frac{f}{5 \times 10^4}\right) - \tan^{-1}\left(\frac{f}{10^5}\right) - \tan^{-1}\left(\frac{f}{5 \times 10^5}\right)$$

$$\text{By trial and error, at } f = 10^5 \text{ Hz, } \phi \cong -120^\circ$$

Then

$$\begin{aligned} |T| = 1 &= \frac{\beta(10^5)}{\sqrt{1 + \left(\frac{10^5}{5 \times 10^4}\right)^2} \cdot \sqrt{1 + \left(\frac{10^5}{10^5}\right)^2} \cdot \sqrt{1 + \left(\frac{10^5}{5 \times 10^5}\right)^2}} \\ 1 &= \frac{\beta(10^5)}{(2.236)(1.414)(1.02)} \Rightarrow \underline{\beta = 3.22 \times 10^{-5}} \end{aligned}$$

12.57

a. Phase Margin =  $60^\circ \Rightarrow \phi = -120^\circ$   
Then

$$\phi = -120^\circ = -2 \tan^{-1}\left(\frac{f}{10^3}\right)$$

$$\text{or } f = 1.732 \times 10^3 \text{ Hz}$$

Then

$$|T(f)| = 1 = \frac{\beta(10^3)}{\left[1 + \left(\frac{1.732 \times 10^3}{10^3}\right)^2\right]}$$

which yields

$$\underline{\beta = 4 \times 10^{-3}}$$

12.58

$$T(0) = A(0)\beta = (500)(0.6) = 300$$

$$T(f) = \frac{300}{\left(1 + j\frac{f}{10^4}\right)\left(1 + j\frac{f}{10^5}\right)\left(1 + j\frac{f}{10^6}\right)}$$

Find  $f$  at which  $|T| = 1$

$$1 = \frac{300}{\sqrt{1 + \left(\frac{f_1}{10^4}\right)^2} \cdot \sqrt{1 + \left(\frac{f_1}{10^5}\right)^2} \cdot \sqrt{1 + \left(\frac{f_1}{10^6}\right)^2}}$$

By trial and error,  $f_1 = 5.12 \times 10^5 \text{ Hz}$


Then

$$\phi = -\tan^{-1}\left(\frac{f_1}{10^4}\right) - \tan^{-1}\left(\frac{f_1}{10^5}\right) - \tan^{-1}\left(\frac{f_1}{10^6}\right)$$

$$= -88.88 - 78.95 - 27.1 = -194.9^\circ$$

System is unstable, Phase margin is not defined.

12.59

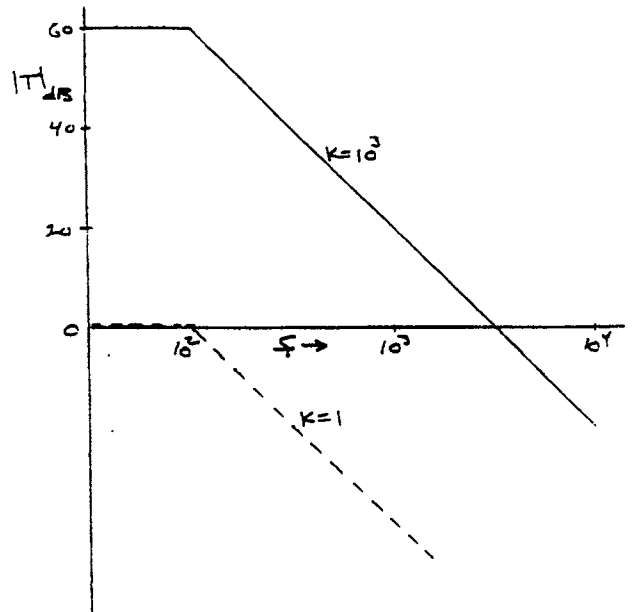

12.60

$$\text{Phase Margin} = 45^\circ \Rightarrow \phi = -135^\circ$$

$$\phi = -135^\circ$$

$$\begin{aligned} &= -\tan^{-1}\left(\frac{f}{10^3}\right) - \tan^{-1}\left(\frac{f}{10^4}\right) - \tan^{-1}\left(\frac{f}{10^5}\right) \\ &\quad - \tan^{-1}\left(\frac{f}{10^6}\right) \end{aligned}$$

$$\text{At } f = 10^4 \text{ Hz, } \phi = -135.6^\circ$$

$$\begin{aligned}
 |T| = 1 &= \\
 &= \beta(10^3) \times \frac{1}{\sqrt{1 + \left(\frac{10^4}{10^3}\right)^2}} \times \frac{1}{\sqrt{1 + \left(\frac{10^4}{10^4}\right)^2}} \times \\
 &\quad \times \frac{1}{\sqrt{1 + \left(\frac{10^4}{10^5}\right)^2}} \times \frac{1}{\sqrt{1 + \left(\frac{10^4}{10^6}\right)^2}} \\
 1 &= \frac{\beta(10^3)}{(10.05)(1.414)(1.005)(1.00)}
 \end{aligned}$$

or

$$\beta = 0.01428$$

12.61

$$\begin{aligned}
 T &= 5000 \times \frac{1}{\left(1 + j\frac{f}{f_{PD}}\right)} \times \frac{1}{\left(1 + j\frac{f}{300 \times 10^3}\right)} \\
 &\quad \times \frac{1}{\left(1 + j\frac{f}{2 \times 10^6}\right)} \times \frac{1}{\left(1 + j\frac{f}{25 \times 10^6}\right)}
 \end{aligned}$$

Phase Margin = 45° ⇒ φ = -135° at f = 300 kHz

$$\begin{aligned}
 -135^\circ &= -\tan^{-1}\left(\frac{300 \times 10^3}{f_{PD}}\right) \\
 &\quad - \tan^{-1}\left(\frac{300 \times 10^3}{300 \times 10^3}\right) - 0 - 0 \\
 &= -90^\circ - 45^\circ
 \end{aligned}$$

Now

|T| = 1 @ f = 300 kHz

$$|T| = 1 \approx \frac{5000}{\sqrt{1 + \left(\frac{300 \times 10^3}{f_{PD}}\right)^2}} \cdot \sqrt{2} \cdot 1 \cdot 1$$

$$1 + \left(\frac{300 \times 10^3}{f_{PD}}\right)^2 = \left(\frac{5000}{\sqrt{2}}\right)^2$$

$$\begin{aligned}
 f_{PD} &\approx \frac{300 \times 10^3 \sqrt{2}}{5000} \\
 &\Rightarrow \underline{f_{PD} = 84.8 \text{ Hz}}
 \end{aligned}$$

12.62

$$\text{a. } T(0) = 100 \text{ dB} \Rightarrow T(0) = 10^5$$

T(f)

$$\begin{aligned}
 &= \frac{10^5}{\left(1 + j\frac{f}{10}\right) \left(1 + j\frac{f}{5 \times 10^6}\right) \left(1 + j\frac{f}{10 \times 10^6}\right)}
 \end{aligned}$$

$$\begin{aligned}
 |T| = 1 &= \\
 &= 10^5 \times \frac{1}{\sqrt{1 + \left(\frac{f}{10}\right)^2}} \times \frac{1}{\sqrt{1 + \left(\frac{f}{5 \times 10^6}\right)^2}} \\
 &\quad \times \frac{1}{\sqrt{1 + \left(\frac{f}{10 \times 10^6}\right)^2}}
 \end{aligned}$$

By trial and error

$$\underline{f = 0.976 \text{ MHz}}$$

$$\begin{aligned}
 \phi &= -\tan^{-1}\left(\frac{0.976 \times 10^6}{10}\right) - \tan^{-1}\left(\frac{0.976}{5}\right) \\
 &\quad - \tan^{-1}\left(\frac{0.976}{10}\right) \\
 &= -90^\circ - 11.05^\circ - 5.574^\circ = -106.6^\circ
 \end{aligned}$$

$$\text{Phase Margin} = 180^\circ - 106.6^\circ = \underline{73.4^\circ}$$

$$\text{b. } f'_{P1} \propto \frac{1}{C_F} \text{ so } \frac{10}{f'_{P1}} = \frac{75}{20}$$

or

$$\underline{f'_{P1} = 2.67 \text{ Hz}}$$

Now

$$\begin{aligned}
 |T| = 1 &= \\
 &= 10^5 \times \frac{1}{\sqrt{1 + \left(\frac{f}{2.67}\right)^2}} \times \frac{1}{\sqrt{1 + \left(\frac{f}{5 \times 10^6}\right)^2}} \\
 &\quad \times \frac{1}{\sqrt{1 + \left(\frac{f}{10 \times 10^6}\right)^2}}
 \end{aligned}$$

By trial and error

$$f \approx 2.66 \times 10^5 \text{ Hz}$$

then

$$\begin{aligned}
 \phi &= -\tan^{-1}\left(\frac{2.66 \times 10^5}{2.67}\right) - \tan^{-1}\left(\frac{0.266}{5}\right) \\
 &\quad - \tan^{-1}\left(\frac{0.266}{10}\right) \\
 &= -90^\circ - 3.045^\circ - 1.524^\circ = -94.57^\circ
 \end{aligned}$$

$$\text{Phase Margin} = 180^\circ - 94.57^\circ = \underline{85.4^\circ}$$

12.63

$$(a) f_{3-dB} = \frac{1}{2\pi\tau} \text{ where } \tau = (R_{o1} \parallel R_{i2})C_i \\ = (500 \parallel 1000) \times 10^3 \times 2 \times 10^{-12} \Rightarrow \tau = 6.67 \times 10^{-7} \text{ s}$$

Then

$$f_{3-dB} = \frac{1}{2\pi(6.67 \times 10^{-7})} \Rightarrow \underline{f_{3-dB} = 239 \text{ kHz}}$$

(b) For

$$f_{PD} = 10 \text{ Hz}, \quad \tau = \frac{1}{2\pi f_{PD}} = \frac{1}{2\pi(10)} = 0.0159 \text{ s}$$

$$\text{Then } \tau = (R_{o1} \parallel R_{i2})(C_i + C_M)$$

$$0.0159 = (500 \parallel 1000) \times 10^3 \times (C_i + C_M)$$

or

$$(C_i + C_M) = 4.77 \times 10^{-8} = 2 \times 10^{-12} + C_M \Rightarrow$$

$$\underline{C_M = 477 \mu\text{F}}$$

12.64

Want  $f_i = 12 \text{ MHz}$  for a phase margin of  $45^\circ$ 

$$T_{dB}(0) = 80 \text{ dB} \Rightarrow T(0) = 10^4$$

Then

$$T(f) = \frac{T(0)}{\left(1 + j\frac{f}{f_{PD}}\right)\left(1 + j\frac{f}{12 \times 10^6}\right)}$$

$$\text{Set } f = f_i \text{ and } |T| = 1$$

So

$$|T| = 1 = \frac{10^4}{\sqrt{1 + \left(\frac{12 \times 10^6}{f_{PD}}\right)^2} \cdot \sqrt{2}}$$

which yields

$$\frac{12 \times 10^6}{f_{PD}} = \frac{10^4}{\sqrt{2}} \Rightarrow \underline{f_{PD} = 1.70 \text{ kHz}}$$

12.65

$$A_0 = 80 \text{ dB} \Rightarrow A_0 = 10^4$$

$$A_f(0) = \frac{A_0}{1 + \beta A_0}$$

$$\text{or } 5 = \frac{10^4}{1 + \beta(10^4)} \Rightarrow \beta \approx 0.2$$

$$\text{Then } T(0) = \beta A_0 = 0.2 \times 10^4$$

Inserting a dominate pole

$$\phi = -\tan^{-1}\left(\frac{f}{f_{PD}}\right) - \tan^{-1}\left(\frac{f}{10^6}\right) - \tan^{-1}\left(\frac{f}{10^7}\right)$$

If we want a phase margin of  $45^\circ$ , then

$$-135^\circ \approx -90^\circ - \tan^{-1}\left(\frac{f}{10^6}\right) - \tan^{-1}\left(\frac{f}{10^7}\right)$$

By trial and error,  $f \approx 0.845 \text{ MHz}$ 

Then

$$|T| = 1 = \frac{0.2 \times 10^4}{\sqrt{1 + \left(\frac{0.845 \times 10^6}{f_{PD}}\right)^2} \sqrt{1 + \left(\frac{0.845}{1}\right)^2}} \\ \times \frac{1}{\sqrt{1 + \left(\frac{0.845}{10}\right)^2}}$$

$$\frac{0.845 \times 10^6}{f_{PD}} \approx \frac{0.2 \times 10^4}{(1.309)(1.0036)}$$

$$\text{so } \underline{f_{PD} = 555 \text{ Hz}}$$

12.66

Assuming a phase margin of  $45^\circ$ ,

$$-135^\circ \approx -90^\circ - \tan^{-1}\left(\frac{f}{2 \times 10^6}\right) \\ - \tan^{-1}\left(\frac{f}{25 \times 10^6}\right)$$

By trial and error,  $f \approx 1.74 \text{ MHz}$ 

Then

$$|T| = 1 \\ = 5000 \times \frac{1}{\sqrt{1 + \left(\frac{1.74 \times 10^6}{f_{PD}}\right)^2}} \\ \times \frac{1}{\sqrt{1 + \left(\frac{1.74}{2}\right)^2}} \times \frac{1}{\sqrt{1 + \left(\frac{1.74}{25}\right)^2}}$$

or

$$\frac{1.74 \times 10^6}{f_{PD}} \approx \frac{5000}{(1.325)(1.0024)}$$

$$\text{so } \underline{f_{PD} = 462 \text{ Hz}}$$



## Chapter 13

## Exercise Solutions

E13.3

$$V_{iN}(\max) = V^+ - V_{BE}(\text{on}) = 15 - 0.6 = 14.4 \text{ V}$$

$$\begin{aligned} V_{iN}(\min) &\approx 4V_{BE}(\text{on}) + V^+ \\ &= 4(0.6) - 15 = -12.6 \text{ V} \\ &\underline{-12.6 \leq V_{iN}(\text{cm}) \leq 14.4 \text{ V}} \end{aligned}$$

E13.4

$$\text{a. } V_0(\max) \approx V^+ - 2V_{BE}(\text{on}) = 15 - 2(0.6)$$

$$V_0(\max) = 13.8 \text{ V}$$

$$V_0(\min) = 3V_{BE}(\text{on}) + V^- = 3(0.6) - 15$$

$$V_0(\min) \approx -13.2 \text{ V}$$

$$\underline{-13.2 \leq V_0 \leq 13.8 \text{ V}}$$

$$\text{b. } V_0(\max) = 5 - 1.2 = 3.8 \text{ V}$$

$$V_0(\min) \approx 3V_{BE} + V^- = 3(0.6) - 5 = -3.2 \text{ V}$$

$$\underline{-3.2 \leq V_0 \leq 3.8 \text{ V}}$$

E13.5

$$I_{C1} = I_{C2} \approx 9.5 \mu\text{A}$$

$$I_{B1} = I_{B2} = \frac{9.5 \mu\text{A}}{200} = 0.0475 \mu\text{A}$$

$$\Rightarrow \underline{I_{B1} = I_{B2} = 47.5 \text{ nA}}$$

E13.6

$$I_{REF} \approx \frac{15 - 2(0.6) - (-15)}{40} = 0.72 \text{ mA}$$

$$\begin{aligned} V_{BE} &= V_T \ln \left( \frac{I_{REF}}{I_S} \right) = (0.026) \ln \left( \frac{0.72 \times 10^{-3}}{10^{-14}} \right) \\ &= 0.650 \text{ V} \end{aligned}$$

So

$$I_{REF} = \frac{30 - 2(0.65)}{40} \Rightarrow \underline{I_{REF} = 0.718 \text{ mA}}$$

$$\underline{V_{BE11} = 0.650 \text{ V}}$$

$$I_{C10}R_4 = V_T \ln \left( \frac{I_{REF}}{I_{C10}} \right)$$

$$I_{C10}(5) = (0.026) \ln \left( \frac{0.718}{I_{C10}} \right)$$

By trial and error:  $I_{C10} = 18.9 \mu\text{A}$ 


$$V_{BE10} = V_{BE11} - I_{C10}R_4 = 0.650 - (0.0189)(5)$$

$$\Rightarrow \underline{V_{BE10} \approx 0.556 \text{ V}}$$

$$I_{C6} \approx \frac{I_{C10}}{2} = \frac{18.9}{2} = 9.45 \mu\text{A}$$

$$\begin{aligned} V_{BE6} &= V_T \ln \left( \frac{I_{C6}}{I_S} \right) = (0.026) \ln \left( \frac{9.45 \times 10^{-6}}{10^{-14}} \right) \\ &\Rightarrow \underline{V_{BE6} = 0.537 \text{ V}} \end{aligned}$$

E13.7

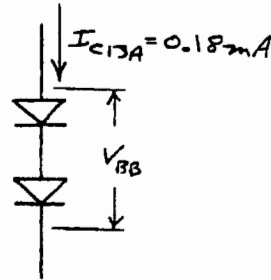

$$0.18 \times 10^{-3} = 10^{-14} \exp \left( \frac{V_D}{V_T} \right)$$

$$V_D = V_T \ln \left( \frac{0.18 \times 10^{-3}}{10^{-14}} \right)$$

$$= (0.026) \ln \left( \frac{0.18 \times 10^{-3}}{10^{-14}} \right)$$

$$V_D = 0.6140$$

$$\underline{V_{BB} = 2V_{DD} \approx 1.228 \text{ V}}$$

$$I_{C14} = I_{C20} = I_S \exp \left( \frac{V_{BB}/2}{V_T} \right)$$

$$= 3 \times 10^{-14} \exp \left( \frac{0.6140}{0.026} \right)$$

$$\underline{I_{C14} = I_{C20} = 0.541 \text{ mA}}$$

E13.8

$$I_{REF} = \frac{10 - 0.6 - 0.6 - (-10)}{40}$$

$$\Rightarrow \underline{I_{REF} = 0.47 \text{ mA}}$$

$$I_{C10}R_4 = V_T \ln \left( \frac{I_{REF}}{I_{C10}} \right)$$

$$I_{C10}(5) = (0.026) \ln \left( \frac{0.47}{I_{C10}} \right)$$

By trial and error:


$$\Rightarrow \underline{I_{C10} \approx 17.2 \mu\text{A}}$$

$$I_{C6} \approx \frac{I_{C10}}{2} \Rightarrow \underline{I_{C6} = 8.6 \mu\text{A}}$$

$$I_{C13B} = (0.75)I_{REF} \Rightarrow \underline{I_{C13B} = 0.353 \text{ mA}}$$

$$I_{C13A} = (0.25)I_{REF} \Rightarrow \underline{I_{C13A} = 0.118 \text{ mA}}$$

E13.9

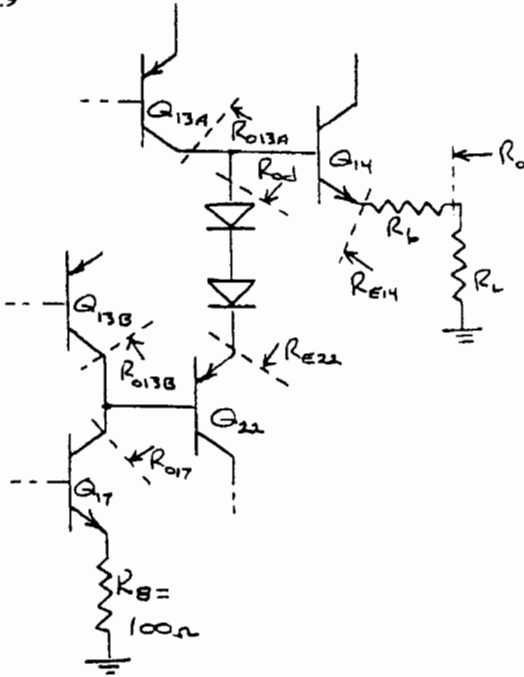

$$R_0 = R_6 + R_{E14}$$

$$R_{E14} = \frac{r_{\pi 14} + R_{0d} \parallel R_{013A}}{1 + \beta_n}$$

The diode resistance can be found as

$$I_D = I_S \exp\left(\frac{V_D}{V_T}\right)$$

$$\frac{1}{r_d} = \frac{\partial I_D}{\partial V_D} = I_S \left(\frac{1}{V_T}\right) \cdot \exp\left(\frac{V_D}{V_T}\right) = \frac{I_D}{V_T}$$

or

$$r_d = \frac{V_T}{I_D} = \frac{V_T}{I_{C13A}} = \frac{0.026}{0.18} \Rightarrow 144 \Omega$$

$$R_{E22} = \frac{r_{\pi 22} + R_{017} \parallel R_{013B}}{1 + \beta_P}$$

$$R_{013B} = r_{013B} = 92.6 \text{ k}\Omega$$

$$R_{017} = r_{017} [1 + g_{m17} (R_8 \parallel r_{\pi 17})] = 283 \text{ k}\Omega$$

From previous calculations

$$R_{E22} = 1.51 \text{ k}\Omega$$

$$R_{0d} = 2r_d + R_{E22} = 2(0.144) + 1.51 = 1.80 \text{ k}\Omega$$

$$R_{013A} = r_{013A} = 278 \text{ k}\Omega$$

$$r_{\pi 14} = \frac{\beta_n V_T}{I_{C14}} = \frac{(200)(0.026)}{5} = 1.04 \text{ k}\Omega$$

$$R_{E14} = \frac{1.04 + 1.8 \parallel 278}{201} \Rightarrow 14.1 \Omega$$

$$R_0 = R_6 + R_{E14} = 27 + 14.1$$

$$\Rightarrow \underline{R_0 \approx 41 \Omega}$$

E13.10

For  $Q_6$  we have  $V_{SG5} = V_{SG6} = 1.06 \text{ V}$

So

$$V_{SD6}(\text{sat}) = 1.06 - 0.5 = 0.56 \text{ V}$$

For  $M_1$  and  $M_2$

$$I_D = \frac{I_Q}{2} = K_p (V_{SG1} + V_{TP})^2$$

$$\frac{0.0397}{2} = 0.125 (V_{SG1} - 0.5)^2$$

$$\Rightarrow V_{SG1} = 0.898 \text{ V}$$

So maximum input voltage

$$= V^+ - V_{SD6}(\text{sat}) - V_{SG1}$$

$$= 5 - 0.56 - 0.898$$

$$\Rightarrow \underline{V_{iN}(\text{max}) = 3.54 \text{ V}}$$

For  $M_3$ ,

$$K_p = (6.25)(20) = 125 \mu\text{A}/\text{V}^2$$

$$I_{D3} = \frac{I_Q}{2} = \frac{39.7}{2} \mu\text{A}$$

$$\frac{39.7}{2} = 125 (V_{GS3} - V_{TN})^2$$

$$V_{TN} = 0.5 \text{ V} \Rightarrow$$

$$V_{GS3} = 0.898 \text{ V}$$

$$V_{SD1}(\text{sat}) = 0.898 - 0.5 = 0.398 \text{ V}$$

$$V_{iN}(\text{min}) = V^- + V_{GS3} + V_{SD1}(\text{sat}) - V_{SG1}$$

$$= -5 + 0.898 + 0.398 - 0.898$$

$$\underline{V_{iN}(\text{min}) = -4.60 \text{ V}}$$

$$\underline{-4.60 \leq V_{iN}(\text{cm}) \leq 3.54 \text{ V}}$$

E13.11

$$V_0(\text{max}) = V^+ - V_{SD8}(\text{sat})$$

$$V_{SG8} = V_{SG5} = 1.06 \text{ V}$$

$$V_{SD8}(\text{sat}) = 1.06 - 0.5 = 0.56 \text{ V}$$

$$V_0(\text{max}) = 5 - 0.56 = 4.44 \text{ V}$$

$$V_0(\text{min}) = V^- + V_{D57}(\text{sat})$$

$$V_{GS7} = 1.06 \Rightarrow V_{D57}(\text{sat}) = 1.06 - 0.5 = 0.56$$

$$V_0(\text{min}) = -5 + 0.56 = -4.44$$

$$\underline{-4.44 \leq V_0 \leq 4.44 \text{ V}}$$

E13.12

(a) For  $M_5$ ,  $K_{p5} = 125 \mu\text{A}/\text{V}^2$

$$K_{p5}(V_{SG5} + V_{TP})^2 = \frac{V^+ - V^- - V_{SG5}}{R_{m1}}$$

$$0.125(V_{SG5} - 0.5)^2 = \frac{5 + 5 - V_{SG5}}{100}$$

$$12.5(V_{SG5}^2 - V_{SG5} + 0.25) = 10 - V_{SG5}$$

$$12.5V_{SG5}^2 - 11.5V_{SG5} - 6.875 = 0$$

$$V_{SG5} = \frac{11.5 \pm \sqrt{(11.5)^2 + 4(12.5)(6.875)}}{2(12.5)}$$

$$V_{SG5} = 1.33 \text{ V}$$

Then

$$I_{REF} = I_Q = I_{D8} = I_{D7} = \frac{10 - 1.33}{100} \Rightarrow 86.7 \mu\text{A}$$

$$I_{D1} = I_{D2} = I_{D3} = I_{D4} = \frac{I_Q}{2} = 43.35 \mu\text{A}$$

(b)  $K_{p1} = K_{p2} = 125 \mu\text{A}/\text{V}^2$

$$r_{o2} = r_{o4} = \frac{1}{\lambda I_D} = \frac{1}{(0.02)(0.04335)} = 1153 \text{ k}\Omega$$

Input stage gain

$$A_d = \sqrt{2K_{p1}I_Q} \cdot (r_{o2} \parallel r_{o4})$$

$$= \sqrt{2(0.125)(0.0867)} \cdot (1153 \parallel 1153) \Rightarrow$$

$$A_d = 84.9$$

Transconductance of  $M_7$

$$g_{m7} = 2\sqrt{K_{p7}I_{D7}} = 2\sqrt{(0.250)(0.0867)}$$

$$= 0.294 \text{ mA/V}$$

$$r_{o7} = r_{o8} = \frac{1}{\lambda I_{D7}} = \frac{1}{(0.02)(0.0867)} = 577 \text{ k}\Omega$$

Second stage gain

$$A_{v2} = g_{m7}(r_{o7} \parallel r_{o8}) = (0.294)(577 \parallel 577) \Rightarrow$$

$$A_{v2} = 84.8$$

$$\text{Overall gain} = A_d \cdot A_{v2} = (84.9)(84.8) \Rightarrow$$

$$A = 7,200$$

E13.13

$$I_{D1} = I_{D2} = 25 \mu\text{A}$$

$$g_{m1} = g_{m2} = 2\sqrt{\left(\frac{k'_p}{2}\right)\left(\frac{W}{L}\right)I_{DQ}} = 2\sqrt{\left(\frac{40}{2}\right)(25)(25)} \Rightarrow$$

$$g_{m1} = g_{m2} = 224 \mu\text{A/V}$$

$$g_{m6} = 2\sqrt{\left(\frac{k'_n}{2}\right)\left(\frac{W}{L}\right)I_{DQ}} = 2\sqrt{\left(\frac{80}{2}\right)(25)(25)} \Rightarrow$$

$$g_{m6} = 316 \mu\text{A/V}$$

$$r_{o1} = r_{o6} = r_{o8} = r_{o10} = \frac{1}{\lambda I_D} = \frac{1}{(0.02)(25)} = 2 \text{ M}\Omega$$

$$r_{o4} = \frac{1}{\lambda I_{D4}} = \frac{1}{(0.02)(50)} = 1 \text{ M}\Omega$$

$$R_{o8} = g_{m2}(r_{o8}r_{o10}) = (224)(2)(2) = 896 \text{ M}\Omega$$

$$R_{o6} = g_{m6}(r_{o6})(r_{o4} \parallel r_{o1}) = 316(2)(1 \parallel 2) = 421 \text{ M}\Omega$$

Then

$$A_d = g_{m1}(R_{o6} \parallel R_{o8}) = 224(421 \parallel 896) \Rightarrow$$

$$A_d = 64,158$$

E13.14

(a)  $A_d = Bg_{m1}(r_{o6} \parallel r_{o8})$

$$g_{m1} = 2\sqrt{\left(\frac{k'_n}{2}\right)\left(\frac{W}{L}\right)I_{D1}} = 2\sqrt{\left(\frac{80}{2}\right)(20)(50)}$$

$$g_{m1} = 400 \mu\text{A/V}$$

$$r_{o6} = \frac{1}{\lambda_p I_{D6}} = \frac{1}{(0.02)(150)} = 0.333 \text{ M}\Omega$$

$$r_{o8} = \frac{1}{\lambda_n I_{D8}} = \frac{1}{(0.02)(150)} = 0.333 \text{ M}\Omega$$

$$A_d = 3(400)(0.333 \parallel 0.333) \Rightarrow A_d = 200$$

(b)  $f_{PD} = \frac{1}{2\pi R_o(C_L + C_P)}$

where  $R_o = r_{o6} \parallel r_{o8} = 0.333 \parallel 0.333 \text{ M}\Omega$

$$f_{PD} = \frac{1}{2\pi(0.333 \parallel 0.333) \times 10^6 \times 2 \times 10^{-12}} \Rightarrow$$

$$f_{PD} = 477 \text{ kHz}$$

$$f_{PD} \cdot A_d = (477 \times 10^3)(200) \Rightarrow 95.4 \text{ MHz}$$

E13.15

(a) From Exercise 13.14,  $g_{m1} = 400 \mu\text{A/V}$

$$r_{o6} = r_{o8} = r_{o10} = r_{o12} = 0.333 \text{ M}\Omega$$

$$g_{m10} = 2\sqrt{\left(\frac{k'_p}{2}\right)\left(\frac{W}{L}\right)I_{D10}} = 2\sqrt{\left(\frac{40}{2}\right)(20)(150)} \Rightarrow$$

$$g_{m10} = 490 \mu\text{A/V}$$

$$g_{m12} = 2\sqrt{\left(\frac{k'_n}{2}\right)\left(\frac{W}{L}\right)I_{D12}} = 2\sqrt{\left(\frac{80}{2}\right)(20)(150)} \Rightarrow$$

$$g_{m12} = 693 \mu\text{A/V}$$

$$R_{o10} = g_{m10}(r_{o10}r_{o6}) = (490)(0.333)(0.333) = 54.3 \text{ M}\Omega$$

$$R_{o12} = g_{m12}(r_{o12}r_{o8}) = (693)(0.333)(0.333) = 76.8 \text{ M}\Omega$$

$$A_d = Bg_{m1}(R_{o10} \parallel R_{o12}) = 3(400)(54.3 \parallel 76.8) \Rightarrow$$

$$A_d = 38,172$$

(b)  $R_o = R_{o10} \parallel R_{o12} = 54.3 \parallel 76.8 = 31.8 \text{ M}\Omega$

$$f_{PD} = \frac{1}{2\pi(31.8 \times 10^6)(2 \times 10^{-12})} = 2.50 \text{ kHz}$$

$$f_{PD} \cdot A_d = (2.5 \times 10^3)(38,172) \Rightarrow 95.4 \text{ MHz}$$

E13.16

(a)  $A_d = g_{m1}(R_{o6} \parallel R_{o8})$

From Example 13.10,

$g_{m1} = 316 \mu A/V, R_{o6} = 316 M\Omega$

Now

$R_{o6} = g_{m6}(r_{o6})(r_{o4} \parallel r_{o1})$

$r_{o1} = 1 M\Omega, r_{o4} = 0.5 M\Omega$

$g_{m6} = \frac{I_{C6}}{V_T} = \frac{50}{0.026} \Rightarrow 1923 mA/V$

$r_{o6} = \frac{V_{A6}}{I_{C6}} = \frac{80}{50} = 1.6 M\Omega$

Then

$R_{o6} = (1923)(1600)(0.5 \parallel 1) = 1026 M\Omega$

$A_d = (316)(1026 \parallel 316) \Rightarrow A_d = 76,343$

(b)  $f_{PD} = \frac{1}{2\pi(316 \parallel 1026) \times 10^6 \times 2 \times 10^{-12}} \Rightarrow$

$f_{PD} = 329 Hz$

$f_{PD} \cdot A_d = (329)(76,343) \Rightarrow 25.1 MHz$

E13.17

$V^+ - V^- = V_{EB1} + V_{EB6} + V_{EB7} + I_1 R_1$   
 $= 0.6 + 0.6 + 0.6 + (0.24)(8) = 3.72 V$

So

$V^+ = -V^- = 1.86 V$

E13.18

For  $Q_7$  and  $R_1$

$V_{SG} = V_{BE7} + I_1 R_1 = 0.6 + I_1(5)$

For  $M_8$ :

$I_2 = K_p(V_{SG} + V_{TP})^2$


$I_2 = 0.3(V_{SG} - 1.4)^2$

By trial and error:

$V_{SG} = 2.54 V$

$I_1 = I_2 = 0.388 mA$

E13.19

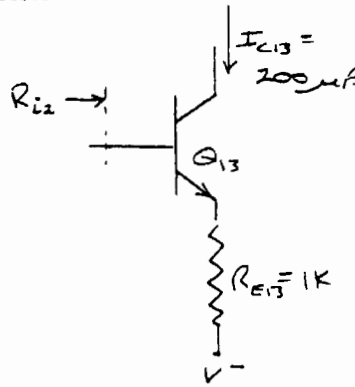

$r_{\pi 13} = \frac{\beta V_T}{I_{C13}} = \frac{(200)(0.026)}{0.20}$   
 $= 26 k\Omega$

$R_{i2} = r_{\pi 13} + (1 + \beta)R_{E13} = 26 + 201(1)$   
 $= 227 k\Omega$

$r_{o10} = \frac{1}{\lambda I_{D10}} = \frac{1}{(0.02)(0.1)} = 500 k\Omega$

$r_{o12} = \frac{V_A}{I_{C12}} = \frac{50}{0.1} = 500 k\Omega$

$g_{m12} = \frac{I_{C12}}{V_T} = \frac{0.1}{0.026} = 3.85 mA/V$

$r_{\pi 12} = \frac{\beta V_T}{I_{C12}} = \frac{(200)(0.026)}{0.1} = 52 k\Omega$

$R_{act1} = r_{o12}[1 + g_{m12}(r_{\pi 12} \parallel R_5)]$   
 $= 500[1 + (3.85)(52 \parallel 0.5)] = 1453 k\Omega$

$A_d = \sqrt{2K_n I_{Q5}} \cdot (r_{o10} \parallel R_{act1} \parallel R_{12})$   
 $= \sqrt{2(0.6)(0.2)} \cdot (500 \parallel 1453 \parallel 227)$   
 $= (0.490)(141) \Rightarrow A_d = 69.1$

E13.20

For  $J_6$  biased in the saturation region

$\Rightarrow I_{C3} = I_{DSS} = 300 \mu A$

$Q_1, Q_2, Q_3$  are matched

$\Rightarrow I_{C1} = I_{C2} = I_{C3} = 300 \mu A$

## Chapter 13

## Problem Solutions

13.3

$$(a) A_d = g_{m1}(r_{o2} \| r_{o4} \| R_{16})$$

$$g_{m1} = \frac{I_{C1}}{V_T} = \frac{20}{0.026} \Rightarrow 0.769 \text{ mA/V}$$

$$r_{o2} = \frac{V_{A2}}{I_{C2}} = \frac{80}{20} = 4 \text{ M}\Omega$$

$$r_{o4} = \frac{V_{A4}}{I_{C2}} = \frac{80}{20} = 4 \text{ M}\Omega$$

$$R_{16} = r_{\pi 6} + (1 + \beta_n)(R_1 \| r_{\pi 7})$$

$$r_{\pi 7} = \frac{(120)(0.026)}{0.2} = 15.6 \text{ k}\Omega$$

$$I_{C6} \cong \frac{V_{BE(\text{on})}}{R_1} = \frac{0.6}{20} = 0.030 \text{ mA}$$

$$r_{\pi 6} = \frac{(120)(0.026)}{0.030} = 104 \text{ k}\Omega$$

Then

$$R_{16} = 104 + (121)[20 \| 15.6] \Rightarrow 1.16 \text{ M}\Omega$$

Then

$$A_d = 769(4 \| 4 \| 1.16) \Rightarrow \underline{A_d = 565}$$

Now

$$V_o = -I_{c7}r_{o7} = -(\beta_n I_{b7})r_{o7} = -\beta_n r_{o7} \left( \frac{R_1}{R_1 + r_{\pi 7}} \right) I_{c6}$$

$$= -\beta_n (1 + \beta_n) r_{o7} \left( \frac{R_1}{R_1 + r_{\pi 7}} \right) I_{b6} \text{ and } I_{b6} = \frac{V_{o1}}{R_{16}}$$

Then

$$A_{v2} = \frac{V_o}{V_{o1}} = \frac{-\beta_n (1 + \beta_n) r_{o7} \left( \frac{R_1}{R_1 + r_{\pi 7}} \right)}{R_{16}}$$

$$r_{o7} = \frac{V_A}{I_{C7}} = \frac{80}{0.2} = 400 \text{ k}\Omega$$

So

$$A_{v2} = \frac{-(120)(121)(400) \left( \frac{20}{20 + 15.6} \right)}{1160} \Rightarrow$$

$$\underline{A_{v2} = -2813}$$

$$\text{Overall gain} = A_d \cdot A_{v2} = (565)(-2813) \Rightarrow$$

$$\underline{A = -1.59 \times 10^6}$$

$$(b) R_{id} = 2r_{\pi 1} \text{ and } r_{\pi 1} = \frac{(80)(0.026)}{0.020} = 104 \text{ k}\Omega$$

$$\underline{R_{id} = 208 \text{ k}\Omega}$$

$$(c) f_{PD} = \frac{1}{2\pi R_{eq} C_M} \text{ and}$$

$$C_M = (10)(1 + 2813) = 28,140 \text{ pF}$$

$$R_{eq} = r_{o2} \| r_{o4} \| R_{16} = 4 \| 4 \| 1.16 = 0.734 \text{ M}\Omega$$

$$f_{PD} = \frac{1}{2\pi(0.734 \times 10^6)(28,140 \times 10^{-12})} = 7.71 \text{ Hz}$$

$$\text{Gain-Bandwidth Product} = (7.71)(1.59 \times 10^6) \Rightarrow \underline{12.3 \text{ MHz}}$$

13.4

- $Q_3$  acts as the protection device.
- Same as part (a).

13.5

If we assume  $V_{BE(\text{on})} = 0.7 \text{ V}$ , then

$$V_{in} = 0.7 + 0.7 + 50 + 5$$

So breakdown voltage  $\approx \underline{56.4 \text{ V}}$ .

13.6

$$(a) I_{REF} = \frac{15 - 0.6 - 0.6 - (-15)}{R_5} = 0.50$$

$$\Rightarrow R_5 = 57.6 \text{ k}\Omega$$

$$I_{C10} R_4 = V_T \ln \left( \frac{I_{REF}}{I_{C10}} \right)$$

$$R_4 = \frac{0.026}{0.030} \ln \left( \frac{0.50}{0.030} \right) \Rightarrow \underline{R_4 = 2.44 \text{ k}\Omega}$$

$$(b) I_{REF} = \frac{5 - 0.6 - 0.6 - (-5)}{57.6} \Rightarrow \underline{I_{REF} = 0.153 \text{ mA}}$$

$$I_{C10}(2.44) = (0.026) \ln \left( \frac{0.153}{I_{C10}} \right)$$

By trial and error,  $\underline{I_{C10} \cong 21.1 \mu\text{A}}$ 

13.7

$$(a) I_{REF} \cong 0.50 \text{ mA}$$

$$V_{BE} = V_T \ln \left( \frac{I_{REF}}{I_S} \right) = (0.026) \ln \left( \frac{0.50 \times 10^{-3}}{10^{-14}} \right) \Rightarrow$$

$$\underline{V_{BE11} = 0.641 \text{ V} = V_{BE12}}$$

Then

$$R_5 = \frac{15 - 0.641 - 0.641 - (-15)}{0.50} \Rightarrow \underline{R_5 = 57.4 \text{ k}\Omega}$$

$$R_4 = \frac{0.026}{0.030} \ln \left( \frac{0.50}{0.030} \right) \Rightarrow \underline{R_4 = 2.44 \text{ k}\Omega}$$

$$V_{BE10} = 0.026 \ln \left( \frac{0.030 \times 10^{-3}}{10^{-14}} \right) \Rightarrow \underline{V_{BE10} = 0.567 \text{ V}}$$

(b) From Problem 13.6,  $I_{REF} \cong 0.15 \text{ mA}$ 

$$V_{BE11} = V_{BE12} = 0.026 \ln \left( \frac{0.15 \times 10^{-3}}{10^{-14}} \right) = 0.609 \text{ V}$$

$$\text{Then } I_{REF} = \frac{5 - 0.609 - 0.609 - (-5)}{57.4} \Rightarrow$$

$$I_{REF} = 0.153 \text{ mA}$$

Then  $I_{C10} \cong 21.1 \mu\text{A}$  from Problem 13.6

13.8

$$\text{a. } I_{REF} = \frac{5 - 0.6 - 0.6 - (-5)}{40}$$

$$\Rightarrow I_{REF} = 0.22 \text{ mA}$$

$$I_{C10} R_4 = V_T \ln \left( \frac{I_{REF}}{I_{C10}} \right)$$

$$I_{C10}(5) = (0.026) \ln \left( \frac{0.22}{I_{C10}} \right)$$

By trial and error;

$$I_{C10} \cong 14.2 \mu\text{A}$$

$$I_{C6} \cong \frac{I_{C10}}{2} \Rightarrow I_{C6} = 7.10 \mu\text{A}$$

$$I_{C17} = 0.75 I_{REF} \Rightarrow I_{C17} = 0.165 \text{ mA}$$

$$I_{C13A} = 0.25 I_{REF} \Rightarrow I_{C13A} = 0.055 \text{ mA}$$

b. Using Example 13.4

$$r_{\pi 17} = 31.5 \text{ k}\Omega$$

$$R'_E = 50 \parallel [31.5 + (201)(0.1)] = 50 \parallel 51.6 \\ = 25.4 \text{ k}\Omega$$

$$r_{\pi 16} = \frac{\beta_n V_T}{I_{C16}} \text{ and}$$

$$I_{C16} = \frac{0.165}{200} + \frac{(0.165)(0.1) + 0.6}{50} = 0.0132 \text{ mA}$$

$$r_{\pi 16} = 394 \text{ k}\Omega$$

Then

$$R_{i2} = 394 + (201)(25.4) \Rightarrow 5.5 \text{ M}\Omega$$

$$r_{\pi 6} = 732 \text{ k}\Omega$$

$$g_{m6} = \frac{0.00710}{0.026} = 0.273 \text{ mA/V}$$

$$r_{o6} = \frac{50}{0.0071} = 7.04 \text{ M}\Omega$$

Then

$$R_{act1} = 7.04 [1 + (0.273)(1 \parallel 732)] = 8.96 \text{ M}\Omega$$

$$r_{o4} = \frac{50}{0.0071} = 7.04 \text{ M}\Omega$$

Then

$$A_d = - \left( \frac{7.1}{0.026} \right) (7.04 \parallel 8.96 \parallel 5.5)$$

or

$$A_d = -627 \text{ Gain of differential amp stage}$$

Using Example 13.5, and neglecting the input resistance to the output stage:

$$R_{act2} = \frac{V_A}{I_{C13B}} = \frac{50}{0.165} = 303 \text{ k}\Omega$$

$$A_{v2} = \frac{-(200)(201)(50)(303)}{(5500)[50 + 31.5 + (201)(0.1)]}$$

or

$$A_{v2} = -1090 \text{ Gain of second stage}$$

13.9

$$I_{C10} = 19 \mu\text{A}$$

From Equation (13.6)

$$I_{C10} = 2I \left[ \frac{\beta_P^2 + 2\beta_P + 2}{\beta_P^2 + 3\beta_P + 2} \right] = 2I \left[ \frac{(10)^2 + 2(10) + 2}{(10)^2 + 3(10) + 2} \right] \\ = 2I \left[ \frac{122}{132} \right]$$

So

$$2I = (19) \left( \frac{132}{122} \right) = 20.56 \mu\text{A}$$

$$I_{C2} = I = 10.28 \mu\text{A}$$

$$I_{C9} = \frac{2I}{\left(1 + \frac{2}{\beta_P}\right)} = \frac{20.56}{\left(1 + \frac{2}{10}\right)} \Rightarrow I_{C9} = 17.13 \mu\text{A}$$

$$I_{B9} = \frac{I_{C9}}{\beta_P} = \frac{17.13}{10} \Rightarrow I_{B9} = 1.713 \mu\text{A}$$

$$I_{B4} = \frac{I}{(1 + \beta_P)} = \frac{10.28}{11} \Rightarrow I_{B4} = 0.9345 \mu\text{A}$$

$$I_{C4} = I \left( \frac{\beta_P}{1 + \beta_P} \right) = (10.28) \left( \frac{10}{11} \right) \\ \Rightarrow I_{C4} = 9.345 \mu\text{A}$$

13.10

$$V_{B5} - V^- = V_{BE(on)} + I_{C5}(1)$$

$$= 0.6 + (0.0095)(1) = 0.6095$$

$$I_{C7} = \frac{0.6095}{50} \Rightarrow I_{C7} = 12.2 \mu\text{A}$$

$$I_{C8} = I_{C9} = 19 \mu\text{A}$$

$$I_{REF} = 0.72 \text{ mA}$$

$$I_{E13} = I_{REF} = 0.72 \text{ mA}$$

$$I_{C14} = 138 \mu\text{A}$$

$$\begin{aligned} \text{Power} &= (V^+ - V^-)(I_{C7} + I_{C8} + I_{C9} \\ &\quad + I_{REF} + I_{E13} + I_{C14}) \\ &= 30[0.0122 + 0.019 + 0.019 \\ &\quad + 0.72 + 0.72 + 0.138] \\ &\Rightarrow \text{Power} = \underline{48.8 \text{ mW}} \end{aligned}$$

$$\begin{aligned} \text{Current supplied by } V^+ \text{ and } V^- \\ &= I_{C7} + I_{C8} + I_{C9} + I_{REF} + I_{E13} + I_{C14} \\ &= \underline{1.63 \text{ mA}} \end{aligned}$$

13.11

$$\begin{aligned} \text{(a) } v_{cm}(\text{min}) &= -15 + 0.6 + 0.6 + 0.6 + 0.6 = -12.6 \text{ V} \\ v_{cm}(\text{max}) &= +15 - 0.6 = 14.4 \text{ V} \\ \text{So } -12.6 \leq v_{cm} &\leq 14.4 \text{ V} \end{aligned}$$

$$\begin{aligned} \text{(b) } v_{cm}(\text{min}) &= -5 + 4(0.6) = -2.6 \text{ V} \\ v_{cm}(\text{max}) &= 5 - 0.6 = 4.4 \text{ V} \\ \text{So } -2.6 \leq v_{cm} &\leq 4.4 \text{ V} \end{aligned}$$

13.12

If  $v_0 = V^- = -15 \text{ V}$ , the base voltage of  $Q_{14}$  is pulled low, and  $Q_{18}$  and  $Q_{19}$  are effectively cut off. As a first approximation

$$\begin{aligned} I_{C14} &= \frac{0.6}{0.027} = 22.2 \text{ mA} \\ I_{B14} &= \frac{22.2}{200} = 0.111 \text{ mA} \end{aligned}$$

Then

$$I_{C15} = I_{C13A} - I_{B14} = 0.18 - 0.111 = 0.069 \text{ mA}$$

Now

$$\begin{aligned} V_{BE15} &= V_T \ln \left( \frac{I_{C15}}{I_S} \right) \\ &= (0.026) \ln \left( \frac{0.069 \times 10^{-3}}{10^{-14}} \right) \\ &= 0.589 \text{ V} \end{aligned}$$

As a second approximation

$$\begin{aligned} I_{C14} &= \frac{0.589}{0.027} \Rightarrow \underline{I_{C14} = 21.8 \text{ mA}} \\ I_{B14} &= \frac{21.8}{200} = 0.109 \text{ mA} \end{aligned}$$

and

$$I_{C15} = 0.18 - 0.109 \Rightarrow \underline{I_{C15} = 0.071 \text{ mA}}$$

13.13

a. Neglecting base currents:

$$I_D = I_{BIAS}$$

Then

$$\begin{aligned} V_{BB} &= 2V_D = 2V_T \ln \left( \frac{I_D}{I_S} \right) \\ &= 2(0.026) \ln \left( \frac{0.25 \times 10^{-3}}{2 \times 10^{-14}} \right) \end{aligned}$$

or

$$\begin{aligned} \underline{V_{BB} = 1.2089 \text{ V}} \\ I_{CN} = I_{CP} &= I_S \exp \left( \frac{V_{BB}/2}{V_T} \right) \\ &= 5 \times 10^{-14} \exp \left( \frac{1.2089}{2(0.026)} \right) \end{aligned}$$

So

$$\underline{I_{CN} = I_{CP} = 0.625 \text{ mA}}$$

b. For  $v_I = 5 \text{ V}$ ,  $v_0 \approx 5 \text{ V}$

$$\underline{i_L \approx \frac{5}{4} = 1.25 \text{ mA}}$$

As a first approximation

$$I_{CN} \approx i_L = 1.25 \text{ mA}$$

$$V_{BEN} = (0.026) \ln \left( \frac{1.25 \times 10^{-3}}{5 \times 10^{-14}} \right) = 0.6225 \text{ V}$$

Neglecting base currents,

$$\underline{V_{BB} = 1.2089 \text{ V}}$$

Then  $V_{EBP} = 1.2089 - 0.6225 = 0.5864 \text{ V}$

$$I_{CP} = 5 \times 10^{-14} \exp \left( \frac{0.5864}{0.026} \right) \Rightarrow \underline{I_{CP} = 0.312 \text{ mA}}$$

As a second approximation,

$$I_{CN} = i_L + I_{CP} = 1.25 + 0.31 \Rightarrow \underline{I_{CN} \approx 1.56 \text{ mA}}$$

$$V_{BEN} = (0.026) \ln \left( \frac{1.56 \times 10^{-3}}{5 \times 10^{-14}} \right) = 0.62826 \text{ V}$$

$$V_{EBP} = 1.2089 - 0.62826 = 0.5806 \text{ V}$$

$$I_{CP} = 5 \times 10^{-14} \exp \left( \frac{0.5806}{0.026} \right) \Rightarrow \underline{I_{CP} = 0.25 \text{ mA}}$$

13.14

$$R_1 + R_2 = \frac{V_{BB}}{(0.1)I_{BIAS}} = \frac{1.157}{0.018} = 64.28 \text{ k}\Omega$$

$$\begin{aligned} V_{BE} &= V_T \ln \left( \frac{I_C}{I_S} \right) = (0.026) \ln \left( \frac{(0.9)I_{BIAS}}{I_S} \right) \\ &= (0.026) \ln \left( \frac{0.162 \times 10^{-3}}{10^{-14}} \right) \end{aligned}$$

$$V_{BE} = 0.6112 \text{ V}$$

$$V_{BE} = \left( \frac{R_2}{R_1 + R_2} \right) V_{BB}$$

$$0.6112 = \left( \frac{R_2}{64.28} \right) (1.157)$$

So

$$R_2 = 33.96 \text{ k}\Omega$$

Then

$$R_1 = 30.32 \text{ k}\Omega$$

13.15

(a)  $A_d = -g_m(r_{o4} \| r_{o6} \| R_{i2})$

From example 13.4

$$g_m = \frac{9.5}{0.026} = 365 \mu\text{A/V}, \quad r_{o4} = 5.26 \text{ M}\Omega$$

Now

$$r_{o6} = r_{o4} = 5.26 \text{ M}\Omega$$

Assuming  $R_s = 0$ , we find

$$R_{i2} = r_{\pi 6} + (1 + \beta_n)R_E'$$

$$= 329 + (201)(50 \| 9.63) \Rightarrow 1.95 \text{ M}\Omega$$

Then

$$A_d = -(365)(5.26 \| 5.26 \| 1.95) \Rightarrow A_d = -409$$

(b) From Equation (13.20),

$$A_{v2} = \frac{-\beta_n(1 + \beta_n)R_9(R_{oc2} \| R_{i3} \| R_{o17})}{R_{i2}\{R_9 + [r_{\pi 17} + (1 + \beta_n)R_8]\}}$$

For  $R_8 = 0$ ,  $R_{i2} = 1.95 \text{ M}\Omega$

Using the results of Example 13.5

$$A_{v2} = \frac{-200(201)(50)(92.6 \| 4050 \| 92.6)}{(1950)(50 + 9.63)} \Rightarrow$$

$$A_{v2} = -792$$

13.16

Let  $I_{C10} = 40 \mu\text{A}$ , then  $I_{C1} = I_{C2} = 20 \mu\text{A}$ . Using Example 13.5,

$$R_{i2} = 4.07 \text{ M}\Omega$$

$$r_{\pi 6} = \frac{(200)(0.026)}{0.020} = 260 \text{ k}\Omega$$

$$g_{m6} = \frac{0.020}{0.026} = 0.769 \text{ mA/V}$$

$$r_{o6} = \frac{50}{0.02} \Rightarrow 2.5 \text{ M}\Omega$$

Then

$$R_{act1} = 2.5[1 + (0.769)(1 \| 260)] = 4.42 \text{ M}\Omega$$

$$r_{o6} = \frac{50}{0.02} \Rightarrow 2.5 \text{ M}\Omega$$

Then

$$A_d = -\left( \frac{I_{CQ}}{V_T} \right) (r_{o4} \| R_{act1} \| R_{i2})$$

$$= -\left( \frac{20}{0.026} \right) (2.5 \| 4.42 \| 4.07)$$

So

$$A_d = -882$$

13.17

Now

$$R_{e14} = \frac{r_{\pi 14} + R_{o1}}{1 + \beta_P} \text{ and } R_o = R_6 + R_{e14}$$

Assume series resistance of  $Q_{18}$  and  $Q_{19}$  is small. Then

$$R_{o1} = r_{o13A} \| R_{e22}$$

where  $R_{e22} = \frac{r_{\pi 22} + R_{o17} \| r_{o13B}}{1 + \beta_P}$

and  $R_{o17} = r_{o17}[1 + g_{m17}(R_8 \| r_{\pi 17})]$

Using results from Example 13.6,

$$r_{\pi 17} = 9.63 \text{ k}\Omega \quad r_{\pi 22} = 7.22 \text{ k}\Omega$$

$$g_{m17} = 20.8 \text{ mA/V} \quad r_{o17} = 92.6 \text{ k}\Omega$$

Then

$$R_{o17} = 92.6[1 + (20.8)(0.1 \| 9.63)] = 283 \text{ k}\Omega$$

$$r_{o13B} = \frac{50}{0.54} = 92.6 \text{ k}\Omega$$

Then

$$R_{e22} = \frac{7.22 + 283 \| 92.6}{51} = 1.51 \text{ k}\Omega$$

$$R_{o1} = r_{o13A} \| R_{e22} = 278 \| 1.51 = 1.50 \text{ k}\Omega$$

$$r_{\pi 14} = \frac{(50)(0.026)}{2} = 0.65 \text{ k}\Omega$$

Then

$$R_{e14} = \frac{0.65 + 1.50}{51} = 0.0422 \text{ k}\Omega$$

or

$$R_{e14} = 42.2 \Omega$$

Then

$$R_o = 42.2 + 27 \Rightarrow R_o = 69.2 \Omega$$

13.18

$$R_{id} = 2 \left[ r_{\pi 1} + (1 + \beta_n) \left( \frac{r_{\pi 3}}{1 + \beta_P} \right) \right]$$

Assume  $\beta_n = 200$  and  $\beta_P = 10$ 

Then

$$r_{\pi 1} = \frac{(200)(0.026)}{0.0095} = 547 \text{ k}\Omega$$

$$r_{\pi 3} = \frac{(10)(0.026)}{0.0095} = 27.4 \text{ k}\Omega$$

Then

$$R_{id} = 2 \left[ 547 + \frac{(201)(27.4)}{11} \right]$$

or

$$R_{id} = 2.095 \text{ M}\Omega$$

13.19

We can write

$$A(f) = \frac{A_0}{\left(1 + j \frac{f}{f_{PD}}\right) \left(1 + j \frac{f}{f_1}\right)}$$

$$= \frac{356,796}{\left(1 + j \frac{f}{5.43}\right) \left(1 + j \frac{f}{f_1}\right)}$$

Phase:

$$\phi = -\tan^{-1} \left( \frac{f}{5.43} \right) - \tan^{-1} \left( \frac{f}{f_1} \right)$$

For a phase margin =  $70^\circ$ ,  $\phi = -110^\circ$ 

So

$$-110^\circ = -\tan^{-1} \left( \frac{f}{5.43} \right) - \tan^{-1} \left( \frac{f}{f_1} \right)$$

Assuming  $f \gg 5.43$ , we have

$$\tan^{-1} \left( \frac{f}{f_1} \right) = 20^\circ \Rightarrow \frac{f}{f_1} = 0.364$$

At this frequency,  $|A(f)| = 1$ , so

$$1 = \frac{356,796}{\sqrt{1 + \left(\frac{f}{5.43}\right)^2} \cdot \sqrt{1 + (0.364)^2}}$$

$$= \frac{335,275}{\sqrt{1 + \left(\frac{f}{5.43}\right)^2}}$$

$$\text{or } \frac{f}{5.43} = 335,275 \Rightarrow f = 1.82 \text{ MHz}$$

Then, second pole at

$$f_1 = \frac{f}{0.364} \Rightarrow \underline{f_1 = 5 \text{ MHz}}$$

13.20

a. Original  $g_{m1}$  and  $g_{m2}$ 

$$K_{p1} = K_{p2} = \left( \frac{W}{L} \right) \left( \frac{\mu_p C_{ox}}{2} \right) = (12.5)(10)$$

$$= 125 \mu\text{A}/\text{V}^2$$

So

$$g_{m1} = g_{m2} = 2 \sqrt{K_{p1} \left( \frac{I_Q}{2} \right)} = 2 \sqrt{(0.125)(10)}$$

$$= 0.09975 \text{ mA}/\text{V}$$

If  $\left( \frac{W}{L} \right)$  is increased to 50, then

$$K_{p1} = K_{p2} = (50)(10) = 500 \mu\text{A}/\text{V}^2$$

So

$$g_{m1} = g_{m2} = 2 \sqrt{(0.5)(0.0199)} = 0.1995 \text{ mA}/\text{V}$$

b. Gain of first stage

$$A_d = g_{m1} (r_{o2} \parallel r_{o4}) = (0.1995)(5025 \parallel 5025)$$

or

$$\underline{A_d = 501}$$

Voltage gain of second stage remains the same, or

$$A_{v2} = 251$$

Then  $A_v = A_d \cdot A_{v2} = (501)(251)$ 

or

$$\underline{A_d = 125,751}$$

13.22

$$\text{a. } K_p = (10)(20) = 200 \mu\text{A}/\text{V}^2 = 0.2 \text{ mA}/\text{V}^2$$

$$I_{REF} = I_{SET} = \frac{10 - V_{SG} - (-10)}{200}$$

$$= k_P (V_{SG} - 1.5)^2$$

$$20 - V_{SG} = (0.2)(200)(V_{SG}^2 - 3V_{SG} + 2.25)$$

$$40V_{SG}^2 - 119V_{SG} + 70 = 0$$

$$V_{SG} = \frac{119 \pm \sqrt{(119)^2 - 4(40)(70)}}{2(40)}$$

$$\Rightarrow \underline{V_{SG} = 2.17 \text{ V}}$$

Then

$$I_{REF} = \frac{20 - 2.17}{200} \Rightarrow \underline{I_{REF} = 89.2 \mu\text{A}}$$

 $M_s$ ,  $M_6$ ,  $M_8$  matched transistors so that

$$\underline{I_Q = I_{D7} = I_{REF} = 89.2 \mu\text{A}}$$

b. Small-signal voltage gain of input stage:

$$A_d = \sqrt{2K_{p1}I_Q} \cdot (r_{o2} \| r_{o4})$$

$$r_{o2} = \frac{1}{\lambda_P I_D} = \frac{1}{(0.02) \left( \frac{89.2}{2} \right)} = 1.12 \text{ M}\Omega$$

$$r_{o4} = \frac{1}{\lambda_n I_D} = \frac{1}{(0.01) \left( \frac{89.2}{2} \right)} = 2.24 \text{ M}\Omega$$

Then

$$A_d = \sqrt{2(200)(89.2)} \cdot (1.12 \| 2.24)$$

or

$$\underline{A_d = 141}$$

Small-signal voltage gain of second stage:

$$A_{v2} = g_{m7}(r_{o7} \| r_{o8})$$

$$K_{n7} = (20)(20) = 400 \mu\text{A}/\text{V}^2$$

So

$$g_{m7} = 2\sqrt{K_{n7}I_{D7}} = 2\sqrt{(0.4)(0.0892)}$$

$$= 0.378 \text{ mA/V}$$

$$r_{o8} = \frac{1}{\lambda_P I_{D7}} = \frac{1}{(0.02)(0.0892)} = 561 \text{ k}\Omega$$

$$r_{o7} = \frac{1}{\lambda_n I_{D7}} = \frac{1}{(0.01)(0.0892)} = 1121 \text{ k}\Omega$$

So

$$A_{v2} = (0.378)(1121 \| 561) \Rightarrow \underline{A_{v2} = 141}$$

Then overall voltage gain

$$A_v = A_d \cdot A_{v2} = (141)(141) \Rightarrow \underline{A_v = 19,881}$$

13.23

Small-signal voltage gain of input stage:

$$A_d = \sqrt{2K_{p1}I_Q} \cdot (r_{o2} \| r_{o4})$$

$$K_{p1} = (10)(10) = 100 \mu\text{A}/\text{V}^2$$

$$r_{o2} = \frac{1}{\lambda_P \left( \frac{I_Q}{2} \right)} = \frac{1}{(0.01) \left( \frac{0.2}{2} \right)} = 1000 \text{ k}\Omega$$

$$r_{o4} = \frac{1}{\lambda_n \left( \frac{I_Q}{2} \right)} = \frac{1}{(0.005) \left( \frac{0.2}{2} \right)} = 2000 \text{ k}\Omega$$

Then

$$A_d = \sqrt{2(0.1)(0.2)} \cdot (1000 \| 2000)$$

or

$$\underline{A_d = 133}$$

Small-signal voltage gain of second stage:

$$A_{v2} = g_{m7}(r_{o7} \| r_{o8})$$

$$K_{n7} = (20)(20) = 400 \mu\text{A}/\text{V}^2$$

So

$$g_{m7} = 2\sqrt{K_{n7}I_{D7}} = 2\sqrt{(0.4)(0.2)}$$

$$= 0.566 \text{ mA/V}$$

$$r_{o8} = \frac{1}{\lambda_P I_{D7}} = \frac{1}{(0.01)(0.2)} = 500 \text{ k}\Omega$$

$$r_{o7} = \frac{1}{\lambda_n I_{D7}} = \frac{1}{(0.005)(0.2)} = 1000 \text{ k}\Omega$$

So

$$A_{v2} = (0.566)(1000 \| 500) \Rightarrow \underline{A_{v2} = 189}$$

Then overall voltage gain is

$$A_v = A_d \cdot A_{v2} = (133)(189) \Rightarrow \underline{A_v = 25,137}$$

13.24

$$f_{PD} = \frac{1}{2\pi R_{eq} C_i}$$

where  $R_{eq} = r_{o4} \| r_{o2}$  and  $C_i = C_1(1 + |A_{v2}|)$

We can find that

$$A_{v2} = 251 \text{ and } r_{o4} = r_{o2} = 5.025 \text{ M}\Omega$$

Now

$$R_{eq} = 5.025 \| 5.025 = 2.51 \text{ M}\Omega$$

and

$$C_i = 12(1 + 251) = 3024 \text{ pF}$$

So

$$f_{PD} = \frac{1}{2\pi(2.51 \times 10^6)(3024 \times 10^{-12})}$$

or

$$\underline{f_{PD} = 21.0 \text{ Hz}}$$

13.25

$$f_{PD} = \frac{1}{2\pi R_{eq} C_i}$$

where  $R_{eq} = r_{o4} \| r_{o2}$

From Problem 13.22,

$$r_{o2} = 1.12 \text{ M}\Omega, r_{o4} = 2.24 \text{ M}\Omega \text{ and } A_{v2} = 141$$

So

$$8 = \frac{1}{2\pi(1.12\|2.24) \times 10^6 \times C_i}$$

or

$$C_i = 2.66 \times 10^{-8} = C_1(1 + |A_{v2}|) = C_1(142)$$

or

$$C_1 = 188 \text{ pF}$$

13.26

$$R_o = r_{o7}\|r_{o8}$$

We can find that

$$r_{o7} = r_{o8} = 2.52 \text{ M}\Omega$$

Then


$$R_o = 2.52\|2.52$$

or

$$R_o = 1.26 \text{ M}\Omega$$

13.27

a.

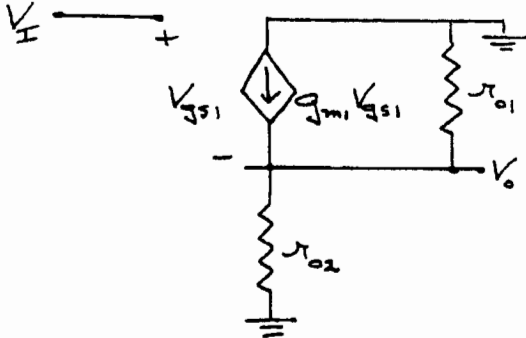

$$V_o = (g_{m1} V_{gs1})(r_{o1}\|r_{o2})$$

$$V_i = V_{gs1} + V_o$$

$$\text{Then } V_o = g_{m1}(r_{o1}\|r_{o2})(V_i - V_o)$$

or

$$A_v = \frac{g_{m1}(r_{o1}\|r_{o2})}{1 + g_{m1}(r_{o1}\|r_{o2})}$$

$$\text{b. } I_X + g_{m1} V_{gs1} = \frac{V_X}{r_{o2}} + \frac{V_X}{r_{o1}} \text{ and } V_{gs1} = -V_X$$

$$R_o = \frac{1}{g_{m1} \parallel r_{o1} \parallel r_{o2}}$$

13.28

$$\text{(a) } A_d = g_{m1}(R_{o6}\|R_{o8})$$

$$g_{m1} = 2\sqrt{K_n I_{DQ}} = 2\sqrt{(0.5)(0.025)} \Rightarrow 224 \mu\text{A/V}$$

$$g_{m1} = g_{m8}$$

$$g_{m6} = 2\sqrt{(0.5)(0.025)} \Rightarrow 224 \mu\text{A/V}$$

$$r_{o1} = r_{o6} = r_{o8} = r_{o10} = \frac{1}{\lambda I_{DQ}} = \frac{1}{(0.015)(25)} = 2.67 \text{ M}\Omega$$

$$r_{o4} = \frac{1}{\lambda I_{D4}} = \frac{1}{(0.015)(50)} \Rightarrow 133 \text{ M}\Omega$$

Now

$$R_{o8} = g_{m8}(r_{o8}\|r_{o10}) = (224)(2.67)(2.67) = 1597 \text{ M}\Omega$$

$$R_{o6} = g_{m6}(r_{o6})(r_{o4}\|r_{o1}) = (224)(2.67)(2.67\|133) \Rightarrow$$

$$R_{o6} = 531 \text{ M}\Omega$$

Then

$$A_d = (224)(531\|1597) \Rightarrow A_d = 89,264$$

$$\text{(b) } R_o = R_{o6}\|R_{o8} = 531\|1597 \Rightarrow R_o = 398 \text{ M}\Omega$$

$$\text{(c) } f_{PD} = \frac{1}{2\pi R_o C_L} = \frac{1}{2\pi(398 \times 10^6)(5 \times 10^{-12})} \Rightarrow$$

$$f_{PD} = 80 \text{ Hz}$$

$$GBW = (89,264)(80) \Rightarrow GBW = 7.14 \text{ MHz}$$

13.29

$$\text{(a) } r_{o1} = r_{o8} = r_{o10} = \frac{1}{\lambda_p I_D} = \frac{1}{(0.02)(25)} = 2 \text{ M}\Omega$$

$$r_{o6} = \frac{1}{\lambda_n I_D} = \frac{1}{(0.015)(25)} = 2.67 \text{ M}\Omega$$

$$r_{o4} = \frac{1}{\lambda_n I_{D4}} = \frac{1}{(0.015)(50)} = 1.33 \text{ M}\Omega$$

$$g_{m1} = 2\sqrt{\left(\frac{35}{2}\right)\left(\frac{W}{L}\right)_1 (25)} = 418 \sqrt{\left(\frac{W}{L}\right)_1} = g_{m8}$$

$$g_{m6} = 2\sqrt{\left(\frac{80}{2}\right)\left(\frac{W}{L}\right)_6 (25)} = 63.2 \sqrt{\left(\frac{W}{L}\right)_6}$$

$$R_o = R_{o6}\|R_{o8} = [g_{m6}(r_{o6})(r_{o4}\|r_{o1})][g_{m8}(r_{o8}\|r_{o10})]$$

$$\text{Define } X_1 = \sqrt{\left(\frac{W}{L}\right)_1} \text{ and } X_6 = \sqrt{\left(\frac{W}{L}\right)_6}$$

$$\text{Then } R_o = [63.2 X_6 (2.67)(1.33\|2)][418 X_1 (2)(2)]$$

$$= 134.8 X_6 \parallel 167.2 X_1 = \frac{22,539 X_1 X_6}{134.8 X_6 + 167.2 X_1}$$

$$A_d = g_{m1} R_o = (418 X_1) \left( \frac{22,539 X_1 X_6}{134.8 X_6 + 167.2 X_1} \right)$$

$$= 10,000$$

$$\text{Now } X_6 = \sqrt{\left(\frac{W}{L}\right)_6} = \sqrt{\frac{1}{2.2} \left(\frac{W}{L}\right)_1} = 0.674 X_1$$

We then find

$$X_1^2 = \left(\frac{W}{L}\right)_1 = 4.06 = \left(\frac{W}{L}\right)_p$$

and

$$\left(\frac{W}{L}\right)_n = 1.85$$

13.30

Let  $V^+ = 5V$ ,  $V^- = -5V$

$$P = I_T(10) = 3 \Rightarrow I_T = 0.3 \text{ mA}$$

$$\Rightarrow I_{REF} = 0.1 \text{ mA} = 100 \mu\text{A}$$

$$r_{o1} = r_{o8} = r_{o10} = \frac{1}{(0.02)(50)} = 1 \text{ M}\Omega$$

$$r_{o6} = \frac{1}{(0.015)(50)} = 1.33 \text{ M}\Omega$$

$$r_{o4} = \frac{1}{(0.015)(100)} = 0.667 \text{ M}\Omega$$

$$g_{m1} = 2 \sqrt{\left(\frac{35}{2}\right) \left(\frac{W}{L}\right)_1 (50)} = 59.2 X_1 = g_{m8}$$

$$\text{where } X_1 = \sqrt{\left(\frac{W}{L}\right)_1}$$

Assume all width-to-length ratios are the same.

$$g_{m6} = 2 \sqrt{\left(\frac{80}{2}\right) \left(\frac{W}{L}\right) (50)} = 89.4 X_1$$

Now

$$\begin{aligned} R_o &= R_{o6} \parallel R_{o8} = [g_{m6}(r_{o6})(r_{o4} \parallel r_{o1})] \parallel [g_{m8}(r_{o8}r_{o10})] \\ &= [89.4 X_1 (1.33)(0.667 \parallel 1)] \parallel [59.2 X_1 (1)(1)] \\ &= [47.6 X_1] \parallel [59.2 X_1] = \frac{(47.6 X_1)(59.2 X_1)}{47.6 X_1 + 59.2 X_1} \end{aligned}$$

$$\text{So } R_o = 26.4 X_1$$

Now

$$A_d = g_{m1} R_o = (59.2 X_1)(26.4 X_1) = 25,000$$

$$\text{So that } X_1^2 = \frac{W}{L} = 16 \text{ for all transistors}$$

$$(b) R_o = r_{o6} \parallel r_{o8} = 0.741 \parallel 0.741 \Rightarrow R_o = 371 \text{ k}\Omega$$

$$(c) f_{PD} = \frac{1}{2\pi R_o C} = \frac{1}{2\pi (371 \times 10^3)(5 \times 10^{-12})} \Rightarrow f_{PD} = 85.8 \text{ kHz}$$

$$GBW = (272)(85.8 \times 10^3) \Rightarrow GBW = 23.3 \text{ MHz}$$

13.32

$$(a) r_{o6} = \frac{1}{(0.02)(2.5)(40)} = 0.5 \text{ M}\Omega$$

$$r_{o8} = \frac{1}{(0.015)(2.5)(40)} = 0.667 \text{ M}\Omega$$

$$A_d = B g_{m1} (r_{o6} \parallel r_{o8})$$

$$400 = (2.5) g_{m1} (0.5 \parallel 0.667) \Rightarrow g_{m1} = 560 \mu\text{A/V}$$


$$g_{m1} = 560 = 2 \sqrt{\left(\frac{80}{2}\right) \left(\frac{W}{L}\right) (40)} \Rightarrow \left(\frac{W}{L}\right) = 49$$

Assume all  $(W/L)$  ratios are the same except for

$$M_5 \text{ and } M_6. \left(\frac{W}{L}\right)_5 = \left(\frac{W}{L}\right)_6 = 122.5$$

(b) Assume the bias voltages are

$$V^+ = 5V, V^- = -5V.$$

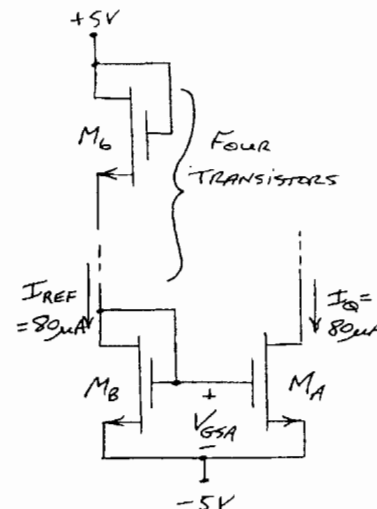

$$\text{Assume } \left(\frac{W}{L}\right)_A = \left(\frac{W}{L}\right)_B = 49$$

$$I_Q = \left(\frac{80}{2}\right) (49) (V_{GS4} - 0.5)^2 = 80 \Rightarrow V_{GS4} = 0.702 \text{ V}$$

Then

$$I_{REF} = 80 = \left(\frac{80}{2}\right) \left(\frac{W}{L}\right)_C (V_{GS4} - 0.5)^2$$

13.31

$$(a) A_d = B g_{m1} (r_{o6} \parallel r_{o8})$$

$$r_{o6} = r_{o8} = \frac{1}{\lambda I_{DQ}} = \frac{1}{(0.015)(90)} = 0.741 \text{ M}\Omega$$

$$g_{m1} = 2 \sqrt{\left(\frac{k'_n}{2}\right) \left(\frac{W}{L}\right) I_{D1}} = 2 \sqrt{(500)(30)} = 245 \mu\text{A/V}$$

$$A_d = (3)(245)(0.741 \parallel 0.741) \Rightarrow A_d = 272$$

For four transistors

$$V_{GSC} = \frac{10 - 0.702}{4} = 2.325 V$$

$$80 = \left(\frac{80}{2}\right) \left(\frac{W}{L}\right)_c (2.325 - 0.5)^2 \Rightarrow \left(\frac{W}{L}\right)_c = 0.60$$

$$(c) f_{3-dB} = \frac{1}{2\pi R_o C} \quad R_o = 0.5 \parallel 0.667 = 0.286 M\Omega$$

$$f_{3-dB} = \frac{1}{2\pi(286 \times 10^3)(3 \times 10^{-12})} = 185 \text{ kHz}$$

$$GBW = (400)(185 \times 10^3) \Rightarrow 74 \text{ MHz}$$

13.33

(a) From previous results, we can write

$$R_{o10} = g_{m10}(r_{o10}r_{o6})$$

$$R_{o12} = g_{m12}(r_{o12}r_{o8})$$

$$A_d = Bg_{m1}(R_{o10} \parallel R_{o12})$$

Now

$$r_{o10} = r_{o6} = \frac{1}{\lambda_p B(I_Q/2)} = \frac{1}{(0.02)(2.5)(40)} = 0.5 M\Omega$$

$$r_{o12} = r_{o8} = \frac{1}{\lambda_n B(I_Q/2)} = \frac{1}{(0.015)(2.5)(40)} = 0.667 M\Omega$$

Assume all transistors have the same width-to-length ratios except for  $M_5$  and  $M_6$ .

$$\text{Let } \left(\frac{W}{L}\right) = X^2$$

Then

$$g_{m10} = 2\sqrt{\left(\frac{k'_p}{2}\right) \left(\frac{W}{L}\right)_{10} (I_{DQ10})} = 2\sqrt{\left(\frac{35}{2}\right) X^2 (2.5)(40)} = 83.67 X$$

$$g_{m12} = 2\sqrt{\left(\frac{k'_n}{2}\right) \left(\frac{W}{L}\right)_{12} (I_{DQ12})} = 2\sqrt{\left(\frac{80}{2}\right) X^2 (2.5)(40)} = 126.5 X$$

$$g_{m1} = 2\sqrt{\left(\frac{80}{2}\right) X^2 (40)} = 80 X$$

Then

$$R_{o10} = (83.67 X)(0.5)(0.5) = 20.9 X M\Omega$$

$$R_{o12} = (126.5 X)(0.667)(0.667) = 56.3 X M\Omega$$

We want

$$20,000 = (2.5)(80 X)[20.9 X \parallel 56.3 X] \\ = 200 X \left[ \frac{(20.9 X)(56.3 X)}{20.9 X + 56.3 X} \right] = 3048 X^2$$


Then

$$X^2 = 6.56 = \left(\frac{W}{L}\right)$$

Then

$$\left(\frac{W}{L}\right)_6 = \left(\frac{W}{L}\right)_5 = (2.5)(6.56) = 16.4$$

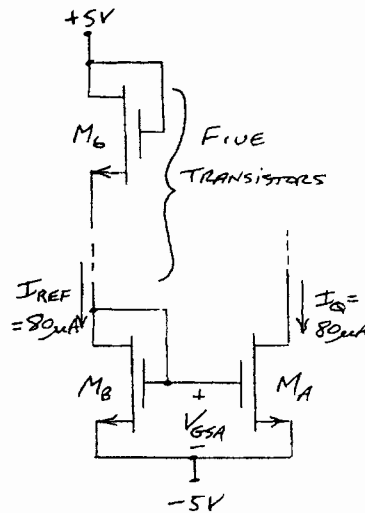(b) Assume bias voltages are  $V^+ = 5V$ ,  $V^- = -5V$



$$\text{Assume } \left(\frac{W}{L}\right)_A = \left(\frac{W}{L}\right)_B = 6.56$$

$$I_Q = 80 = \left(\frac{80}{2}\right) (6.56)(V_{GS4} - 0.5)^2 \Rightarrow$$

$$V_{GS4} = 1.052 V$$

Need 5 transistors in series

$$V_{GSC} = \frac{10 - 1.052}{5} = 1.79 V$$

Then

$$I_{REF} = 80 = \left(\frac{80}{2}\right) \left(\frac{W}{L}\right)_c (1.79 - 0.5)^2 \Rightarrow$$

$$\left(\frac{W}{L}\right)_c = 1.20$$

$$(c) f_{3-dB} = \frac{1}{2\pi R_o C} \quad \text{where } R_o = R_{o10} \parallel R_{o12}$$

Now

$$R_{o10} = 20.9\sqrt{6.56} = 53.5 M\Omega$$

$$R_{o12} = 56.3\sqrt{6.56} = 144 M\Omega$$

Then

$$R_o = 53.5 \parallel 144 = 39 M\Omega$$

$$f_{3-dB} = \frac{1}{2\pi(39 \times 10^6)(3 \times 10^{-12})} = 1.36 \text{ kHz}$$

$$GBW = (20,000)(1.36 \times 10^3) \Rightarrow GBW = 27.2 \text{ MHz}$$

13.34

$$A_d = g_m(M_2) \cdot [r_{o2}(M_2) \parallel r_{o2}(Q_2)]$$

$$g_m(M_2) = 2 \sqrt{\left(\frac{40}{2}\right)(25)(100)} = 447 \mu A/V$$

$$r_{o2}(M_2) = \frac{1}{\lambda_{DQ}} = \frac{1}{(0.02)(0.1)} = 500 \text{ k}\Omega$$

$$r_{o2}(Q_2) = \frac{V_A}{I_{CQ}} = \frac{120}{0.1} = 1200 \text{ k}\Omega$$

Then

$$A_d = 447(0.5 \parallel 1.2) \Rightarrow A_d = 158$$

13.35

$$A_d = g_m(M_2) \cdot [r_{o2}(M_2) \parallel r_{o2}(Q_2)]$$

$$g_m(M_2) = 2 \sqrt{\left(\frac{80}{2}\right)(25)(100)} = 632 \mu A/V$$

$$r_{o2}(M_2) = \frac{1}{\lambda_{DQ}} = \frac{1}{(0.015)(0.1)} = 667 \text{ k}\Omega$$

$$r_{o2}(Q_2) = \frac{V_A}{I_{CQ}} = \frac{80}{0.1} = 800 \text{ k}\Omega$$

$$A_d = (632)(0.667 \parallel 0.80) \Rightarrow A_d = 230$$

13.36

$$I_{REF} = 200 \mu A \quad K_n = K_p = 0.5 \text{ mA}/V^2$$

$$\lambda_n = \lambda_p = 0.015 V^{-1}$$

$$A_d = g_{m1}(R_{o6} \parallel R_{o8})$$

where

$$R_{o8} = g_{m8}(r_{o8} r_{o10})$$

$$R_{o6} = g_{m6}(r_{o6})(r_{o4} \parallel r_{o1})$$

Now

$$g_{m8} = 2 \sqrt{K_p I_{D8}} = 2 \sqrt{(0.5)(0.1)} = 0.447 \text{ mA}/V$$

$$r_{o8} = \frac{1}{\lambda_p I_{D8}} = \frac{1}{(0.015)(0.1)} = 667 \text{ k}\Omega$$

$$r_{o10} = \frac{1}{\lambda_p I_{D8}} = 667 \text{ k}\Omega$$

$$g_{m6} = \frac{I_{C6}}{V_T} = \frac{0.1}{0.026} = 3.846 \text{ mA}/V$$

$$r_{o6} = \frac{V_A}{I_{C6}} = \frac{80}{0.1} = 800 \text{ k}\Omega$$

$$r_{o4} = \frac{1}{\lambda_n I_{D4}} = \frac{1}{(0.015)(0.2)} = 333 \text{ k}\Omega$$

$$r_{o1} = \frac{1}{\lambda_p I_{D1}} = \frac{1}{(0.015)(0.1)} = 667 \text{ k}\Omega$$

$$g_{m1} = 2 \sqrt{K_p I_{D1}} = 2 \sqrt{(0.5)(0.1)} = 0.447 \text{ mA}/V$$

So

$$R_{o8} = (0.447)(667)(667) \Rightarrow 198.9 \text{ M}\Omega$$

$$R_{o6} = (3.846)(800)(333 \parallel 667) \Rightarrow 683.4 \text{ M}\Omega$$

Then

$$A_d = 447(198.9 \parallel 683.4) \Rightarrow A_d = 68,865$$

13.37

Assume biased at  $V^+ = 10V$ ,  $V^- = -10V$ .

$$P = 3I_{REF}(20) = 10 \Rightarrow I_{REF} = 167 \mu A$$

$$A_d = g_{m1}(R_{o6} \parallel R_{o8}) = 25,000$$

$$k'_n = 80 \mu A/V^2, k'_p = 35 \mu A/V^2$$

$$\lambda_n = 0.015 V^{-1}, \lambda_p = 0.02 V^{-1}$$

Assume  $\left(\frac{W}{L}\right)_p = 2.2 \left(\frac{W}{L}\right)_n$

$$R_{o8} = g_{m8}(r_{o8} r_{o10})$$

$$R_{o6} = g_{m6}(r_{o6})(r_{o4} \parallel r_{o1})$$

$$r_{o8} = \frac{1}{\lambda_p I_{D8}} = \frac{1}{(0.02)(83.3)} = 0.60 \text{ M}\Omega$$

$$r_{o10} = \frac{1}{\lambda_p I_{D8}} = 0.60 \text{ M}\Omega$$

$$g_{m8} = 2 \sqrt{\left(\frac{k'_p}{2}\right)\left(\frac{W}{L}\right)_8 I_{D8}} = 2 \sqrt{\left(\frac{35}{2}\right)(2.2)X^2(83.3)}$$

$$= 113.3X$$

where  $X^2 = \left(\frac{W}{L}\right)_n$

$$r_{o6} = \frac{V_A}{I_{C6}} = \frac{80}{83.3} = 0.960 \text{ M}\Omega$$

$$r_{o4} = \frac{1}{\lambda_n I_{D4}} = \frac{1}{(0.015)(167)} = 0.40 \text{ M}\Omega$$

$$r_{o1} = \frac{1}{\lambda_p I_{D1}} = \frac{1}{(0.02)(83.3)} = 0.60 \text{ M}\Omega$$

$$g_{m6} = \frac{I_{C6}}{V_T} = \frac{83.3}{0.026} = 3204 \mu A/V$$

$$g_{m1} = 2 \sqrt{\left(\frac{k'_p}{2}\right)\left(\frac{W}{L}\right)_1 I_{D1}} = 2 \sqrt{\left(\frac{35}{2}\right)(2.2)X^2(83.3)}$$

$$= 113.3X$$

Now

$$R_{o6} = (3204)(0.960)[0.40 \parallel 0.60] = 738 \text{ M}\Omega$$

$$R_{o8} = (113.3X)(0.60)(0.60) = 40.8X \text{ M}\Omega$$

Then

$$A_d = 25,000 = (113.3X)[738 \parallel 40.8X]$$

$$= (113.3X) \left[ \frac{30,110X}{738 + 40.8X} \right]$$

which yields  $X = 2.48$   
or

$$X^2 = 6.16 = \left(\frac{W}{L}\right)_n$$

and

$$\left(\frac{W}{L}\right)_p = (2.2)(6.16) = 12.3$$

13.38

For  $v_{cm}(\max)$ , assume  $V_{CB}(Q_3) = 0$ . Then

$$V_S = 15 - 0.6 - 0.6 = 13.8 \text{ V}$$

$$I_{D9} = I_{D10} = \frac{0.236}{2} = 0.118 \text{ mA}$$

Using parameters given in Example 13.11

$$V_{SG} = \sqrt{\frac{I_{D9}}{K_p}} - V_{TP} = \sqrt{\frac{0.118}{0.20}} + 1.4 = 2.17 \text{ V}$$

Then

$$v_{cm}(\max) = 13.8 - 2.17 \Rightarrow v_{cm}(\max) = 11.6 \text{ V}$$

For

$v_{cm}(\min)$ , assume

$$\begin{aligned} V_{SD}(M_9) = V_{SD}(\text{sat}) = V_{SG} + V_{TP} \\ = 2.17 - 1.4 = 0.77 \text{ V} \end{aligned}$$

Now

$$\begin{aligned} V_{D10} = I_{D10}(0.5) + 0.6 + I_{D10}(0.5) - 15 \\ = 0.118 + 0.6 - 15 \Rightarrow V_{D10} = -14.28 \text{ V} \end{aligned}$$

Then

$$\begin{aligned} v_{cm}(\min) = -14.28 + V_{SD}(\text{sat}) - V_{SG} \\ = -14.28 + 0.77 - 2.17 = -15.68 \text{ V} \end{aligned}$$

Then, common-mode voltage range

$$\underline{-15.68 < v_{cm} < 11.6}$$

Or, assuming the input is limited to  $\pm 15 \text{ V}$ , then

$$\underline{-15 < v_{cm} < 11.6 \text{ V}}$$

13.39

For  $I_1 = I_2 = 300 \mu\text{A}$ ,

$$V_{SG} = V_{BE} + (0.3)(8) = 0.6 + 2.4 = 3.0 \text{ V}$$

Then

$$\begin{aligned} I_2 = K_p(V_{SG} + V_{TP})^2 \\ 0.3 = K_p(3 - 1.4)^2 \\ \Rightarrow \underline{K_p = 0.117 \text{ mA/V}^2} \end{aligned}$$

13.40

For  $V_{CB} = 0$  for both  $Q_6$  and  $Q_7$ , then

$$V_S = 0.6 + 0.6 + V_{SG} + (-V_S)$$

$$\text{So } 2V_S = 1.2 + V_{SG}$$

Now

$$0.6 + I_2 R_1 = V_{SG} = \sqrt{\frac{I_1}{K_p}} + V_{TP} \text{ and } I_1 = I_2$$

$$\text{Also } I_1 = I_2 = K_p(V_{SG} + V_{TP})^2 \text{ so}$$

$$0.6 + (0.25)(8)(V_{SG} - 1.4)^2 = V_{SG}$$

$$0.6 + 2(V_{SG}^2 - 2.8V_{SG} + 1.96) = V_{SG}$$

$$2V_{SG}^2 - 6.6V_{SG} + 4.52 = 0$$

$$V_{SG} = \frac{6.6 \pm \sqrt{(6.6)^2 - 4(2)(4.52)}}{2(2)} = 2.33 \text{ V}$$

$$\text{Then } 2V_S = 1.2 + 2.33 = 3.53 \text{ and}$$

$$\underline{V_S = 1.765 \text{ V}}$$

13.41

$$I_{C3} = I_{C4} = 300 \mu\text{A}$$

Using the parameters from Examples 13.12 and 13.13, we have

$$R_{12} = r_{\pi 13} = \frac{\beta_n V_T}{I_{C13}} = \frac{(200)(0.026)}{0.3} = 17.3 \text{ k}\Omega$$

$$A_d = \sqrt{2K_p I_{Q3}} \cdot (R_{12}) = \sqrt{2(0.6)(0.3)} \cdot (17.3)$$

or

$$\underline{A_d = 10.38}$$

Now

$$g_{m13} = \frac{I_{C13}}{V_T} = \frac{0.3}{0.026} = 11.5 \text{ mA/V}$$

$$r_{o13} = \frac{V_A}{I_{C13}} = \frac{50}{0.3} = 167 \text{ k}\Omega$$

Then

$$|A_{v2}| = g_{m13} \cdot r_{o13} = (11.5)(167)$$

or

$$\underline{|A_{v2}| = 1917}$$

Overall gain:

$$\underline{|A_v| = (10.38)(1917) = 19,895}$$

13.42

Assuming the resistances looking into  $Q_4$  and into the output stage are very large, we have

$$|A_{v2}| = \frac{\beta R_{o13}}{r_{\pi 13} + (1 + \beta)R_{E13}}$$

$$\text{where } R_{o13} = r_{o13}[1 + g_{m13}(R_{E13} || r_{\pi 13})]$$

$$I_{C13} = 300 \mu\text{A}, r_{o13} = \frac{50}{0.3} = 167 \text{ k}\Omega$$

$$g_{m13} = \frac{0.3}{0.026} = 11.5 \text{ mA/V}$$

$$r_{\pi13} = \frac{(200)(0.026)}{0.3} = 17.3 \text{ k}\Omega$$

So

$$R_{o13} = (167)[1 + (11.5)(1||17.3)] \Rightarrow 1.98 \text{ M}\Omega$$

Then

$$|A_{v2}| = \frac{(200)(1980)}{17.3 + (201)(1)} = 1814$$

Now

$$C_i = C_1(1 + |A_{v2}|) = 12[1 + 1814]$$

$$\Rightarrow C_i = 21,780 \text{ pF}$$

$$f_{PD} = \frac{1}{2\pi R_{eq} C_i}$$

$$R_{eq} = R_{i2} || r_{o12} || r_{o10}$$

Neglecting  $R_3$ ,

$$r_{o10} = \frac{1}{\lambda I_{D10}} = \frac{1}{(0.02)(0.15)} = 333 \text{ k}\Omega$$

Neglecting  $R_5$ ,

$$r_{o12} = \frac{50}{0.15} = 333 \text{ k}\Omega$$

$$R_{i2} = r_{\pi13} + (1 + \beta)R_{E13} = 17.3 + (201)(1) = 218 \text{ k}\Omega$$

Then

$$f_{PD} = \frac{1}{2\pi[218 || 333 || 333] \times 10^3 \times (21,780) \times 10^{-12}}$$

or

$$f_{PD} = 77.4 \text{ Hz}$$

Unity-Gain Bandwidth

Gain of first stage:

$$\begin{aligned} A_d &= \sqrt{2K_n I_{Q5}} \cdot (R_{i2} || r_{o12} || r_{o10}) \\ &= \sqrt{2(0.6)(0.3)} \cdot (218 || 333 || 333) \\ &= (0.6)(218 || 333 || 333) \end{aligned}$$

or  $A_d = 56.6$

Overall gain:

$$A_v = (56.6)(1814) = 102,672$$

Then unity-gain bandwidth =  $(77.4)(102,672)$

$$\Rightarrow 7.95 \text{ MHz}$$

13.43

Since  $V_{GS} = 0$  in  $J_6$ ,  $I_{REF} = I_{DSS}$

$$\Rightarrow I_{DSS} = 0.8 \text{ mA}$$

13.44

a.  $R_{i2} = r_{\pi5} + (1 + \beta)[r_{\pi6} + (1 + \beta)R_E]$

$$r_{\pi6} = \frac{(100)(0.026)}{0.2} = 13 \text{ k}\Omega$$

$$I_{C5} \approx \frac{I_{C6}}{\beta} = \frac{200 \mu\text{A}}{100} = 2 \mu\text{A}$$

So

$$r_{\pi5} = \frac{(100)(0.026)}{0.002} = 1300 \text{ k}\Omega$$

Then

$$R_{i2} = 1300 + (101)[13 + (101)(0.3)]$$

or

$$R_{i2} = 5.67 \text{ M}\Omega$$

b.  $A_v = g_{m2}(r_{o2} || r_{o4} || R_{i2})$

$$g_{m2} = \frac{2}{V_P} \cdot \sqrt{I_D \cdot I_{DSS}} = \frac{2}{3} \cdot \sqrt{(0.1)(0.2)} = 0.0943 \text{ mA/V}$$

$$r_{o2} = \frac{1}{\lambda I_D} = \frac{1}{(0.02)(0.1)} = 500 \text{ k}\Omega$$

$$r_{o4} = \frac{V_A}{I_{C4}} = \frac{5.0}{0.1} = 500 \text{ k}\Omega$$

Then

$$A_v = (0.0943)[500 || 500 || 5670]$$

or

$$A_v = 22.6$$

13.45

a. Need  $V_{SD}(Q_E) \geq V_{SD}(\text{sat}) = V_P$   
For minimum bias  $\pm 3 \text{ V}$

Set  $V_P = 3 \text{ V}$  and  $V_{ZK} = 3 \text{ V}$

$$I_{REF2} = \frac{V_{ZK} - V_{D1}}{R_3}$$

so that  $R_3 = \frac{3 - 0.6}{0.1} \Rightarrow R_3 = 24 \text{ k}\Omega$

Set bias in  $Q_E = I_{REF2} + I_{Z2} = 0.1 + 0.1 = 0.2 \text{ mA}$

Therefore,

$$I_{DSS} = 0.2 \text{ mA}$$

b. Neglecting base currents

$$I_{O1} = I_{REF1} = 0.5 \text{ mA} = \frac{12 - 0.6}{R_4}$$

so that

$$\underline{R_4 = 22.8 \text{ k}\Omega}$$

13.46

a. We have

$$g_{m2} = \frac{2}{|V_P|} \cdot \sqrt{I_D \cdot I_{DSS}} = \frac{2}{4} \cdot \sqrt{(0.5)(1)}$$

$$= 0.354 \text{ mA/V}$$

$$r_{o2} = \frac{1}{\lambda I_D} = \frac{1}{(0.02)(0.5)} = 100 \text{ k}\Omega$$

$$r_{o4} = \frac{V_A}{I_D} = \frac{100}{0.5} = 200 \text{ k}\Omega$$

$$g_{m4} = \frac{0.5}{0.026} = 19.23 \text{ mA/V}$$

$$r_{\pi 4} = \frac{(200)(0.026)}{0.5} = 10.4 \text{ k}\Omega$$

So

$$R_{o4} = r_{o4} [1 + g_{m4} (r_{\pi 4} \parallel R_2)]$$

$$= 200 [1 + (19.23)(10.4 \parallel 0.5)]$$

$$= 2035 \text{ k}\Omega$$

$$|A_d| = g_{m2} (r_{o2} \parallel R_{o4} \parallel R_L)$$

For  $R_L \rightarrow \infty$

$$|A_d| = 0.354(100 \parallel 2035) = 33.7$$

With these parameter values, gain can never reach 500.

b. Similarly for this part, gain can never reach 700.



## Chapter 14

## Exercise Solutions

E14.1

$$v_{iCM}(\max) = V^+ - V_{SD1}(\text{sat}) - V_{SD1}$$

$$v_{iCM}(\min) = V^- + V_{DS4}(\text{sat}) + V_{SD1}(\text{sat}) - V_{SD1}$$

We have:

$$I_{REF} = 100 \mu\text{A}, \quad k'_n = 80 \mu\text{A}/V^2, \quad k'_p = 40 \mu\text{A}/V^2,$$

$$\left(\frac{W}{L}\right) = 25$$

For  $M_1$ :

$$I_D = 50 = \left(\frac{40}{2}\right)(25)(V_{SD1} + V_{TP})^2$$

$$\text{So } 50 = 500(V_{SD1} - 0.5)^2 \Rightarrow V_{SD1} = 0.816\text{V}$$

$$V_{SD1}(\text{sat}) = 0.816 - 0.5 = 0.316\text{V}$$

Then

$$v_{CM}(\max) = V^+ - 0.316 - 0.816 = V^+ - 1.13\text{V}$$

For  $M_4$ :

$$I_D = 100 = \left(\frac{80}{2}\right)(25)(V_{GS4} - V_{TN})^2$$

$$\text{So } 100 = 1000(V_{GS4} - 0.5)^2 \Rightarrow V_{GS4} = 0.816\text{V}$$

$$V_{DS4}(\text{sat}) = 0.816 - 0.5 = 0.316\text{V}$$

$$v_{CM}(\min) = V^- + 0.316 + 0.316 - 0.816 = V^- - 0.184$$

So

$$\underline{V^- - 0.184 \leq v_{CM} \leq V^+ - 1.13\text{V}}$$

E14.2

$$v_o(\max) = V^+ - V_{SD8}(\text{sat}) - V_{SD10}(\text{sat})$$

$$v_o(\min) = V^- + V_{DS4}(\text{sat}) + V_{DS6}(\text{sat})$$

Now

$$V_{SD8} = V_{SD10} = \sqrt{\frac{50}{(40/2)(25)}} + 0.5 = 0.816\text{V}$$

$$V_{SD8}(\text{sat}) = V_{SD10}(\text{sat}) = 0.316\text{V}$$

$$\text{So } v_o(\max) = V^+ - 0.316 - 0.316 = V^+ - 0.632$$

Also

$$V_{GS6} = \sqrt{\frac{50}{(80/2)(25)}} + 0.5 = 0.724\text{V}$$

$$V_{GS4} = \sqrt{\frac{100}{(80/2)(25)}} + 0.5 = 0.816\text{V}$$

$$V_{DS6}(\text{sat}) = 0.724 - 0.5 = 0.224\text{V}$$

$$V_{DS4}(\text{sat}) = 0.816 - 0.5 = 0.316\text{V}$$

$$\text{So } v_o(\min) = V^- + 0.316 + 0.224 = V^- + 0.54$$

Then

$$\underline{V^- + 0.54 \leq v_o \leq V^+ - 0.632\text{V}}$$

E14.3

$$\text{a. } A_{CL} = \frac{-50}{1 + \left(\frac{1}{5 \times 10^4}\right)(51)} \Rightarrow \underline{A_{CL} = -49.949}$$

$$\text{b. } \frac{dA_{CL}}{A_{CL}} = 10 \times \frac{51}{5 \times 10^4} \Rightarrow \frac{dA_{CL}}{A_{CL}} = 0.0102\%$$

$$A_{CL} = \frac{-50}{1 + \frac{51}{4.5 \times 10^4}} \Rightarrow \underline{A_{CL} = -49.943}$$

E14.4

$$A_{CL}(\text{ideal}) = -\frac{500}{20} = -25$$

$$\text{Within } 0.1\% \Rightarrow -25 + (0.001)(25)$$

$$\Rightarrow A_{CL} = -24.975$$

$$-24.975 = \frac{-25}{1 + \frac{26}{A_{0L}}}$$

$$\frac{26}{A_{0L}} = \frac{-25}{-24.975} - 1 = 0.0010$$

$$\underline{A_{0L} = 25.974}$$

E14.5

$$\text{a. } A_{CL} = \frac{A_{CL}(\infty)}{1 + \left[\frac{A_{CL}(\infty)}{A_{0L}}\right]}$$

$$A_{CL}(\infty) = 1 + \frac{R_2}{R_1} = 1 + \frac{495}{5} = 100$$

$$A_{CL} = \frac{100}{1 + \frac{100}{10^5}} \Rightarrow \underline{A_{CL} = 99.90}$$

$$\underline{A_{CL}(\infty) = 100}$$

$$\text{b. } \frac{dA_{CL}}{A_{CL}} = 10 \times \frac{100}{10^5} = 0.01\%$$

$$A_{CL} = 99.90 - (0.0001)(99.90)$$

$$\Rightarrow \underline{A_{CL} = 99.89}$$

E14.6

$$\frac{A_{CL}(\infty) - A_{CL}}{A_{CL}(\infty)} = 1 - \frac{A_{CL}}{A_{CL}(\infty)} = 1 - \frac{1}{1 + \frac{A_{CL}(\infty)}{A_{CL}}}$$

$$\text{So } 0.001 = \frac{1 + \frac{A_{CL}(\infty)}{A_{CL}} - 1}{1 + \frac{A_{CL}(\infty)}{A_{CL}}} = \frac{\frac{A_{CL}(\infty)}{A_{CL}}}{1 + \frac{A_{CL}(\infty)}{A_{CL}}}$$

$$0.001 = 0.999 \cdot \frac{A_{CL}(\infty)}{A_{OL}}$$

$$A_{CL}(\infty) = \frac{0.001}{0.999} \cdot A_{OL} = \frac{0.001}{0.999} \cdot (10^4)$$

$$\Rightarrow \underline{A_{CL}(\infty) = 10.010}$$

or

$$A_{CL} = (1 - 0.001)(10.010)$$

$$\Rightarrow \underline{A_{CL} = 10.0}$$

E14.7

a. For  $R_o = 0$ 

$$\frac{1}{R_{i,f}} = \frac{1}{10} + \frac{1}{10}(1 + 10^4) = 0.1 + 10^3$$

$$\Rightarrow \underline{R_{i,f} = 10^{-3} \text{ k}\Omega = 1 \text{ }\Omega}$$

b. For  $R_o = 10 \text{ k}\Omega$ 

$$\frac{1}{R_{i,f}} = \frac{1}{10} + \frac{1}{10} \times \left[ \frac{1 + 10^4 + 1}{1 + 1 + 1} \right] \approx 0.1 + \frac{10^4}{3(10)}$$

$$R_{i,f} = 3 \times 10^{-3} \text{ k}\Omega$$

$$\Rightarrow \underline{R_{i,f} = 3 \text{ }\Omega}$$

E14.8

$$\frac{i_I}{i_1} = \left( \frac{R_{i,f}}{R_1} \right)$$

$$\text{a. } \frac{i_I}{i_1} = \frac{0.1}{10^4} = \underline{1 \times 10^{-5}}$$

$$\text{b. } \frac{i_I}{i_1} = \frac{10}{10^4} = \underline{1 \times 10^{-3}}$$

E14.9

$$R_{i,f} = \frac{40(1 + 10^4) + 99 \left( 1 + \frac{40}{1} \right)}{1 + \frac{99}{1}}$$

$$\approx \frac{4 \times 10^5 + 4.059 \times 10^3}{100}$$

$$R_{i,f} = 4.04 \times 10^3 \text{ k}\Omega \Rightarrow \underline{R_{i,f} = 4.04 \text{ M}\Omega}$$

E14.10

Voltage follower  $R_2 = 0$ ,  $R_1 = \infty$ 

$$R_{i,f} = R_i(1 + A_{OL}) = 10(1 + 5 \times 10^5)$$

$$\approx 5 \times 10^6 \text{ k}\Omega \Rightarrow \underline{R_{i,f} = 5000 \text{ M}\Omega}$$

E14.11

$$1 + \frac{R_2}{R_1} = 100$$

$$\text{a. } \frac{1}{R_{o,f}} = \frac{1}{100} \left[ \frac{10^5}{100} \right] = 10$$

$$\Rightarrow \underline{R_{o,f} = 0.1 \text{ }\Omega}$$

$$\text{b. } \frac{1}{R_{o,f}} = \frac{1}{10} \left[ \frac{10^5}{100} \right] = 10^2$$

$$R_{o,f} = 10^{-2} \text{ k}\Omega \Rightarrow \underline{R_{o,f} = 10 \text{ }\Omega}$$

E14.12

From Equation (14.43)

$$A_{CL}(f) = \frac{A_{CL0}}{1 + j \cdot \frac{f}{f_{PD}(A_0/A_{CL0})}}$$

$$= \frac{25}{1 + j \cdot \frac{f}{(50)(10^4/25)}} = \frac{25}{1 + j \cdot \frac{f}{2 \times 10^4}}$$

a. For  $f = 2 \text{ kHz}$ 

$$\frac{\nu_o}{\nu_I} = 25 \Rightarrow \underline{\nu_o(\text{peak}) = 1.25 \text{ mV}}$$

b.  $f = 20 \text{ kHz}$ 

$$\frac{\nu_o}{\nu_I} = \frac{1}{\sqrt{2}} \cdot 25 \Rightarrow \underline{\nu_o(\text{peak}) = 0.884 \text{ mV}}$$

c.  $f = 100 \text{ kHz}$ 

$$\frac{\nu_o}{\nu_I} = \frac{25}{\sqrt{1 + (100/20)^2}} = \frac{25}{5.099} = 4.90$$

$$\Rightarrow \underline{\nu_o = 0.245 \text{ mV}}$$

E14.13

Full-scale response =  $1 \times 5 = 5 \text{ V}$ 

$$t = \frac{5}{2} \Rightarrow \underline{t = 2.5 \text{ }\mu\text{s}}$$

E14.14

$$\text{a. } F_{PBW} = \frac{SR}{2\pi V_o(\text{max})} = \frac{0.63 \times 10^6}{2\pi(1)}$$

$$F_{PBW} = 1.0 \times 10^5 \Rightarrow \underline{F_{PBW} = 100 \text{ kHz}}$$

$$\text{b. } F_{PBW} = \frac{0.63 \times 10^6}{2\pi(10)} = 1.0 \times 10^4$$

$$\Rightarrow \underline{F_{PBW} = 10 \text{ kHz}}$$

E14.15

$$f_{3dB} = \frac{f_T}{A_{CL0}} = \frac{(10^5)(10)}{50} \Rightarrow 20 \text{ kHz}$$

$$f_{\max} = f_{3dB} = \frac{SR}{2\pi V_0(\max)}$$

$$V_0(\max) = \frac{SR}{2\pi f_{3dB}} = \frac{0.8 \times 10^6}{2\pi(20 \times 10^3)}$$

$$\Rightarrow \underline{V_0(\max) = 6.37 \text{ V}}$$

E14.16

$$|V_{OS}| = \left| V_T \ln \left( \frac{I_{S2}}{I_{S1}} \right) \right| = (0.026) \ln \left( \frac{1.85 \times 10^{-14}}{2 \times 10^{-14}} \right)$$

$$\Rightarrow \underline{V_{OS} = 2.03 \text{ mV}}$$

E14.17

We need

$$i_{C1} = i_{C2}, v_{EC3} = v_{EC4} = 0.6 \text{ V, and}$$

$$v_{CE1} = v_{CE2} = 10 \text{ V}$$

By Equation (14.60(a))

$$i_{C1} = I_{S1} \left[ \exp \left( \frac{v_{BE1}}{V_T} \right) \right] \left( 1 + \frac{10}{50} \right)$$

$$= I_{S3} \left[ \exp \left( \frac{v_{EB3}}{V_T} \right) \right] \left( 1 + \frac{0.6}{50} \right)$$

By Equation (14.60(b))

$$i_{C2} = I_{S2} \left[ \exp \left( \frac{v_{BE2}}{V_T} \right) \right] \left( 1 + \frac{10}{50} \right)$$

$$= I_{S4} \left[ \exp \left( \frac{v_{EB4}}{V_T} \right) \right] \left( 1 + \frac{0.6}{50} \right)$$

$I_{S1} = I_{S2}$ , take the ratio:

$$\exp \left( \frac{v_{BE1} - v_{BE2}}{V_T} \right) = \frac{I_{S3}}{I_{S4}}$$

$$v_{BE1} - v_{BE2} = V_{OS} = V_T \ln \left( \frac{I_{S3}}{I_{S4}} \right)$$

$$= 0.026 \cdot \ln(1.05)$$

$$\Rightarrow \underline{V_{OS} = 1.27 \text{ mV}}$$

E14.18

$$V_{OS} = \frac{1}{2} \cdot \sqrt{\frac{I_Q}{2K_n}} \cdot \left( \frac{\Delta K_n}{K_n} \right)$$

$$0.020 = \frac{1}{2} \cdot \sqrt{\frac{150}{2(50)}} \cdot \left( \frac{\Delta K_n}{50} \right)$$

$$\Rightarrow \underline{\Delta K_n = 1.63 \mu A / V^2}$$

$$\Rightarrow \frac{\Delta K_n}{K_n} = \frac{1.63}{50} \Rightarrow \underline{3.26\%}$$

E14.19

Want  $\left( \frac{R_5}{R_5 + R_4} \right) V^+ = 5 \text{ mV}$

$R_5 \ll R_4$  so  $\frac{R_5}{R_4} \times V^+ = 0.005$

$$R_5 = \frac{(0.005)(100)}{10} = 0.05 \text{ k}\Omega$$

$$\Rightarrow \underline{R_5 = 50 \Omega}$$

E14.20

$$R'_1 = 25 \parallel 1 = 0.9615 \text{ k}\Omega$$

$$R'_2 = 75 \parallel 1 = 0.9868 \text{ k}\Omega$$

For  $I_Q = 100 \mu A \Rightarrow i_{C1} = i_{C2} = 50 \mu A$

From Equation (14.75)

$$(0.026) \ln \left( \frac{50 \times 10^{-6}}{10^{-14}} \right) + (0.050)(0.9615)$$

$$= (0.026) \ln \left( \frac{i_{C2}}{I_{S4}} \right) + (0.050)(0.9868)$$

$$0.58065 + 0.048075$$

$$= (0.026) \ln \left( \frac{i_{C2}}{I_{S4}} \right) + 0.04934$$

$$\ln \left( \frac{i_{C2}}{I_{S4}} \right) = 22.284$$

$$\frac{50 \times 10^{-6}}{I_{S4}} = 4.7625 \times 10^9$$

$$\underline{I_{S4} \approx 1.05 \times 10^{-14} \text{ A}}$$

E14.21

From Equation (14.79)

$$v_o = I_{B1} R_2 - I_{B2} R_3 \left( 1 + \frac{R_2}{R_1} \right)$$

For  $v_o = 0$

$$0 = (1.1 \times 10^{-6})(100 \text{ k}\Omega) - (1.0 \times 10^{-6}) R_3 \left( 1 + \frac{100}{10} \right)$$

$$R_3(11) = (1.1)(100 \text{ k}\Omega) \Rightarrow \underline{R_3 = 10 \text{ k}\Omega}$$

E14.22

a.  $v_o = I_{B1} R_3 = (10^{-6})(200 \times 10^3)$

$$\Rightarrow \underline{v_o = 0.20 \text{ V}}$$

b.  $R_4 = R_1 \parallel R_2 \parallel R_3 = 100 \parallel 50 \parallel 200$


$$\Rightarrow \underline{R_4 = 28.6 \text{ k}\Omega}$$



## Chapter 14

### Problem Solutions

14.1

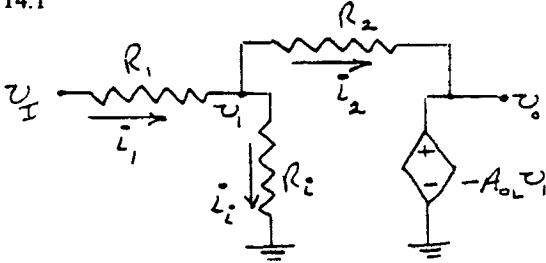

$$\frac{v_I - v_1}{R_1} = \frac{v_1 - v_o}{R_2} + \frac{v_1}{R_i} \text{ and } v_o = -A_{OL}v_1$$

so that  $v_1 = -\frac{v_o}{A_{OL}}$

$$\frac{v_I}{R_1} + \frac{v_o}{R_2} = v_1 \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_i} \right)$$

So

$$\frac{v_I}{R_1} = -v_o \left[ \frac{1}{R_2} + \frac{1}{A_{OL}} \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_i} \right) \right]$$

Then

$$\frac{v_o}{v_I} = \frac{-(1/R_1)}{\left[ \frac{1}{R_2} + \frac{1}{A_{OL}} \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_i} \right) \right]} = A_{CL}$$

From Equation (14.20) for  $R_L = \infty$  and  $R_o = 0$

$$\frac{1}{R_{if}} = \frac{1}{R_i} + \frac{1}{R_2} \cdot \frac{(1 + A_{OL})}{1}$$

a. For  $R_i = 1 \text{ k}\Omega$

$$A_{CL} = \frac{-(1/20)}{\left[ \frac{1}{100} + \frac{1}{10^3} \left( \frac{1}{20} + \frac{1}{100} + \frac{1}{1} \right) \right]} = \frac{-0.05}{[0.01 + 1.06 \times 10^{-3}]}$$

or

$$\Rightarrow A_{CL} = -4.52$$

$$\frac{1}{R_{if}} = \frac{1}{1} + \frac{1 + 10^3}{100} \Rightarrow R_{if} = 90.8 \Omega$$

b. For  $R_i = 10 \text{ k}\Omega$

$$A_{CL} = \frac{-(1/20)}{\left[ \frac{1}{100} + \frac{1}{10^3} \left( \frac{1}{20} + \frac{1}{100} + \frac{1}{10} \right) \right]} = \frac{-0.05}{[0.01 + 1.6 \times 10^{-4}]}$$

or

$$\Rightarrow A_{CL} = -4.92$$

$$\frac{1}{R_{if}} = \frac{1}{10} + \frac{1 + 10^3}{100} \Rightarrow R_{if} = 98.9 \Omega$$

c. For  $R_i = 100 \text{ k}\Omega$


$$A_{CL} = \frac{-(1/20)}{\left[ \frac{1}{100} + \frac{1}{10^3} \left( \frac{1}{20} + \frac{1}{100} + \frac{1}{100} \right) \right]} = \frac{-0.05}{[0.01 + 7 \times 10^{-5}]}$$

or

$$\Rightarrow A_{CL} = -4.965$$

$$\frac{1}{R_{if}} = \frac{1}{100} + \frac{1 + 10^3}{100} \Rightarrow R_{if} = 99.8 \Omega$$

14.2

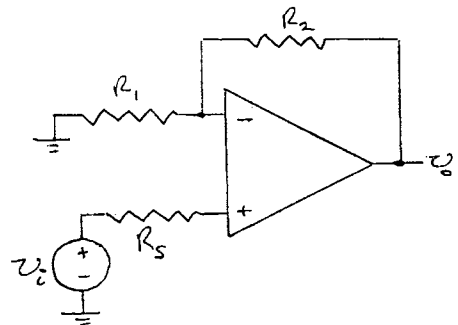

$$A_{CL} = \frac{v_o}{v_i} = \frac{\left( 1 + \frac{R_2}{R_1} \right)}{\left[ 1 + \frac{1}{A_{OL}} \left( 1 + \frac{R_2}{R_1} \right) \right]}$$

For the ideal:

$$\left( 1 + \frac{R_2}{R_1} \right) = \frac{0.10}{0.002} = 50$$

$$v_o(\text{actual}) = (0.10)(1 - 0.001) = 0.0999$$

So

$$\frac{0.0999}{0.002} = \frac{50}{1 + \frac{1}{A_{OL}}(50)} = 49.95$$

which yields

$$A_{OL} = 1000$$

14.3

$$A_{v1} = \frac{v_{o1}}{v_i} = \frac{-\left( \frac{A_{OL} - 1}{R_o - R_2} \right)}{\left( \frac{1}{R_L} + \frac{1}{R_o} + \frac{1}{R_2} \right)}$$

Or

$$v_{o1} = \frac{-\left(\frac{5 \times 10^3}{1} - \frac{1}{100}\right)}{\left(\frac{1}{10} + \frac{1}{1} + \frac{1}{100}\right)} \cdot v_i = \frac{-(4.99999 \times 10^3)}{1.11} \cdot v_i$$

$$v_{o1} = -4.504495 \times 10^3 \cdot v_i$$

Now

$$\frac{i_i}{v_i} = \frac{v_i - v_1}{R_1 v_1} \equiv K$$

Then

$$v_i - v_1 = KR_1 v_1$$

which yields

$$v_i = \frac{v_1}{KR_1 + 1}$$

Now

$$K = \frac{1}{10} + \frac{1}{100} \left[ \frac{1 + 5 \times 10^3 + \frac{1}{10}}{1 + \frac{1}{10} + \frac{1}{100}} \right]$$

$$= (0.1) + (0.01) \left[ \frac{5.001 \times 10^3}{1.11} \right] = 45.15495$$

Then

$$v_1 = \frac{v_i}{(45.15495)(10) + 1} = \frac{v_i}{452.5495}$$

We find

$$v_{o1} = -4.504495 \times 10^3 \left[ \frac{v_i}{452.5495} \right]$$

Or

$$A_{v_{o1}} = \frac{v_{o1}}{v_i} = -9.9536$$

For the second stage,  $R_L = \infty$

$$v_{o2} = \frac{-\left(\frac{5 \times 10^3}{1} - \frac{1}{100}\right)}{\left(\frac{1}{1} + \frac{1}{100}\right)} \cdot v_1' = -4.950485 \times 10^3 \cdot v_1'$$

$$K \equiv \frac{1}{10} + \frac{1}{100} \left[ \frac{1 + 5 \times 10^3}{1 + \frac{1}{100}} \right] = 49.61485$$

$$v_1' = \frac{v_{o1}}{KR_1 + 1} = \frac{v_{o1}}{(49.61485)(10) + 1} = \frac{v_{o1}}{497.1485}$$

Then


$$\frac{v_{o2}}{v_{o1}} = \frac{-4.950485 \times 10^3}{497.1485} = -9.95776$$

So

$$A_{v_{o2}} = \frac{v_{o2}}{v_{o1}} = (-9.9536)(-9.95776) \Rightarrow$$

$$A_{v_{o2}} = 99.12$$

14.4

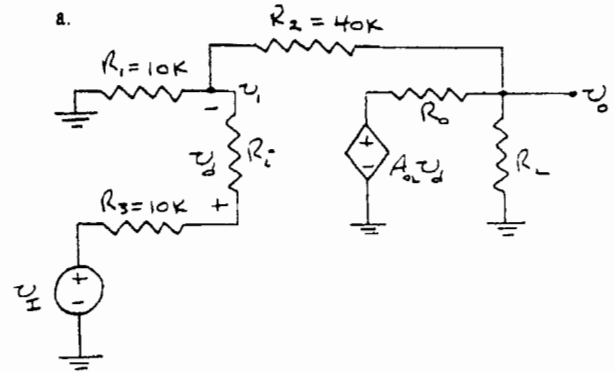

$$\frac{v_1 - v_I}{R_3 + R_1} + \frac{v_1}{R_1} + \frac{v_1 - v_0}{R_2} = 0 \tag{1}$$

$$v_1 \left[ \frac{1}{R_3 + R_1} + \frac{1}{R_1} + \frac{1}{R_2} \right] = \frac{v_0}{R_2} + \frac{v_I}{R_3 + R_1}$$

$$\frac{v_0}{R_L} + \frac{v_0 - A_{oL} v_d}{R_0} + \frac{v_0 - v_1}{R_2} = 0 \tag{2}$$

or

$$v_0 \left[ \frac{1}{R_L} + \frac{1}{R_0} + \frac{1}{R_2} \right] = \frac{v_1}{R_2} + \frac{A_{oL} v_d}{R_0}$$

$$v_d = \left( \frac{v_I - v_1}{R_3 + R_1} \right) \cdot R_1 \tag{3}$$

So substituting numbers:

$$v_1 \left[ \frac{1}{10 + 20} + \frac{1}{10} + \frac{1}{40} \right] = \frac{v_0}{40} + \frac{v_I}{10 + 20} \tag{1}$$

or

$$v_1 [0.15833] = v_0 [0.025] + v_I [0.03333]$$

$$v_0 \left[ \frac{1}{1} + \frac{1}{0.5} + \frac{1}{40} \right] = \frac{v_1}{40} + \frac{(10^4) v_d}{0.5} \tag{2}$$

or

$$v_0 [3.025] = v_1 [0.025] + (2 \times 10^4) v_d$$

$$v_d = \left( \frac{v_I - v_1}{10 + 20} \right) \cdot 20 = 0.6667(v_I - v_1) \tag{3}$$

So

$$v_0 [3.025] = v_1 [0.025] + (2 \times 10^4) (0.6667)(v_I - v_1)$$

$$\text{or} \tag{2}$$

$$v_0 [3.025] = 1.333 \times 10^4 v_I - 1.333 \times 10^4 v_1$$

From (1):

$$v_1 = v_0(0.1579) + v_I(0.2105)$$

Then

$$v_0[3.025] = 1.333 \times 10^4 v_I - 1.333 \times 10^4 [v_0(0.1579) + v_I(0.2105)]$$

$$v_0[2.1078 \times 10^3] = v_I[1.0524 \times 10^4]$$

or

$$A_{CL} = \frac{v_0}{v_I} = 4.993$$

To find  $R_{if}$ : Use Equation (14.27)

$$i_I \left( 1 + \frac{0.5}{1} + \frac{0.5}{40} \right) = v_1 \left\{ \left( \frac{1}{10} + \frac{1}{40} \right) \left( 1 + \frac{0.5}{1} + \frac{0.5}{40} \right) - \frac{0.5}{(40)^2} \right\} - \frac{(10^3)v_d}{40}$$

$$i_I(1.5125) = v_1\{(0.125)(1.5125) - 0.0003125\} - 25v_d$$

or

$$i_I(1.5125) = v_I\{0.18875\} - 25v_d$$

Now

$$v_d = i_I R_i = i_I(20) \text{ and } v_1 = v_I - i_I(20)$$

So

$$i_I(1.5125) = [v_I - i_I(20)] \cdot [0.18875] - 25i_I(20)$$

$$i_I[505.3] = v_I(0.18875)$$

or

$$\frac{v_I}{i_I} = 2677 \text{ k}\Omega$$

$$\text{Now } R_{if} = 10 + 2677 \Rightarrow R_{if} = 2.687 \text{ M}\Omega$$

To determine  $R_{of}$ : Using Equation (14.36)

$$\frac{1}{R'_{of}} = \frac{1}{R_o} \cdot \left[ \frac{A_{oL}}{1 + \frac{R_2}{R_i \parallel R_i}} \right] = \frac{1}{0.5} \cdot \left[ \frac{10^3}{1 + \frac{40}{10 \parallel 20}} \right]$$

$$\text{or } R'_{of} = 3.5 \Omega$$

$$\text{Then } R_{of} = 1 \text{ k}\Omega \parallel 3.5 \Omega$$


$$\Rightarrow R_{of} = 3.49 \Omega$$

b. Using Equation (14.16)

$$\frac{dA_{CL}}{A_{CL}} = (-10) \left( \frac{5}{10^3} \right) \Rightarrow \frac{dA_{CL}}{A_{CL}} = -(0.05)\%$$

14.5

a.

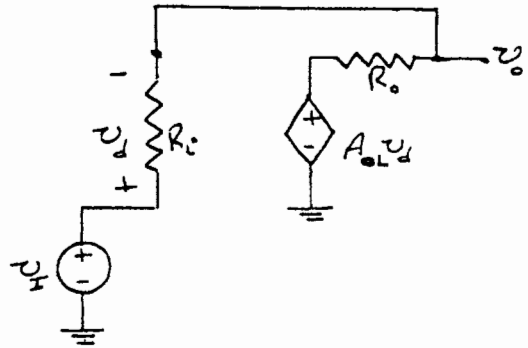

$$\frac{v_0 - A_{oL}v_d}{R_o} + \frac{v_0 - v_I}{R_i} = 0 \text{ and } v_d = v_I - v_0$$

So

$$\frac{v_0}{R_o} - \frac{A_{oL}}{R_o} \cdot (v_I - v_0) + \frac{v_0}{R_i} - \frac{v_I}{R_i} = 0$$

$$v_0 \left[ \frac{1}{R_o} + \frac{A_{oL}}{R_o} + \frac{1}{R_i} \right] = v_I \left[ \frac{1}{R_i} + \frac{A_{oL}}{R_o} \right]$$

$$v_0 \left[ \frac{1}{0.2} + \frac{(10^4)}{0.2} + \frac{1}{100} \right] = v_I \left[ \frac{1}{100} + \frac{(10^4)}{0.2} \right]$$

$$v_0 [5.000501 \times 10^4] = v_I [5.000001 \times 10^4]$$

$$\text{So } A_{CL} = \frac{v_0}{v_I} = 0.9999$$

b. Set  $v_I = 0$

$$i_o = \frac{v_0 - A_{oL}v_d}{R_o} + \frac{v_0}{R_i} \text{ and } v_d = -v_0$$

$$i_o = v_0 \left[ \frac{1}{R_o} + \frac{A_{oL}}{R_o} + \frac{1}{R_i} \right]$$

Then

$$\frac{1}{R_{of}} = \frac{1}{R_o} + \frac{A_{oL}}{R_o} + \frac{1}{R_i}$$


or

$$\frac{1}{R_{of}} = \frac{1}{0.2} + \frac{(10^4)}{0.2} + \frac{1}{100}$$

which yields

$$R_{of} \approx 0.02 \Omega$$

14.6

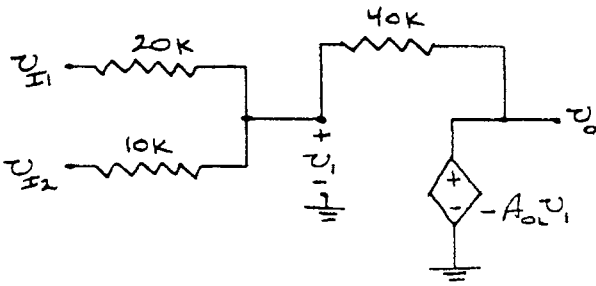

$$\frac{v_{I1} - v_1}{20} + \frac{v_{I2} - v_1}{10} = \frac{v_1 - v_0}{40}$$

$$\frac{v_{I1}}{20} + \frac{v_{I2}}{10} + \frac{v_0}{40} = v_1 \left[ \frac{1}{20} + \frac{1}{10} + \frac{1}{40} \right]$$

and  $v_0 = -A_{OL}v_1$  so that  $v_1 = -\frac{v_0}{A_{OL}}$

Then


$$v_{I1}(0.05) + v_{I2}(0.10) = -v_0 \left\{ \frac{1}{40} + \frac{1}{2 \times 10^3} \cdot \left( \frac{7}{40} \right) \right\}$$

$$= -v_0 [2.50875 \times 10^{-2}]$$

$$\Rightarrow v_0 = -1.993v_{I1} - 3.986v_{I2}$$

$$\frac{\Delta v_0}{v_0} = \frac{2 - 1.993}{2} \Rightarrow \frac{\Delta v_0}{v_0} = 0.35\%$$

14.7

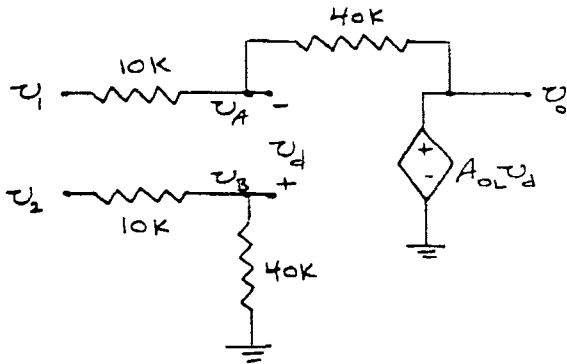

$$v_B = \left( \frac{40}{40 + 10} \right) v_2 = \left( \frac{4}{5} \right) v_2 = 0.8v_2 \tag{1}$$

$$\frac{v_1 - v_A}{10} = \frac{v_A - v_0}{40}$$

$$\frac{v_1}{10} + \frac{v_0}{40} = v_A \left( \frac{1}{10} + \frac{1}{40} \right)$$

$$v_1(0.1) + v_0(0.025) = v_A(0.125) \tag{2}$$

$$v_0 = A_{OL}v_d = A_{OL}(v_B - v_A) \tag{3}$$

or

$$v_0 = A_{OL}[0.8v_2 - v_A]$$

$$\frac{v_0}{A_{OL}} - 0.8v_2 = -v_A$$

$$\Rightarrow v_A = 0.8v_2 - \frac{v_0}{A_{OL}}$$

Then

$$v_1(0.1) + v_0(0.025) = (0.125) \left[ 0.8v_2 - \frac{v_0}{A_{OL}} \right]$$

$$v_1(0.1) - v_2(0.1) = -v_0 \left[ 0.025 + \frac{0.125}{10^3} \right]$$

$$= -v_0 [2.5125 \times 10^{-2}]$$

$$\Rightarrow A_d = \frac{v_0}{v_2 - v_1} = 3.9801$$

$$\Rightarrow \frac{\Delta A_d}{A_d} = \frac{0.0199}{4} \Rightarrow 0.4975\%$$

14.8

a. Considering the second op-amp and Equation (14.20), we have

$$\frac{1}{R_{f2}} = \frac{1}{10} + \frac{1}{0.1} \cdot \left[ \frac{1 + 100}{1 + \frac{1}{0.1}} \right] = 0.10 + \frac{101}{(0.1)(11)}$$

So  $R_{f2} = 0.0109 \text{ k}\Omega$

The effective load on the first op-amp is then

$$R_{L1} = 0.1 + R_{f2} = 0.1109 \text{ k}\Omega$$

Again using Equation (14.20), we have

$$\frac{1}{R_{if}} = \frac{1}{10} + \frac{1}{1} \cdot \frac{1 + 100 + \frac{1}{0.1109}}{1 + \frac{1}{0.1109} + \frac{1}{1}} = 0.10 + \frac{110.017}{11.017}$$

so that

$$R_{if} = 99.1 \Omega$$

b. To determine  $R_{of}$ :

For the first op-amp, we can write, using Equation (14.36)

$$\frac{1}{R_{of1}} = \frac{1}{R_o} \cdot \left[ \frac{A_{OL}}{1 + \frac{R_2}{R_1 || R_i}} \right] = \frac{1}{1} \cdot \left[ \frac{100}{1 + \frac{40}{1 || 10}} \right]$$

which yields  $R_{of1} = 0.021 \text{ k}\Omega$


For the second op-amp, then

$$\frac{1}{R_{of}} = \frac{1}{R_o} \cdot \left[ \frac{A_{oL}}{1 + \frac{R_2}{(R_1 + R_{of1}) \parallel R_i}} \right]$$

$$= \frac{1}{1} \cdot \left[ \frac{100}{1 + \frac{0.10}{(0.121) \parallel 10}} \right]$$

or  $R_{of} = 18.4 \Omega$

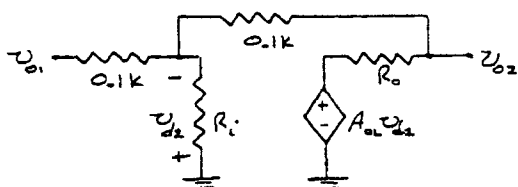c. To find the gain, consider the second op-amp.



$$\frac{v_{o1} - (-v_{d2})}{0.1} + \frac{v_{d2}}{R_i} = \frac{-v_{d2} - v_{o2}}{0.1} \quad (1)$$

$$\frac{v_{o1}}{0.1} + v_{d2} \left( \frac{1}{0.1} + \frac{1}{10} + \frac{1}{0.1} \right) = -\frac{v_{o2}}{0.1}$$

or

$$v_{o1}(10) + v_{d2}(20.1) = -v_{o2}(10)$$

$$\frac{v_{o2} - A_{oL}v_{d2}}{R_o} + \frac{v_{o2} - (-v_{d2})}{0.1} = 0 \quad (2)$$

$$\frac{v_{o2}}{1} - v_{d2} \left( \frac{100}{1} - \frac{1}{0.1} \right) + \frac{v_{o2}}{0.1} = 0$$

$$v_{o2}(11) - v_{d2}(90) = 0$$

or

$$v_{d2} = v_{o2}(0.1222)$$


Then Equation (1) becomes

$$v_{o1}(10) + v_{o2}(0.1222)(20.1) = -v_{o2}(10)$$

or

$$v_{o1} = -v_{o2}(1.246)$$

Now consider the first op-amp.

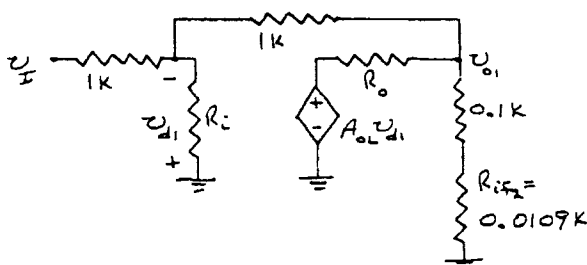

$$\frac{v_I - (-v_{d1})}{1} + \frac{v_{d1}}{R_i} = \frac{-v_{d1} - v_{o1}}{1} \quad (1)$$

$$v_I(1) + v_{d1} \left( \frac{1}{1} + \frac{1}{10} + \frac{1}{1} \right) = -v_{o1}(1)$$

or

$$v_I(1) + v_{d1}(2.1) = -v_{o1}(1)$$

$$\frac{v_{o1}}{0.1109} + \frac{v_{o1} - A_{oL}v_{d1}}{R_o} + \frac{v_{o1} - (-v_{d1})}{1} = 0 \quad (2)$$

$$v_{o1} \left( \frac{1}{0.1109} + \frac{1}{1} + \frac{1}{1} \right) - v_{d1} \left( \frac{100}{1} - \frac{1}{1} \right) = 0$$

$$v_{o1}(11.017) - v_{d1}(99) = 0$$

or

$$v_{d1} = v_{o1}(0.1113)$$

Then Equation (1) becomes

$$v_I(1) + v_{o1}(0.1113)(2.1) = -v_{o1}$$

$$\text{or } v_I = -v_{o1}(1.234)$$

$$\text{We had } v_{o1} = -v_{o2}(1.246)$$

$$\text{So } v_I = v_{o2}(1.246)(1.234)$$

$$\text{or } \frac{v_{o2}}{v_I} = 0.650$$

d. Ideal  $\frac{v_{o2}}{v_I} = 1$

So ratio of actual to ideal = 0.650.

14.9

The open loop gain can be written as

$$A_{oL}(f) = \frac{A_0}{\left(1 + j \cdot \frac{f}{f_{PD}}\right) \left(1 + j \cdot \frac{f}{5 \times 10^6}\right)}$$

where  $A_0 = 2 \times 10^5$ .

The closed-loop response is

$$A_{CL} = \frac{A_{oL}}{1 + \beta A_{oL}}$$

At low frequency,

$$100 = \frac{2 \times 10^5}{1 + \beta(2 \times 10^5)}$$

So that  $\beta = 9.995 \times 10^{-3}$ .

Assuming the second pole is the same for both the open-loop and closed-loop, then

$$\phi = -\tan^{-1}\left(\frac{f}{f_{PD}}\right) - \tan^{-1}\left(\frac{f}{5 \times 10^6}\right)$$

For a phase margin of  $80^\circ$ ,  $\phi = -100^\circ$ .

So

$$-100 = -90 - \tan^{-1}\left(\frac{f}{5 \times 10^6}\right)$$

or

$$f = 8.816 \times 10^5 \text{ Hz}$$

Then

$$|A_{oL}| = 1 = \frac{2 \times 10^5}{\sqrt{1 + \left(\frac{8.816 \times 10^5}{f_{PD}}\right)^2} \sqrt{1 + \left(\frac{8.816 \times 10^5}{5 \times 10^6}\right)^2}}$$

or

$$\frac{8.816 \times 10^5}{f_{PD}} \approx 1.9696 \times 10^5$$

or

$$f_{PD} = 4.48 \text{ Hz}$$

14.10

(a) 1<sup>st</sup> stage

$$(10)f_{3-dB} = 1 \text{ MHz} \Rightarrow f_{3-dB} = 100 \text{ kHz}$$

2<sup>nd</sup> stage

$$(50)f_{3-dB} = 1 \text{ MHz} \Rightarrow f_{3-dB} = 20 \text{ kHz}$$

Bandwidth of overall system  $\approx 20 \text{ kHz}$


(b) If each stage has the same gain, so

$$K^2 = 500 \Rightarrow K = 22.36$$

Then bandwidth of each stage

$$(22.36)f_{3-dB} = 1 \text{ MHz} \Rightarrow f_{3-dB} = 44.7 \text{ kHz}$$

14.11

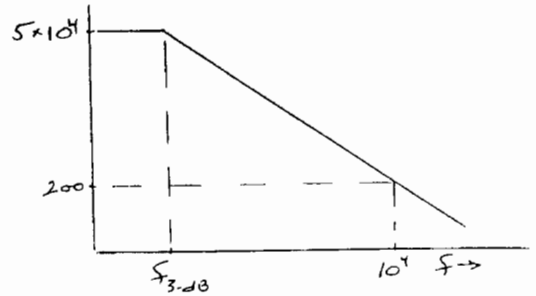

$$A = \frac{A_0}{1 + j \frac{f}{f_{3-dB}}}$$

$$|A| = \frac{A_0}{\sqrt{1 + \left(\frac{f}{f_{3-dB}}\right)^2}} \Rightarrow$$

$$200 = \frac{5 \times 10^4}{\sqrt{1 + \left(\frac{10^4}{f_{3-dB}}\right)^2}} \Rightarrow f_{3-dB} = 40 \text{ Hz}$$

Then

$$f_T = (5 \times 10^4)(40) \Rightarrow f_T = 2 \text{ MHz}$$

14.12

$$(5 \times 10^4)f_{PD} = 10^6 \Rightarrow f_{PD} = 20 \text{ Hz}$$

$$(25)f_{3-dB} 10^6 = f_{3-dB} = 40 \text{ kHz}$$

$$A_v = \frac{A_{vo}}{1 + j \frac{f}{f_{3-dB}}} \Rightarrow |A_v| = \frac{25}{\sqrt{1 + \left(\frac{f}{40 \times 10^3}\right)^2}}$$

At  $f = 0.5f_{3-dB} = 20 \text{ kHz}$

$$|A_v| = \frac{25}{\sqrt{1 + (0.5)^2}} = 22.36$$

At  $f = 2f_{3-dB} = 80 \text{ kHz}$

$$|A_v| = \frac{25}{\sqrt{1 + (2)^2}} = 11.18$$

14.13

$$(20 \times 10^3) \cdot |A_v|_{max} = 10^6 \Rightarrow |A_v|_{max} = 50$$

14.14

From Equation (14.55),

$$FPBW = \frac{SR}{2\pi V_{P0}} = \frac{10 \times 10^6}{2\pi(10)}$$

or

$$FPBW = f_{max} = 159 \text{ kHz}$$

14.15


a. Using Equation (14.55),

$$V_{P0} = \frac{8 \times 10^6}{2\pi(250 \times 10^3)}$$

or

$$\underline{V_{P0} = 5.09 \text{ V}}$$

b.

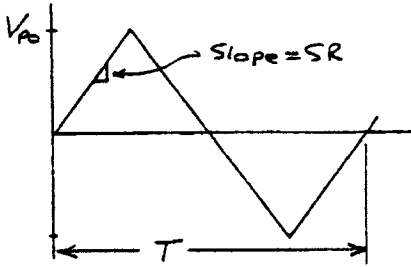

$$\text{Period } T = \frac{1}{f} = \frac{1}{250 \times 10^3} = 4 \times 10^{-6} \text{ s}$$

$$\text{One-fourth period} = 1 \mu\text{s}$$

$$\text{Slope} = \frac{V_{P0}}{1 \mu\text{s}} = SR = 8 \text{ V}/\mu\text{s}$$


$$\Rightarrow \underline{V_{P0} = 8 \text{ V}}$$

14.16


For input (a), maximum output is 5 V.

$$SR = 1 \text{ V}/\mu\text{s}$$


so

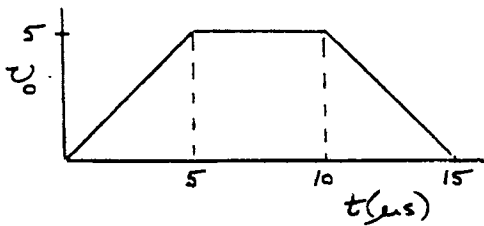

For input (b), maximum output is 2 V.

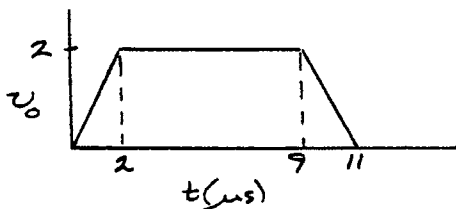


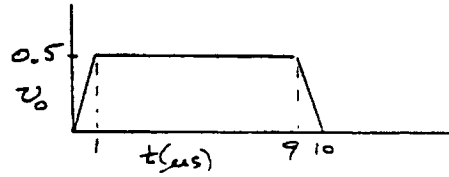For input (c), maximum output is 0.5 V so the output is




14.17


For input (a),  $\max |v_{o1}| = 3 \text{ V}$ .

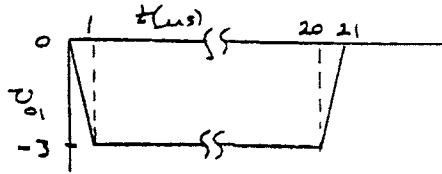


$$\text{Then } |v_{o2}|_{\max} = 3(3) = 9 \text{ V}$$

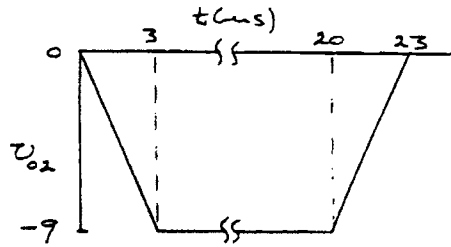

For input (b),  $\max |v_{o1}| = 1.5 \text{ V}$ .

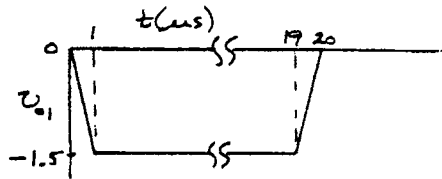

$$\text{Then } |v_{o2}|_{\max} = 3(1.5) = 4.5 \text{ V}$$

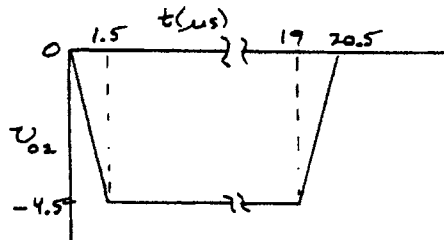

14.18

$$f_{max} = 20 \text{ kHz}, \quad SR = 0.8 \text{ V} / \mu\text{s}$$

$$V_{po} = \frac{SR}{2\pi f_{max}} = \frac{0.8 \times 10^6}{2\pi(20 \times 10^3)} \Rightarrow$$

$$V_{po} = 6.37 \text{ V}$$

14.19

$$I_1 = I_{S1} \exp\left(\frac{V_{BE1}}{V_T}\right), \quad I_2 = I_{S2} \exp\left(\frac{V_{BE2}}{V_T}\right)$$

Want  $I_1 = I_2$ , so

$$\frac{I_1}{I_2} = 1 = \frac{5 \times 10^{-14}(1+x) \exp\left(\frac{V_{BE1}}{V_T}\right)}{5 \times 10^{-14}(1-x) \exp\left(\frac{V_{BE2}}{V_T}\right)}$$

$$= \frac{(1+x)}{(1-x)} \exp\left(\frac{V_{BE1} - V_{BE2}}{V_T}\right)$$

Or

$$\frac{1+x}{1-x} = \exp\left(\frac{V_{BE2} - V_{BE1}}{V_T}\right) = \exp\left(\frac{V_{OS}}{V_T}\right)$$

$$= \exp\left(\frac{0.0025}{0.026}\right) = 1.10$$

Now

$$1+x = (1-x)(1.10) \Rightarrow$$

$$x = 0.0476 \Rightarrow 4.76\%$$

14.20

From Equation (14.62),

$$\left(\frac{1 + \frac{V_{CE1}}{V_{AN}}}{1 + \frac{V_{EB}}{V_{AP}}}\right) = \frac{I_{S3}}{I_{S4}} \cdot \left(\frac{1 + \frac{V_{CE2}}{V_{AN}}}{1 + \frac{V_{EC4}}{V_{AP}}}\right)$$

For  $V_{CE2} = 0.6 \text{ V}$ , then  $V_{EC4} = 5 \text{ V}$ . We have  $V_{CE1} = 5 \text{ V}$  so

$$\left(\frac{1 + \frac{5}{80}}{1 + \frac{0.6}{80}}\right) = \frac{I_{S3}}{I_{S4}} \cdot \left(\frac{1 + \frac{0.6}{80}}{1 + \frac{5}{80}}\right)$$

or

$$\frac{I_{S3}}{I_{S4}} = \frac{(1.0625)^2}{(1.0075)^2} = 1.112$$


So

$$I_{S3} = (10^{-14})(1.112)$$

or

$$I_{S3} = 1.112 \times 10^{-14} \text{ A}$$

14.21

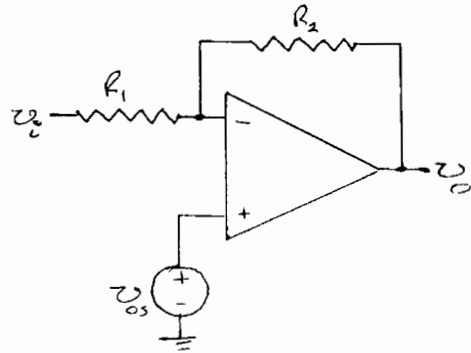

By superposition:

$$v_o(v_i) = -\frac{R_2}{R_1} \cdot v_i = -50v_i$$

$$v_o(v_{os}) = \left(1 + \frac{R_2}{R_1}\right) \cdot v_{os} = 51v_{os}$$

So

$$v_o = v_o(v_i) + v_o(v_{os}) = -50v_i + 51v_{os}$$

For  $v_i = 20 \text{ mV}$  and  $v_{os} = +2.5 \text{ mV}$

$$v_o = -50(0.02) + 51(0.0025) = -0.8725 \text{ V}$$


For  $v_i = 20 \text{ mV}$  and  $v_{os} = -2.5 \text{ mV}$

$$v_o = -50(0.02) + 51(-0.0025) = -1.1275 \text{ V}$$

So

$$-1.1275 \leq v_o \leq -0.8725 \text{ V}$$

14.22

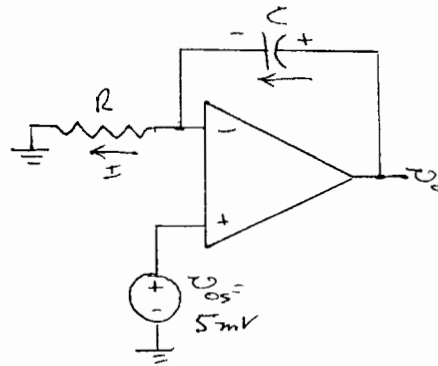

$$I = \frac{0.5 \times 10^{-3}}{10^4} = 5 \times 10^{-8} \text{ A}$$

Also

$$I = C \frac{dv_o}{dt} \Rightarrow v_o = \frac{1}{C} \int I dt = \frac{I}{C} \cdot t$$

Then

$$5 = \frac{5 \times 10^{-8}}{10 \times 10^{-6}} t \Rightarrow t = 10^3 \text{ s}$$

14.23

a.

$$|\nu_{01}| = 10 \left( 1 + \frac{100}{10} \right) \text{ or } \underline{|\nu_{01}| = 110 \text{ mV}}$$

Then

$$|\nu_{02}| = |\nu_{01}|(5) + 10 \left( 1 + \frac{50}{10} \right) = (110)(5) + (10)(6)$$

or

$$\underline{|\nu_{02}| = 610 \text{ mV}}$$

14.24

$\nu_0$  due to  $\nu_I$

$$\nu_0 = (0.5) \left( 1 + \frac{1}{1.1} \right) = 0.9545 \text{ V}$$

Wiper arm at  $V^+ = 10 \text{ V}$ , (using superposition)

$$\nu_1 = \left( \frac{R_1 \parallel R_5}{R_1 \parallel R_5 + R_4} \right) (10) = \left( \frac{0.0909}{0.0909 + 10} \right) (10) = 0.090$$

$$\text{Then } \nu_{01} = - \left( \frac{1}{1} \right) (0.090) = -0.090$$

Wiper arm in center,  $\nu_1 = 0$  and  $\nu_{02} = 0$

Wiper arm at  $V^- = -10 \text{ V}$ ,  $\nu_1 = -0.090$

So

$$\nu_{03} = 0.090$$

Finally, total output  $\nu_0$ : (from superposition)

Wiper arm at  $V^+$ ,

$$\underline{\nu_0 = 0.8645 \text{ V}}$$

Wiper arm in center,

$$\underline{\nu_0 = 0.9545 \text{ V}}$$

Wiper arm at  $V^-$ ,

$$\underline{\nu_0 = 1.0445 \text{ V}}$$

14.25

a.  $R'_1 = R'_2 = 0.5 \parallel 25 = 0.490 \text{ k}\Omega$

or

$$\underline{R'_1 = R'_2 = 490 \Omega}$$

b. From Equation (14.75),

$$(0.026) \ln \left( \frac{125 \times 10^{-6}}{2 \times 10^{-14}} \right) + (0.125) R'_1 \\ = (0.026) \ln \left( \frac{125 \times 10^{-6}}{2.2 \times 10^{-14}} \right) + (0.125) R'_2$$

$$0.586452 + (0.125) R'_1 = 0.583974 + (0.125) R'_2$$

$$0.002478 = (0.125)(R'_2 - R'_1)$$

$$\text{So } R'_2 - R'_1 = 0.0198 \text{ k}\Omega \Rightarrow 19.8 \Omega$$

Then

$$\frac{R_2(1-x)R_x}{R_2 + (1-x)R_x} - \frac{R_1 x R_x}{R_1 + x R_x} = 0.0198$$

$$\frac{(0.5)(1-x)(50)}{(0.5) + (1-x)(50)} - \frac{(0.5)(50)x}{(0.5) + x(50)} = 0.0198$$

$$\frac{25(1-x)}{50.5 - 50x} - \frac{25x}{0.5 + 50x} = 0.0198$$

$$\frac{(0.5 + 50x)(25 - 25x) - (25x)(50.5 - 50x)}{(50.5 - 50x)(0.5 + 50x)} = 0.0198$$

$$25\{0.5 - 0.5x + 50x - 50x^2 - 50.5x + 50x^2\} \\ = 0.0198\{25.25 + 2525x - 25x - 2500x^2\}$$

$$25\{0.5 - x\} = 0.0198\{25.25 + 2500x - 2500x^2\}$$

$$0.5 - x = 0.019998 + 1.98x - 1.98x^2$$

$$1.98x^2 - 2.98x + 0.48 = 0$$

$$x = \frac{2.98 \pm \sqrt{(2.98)^2 - 4(1.98)(0.48)}}{2(1.98)}$$

So

$$\underline{x = 0.183}$$

and

$$\underline{1 - x = 0.817}$$

14.26

$$R'_1 = R_1 \parallel 15 = 0.5 \parallel 15 = 0.4839 \text{ k}\Omega$$

$$R'_2 = R_2 \parallel 35 = 0.5 \parallel 35 = 0.4930 \text{ k}\Omega$$

From Equation (14.75),

$$(0.026) \ln \left( \frac{i_{C1}}{I_{S3}} \right) + i_{C1} R'_1 = (0.026) \ln \left( \frac{i_{C2}}{I_{S4}} \right) + i_{C2} R'_2$$

$$(0.026) \ln \left( \frac{i_{C1}}{i_{C2}} \right) = i_{C2} R'_2 - i_{C1} R'_1$$

$$(0.026) \ln \left( \frac{i_{C1}}{i_{C2}} \right) = i_{C2} R'_2 \left[ 1 - \frac{i_{C1}}{i_{C2}} \cdot \frac{R'_1}{R'_2} \right]$$

$$(0.026) \ln \left( \frac{i_{C1}}{i_{C2}} \right) = i_{C2} (0.4930) \left[ 1 - (0.9815) \left( \frac{i_{C1}}{i_{C2}} \right) \right]$$

By trial and error:


$$i_{C1} = 252 \mu\text{A} \text{ and } i_{C2} = 248 \mu\text{A}$$

or

$$\frac{i_{C1}}{i_{C2}} = 1.0155$$

14.27

a.

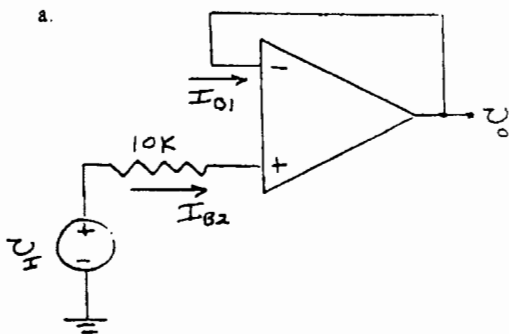


For  $I_{B2} = 1 \mu\text{A}$ , then  $v_o = -(10^{-6})(10^4)$

or

$$v_o = -0.010 \text{ V}$$

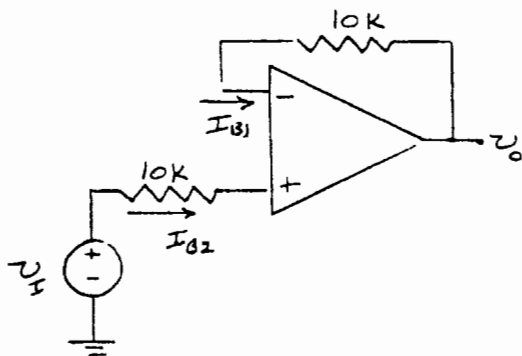b. If a  $10 \text{ k}\Omega$  resistor is included in the feedback loop



Now  $v_o = -I_{B2}(10) + I_{B1}(10) = 0$

Circuit is compensated if  $I_{B1} = I_{B2}$ .

14.28

From Equation (14.83), we have

$$v_o = R_2 I_{OS}$$

where  $R_2 = 40 \text{ k}\Omega$  and  $I_{OS} = 3 \mu\text{A}$ .

Then

$$v_o = (40 \times 10^3)(3 \times 10^{-6})$$

or

$$v_o = 0.12 \text{ V}$$

14.29

a. Assume all bias currents are in the same direction and into each op-amp.

$$v_{o1} = I_{B1}(100 \text{ k}\Omega) = (10^{-6})(10^5) \Rightarrow v_{o1} = 0.1 \text{ V}$$

Then

$$\begin{aligned} v_{o2} &= v_{o1}(-5) + I_{B1}(50 \text{ k}\Omega) \\ &= (0.1)(-5) + (10^{-6})(5 \times 10^4) \\ &= -0.5 + 0.05 \end{aligned}$$

or

$$v_{o2} = -0.45 \text{ V}$$

b. Connect  $R_3 = 10 \parallel 100 = 9.09 \text{ k}\Omega$  resistor to noninverting terminal of first op-amp, and  $R_3 = 10 \parallel 50 = 8.33 \text{ k}\Omega$  resistor to noninverting terminal of second op-amp.

14.30

a. For a constant current through a capacitor,

$$v_o = \frac{1}{C} \int_0^t I dt$$

or  $v_o = \frac{0.1 \times 10^{-6}}{10^{-6}} \cdot t \Rightarrow v_o = (0.1)t$

b. At  $t = 10 \text{ s}$ ,  $v_o = 1 \text{ V}$

c. Then

$$v_o = \frac{100 \times 10^{-12}}{10^{-6}} \cdot t \Rightarrow v_o = (10^{-4})t$$

At  $t = 10 \text{ s}$ ,  $v_o = 1 \text{ mV}$

14.31

a. Assume all bias currents are into the op-amp.

$$v_{o1} = I_{B1}(50 \text{ k}\Omega) = (10 \times 10^{-6})(50 \times 10^3)$$

or

$$v_{o1} = v_{o2} = 0.5 \text{ V}$$

$$v_{o3} = (-1)(v_{o1}) + (10 \times 10^{-6})(20 \times 10^3)$$

or

$$v_{o3} = -0.3 \text{ V}$$

b.  $R_A = 10 \parallel 50 \Rightarrow R_A = 8.33 \text{ k}\Omega$

$$R_B = 20 \parallel 20 \Rightarrow R_B = 10 \text{ k}\Omega$$

- c. Assume the worst case offset current, that is,  $I_{OS} = I_{B1} - I_{B2}$  or  $I_{OS} = I_{B2} - I_{B1}$ .  
From Equation (14.83),

$$\nu_{01} = R_2 I_{OS} = (50 \times 10^3)(2 \times 10^{-6})$$

or

$$\underline{\nu_{01} = \nu_{02} = 0.1 \text{ V}}$$

$$\begin{aligned} \nu_{03} &= (-1)\nu_{01} - I_{OS}R_2 \\ &= (-1)(0.1) - (2 \times 10^{-6})(20 \times 10^3) \end{aligned}$$

or

$$\underline{\nu_{03} = -0.14 \text{ V}}$$

14.32

- a. Using Equation (14.79),

Circuit (a),

$$\begin{aligned} \nu_0 &= (0.8 \times 10^{-6})(50 \times 10^3) \\ &\quad - (0.8 \times 10^{-6})(25 \times 10^3) \left(1 + \frac{50}{50}\right) \end{aligned}$$

or

$$\underline{\nu_0 = 0}$$

Circuit (b),

$$\begin{aligned} \nu_0 &= (0.8 \times 10^{-6})(50 \times 10^3) \\ &\quad - (0.8 \times 10^{-6})(10^3) \left(1 + \frac{50}{50}\right) \\ &= 4 \times 10^{-2} - 1.6 \end{aligned}$$

or

$$\underline{\nu_0 = -1.56 \text{ V}}$$

- b. Assume  $I_{B1} = 0.7 \mu\text{A}$  and  $I_{B2} = 0.9 \mu\text{A}$ , then using Equation (14.79):

Circuit (a),

$$\begin{aligned} \nu_0 &= (0.7 \times 10^{-6})(50 \times 10^3) \\ &\quad - (0.9 \times 10^{-6})(25 \times 10^3) \left(1 + \frac{50}{50}\right) \\ &= 0.035 - 0.045 \end{aligned}$$

or

$$\underline{\nu_0 = -0.010 \text{ V}}$$

Circuit (b),

$$\begin{aligned} \nu_0 &= (0.7 \times 10^{-6})(50 \times 10^3) \\ &\quad - (0.9 \times 10^{-6})(10^3) \left(1 + \frac{50}{50}\right) \\ &= 0.035 - 1.8 \end{aligned}$$


or

$$\underline{\nu_0 = -1.765 \text{ V}}$$

- a. If  $R = 0$ ,

$$\begin{aligned} \nu_{0,\max} &= \left(1 + \frac{100}{10}\right) V_{OS} + I_B(100 \text{ k}\Omega) \\ &= (11)(10 \times 10^{-3}) + (2 \times 10^{-6})(100 \times 10^3) \\ \nu_{0,\max} &= 0.110 + 0.20 \\ &\Rightarrow \underline{\nu_{0,\max} = 0.310 \text{ V}} \end{aligned}$$

b.

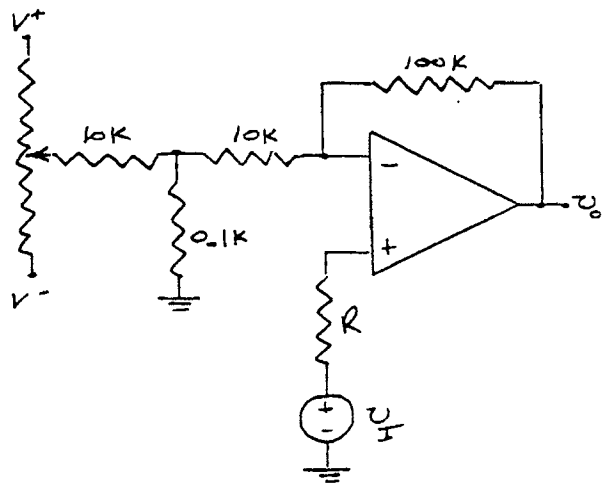

$$R = 10.1 \parallel 100 = \underline{9.17 \text{ k}\Omega = R}$$

14.34

a.  $\left(\frac{R_i}{R_i + R_2}\right)(15) = 0.010 \text{ V}$

$$\frac{15}{15 + R_2} = 0.0006667$$

$$15(1 - 0.0006667) = 0.0006667 R_2$$

Then

$$\underline{R_2 = 22.48 \text{ M}\Omega}$$

b.  $R_1 = R_i \parallel R_F = 15 \parallel 10 \Rightarrow \underline{R_1 = 6 \text{ k}\Omega}$

14.35

- a. Assume the offset voltage polarities are such as to produce the worst case values, but the bias currents are in the same direction.

Use superposition:  
Offset voltages

$$|\nu_{01}| = \left(1 + \frac{100}{10}\right)(10) = 110 \text{ mV} = |\nu_{01}|$$

$$|\nu_{02}| = (5)(110) + \left(1 + \frac{50}{10}\right)(10)$$

$$\Rightarrow |\nu_{02}| = 610 \text{ mV}$$

Bias Currents:

$$\nu_{01} = I_B(100 \text{ k}\Omega) = (2 \times 10^{-6})(100 \times 10^3) = 0.2 \text{ V}$$


Then

$$\nu_{02} = (-5)(0.2) + (2 \times 10^{-6})(50 \times 10^3) = -0.9 \text{ V}$$

Worst case:  $\nu_{01}$  is positive and  $\nu_{02}$  is negative, then

$$\underline{\nu_{01} = 0.31 \text{ V and } \nu_{02} = -1.51 \text{ V}}$$

- b. Compensation network:

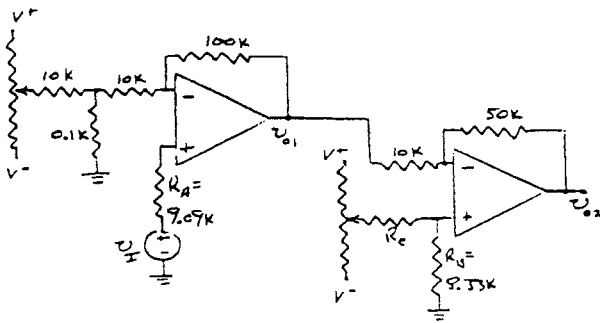

If we want

$$\left(\frac{R_B}{R_B + R_C}\right)V^+ = 20 \text{ mV and } V^+ = 10 \text{ V}$$

$$\left(\frac{8.33}{8.33 + R_C}\right)(10) = 0.020$$

or

$$\underline{R_C \cong 4.15 \text{ M}\Omega}$$

14.36

Assume bias currents are in same direction, but assume polarity of offset voltages are such as to produce the worst case output.

- a. Let  $I_{B1} = 5.5 \mu\text{A}$ ,  $I_{B2} = 4.5 \mu\text{A}$

Bias Current Effects:

$$\nu_{01} = I_{B1}(50 \text{ k}\Omega) = 0.275 \text{ V} \Rightarrow \nu_{02} = 0.275 \text{ V}$$

$$\nu_{03} = I_{B1}(20 \text{ k}\Omega) - \nu_{01} \Rightarrow \nu_{03} = -0.165 \text{ V}$$

Offset Voltage Effects:

$$\nu_{01} = (5)\left(1 + \frac{50}{10}\right) = 30 \text{ mV} \Rightarrow \nu_{02} = 30 \text{ mV}$$

$$\nu_{03} = -\nu_{01} - 5\left(1 + \frac{20}{20}\right) \Rightarrow \nu_{03} = -40 \text{ mV}$$

Total Effect:

$$\underline{\nu_{01} = 0.305 \text{ V and } \nu_{02} = 0.305 \text{ V}}$$

$$\underline{\nu_{03} = -0.205 \text{ V}}$$

14.37

For circuit (a), effect of bias current:

$$\nu_0 = (50 \times 10^3)(100 \times 10^{-9}) \Rightarrow 5 \text{ mV}$$

Effect of offset voltage

$$\nu_0 = (2)\left(1 + \frac{50}{50}\right) = 4 \text{ mV}$$

So net output voltage is  $\underline{\nu_0 = 9 \text{ mV}}$

For circuit (b), effect of bias current:

Let  $I_{B2} = 550 \text{ nA}$ ,  $I_{B1} = 450 \text{ nA}$ , then from Equation (14.79),

$$\nu_0 = (450 \times 10^{-9})(50 \times 10^3)$$

$$- (550 \times 10^{-9})(10^6)\left(1 + \frac{50}{50}\right)$$

$$= 2.25 \times 10^{-2} - 1.1$$

or

$$\nu_0 = -1.0775 \text{ V}$$

If the offset voltage is negative, then

$$\nu_0 = (-2)(2) = -4 \text{ mV}$$

So the net output voltage is

$$\underline{\nu_0 = -1.0815 \text{ V}}$$

14.38

- a. At  $T = 25^\circ\text{C}$ ,  $V_{OS} = 2\text{ mV}$  so the output voltage for each circuit is

$$\underline{\nu_0 = 4\text{ mV}}$$

- b. For  $T = 50^\circ\text{C}$ , the offset voltage for is

$$V_{OS} = 2\text{ mV} + (0.0067)(25) = 2.1675\text{ mV}$$

so the output voltage for each circuit is

$$\underline{\nu_0 = 4.335\text{ mV}}$$

14.39

- a. At  $T = 25^\circ\text{C}$ ,  $V_{OS} = 1\text{ mV}$ , then

$$\nu_{01} = (1)\left(1 + \frac{50}{10}\right) \Rightarrow \underline{\nu_{01} = 6\text{ mV}}$$

and

$$\begin{aligned} \nu_{02} &= \nu_{01}\left(1 + \frac{60}{20}\right) + (1)\left(1 + \frac{60}{20}\right) \\ &= 6(4) + (1)(4) \Rightarrow \underline{\nu_{02} = 28\text{ mV}} \end{aligned}$$

- b. At  $T = 50^\circ\text{C}$ ,  $V_{OS} = 1 + (0.0033)(25) = 1.0825\text{ mV}$ , then

$$\nu_{01} = (1.0825)(6) \Rightarrow \underline{\nu_{01} = 6.495\text{ mV}}$$

and

$$\nu_{02} = (6.495)(4) + (1.0825)(4)$$

or

$$\underline{\nu_{02} = 30.31\text{ mV}}$$

14.40

$$25^\circ\text{C}; I_B = 500\text{ nA}, I_{OS} = 200\text{ nA}$$

$$50^\circ\text{C}, I_B = 500\text{ nA} + (8\text{ nA}/^\circ\text{C})(25^\circ\text{C}) = 700\text{ nA}$$

$$I_{OS} = 200\text{ nA} + (2\text{ nA}/^\circ\text{C})(25^\circ\text{C}) = 250\text{ nA}$$

- a. Circuit (a): For  $I_B$ , bias current cancellation,  $\underline{\nu_0 = 0}$

Circuit (b): For  $I_B$ , Equation (14.79),

$$\begin{aligned} \nu_0 &= (500 \times 10^{-9})(50 \times 10^3) \\ &\quad - (500 \times 10^{-9})(10^6)\left(1 + \frac{50}{50}\right) \\ &= 0.025 - 1.00 \Rightarrow \underline{\nu_0 = -0.975\text{ V}} \end{aligned}$$

- b. Due to offset bias currents.

Circuit (a):

$$\nu_0 = (200 \times 10^{-9})(50 \times 10^3) \Rightarrow \underline{\nu_0 = 0.010\text{ V}}$$

Circuit (b):

$$\text{Let } I_{B2} = 600\text{ nA}$$

$$I_{B1} = 400\text{ nA}$$

Then

$$\begin{aligned} \nu_0 &= (400 \times 10^{-9})(50 \times 10^3) \\ &\quad - (600 \times 10^{-9})(10^6)\left(1 + \frac{50}{50}\right) \\ &= 0.020 - 1.20 \Rightarrow \underline{\nu_0 = -1.18\text{ V}} \end{aligned}$$

- c. Circuit (a): Due to  $I_B$ ,  $\underline{\nu_0 = 0}$

Circuit (b): Due to  $I_B$ ,

$$\begin{aligned} \nu_0 &= (700 \times 10^{-9})(50 \times 10^3) \\ &\quad - (700 \times 10^{-9})(10^6)\left(1 + \frac{50}{50}\right) \\ &= 0.035 - 1.40 \Rightarrow \underline{\nu_0 = -1.365\text{ V}} \end{aligned}$$

Circuit (a): Due to  $I_{OS}$ ,

$$\nu_0 = (250 \times 10^{-9})(50 \times 10^3) \Rightarrow \underline{\nu_0 = 0.0125\text{ V}}$$

Circuit (b): Due to  $I_{OS}$ ,

$$\text{Let } I_{B2} = 825\text{ nA}$$

$$I_{B1} = 575\text{ nA}$$

Then

$$\begin{aligned} \nu_0 &= (575 \times 10^{-9})(50 \times 10^3) \\ &\quad - (825 \times 10^{-9})(10^6)\left(1 + \frac{50}{50}\right) \\ &= 0.02875 - 1.65 \Rightarrow \underline{\nu_0 = -1.62\text{ V}} \end{aligned}$$

14.41

$$25^\circ\text{C}; I_B = 2\text{ }\mu\text{A}, I_{OS} = 0.2\text{ }\mu\text{A}$$

$$50^\circ\text{C}, I_B = 2\text{ }\mu\text{A} + (0.020\text{ }\mu\text{A}/^\circ\text{C})(25^\circ\text{C}) = 2.5\text{ }\mu\text{A}$$

$$I_{OS} = 0.2\text{ }\mu\text{A} + (0.005\text{ }\mu\text{A}/^\circ\text{C})(25^\circ\text{C})$$

$$= 0.325\text{ }\mu\text{A}$$

- a. Due to  $I_B$ : (Assume bias currents into op-amp).

$$\begin{aligned} \nu_{01} &= I_B(50\text{ k}\Omega) = (2 \times 10^{-6})(50 \times 10^3) \\ &\Rightarrow \underline{\nu_{01} = 0.10\text{ V}} \end{aligned}$$

$$\begin{aligned} \nu_{02} &= \nu_{01}\left(1 + \frac{60}{20}\right) + I_B(60\text{ k}\Omega) \\ &\quad - I_B(50\text{ k}\Omega)\left(1 + \frac{60}{20}\right) \\ &= (0.1)(4) + (2 \times 10^{-6})(60 \times 10^3) \\ &\quad - (2 \times 10^{-6})(50 \times 10^3)(4) \end{aligned}$$

or

$$\nu_{02} = 0.12 \text{ V}$$

b. Due to  $I_{OS}$ :

1st op-amp. Let  $I_{B1} = 2.1 \mu\text{A}$

2nd op-amp. Let  $I_{B1} = 2.1 \mu\text{A}$

$$I_{B2} = 1.9 \mu\text{A}$$

$$\nu_{01} = I_{B1}(50 \text{ k}\Omega) = (2.1 \times 10^{-6})(50 \times 10^3)$$

$$\Rightarrow \nu_{01} = 0.105 \text{ V}$$

$$\nu_{02} = \nu_{01} \left(1 + \frac{60}{20}\right) + I_{B1}(60 \text{ k}\Omega)$$

$$- I_{B2}(50 \text{ k}\Omega) \left(1 + \frac{60}{20}\right)$$

$$= (0.105)(4) + (2.1 \times 10^{-6})(60 \times 10^3)$$

$$- (1.9 \times 10^{-6})(50 \times 10^3)(4)$$

or

$$\nu_{02} = 0.166 \text{ V}$$

c. Due to  $I_B$ :

$$\nu_{01} = (2.5 \times 10^{-6})(50 \times 10^3) \Rightarrow \nu_{01} = 0.125 \text{ V}$$

$$\nu_{02} = \nu_{01} \left(1 + \frac{60}{20}\right) + I_B(60 \text{ k}\Omega)$$

$$- I_B(50 \text{ k}\Omega) \left(1 + \frac{60}{20}\right)$$

$$= (0.125)(4) + (2.5 \times 10^{-6})(60 \times 10^3)$$

$$- (2.5 \times 10^{-6})(50 \times 10^3)(4)$$

or

$$\nu_{02} = 0.15 \text{ V}$$

Due to  $I_{OS}$ :

Let  $I_{B1} = 2.6625 \mu\text{A}$

$$I_{B2} = 2.3375 \mu\text{A}$$

$$\nu_{01} = I_{B1}(50 \text{ k}\Omega) = (2.6625 \times 10^{-6})(50 \times 10^3)$$

$$\Rightarrow \nu_{01} = 0.133 \text{ V}$$

$$\nu_{02} = \nu_{01} \left(1 + \frac{60}{20}\right) + I_{B1}(60 \text{ k}\Omega)$$

$$- I_{B2}(50 \text{ k}\Omega) \left(1 + \frac{60}{20}\right)$$


$$= (0.133)(4) + (2.6625 \times 10^{-6})(60 \times 10^3)$$

$$- (2.3375 \times 10^{-6})(50 \times 10^3)(4)$$

or

$$\nu_{02} = 0.224 \text{ V}$$

14.42

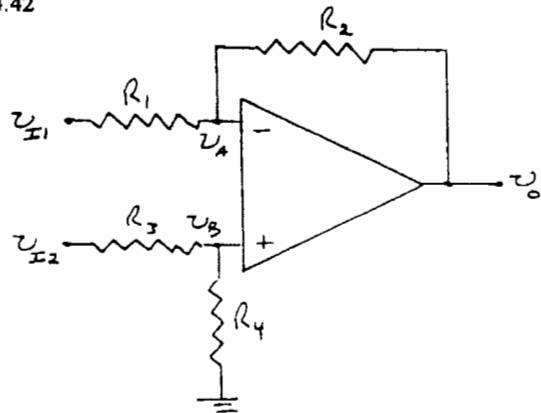

$$\nu_B = \left(\frac{R_4}{R_3 + R_4}\right) \nu_{I2} \text{ and } v_o(\nu_{I2}) = \nu_B \left(1 + \frac{R_2}{R_1}\right)$$

or

$$v_o(\nu_{I2}) = \left(\frac{R_4}{R_3 + R_4}\right) \left(1 + \frac{R_2}{R_1}\right) \nu_{I2}$$

For  $\nu_{I1}$ ,

$$v_o(\nu_{I1}) = -\frac{R_2}{R_1} \cdot \nu_{I1}$$

Then

$$v_o = \left(\frac{R_4}{R_3 + R_4}\right) \left(1 + \frac{R_2}{R_1}\right) \nu_{I2} - \frac{R_2}{R_1} \cdot \nu_{I1}$$

We can write  $\nu_{I2} = V_{cm} + \frac{V_d}{2}$  and  $\nu_{I1} = V_{cm} - \frac{V_d}{2}$ . Then

$$v_o = \left(\frac{R_4}{R_3 + R_4}\right) \left(1 + \frac{R_2}{R_1}\right) \left(V_{cm} + \frac{V_d}{2}\right)$$

$$- \frac{R_2}{R_1} \cdot \left(V_{cm} - \frac{V_d}{2}\right)$$

Common-mode gain

$$A_{cm} = \frac{v_o}{V_{cm}} = \left(\frac{R_4}{R_3 + R_4}\right) \left(1 + \frac{R_2}{R_1}\right) - \frac{R_2}{R_1}$$

Differential mode gain

$$A_d = \frac{v_o}{V_d} = \frac{1}{2} \left[ \left(\frac{R_4}{R_3 + R_4}\right) \left(1 + \frac{R_2}{R_1}\right) + \frac{R_2}{R_1} \right]$$

Then

$$CMRR = \left| \frac{A_d}{A_{cm}} \right|$$

$$= \frac{\frac{1}{2} \left[ \left(\frac{R_4}{R_3 + R_4}\right) \left(1 + \frac{R_2}{R_1}\right) + \frac{R_2}{R_1} \right]}{\left[ \left(\frac{R_4}{R_3 + R_4}\right) \left(1 + \frac{R_2}{R_1}\right) - \frac{R_2}{R_1} \right]}$$

$$CMRR = \frac{\frac{1}{2} \left[ \frac{R_4}{R_3} \cdot \frac{1}{\left(1 + \frac{R_4}{R_3}\right)} \cdot \left(1 + \frac{R_2}{R_1}\right) + \frac{R_2}{R_1} \right]}{\left[ \frac{R_4}{R_3} \cdot \frac{1}{\left(1 + \frac{R_4}{R_3}\right)} \cdot \left(1 + \frac{R_2}{R_1}\right) - \frac{R_2}{R_1} \right]}$$

Minimum  $CMRR \Rightarrow$  Maximum denominator

$\Rightarrow$  maximum  $\frac{R_4}{R_3}$  and minimum  $\frac{R_2}{R_1}$ . Then

$$\frac{R_4}{R_3} = \frac{(1.02)(50)}{(0.98)(10)} = 5.204$$

$$\frac{R_2}{R_1} = \frac{(0.98)(50)}{(1.02)(10)} = 4.804$$

Then

$$CMRR = \frac{\frac{1}{2} \left[ \frac{5.204}{6.204} \cdot (5.804) + (4.804) \right]}{\left[ \frac{5.204}{6.204} \cdot (5.804) - (4.804) \right]}$$

$$= \frac{\frac{1}{2} \cdot (9.6725)}{(0.06447)}$$

$$CMRR = 75.0 \Rightarrow CMRR_{dB} = 20 \log_{10} (75.0)$$

$$\Rightarrow \underline{CMRR_{dB} = 37.5 \text{ dB}}$$

14.43

Use the results of Problem 14.42:

$$\text{Let } \frac{R_4}{R_3} = \frac{1+x}{1-x} \cdot \left(\frac{50}{10}\right) \approx (1+2x)(5)$$

$$\text{Let } \frac{R_2}{R_1} = \frac{1-x}{1+x} \cdot \left(\frac{50}{10}\right) \approx (1-2x)(5)$$

Then

$$CMRR = \frac{\frac{1}{2} \left[ \frac{(1+2x)5}{6+10x} \cdot (6-10x) + (1-2x)(5) \right]}{\left[ \frac{(1+2x)5}{6+10x} \cdot (6-10x) - (1-2x)(5) \right]}$$

$$= \frac{\frac{1}{2} [30 + 10x - 100x^2 + 30 - 10x - 100x^2]}{[30 + 10x - 100x^2 - (30 - 10x - 100x^2)]}$$

$$= \frac{\frac{1}{2} \cdot [60 - 200x^2]}{20x} = \frac{30 - 100x^2}{20x}$$

a. For  $CMRR_{dB} = 90 \text{ dB} \Rightarrow CMRR = 31,623$   
 $x$  will be small, neglect the  $x^2$  term. Then

$$20x = \frac{30}{31,623} \Rightarrow x = 0.0000474 = \underline{0.00474\%}$$

b. For  $CMRR_{dB} = 60 \text{ dB} \Rightarrow CMRR = 1000$ . Then

$$20x = \frac{30}{1000} \Rightarrow x = 0.0015 = \underline{0.15\%}$$



## Chapter 15

## Exercise Solutions

E15.1

$$f_{3dB} = \frac{1}{2\pi RC}$$

$$RC = \frac{1}{2\pi f_{3dB}} = \frac{1}{2\pi(10^4)} = 1.59 \times 10^{-5}$$

$$\text{Let } C = 0.01 \mu\text{F} \Rightarrow \underline{R = 1.59 \text{ k}\Omega}$$

Then

$$C_1 = 0.03546 \mu\text{F}$$

$$C_2 = 0.01392 \mu\text{F}$$

$$C_3 = 0.002024 \mu\text{F}$$

$$|T| = \frac{1}{\sqrt{1 + \left(\frac{f}{f_{3dB}}\right)^6}} = \frac{1}{\sqrt{1 + \left(\frac{20}{10}\right)^6}}$$

$$|T| = 0.124 \text{ or } |T| = -18.1 \text{ dB}$$

E15.2

$$f_{3dB} = \frac{1}{2\pi RC} \Rightarrow RC = \frac{1}{2\pi f_{3dB}}$$

$$RC = \frac{1}{2\pi(50 \times 10^3)} = 3.18 \times 10^{-6}$$

$$\text{Let } C = 0.001 \mu\text{F} = 1 \text{ nF} \Rightarrow \underline{R = 3.18 \text{ k}\Omega}$$

Then

$$R_1 = 2.94 \text{ k}\Omega$$

$$R_2 = 3.44 \text{ k}\Omega$$

$$R_3 = 1.22 \text{ k}\Omega$$

$$R_4 = 8.31 \text{ k}\Omega$$

$$|T| = 0.01 = \frac{1}{\sqrt{1 + \left(\frac{f_{3dB}}{f}\right)^8}}$$

$$1 + \left(\frac{f_{3dB}}{f}\right)^8 = \left(\frac{1}{0.01}\right)^2 = 10^4$$

$$\left(\frac{f_{3dB}}{f}\right)^2 \approx 10 \Rightarrow f = \frac{f_{3dB}}{\sqrt{10}}$$

$$\Rightarrow \underline{f \approx 15.8 \text{ kHz}}$$

E15.3

$$\text{1-pole } |T| = \frac{1}{\sqrt{1 + \left(\frac{12}{10}\right)^2}} \Rightarrow -3.87 \text{ dB}$$

$$\text{2-pole } |T| = \frac{1}{\sqrt{1 + \left(\frac{12}{10}\right)^4}} \Rightarrow -4.88 \text{ dB}$$

$$\text{3-pole } |T| = \frac{1}{\sqrt{1 + \left(\frac{12}{10}\right)^6}} \Rightarrow -6.0 \text{ dB}$$

$$\text{4-pole } |T| = \frac{1}{\sqrt{1 + \left(\frac{12}{10}\right)^8}} \Rightarrow -7.24 \text{ dB}$$

E15.4

$$R_{eq} = \frac{1}{f_c C}$$

$$\text{or } f_c C = \frac{1}{R_{eq}} = \frac{1}{5 \times 10^6} = 2 \times 10^{-7}$$

$$\text{If } C = 10 \text{ pF} \Rightarrow \underline{f_c = 20 \text{ kHz}}$$

E15.5

$$\text{Low-frequency gain: } T = -\frac{C_1}{C_2} = -\frac{30}{5} = -6$$

$$f_{3dB} = \frac{f_c C_2}{2\pi C_F} = \frac{(100 \times 10^3)(5 \times 10^{-12})}{2\pi(12 \times 10^{-12})}$$

$$\Rightarrow \underline{f_{3dB} = 6.63 \text{ kHz}}$$

E15.6

$$f_0 = \frac{1}{2\pi\sqrt{3}RC}$$

$$RC = \frac{1}{2\pi f_0 \sqrt{3}} = \frac{1}{2\pi(15 \times 10^3)\sqrt{3}} = 6.13 \times 10^{-6}$$

$$\text{Let } C = 0.001 \mu\text{F} = 1 \text{ nF}$$

$$\text{Then } \underline{R = 6.13 \text{ k}\Omega} \text{ so } \underline{R_2 = 8R = 49 \text{ k}\Omega}$$

E15.7

$$f_0 = \frac{1}{2\pi\sqrt{6}RC} = \frac{1}{2\pi\sqrt{6}(10^4)(100 \times 10^{-12})}$$

$$\Rightarrow \underline{f_0 \approx 65 \text{ kHz}}$$

$$R_2 = 29R = 29(10^4)$$

$$\Rightarrow \underline{R_2 = 290 \text{ k}\Omega}$$

E15.8

$$f_0 = \frac{1}{2\pi RC} \Rightarrow C = \frac{1}{2\pi f_0 R}$$

$$C = \frac{1}{2\pi(800)(10^4)} \Rightarrow \underline{C \approx 0.02 \mu\text{F}}$$

$$R_2 = 2R_1 = 2(10) \Rightarrow \underline{R_2 = 20 \text{ k}\Omega}$$

E15.9

$$f_0 = \frac{1}{2\pi\sqrt{L \cdot \left(\frac{C_1 C_2}{C_1 + C_2}\right)}} = \frac{1}{2\pi\sqrt{(10^{-6}) \left[\frac{(10^{-9})^2}{2 \times 10^{-9}}\right]}}$$

$$\Rightarrow f_0 = 7.12 \text{ MHz}$$

$$\frac{C_2}{C_1} = g_m R$$

$$g_m = \frac{C_2}{C_1} \cdot \frac{1}{R} = \frac{1}{4 \times 10^3} \Rightarrow g_m = 0.25 \text{ mA/V}$$

We have

$$g_m = 2 \left(\frac{k'}{2}\right) \left(\frac{W}{L}\right) (V_{GS} - V_{Th})$$

$$k' \cong 20 \mu\text{A/V}^2, V_{GS} - V_{Th} \cong 1 \text{ V}$$

$$\text{So } \frac{W}{L} = \frac{0.25 \times 10^{-3}}{(20 \times 10^{-6})(1)} = 12.5$$

 and a value of  $W/L = 12.5$  is certainly reasonable.

E15.10

$$V_{TH} = \left(\frac{R_1}{R_1 + R_2}\right) V_H$$

$$2 = \left(\frac{R_1}{R_1 + 20}\right) (12)$$

$$2(R_1 + 20) = 12R_1$$

$$40 = 10R_1 \Rightarrow R_1 = 4 \text{ k}\Omega$$

E15.11

$$V_{TH} = -\left(\frac{R_1}{R_2}\right) V_L$$

$$0.10 = -\left(\frac{R_1}{R_2}\right) (-10) \Rightarrow \frac{R_1}{R_2} = 0.010$$

$$\text{Let } R_1 = 0.10 \text{ k}\Omega \text{ then } R_2 = 10 \text{ k}\Omega$$

E15.12

$$\text{a. } V_S = \left(\frac{R_2}{R_1 + R_2}\right) V_{REF} = \left(\frac{10}{1 + 10}\right) (2)$$

$$V_S = 1.82 \text{ V}$$


$$V_{TH} = V_S + \left(\frac{R_1}{R_1 + R_2}\right) V_H = 1.82 + \left(\frac{1}{1 + 10}\right) (10)$$

$$V_{TH} = 2.73 \text{ V}$$

$$V_{TL} = V_S + \left(\frac{R_1}{R_1 + R_2}\right) V_L = 1.82 + \left(\frac{1}{1 + 10}\right) (-10)$$

$$V_{TL} = 0.91 \text{ V}$$

b.

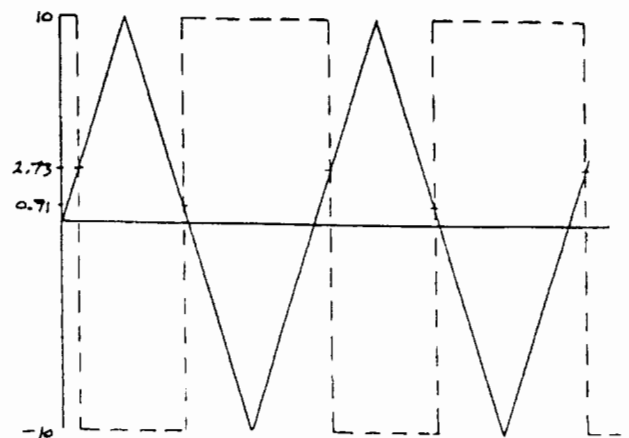

E15.13

$$V_S = \left(1 + \frac{R_1}{R_2}\right) V_{REF}$$

$$V_{TH} = V_S - \left(\frac{R_1}{R_2}\right) V_L \text{ and } V_{TL} = V_S - \left(\frac{R_1}{R_2}\right) V_H$$

$$\text{Hysteresis Width} = V_{TH} - V_{TL} = \left(\frac{R_1}{R_2}\right) (V_H - V_L)$$

$$2.5 = \left(\frac{R_1}{R_2}\right) (5 - [-5]) = 10 \left(\frac{R_1}{R_2}\right)$$

$$\text{So } \frac{R_1}{R_2} = 0.25$$

Then

$$V_S = -1 = \left(1 + \frac{R_1}{R_2}\right) V_{REF} = (1 + 0.25) V_{REF}$$

$$\Rightarrow V_{REF} = -0.8 \text{ V}$$

Then

$$V_{TH} = -1 - (0.25)(-5) \Rightarrow V_{TH} = 0.25 \text{ V}$$

$$V_{TL} = -1 - (0.25)(5) \Rightarrow V_{TL} = -2.25 \text{ V}$$

E15.14

$$V_{TH} - V_{TL} = \left(\frac{R_1}{R_1 + R_2}\right) (V_H - V_L)$$

$$0.10 = \left(\frac{R_1}{R_1 + R_2}\right) (10 - [-10])$$

$$1 + \frac{R_2}{R_1} = \frac{20}{0.10} = 200 \Rightarrow \frac{R_2}{R_1} = 199$$

$$V_S = \left(\frac{R_2}{R_1 + R_2}\right) V_{REF}$$

$$V_{REF} = \left(1 + \frac{R_1}{R_2}\right) V_S = \left(1 + \frac{1}{199}\right) (1)$$

$$\Rightarrow V_{REF} = 1.005 \text{ V}$$

$$I = \frac{V_H - V_{BE(ON)} - V_T}{R + 0.1}$$

$$R + 0.1 = \frac{10 - 0.7 - 0.7}{0.2} = 43 \text{ k}\Omega$$

$$R = 42.9 \text{ k}\Omega$$

E15.15

At  $t = 0^-$ , let  $v_o = -5$  so  $v_x = -2.5$ . For  $t > 0$

$$v_x = 10 + (-2.5 - 10) \exp\left(\frac{-t}{\tau_x}\right)$$

When  $v_x = 5.0$ , output switches

$$5.0 = 10 - 12.5 \exp\left(-\frac{t_1}{\tau_x}\right)$$

$$\exp\left(-\frac{t_1}{\tau_x}\right) = \frac{10 - 5}{12.5} = \frac{5.0}{12.5}$$

$$\exp\left(+\frac{t_1}{\tau_x}\right) = \frac{12.5}{5.0} \Rightarrow t_1 = \tau_x \cdot \ln\left(\frac{12.5}{5.0}\right)$$

$$\Rightarrow t_1 = \tau_x(0.916)$$

During the next part of the cycle

$$v_x = -5 + (5 - [-5]) \exp\left(-\frac{t}{\tau_x}\right)$$

When  $v_x = -2.5$ , output switches

$$-2.5 = -5 + 10 \exp\left(-\frac{t_2}{\tau_x}\right)$$

$$\exp\left(-\frac{t_2}{\tau_x}\right) = \frac{5 - 2.5}{10} = \frac{2.5}{10}$$

$$\exp\left(+\frac{t_2}{\tau_x}\right) = \frac{10}{2.5} \Rightarrow t_2 = \tau_x \cdot \ln\left(\frac{10}{2.5}\right)$$

$$\Rightarrow t_2 = \tau_x(1.39)$$

Period =  $t_1 + t_2 = T = [(0.916) + (1.39)]\tau_x$

$$= 2.31\tau_x$$

$$\Rightarrow \text{Frequency} = \frac{1}{2.31\tau_x}$$


$$\tau_x = (50 \times 10^3)(0.01 \times 10^{-6}) = 5 \times 10^{-4} \text{ s}$$

$$\Rightarrow f = 866 \text{ Hz}$$

$$\text{Duty cycle} = \frac{t_1}{t_1 + t_2} \times 100\%$$

$$= \frac{(0.916)}{(0.916) + (1.39)} \times 100\%$$
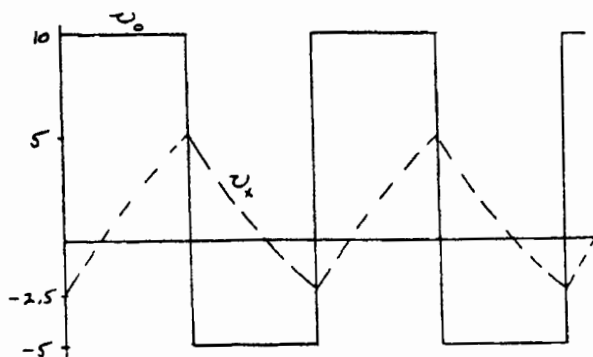
$$\Rightarrow \text{Duty cycle} = 39.7\%$$



E15.16

$$v_x = \left(\frac{R_1}{R_1 + R_2}\right)v_o = \left(\frac{10}{10 + 20}\right)v_o = \frac{1}{3}v_o$$

$$t = 0, v_x = -\frac{10}{3}$$

$$v_x = 10 + \left(-\frac{10}{3} - 10\right) \exp\left(-\frac{t}{\tau_x}\right)$$

Output switches when  $v_x = \frac{10}{3}$

$$\frac{10}{3} = 10 - 13.33 \exp\left(-\frac{t_1}{\tau_x}\right)$$

$$\exp\left(-\frac{t_1}{\tau_x}\right) = \frac{10 - 3.33}{13.33} = \frac{6.67}{13.33}$$

$$\exp\left(+\frac{t_1}{\tau_x}\right) = \frac{13.33}{6.67} \approx 2$$

$$t_1 = \tau_x \ln(2) = (0.693)\tau_x$$


$$T = 2(0.693)\tau_x$$

$$f = \frac{1}{2(0.693)\tau_x}$$

$$\tau_x = R_x C_x = (10^4)(0.1 \times 10^{-6}) = 1 \times 10^{-3}$$

$$\Rightarrow f = 722 \text{ Hz}$$

$$\Rightarrow \text{Duty cycle} = 50\%$$

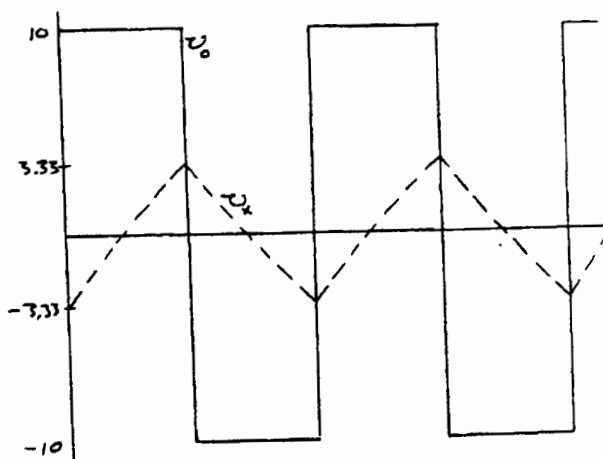

E15.17

a.  $\tau_X = R_X C_X$

$$v_Y = \left( \frac{R_1}{R_1 + R_2} \right) v_0 = \left( \frac{10}{10 + 90} \right) (12) = 1.2 \text{ V}$$

$$\beta = \frac{R_1}{R_1 + R_2} = 0.10$$

$$T = \tau_X \ln \left[ \frac{1 + V_Y/V_P}{1 - \beta} \right] = \tau_X \ln \left[ \frac{1 + \frac{0.7}{12}}{1 - (0.10)} \right]$$

$$T = 50 \times 10^{-6} = \tau_X \ln [1.18] = (0.162) \tau_X$$

$$R_X = \frac{50 \times 10^{-6}}{(0.1 \times 10^{-6})(0.162)} \Rightarrow \underline{R_X = 3.09 \text{ k}\Omega}$$

b. Recovery time

$$v_X = V_P + (-1.2 - V_P) \exp \left( -\frac{t}{\tau_X} \right)$$

When  $v_X = V_Y$ ,  $t = t_2$

$$0.7 = 12 + (-1.2 - 12) \exp \left( -\frac{t_2}{\tau_X} \right)$$

$$\exp \left( -\frac{t_2}{\tau_X} \right) = \frac{12 - 0.7}{13.2} = 0.856$$

$$t_2 = \tau_X \ln \left( \frac{1}{0.856} \right) = (0.155) \tau_X$$

$$\tau_X = (3.09 \times 10^3)(0.1 \times 10^{-6}) = 3.09 \times 10^{-4} \Rightarrow \underline{t_2 = 47.9 \mu\text{s}}$$

E15.18

$$\beta = \left( \frac{R_1}{R_1 + R_2} \right) = \frac{20}{20 + 40} = 0.333$$

$$\tau_X = R_X C_X = (10^4)(0.01 \times 10^{-6}) = 1 \times 10^{-4}$$

$$T = \tau_X \ln \left( \frac{1 + V_Y/V_P}{1 - \beta} \right) = (1 \times 10^{-4}) \ln \left[ \frac{1 + \frac{0.7}{8}}{1 - 0.333} \right]$$

$$\Rightarrow \underline{T = 48.9 \mu\text{s}}$$

Recovery time

$$0.7 = 8 + (-2.66 - 8) \exp \left( -\frac{t_2}{\tau_X} \right)$$

$$\exp \left( -\frac{t_2}{\tau_X} \right) = \frac{8 - 0.7}{10.66} = 0.685$$

$$t_2 = \tau_X \ln \left( \frac{1}{0.685} \right) \Rightarrow \underline{t_2 = 37.8 \mu\text{s}}$$

E15.19

$$f = \frac{1}{0.693(R_A + 2R_B)C}$$

$$= \frac{1}{(0.693)[20 + 2(80)] \times 10^3 \times (0.01 \times 10^{-6})}$$

$$\Rightarrow \underline{f = 802 \text{ Hz}}$$

$$\text{Duty cycle} = \frac{R_A + R_B}{R_A + 2R_B} \times 100\%$$

$$= \frac{20 + 80}{20 + 2(80)} \times 100\%$$

$$\Rightarrow \underline{\text{Duty cycle} = 55.6\%}$$

E15.20

$$f = \frac{1}{(0.693)(R_A + R_B)C}$$

$$R_A + R_B = \frac{1}{(0.693)fc}$$

Let  $C = 0.01 \mu\text{F}$ ,  $f = 1 \text{ kHz}$

$$R_A + R_B = \frac{1}{(0.693)(10^3)(0.01 \times 10^{-6})} = 1.44 \times 10^5$$

$$\text{Duty cycle} = 55 = \frac{R_A + R_B}{R_A + 2R_B} \times 100\%$$

$$55 = \frac{(1.44 \times 10^5)(100)}{(1.44 \times 10^5) + R_B}$$

$$R_B = \frac{(1.44 \times 10^5)(100 - 55)}{55}$$

$$\Rightarrow \underline{R_B = 118 \text{ k}\Omega} \text{ so } \underline{R_A = 26 \text{ k}\Omega}$$

E15.21

a.  $\bar{P} = \frac{1}{2} \frac{V_P^2}{R_L}$

$$V_P = \sqrt{2R_L \bar{P}} = \sqrt{2(8)(1)} \Rightarrow \underline{V_P = 4 \text{ V}}$$

$$I_P = \frac{V_P}{R_L} = \frac{4}{8} \Rightarrow \underline{I_P = 0.5 \text{ A}}$$

b.  $V_{CE} = 12 - 4 = 8 \text{ V}$

$$I_C \approx 0.5 \text{ A}$$

$$\text{So } P = I_C \cdot V_{CE} = (0.5)(8) \Rightarrow \underline{P = 4 \text{ W}}$$

E15.22

a.  $\frac{v_{01}}{v_i} = \left( 1 + \frac{R_2}{R_1} \right) = \left( 1 + \frac{30}{20} \right) = 2.5$

$$\frac{v_{02}}{v_i} = -\frac{R_4}{R_3} = -\frac{50}{20} = -2.5$$

(b)  $\bar{P} = \frac{1}{2} \frac{V_L^2}{R_L} = \frac{1}{2} \frac{[12 - (-12)]^2}{12} = 240 \text{ mW}$

Or

$$\underline{\bar{P} = 0.24 \text{ W}}$$

c.  $\frac{12}{2.5} = V_{P1} = 4.8 \text{ V}$

E15.23

$$\text{Line regulation} = \frac{dV_o}{dV^+} = \frac{dV_o}{dV_z} \cdot \frac{dV_z}{dV^+}$$

Now

$$\frac{dV_o}{dV_z} = \left(1 + \frac{10}{10}\right) = 2$$

$$\frac{dV_z}{dV^+} = \left(\frac{r_z}{r_z + R_1}\right) = \frac{10}{10 + 4400} = 0.00227$$

$$\text{So Line regulation} = (2)(0.00227) = 0.00454$$

$$\underline{0.454\%}$$

$$V_o[0.10 + 2.0 - 0.05 + 1000] + I_o = 12,600$$

$$V_o(1002.05) + I_o = 12,600$$

$$\text{For } I_o = 1 \text{ mA} \Rightarrow V_o = 12.5732$$


$$\text{For } I_o = 100 \text{ mA} \Rightarrow V_o = 12.4744$$

$$\text{Load reg} = \frac{V_o(\text{NL}) - V_o(\text{FL})}{V_o(\text{NL})} \times 100\%$$

$$= \frac{12.5732 - 12.4744}{12.5732} \times 100\%$$

$$\underline{\text{Load reg} = 0.786\%}$$

E15.24

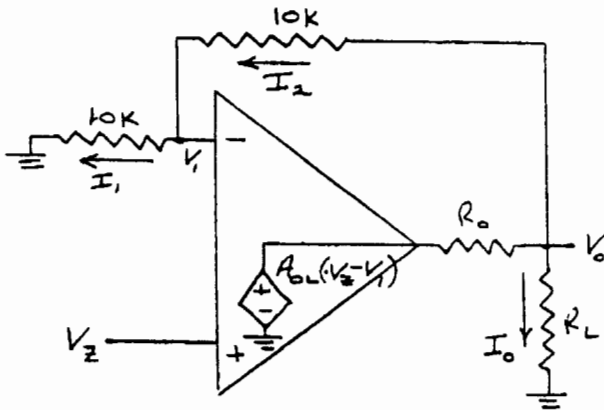

$$\frac{V_1}{10} = \frac{V_o - V_1}{10} \Rightarrow V_1 \left(\frac{1}{10} + \frac{1}{10}\right) = \frac{V_o}{10}$$

$$V_1 \left(\frac{2}{10}\right) = \frac{V_o}{10} \Rightarrow V_o = 2V_1 \Rightarrow V_1 = \frac{V_o}{2}$$

$$\frac{V_o - V_1}{10} + \frac{V_o}{R_L} + \frac{V_o - A_{0L}(V_z - V_1)}{R_o} = 0$$

$$\frac{V_o}{10} + \frac{V_o}{R_L} + \frac{V_o}{R_o} - \frac{A_{0L}V_z}{R_o} = \frac{V_1}{10} - \frac{A_{0L}V_1}{R_o}$$

$$= \frac{V_o}{2(10)} - \frac{A_{0L}V_o}{2R_o}$$

$$\frac{V_o}{10} + I_o + \frac{V_o}{0.5} - \frac{1000(6.3)}{0.5} = \frac{V_o}{20} - \frac{(1000)V_o}{2(0.5)}$$

E15.25

$$\text{a. } I_{C3} = \frac{V_z - 3V_{BE(\text{on})}}{R_1 + R_2 + R_3}$$

$$I_{C3} = \frac{5.6 - 3(0.6)}{3.9 + 3.4 + 0.576} = \frac{3.8}{7.88}$$

$$\Rightarrow \underline{I_{C3} = 0.482 \text{ mA}}$$

$$I_{C4}R_4 = V_T \ln \left(\frac{I_{C3}}{I_{C4}}\right)$$

$$I_{C4}(0.1) = (0.026) \ln \left(\frac{0.482}{I_{C4}}\right)$$

By trial and error

$$\underline{I_{C4} = 0.213 \text{ mA}}$$

$$V_{B7} = 2(0.6) + (0.482)(3.9)$$

$$\Rightarrow \underline{V_{B7} = 3.08 \text{ V}}$$

$$\text{b. } \left(\frac{R_{13}}{R_{13} + R_{12}}\right)V_o = V_{B8} = V_{B7}$$

$$\left(\frac{2.23}{2.23 + R_{12}}\right)(5) = 3.08$$

$$(2.23)(5) = (3.08)(2.23) + (3.08)R_{12}$$

$$11.15 = 6.868 = 3.08R_{12}$$

$$\Rightarrow \underline{R_{12} = 1.39 \text{ k}\Omega}$$




## Chapter 15

### Problem Solutions

15.1

(a) For example:

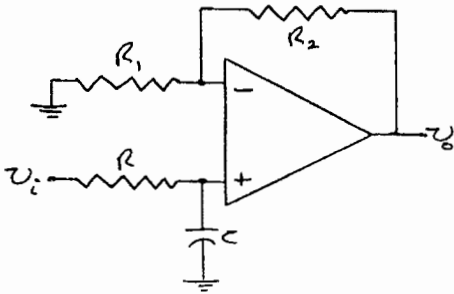


Low-Frequency:  $\frac{v_o}{v_i} = \left(1 + \frac{R_2}{R_1}\right) = 10 \Rightarrow \frac{R_2}{R_1} = 9$

Corner Frequency:

$f = \frac{1}{2\pi RC} = 5 \times 10^3 \Rightarrow RC = 3.18 \times 10^{-5}$

(b) For Example:

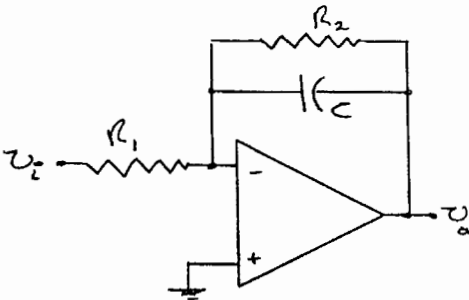

$$\frac{v_o}{v_i} = \frac{-R_2 \left\| \frac{1}{j\omega C} \right.}{R_1} = -\frac{R_2}{R_1} \cdot \frac{1}{1 + j\omega R_2 C}$$

So, set

$\frac{R_2}{R_1} = 15 \Rightarrow$  For example,  $R_1 = 10 \text{ k}\Omega$ ,  $R_2 = 150 \text{ k}\Omega$

$R_2 C = \frac{1}{2\pi f_{3-dB}} = \frac{1}{2\pi(15 \times 10^3)} = 1.06 \times 10^{-5}$

Then  $C = 70.7 \text{ pF}$

15.2

(a)  $|A_v| = \frac{1}{\sqrt{1 + \left(\frac{f}{f_{3-dB}}\right)^2}} = \frac{1}{\sqrt{1 + (2)^2}} = 0.447 \Rightarrow$

$|A_v| = -7 \text{ dB}$

(b)  $|A_v| = \frac{1}{\sqrt{1 + \left(\frac{f}{f_{3-dB}}\right)^2}} = \frac{1}{\sqrt{1 + (2)^4}} = 0.2425 \Rightarrow$

$|A_v| = -12.3 \text{ dB}$

(c)  $|A_v| = \frac{1}{\sqrt{1 + \left(\frac{f}{f_{3-dB}}\right)^2}} = \frac{1}{\sqrt{1 + (2)^6}} = 0.1240 \Rightarrow$

$|A_v| = -18.1 \text{ dB}$

15.3

Using Figure 15.9(a)

$$f_{3-dB} = \frac{1}{2\pi RC}$$

So

$$RC = \frac{1}{2\pi f_{3-dB}} = \frac{1}{2\pi(10 \times 10^3)} = 1.59 \times 10^{-5}$$

For example,  $C = 0.001 \mu\text{F}$ ,  $R = 15.9 \text{ k}\Omega$

so that  $R_3 = 11.2 \text{ k}\Omega$  and  $R_4 = 22.4 \text{ k}\Omega$

15.4

Use Figure 15.10(b)

$$f_{3-dB} = \frac{1}{2\pi RC}$$

or

$$RC = \frac{1}{2\pi(50 \times 10^3)} = 3.18 \times 10^{-6}$$

For example, let  $C = 100 \text{ pF}$  Then  $R = 31.8 \text{ k}\Omega$

And  $R_1 = 8.97 \text{ k}\Omega$

$R_2 = 22.8 \text{ k}\Omega$

$R_3 = 157 \text{ k}\Omega$

From Equation (15.26)

$$|T| = \frac{1}{\sqrt{1 + \left(\frac{f_{3dB}}{f}\right)^2}}$$

We find

$f$ kHz	$ T $
30	0.211
35	0.324
40	0.456
45	0.589

15.5

From Equation (15.7),

$$T(s) = \frac{Y_1 Y_2}{Y_1 Y_2 + Y_4(Y_1 + Y_2 + Y_3)}$$

For a high-pass filter, let  $Y_1 = Y_2 = sC$ ,

$$Y_3 = \frac{1}{R_3}, \text{ and } Y_4 = \frac{1}{R_4}$$

Then

$$\begin{aligned} T(s) &= \frac{s^2 C^2}{s^2 C^2 + \frac{1}{R_4} \left( sC + sC + \frac{1}{R_3} \right)} \\ &= \frac{1}{1 + \frac{1}{sR_4 C} \left( 2 + \frac{1}{sR_3 C} \right)} \end{aligned}$$

Define  $\tau_3 = R_3 C$  and  $\tau_4 = R_4 C$

$$T(s) = \frac{1}{1 + \frac{1}{s\tau_4} \left( 2 + \frac{1}{s\tau_3} \right)}$$

Set  $s = j\omega$

$$\begin{aligned} T(j\omega) &= \frac{1}{1 + \frac{1}{j\omega\tau_4} \left( 2 + \frac{1}{j\omega\tau_3} \right)} \\ &= \frac{1}{1 - \frac{j}{\omega\tau_4} \left( 2 - \frac{j}{\omega\tau_3} \right)} \\ &= \frac{1}{\left( 1 - \frac{1}{\omega^2\tau_3\tau_4} \right) - \frac{2j}{\omega\tau_4}} \end{aligned}$$

$$|T(j\omega)| = \left\{ \left( 1 - \frac{1}{\omega^2\tau_3\tau_4} \right)^2 + \frac{4}{\omega^2\tau_4^2} \right\}^{-1/2}$$

For a maximally flat filter, we want

$$\left. \frac{d|T|}{d\omega} \right|_{\omega \rightarrow \infty} = 0$$

Taking the derivative, we find

$$\begin{aligned} \frac{d|T(j\omega)|}{d\omega} &= -\frac{1}{2} \left\{ \left( 1 - \frac{1}{\omega^2\tau_3\tau_4} \right)^2 + \frac{4}{\omega^2\tau_4^2} \right\}^{-3/2} \\ &\quad \times \left[ 2 \left( 1 - \frac{1}{\omega^2\tau_3\tau_4} \right) \left( \frac{2}{\omega^3\tau_3\tau_4} \right) + \frac{4(-2)}{\omega^3\tau_4^2} \right] \end{aligned}$$

or

$$\begin{aligned} \left. \frac{d|T(j\omega)|}{d\omega} \right|_{\omega \rightarrow \infty} &= 0 \\ &= \left[ \left( \frac{4}{\omega^3\tau_3\tau_4} \right) \left( 1 - \frac{1}{\omega^2\tau_3\tau_4} \right) - \frac{8}{\omega^3\tau_4^2} \right] \\ &= \frac{4}{\omega^3} \left[ \frac{1}{\tau_3\tau_4} \left( 1 - \frac{1}{\omega^2\tau_3\tau_4} \right) - \frac{2}{\tau_4^2} \right] \end{aligned}$$

Then

$$\left[ \frac{1}{\tau_3\tau_4} \left( 1 - \frac{1}{\omega^2\tau_3\tau_4} \right) - \frac{2}{\tau_4^2} \right] \Big|_{\omega \rightarrow \infty} = 0$$

So that  $\frac{1}{\tau_3} = \frac{2}{\tau_4} \Rightarrow 2\tau_3 = \tau_4$

Then the transfer function can be written as:

$$\begin{aligned} |T(j\omega)| &= \left\{ \left[ 1 - \frac{1}{\omega^2(2\tau_3^2)} \right]^2 + \frac{4}{\omega^2(4\tau_3^2)} \right\}^{-1/2} \\ &= \left\{ 1 - \frac{1}{\omega^2\tau_3^2} + \frac{1}{4(\omega^2\tau_3^2)^2} + \frac{1}{\omega^2\tau_3^2} \right\}^{-1/2} \\ &= \left\{ 1 + \frac{1}{4(\omega^2\tau_3^2)^2} \right\}^{-1/2} \end{aligned}$$

3 - dB frequency

$$2\omega^2\tau_3^2 = 1 \text{ or } \omega = \frac{1}{\sqrt{2}\tau_3} = \frac{1}{\sqrt{2}R_3C}$$

Define

$$\omega = \frac{1}{RC}$$

So that

$$R_3 = \frac{R}{\sqrt{2}}$$

We had  $2\tau_3 = \tau_4$  or  $2(R_3C) = R_4C \Rightarrow R_4 = 2R_3$

So that  $R_4 = \sqrt{2} \cdot R$

15.6

From Equation (15.25)

$$|T| = \frac{1}{\sqrt{1 + \left( \frac{f}{f_{3-dB}} \right)^{2N}}}$$

- 25 dB  $\Rightarrow |T| = 0.0562$

$$\frac{f}{f_{3-dB}} = \frac{20}{10} = 2$$

So

$$0.0562 = \frac{1}{\sqrt{1 + (2)^{2N}}}$$


$$1 + (2)^{2N} = 316.6 \Rightarrow (2)^{2N} = 315.6$$

$$2N \cdot \ln(2) = \ln(315.6)$$

$$\Rightarrow N = 4.15 \Rightarrow \underline{N = 5} \text{ A 5-pole filter}$$

15.7

Consider

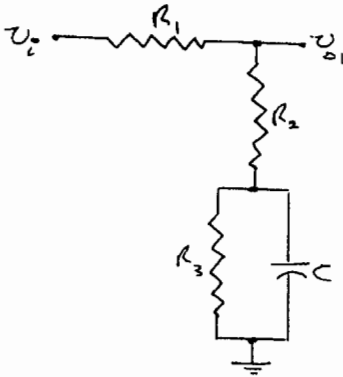


For low-frequency:  $\frac{v_o}{v_i} = \frac{R_2 + R_3}{R_1 + R_2 + R_3}$

For high-frequency:  $\frac{v_o}{v_i} = \frac{R_2}{R_1 + R_2}$

So we need
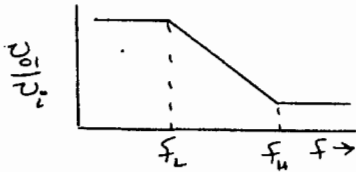
$$\frac{R_2 + R_3}{R_1 + R_2 + R_3} = 25 \left( \frac{R_2}{R_1 + R_2} \right)$$




Let  $R_1 + R_2 = 50 \text{ k}\Omega$  and  $R_2 = 15 \text{ k}\Omega \Rightarrow$

$R_1 = 48.5 \text{ k}\Omega$

Then

$$\frac{15 + R_3}{50 + R_3} = 25 \left( \frac{15}{50} \right) \Rightarrow \underline{R_3 = 144 \text{ k}\Omega}$$

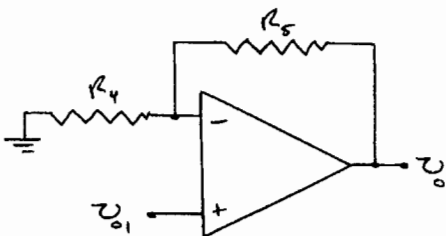Connect the output of this circuit to a non-inverting op-amp circuit.



At low-frequency:

$$v_{o1} = \frac{R_2 + R_3}{R_1 + R_2 + R_3} \cdot v_i = \frac{15 + 144}{48.5 + 15 + 144} \cdot v_i = 0.75v_i$$

Need to have  $v_o = 25$ .

$$v_o = 25 = \left( 1 + \frac{R_5}{R_4} \right) \cdot v_{o1} = \left( 1 + \frac{R_5}{R_4} \right) (0.75)v_i \Rightarrow$$

$$\frac{R_5}{R_4} = 32.3$$

To check at high-frequency.

$$v_{o1} = \frac{R_2}{R_1 + R_2} v_i = \frac{15}{15 + 48.5} v_i = 0.03v_i$$

$$v_o = (1 + 32.3)v_{o1} = (33.3)(0.03)v_i = (1.0)v_i$$

which meets the design specification

Consider the frequency response.

$$\frac{v_{o1}}{v_i} = \frac{R_2 + R_3 \parallel \frac{1}{sC}}{R_1 + R_2 + R_3 \parallel \frac{1}{sC}}$$

Now

$$R_3 \parallel \frac{1}{sC} = \frac{R_3}{1 + sR_3C}$$

Then, we find

$$\frac{v_{o1}}{v_i} = \frac{R_2 + R_3(1 + sR_3C)}{R_3 + (R_1 + R_2)(1 + sR_3C)}$$

which can be rearranged as

$$\frac{v_{o1}}{v_i} = \frac{(R_2 + R_3)(1 + s(R_2 \parallel R_3)C)}{(R_1 + R_2 + R_3)(1 + s(R_3 \parallel (R_1 + R_2))C)}$$

So

$$f_L \cong \frac{1}{2\pi(R_2 \parallel R_3)C} = \frac{1}{2\pi(15 \parallel 144) \times 10^3 C} = \frac{1}{(9.33 \times 10^3)C}$$

$$f_H \cong \frac{1}{2\pi(R_3 \parallel (R_1 + R_2))C} = \frac{1}{2\pi(144 \parallel 50) \times 10^3 C} = \frac{1}{(2.33 \times 10^5)C}$$


Set

$$25 \text{ kHz} = \frac{f_L + f_H}{2} = \frac{1}{2} \left[ \frac{1}{(9.33 \times 10^3)C} + \frac{1}{(2.33 \times 10^5)C} \right]$$

Which yields

$$\underline{C = 2.23 \text{ nF}}$$

15.8

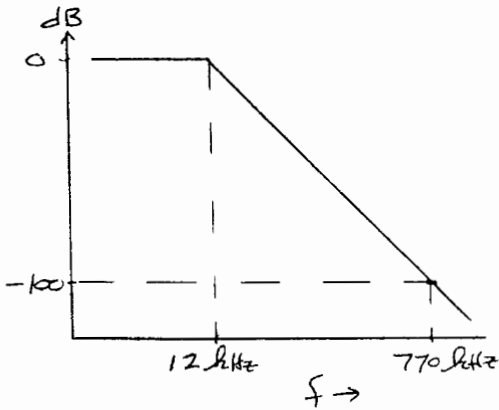

$$|A_v| = \frac{1}{\sqrt{1 + \left(\frac{f}{f_{3-dB}}\right)^{2N}}}$$

$$-100 \text{ dB} \Rightarrow 10^{-5}$$

So

$$10^{-5} = \frac{1}{\sqrt{1 + \left(\frac{770}{12}\right)^{2N}}}$$

or

$$1 + (64.2)^{2N} = \left(\frac{1}{10^{-5}}\right)^2 = 10^{10}$$

or

$$(64.2)^{2N} \cong 10^{10}$$

Now

N	Left Side
1	$4.112 \times 10^3$
2	$1.7 \times 10^7$
3	$7 \times 10^{10}$

So, we need a 3<sup>rd</sup> order filter.

Low-pass:  $-50 \text{ dB} \Rightarrow 3.16 \times 10^{-3}$

Then

$$3.16 \times 10^{-3} = \frac{1}{\sqrt{1 + \left(\frac{f}{f_L}\right)^4}} = \frac{1}{\sqrt{1 + \left(\frac{60}{f_L}\right)^4}}$$

We find  $f_L = 3.37 \text{ Hz}$

High Pass:

$$3.16 \times 10^{-3} = \frac{1}{\sqrt{1 + \left(\frac{f_H}{f}\right)^4}} = \frac{1}{\sqrt{1 + \left(\frac{f_H}{60}\right)^4}}$$

We find  $f_H = 1067 \text{ Hz}$

Bandwidth:  $BW = f_H - f_L = 1067 - 3.37 \Rightarrow$   
 $BW \cong 1064 \text{ Hz}$

15.10

a.

$$\frac{v_I}{R_4} = -\frac{v_{O2}}{R_3} - \frac{v_0}{R_1 \parallel \left(\frac{1}{sC}\right)} \quad (1)$$

$$\frac{v_0}{R_2} = -\frac{v_{O1}}{\left(\frac{1}{sC}\right)} \quad (2)$$

$$\frac{v_{O1}}{R_5} = -\frac{v_{O2}}{R_5} \Rightarrow v_{O1} = -v_{O2} \quad (3)$$

Then

$$\frac{v_0}{R_2} = +\frac{v_{O2}}{\left(\frac{1}{sC}\right)} \text{ or } v_{O2} = v_0 \left(\frac{1}{sR_2C}\right) \quad (2)$$

And

$$\begin{aligned} \frac{v_I}{R_4} &= -\frac{v_0}{R_3} \cdot \left(\frac{1}{sR_2C}\right) - \frac{v_0}{R_1 \parallel \left(\frac{1}{sC}\right)} \\ &= -v_0 \left[ \frac{1}{R_3(sR_2C)} + \frac{1}{\frac{R_1 \cdot (1/sC)}{R_1 + (1/sC)}} \right] \\ &= -v_0 \left[ \frac{1}{R_3(sR_2C)} + \frac{1 + sR_1C}{R_1} \right] \\ &= -v_0 \left[ \frac{R_1 + (1 + sR_1C)(sR_2R_3C)}{(sC)R_1R_2R_3} \right] \end{aligned} \quad (1)$$


Then

$$\frac{v_0}{v_I} = -\frac{1}{R_4} \left[ \frac{(sC)(R_1R_2R_3)}{R_1 + sR_2R_3C + s^2R_1R_2R_3C^2} \right]$$

or

$$A_v(s) = \frac{v_0}{v_I} = \frac{-\frac{1}{R_4}}{\frac{1}{R_1} + sC + \frac{1}{sCR_2R_3}}$$

15.9

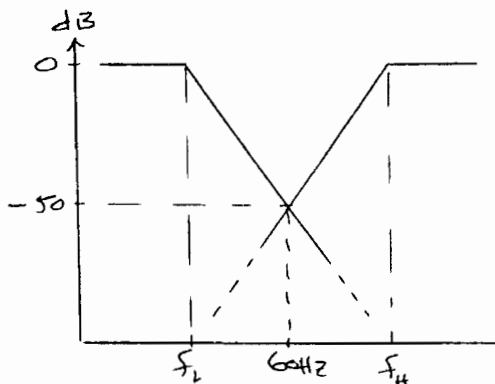

$$\text{b. } A_v(j\omega) = \frac{-\frac{1}{R_4}}{\frac{1}{R_1} + j\omega C + \frac{1}{j\omega C R_2 R_3}}$$

or

$$A_v(j\omega) = \frac{-\frac{1}{R_4}}{\frac{1}{R_1} + j\left[\omega C - \frac{1}{\omega C R_2 R_3}\right]}$$

$$= -\frac{R_1}{R_4} \cdot \frac{1}{\left\{1 + j\left[\omega R_1 C - \frac{R_1}{\omega C R_2 R_3}\right]\right\}}$$

$$|A_v(j\omega)| = \frac{R_1}{R_4} \cdot \frac{1}{\left\{1 + \left[\omega R_1 C - \frac{R_1}{\omega C R_2 R_3}\right]^2\right\}^{1/2}}$$

$$|A_v|_{\max} \text{ when } \left[\omega R_1 C - \frac{R_1}{\omega C R_2 R_3}\right] = 0$$

Then

$$|A_v|_{\max} = \frac{R_1}{R_4} = \frac{85}{3} \Rightarrow |A_v|_{\max} = 28.3$$

Now

$$\omega R_1 C \left[1 - \frac{1}{\omega^2 C^2 R_2 R_3}\right] = 0 \text{ or } \omega = \frac{1}{C\sqrt{R_2 R_3}}$$

Then

$$f = \frac{1}{2\pi C\sqrt{R_2 R_3}} = \frac{1}{2\pi(0.1 \times 10^{-6})\sqrt{(300)^2}}$$

So

$$\underline{f = 5.305 \text{ kHz}}$$

To find the two 3-dB frequencies,

$$\left[\omega R_1 C - \frac{R_1}{\omega C R_2 R_3}\right] = \pm 1$$

$$\omega^2 R_1 R_2 R_3 C^2 - R_1 = \pm \omega R_2 R_3 C$$

$$\omega^2 (85 \times 10^3)(300)^2 (0.1 \times 10^{-6})^2 - 85 \times 10^3$$

$$= \pm \omega (300)^2 (0.1 \times 10^{-6})$$

$$\omega^2 (7.65 \times 10^{-5}) - 85 \times 10^3 = \pm \omega (9 \times 10^{-3})$$

$$\omega^2 (7.65 \times 10^{-5}) \pm \omega (9 \times 10^{-3}) - 85 \times 10^3 = 0$$

$$\omega = \frac{\pm(9 \times 10^{-3})}{2(7.65 \times 10^{-5})}$$

$$\pm \frac{\sqrt{(9 \times 10^{-3})^2 + 4(7.65 \times 10^{-5})(85 \times 10^3)}}{2(7.65 \times 10^{-5})}$$

We find  $f = 5.315 \text{ kHz}$  and  $f = 5.296 \text{ kHz}$ 

15.11

a.

$$\frac{v_I - v_A}{R} = \frac{v_A}{\left(\frac{1}{sC}\right)} \quad (1)$$

$$\frac{v_I - v_B}{R} = \frac{v_B - v_O}{R} \quad (2)$$

and  $v_A = v_B$ 

So

$$\frac{v_I}{R} = v_A \left(\frac{1}{R} + sC\right) = v_A \left(\frac{1 + sRC}{R}\right) \quad (1)$$

or

$$v_A = \frac{v_I}{1 + sRC}$$

Then

$$v_I + v_O = 2v_B = 2v_A = \frac{2v_I}{1 + sRC} \quad (2)$$

$$v_O = v_I \left[\frac{2}{1 + sRC} - 1\right] = v_I \left[\frac{1 - sRC}{1 + sRC}\right]$$

Now

$$\frac{v_O}{v_I} = A(j\omega) = \frac{1 - j\omega RC}{1 + j\omega RC}$$

$$|A| = \frac{\sqrt{1 + \omega^2 R^2 C^2}}{\sqrt{1 + \omega^2 R^2 C^2}} \Rightarrow |A| = 1$$

Phase:

$$\phi = -2 \tan^{-1}(\omega RC)$$

$$\text{b. } RC = (10^4)(15.9 \times 10^{-9}) = 1.59 \times 10^{-4}$$

$f$	$\phi$
0	0
$10^2$	-11.4
$5 \times 10^3$	-53.1
$1/2\pi RC = 10^3 \text{ Hz}$	-90°
$5 \times 10^3$	-157
$10^4$	-169

15.12

a.  $\frac{V_i}{R_1} + \frac{V_i - V_0}{R_2 \parallel (1/sC)} = 0$   
 $\frac{V_i}{R_1} + \frac{V_i - V_0}{\frac{R_2}{1 + sR_2C}} = 0$   
 $\frac{R_2}{R_1} \cdot \frac{1}{1 + sR_2C} (V_i + V_i) = V_0$   
 $\frac{V_0}{V_i} = \frac{R_2 + R_1(1 + sR_2C)}{R_1(1 + sR_2C)}$   
 $= \frac{(R_2 + R_1)[1 + s(R_1 \parallel R_2)C]}{R_1(1 + sR_2C)}$   
 $\Rightarrow \frac{V_0}{V_i} = \left(1 + \frac{R_2}{R_1}\right) \left[\frac{1 + s(R_1 \parallel R_2)C}{(1 + sR_2C)}\right]$   
 $\Rightarrow f_{3dB1} = \frac{1}{2\pi R_2 C}$   
 $\Rightarrow f_{3dB2} = \frac{1}{2\pi(R_1 \parallel R_2)C}$

b.  $\frac{V_i}{R_1 \parallel (1/sC)} + \frac{V_i - V_0}{R_2} = 0$   
 $\frac{V_i}{\left(\frac{R_1}{1 + sR_1C}\right)} + \frac{V_i}{R_2} = \frac{V_0}{R_2}$   
 $V_i \left[ \frac{R_2}{R_1} \cdot (1 + sR_1C) + 1 \right] = V_0$   
 $\frac{V_i}{R_1} \cdot [R_2 + R_1 + sR_1R_2C] = V_0$   
 $\frac{V_0}{V_i} = \frac{R_2 + R_1}{R_1} \cdot [1 + s(R_1 \parallel R_2)C]$   
 $\Rightarrow \frac{V_0}{V_i} = \left(1 + \frac{R_2}{R_1}\right) [1 + s(R_1 \parallel R_2)C]$   
 $\Rightarrow f_{3dB} = \frac{1}{2\pi(R_1 \parallel R_2)C}$

15.13

a.  $\frac{V_i}{R_1 + (1/sC_1)} = \frac{-V_0}{R_2 \parallel (1/sC_2)}$   
 $V_i \left( \frac{sC_1}{1 + sR_1C_1} \right) = -V_0 \left( \frac{1 + sR_2C_2}{sC_2} \right)$   
 $\frac{V_0}{V_i} = \frac{-sR_2C_1}{(1 + sR_1C_1)(1 + sR_2C_2)}$   
 $= \frac{-sR_2C_1}{1 + sR_1C_1 + sR_2C_2 + s^2R_1R_2C_1C_2}$   
 $\frac{V_0}{V_i} = -\frac{R_2}{R_1} \times$   
 $\times \left[ \frac{sC_1}{\frac{1}{R_1} + sC_1 \left(1 + \frac{R_2}{R_1} \cdot \frac{C_2}{C_1}\right) + s^2R_2C_1C_2} \right]$

or

$$T(s) = \frac{V_0}{V_i} = -\frac{R_2}{R_1} \cdot \left[ \frac{1}{\frac{1}{sR_1C_1} + \left(1 + \frac{R_2}{R_1} \cdot \frac{C_2}{C_1}\right) + sR_2C_2} \right]$$

b.

$$|T(j\omega)| = -\frac{R_2}{R_1} \times \frac{1}{\left\{ \left(1 + \frac{R_2}{R_1} \cdot \frac{C_2}{C_1}\right)^2 + \left(\omega R_2C_2 - \frac{1}{\omega R_1C_1}\right)^2 \right\}^{1/2}}$$

when  $\left(\omega R_2C_2 - \frac{1}{\omega R_1C_1}\right) = 0$ , we want

$$|T(j\omega)| = 50 = \frac{R_2}{R_1} \cdot \frac{1}{\left(1 + \frac{R_2}{R_1} \cdot \frac{C_2}{C_1}\right)}$$

At the 3 - dB frequencies, we want

$$\left(\omega R_2C_2 - \frac{1}{\omega R_1C_1}\right) = \pm \left(1 + \frac{R_2}{R_1} \cdot \frac{C_2}{C_1}\right)$$

For  $f = 5$  kHz, use + sign and for  $f = 200$  Hz, use - sign.

$$\omega_1 = 2\pi(200) = 1257$$

$$\omega_2 = 2\pi(5 \times 10^3) = 3.142 \times 10^4$$

Define  $\tau_2 = R_2C_2$  and  $\tau_1 = R_1C_1$

Then

$$50 = \frac{R_2}{R_1} \cdot \frac{1}{1 + \frac{\tau_2}{\tau_1}} \tag{1}$$

$$\left(\omega_2\tau_2 - \frac{1}{\omega_2\tau_1}\right) = + \left(1 + \frac{\tau_2}{\tau_1}\right) \tag{2}$$

$$\left(\omega_1\tau_2 - \frac{1}{\omega_1\tau_1}\right) = - \left(1 + \frac{\tau_2}{\tau_1}\right) \tag{3}$$

From (2)

$$\frac{\omega_2^2\tau_1\tau_2 - 1}{\omega_2\tau_1} = \frac{\tau_1 + \tau_2}{\tau_1}$$

or

$$\omega_2\tau_1\tau_2 - \frac{1}{\omega_2} = \tau_1 + \tau_2$$

$$\tau_1(\omega_2\tau_2 - 1) = \frac{1}{\omega_2} + \tau_2$$

So

$$\tau_1 = \frac{1}{\omega_2} + \tau_2$$

Substituting into (3), we find

$$\omega_1 \tau_2 - \frac{1}{\omega_1 \left[ \frac{1}{\omega_2} + \tau_2 \right]} = - \left[ 1 + \frac{\tau_2 (\omega_2 \tau_2 - 1)}{\frac{1}{\omega_2} + \tau_2} \right]$$

$$\begin{aligned} \omega_1 \tau_2 \left[ \frac{1}{\omega_2} + \tau_2 \right] - \frac{1}{\omega_1} (\omega_2 \tau_2 - 1) \\ = - \left[ \left( \frac{1}{\omega_2} + \tau_2 \right) + \tau_2 (\omega_2 \tau_2 - 1) \right] \end{aligned}$$

$$\begin{aligned} \frac{\omega_1}{\omega_2} \cdot \tau_2 + \omega_1 \tau_2^2 - \frac{\omega_2}{\omega_1} \cdot \tau_2 + \frac{1}{\omega_1} \\ = - \frac{1}{\omega_2} - \tau_2 - \omega_2 \tau_2^2 + \tau_2 \end{aligned}$$

$$\begin{aligned} (\omega_1 + \omega_2) \tau_2^2 + \left( \frac{\omega_1}{\omega_2} - \frac{\omega_2}{\omega_1} \right) \tau_2 + \left( \frac{1}{\omega_1} + \frac{1}{\omega_2} \right) = 0 \\ (3.2677 \times 10^4) \tau_2^2 - 24.96 \tau_2 + 8.273 \times 10^{-4} = 0 \end{aligned}$$

$$\begin{aligned} \tau_2 = \frac{24.96}{2(3.2677 \times 10^4)} \\ \pm \frac{\sqrt{(24.96)^2 - 4(3.2677 \times 10^4)(8.273 \times 10^{-4})}}{2(3.2677 \times 10^4)} \end{aligned}$$

Since  $\omega_2$  is large,  $\tau_2$  should be small so use minus sign:

$$\tau_2 = 3.47 \times 10^{-5}$$

Then

$$\tau_1 = \frac{3.18 \times 10^{-5} + 3.47 \times 10^{-5}}{9.09 \times 10^{-2}} \Rightarrow \tau_1 = 7.32 \times 10^{-4}$$

Now

$$50 = \frac{R_2}{R_1} \cdot \frac{1}{1 + \frac{3.47 \times 10^{-5}}{7.32 \times 10^{-4}}}$$

Then

$$\frac{R_2}{R_1} = 52.37 \text{ or } \underline{R_2 = 524 \text{ k}\Omega}$$

Also


$$\tau_1 = R_1 C_1 \text{ so that } C_1 = 0.0732 \mu\text{F}$$

$$\tau_2 = R_2 C_2 \text{ so that } C_2 = 66.3 \text{ pF}$$

15.14

$$\text{Gain} = 10 \text{ dB} \Rightarrow \text{Gain} = 3.162$$

For example, we may have

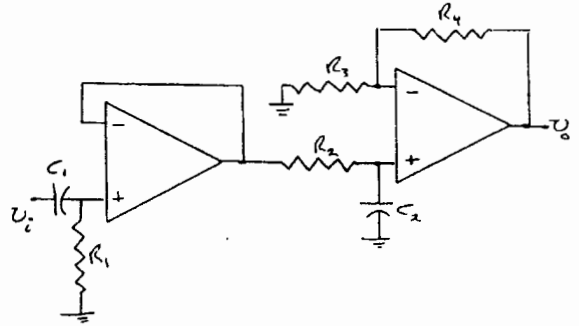

$$\text{Want } \frac{R_4}{R_3} = 2.162$$

$$\begin{aligned} \text{For example, let } R_3 = 50 \text{ k}\Omega, \\ R_4 = 108 \text{ k}\Omega \end{aligned}$$

$$f_1 = \frac{1}{2\pi R_1 C_1} = 200$$

So

$$R_1 C_1 = \frac{1}{2\pi(200)} = 0.796 \times 10^{-3}$$

For example, let  $R_1 = 200 \text{ k}\Omega \Rightarrow$  A large input resistance

$$C_1 = 0.00398 \mu\text{F}$$

$$f_2 = \frac{1}{2\pi R_2 C_2} = 50 \times 10^3$$

$$\Rightarrow R_2 C_2 = \frac{1}{2\pi(50 \times 10^3)} = 3.18 \times 10^{-6}$$

For example, let

$$R_2 = 10 \text{ k}\Omega \text{ and } C_2 = 318 \text{ pF}$$

15.15

$$f_c = 100 \text{ kHz}$$

$$R_{eq} = \frac{1}{f_c C}$$

- For  $C = 1 \text{ pF}$ ,  $R_{eq} = 10 \text{ M}\Omega$
- For  $C = 10 \text{ pF}$ ,  $R_{eq} = 1 \text{ M}\Omega$
- For  $C = 30 \text{ pF}$ ,  $R_{eq} = 333 \text{ k}\Omega$

15.16

a. From Equation (15.28),

$$Q = \frac{V_1 - V_2}{R_{eq}} \cdot T_C$$

and  $f_C = 100 \text{ kHz}$  so that  $T_C = \frac{1}{100 \times 10^3} \Rightarrow 10 \mu\text{s}$

Now

$$R_{eq} = \frac{1}{f_C C} = \frac{1}{(100 \times 10^3)(10 \times 10^{-12})} \Rightarrow 1 \text{ M}\Omega$$

So

$$Q = \frac{(2 - 1)(10 \times 10^{-6})}{10^6} = 10 \times 10^{-12} \text{ C}$$

or

$$Q = 10 \text{ pC}$$

b.  $I_{eq} = \frac{Q}{T_C} = \frac{10 \times 10^{-12}}{10 \times 10^{-6}} \text{ or } I_{eq} = 1 \mu\text{A}$

c.

$Q = CV$  so find the time that  $V_0$  reaches 99% of its full value.

$$V_0 = V_1(1 - e^{-t/\tau}) \text{ where } \tau = RC$$

$$\text{Then } 0.99 = 1 - e^{-t/\tau} \text{ or } e^{-t/\tau} = 0.01$$

$$\text{or } t = \tau \ln(100)$$

$$\tau = RC = (10^3)(10 \times 10^{-12}) = 10^{-6} \text{ s}$$

Then

$$t = 4.61 \times 10^{-6} \text{ s}$$

15.17

$$\text{Low frequency gain} = -10 \Rightarrow \frac{C_1}{C_2} = 10$$

$$f_{3dB} = 10 \times 10^3 \text{ Hz} = \frac{f_C C_2}{2\pi C_F}$$

Set

$$f_C = 10 f_{3dB} = 100 \text{ kHz}$$

Then

$$\frac{C_2}{C_F} = \frac{2\pi(10 \times 10^3)}{100 \times 10^3} = 0.628$$

The largest capacitor is  $C_1$ , so let

$$C_1 = 30 \text{ pF}$$

Then

$$C_2 = 3 \text{ pF}$$

and

$$C_F = 4.78 \text{ pF}$$

15.18

a. Time constant =  $R_{eq} \cdot C_F = \tau$  where

$$R_{eq} = \frac{1}{f_C C_1} = \frac{1}{(100 \times 10^3)(5 \times 10^{-12})} = 2 \times 10^6 \Omega$$

Then

$$\tau = (2 \times 10^6)(30 \times 10^{-12})$$

or

$$\tau = 60 \mu\text{s}$$

b.  $v_0 = -\frac{1}{\tau} \int v_I \cdot dt$

or

$$\Delta v_0 = \frac{(1)T_C}{\tau}, T_C = \frac{1}{f_C}$$

So

$$\Delta v_0 = \frac{1}{(60 \times 10^{-6})(100 \times 10^3)}$$

or

$$\Delta v_0 = 0.167 \text{ V}$$

c. Now  $\Delta v_0 = 13 = N(0.167)$

or

$$N = 78 \text{ clock pulses}$$

15.19

Using Equation (15.41)

$$f_0 = \frac{1}{2\pi\sqrt{3}RC} = \frac{1}{2\pi\sqrt{3}(4 \times 10^3)(10 \times 10^{-9})}$$

or

$$f_0 = 2.3 \text{ kHz}$$

$$\frac{R_2}{R} = 8 \text{ so that } R_2 = 8(4 \times 10^3)$$

$$\Rightarrow R_2 = 32 \text{ k}\Omega$$

15.20

a.  $v_1 = \frac{R}{R + (1/sC_V)} \cdot v_0 = \left( \frac{sRC_V}{1 + sRC_V} \right) \cdot v_0$

$$v_2 = \frac{R}{R + \frac{1}{sC}} \cdot v_1 = \left( \frac{sRC}{1 + sRC} \right) \cdot v_1$$

$$v_3 = \frac{R}{R + \frac{1}{sC}} \cdot v_2 = \left( \frac{sRC}{1 + sRC} \right) \cdot v_2$$

$$v_0 = -\frac{R_2}{R} \cdot v_3$$

Then

$$v_0 = -\frac{R_2}{R} \left( \frac{sRC}{1+sRC} \right)^2 \left( \frac{sRCV}{1+sRCV} \right) v_0$$

Set  $s = j\omega$ 

$$1 = -\frac{R_2}{R} \left( \frac{-\omega^2 R^2 C^2}{1+2j\omega RC - \omega^2 R^2 C^2} \right) \left( \frac{j\omega RCV}{1+j\omega RCV} \right)$$

The real part of the denominator must be zero.

$$1 - \omega^2 R^2 C^2 - 2\omega^2 R^2 C V = 0$$

so

$$\omega_0 = \frac{1}{R\sqrt{C(C+2CV)}}$$

$$b. f_{0,\max} = \frac{1}{2\pi(10^4)\sqrt{(10^{-11})(10^{-11} + 2[10^{-11}]})}$$

$$f_{0,\max} = 919 \text{ kHz}$$

$$f_{0,\min} = \frac{1}{2\pi(10^4)\sqrt{(10^{-11})(10^{-11} + 2[50 \times 10^{-12}])}}$$

$$f_{0,\min} = 480 \text{ kHz}$$

15.21

From Equation (15.46)

$$f_0 = \frac{1}{2\pi\sqrt{6}RC}$$

$$\text{so } R = \frac{1}{2\pi\sqrt{6}(80 \times 10^3)(100 \times 10^{-12})} \text{ or}$$

$$R = 8.12 \text{ k}\Omega$$

We need

$$\frac{R_2}{R} = 29$$

so that

$$R_2 = 236 \text{ k}\Omega$$

15.22

$$\frac{v_0 - v_1}{\frac{1}{sC}} = \frac{v_1}{R} + \frac{v_1 - v_2}{\frac{1}{sC}} \quad (1)$$

$$\text{or } (v_0 - v_1)sC = \frac{v_1}{R} + (v_1 - v_2)sC$$

$$\frac{v_1 - v_2}{\frac{1}{sC}} = \frac{v_2}{R} + \frac{v_2}{\frac{1}{sC} + R} \quad (2)$$

$$\text{or } (v_1 - v_2)sC = \frac{v_2}{R} + \frac{v_2(sC)}{1+sRC}$$

$$\frac{v_2}{\frac{1}{sC} + R} = -\frac{v_0}{R_2} \quad (3)$$

$$\text{or } \frac{v_2 sC}{1+sRC} = -\frac{v_0}{R_2}$$

so

$$v_2 = \frac{-v_0}{sR_2C}(1+sRC)$$

From (2)

$$v_1(sC) = v_2 \left[ sC + \frac{1}{R} + \frac{sC}{1+sRC} \right]$$

or

$$v_1 = -\frac{v_0(1+sRC)}{sR_2C} \cdot \left[ 1 + \frac{1}{sRC} + \frac{1}{1+sRC} \right]$$

From (1)

$$v_0(sC) = v_1 \left[ sC + \frac{1}{R} + sC \right] - v_2(sC)$$

Then

$$v_0 = \left[ 2 + \frac{1}{sRC} \right] \left[ \frac{-v_0(1+sRC)}{sR_2C} \right] \times$$

$$\times \left[ \frac{1+sRC}{sRC} + \frac{1}{1+sRC} \right] + \frac{v_0}{sR_2C} (1+sRC)$$

$$-1 = \left[ \frac{1+2sRC}{sRC} \right] \left[ \frac{1+sRC}{sR_2C} \right] \left[ \frac{(1+sRC)^2 + sRC}{(sRC)(1+sRC)} \right]$$

$$- \frac{1+sRC}{sR_2C}$$

$$-1 = \frac{(1+2sRC)(1+2sRC + s^2 R^2 C^2 + sRC)}{(sRC)^2 (sR_2C)} - \frac{(1+sRC)(sRC)^2}{(sRC)^2 (sR_2C)}$$

Set  $s = j\omega$ 

$$-1 = \frac{(1+2j\omega RC)(1+3j\omega RC + \omega^2 R^2 C^2)}{(-\omega^2 R^2 C^2)(j\omega R_2C)} - \frac{(1+j\omega RC)(-\omega^2 R^2 C^2)}{(-\omega^2 R^2 C^2)(j\omega R_2C)}$$

The real part of the numerator must be zero.

$$1 - \omega^2 R^2 C^2 - 6\omega^2 R^2 C^2 + \omega^2 R^2 C^2 = 0$$

$$6\omega^2 R^2 C^2 = 1$$

so that

$$\omega_0 = \frac{1}{\sqrt{6}RC}$$

Condition for oscillation:

$$-1 = \frac{2j\omega RC + 3j\omega RC - 2j\omega^3 R^3 C^3 + j\omega^3 R^3 C^3}{(-\omega^2 R^2 C^2)(j\omega R_2C)}$$

$$1 = \frac{5 - \omega^2 R^2 C^2}{(\omega RC)(\omega R_2C)}$$

But

$$\omega = \omega_0 = \frac{1}{\sqrt{6}RC}$$

Then

$$1 = \frac{5 - \frac{1}{6}}{\frac{(RC)(R_2C)}{6R^2C^2}} = \frac{\left(5 - \frac{1}{6}\right)(6R^2C^2)}{RR_2C^2}$$

$$1 = \frac{\left(\frac{29}{6}\right)(6R)}{R_2} \text{ or } \underline{\underline{\frac{R_2}{R} = 29}}$$

15.23

a.

$$\nu_{01} = \left(1 + \frac{R_{F1}}{R_{A1}}\right) \left(\frac{\frac{1}{sC_1}}{\frac{1}{sC_1} + R_1}\right) \cdot \nu_0 \quad (1)$$

$$\nu_{02} = \left(1 + \frac{R_{F2}}{R_{A2}}\right) \left(\frac{\frac{1}{sC_2}}{\frac{1}{sC_2} + R_2}\right) \cdot \nu_{01} \quad (2)$$

$$\nu_{03} = \left(\frac{R_{A3} \parallel \frac{1}{sC_3}}{R_{A3} \parallel \frac{1}{sC_3} + R_3}\right) \cdot \nu_{02} \quad (3)$$

$$\nu_0 = -\frac{R_{F3}}{R_{A3}} \cdot \nu_{03} \quad (4)$$

With all resistors equal and all capacitors equal, we find:

$$\nu_{01} = (2) \left(\frac{1}{1 + sRC}\right) \nu_0 \quad (1)$$

$$\nu_{02} = (2) \left(\frac{1}{1 + sRC}\right) \nu_{01} \quad (2)$$

$$\nu_{03} = (2) \left(\frac{\frac{R}{1 + sRC}}{\frac{R}{1 + sRC} + R}\right) \nu_{02}$$

$$= \left[\frac{R}{R + R(1 + sRC)}\right] \nu_{02}$$

$$\nu_{03} = \left(\frac{1}{2 + sRC}\right) \nu_{02} \quad (3)$$

and

$$\nu_0 = -\nu_{03} \quad (4)$$

Then

$$\nu_0 = -\left(\frac{1}{2 + sRC}\right) (2) \left(\frac{1}{1 + sRC}\right) (2) \left(\frac{1}{1 + sRC}\right) \nu_0$$

Let  $s = j\omega$

$$(2 + j\omega RC)(1 + j\omega RC)(1 + j\omega RC) = -4$$

$$(2 + j\omega RC)(1 + 2j\omega RC - \omega^2 R^2 C^2) = -4 \quad (A)$$

The imaginary term on the left must be zero.

$$4j\omega RC + j\omega RC - j\omega^3 R^3 C^3 = 0$$

$$\omega RC(5 - \omega^2 R^2 C^2) = 0$$

or

$$\omega = \frac{\sqrt{5}}{RC} \quad (\text{Not the same as in book})$$

15.24

a.

$$\frac{\nu_0 - \nu_{01}}{R} = \frac{\nu_{01}}{\left(\frac{1}{sC}\right)} + \frac{\nu_{01} - \nu_{02}}{R} \quad (1)$$

$$\frac{\nu_{01} - \nu_{02}}{R} = \frac{\nu_{02}}{\left(\frac{1}{sC}\right)} + \frac{\nu_{02} - \nu_{03}}{R} \quad (2)$$

$$\frac{\nu_{02} - \nu_{03}}{R} = \frac{\nu_{03}}{\left(\frac{1}{sC}\right)} + \frac{\nu_{03}}{R} \quad (3)$$

$$\nu_0 = -\frac{R_F}{R} \cdot \nu_{03} \quad (4)$$

We can write the equations as

$$\nu_0 - \nu_{01} = \nu_{01}(sRC) + \nu_{01} - \nu_{02} \quad (1)$$

$$\nu_{01} - \nu_{02} = \nu_{02}(sRC) + \nu_{02} - \nu_{03} \quad (2)$$

$$\nu_{02} - \nu_{03} = \nu_{03}(sRC) + \nu_{03} \quad (3)$$

and

$$\nu_0 = -\frac{R_F}{R} \cdot \nu_{03} \quad (4)$$

Combining terms, we find

$$\nu_0 = \nu_{01}(2 + sRC) - \nu_{02} \quad (1)$$

$$\nu_{01} = \nu_{02}(2 + sRC) - \nu_{03} \quad (2)$$

$$\nu_{02} = \nu_{03}(2 + sRC) \quad (3)$$

and

$$\nu_0 = -\frac{R_F}{R} \cdot \nu_{03} \quad (4)$$

Combining Equations (3) and (2)

$$\nu_{01} = \nu_{03}(2 + sRC)^2 - \nu_{03} = \nu_{03}[(2 + sRC)^2 - 1] \quad (2)$$

Then Equation (1) is

$$\nu_0 = \nu_{03}[(2 + sRC)^2 - 1](2 + sRC) - \nu_{03}(2 + sRC)$$

Using Equation (4), we find

$$-\frac{R_F}{R} \cdot v_{03} = v_{03} \left\{ \frac{[(2 + sRC)^2 - 1](2 + sRC)}{-(2 + sRC)} \right\}$$

To find the frequency of oscillation, set  $s = j\omega$  and set the imaginary part of the right side of the equation to zero.

We will have

$$-\frac{R_F}{R} = (2 + j\omega RC)[4 + 4j\omega RC - \omega^2 R^2 C^2 - 1 - 1]$$

Then

$$j\omega RC(2 - \omega^2 R^2 C^2) + 8j\omega RC = 0$$

or

$$j\omega RC[2 - \omega^2 R^2 C^2 + 8] = 0$$

Then the frequency of oscillation is

$$f_0 = \frac{1}{2\pi} \cdot \frac{\sqrt{10}}{RC}$$

The condition to sustain oscillations is determined from

$$-\frac{R_F}{R} = 2[2 - \omega^2 R^2 C^2] - 4\omega^2 R^2 C^2$$

or

$$-\frac{R_F}{R} = 4 - 6\omega^2 R^2 C^2$$

Setting  $\omega^2 = \frac{10}{R^2 C^2}$ , we have

$$-\frac{R_F}{R} = 4 - 6(10)$$

or

$$\frac{R_F}{R} = 56$$

b. For  $R = 5 \text{ k}\Omega$  and  $f_0 = 5 \text{ kHz}$ , we find

$$C = \frac{\sqrt{10}}{2\pi(5 \times 10^3)(5 \times 10^3)} \Rightarrow C = 0.02 \text{ }\mu\text{F}$$

$$\text{and } R_F = 56(5) \Rightarrow R_F = 280 \text{ k}\Omega$$

## 15.25

a. We can write

$$v_A = \left( \frac{R_1}{R_1 + R_2} \right) v_0 \text{ and } v_B = \left( \frac{Z_p}{Z_p + Z_s} \right) v_0$$

$$\text{where } Z_p = R_B \parallel \frac{1}{sC_B} = \frac{R_B}{1 + sR_B C_B}$$

$$\text{and } Z_s = R_A + \frac{1}{sC_A} = \frac{1 + sR_A C_A}{sC_A}$$

Setting  $v_A = v_B$ , we have

$$\frac{R_1}{R_1 + R_2} = \frac{\frac{R_B}{1 + sR_B C_B}}{\frac{R_B}{1 + sR_B C_B} + \frac{1 + sR_A C_A}{sC_A}}$$

$$\frac{R_1}{R_1 + R_2} = \frac{sR_B C_A}{sR_B C_A + (1 + sR_A C_A)(1 + sR_B C_B)} \quad (1)$$

To find the frequency of oscillation, set  $s = j\omega$  and set the real part of the denominator on the right side of Equation (1) equal to zero.

The denominator term is

$$j\omega R_B C_A + (1 + j\omega R_A C_A)(1 + j\omega R_B C_B)$$

or

$$j\omega R_B C_A + 1 + j\omega R_A C_A + j\omega R_B C_B - \omega^2 R_A R_B C_A C_B \quad (2)$$

Then from (2), we must have

$$1 - \omega_0^2 R_A R_B C_A C_B = 0$$

or

$$f_0 = \frac{1}{2\pi\sqrt{R_A R_B C_A C_B}}$$

b. To find the condition for sustained oscillation, combine Equations (1) and (2). Then

$$\frac{R_1}{R_1 + R_2} = \frac{j\omega R_B C_A}{j\omega R_B C_A + j\omega R_A C_A + j\omega R_B C_B}$$

or

$$1 + \frac{R_2}{R_1} = 1 + \frac{R_A}{R_B} + \frac{C_B}{C_A}$$

Then

$$\frac{R_2}{R_1} = \frac{R_A}{R_B} + \frac{C_B}{C_A}$$

15.26

a. We can write

$$v_A = \left( \frac{R_1}{R_1 + R_2} \right) v_0$$

and

$$v_B = \left( \frac{R \parallel sL}{R \parallel sL + R + sL} \right) v_0$$

Setting  $v_A = v_B$ , we have

$$\frac{R_1}{R_1 + R_2} = \left[ \frac{\frac{sRL}{R + sL}}{\frac{sRL}{R + sL} + R + sL} \right] \cdot v_0$$

$$\frac{R_1}{R_1 + R_2} = \frac{sRL}{sRL + (R + sL)^2} \quad (1)$$

To find the frequency of oscillation, set  $s = j\omega$  and set the real part of the denominator on the right side of Equation (1) equal to zero.

The denominator term is:

$$j\omega RL + (R + j\omega L)^2$$

or

$$j\omega RL + R^2 + 2j\omega RL - \omega^2 L^2 \quad (2)$$

Then

$$R^2 - \omega_0^2 L^2 = 0$$

or

$$f_0 = \frac{1}{2\pi} \cdot \sqrt{\frac{R}{L}}$$

b. To find the condition for sustained oscillations, combine Equations (1) and (2).

$$\frac{R_1}{R_1 + R_2} = \frac{j\omega RL}{j\omega RL + 2j\omega RL} = \frac{1}{3}$$

Then

$$1 + \frac{R_2}{R_1} = 3$$

so that

$$\frac{R_2}{R_1} = 2$$

15.27

From Equation (15.52(b))

$$f_0 = \frac{1}{2\pi RC}$$

or

$$RC = \frac{1}{2\pi f} = \frac{1}{2\pi(80 \times 10^3)}$$

$$RC \approx 2 \times 10^{-6}$$

Set  $R = 20 \text{ k}\Omega$  and  $C = 100 \text{ pF}$

We must have

$$\frac{R_2}{R_1} = 2$$

Set  $R_2 = 40 \text{ k}\Omega$  and  $R_1 = 20 \text{ k}\Omega$ , for example.

15.28

From Equation (15.59)

$$f_0 = \frac{1}{2\pi \sqrt{L \left( \frac{C_1 C_2}{C_1 + C_2} \right)}}$$

and from Equation (15.61)

$$\frac{C_2}{C_1} = g_m R$$

Now,

$$g_m = 2\sqrt{k_n I_{DQ}} = 2\sqrt{(0.5)(1)} = 1.414 \text{ mA/V}$$

We have  $C_1 = 0.01 \text{ }\mu\text{F}$ ,  $R = 4 \text{ k}\Omega$ ,  $f_0 = 400 \text{ kHz}$

So

$$C_2 = g_m R C_1 = (1.414)(4)(0.01)$$

or

$$C_2 = 0.0566 \text{ }\mu\text{F}$$

and

$$400 \times 10^3 = \frac{1}{2\pi \sqrt{L \left[ \frac{(0.01)(0.0566)}{0.01 + 0.0566} \right] \times 10^{-6}}}$$

$$L(8.5 \times 10^{-9}) = \left[ \frac{1}{2\pi(400 \times 10^3)} \right]^2 = 1.58 \times 10^{-13}$$

Then

$$L = 18.6 \text{ }\mu\text{H}$$

15.29

$$V_{\pi} = -V_0$$

$$\frac{V_0}{\left(\frac{1}{sC_2}\right)} + \frac{V_0}{R_L} + \frac{V_0 - V_1}{\left(\frac{1}{sC_1}\right)} = g_m V_{\pi} = -g_m V_0$$

$$V_0 \left[ sC_2 + sC_1 + \frac{1}{R_L} + g_m \right] = V_1 (sC_1) \quad (1)$$

$$\frac{V_1}{sL} + \frac{V_0 - V_1}{\left(\frac{1}{sC_1}\right)} + g_m V_{\pi} = 0 \quad (2)$$

$$V_1 \left( \frac{1}{sL} + sC_1 \right) = V_0 (sC_1 + g_m)$$

$$V_1 = \frac{V_0 (sC_1 + g_m)}{\left( \frac{1}{sL} + sC_1 \right)}$$

Then

$$V_0 \left[ s(C_1 + C_2) + \frac{1}{R_L} + g_m \right] = \frac{V_0 (sC_1)(sC_1 + g_m)}{\left( \frac{1}{sL} + sC_1 \right)}$$

$$\left[ s(C_1 + C_2) + \frac{1}{R_L} + g_m \right] \left( \frac{1}{sL} + sC_1 \right) = sC_1 (sC_1 + g_m)$$

$$\frac{C_1 + C_2}{L} + s^2 C_1 (C_1 + C_2) + \frac{1}{sR_L L} + \frac{sC_1}{R_L} + s g_m C_1 + \frac{g_m}{sL} = s^2 C_1^2 + s g_m C_1$$

$$\frac{C_1 + C_2}{L} + s^2 C_1 C_2 + \frac{1}{sR_L L} + \frac{sC_1}{R_L} + \frac{g_m}{sL} = 0$$

Set  $s = j\omega$

$$\frac{C_1 + C_2}{L} - \omega^2 C_1 C_2 + \frac{1}{j\omega R_L L} + \frac{j\omega C_1}{R_L} + \frac{g_m}{j\omega L} = 0$$

Then

$$\omega^2 = \frac{C_1 + C_2}{C_1 C_2 L} \Rightarrow \omega_0 = \sqrt{\frac{C_1 + C_2}{C_1 C_2 L}}$$

and

$$\frac{g_m}{\omega L} + \frac{1}{\omega R_L L} = \frac{\omega C_1}{R_L}$$

Then

$$\frac{g_m}{L} + \frac{1}{R_L L} = \frac{(C_1 + C_2) C_1}{C_1 C_2 L R_L}$$

$$g_m + \frac{1}{R_L} = \frac{C_1 + C_2}{C_2 R_L}$$

$$g_m R_L + 1 = \frac{C_1}{C_2} + 1 \text{ or } \frac{C_1}{C_2} = g_m R_L$$

15.30

a.

$$\frac{V_0}{sL_1} + \frac{V_0}{R} + g_m V_{\pi} + \frac{V_0}{\frac{1}{sC} + sL_2} = 0 \quad (1)$$

$$V_{\pi} = \left( \frac{sL_2}{\frac{1}{sC} + sL_2} \right) V_0 \quad (2)$$

Then

$$V_0 \left\{ \frac{1}{sL_1} + \frac{1}{R} + \frac{sC}{1 + s^2 L_2 C} + \frac{g_m (s^2 L_2 C)}{1 + s^2 L_2 C} \right\} = 0$$

$$\left\{ \frac{R(1 + s^2 L_2 C) + (sL_1)(1 + s^2 L_2 C)}{(sRL_1)(1 + s^2 L_2 C)} + \frac{s^2 RL_1 C + g_m (sRL_1)(s^2 L_2 C)}{(sRL_1)(1 + s^2 L_2 C)} \right\} = 0$$

Set  $s = j\omega$ . Both real and imaginary parts of the numerator must be zero.

$$R(1 - \omega^2 L_2 C) + j\omega L_1 (1 - \omega^2 L_2 C) - \omega^2 RL_1 C + (j\omega g_m RL_1)(-\omega^2 L_2 C) = 0$$

Real part

$$R(1 - \omega^2 L_2 C) - \omega^2 RL_1 C = 0$$

$$R = \omega^2 RC(L_1 + L_2)$$

or

$$\omega_0 = \frac{1}{\sqrt{C(L_1 + L_2)}}$$

b. Imaginary part:

$$j\omega L_1 (1 - \omega^2 L_2 C) - j\omega g_m RL_1 (\omega^2 L_2 C) = 0$$

$$L_1 = \omega^2 L_1 L_2 C + g_m RL_1 (\omega^2 L_2 C)$$

$$\text{Now } \omega^2 = \frac{1}{(L_1 + L_2)}$$

$$1 = \frac{1}{C(L_1 + L_2)} [L_2 C + g_m RL_2 C]$$

$$1 = \frac{L_2}{L_1 + L_2} (1 + g_m R) \Rightarrow \frac{L_1}{L_2} = (1 + g_m R)$$

or

$$\frac{L_1}{L_2} = g_m R$$

15.31

$$\omega_0 = 2\pi(800 \times 10^3) = \frac{1}{\sqrt{C(L_1 + L_2)}}$$

or

$$C(L_1 + L_2) = 3.96 \times 10^{-14}$$

Also  $\frac{L_1}{L_2} = g_m R$

For example, if  $R = 1 \text{ k}\Omega$ , then  $\frac{L_1}{L_2} = (20)(1) = 20$

So

$$L_1 = 20L_2$$

Then

$$C(21L_2) = 3.96 \times 10^{-14} \text{ or } CL_2 = 1.89 \times 10^{-15}$$

If  $C = 0.01 \text{ }\mu\text{F}$

then  $L_2 = 0.189 \text{ }\mu\text{H}$

and  $L_1 = 3.78 \text{ }\mu\text{H}$

15.32

$$\frac{\nu_0 - \nu_1}{\left(\frac{1}{sC}\right)} = \frac{\nu_1}{R} + \frac{\nu_1 - \nu_B}{R} \tag{1}$$

and

$$\frac{\nu_B}{\left(\frac{1}{sC}\right)} + \frac{\nu_B - \nu_1}{R} = 0 \tag{2}$$

or

$$\nu_B \left(sC + \frac{1}{R}\right) = \frac{\nu_1}{R} \Rightarrow \nu_1 = \nu_B(1 + sRC)$$

From (1)

$$\nu_0(sC) = \nu_1 \left(sC + \frac{2}{R}\right) - \frac{\nu_B}{R}$$

or

$$\begin{aligned} \nu_0(sRC) &= \nu_B(1 + sRC)(2 + sRC) - \nu_B \\ &= \nu_B[(1 + sRC)(2 + sRC) - 1] \end{aligned}$$

Now

$$\begin{aligned} T(s) &= \left(1 + \frac{R_2}{R_1}\right) \left[ \frac{sRC}{(1 + sRC)(2 + sRC) - 1} \right] \\ &= \left(1 + \frac{R_2}{R_1}\right) \left[ \frac{sRC}{2 + 3sRC + s^2R^2C^2 - 1} \right] \end{aligned}$$

or

$$T(s) = \left(1 + \frac{R_2}{R_1}\right) \left[ \frac{sRC}{s^2R^2C^2 + 3sRC + 1} \right]$$

$$T(j\omega) = \left(1 + \frac{R_2}{R_1}\right) \left[ \frac{j\omega RC}{1 - \omega^2R^2C^2 + 3j\omega RC} \right]$$

Frequency of oscillation:

$$f_0 = \frac{1}{2\pi RC}$$

Condition for oscillation:

$$1 = \left(1 + \frac{R_2}{R_1}\right) \left[ \frac{j\omega RC}{3j\omega RC} \right]$$

or

$$\frac{R_2}{R_1} = 2$$

15.33

$$\frac{\nu_0 - \nu_1}{sL} = \frac{\nu_1}{R} + \frac{\nu_1 - \nu_B}{R} \tag{1}$$

$$\nu_B = \left(\frac{sL}{R + sL}\right) \nu_1 \tag{2}$$

or

$$\nu_1 = \left(\frac{R + sL}{sL}\right) \nu_B$$

Then

$$\frac{\nu_0}{sL} = \nu_1 \left(\frac{1}{sL} + \frac{2}{R}\right) - \frac{\nu_B}{R}$$

or

$$\begin{aligned} \frac{\nu_0}{sL} &= \left(\frac{R + sL}{sL}\right) \left(\frac{1}{sL} + \frac{2}{R}\right) \nu_B - \frac{\nu_B}{R} \\ &= \nu_B \left\{ \left(\frac{R + sL}{sL}\right) \left(\frac{R + 2sL}{sRL}\right) - \frac{1}{R} \right\} \end{aligned} \tag{1}$$

Then

$$\nu_B = \frac{\nu_0}{sL} \cdot \frac{1}{\left\{ \frac{(R + sL)(R + 2sL) - (sL)^2}{(sL)(sRL)} \right\}}$$

Now

$$T(s) = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{sRL}{R^2 + 3sRL + 2s^2L^2 - s^2L^2}\right)$$

or

$$T(s) = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{sRL}{s^2L^2 + 3sRL + R^2}\right)$$

And

$$T(j\omega) = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{j\omega RL}{R^2 - \omega^2L^2 + 3j\omega RL}\right)$$

Frequency of oscillation:  $f_0 = \frac{R}{2\pi L}$

Condition for oscillation:

$$1 = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{1}{3}\right)$$

or

$$\frac{R_2}{R_1} = 2$$

15.34

From Equation (15.65(b)), the crossover voltage is

$$\nu_I = -\frac{R_2}{R_1} \cdot V_{REF}$$

Let  $R_2 = R_{VAR} + R_F$  where  $R_{VAR}$  is the potentiometer and  $R_F$  is the fixed resistor.Let  $V_{REF} = -5$  V,  $R_F = 10$  k $\Omega$ , and  $R_{VAR} = 40$  k $\Omega$ 

Then we have

$$\nu_I = -\frac{R_F}{R_1} \cdot V_{REF} = -\left(\frac{10}{50}\right)(-5) = 1$$
 V

and

$$\nu_I = -\left(\frac{50}{50}\right)(-5) = 5$$
 V

15.35

$$i_{\max} = \frac{10}{R_1 + R_2} = 0.1 \Rightarrow R_1 + R_2 = 100$$
 k $\Omega$

Hysteresis width

$$\Delta V = V_{TH} - V_{TL} = \left(\frac{R_1}{R_1 + R_2}\right)(V_H - V_L)$$

$$\text{or } 0.1 = \left(\frac{R_1}{100}\right)(20)$$

so that

$$\underline{R_1 = 0.5 \text{ k}\Omega}$$

$$\underline{R_2 = 99.5 \text{ k}\Omega}$$

15.36

$$\text{a. } V_{TH} = \left(\frac{R_1}{R_1 + R_2}\right)V_H = \left(\frac{10}{10 + 40}\right)(10)$$

$$\text{so } \underline{V_{TH} = 2 \text{ V}}$$

$$V_{TL} = \left(\frac{R_1}{R_1 + R_2}\right)V_L = \left(\frac{10}{10 + 40}\right)(-10)$$

$$\text{so } \underline{V_{TL} = -2 \text{ V}}$$

$$\text{b. } \nu_I = 5 \sin \omega t$$

15.37

a. Upper crossover voltage when  $\nu_0 = +V_P$ .

Now

$$\nu_B = \left(\frac{R_1}{R_1 + R_2}\right)(+V_P)$$

and

$$\nu_A = \left(\frac{R_A}{R_A + R_B}\right)V_{REF} + \left(\frac{R_B}{R_A + R_B}\right)V_{TH}$$

 $\nu_A = \nu_B$  so that

$$\begin{aligned} &\left(\frac{R_1}{R_1 + R_2}\right)V_P \\ &= \left(\frac{R_A}{R_A + R_B}\right)V_{REF} + \left(\frac{R_B}{R_A + R_B}\right)V_{TH} \end{aligned}$$

or

$$V_{TH} = \left(\frac{R_A + R_B}{R_1 + R_2}\right)\left(\frac{R_1}{R_B}\right)V_P - \left(\frac{R_A}{R_B}\right)V_{REF}$$

Lower crossover voltage when  $\nu_0 = -V_P$ 

So

$$V_{TL} = -\left(\frac{R_A + R_B}{R_1 + R_2}\right)\left(\frac{R_1}{R_B}\right)V_P - \left(\frac{R_A}{R_B}\right)V_{REF}$$

$$\text{b. } V_{TH} = \left(\frac{10 + 20}{5 + 20}\right)\left(\frac{5}{20}\right)(10) - \left(\frac{10}{20}\right)(2)$$

$$\text{or } \underline{V_{TH} = 2 \text{ V}}$$

and

$$V_{TL} = -\left(\frac{10 + 20}{5 + 20}\right)\left(\frac{5}{20}\right)(10) - 1 \Rightarrow \underline{V_{TL} = -4 \text{ V}}$$

15.38

$$\text{a. } \frac{\nu_B}{R_1} = \frac{V_{REF} - \nu_B}{R_3} + \frac{\nu_0 - \nu_B}{R_2}$$

$$\nu_B \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}\right) = \frac{V_{REF}}{R_3} + \frac{\nu_0}{R_2}$$

 $V_{TH} = \nu_B$  when  $\nu_0 = +V_P$  and  $V_{TL} = \nu_B$  when  $\nu_0 = -V_P$ 

So

$$V_{TH} = \frac{\frac{V_{REF}}{R_3} + \frac{V_P}{R_2}}{\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}\right)}$$

and

$$V_{TL} = \frac{\frac{V_{REF}}{R_3} - \frac{V_P}{R_2}}{\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}\right)}$$

b.

$$\begin{aligned} V_S &= \frac{V_{REF}}{R_3 \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}\right)} \\ -5 &= \frac{-10}{10 \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{10}\right)} \end{aligned}$$

$$\frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{5} - \frac{1}{10} = 0.10$$

$$\Delta V_T = V_{TH} - V_{TL} = \frac{\frac{2V_P}{R_2}}{\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}\right)}$$

$$0.2 = \frac{2(12)}{R_2(0.10 + 0.10)}$$

So  $R_2 = 600 \text{ k}\Omega$

Then

$$\frac{1}{R_1} + \frac{1}{R_2} = 0.10$$

$$\frac{1}{R_1} + \frac{1}{600} = 0.10 \Rightarrow R_1 = 10.17 \text{ k}\Omega$$

c.  $V_{TH} = -5 + 0.1 = -4.9$

$$V_{TL} = -5 - 0.1 = -5.1$$

15.39

- a. If the saturated output voltage is  $|V_P| < 6.2 \text{ V}$ , then the circuit behaves as a comparator

where  $|\nu_0| < 6.2 \text{ V}$ .

If the saturated output voltage is  $|V_P| > 6.2 \text{ V}$ , the output will flip to either  $+V_P$  or  $-V_P$  and the input has no control.

- b. Same as part (a) except the curve at  $\nu_I \approx 0$  will have a finite slope.

c.

Circuit works as a comparator as long as  $\nu_{01} < 8.7 \text{ V}$  and  $\nu_{02} > -3.7 \text{ V}$ . Otherwise the input has no control.

15.40

- a. Switching point is when  $\nu_0 = 0$ . Then

$$\nu_+ = \nu_I \equiv V_S = \left(\frac{R_2}{R_1 + R_2}\right) V_{REF}$$

$V_{TH}$  occurs when  $\nu_0 = V_H$ , then by superposition

$$\nu_+ = V_{TH} = \left(\frac{R_1}{R_1 + R_2}\right) V_H + \left(\frac{R_2}{R_1 + R_2}\right) V_{REF}$$

or

$$V_{TH} = V_S + \left(\frac{R_1}{R_1 + R_2}\right) V_H$$

$V_{TL}$  occurs when  $\nu_0 = V_L$ , then by superposition

$$\nu_+ = V_{TL} = \left(\frac{R_1}{R_1 + R_2}\right) V_L + \left(\frac{R_2}{R_1 + R_2}\right) V_{REF}$$

or

$$V_{TL} = V_S + \left(\frac{R_1}{R_1 + R_2}\right) V_L$$

- b. For  $V_{TH} = 2 \text{ V}$  and  $V_{TL} = 1 \text{ V}$ , then  $V_S = 1.5 \text{ V}$

Now

$$2 = 1.5 + \left(\frac{10}{10 + R_2}\right)(10)$$

$$\frac{0.5}{10} = \frac{10}{10 + R_2} \Rightarrow R_2 = 190 \text{ k}\Omega$$

Now  $V_S = 1.5 = \left(\frac{190}{10 + 190}\right) V_{REF}$

so

$$V_{REF} = 1.579 \text{ V}$$

15.41

- a. Switching point when  $\nu_0 = 0$ .

Now

$$\nu_+ = V_{REF} = \left(\frac{R_2}{R_1 + R_2}\right) \nu_I \text{ where } \nu_I = V_S.$$

Then

$$V_S = \left(\frac{R_1 + R_2}{R_2}\right) V_{REF} = \left(1 + \frac{R_1}{R_2}\right) V_{REF}$$

Now upper crossover voltage for  $\nu_I$  occurs when  $\nu_0 = V_L$  and  $\nu_+ = V_{REF}$ . Then

$$\frac{V_{TH} - V_{REF}}{R_1} = \frac{V_{REF} - V_L}{R_2}$$

$$\text{or } V_{TH} = -\frac{R_1}{R_2} \cdot V_L + V_{REF} \left(1 + \frac{R_1}{R_2}\right)$$

$$\text{or } V_{TH} = V_S - \frac{R_1}{R_2} \cdot V_L$$

Lower crossover voltage for  $\nu_I$  occurs when  $\nu_0 = V_H$  and  $\nu_I = V_{REF}$ . Then

$$\frac{V_H - V_{REF}}{R_2} = \frac{V_{REF} - V_{TL}}{R_1}$$

$$\text{or } V_{TL} = -\frac{R_1}{R_2} \cdot V_H + V_{REF} \left(1 + \frac{R_1}{R_2}\right)$$

$$\text{or } V_{TL} = V_S - \frac{R_1}{R_2} \cdot V_H$$

b. For  $V_{TH} = -1$  and  $V_{TL} = -2$ ,  $V_S = -1.5$  V.

$$\text{Then } V_{TL} = V_S - \frac{R_1}{R_2} \cdot V_H \Rightarrow -2 = -1.5 - \frac{R_1}{20}(12)$$

so that  $R_1 = 0.833 \text{ k}\Omega$

Now

$$V_S = \left(1 + \frac{R_1}{R_2}\right) V_{REF}$$

$$-1.5 = \left(1 + \frac{0.833}{20}\right) V_{REF}$$

which gives

$$\underline{V_{REF} = -1.44 \text{ V}}$$

15.42

a.  $V_H = 5.6 + 0.7 = 6.3$  V and  $V_L = -6.3$  V

From Equation (15.72(b)),

$$V_{TH} = -\left(\frac{R_1}{R_2}\right) V_L$$

and from Equation (15.75(b)),

$$V_{TL} = -\left(\frac{R_1}{R_2}\right) V_H$$

$$V_{TH} - V_{TL} = 1 = -\left(\frac{R_1}{R_2}\right)(V_L - V_H)$$

$$= +\left(\frac{R_1}{R_2}\right)(2)(6.3)$$

$$\text{so } \frac{R_1}{R_2} = 0.07937$$

$$\text{Then } R_2 = \frac{1}{0.07937} \Rightarrow \underline{R_2 = 12.6 \text{ k}\Omega}$$

$$\text{Now } V_{TH} = -(0.07937)(-6.3) = 0.5,$$

$$V_{TL} = -0.5$$

b. For  $\nu_0$  high, we have

$$I = I_D + I_R, \text{ } I \text{ is fixed for a given } R.$$

Assume  $\nu_I$  varies between  $\pm 12$  V

$$I_{R(\max)} = \frac{6.3 - (-12)}{13.6} = 1.35 \text{ mA}$$

$$I_{R(\min)} = \frac{6.3 - 0.5}{13.6} = 0.426 \text{ mA}$$

$$I_{R(\text{avg})} = \frac{1.35 + 0.426}{2} = 0.888 \text{ mA}$$

Then we want

$$I = I_{D(\text{avg})} + I_{R(\text{avg})} = 1 + 0.888 = 1.888 \text{ mA}$$

Then

$$R = \frac{12 - 6.3}{1.888} \Rightarrow \underline{R = 3.02 \text{ k}\Omega}$$

15.43

a.  $\nu_0 = V_{REF} + 2V_\gamma$

$$5 = V_{REF} + 2(0.7)$$

or

$$\underline{V_{REF} = 3.6 \text{ V}}$$

b.  $V_{TH} = \left(\frac{R_1}{R_1 + R_2}\right)(V_{REF} + 2V_\gamma)$

$$0.5 = \left(\frac{R_1}{R_1 + R_2}\right)(5)$$

$$\text{or } 1 + \frac{R_2}{R_1} = 10 \Rightarrow \frac{R_2}{R_1} = 9$$

For example, let  $R_2 = 90 \text{ k}\Omega$  and  $R_1 = 10 \text{ k}\Omega$

c. For  $\nu_I = 10$  V, and  $\nu_0$  is in its low state.  $D_1$  is on and  $D_2$  is off.

$$\frac{\nu_I - (\nu_1 + 0.7)}{100} + \frac{V_{REF} - \nu_1}{1} = \frac{\nu_1 - \nu_0}{1}$$

For  $\nu_1 = -0.7$ , then

$$\frac{10 - 0}{100} + \frac{3.6 - (-0.7)}{1} = \frac{-0.7 - \nu_0}{1}$$

or

$$\underline{\nu_0 = -5.1 \text{ V}}$$

15.44

For  $\nu_0 = \text{High} = (V_{REF} + 2V_\gamma)$ . Then switching point is when

$$\nu_I = \nu_B = \left(\frac{R_1}{R_1 + R_2}\right) \nu_0$$

$$\text{or } V_{TH} = \left(\frac{R_1}{R_1 + R_2}\right)(V_{REF} + 2V_\gamma)$$

Lower switching point is when

$$\nu_1 = \nu_B = \left(\frac{R_1}{R_1 + R_2}\right) \nu_0 \text{ and } \nu_0 = -(V_{REF} + 2V_\gamma)$$

so

$$V_{TL} = -\left(\frac{R_1}{R_1 + R_2}\right)(V_{REF} + 2V_\gamma)$$

15.45

By symmetry, inverting terminal switches about zero.

Now, for  $\nu_0$  low, upper diode is on.

$$V_{REF} - \nu_1 = \nu_1 - \nu_0$$

$$\nu_0 = 2\nu_1 - V_{REF} \text{ where } \nu_1 = -V_\gamma$$

so

$$\underline{\nu_0 = -(V_{REF} + 2V_\gamma)}$$

Similarly, in the high state

$$\underline{\nu_0 = (V_{REF} + 2V_\gamma)}$$

Switching occurs when non-inverting terminal is zero.

So for  $v_o$  low,

$$\frac{V_{TH} - 0}{R_1} = \frac{0 - [-(V_{REF} + 2V_\gamma)]}{R_2}$$

$$\text{or } V_{TH} = \frac{R_1}{R_2} \cdot (V_{REF} + 2V_\gamma)$$

By symmetry

$$V_{TL} = -\frac{R_1}{R_2} \cdot (V_{REF} + 2V_\gamma)$$

15.46

$f_0 = 5$  kHz and 50% duty cycle.

From Equation (15.88)

$$f = \frac{1}{2.2R_X C_X}$$

so

$$R_X C_X = \frac{1}{2.2(5 \times 10^3)} = 9.09 \times 10^{-5}$$

Let  $C_X = 0.01 \mu\text{F}$ . Then  $R_X = 9.09$  k $\Omega$ .

Also let  $R_1 = R_2 = 10$  k $\Omega$

15.47

Switching point occurs when

$$v_X = \left( \frac{R_1}{R_1 + R_2} \right) V_P = \left( \frac{30}{30 + 10} \right) (10)$$

$$\Rightarrow v_X = \pm 7.5 \text{ V}$$

b. Duty cycle = 50%

From Equation (15.83(a)), we can write

$$v_X = V_P + \left( -\frac{3}{4} V_P - V_P \right) e^{-t/\tau_X}$$

$$\text{At time } t = t_1 \text{ (one-half period) } v_X = \frac{3}{4} \cdot V_P$$

So

$$\frac{3}{4} \cdot V_P = V_P - \frac{7}{4} \cdot V_P e^{-t_1/\tau_X}$$

$$1 = 7e^{-t_1/\tau_X}$$

$$\text{or } t_1 = \tau_X \ln(7)$$

One period is  $T = 2\tau_X \ln(7) = 3.89\tau_X$  or the frequency is

$$f = \frac{1}{3.89R_X C_X}$$

Then

$$f = \frac{1}{(3.89)(10^4)(0.1 \times 10^{-6})} \Rightarrow \underline{f = 257 \text{ Hz}}$$

15.48

Only change from Problem (15.47) is that maximum output is  $\pm 15$  V and the  $v_X$  switching voltages are  $\pm 11.25$  V.

15.49

$$t_1 = 1.1R_X C_X = (1.1)(10^4)(0.1 \times 10^{-6})$$

$$\Rightarrow t_1 = 1.1 \text{ ms}$$

$$0 < t < t_1, v_Y = 10(1 - e^{-t/\tau_Y})$$

$$\tau_Y = R_Y C_Y = (2 \times 10^3)(0.02 \times 10^{-6})$$

$$= 4 \times 10^{-5} \text{ s}$$

$$\text{Now } \frac{t_1}{\tau_Y} = 2.75$$

$\Rightarrow C_Y$  completely charges during each cycle.

15.50

a. Switching voltage

$$v_X = \left( \frac{R_1 + R_3}{R_1 + R_3 + R_2} \right) \cdot V_P = \left( \frac{10 + 10}{10 + 10 + 10} \right) (\pm 10)$$

$$\text{So } v_X = \pm 6.667 \text{ V}$$

Using Equation (15.83(b))

$$v_X = V_P + \left( -\frac{2}{3} V_P - V_P \right) e^{-t_1/\tau_X} = \frac{2}{3} V_P$$

$$\text{Then } 1 - \frac{5}{3} \cdot e^{-t_1/\tau_X} = \frac{2}{3}$$

$$\frac{1}{3} = \frac{5}{3} \cdot e^{-t_1/\tau_X} \text{ or } t_1 = \tau_X \ln(5)$$

$$t_1 = \frac{T}{2} = \frac{1}{2f} = \frac{1}{2(500)} \Rightarrow t_1 = 0.001 \text{ s}$$

$$10^{-3} = \tau_X \ln(5) \Rightarrow \tau_X = 6.21 \times 10^{-4}$$

$$= R_X(0.01 \times 10^{-6})$$

$$\text{So } \underline{R_X = 62.1 \text{ k}\Omega}$$

b. Switching voltage

$$v_X = \left( \frac{R_1}{R_1 + R_3 + R_2} \right) (\pm V_P)$$

$$= \left( \frac{10}{10 + 10 + 10} \right) (\pm V_P) = \frac{1}{3} \cdot (\pm V_P)$$

Using Equation (15.83(b))

$$v_X = V_P + \left( -\frac{1}{3} V_P - V_P \right) e^{-t_1/\tau_X} = \frac{1}{3} V_P$$

$$\text{Then } 1 - \frac{4}{3} \cdot e^{-t_1/\tau_X} = \frac{1}{3}$$

$$\frac{2}{3} = \frac{4}{3} \cdot e^{-t_1/\tau_X}$$

$$t_1 = \tau_X \ln(2) = (6.21 \times 10^{-4}) \ln(2) = 4.30 \times 10^{-4} \text{ s}$$

$$T = 2t_1 = 8.6 \times 10^{-4} \text{ s}$$

$$f = \frac{1}{T} \Rightarrow \underline{f = 1.16 \text{ kHz}}$$

15.51

From Equation (15.92)

$$T = \tau_X \ln \left( \frac{1 + \left( \frac{V_T}{V_P} \right)}{1 - \beta} \right)$$

$$\text{where } \beta = \frac{R_1}{R_1 + R_2} = \frac{10}{10 + 25} = 0.2857$$

so

$$100 = \tau_X \ln \left[ \frac{1 + \frac{0.7}{5}}{1 - 0.2857} \right]$$

$$\text{so } \tau_X = 213.9 \mu\text{s} = R_X C_X$$

$$\text{For example, } R_X = 10 \text{ k}\Omega, C_X = 0.0214 \mu\text{F}$$

$$v_Y = \left( \frac{R_1}{R_1 + R_2} \right) V_P = \left( \frac{10}{10 + 25} \right) (5) = 1.43 \text{ V}$$

$$\text{and } v_X = 0.7 \text{ V}$$

To trigger the circuit,  $v_Y$  must be brought to a voltage less than  $v_X$ .

Therefore minimum triggering pulse is  $-0.73 \text{ V}$ .

Using Equation (15.82) for  $T < t < T'$

$$v_X = V_P + (-0.2857V_P - V_P)e^{-t'/\tau_X}$$

Recovery period is when  $v_X = V_T = 0.7 \text{ V}$ .

$$0.7 = 5 + (-6.43)e^{-t'/\tau_X}$$

$$6.43e^{-t'/\tau_X} = 4.3$$

$$\text{or } t' = \tau_X \ln(1.495)$$

$$\tau_X = 213.9 \mu\text{s}$$

so

$$t' = T' - T = 86.1 \mu\text{s}$$

15.52

From Equation (15.92), the pulse width

$$T = \tau_X \ln \left( \frac{1 + \left( \frac{V_T}{V_P} \right)}{1 - \beta} \right)$$

$$\text{where } \beta = \frac{R_1}{R_1 + R_2} = \frac{20}{20 + 20} = 0.5$$

$$\tau_X = R_X C_X = (50 \times 10^3)(0.1 \times 10^{-6}) = 5 \text{ ms}$$

$$\text{So } T = 5 \ln \left[ \frac{1 + \frac{0.7}{10}}{1 - 0.5} \right] \Rightarrow T = 3.80 \text{ ms}$$

Recovery time  $\approx 0.4\tau_X = 2 \text{ ms}$

15.53

a. From Equation (15.95)

$$T = 1.1RC$$

$$\text{For } T = 60 \text{ s} = 1.1RC$$

$$\text{then } RC = 54.55 \text{ s}$$

For example, let

$$C = 50 \mu\text{F} \text{ and } R = 1.09 \text{ M}\Omega$$

b. Recovery time: capacitor is discharged by current through the discharge transistor.

$$\text{If } V^+ = 5 \text{ V, then } I_B \approx \frac{5 - 0.7}{100} = 0.043 \text{ mA}$$

$$\text{If } \beta = 100, I_C = 4.3 \text{ mA}$$

$$V_C = \frac{1}{C} \int I_C dt = \frac{I_C}{C} \cdot t$$

$$\text{Capacitor has charged to } \frac{2}{3} \cdot V^+ = 3.33 \text{ V}$$

$$\text{So that } t = \frac{V_C \cdot C}{I_C} = \frac{(3.33)(50 \times 10^{-6})}{4.3 \times 10^{-3}}$$

$$\text{So recovery time } t \approx 38.7 \text{ ms}$$

15.54

$$T = 1.1RC$$

$$5 \times 10^{-6} = 1.1RC$$

$$\text{so } RC = 4.545 \times 10^{-6} \text{ s}$$

For example, let

$$C = 100 \text{ pF} \text{ and } R = 45.5 \text{ k}\Omega$$

From Problem (15.53), recovery time

$$t \approx \frac{V_C \cdot C}{I_C} = \frac{(3.33)(100 \times 10^{-12})}{4.3 \times 10^{-3}}$$

or

$$t = 77.4 \text{ ns}$$

15.55

From Equation (15.102),

$$f = \frac{1}{(0.693)(20 + 2(20)) \times 10^3 \times (0.1 \times 10^{-6})}$$

$$\text{or } f = 240.5 \text{ Hz}$$

$$\text{Duty cycle} = \frac{20 + 20}{20 + 2(20)} \times 100\% = 66.7\%$$

15.56

$$f = \frac{1}{(0.693)(R_A + 2R_B)C}$$

$$R_A = R_1 = 10 \text{ k}\Omega, R_B = R_2 + zR_3$$

$$\text{So } 10 \text{ k}\Omega \leq R_B \leq 110 \text{ k}\Omega$$

$$f_{\min} = \frac{1}{(0.693)(10 + 2(110)) \times 10^3 \times (0.01 \times 10^{-6})}$$

$$= 627 \text{ Hz}$$

$$f_{\max} = \frac{1}{(0.693)(10 + 2(10)) \times 10^3 \times (0.01 \times 10^{-6})}$$

$$= 4.81 \text{ kHz}$$

So  $627 \text{ Hz} \leq f \leq 4.81 \text{ kHz}$

$$\text{Duty cycle} = \frac{R_A + R_B}{R_A + 2R_B} \times 100\%$$

Now

$$\frac{10 + 10}{10 + 2(10)} \times 100\% = \underline{66.7\%}$$

and

$$\frac{10 + 110}{10 + 2(110)} \times 100\% = \underline{52.2\%}$$

So  $52.2 \leq \text{Duty cycle} \leq 66.7\%$

15.57

$$1 \text{ k}\Omega \leq R_A \leq 51 \text{ k}\Omega$$

$$1 \text{ k}\Omega \leq R_B \leq 51 \text{ k}\Omega$$

$$f_{\min} = \frac{1}{(0.693)(1 + 2(51)) \times 10^3 \times (0.01 \times 10^{-6})}$$

$$= 1.40 \text{ kHz}$$

$$f_{\max} = \frac{1}{(0.693)(51 + 2(1)) \times 10^3 \times (0.01 \times 10^{-6})}$$

$$= 2.72 \text{ kHz}$$

or  $1.40 \text{ kHz} \leq f \leq 2.72 \text{ kHz}$

$$\text{Duty cycle} = \frac{R_A + R_B}{R_A + 2R_B} \times 100\%$$

$$\frac{1 + 51}{1 + 2(51)} \times 100\% = \underline{50.5\%}$$

or

$$\frac{51 + 1}{51 + 2(1)} \times 100\% = \underline{98.1\%}$$

or  $50.5\% \leq \text{Duty cycle} \leq 98.1\%$

15.58

$$\text{a. } I_{E3} = I_{E4} = \frac{V^+ - 3V_{EB}}{R_{1A} + R_{1B}}$$

Assume  $V_{EB} = 0.7$

$$I_{E3} = I_{E4} = \frac{22 - 3(0.7)}{25 + 25} = 0.398 \text{ mA}$$

Now

$$I_{C3} = I_{C4} = I_{C5} = I_{C6} = \left(\frac{20}{21}\right)(0.398)$$

$$\underline{I_{C3} = I_{C4} = I_{C5} = I_{C6} = 0.379 \text{ mA}}$$

$$I_{C1} = I_{C2} = \frac{0.398}{21} \left(\frac{20}{21}\right) \Rightarrow \underline{I_{C1} = I_{C2} = 0.018 \text{ mA}}$$

b.  $I_D = 0.398 \text{ mA}$ , current in  $D_1$  and  $D_2$

$$V_{BB} = 2V_D = 2V_T \ln \left(\frac{I_D}{I_S}\right)$$

$$= 2(0.026) \ln \left(\frac{0.398 \times 10^{-3}}{10^{-13}}\right)$$

$$\text{or } V_{BB} = 1.149 \text{ V} = V_{BE7} + V_{BE8}$$

Now

$$I_{C7} \approx I_{C4} + I_{C9} + I_{E8}$$

$$I_{C4} = 0.379 \text{ mA}$$

$$I_{B9} = I_{C8} = \left(\frac{20}{21}\right) I_{E8}$$

So

$$I_{E8} = 1.05 I_{B9} = 1.05 \left(\frac{I_{C9}}{100}\right)$$

$$I_{C7} = I_{C4} + \left(\frac{100}{1.05}\right) I_{E8} + I_{E8}$$

$$= I_{C4} + (96.24) \left(\frac{21}{20}\right) I_{C8}$$

$$\text{So } I_{C7} = 0.379 \text{ mA} + 101 I_{C8}$$

and

$$V_{BE7} = V_T \ln \left(\frac{I_{C7}}{I_S}\right); V_{BE8} = V_T \ln \left(\frac{I_{C8}}{I_S}\right)$$

Then

$$1.149 = 0.026 \left[ \ln \left(\frac{I_{C7}}{I_S}\right) + \ln \left(\frac{I_{C8}}{I_S}\right) \right]$$

$$44.19 = \ln \left[ \frac{I_{C8}(0.379 \times 10^{-3}) + 101 I_{C8}}{(10^{-13})^2} \right]$$

$$(10^{-13})^2 \exp(44.19) = 101 I_{C8}^2 + 3.79 \times 10^{-4} I_{C8}$$

$$1.554 \times 10^{-7} = 101 I_{C8}^2 + 3.79 \times 10^{-4} I_{C8}$$

$$I_{C8} = \frac{-3.79 \times 10^{-4}}{2(101)}$$

$$\pm \frac{\sqrt{(3.79 \times 10^{-4})^2 + 4(101)(1.554 \times 10^{-7})}}{2(101)}$$

$$\underline{I_{C8} = 37.4 \mu\text{A}}$$

$$I_{C7} = 0.379 + 101(0.0374) \Rightarrow \underline{I_{C7} = 4.16 \text{ mA}}$$

$$I_{C9} = 4.16 - 0.379 - 0.0374 \left(\frac{21}{20}\right)$$

$$\underline{I_{C9} = 3.74 \text{ mA}}$$

$$\text{c. } P = (0.398 + 0.398 + 4.16)(22) \Rightarrow \underline{P = 109 \text{ mW}}$$

15.59

a. From Figure 15.47,  $3.7 \text{ W}$  to the load

b.  $V^+ \approx 19 \text{ V}$

c.  $\bar{P} = \frac{1}{2} \frac{V_P^2}{R_L}$

or

$$V_P = \sqrt{2R_L\bar{P}} = \sqrt{2(10)(3.7)} \Rightarrow V_P = 8.6 \text{ V}$$

15.60

$$\bar{P} = \frac{1}{2} \frac{V_P^2}{R_L}$$

so  $V_P = \sqrt{2R_L\bar{P}} = \sqrt{2(10)(20)} = 20 \text{ V}$

peak-to-peak output voltage

Maximum output voltage of each op-amp =  $\pm 10 \text{ V}$ . Current is  $(20/10) = 2 \text{ A}$ . Bias op-amps at  $\pm 12 \text{ V}$ .

For  $A_1$ ,  $\frac{\nu_{01}}{\nu_I} = \left(1 + \frac{R_2}{R_1}\right) = 15 \Rightarrow \frac{R_2}{R_1} = 14$

For  $A_2$ ,  $\left|\frac{\nu_{02}}{\nu_I}\right| = \frac{R_4}{R_3} = 15$

For example, let  $R_1 = R_3 = 10 \text{ k}\Omega$ , and  $R_2 = 140 \text{ k}\Omega$  and  $R_4 = 150 \text{ k}\Omega$ .

15.61

a.  $\nu_{01} = iR_2 + \nu_I$  where  $i = \frac{\nu_I}{R_1}$

Then

$$\nu_{01} = \nu_I \left(1 + \frac{R_2}{R_1}\right)$$

Now

$$\nu_{02} = -iR_3 = -\nu_I \left(\frac{R_3}{R_1}\right)$$

So

$$\nu_L = \nu_{01} - \nu_{02} = \nu_I \left(1 + \frac{R_2}{R_1}\right) - \left[-\nu_I \left(\frac{R_3}{R_1}\right)\right]$$

$$A_v = \frac{\nu_L}{\nu_I} = 1 + \frac{R_2}{R_1} + \frac{R_3}{R_1}$$

b. Want  $A_v = 10 \Rightarrow \frac{R_2}{R_1} + \frac{R_3}{R_1} = 9$

Also want  $\left(1 + \frac{R_2}{R_1}\right) = \frac{R_3}{R_1}$

Then  $\frac{R_2}{R_1} + \left(1 + \frac{R_2}{R_1}\right) = 9$  so  $\frac{R_2}{R_1} = 4$

For  $R_1 = 50 \text{ k}\Omega$ ,  $R_2 = 200 \text{ k}\Omega$ 

and

$$\frac{R_3}{R_1} = 5 \text{ so } R_3 = 250 \text{ k}\Omega$$

c.  $\bar{P} = \frac{1}{2} \frac{V_P^2}{R_L}$

or

$$V_P = \sqrt{2R_L\bar{P}} = \sqrt{2(20)(10)} = 20 \text{ V}$$

So peak values of output voltages are

$$|\nu_{01}| = |\nu_{02}| = 10 \text{ V}$$

Peak load current =  $\frac{20}{20} = 1 \text{ A}$

15.62

a.  $\nu_{01} = \left(1 + \frac{R_2}{R_1}\right) \nu_I$

$$\nu_{02} = -\frac{R_4}{R_3} \cdot \nu_{01} = -\frac{R_4}{R_3} \left(1 + \frac{R_2}{R_1}\right) \nu_I$$

$$\nu_L = \nu_{01} - \nu_{02} = \left(1 + \frac{R_2}{R_1}\right) \left(1 + \frac{R_4}{R_3}\right) \nu_I$$

so

$$A_v = \left(1 + \frac{R_2}{R_1}\right) \left(1 + \frac{R_4}{R_3}\right)$$

b. Want  $\left(1 + \frac{R_2}{R_1}\right) \nu_I = |\nu_{01}| = |\nu_{02}| \Rightarrow R_4 = R_3$

Then

$$\left(1 + \frac{R_2}{R_1}\right) (2) = 15 \Rightarrow \frac{R_2}{R_1} = 6.5$$

c.  $\bar{P} = \frac{1}{2} \cdot \frac{V_P^2}{R_L}$

or

$$V_P = \sqrt{2R_L\bar{P}} = \sqrt{2(8)(50)} = 28.3 \text{ V}$$

= peak-to-peak load voltage

Then

$$|\nu_{01}| = |\nu_{02}| = 14.15 \text{ V}$$

Load current =  $\frac{28.3}{8} = 3.54 \text{ A}$

15.63

Line regulation =  $\frac{\Delta V_0}{\Delta V^+}$

Now

$$\Delta I = \frac{\Delta V^+}{R_1} \text{ and } \Delta V_Z = r_Z \cdot \Delta I \text{ and } \Delta V_0 = 10 \Delta V_Z$$

So

$$\Delta V_0 = 10 \cdot r_Z \cdot \frac{\Delta V^+}{R_1}$$

So

Line regulation =  $\frac{\Delta V_0}{\Delta V^+} = \frac{10(15)}{9300}$

$$\Rightarrow 1.61\%$$

15.64

$$R_{of} = -\frac{\Delta V_o}{\Delta I_o}$$

$$\text{So } R_{of} = \frac{-(-10 \times 10^{-3})}{1}$$

or

$$R_{of} = 10 \text{ m}\Omega$$

15.65

For  $V_o = 8 \text{ V}$

$$V^+(\text{min}) = V_o + I_o(\text{max})R_{11} + V_{BE11} + V_{BE10} + V_{EB5}$$

This assumes  $V_{BC5} = 0$ .

Then

$$V^+(\text{min}) = 8 + (0.1)(1.9) + 0.6 + 0.6 + 0.6$$

$$V^+(\text{min}) = 9.99 \text{ V}$$

15.66

$$\text{a. } I_{C3} = I_{C5} = \frac{V_Z - 3V_{BE}(\text{nnpn})}{R_1 + R_2 + R_3}$$

$$I_{C3} = I_{C5} = \frac{6.3 - 3(0.6)}{0.576 + 3.4 + 3.9} = 0.571 \text{ mA}$$

$$I_{C8} = \frac{1}{2} \left( \frac{0.6}{2.84} \right) = 0.106 \text{ mA}$$

Neglecting current in  $Q_9$ , total collector current and emitter current in  $Q_5$  is

$$0.571 + 0.106 = 0.677$$

Now

$$I_{Z2}R_4 + V_{EB4} = V_{EB5}$$

$$V_{EB4} = V_T \ln \left( \frac{I_{Z2}}{I_S} \right)$$

$$V_{EB5} = V_T \ln \left( \frac{I_{C5}}{2I_S} \right)$$

$$\text{Then } I_{Z2}R_4 = V_T \ln \left( \frac{I_{C5}}{2I_{Z2}} \right)$$

$$R_4 = \frac{0.026}{0.25} \cdot \ln \left( \frac{0.677}{2(0.25)} \right)$$

or

$$R_4 = 31.5 \Omega$$

b. From Example 15.16,  $V_{B7} = 3.43 \text{ V}$ . Then

$$\left( \frac{R_{13}}{R_{12} + R_{13}} \right) V_o = V_{B8} = V_{B7}$$

or

$$\left( \frac{2.23}{2.23 + R_{12}} \right) (12) = 3.43$$

$$3.43(2.23 + R_{12}) = (2.23)(12)$$

which yields

$$R_{12} = 5.57 \text{ k}\Omega$$

15.67

$$\text{Line regulation} = \frac{\Delta V_o}{\Delta V^+}$$

Now

$$\Delta V_{B7} = \Delta I_{C3} \cdot R_1$$

$$\text{and } \left( \frac{R_{13}}{R_{12} + R_{13}} \right) (\Delta V_o) = \Delta V_{B7} = \Delta I_{C3} R_1$$

$$\text{and } \Delta I_{C3} = \frac{\Delta V_Z}{R_1 + R_2 + R_3} = \frac{\Delta I_Z \cdot r_Z}{R_1 + R_2 + R_3}$$

$$\text{and } \Delta I_Z = \frac{\Delta V^+}{r_o} \text{ where } r_o = \frac{V_A}{I_Z}$$

Then

$$(0.4288)(\Delta V_o) = \Delta I_{C3}(3.9)$$

$$= (3.9)\Delta I_Z \left( \frac{0.015}{7.876} \right)$$

$$r_o = \frac{50}{0.571} = 87.6 \text{ k}\Omega$$

Then

$$(0.4288)(\Delta V_o) = (0.00743) \left( \frac{\Delta V^+}{87.6} \right)$$

So

$$\frac{\Delta V_o}{\Delta V^+} = 0.0198\%$$

15.68

$$\text{a. } I_Z = \frac{25 - 5}{R_1 + r_Z} = 10$$

$$\text{So } R_1 + r_Z = \frac{20}{10} = 2 \text{ k}\Omega = R_1 + 0.01$$

$$\Rightarrow R_1 = 1.99 \text{ k}\Omega$$

b. In the ideal case;

$$\left( \frac{R_3 + R_4}{R_2 + R_3 + R_4} \right) V_o = V_Z$$

$$\left( \frac{2 + 1}{2 + 1 + 1} \right) V_o = 5 \Rightarrow V_o = 6.67 \text{ V}$$

and


$$\left( \frac{R_4}{R_2 + R_3 + R_4} \right) V_o = V_Z$$

$$\left( \frac{1}{2 + 1 + 1} \right) V_o = 5 \Rightarrow V_o = 20 \text{ V}$$

So

$$6.67 \leq V_o \leq 20 \text{ V}$$

c.

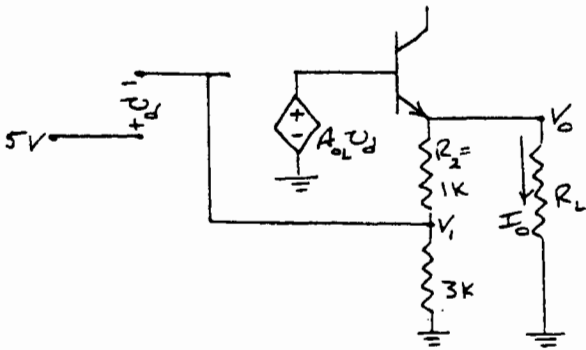

$$V_1 = \frac{3}{4} \cdot V_0 \text{ so } v_d = 5 - \frac{3}{4} \cdot V_0$$

$$\text{and } V_0 = A_{OL} v_d - V_{BE}$$

$$\text{and } V_{BE} = V_T \ln \left( \frac{I_0}{I_S} \right)$$

Now

$$V_0 = A_{OL} \left( 5 - \frac{3}{4} \cdot V_0 \right) - V_{BE}$$

$$V_0 \left( 1 + \frac{3}{4} \cdot A_{OL} \right) = 5A_{OL} - V_{BE}$$

$$V_0 = \frac{5A_{OL} - V_{BE}}{1 + \frac{3}{4} \cdot A_{OL}}$$

$$\text{Load regulation} = \frac{V_0(\text{NL}) - V_0(\text{FL})}{V_0(\text{NL})}$$

$$= \frac{\frac{5A_{OL} - V_{BE}(\text{NL})}{1 + \frac{3}{4}A_{OL}} - \frac{5A_{OL} - V_{BE}(\text{FL})}{1 + \frac{3}{4}A_{OL}}}{\frac{5A_{OL} - V_{BE}(\text{NL})}{1 + \frac{3}{4}A_{OL}}}$$

$$= \frac{V_{BE}(\text{FL}) - V_{BE}(\text{NL})}{5A_{OL} - V_{BE}(\text{NL})} = \frac{V_T \ln \left( \frac{I_0(\text{FL})}{I_0(\text{NL})} \right)}{5A_{OL} - V_{BE}(\text{NL})}$$

$$I_0(\text{FL}) = 1 \text{ A}, \quad I_0(\text{NL}) = \frac{V_0}{4 \text{ k}\Omega} = \frac{6.67}{4 \text{ k}\Omega} = 1.67 \text{ mA}$$

$$\text{Load regulation} = \frac{(0.026) \ln \left( \frac{1}{1.67 \times 10^{-3}} \right)}{5(10^4) - 0.7}$$

$$\Rightarrow 3.33 \times 10^{-4} \%$$

15.69

$$I_E = \frac{V_Z}{R_2} = \frac{5.6}{5} = 1.12 \text{ mA}$$

$$I_0 = \frac{\beta}{1 + \beta} \cdot I_E = \left( \frac{100}{101} \right) (1.12)$$

$$\Rightarrow I_0 = 1.109 \text{ mA Load current}$$

For

$$V_{BC} = 0 \Rightarrow V_0 = 20 - V_Z - 0.6$$

$$= 20 - 5.6 - 0.6$$

or

$$V_0 = 13.8 \text{ V}$$

Then

$$R_L = \frac{V_0}{I_0} = \frac{13.8}{1.109} \Rightarrow R_L = 12.4 \text{ k}\Omega$$

So

$$0 < R_L < 12.4 \text{ k}\Omega$$



## Chapter 16

## Exercise Solutions

E16.1

a. Driver in nonsaturation:

$$i_D = \frac{V_{DD} - v_O}{R_D} = \left(\frac{k'_n}{2}\right)\left(\frac{W}{L}\right) [2(v_I - V_{TN})v_O - v_O^2]$$

$$\frac{5 - (0.15)}{R_D} = \frac{35}{2}(5)[2(5 - 0.8)(0.15) - (0.15)^2]$$

$$\frac{4.85}{R_D} = 87.5[1.2375]$$

$$\Rightarrow R_D = 44.8 \text{ k}\Omega$$

b. From Equation (16-10):

$$\left(\frac{0.035}{2}\right)(5)(44.8)(V_{It} - 0.8)^2 + (V_{It} - 0.8) - 5 = 0$$

$$3.920(V_{It} - 0.8)^2 + (V_{It} - 0.8) - 5 = 0$$

$$V_{It} - 0.8 = \frac{-1 \pm \sqrt{1 + 4(3.92)(5)}}{2(3.92)}$$

$$V_{It} - 0.8 = 1.0 \Rightarrow V_{It} = 1.8 \text{ V}$$

$$V_{O1} = 1.0 \text{ V}$$

E16.2

a. i.  $v_I = 0 \Rightarrow v_O = 4 \text{ V}$ ii.  $v_I = 4 \text{ V}$ , driver in nonsaturation

$$\left(\frac{k'_n}{2}\right)\left(\frac{W}{L}\right)_L (v_{OSL} - V_{TNL})^2$$

$$= \left(\frac{k'_n}{2}\right)\left(\frac{W}{L}\right)_D [2(v_{OSD} - V_{TND})v_{OSD} - v_{OSD}^2]$$

$$2(5 - v_O - 1)^2 = (16)[2(4 - 1)v_O - v_O^2]$$

$$16 - 8v_O + v_O^2 = 8(6v_O - v_O^2)$$

$$9v_O^2 - 56v_O + 16 = 0$$

$$v_O = \frac{56 \pm \sqrt{(56)^2 - 4(9)(16)}}{2(9)}$$

$$v_O = 0.30 \text{ V}$$

b.  $P = i_D \cdot V_{DD}$ 

$$i_D = \frac{35}{2}(2)(5 - 0.30 - 1)^2 = 479 \mu\text{A}$$

$$P = (0.479)(5)$$

$$\Rightarrow P = 2.4 \text{ mW}$$

E16.3

$$P = i_D \cdot V_{DD} \Rightarrow i_D = \frac{750}{5} = 150 \mu\text{A}$$

$$150 = \frac{35}{2}\left(\frac{W}{L}\right)_L (5 - 0.2 - 0.8)^2$$

$$150 = 280\left(\frac{W}{L}\right)_L \Rightarrow \left(\frac{W}{L}\right)_L = 0.536$$

$$i_D = \left(\frac{k'_n}{2}\right)\left(\frac{W}{L}\right)_D [2(v_I - V_{TND})v_O - v_O^2]$$

$$150 = \frac{35}{2}\left(\frac{W}{L}\right)_D [2(4.2 - 0.8)(0.2) - (0.2)^2]$$

$$150 = 23.1 \cdot \left(\frac{W}{L}\right)_D \Rightarrow \left(\frac{W}{L}\right)_D = 6.49$$

E16.4

a. Load in saturation; driver in nonsaturation:

$$\left(\frac{k'_n}{2}\right)\left(\frac{W}{L}\right)_L (v_{OSL} - V_{TNL})^2$$

$$= \left(\frac{k'_n}{2}\right)\left(\frac{W}{L}\right)_D [2(v_{OSD} - V_{TND})v_{OSD} - v_{OSD}^2]$$

$$2(-[-1.5])^2 = (6)[2(5 - 0.7)v_O - v_O^2]$$

$$4.5 = 6(8.6v_O - v_O^2)$$

$$6v_O^2 - 51.6v_O + 4.5 = 0$$

$$v_O = \frac{51.6 \pm \sqrt{(51.6)^2 - 4(6)(4.5)}}{2(6)}$$

$$v_O = 0.0881 \text{ V}$$

b. Load

$$v_{O1} = V_{DD} + V_{TNL} \text{ Equation (16.26(b))}$$

$$= 5 - 1.5 \Rightarrow v_{O1} = 3.5 \text{ V}$$

From Equation (16 - 28(b)) :

$$\sqrt{\frac{K_D}{K_L}}(v_{It} - V_{TND}) = -V_{TNL}$$

$$\sqrt{\frac{6}{2}}(v_{It} - 0.7) = -(-1.5) = 1.5$$

Load:

$$v_{It} = 1.57 \text{ V}$$

$$v_{O1} = 3.5 \text{ V}$$

Driver:

$$v_{It} = 1.57 \text{ V}$$

$$v_{O1} = 0.87 \text{ V}$$

$$c. i_D = \frac{35}{2} \cdot (2)(1.5)^2 = 78.75 \mu\text{A}$$

$$P = I_D \cdot V_{DD} = (78.75)(5)$$

$$\Rightarrow P = 394 \mu\text{W}$$

E16.5

$$P = i_D \cdot V_{DD} \Rightarrow I_D = \frac{350}{5} = 70 \mu\text{A}$$

$$i_D = \left(\frac{k'_n}{2}\right) \left(\frac{W}{L}\right)_L (-V_{TNL})^2$$

$$70 = \frac{35}{2} \cdot \left(\frac{W}{L}\right)_L (2)^2 \Rightarrow \left(\frac{W}{L}\right)_L = 1$$

$$i_D = \frac{35}{2} \cdot \left(\frac{W}{L}\right)_D [2(5 - 0.8)(0.05) - (0.05)^2]$$

$$70 = 7.31 \cdot \left(\frac{W}{L}\right)_D \Rightarrow \left(\frac{W}{L}\right)_D = 9.58$$

E16.6

From Equation (16-35):

$$V_{IH} = 0.85 + \frac{5 - 0.85}{16} \cdot \left\{ \frac{1 + 2(16)}{\sqrt{1 + 3(16)}} - 1 \right\}$$

$$\Rightarrow \underline{V_{IH} = 1.81 \text{ V}}$$

Then from Equation (16-34):

$$V_{OLV} = \frac{(5 - 0.85) + 16(1.81 - 0.85)}{(1 + 2(16))}$$

$$V_{OLV} = 0.591 \text{ V}$$

$$V_{IL} = 0.85$$

$$V_{OHV} = 4.15$$

So

$$NM_L = V_{IL} - V_{OLV} = 0.85 - 0.591$$

$$\Rightarrow \underline{NM_L = 0.259 \text{ V}}$$

$$NM_H = V_{OHV} - V_{IH} = 4.15 - 1.81$$

$$\Rightarrow \underline{NM_H = 2.34 \text{ V}}$$

E16.7

From Equation (16-38):

$$V_{IL} = 1 + \frac{1.7}{\sqrt{(5)(6)}} \Rightarrow \underline{V_{IL} = 1.31 \text{ V}}$$

Then from Equation (16-37):

$$V_{OHV} = (5 - 1.7) + (5)(1.31 - 1) = 4.85 \text{ V}$$

From Equation (16-41):

$$V_{IH} = 1 + \frac{2(1.7)}{\sqrt{(3)(5)}} \Rightarrow \underline{V_{IH} = 1.88 \text{ V}}$$

Then from Equation (16-40):

$$V_{OLV} = \frac{1.88 - 1}{2} \Rightarrow V_{OLV} = 0.44 \text{ V}$$

$$NM_L = V_{IL} - V_{OLV} = 1.31 - 0.44$$

$$\Rightarrow \underline{NM_L = 0.87 \text{ V}}$$

$$NM_H = V_{OHV} - V_{IH} = 4.85 - 1.88$$

$$\Rightarrow \underline{NM_H = 2.97 \text{ V}}$$

E16.8

- a. i.  $A = \text{logic } 1 = 10 \text{ V}$ ,  $B = \text{logic } 0$   
"A" driver in nonsaturation, "B" driver off

$$\left(\frac{k'_n}{2}\right) \left(\frac{W}{L}\right)_L (-V_{TNL})^2$$

$$= \left(\frac{k'_n}{2}\right) \left(\frac{W}{L}\right)_D [2(v_i - V_{TND})V_{OL} - V_{OL}^2]$$

$$2(3)^2 = (10)[2(10 - 1.5)V_{OL} - V_{OL}^2]$$

$$9 = 5(17V_{OL} - V_{OL}^2)$$

$$5V_{OL}^2 - 85V_{OL} + 9 = 0$$

$$V_{OL} = \frac{85 \pm \sqrt{(85)^2 - 4(5)(9)}}{2(5)}$$

$$\Rightarrow \underline{V_{OL} = 0.107 \text{ V}}$$

- ii.  $A = B = \text{logic } 1$

$$\left(\frac{k'_n}{2}\right) \left(\frac{W}{L}\right)_L (-V_{TNL})^2$$

$$= 2 \left(\frac{k'_n}{2}\right) \left(\frac{W}{L}\right)_D [2(v_i - V_{TND})V_{OL} - V_{OL}^2]$$

$$2(3)^2 = (2)(10)[2(10 - 1.5)V_{OL} - V_{OL}^2]$$

$$9 = 10(17V_{OL} - V_{OL}^2)$$

$$10V_{OL}^2 - 170V_{OL} + 9 = 0$$

$$V_{OL} = \frac{170 \pm \sqrt{(170)^2 - 4(10)(9)}}{2(10)}$$

$$\Rightarrow \underline{V_{OL} = 0.0531 \text{ V}}$$

- b. Both cases.

$$i_D = \frac{35}{2} \cdot (2)(3)^2 = 315 \mu\text{A} \Rightarrow P = i_D \cdot V_{DD}$$

$$\Rightarrow \underline{P = 3.15 \text{ mW}}$$

E16.9

$$P = i_D \cdot V_{DD} \Rightarrow i_D = \frac{800}{5} = 160 \mu\text{A}$$

$$i_D = 160 = \frac{35}{2} \cdot \left(\frac{W}{L}\right)_L (1.4)^2 = 34.3 \left(\frac{W}{L}\right)_L$$

$$\Rightarrow \underline{\left(\frac{W}{L}\right)_L = 4.66}$$

$$i_D = 160 = \frac{35}{2} \cdot \left(\frac{W}{L}\right)_D [2(5 - 0.8)(0.12) - (0.12)^2]$$

$$\Rightarrow \underline{\left(\frac{W}{L}\right)_D = 9.20}$$

E16.10

$$P = i_D \cdot V_{DD} \Rightarrow i_D = \frac{800}{5} = 160 \mu\text{A}$$

$$i_D = 160 = \frac{35}{2} \cdot \left(\frac{W}{L}\right)_L (1.4)^2$$

$$\Rightarrow \underline{\left(\frac{W}{L}\right)_L = 4.66}$$

$$i_D = 160 \mu\text{A}$$

$$= \frac{35}{2} \cdot \frac{1}{3} \cdot \left(\frac{W}{L}\right)_D [2(5 - 0.8)(0.12) - (0.12)^2]$$

$$\Rightarrow \left(\frac{W}{L}\right)_D = 27.6$$

E16.11

a. From the load transistor:

$$I_{DL} = \left(\frac{k'_n}{2}\right) \left(\frac{W}{L}\right)_L (V_{GSL} - V_{TNL})^2$$

$$= \frac{35}{2} (0.5)(5 - 0.15 - 0.7)^2$$

or

$$I_{DL} = 150.7 \mu\text{A}$$

Maximum  $v_o$  occurs when either A or B is high and C is high. For the two NMOS in series, the effective  $k_N$  is cut in half, so

$$I_{DL} = \frac{1}{2} \left[ \left(\frac{k'_n}{2}\right) \left(\frac{W}{L}\right)_D \right] [2(V_{GSD} - V_{TND})V_{DS} - V_{DS}^2]$$

or

$$150.7 = \frac{1}{2} \left[ \frac{35}{2} \cdot \left(\frac{W}{L}\right)_D \right] [2(5 - 0.7)(0.15) - (0.15)^2]$$

which yields

$$\left(\frac{W}{L}\right)_D = 13.6$$

b.  $P = i_D \cdot V_{DD} = (150.7)(5) \Rightarrow P = 753 \mu\text{W}$

E16.12

a.  $v_o(\text{max})$  occurs when  $A = B = 1$  and  $C = D = 0$  or  $A = B = 0$  and  $C = D = 1$

$$\left(\frac{W}{L}\right)_L (-V_{TNL})^2 = \frac{1}{2} \cdot \left(\frac{W}{L}\right)_D [2(v_i - V_{TND})v_o - v_o^2]$$

$$(0.5)(1.2)^2 = \frac{1}{2} \cdot \left(\frac{W}{L}\right)_D [2(5 - 0.7)(0.15) - (0.15)^2]$$

$$0.72 = (0.634) \left(\frac{W}{L}\right)_D \Rightarrow \left(\frac{W}{L}\right)_D = 1.14$$

b.  $i_D = \left(\frac{k'_n}{2}\right) \left(\frac{W}{L}\right)_L (-V_{TNL})^2 = \left(\frac{35}{2}\right) (0.5)[-(1.2)]^2$

$$i_D = 12.6 \mu\text{A}$$

$$P = i_D \cdot V_{DD} = (12.6)(5) \Rightarrow P = 63 \mu\text{W}$$

E16.13

a.  $K_n/K_p = 1$

$$V_{It} = \frac{10 - 2 + (1)(2)}{1 + 1} \Rightarrow V_{It} = 5 \text{ V}$$

$$V_{OPt} = V_{It} + |V_{TP}| = 5 + 2 \Rightarrow V_{OPt} = 7 \text{ V}$$

$$V_{ONt} = V_{It} - V_{TN} = 5 - 2 \Rightarrow V_{ONt} = 3 \text{ V}$$

b.  $K_n/K_p = 0.5$

$$\Rightarrow V_{It} = \frac{10 - 2 + \sqrt{0.5}(2)}{1 + \sqrt{0.5}} \Rightarrow V_{It} = 5.52 \text{ V}$$

$$V_{OPt} = 7.52 \text{ V}$$

$$V_{ONt} = 3.52 \text{ V}$$

c.  $K_n/K_p = 2$

$$\Rightarrow V_{It} = \frac{10 - 2 + \sqrt{2}(2)}{1 + \sqrt{2}} \Rightarrow V_{It} = 4.49 \text{ V}$$

$$V_{OPt} = 6.49 \text{ V}$$

$$V_{ONt} = 2.49 \text{ V}$$

E16.14

a.  $K_n = K_p = 50 \mu\text{A}/\text{V}^2$

$$V_{It} = 2.5 \text{ V}$$

$$i_D(\text{max}) = K_n(V_{It} - V_{TN})^2 = 50(2.5 - 0.8)^2$$

$$\Rightarrow i_D(\text{max}) = 145 \mu\text{A}$$

b.  $K_n = K_p = 200 \mu\text{A}/\text{V}^2$

$$V_{It} = 2.5 \text{ V}$$

$$i_D(\text{max}) = (200)(2.5 - 0.8)^2$$

$$\Rightarrow i_D(\text{max}) = 578 \mu\text{A}$$

E16.15

$$P = f \cdot C_L \cdot V_{DD}^2$$

$$(0.10 \times 10^{-6}) = f(0.5 \times 10^{-12})(3)^2$$

$$f = 2.22 \times 10^4 \text{ Hz} \Rightarrow f = 22.2 \text{ kHz}$$

E16.16

a.  $K_n/K_p = 200/80 = 2.5$

$$\Rightarrow V_{It} = \frac{10 - 2 + \sqrt{2.5}(2)}{1 + \sqrt{2.5}} \Rightarrow V_{It} = 4.32 \text{ V}$$

$$V_{OPt} = 6.32 \text{ V}$$

$$V_{ONt} = 2.32 \text{ V}$$

b.  $V_{IL} = 2 + \frac{10 - 2 - 2}{2.5 - 1} \cdot \left[ 2\sqrt{\frac{2.5}{2.5 + 3}} - 1 \right]$

$$\Rightarrow V_{IL} = 3.39 \text{ V}$$

$$V_{OHU} = \frac{1}{2} \{ (1 + 2.5)(3.39) + 10 - (2.5)(2) + 2 \}$$

$$V_{OHU} = 9.43 \text{ V}$$

$$V_{IH} = 2 + \frac{10 - 2 - 2}{2.5 - 1} \cdot \left[ \frac{2(2.5)}{\sqrt{3(2.5) + 1}} - 1 \right]$$

$$\Rightarrow V_{IH} = 4.86 \text{ V}$$

$$V_{OLU} = \frac{(4.86)(1 + 2.5) - 10 - (2.5)(2) + 2}{2(2.5)}$$

$$V_{OLU} = 0.802 \text{ V}$$

c.  $NM_L = V_{IL} - V_{OLU} = 3.39 - 0.802$

$\Rightarrow NM_L = 2.59 \text{ V}$

$NM_H = V_{OHU} - V_{IH} = 9.43 - 4.86$

$\Rightarrow NM_H = 4.57 \text{ V}$

E16.17

a.  $V_{It} = \frac{5 - 2 + (1)(6.8)}{1 + 1}$

$V_{It} = 1.9 \text{ V}$

$V_{OPt} = 3.9 \text{ V}$

$V_{ONt} = 1.1 \text{ V}$

b.  $V_{IL} = 0.8 + \frac{3}{8} \cdot [5 - 2 - 0.8]$

$\Rightarrow V_{IL} = 1.63 \text{ V}$

$V_{OHU} = \frac{1}{2} \{2(1.63) + 5 - 0.8 + 2\}$

$V_{OHU} = 4.73 \text{ V}$

$V_{IH} = 0.8 + \frac{5}{8}(5 - 2 - 0.8)$

$\Rightarrow V_{IH} = 2.18 \text{ V}$

$V_{OLU} = \frac{1}{2} \{2(2.18) - 5 - 0.8 + 2\}$

$V_{OLU} = 0.275 \text{ V}$

c.  $NM_L = V_{IL} - V_{OLU} = 1.63 - 0.275$

$\Rightarrow NM_L = 1.35 \text{ V}$

$NM_H = V_{OHU} - V_{IH} = 4.73 - 2.18$

$\Rightarrow NM_H = 2.55 \text{ V}$

E16.18

a.  $A = 0 \Rightarrow M_{PA}$  (assume zero resistance)

$K_n = \left(\frac{k'_n}{2}\right) \left(\frac{W}{L}\right)_N$

$K_p = \left(\frac{k'_p}{2}\right) \left(\frac{W}{L}\right)_P = \frac{1}{2} \cdot \left(\frac{k'_n}{2}\right) \cdot 8 \left(\frac{W}{L}\right)_N$

$K_p = 2K_n \Rightarrow \frac{K_n}{K_p} = \frac{1}{2}$

From Equation (16-55),

$V_{It} = \frac{5 - 1 + \sqrt{0.5}(1)}{1 + \sqrt{0.5}} \Rightarrow V_{It} = 2.76 \text{ V}$

$V_{OPt} = 3.76 \text{ V}$

$V_{ONt} = 1.76 \text{ V}$

b. From Equation (16-58(b))

$i_D(\text{peak}) = K_n(V_{It} - V_{TN})^2$

$50 = \frac{35}{2} \left(\frac{W}{L}\right)_N (2.76 - 1)^2 = 54.2 \left(\frac{W}{L}\right)_N$

$\Rightarrow \left(\frac{W}{L}\right)_N = 0.923$

$\left(\frac{W}{L}\right)_P = (8)(0.923) = 7.38$

E16.19

Want  $K_{n,\text{eff}} = K_{p,\text{eff}}$

$\left(\frac{k'_n}{2}\right) \cdot \frac{1}{2} \left(\frac{W}{L}\right)_N = \left(\frac{k'_p}{2}\right) \cdot 2 \left(\frac{W}{L}\right)_P = \frac{1}{2} \cdot \frac{k'_n}{2} \cdot 2 \left(\frac{W}{L}\right)_P$

$\Rightarrow \left(\frac{W}{L}\right)_N = 2 \left(\frac{W}{L}\right)_P$

E16.20

Want  $K_{n,\text{eff}} = K_{p,\text{eff}}$

$\left(\frac{k'_n}{2}\right) \cdot 3 \left(\frac{W}{L}\right)_N = \left(\frac{k'_p}{2}\right) \cdot \frac{1}{3} \left(\frac{W}{L}\right)_P = \frac{1}{2} \cdot \frac{k'_n}{2} \cdot \frac{1}{3} \left(\frac{W}{L}\right)_P$

$3 \left(\frac{W}{L}\right)_N = \frac{1}{6} \cdot \left(\frac{W}{L}\right)_P$

Or

$\Rightarrow \frac{(W/L)_P}{(W/L)_N} = 18$

E16.21

Want  $K_{n,\text{eff}} = K_{p,\text{eff}}$

$\left(\frac{k'_n}{2}\right) \cdot \frac{1}{3} \left(\frac{W}{L}\right)_N = \left(\frac{k'_p}{2}\right) \cdot 3 \left(\frac{W}{L}\right)_P = \frac{1}{2} \cdot \frac{k'_n}{2} \cdot 3 \left(\frac{W}{L}\right)_P$

$\frac{1}{3} \left(\frac{W}{L}\right)_N = \frac{3}{2} \cdot \left(\frac{W}{L}\right)_P$

Or

$\Rightarrow \frac{(W/L)_P}{(W/L)_N} = \frac{2}{9}$

E16.22

NMOS:

$M_{NA}, M_{NB}$  in series  $\Rightarrow \left(\frac{W}{L}\right) = 2$

$M_{ND}, M_{NE}$  in parallel  $\Rightarrow \left(\frac{W}{L}\right) = 1$

$M_{NC}$  in series with  $M_{ND} \parallel M_{NE} \Rightarrow \left(\frac{W}{L}\right) = 2$

Effective composite  $\left(\frac{W}{L}\right) = 1$  for each side.

PMOS:


Want the effective composite  $\left(\frac{W}{L}\right)$  of each side to be 2.

$$M_{PA}, M_{PC} \text{ in series} \Rightarrow \left(\frac{W}{L}\right) = 4$$

$$M_{PA}, M_{PB} \text{ in parallel} \Rightarrow \left(\frac{W}{L}\right)_B = 4$$


$$M_{PD}, M_{PE} \text{ in series} \Rightarrow \left(\frac{W}{L}\right) = 8$$

E16.23

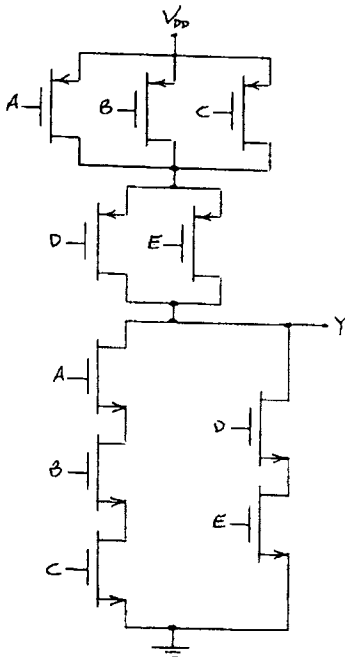


E16.24

The NMOS part of the circuit is:

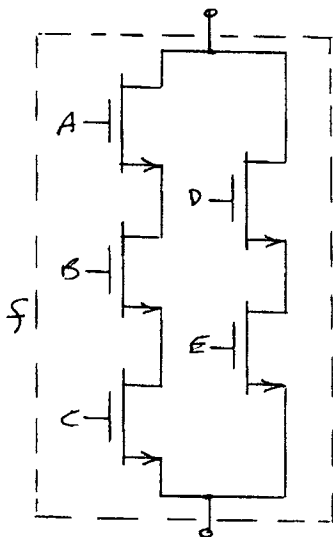

E16.25

The NMOS part of the circuit is:

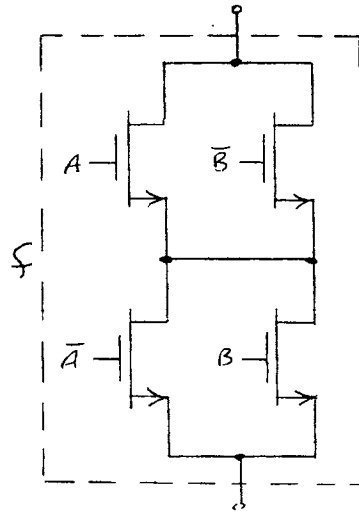

E16.26

- a.  $v_I = \phi = 5 \text{ V} \Rightarrow v_O = 4 \text{ V}$
- b.  $v_I = 3 \text{ V}, \phi = 5 \text{ V} \Rightarrow v_O = 3 \text{ V}$
- c.  $v_I = 4.2 \text{ V}, \phi = 5 \text{ V} \Rightarrow v_O = 4 \text{ V}$
- d.  $v_I = 5 \text{ V}, \phi = 3 \text{ V} \Rightarrow v_O = 2 \text{ V}$

E16.27

(a)  $v_I = 8 \text{ V}, \phi = 10 \text{ V} \Rightarrow v_{GSD} = 8 \text{ V}$

$M_D$  in nonsaturation

$$K_D [2(v_{GSD} - V_{TND})v_O - v_O^2]$$

$$K_L [V_{DD} - v_O - V_{TNL}]^2$$

$$\frac{K_D}{K_L} [2(8-2)(0.5) - (0.5)^2] = [10 - 0.5 - 2]^2$$

$$\Rightarrow \frac{K_D}{K_L} = 9.78$$

(b)  $v_I = \phi = 8 \text{ V} \Rightarrow v_{GSD} = 6 \text{ V}$


$$\frac{K_D}{K_L} [2(6-2)(0.5) - (0.5)^2] = [10 - 0.5 - 2]^2$$

$$\Rightarrow \frac{K_D}{K_L} = 15$$


E16.28

Exclusive-OR

A	B	f
0	0	0
1	0	1
0	1	1
1	1	0

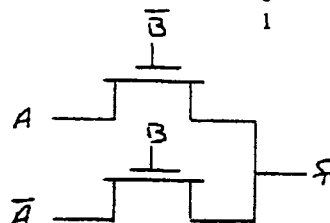

E16.29

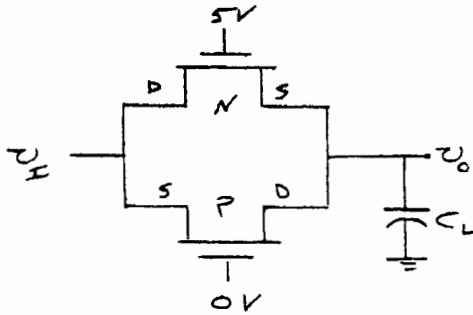

NMOS conducting for  $0 \leq v_i \leq 4.2 \text{ V}$


⇒ NMOS Conducting:  $0 \leq t \leq 8.4 \text{ s}$

NMOS Cutoff:  $8.4 \leq t \leq 10 \text{ s}$

PMOS cutoff for  $0 \leq v_i \leq 1.2 \text{ V}$

⇒ PMOS Cutoff:  $0 \leq t \leq 2.4 \text{ s}$

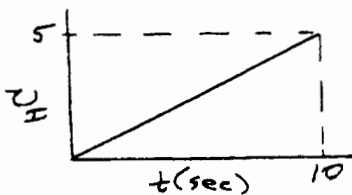PMOS Conducting:  $2.4 \leq t \leq 10 \text{ s}$



E16.30

(a)  $1 \text{ K} \Rightarrow 32 \times 32$  array

Each row and column requires a 5-bit word  $\Rightarrow$   
6 transistors per row and column,  $\Rightarrow$   
 $32 \times 6 + 32 \times 6 = 384$  transistors plus buffer  
transistors.

(b)  $4 \text{ K} \Rightarrow 64 \times 64$  array

Each row and column requires a 6-bit word  $\Rightarrow$   
7 transistors per row and column  $\Rightarrow$   
 $64 \times 7 + 64 \times 7 = 896$  transistors plus buffer  
transistors.

(c)  $16 \text{ K} \Rightarrow 128 \times 128$  array

Each row and column requires a 7-bit word  $\Rightarrow$   
8 transistors per row and column  $\Rightarrow$   
 $128 \times 8 + 128 \times 8 = 2048$  transistors plus buffer  
transistors.

E16.31

$16 \text{ K} \Rightarrow 16384$  cells

Total Power =  $125 \text{ mW} = (2.5)I_T$

$\Rightarrow I_T = 50 \text{ mA}$

Then, for each cell,  $I = \frac{50 \text{ mA}}{16384} \Rightarrow I = 3.05 \mu\text{A}$

Now,  $I \cong \frac{V_{DD}}{R}$  or  $R = \frac{V_{DD}}{I} = \frac{2.5}{3.05} \Rightarrow$

$R = 0.82 \text{ M}\Omega$

E16.32

From Equation (16.93)

$$\frac{(W/L)_{n1}}{(W/L)_{n2}} = \frac{2(V_{DD}V_{TN}) - 3V_{TN}^2}{(V_{DD} - 2V_{TN})^2}$$

$$= \frac{2(2.5)(0.4) - 3(0.4)^2}{(2.5 - 2(0.4))^2} = 0.526$$

From Equation (16.95)

$$\frac{(W/L)_p}{(W/L)_{nb}} = \frac{k'_n \cdot 2(V_{DD}V_{TN}) - 3V_{TN}^2}{k'_p \cdot (V_{DD} + V_{TP})^2}$$

$$= (2.5) \left[ \frac{2(2.5)(0.4) - 3(0.4)^2}{(2.5 - 0.4)^2} \right] = 1.31$$

So  $\left(\frac{W}{L}\right)$  of transmission gate device must be

$< 0.526$  times the  $\left(\frac{W}{L}\right)$  of the NMOS transistors in

the inverter cell. The  $\left(\frac{W}{L}\right)$  of the PMOS transistors

must be  $< 1.31$  times the  $\left(\frac{W}{L}\right)$  of the transmission

gate devices. Then the  $\left(\frac{W}{L}\right)$  of the PMOS devices

must be  $< 0.689$  times  $\left(\frac{W}{L}\right)$  of NMOS devices in  
cell.

E16.33

Initial voltage across the storage capacitor

$$= V_{DD} - V_{TN} = 3 - 0.5 = 2.5 \text{ V}.$$

Now

$$-I = C \frac{dV}{dt} \text{ or } V = -\frac{I}{C} \cdot t + K$$

where  $K = 2.5 \text{ V}$ ,  $t = 1.5 \text{ ms}$ ,  $V = \frac{2.5}{2} = 1.25 \text{ V}$ , and

$C = 0.05 \text{ pF}$ . Then

$$1.25 = 2.5 - \frac{I(15 \times 10^{-3})}{(0.05 \times 10^{-12})} \Rightarrow$$

$$\underline{I = 4.17 \times 10^{-11} \text{ A} \Rightarrow I = 41.7 \text{ pA}}$$

## Chapter 16

### Problem Solutions

16.1

$$(a) \Delta V_{TN} = \frac{\sqrt{2e \epsilon_i N_a}}{C_{ox}} \left[ \sqrt{2\phi_{fp} + V_{SB}} - \sqrt{2\phi_{fp}} \right]$$

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = \frac{(3.9)(8.85 \times 10^{-14})}{450 \times 10^{-8}} = 7.67 \times 10^{-8}$$

$$\begin{aligned} & \sqrt{2e \epsilon_i N_a} \\ &= \left[ 2(1.6 \times 10^{-19})(11.7)(8.85 \times 10^{-14})(8 \times 10^{15}) \right]^{1/2} \\ &= 5.15 \times 10^{-8} \end{aligned}$$

Then

$$\Delta V_{TN} = \frac{5.15 \times 10^{-8}}{7.67 \times 10^{-8}} \left[ \sqrt{2(0.343) + V_{SB}} - \sqrt{2(0.343)} \right]$$

 For  $V_{SB} = 1V$ :

$$\Delta V_{TN} = 0.671 \left[ \sqrt{1.686} - \sqrt{0.686} \right] \Rightarrow \Delta V_{TN} = 0.316V$$

 For  $V_{SB} = 2V$ :

$$\Delta V_{TN} = 0.671 \left[ \sqrt{2.686} - \sqrt{0.686} \right] \Rightarrow \Delta V_{TN} = 0.544V$$

 (b) For  $V_{GS} = 2.5V$ ,  $V_{DS} = 5V$ , transistor biased in the saturation region.

$$I_D = K_n (V_{GS} - V_{TN})^2$$

 For  $V_{SB} = 0$ ,

$$I_D = 0.2(2.5 - 0.8)^2 = 0.578 \text{ mA}$$

 For  $V_{SB} = 1$ ,

$$I_D = 0.2(2.5 - [0.8 + 0.316])^2 = 0.383 \text{ mA}$$

 For  $V_{SB} = 2$ ,

$$I_D = 0.2(2.5 - [0.8 + 0.544])^2 = 0.267 \text{ mA}$$

16.2

$$(a) I_D = \frac{V_{DD} - v_o}{R_D} = K_n [2(V_{GS} - V_{TN})v_o - v_o^2]$$

$$\frac{5 - (0.1)}{40 \times 10^3} = K_n [2(5 - 0.8)(0.1) - (0.1)^2]$$

$$\text{or } K_n = 1.476 \times 10^{-4} \text{ A/V}^2 = \frac{8 \times 10^{-5}}{2} \left( \frac{W}{L} \right)$$

$$\text{So that } \left( \frac{W}{L} \right) = 3.69$$

b. From Equation (16.10),

$$K_n R_D [V_{It} - V_{TN}]^2 + [V_{It} - V_{TN}] - V_{DD} = 0$$

$$(0.1476)(40)[V_{It} - 0.8]^2 + [V_{It} - 0.8] - 5 = 0$$

$$\text{or } [V_{It} - 0.8] = \frac{-1 \pm \sqrt{(1)^2 + 4(0.1476)(40)(5)}}{2(0.1476)(40)}$$

$$\text{or } [V_{It} - 0.8] = 0.839$$

 So that  $V_{It} = 1.64V$ 

$$P = I_D(\text{max}) \cdot V_{DD}$$

$$\text{and } I_D(\text{max}) = \frac{5 - (0.1)}{40} = 0.1225 \text{ mA}$$

$$\text{or } P = 0.6125 \text{ mW}$$

16.3

a. From Equation (16.10), the transistor point is found from

$$K_n R_D (V_{It} - V_{TN})^2 + (V_{It} - V_{TN}) - V_{DD} = 0$$

$$K_n = 50 \mu\text{A/V}^2, R_D = 20 \text{ k}\Omega, V_{TN} = 0.8V$$

$$(0.05)(20)(V_{It} - V_{TN})^2 + (V_{It} - V_{TN}) - 5 = 0$$

$$V_{It} - V_{TN} = \frac{-1 \pm \sqrt{1 + 4(0.05)(20)(5)}}{2(0.05)(20)}$$

$$= 1.79V \text{ So } V_{It} = 2.59V$$

$$V_{o1} = 1.79V$$

 Output voltage for  $v_i = 5V$  is determined from Equation (16.12):

$$v_o = 5 - (0.05)(20)[2(5 - 0.8)v_o - v_o^2]$$

$$v_o^2 - 9.4v_o + 5 = 0$$

$$\text{So } v_o = \frac{9.4 \pm \sqrt{(9.4)^2 - 4(1)(5)}}{2(1)} = 0.566V$$

 b. For  $R_D = 200 \text{ k}\Omega$ ,

$$(V_{It} - V_{TN}) = \frac{-1 \pm \sqrt{1 + 4(0.05)(200)(5)}}{2(0.05)(200)}$$


$$= 0.659V \text{ So } V_{It} = 1.46V$$

$$V_{o1} = 0.659V$$

$$v_o = 5 - (0.05)(200)[2(5 - 0.8)v_o - v_o^2]$$

$$\text{or } 10v_o^2 - 85v_o + 5 = 0$$
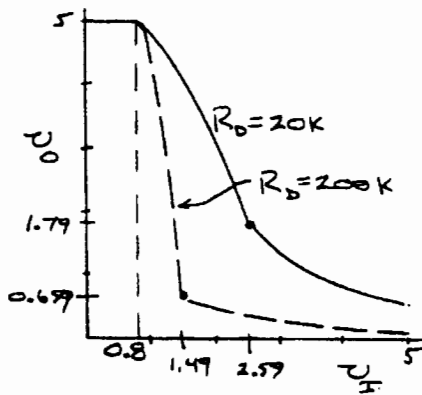
$$v_o = \frac{85 \pm \sqrt{(85)^2 - 4(10)(5)}}{2(10)} = 0.0592V$$



16.4

$$P = i_D \cdot V_{DD}$$

$$1 = i_D(5) \Rightarrow i_D = 0.2 \text{ mA}$$

Now

$$i_D = K_n [2(v_i - V_{TN})v_o - v_o^2]$$

$$0.2 = K_n [2(5 - 0.8)(0.2) - (0.2)^2]$$

$$\text{or } K_n = 0.122 \text{ mA/V}^2 = \left(\frac{0.080}{2}\right) \left(\frac{W}{L}\right) \Rightarrow$$

$$\left(\frac{W}{L}\right) = 3.05$$

Also

$$v_o = V_{DD} - K_n R_D [2(v_i - V_{TN})v_o - v_o^2]$$

$$0.2 = 5 - (0.122)R_D [2(5 - 0.8)(0.2) - (0.2)^2] \Rightarrow$$

$$R_D = 24 \text{ k}\Omega$$

16.5

From Equation (16.21) :

$$V_{It} = \frac{10 - 2 + 2 \left(1 + \sqrt{\frac{200}{50}}\right)}{1 + \sqrt{\frac{200}{50}}}$$

$$\text{or } V_{It} = 4.67 \text{ V}$$

$$V_{Ox} = V_{It} - V_{TND} = 4.67 - 2 \Rightarrow V_{Ox} = 2.67 \text{ V}$$

From Equation (16.23):

$$200 [2(8 - 2)v_o - v_o^2] = 50 [10 - v_o - 2]^2$$

$$4 [12v_o - v_o^2] = [8 - v_o]^2 = [64 - 16v_o + v_o^2]$$

$$5v_o^2 - 64v_o + 64 = 0$$

$$v_o = \frac{64 \pm \sqrt{(64)^2 - 4(5)(64)}}{2(5)}$$

$$\text{or } v_o = 1.09 \text{ V}$$

16.6

(a) From Equation (16.23)

$$\frac{K_D}{K_L} [2(3 - 0.5)(0.25) - (0.25)^2] = (3 - 0.25 - 0.5)^2$$

$$\Rightarrow \frac{K_D}{K_L} = 4.26$$

$$(b) \frac{K_D}{K_L} [2(2.5 - 0.5)(0.25) - (0.25)^2] = (3 - 0.25 - 0.5)^2$$

$$\Rightarrow \frac{K_D}{K_L} = 5.06$$

$$(c) i_D = K_L (V_{GS} - V_{TNL})^2 = K_L (V_{DD} - v_o - V_{TNL})^2$$

$$= \left(\frac{0.080}{2}\right) (1)(3 - 0.25 - 0.5)^2 \Rightarrow$$

$$i_D = 0.203 \text{ mA}$$

$$P = i_D \cdot V_{DD} = (0.203)(3) \Rightarrow P = 0.608 \text{ mW}$$

for both parts (a) and (b).

16.7

$$(a) P = 0.4 \text{ mW} = i_D \cdot V_{DD} = i_D(3) \Rightarrow$$

$$i_D = 0.133 \text{ mA}$$

$$i_D = K_L (V_{DD} - v_o - V_{TNL})^2$$

$$0.133 = \left(\frac{0.080}{2}\right) \left(\frac{W}{L}\right)_L (3 - 0.1 - 0.5)^2 = (0.2304) \left(\frac{W}{L}\right)_L$$

$$\text{So } \left(\frac{W}{L}\right)_L = 0.577$$

$$\frac{K_D}{K_L} [2(2.5 - 0.5)(0.1) - (0.1)^2] = (3 - 0.1 - 0.5)^2$$

$$\Rightarrow \frac{K_D}{K_L} = 14.8 \text{ so that } \left(\frac{W}{L}\right)_D = 8.54$$

$$V_{It} = \frac{3 - 0.5 + 0.5(1 + \sqrt{14.8})}{1 + \sqrt{14.8}}$$

or

$$V_{It} = 1.02 \text{ V}, V_{Ox} = 0.52 \text{ V}$$

$$(b) NM_L = V_{IL} - V_{OLU}$$

$$NM_H = V_{OHU} - V_{IH}$$

From Equation (16.35)

$$V_{IH} = 0.5 + \frac{(3 - 0.5)}{14.8} \left\{ \frac{(1 + 2(14.8))}{\sqrt{1 + 3(14.8)}} - 1 \right\} \Rightarrow$$

$$V_{IH} = 1.10 \text{ V}$$

$$V_{OHU} = 3.0 - 0.5 = 2.5 \text{ V}$$

$$NM_H = V_{OHU} - V_{IH} = 2.5 - 1.10 \Rightarrow NM_H = 1.40 \text{ V}$$

$$V_{IL} = V_{TND} = 0.5 \text{ V}$$

$$V_{OLU} = \frac{(V_{DD} - V_{TNL}) + \frac{K_D}{K_L}(V_i - V_{TND})}{1 + 2\left(\frac{K_D}{K_L}\right)}$$

$$= \frac{(3 - 0.5) + 14.8(1.1 - 0.5)}{1 + 2(14.8)} \Rightarrow$$

$$V_{OLU} = 0.372 V$$

$$\text{Then } NM_L = V_{IL} - V_{OLU} = 0.5 - 0.372 \Rightarrow$$

$$NM_L = 0.128 V$$

16.8

We have

$$\frac{K_D}{K_L} [2(v_i - V_{TND})v_o - v_o^2] = (V_{DD} - v_o - V_{TNL})^2$$

$$\frac{(W/L)_D}{(W/L)_L} [2(V_{DD} - V_{TN} - V_{TN})(0.08V_{DD}) - (0.08V_{DD})^2]$$

$$= (V_{DD} - 0.08V_{DD} - V_{TN})^2$$

$$\frac{(W/L)_D}{(W/L)_L} [2(V_{DD} - 2(0.2)V_{DD})(0.08V_{DD}) - 0.0064V_{DD}^2]$$

$$= [(0.92 - 0.2)V_{DD}]^2 = 0.5184V_{DD}^2$$

$$\frac{(W/L)_D}{(W/L)_L} [0.096] = 0.5184 \Rightarrow \frac{(W/L)_D}{(W/L)_L} = 5.4$$

16.9

$$V_{OH} = V_B - V_{GS} = \text{Logic 1}$$

So

$$(a) V_B = 4V \Rightarrow V_{OH} = 3V$$

$$(b) V_B = 5V \Rightarrow V_{OH} = 4V$$

$$(c) V_B = 6V \Rightarrow V_{OH} = 5V$$

$$(d) V_B = 7V \Rightarrow V_{OH} = 6V$$

 For  $v_i = V_{OH}$ 

$$K_D [2(v_i - V_T)v_o - v_o^2] = K_L [V_B - v_o - V_T]^2$$

Then

$$(a) (1) [2(3-1)V_{OL} - V_{OL}^2] = (0.4) [4 - V_{OL} - 1]^2 \Rightarrow$$

$$V_{OL} = 0.657 V$$

$$(b) (1) [2(4-1)V_{OL} - V_{OL}^2] = (0.4) [5 - V_{OL} - 1]^2 \Rightarrow$$

$$V_{OL} = 0.791 V$$

$$(c) (1) [2(5-1)V_{OL} - V_{OL}^2] = (0.4) [6 - V_{OL} - 1]^2 \Rightarrow$$

$$V_{OL} = 0.935 V$$

$$(d) (1) [2(6-1)V_{OL} - V_{OL}^2] = (0.4) [7 - V_{OL} - 1]^2 \Rightarrow$$

$$V_{OL} = 1.08 V$$

16.10

 a. For load  $V_{OL} = V_{DD} + V_{TNL} = 5 - 2 = 3V$ 

$$\sqrt{\frac{K_D}{K_L}} (V_H - V_{TND}) = -V_{TNL}$$

$$\sqrt{\frac{500}{100}} (V_{It} - 0.8) = -(-2)$$

$$\Rightarrow V_{It} = 1.69 V$$

$$V_{Ot} = 3 V \quad \left. \vphantom{V_{It}} \right\} \text{Load}$$

 Driver:  $V_{OL} = V_H - V_{TND} = 1.69 - 0.8 = 0.89 V$ 

$$V_{It} = 1.69 V$$

$$V_{Ot} = 0.89 V \quad \left. \vphantom{V_{It}} \right\} \text{Driver}$$

b. From Equation (16.29(b)):

$$\frac{500}{100} [2(5 - 0.8)v_o - v_o^2] = [ -(-2) ]^2$$

$$5v_o^2 - 42v_o + 4 = 0$$

$$v_o = \frac{42 \pm \sqrt{(42)^2 - 4(5)(4)}}{2(5)} \Rightarrow v_o = 0.0963 V$$

 c.  $i_D = K_L (-V_{TNL})^2 = 100 [ -(-2) ]^2 \Rightarrow$ 

$$i_D = 400 \mu A$$

16.11

$$\left(\frac{500}{50}\right) [2(3 - 0.5)(0.1) - (0.1)^2] = (-V_{TNL})^2$$

So

$$(-V_{TNL})^2 = 4.9 \Rightarrow V_{TNL} = -2.21 V$$

16.12

 (a)  $P = i_D \cdot V_{DD}$ 

$$150 = i_D \cdot (3) \Rightarrow i_D = 50 \mu A$$

$$i_D = K_L (-V_{TNL})^2$$

$$50 = \left(\frac{80}{2}\right) \left(\frac{W}{L}\right)_L [ -(-1) ]^2 \Rightarrow \left(\frac{W}{L}\right)_L = 1.25$$

$$\frac{K_D}{K_L} [2(3 - 0.5)(0.1) - (0.1)^2] = [ -(-1) ]^2$$

$$\frac{K_D}{K_L} = \frac{(W/L)_D}{(W/L)_L} = 2.04 \Rightarrow \left(\frac{W}{L}\right)_D = 2.55$$

For the Load:

$$V_{OL} = V_{DD} + V_{TNL} = 3 - 1 \Rightarrow V_{OL} = 2V$$

$$\sqrt{2.04}(V_H - 0.5) = [ -(-1) ] \Rightarrow V_H = 1.20 V$$

For the Driver:

$$V_{OL} = V_H - V_{TND} = 1.20 - 0.5 \Rightarrow V_{OL} = 0.70 V$$

$$V_H = 1.20 V$$

(b)  $NM_L = V_{IL} - V_{OLU}$   
 $NM_H = V_{OHU} - V_{IH}$

$$V_{IL} = 0.5 + \frac{[-(-1)]}{\sqrt{(2.04)(1+2.04)}} = 0.902 V$$

$$V_{IH} = 0.5 + \frac{2[-(-1)]}{\sqrt{3(2.04)}} = 1.31 V$$

Then  $V_{OHU} = (3-1) + (2.04)(0.902-0.5) = 2.82 V$

$$V_{OLU} = \frac{(1.31-0.5)}{2} = 0.405 V$$

$$NM_L = 0.902 - 0.405 \Rightarrow NM_L = 0.497 V$$

$$NM_H = 2.82 - 1.31 \Rightarrow NM_H = 1.51 V$$

16.13

a. From Equation (16.29(b)):

$$\left(\frac{W}{L}\right)_D [2(2.5-0.5)(0.05) - (0.05)^2]$$

$$= \left(\frac{W}{L}\right)_L [-(-1)]^2$$

$$\left(\frac{W}{L}\right)_L = 1$$

Then  $\left(\frac{W}{L}\right)_D = 5.06$

b.  $i_D = \left(\frac{80}{2}\right)(1)[-(-1)]^2$

or  $i_D = 40 \mu A$

$$P = i_D \cdot V_{DD} = (40)(2.5)$$

$$\Rightarrow P = 100 \mu W$$

16.14

a. i.  $v_I = 0.5 V \Rightarrow i_D = 0 \Rightarrow P = 0$

ii.  $v_I = 5 V$ , From Equation (16.12),

$$v_0 = 5 - (0.1)(20)[2(5-1.5)v_0 - v_0^2]$$

$$2v_0^2 - 15v_0 + 5 = 0$$

$$v_0 = \frac{15 \pm \sqrt{(15)^2 - 4(2)(5)}}{2(2)} \Rightarrow v_0 = 0.35 V$$

$$i_D = \frac{5-0.35}{20} = 0.2325 mA$$

$$P = i_D \cdot V_{DD} = (0.2325)(5) \Rightarrow P = 1.16 mW$$

b. i.  $v_I = 0.25 V \Rightarrow i_D = 0 \Rightarrow P = 0$

ii.  $v_I = 4.3 V$ , From Equation (16.23),

$$100[2(4.3-0.7)v_0 - v_0^2] = 10[5-v_0-0.7]^2$$

$$10[7.2v_0 - v_0^2] = 18.49 - 8.6v_0 + v_0^2$$

Then

$$11v_0^2 - 80.6v_0 + 18.49 = 0$$

$$v_0 = \frac{80.6 \pm \sqrt{(80.6)^2 - 4(11)(18.49)}}{2(11)}$$

$$\Rightarrow v_0 = 0.237 V$$

Then

$$i_D = 10[5 - 0.237 - 0.7]^2 = 165 \mu A$$

$$P = i_D \cdot V_{DD} = (165)(5) \Rightarrow P = 825 \mu W$$

c. i.  $v_I = 0.03 V \Rightarrow i_D = 0 \Rightarrow P = 0$

ii.  $v_I = 5 V$

$$i_D = K_L(-V_{TN})^2 = (10)[-(-2)]^2 = 40 \mu A$$

$$P = i_D \cdot V_{DD} = (40)(5) \Rightarrow P = 200 \mu W$$

16.15

From Equation (16.35)

$$V_{IH} = 0.8 + \frac{5-(0.8)}{10} \cdot \left\{ \frac{1+2(10)}{\sqrt{1+3(10)}} - 1 \right\}$$

$$V_{IH} = 0.8 + 0.42 \cdot \left\{ \frac{21}{5.57} - 1 \right\}$$

or

$$V_{IH} = 1.96 V$$

$M_{D2}$  in non-saturation region. Then

$$K_D[2(v_{GS2} - V_{TN})v_{DS2} - v_{DS2}^2]$$

$$= K_L[V_{DD} - v_{O2} - V_{TN}]^2$$

$$v_{DS2} = v_{O2} \text{ and } v_{GS2} = V_{IH} = 1.96$$

$$10[2(1.96-0.8)v_{O2} - v_{O2}^2] = [5-v_{O2}-0.8]^2$$

$$23.2v_{O2} - 10v_{O2}^2 = 17.64 - 8.4v_{O2} + v_{O2}^2$$

or

$$11v_{O2}^2 - 31.6v_{O2} + 17.64 = 0$$

$$v_{O2} = \frac{31.6 \pm \sqrt{(31.6)^2 - 4(11)(17.64)}}{2(11)}$$

$$\Rightarrow v_{O2} = 0.758 V$$

Now  $M_{D1}$  in saturation region. Then

$$K_D [v_I - V_{TN}]^2 = K_L [V_{DD} - v_{O1} - V_{TN}]^2$$

$$\sqrt{10} \cdot (v_I - 0.8) = 5 - 1.96 - 0.8 = 2.24$$

Then  $v_I = 1.51$  V

16.16

a. From Equation (16.41),

$$V_{IH} = 0.8 + \frac{2[-(-2)]}{\sqrt{3(4)}} \Rightarrow V_{IH} = 1.95 \text{ V} = v_{O1}$$

$M_{D2}$  in non-saturation and  $M_{L2}$  in saturation.

$$K_D [2(v_{O1} - V_{TND})v_{O2} - v_{O2}^2] = K_L (-V_{TNL})^2$$

$$4[2(1.95 - 0.8)v_{O2} - v_{O2}^2] = (1)[-(-2)]^2$$

$$4v_{O2}^2 - 9.2v_{O2} + 4 = 0$$

$$v_{O2} = \frac{9.2 \pm \sqrt{(9.2)^2 - 4(4)(4)}}{2(4)} \Rightarrow v_{O2} = 0.582 \text{ V}$$

Both  $M_{D1}$  and  $M_{L1}$  in saturation region. From Equation (16.28(b)),

$$\sqrt{4} \cdot (v_I - 0.8) = -(-2)$$

or  $v_I = 1.8$  V

b.  $V_{IL} = 0.8 + \frac{(+2)}{\sqrt{4(1+4)}} = 1.25 \text{ V} = v_{O1}$

$M_{D2}$  in saturation,  $M_{L2}$  in non-saturation

$$K_D [v_{O1} - V_{TND}]^2 = K_L [2(-V_{TNL})(5 - v_{O2}) - (5 - v_{O2})^2]$$

$$4(1.25 - 0.8)^2 = 2(2)(5 - v_{O2}) - (5 - v_{O2})^2$$

$$(5 - v_{O2})^2 - 4(5 - v_{O2}) + 0.81 = 0$$

$$5 - v_{O2} = \frac{4 \pm \sqrt{(4)^2 - 4(1)(0.81)}}{2(1)} = 0.214 \text{ V}$$

so

$$v_{O2} = 4.786 \text{ V}$$

To find  $v_I$ :

$$4(v_{O1} - 0.8)^2 = (1)(-(-2))^2$$

$$v_{O1} - 0.8 = 1$$

$$v_{O1} = 1.8 \text{ V}$$

c.  $V_{IH} = 1.95$  V,  $V_{IL} = 1.25$  V

16.17

a. i. Neglecting the body effect,

$$v_0 = V_{DD} - V_{Th}$$

Assume  $V_{DD} = 5$  V, then  $v_0 = 4.2$  V

ii. Taking the body effect into account:  
From Problem 16.1,

$$V_{TN} = V_{TN0} + 0.671[\sqrt{0.686 + V_{SB}} - \sqrt{0.686}]$$

and  $V_{SB} = v_0$

Then

$$v_0 = 5 - [0.8 + 0.671(\sqrt{0.686 + v_0} - \sqrt{0.686})]$$

$$v_0 = 4.756 - 0.671\sqrt{0.686 + v_0}$$

$$0.671\sqrt{0.686 + v_0} = 4.756 - v_0$$

$$0.450(0.686 + v_0) = 22.62 - 9.51v_0 + v_0^2$$

$$v_0^2 - 9.96v_0 + 22.3 = 0$$

$$v_0 = \frac{9.96 \pm \sqrt{(9.96)^2 - 4(22.3)}}{2} \Rightarrow v_0 = 3.40 \text{ V}$$

b. PSpice results similar to Figure 16.18(a).

16.18

Results similar to Figure 16.18(b).

16.19

a.  $M_X$  on,  $M_Y$  cutoff.

From Equation (16.29(b)):

$$\frac{K_D}{K_L} [2(5 - 0.8)(0.2) - (0.2)^2] = [-(-2)]^2$$

or  $\frac{K_D}{K_L} = 2.44$

b. For  $v_X = v_Y = 5$  V

$$2(2.44)[2(5 - 0.8)v_0 - v_0^2] = [-(-2)]^2$$

$$4.88v_0^2 - 41.0v_0 + 4 = 0$$

$$v_0 = \frac{41 \pm \sqrt{(41)^2 - 4(4.88)(4)}}{2(4.88)}$$

or

$$v_0 = 0.0987 \text{ V}$$

c.  $i_D = \left(\frac{80}{2}\right)(1)[-(-2)]^2 = 160 \mu\text{A}$

$$P = (160)(5) \Rightarrow P = 800 \mu\text{W}$$

for both parts (a) and (b).

16.20

(a) Maximum value of  $v_o$  in low state- when only one input is high, then,

$$\frac{K_D}{K_L} [2(3-0.5)(0.1) - (0.1)^2] = [ -(-1) ]^2$$

$$\frac{K_D}{K_L} = 2.04$$

(b)  $P = i_D \cdot V_{DD}$

$$0.1 = i_D(3) \Rightarrow i_D = 33.3 \mu A$$

$$i_D = \left( \frac{k'_n}{2} \right) \left( \frac{W}{L} \right)_L (-V_{TNL})^2$$

$$33.3 = \left( \frac{80}{2} \right) \left( \frac{W}{L} \right)_L [ -(-1) ]^2 \Rightarrow \left( \frac{W}{L} \right)_L = 0.8325$$

Then  $\left( \frac{W}{L} \right)_D = 1.70$

(c)  $3(2.04)[2(3-0.5)v_o - v_o^2] = [ -(-1) ]^2 \Rightarrow$

$$v_o = 0.0329 V$$

16.21

a.  $P = i_D \cdot V_{DD}$

$$250 = i_D(5) \Rightarrow i_D = 50 \mu A$$

$$i_D = \left( \frac{k'_n}{2} \right) \left( \frac{W}{L} \right)_{ML1} [-V_{TNL1}]^2$$

$$50 = \left( \frac{60}{2} \right) \left( \frac{W}{L} \right)_{ML1} [ -(-2) ]^2$$

So that  $\left( \frac{W}{L} \right)_{ML1} = 0.417$

$$\frac{K_D}{K_L} [2(v_I - V_{TND})v_o - v_o^2] = [-V_{TNL}]^2$$

$$\frac{K_D}{K_L} [2(5-0.8)(0.15) - (0.15)^2] = [ -(-2) ]^2$$

or  $\frac{K_D}{K_L} = 3.23 \Rightarrow \left( \frac{W}{L} \right)_{MD1} = 1.35$

b. For  $v_X = v_Y = 0 \Rightarrow v_{01} = 5$  and  $v_{03} = 4.2$

Then

$$K_{D2} [2(v_{01} - V_{TND})v_{02} - v_{02}^2] + K_{D3} [2(v_{03} - V_{TND})v_{02} - v_{02}^2] = K_{L2} [-V_{TNL2}]^2$$

$$K_{D2} \propto 8, K_{D3} \propto 8, K_{L2} \propto 1$$

$$8[2(5-0.8)v_{02} - v_{02}^2] + 8[2(4.2-0.8)v_{02} - v_{02}^2] = (1)[-(-2)]^2$$

$$67.2v_{02} - 8v_{02}^2 + 54.4v_{02} - 8v_{02}^2 = 4$$

Then

$$16v_0^2 - 121.6v_0 + 4 = 0$$

$$v_{02} = \frac{121.6 \pm \sqrt{(121.6)^2 - 4(16)(4)}}{2(16)}$$

So  $v_{02} = 0.0330 V$

16.22

a. We can write

$$K_x [2(v_X - V_{TN})v_{DSX} - v_{DSX}^2] = K_y [2(v_Y - v_{DSX} - V_{TN})v_{DST} - v_{DST}^2]$$

$$= K_L [V_{DD} - v_o - V_{TN}]^2$$

where  $v_o = v_{DSX} + v_{DSY}$

We have

$$v_X = v_Y = 9.2 V, V_{DD} = 10 V, V_{TN} = 0.8 V$$

As a good first approximation, neglect the  $v_{DSX}^2$  and  $v_{DSY}^2$  terms. Let  $v_o \approx 2v_{DSX}$ . Then from the first and third terms in the above equation,

$$9[2(9.2 - 0.8)v_{DSX}] \approx (1)(10 - 2v_{DSX} - 0.8)^2$$

$$(151.2)v_{DSX} \approx 84.64 - 36.8v_{DSX}$$

So that  $v_{DSX} = 0.450 V$

From the first and second terms of the above equation,

$$9[2(9.2 - 0.8)v_{DSX}] \approx 9[2(9.2 - v_{DSX} - 0.8)v_{DSY}]$$

or

$$(16.8)(0.45) = 2(9.2 - 0.45 - 0.8)v_{DSY}$$

which yields  $v_{DSY} = 0.475 V$

Then  $v_o = v_{DSX} + v_{DSY} = 0.450 + 0.475$

or  $v_o = 0.925 V$

We have  $v_{GSX} = 9.2 V$

and  $v_{GSY} = 9.2 - v_{DSX} = 9.2 - 0.45$

or  $v_{GSY} = 8.75 V$

b. Since  $v_o$  is close to ground potential, the body effect will have minimal effect on the results.

From a PSpice analysis:

For part (a) :

$$v_{DSX} = 0.462 V, v_{DSY} = 0.491 V, v_o = 0.9536 V,$$

$$v_{GSX} = 9.2 V, \text{ and } v_{GSY} = 8.738 V$$

For part (b) :

$$v_{DSX} = 0.441 V, v_{DSY} = 0.475 V, v_o = 0.9154 V,$$

$$v_{GSX} = 9.2 V, \text{ and } v_{GSY} = 8.759 V$$



(iii) For  $v_o = 0.4V$  : NMOS: Non-sat: PMOS: Sat

$$K_n [2(V_{GSN} - V_{TN})V_{DS} - V_{DS}^2] = K_p [V_{SGP} + V_{TP}]^2$$

$$2(v_i - 0.4)(0.4) - (0.4)^2 = (3.3 - v_i - 0.4)^2 \Rightarrow$$

$$v_i = 1.89V$$

For  $v_o = 2.9V$ , By symmetry

$$v_i = 1.65 - (1.89 - 1.65) \Rightarrow v_i = 1.41V$$

(b)  $K_n = \left(\frac{80}{2}\right)(2) = 80 \mu A/V^2$

$$K_p = \left(\frac{40}{2}\right)(2) = 40 \mu A/V^2$$

(i) 
$$V_{It} = \frac{3.3 - 0.4 + \sqrt{\frac{80}{40} \cdot (0.4)}}{1 + \sqrt{\frac{80}{40}}} \Rightarrow V_{It} = 1.44V$$

PMOS:

$$V_{O1} = 1.44 - (-0.4) \Rightarrow V_{O1} = 1.84V$$

NMOS:

$$V_{O1} = 1.44 - 0.4 \Rightarrow V_{O1} = 1.04V$$

(iii) For  $v_o = 0.4V$

$$(80)[2(v_i - 0.4)(0.4) - (0.4)^2] = (40)[3.3 - v_i - 0.4]^2$$

$$\Rightarrow v_i = 1.62V$$

For  $v_o = 2.9V$  : NMOS: Sat, PMOS: Non-sat

$$(80)[v_i - 0.4]^2 = (40)[2(3.3 - v_i - 0.4)(0.4) - (0.4)^2]$$

$$\Rightarrow v_i = 1.16V$$

16.30

a. For  $v_{o1} = 0.6 < V_{TN} \Rightarrow v_{o2} = 5V$

$N_1$  in nonsaturation and  $P_1$  in saturation. From Equation (16.57),

$$[2(v_i - 0.8)(0.6) - (0.6)^2] = [5 - v_i - 0.8]^2$$

$$1.2v_i - 1.32 = 17.64 - 8.4v_i + v_i^2$$

or

$$v_i^2 - 9.6v_i + 18.96 = 0$$

$$v_i = \frac{9.6 \pm \sqrt{(9.6)^2 - 4(1)(18.96)}}{2}$$

or

$$v_i = 2.78V$$

b.  $V_{0Nt} \leq v_{o2} \leq V_{0Pt}$

From symmetry,  $V_{It} = 2.5V$

$$V_{0Pt} = 2.5 + 0.8 = 3.3V$$

$$\text{and } V_{0Nt} = 2.5 - 0.8 = 1.7V$$

$$\text{So } 1.7 < v_{o2} < 3.3V$$

16.31

a.  $V_{0Nt} \leq v_{o1} \leq V_{0Pt}$

By symmetry,  $V_{It} = 2.5V$

$$V_{0Pt} = 2.5 + 0.8 = 3.3V$$

$$\text{and } V_{0Nt} = 2.5 - 0.8 = 1.7V$$

$$\text{So } 1.7 \leq v_{o1} \leq 3.3V$$

b. For  $v_{o2} = 0.6 < V_{TN} \Rightarrow v_{o3} = 5V$

$N_2$  in nonsaturation and  $P_2$  in saturation. From Equation (16.57),

$$[2(v_{I2} - 0.8)(0.6) - (0.6)^2] = [5 - v_{I2} - 0.8]^2$$

$$1.2v_{I2} - 1.32 = 17.64 - 8.4v_{I2} + v_{I2}^2$$

or

$$v_{I2}^2 - 9.6v_{I2} + 18.96 = 0$$

$$\text{So } v_{I2} = v_{o1} = 2.78V$$

For  $v_{o1} = 2.78$ , both  $N_1$  and  $P_1$  in saturation. Then


$$v_{I1} = 2.5V$$

16.32

a.  $\sqrt{i_{peak}} = \sqrt{K_n}(v_i - V_{TN})$

$$\sqrt{i_{peak}} = \sqrt{0.1} \cdot (2.5 - 0.8) = 0.538 \text{ (mA)}^{1/2}$$

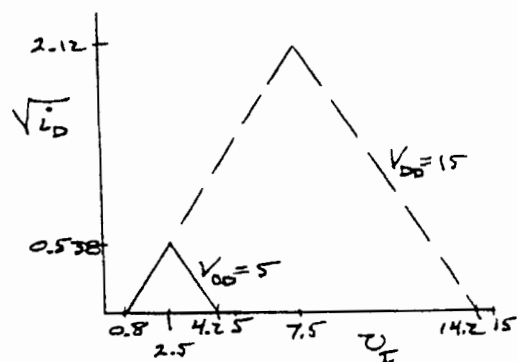b.  $\sqrt{i_{peak}} = \sqrt{0.1} \cdot (7.5 - 0.8) = 2.12 \text{ (mA)}^{1/2}$



16.33

(a)  $K_n = \left(\frac{50}{2}\right)(2) = 50 \mu A/V^2$

$$K_p = \left(\frac{25}{2}\right)(4) = 50 \mu A/V^2$$

$$I_{D,peak} = K_n(v_i - V_{TN})^2 = 50(2.5 - 0.8)^2$$

$$\text{or } I_{D,peak} = 144.5 \mu A$$

$$(b) K_n = 50 \mu A/V^2, K_p = 25 \mu A/V^2$$

From Equation (16.55),

$$V_H = \frac{5 - 0.8 + \sqrt{\frac{50}{25}(0.8)}}{1 + \sqrt{\frac{50}{25}}} = 2.21 V$$

Then

$$I_{D, \text{peak}} = K_n (V_H - V_{TN})^2 = 50(2.21 - 0.8)^2$$

$$\text{or } I_{D, \text{peak}} = 99.4 \mu A$$

16.34

$$a. P = f C_L V_{DD}^2$$

$$\text{For } V_{DD} = 5 V, P = (10 \times 10^6)(0.2 \times 10^{-12})(5)^2$$

$$\text{or } P = 50 \mu W$$

$$\text{For } V_{DD} = 15 V, P = (10 \times 10^6)(0.2 \times 10^{-12})(15)^2$$

$$\text{or } P = 450 \mu W$$

$$b. \text{ For } V_{DD} = 5 V, P = (10 \times 10^6)(0.2 \times 10^{-12})(5)^2$$

$$\text{or } P = 50 \mu W$$

16.35

$$(a) P = f C_L V_{DD}^2 = (150 \times 10^6)(0.4 \times 10^{-12})(5)^2$$

$$= 1.5 \times 10^{-3} \text{ W/inverter}$$

$$\text{Total power: } P_T = (2 \times 10^6)(1.5 \times 10^{-3}) \Rightarrow$$

$$P_T = 3000 \text{ W!!!!}$$

$$(b) \text{ For } f = 300 \text{ MHz}$$

$$1.5 \times 10^{-3} = (300 \times 10^6)(0.4 \times 10^{-12})V_{DD}^2 \Rightarrow$$

$$V_{DD} = 3.54 V$$

16.36

$$(a) \text{ For } v_i \cong V_{DD}, \text{ NMOS in nonsaturation}$$

$$i_D = K_n [2(v_i - V_{TN})v_{DS} - v_{DS}^2] \text{ and } v_{DS} \cong 0$$

$$\text{So } \frac{1}{r_{ds}} = \frac{di_D}{dv_{DS}} \cong K_n [2(V_{DD} - V_{TN})]$$

Or

$$r_{ds} = \frac{1}{\left(\frac{k'_n}{2}\right)\left(\frac{W}{L}\right)_n \cdot 2(V_{DD} - V_{TN})}$$

or

$$r_{ds} = \frac{1}{k'_n \left(\frac{W}{L}\right)_n \cdot (V_{DD} - V_{TN})}$$

For  $v_i \cong 0$ , PMOS in nonsaturation

$$i_D = K_p [2(V_{DD} - v_i + V_{TP})v_{SD} - v_{SD}^2]$$

and  $v_{SD} \cong 0$  for  $v_i \cong 0$ .

So

$$\frac{1}{r_{sd}} = \frac{di_D}{dv_{SD}} \cong \left(\frac{k'_p}{2}\right)\left(\frac{W}{L}\right)_p \cdot 2(V_{DD} + V_{TP})$$

or

$$r_{sd} = \frac{1}{k'_p \left(\frac{W}{L}\right)_p \cdot (V_{DD} + V_{TP})}$$

$$(b) \text{ For } \left(\frac{W}{L}\right)_n = 2, \left(\frac{W}{L}\right)_p = 4$$

$$r_{ds} = \frac{1}{(50)(2)(5 - 0.8)} \Rightarrow r_{ds} = 2.38 \text{ k}\Omega$$

$$r_{sd} = \frac{1}{(25)(4)(5 - 0.8)} \Rightarrow r_{sd} = 2.38 \text{ k}\Omega$$

$$\text{For } \left(\frac{W}{L}\right)_p = 2, .$$

$$r_{sd} = \frac{1}{(25)(2)(5 - 0.8)} \Rightarrow r_{sd} = 4.76 \text{ k}\Omega$$

Now, for NMOS:

$$v_{ds} = i_d r_{ds} \text{ or } i_d = \frac{v_{ds}}{r_{ds}} = \frac{0.5}{2.38} \Rightarrow \underline{i_d = 0.21 \text{ mA}}$$

For PMOS:

$$\text{For } r_{sd} = 2.38 \text{ k}\Omega,$$

$$i_d = \frac{v_{sd}}{r_{sd}} = \frac{0.5}{2.38} \Rightarrow \underline{i_d = 0.21 \text{ mA}}$$

$$\text{For } r_{sd} = 4.76 \text{ k}\Omega,$$

$$i_d = \frac{v_{sd}}{r_{sd}} = \frac{0.5}{4.76} \Rightarrow \underline{i_d = 0.105 \text{ mA}}$$

16.37

From Equation (16.73)

$$V_{IL} = 1.5 + \frac{3}{8} \cdot (10 - 1.5 - 1.5) \Rightarrow \underline{V_{IL} = 4.125 V}$$

and Equation (16.72)

$$V_{OHU} = \frac{1}{2} \cdot [2(4.125) + 10 - 1.5 + 1.5]$$

$$\text{or } \underline{V_{OHU} = 9.125 V}$$

From Equation (16.79)

$$V_{IH} = 1.5 + \frac{5}{8} \cdot (10 - 1.5 - 1.5) \Rightarrow \underline{V_{IH} = 5.875 V}$$

and Equation (16.78)

$$V_{OLU} = \frac{1}{2} \cdot [2(5.875) - 10 - 1.5 + 1.5]$$

$$\text{or } \underline{V_{OLU} = 0.875 V}$$

Now

$$NM_L = V_{IL} - V_{OLV} = 4.125 - 0.875$$

$$\Rightarrow NM_L = 3.25 \text{ V}$$

$$NM_H = V_{OHV} - V_{TH} = 9.125 - 5.875$$

$$\Rightarrow NM_H = 3.25 \text{ V}$$

16.38

From Equation (16.71)

$$V_{IL} = 1.5 + \frac{(10 - 1.5 - 1.5)}{\left(\frac{100}{50} - 1\right)} \left[ 2 \sqrt{\frac{\frac{100}{50}}{\frac{100}{50} + 3}} - 1 \right]$$

$$= 1.5 + 7[2(0.632) - 1]$$

or

$$V_{IL} = 3.348 \text{ V}$$

From Equation (16.70)

$$V_{OHV} = \frac{1}{2} \cdot \left\{ \left( 1 + \frac{100}{50} \right) (3.348) + 10 - \left( \frac{100}{50} \right) (1.5) + 1.5 \right\}$$

$$\text{or } V_{OHV} = 9.272 \text{ V}$$

From Equation (16.77)

$$V_{IH} = 1.5 + \frac{(10 - 1.5 - 1.5)}{\left(\frac{100}{50} - 1\right)} \left[ \frac{2\left(\frac{100}{50}\right)}{\sqrt{3\left(\frac{100}{50}\right) + 1}} - 1 \right]$$

$$= 1.5 + 7[1.51 - 1]$$

or

$$V_{IH} = 5.07 \text{ V}$$

From Equation (16.76)

$$V_{OLV} = \frac{(5.07) \left( 1 + \frac{100}{50} \right) - 10 - \left( \frac{100}{50} \right) (1.5) + 1.5}{2 \left( \frac{100}{50} \right)}$$

$$\text{or } V_{OLV} = 0.9275 \text{ V}$$

$$\text{Now } NM_L = V_{IL} - V_{OLV} = 3.348 - 0.9275$$

$$\text{or } NM_L = 2.42 \text{ V}$$

$$NM_H = V_{OHV} - V_{IH} = 9.272 - 5.07$$

$$\text{or } NM_H = 4.20 \text{ V}$$

16.39

a.  $v_A = v_B = 5 \text{ V}$

$N_1$  and  $N_2$  on, so  $v_{DS1} \approx v_{DS2} \approx 0 \text{ V}$

$P_1$  and  $P_2$  off

So we have a  $P_3 - N_3$  CMOS inverter. By symmetry,  $v_C = 2.5 \text{ V}$  (Transition Point).

b. For  $v_A = v_B = v_C \equiv v_i$

Want  $K_{n,eff} = K_{p,eff}$

$$\frac{k'_n}{2} \cdot \left( \frac{W}{3L} \right)_n = \frac{k'_p}{2} \cdot \left( \frac{3W}{L} \right)_p$$

With  $k'_n = 2k'_p$ , then

$$\frac{2}{2} \cdot \frac{1}{3} \cdot \left( \frac{W}{L} \right)_n = \frac{1}{2} \cdot 3 \cdot \left( \frac{W}{L} \right)_p$$

$$\text{Or } \left( \frac{W}{L} \right)_n = \frac{9}{2} \left( \frac{W}{L} \right)_p$$

c. We have

$$K_n = \left( \frac{k'_n}{2} \right) \left( \frac{W}{L} \right)_n = \left( \frac{2k'_p}{2} \right) \left( \frac{9}{2} \right) \left( \frac{W}{L} \right)_p$$

$$K_p = \left( \frac{k'_p}{2} \right) \left( \frac{W}{L} \right)_p$$

Then from Equation (16.55)

$$V_H = \frac{5 + (-0.8) + \sqrt{\frac{K_n}{K_p}} \cdot (0.8)}{1 + \sqrt{\frac{K_n}{K_p}}}$$

Now

$$\frac{K_n}{K_p} = (2) \left( \frac{9}{2} \right) = 9$$

Then

$$V_H = \frac{5 + (-0.8) + 3(0.8)}{1 + 3} \Rightarrow V_H = 1.65 \text{ V}$$

16.40

By definition, NMOS is on if gate voltage is 5 V and is off if gate voltage is 0 V.


State	$N_1$	$N_2$	$N_3$	$N_4$	$N_5$	$v_o$
1	off	on	off	on	on	0
2	off	off	on	on	off	0
3	on	on	off	off	on	5
4	on	on	off	on	on	0

Logic function  $(v_X \text{ OR } v_Y) \otimes (v_X \text{ AND } v_Z)$

Exclusive OR of  $(v_X \text{ OR } v_Y)$  with  $(v_X \text{ AND } v_Z)$

16.41

(a) A classic design is shown:

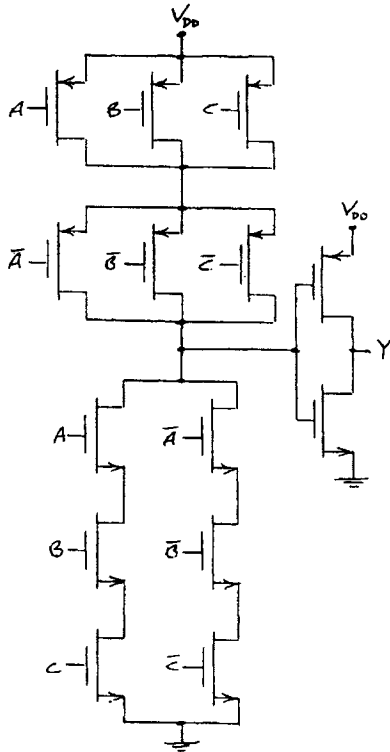

$\bar{A}, \bar{B}, \bar{C}$  signals supplied through inverters.


(b) For Inverters,  $\left(\frac{W}{L}\right)_n = 1$  and  $\left(\frac{W}{L}\right)_p = 2$

For PMOS in Logic function, let  $\left(\frac{W}{L}\right)_p = 1$ , then

for NMOS in Logic function,  $\left(\frac{W}{L}\right)_n = 2.25$

16.42

(a) A classic design is shown:

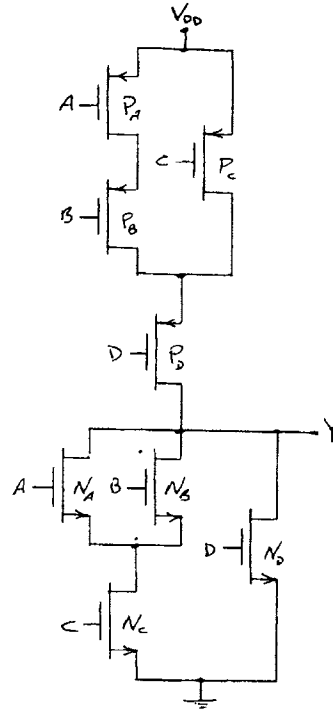

(b)  $\left(\frac{W}{L}\right)_{ND} = 1, \left(\frac{W}{L}\right)_{NA, NB, NC} = 2$

$\left(\frac{W}{L}\right)_{PA, PB} = 8, \left(\frac{W}{L}\right)_{PC, PD} = 4$

16.43

$$\overline{(A \text{ OR } B) \text{ AND } C}$$

16.44

Let  $\left(\frac{W}{L}\right)_p = 1$  for each PMOS: Composite PMOS

$\left(\frac{W}{L}\right)_n = 5$ . Want composite  $\left(\frac{W}{L}\right) = 2.5$  for NMOS,

So that  $\left(\frac{W}{L}\right)_n = 5(2.5) = 12.5$  for each NMOS.

16.45

(a) Let  $\left(\frac{W}{L}\right)_n = 1$  for each NMOS. Composite  $\left(\frac{W}{L}\right)$  of NMOS = 6. Want composite  $\left(\frac{W}{L}\right)$  of PMOS = 12. Then  $\left(\frac{W}{L}\right)_p = 6(12) = 72$  for each PMOS. Let  $\left(\frac{W}{L}\right)_n = 1$  and  $\left(\frac{W}{L}\right)_p = 2$  for each transistor in inverter.

(a) For 3-input NOR:

Let  $\left(\frac{W}{L}\right)_n = 1$  for each NMOS. Composite  $\left(\frac{W}{L}\right)$  of NMOS = 3. Want composite  $\left(\frac{W}{L}\right)$  of PMOS = 6.

Then  $\left(\frac{W}{L}\right)_p = 3(6) = 18$  for each PMOS.

For 2-input NAND:

Let  $\left(\frac{W}{L}\right)_p = 1$  for each PMOS. Composite  $\left(\frac{W}{L}\right)$  of PMOS = 2. Want composite  $\left(\frac{W}{L}\right)$  of NMOS = 1.

Then  $\left(\frac{W}{L}\right)_n = 2$  for each NMOS.

Sizes of PMOS transistors in (b) are substantially less than those in (a).

16.46

By definition:

NMOS off if gate voltage = 0

NMOS on if gate voltage = 5 V

PMOS off if gate voltage = 5 V

PMOS on if gate voltage = 0

State	$N_1$	$P_1$	$N_A$	$N_B$	$N_C$	$\nu_{01}$	$N_2$	$P_2$	$\nu_{02}$
1	off	on	off	off	off	5	on	off	0
2	on	off	on	off	off	5	on	off	0
3	off	on	off	off	off	5	on	off	0
4	on	off	off	off	on	5	on	off	0
5	off	on	off	off	off	5	on	off	0
6	on	off	off	on	on	0	off	on	5

Logic function is

$$\nu_{02} = (\nu_A \text{ OR } \nu_B) \text{ AND } \nu_C$$


16.47

State	$\nu_{01}$	$\nu_{02}$	$\nu_{03}$
1	5	5	0
2	0	0	5
3	5	5	0
4	5	0	5
5	5	5	0
6	0	5	0


Logic function:

$$\nu_{03} = (\nu_X \text{ OR } \nu_Z) \text{ AND } \nu_Y$$


16.48

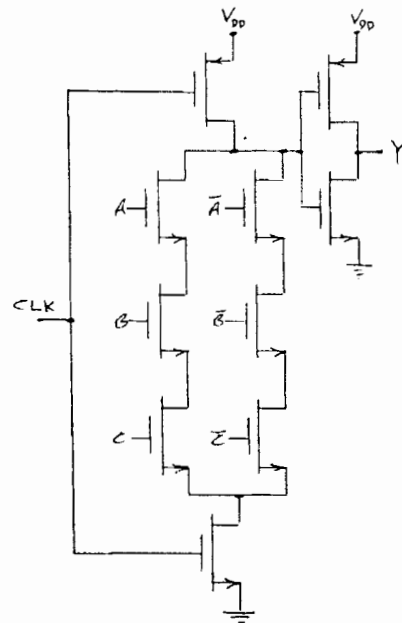

16.49

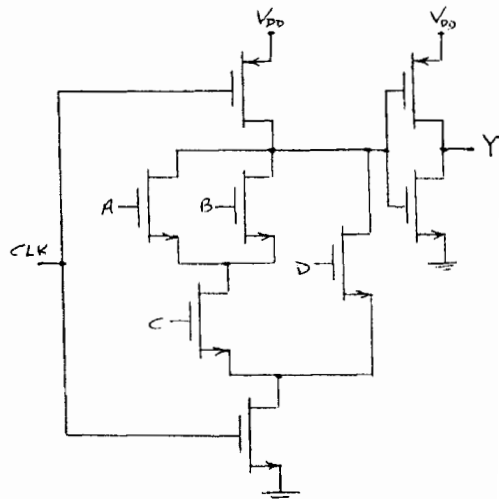

16.50

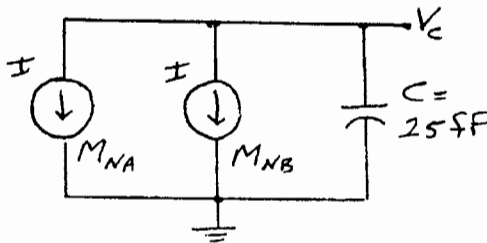

$$2I = -C \frac{dV_c}{dt}$$

So

$$\Delta V_c = -\frac{1}{C}(2I) \cdot t$$

$$\text{For } \Delta V_c = -0.5V$$

$$-0.5 = -\frac{2(2 \times 10^{-12}) \cdot t}{25 \times 10^{-15}} \Rightarrow t = 3.125 \text{ ms}$$

16.51

- (a)  
 (i)  $v_o = 0$   
 (ii)  $v_o = 4.2V$   
 (iii)  $v_o = 2.5V$

- (b)  
 (i)  $v_o = 0$   
 (ii)  $v_o = 3.2V$   
 (iii)  $v_o = 2.5V$

16.52

Neglect the body effect.

a.  $v_{o1}(\text{logic } 1) = 4.2V, v_{o2}(\text{logic } 1) = 5V$

b.  $v_I = 5V \Rightarrow v_{GS1} = 4.2V$

$M_1$  in nonsaturation and  $M_2$  in saturation. From Equation (16.23)

$$\left(\frac{W}{L}\right)_D [2(v_{GS1} - V_{TND})v_{o1} - v_{o1}^2]$$

$$= \left(\frac{W}{L}\right)_L (V_{DD} - v_{o1} - V_{TNL})^2$$

$$\left(\frac{W}{L}\right)_D [2(4.2 - 0.8)(0.1) - (0.1)^2]$$

$$= (1)[5 - 0.1 - 0.8]^2$$

Or

$$\left(\frac{W}{L}\right)_D (0.67) = 16.81 \Rightarrow \left(\frac{W}{L}\right)_D = 25.1$$

Now

$$v_{o1} = 4.2V \Rightarrow v_{GS3} = 4.2V$$

$M_3$  in nonsaturation and  $M_4$  in saturation. From Equation (16.29(b)).

$$\left(\frac{W}{L}\right)_D [2(v_{GS3} - V_{TND})v_{o2} - v_{o2}^2] = \left(\frac{W}{L}\right)_L [-V_{TNL}]^2$$

$$\left(\frac{W}{L}\right)_D [2(4.2 - 0.8)(0.1) - (0.1)^2] = (2)[-(-1.5)]^2$$

$$\left(\frac{W}{L}\right)_D (0.67) = 2.25$$

$$\text{Or } \left(\frac{W}{L}\right)_D = 3.36$$

16.53

For  $\phi = 1, \bar{\phi} = 0$ , then  $Y = B$ . And for  $\phi = 0, \bar{\phi} = 1$ , then  $Y = A$ .

A multiplexer.

16.54

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0, 1 $\Rightarrow$ indeterminate

Without the top transistor, the circuit performs the exclusive-NOR function.

16.55

A	B	Y
0	0	0
1	0	1
0	1	1
1	1	0

Exclusive-OR function.

16.56

This circuit is referred to as a ratioless circuit. Identical minimum-sized transistors can be used throughout.

When  $\phi_1$  is low,  $C_3$  is charged to  $V_{DD}$ . Then when  $\phi_1$  is high and  $\phi_2$  is low,  $M_6$  turns on. If  $A = B = 0$ , then  $M_3$  and  $M_4$  are off so  $C_3$  remains charged and  $v_{o1} = \text{high}$ . When  $\phi_2$  goes high, then  $v_{o1}$  is applied to the gates of  $M_9$  and  $M_{10}$ . The circuit performs the OR logic function.

16.57

This circuit is referred to as a two-phase ratioed circuit. The same width-to-length ratios between the driver and load transistors must be maintained as discussed previously with the enhancement load inverter.

When  $\phi_1$  is high,  $v_{o1}$  becomes the complement of  $v_I$ . When  $\phi_2$  goes high, then  $v_o$  becomes the complement of  $v_{o1}$  or is the same as  $v_I$ . The circuit is a shift register.

16.58

Let  $Q = 0$  and  $\bar{Q} = 1$ ; as  $S$  increases,  $\bar{Q}$  decreases.  
 When  $\bar{Q}$  reaches the transition point of the  $M_3 - M_6$  inverter, the flip-flop will change state.  
 From Equation (16.28(b)),

$$V_H = \sqrt{\frac{K_L}{K_D}} \cdot (-V_{TNL}) + V_{TND}$$

where  $K_L = K_6$  and  $K_D = K_3$ .

Then

$$V_H = \sqrt{\frac{30}{100}} \cdot [ -(-2) ] + 1 \Rightarrow V_H = \bar{Q} = 2.095V$$

This is the region where both  $M_1$  and  $M_3$  are biased in the saturation region. Then


$$S = \sqrt{\frac{K_3}{K_1}} \cdot (-V_{TNL}) + V_{TND} = \sqrt{\frac{30}{200}} \cdot [ -(-2) ] + 1$$

or  $S = 1.77V$

This analysis neglects the effect of  $M_2$  starting to turn on at the same time.

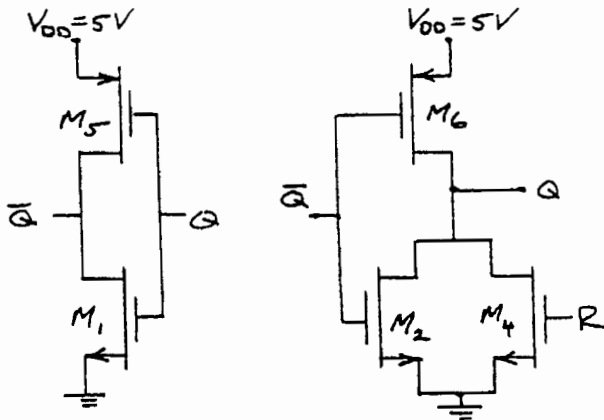16.59

Let  $v_Y = R$ ,  $v_X = S$ ,  $v_{02} = Q$ , and  $v_{01} = \bar{Q}$ . Assume  $V_{TN,N} = 0.5V$  and  $V_{TN,P} = -0.5V$ . For  $S = 0$ , we have the following:



If we want the switching to occur for  $R = 2.5V$ , then because of the nonsymmetry between the two circuits, we cannot have  $Q$  and  $\bar{Q}$  both equal to  $2.5V$ .

Set  $R = Q = 2.5V$  and assume  $\bar{Q}$  goes low.

For the  $M_1 - M_5$  inverter,  $M_1$  in nonsaturation and  $M_5$  in saturation. Then

$$K_n [ 2(2.5 - 0.5)\bar{Q} - \bar{Q}^2 ] = K_p [ 2.5 - 0.5 ]^2$$

Or

$$4\bar{Q} - \bar{Q}^2 = 4 \left( \frac{K_p}{K_n} \right)$$


For the other circuit,  $M_2 - M_4$  in saturation and  $M_6$  in nonsaturation. Then

$$K_n (2.5 - 0.5)^2 + K_n (\bar{Q} - 0.5)^2 = K_p [ 2(5 - \bar{Q} - 0.5)(2.5) - (2.5)^2 ]$$

Combining these equations and neglecting the  $\bar{Q}^3$  term, we find

$$\bar{Q} = 1.4V \text{ and } \frac{K_p}{K_n} = 0.9$$

16.60

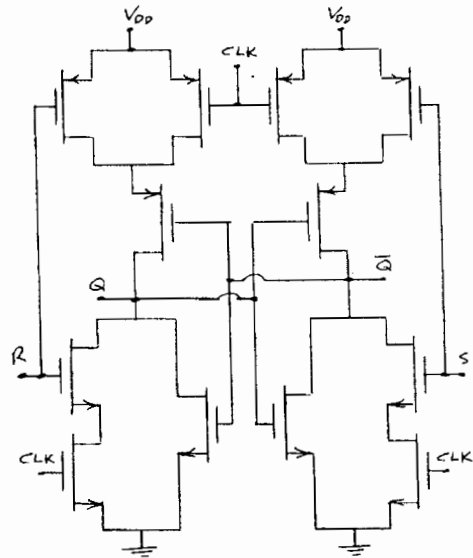

16.61

- Positive edge triggered flip-flop when  $CLK = 1$ , output of first inverter is  $\bar{D}$  and then  $Q = \bar{\bar{D}} = D$ .
- For example, put a CMOS transmission gate between the output and the gate of  $M_1$  driven by a  $\overline{CLK}$  pulse.

16.62

For  $J = 1$ ,  $K = 0$ , and  $CLK = 1$ ; this makes  $Q = 1$  and  $\bar{Q} = 0$ .

For  $J = 0$ ,  $K = 1$ , and  $CLK = 1$ , and if  $Q = 1$ , then the circuit is driven so that  $Q = 0$  and  $\bar{Q} = 1$ .

If initially,  $Q = 0$ , then the circuit is driven so that there is no change and  $Q = 0$  and  $\bar{Q} = 1$ .

$J = 1$ ,  $K = 1$ , and  $CLK = 1$ , and if  $Q = 1$ , then the circuit is driven so that  $Q = 0$ .

If initially,  $Q = 0$ , then the circuit is driven so that  $Q = 1$ .

So if  $J = K = 1$ , the output changes state.

16.63

For  $J = \nu_X = 1$ ,  $K = \nu_Y = 0$ , and  $CLK = \nu_Z = 1$ , then  $\nu_0 = 0$ .

For  $J = \nu_X = 0$ ,  $K = \nu_Y = 1$ , and  $CLK = \nu_Z = 1$ , then  $\nu_0 = 1$ .

Now consider  $J = K = CLK = 1$ . With  $\nu_X = \nu_Z = 1$ , the output is always  $\nu_0 = 0$ . So the output does not change state when  $J = K = CLK = 1$ . This is not actually a  $J - K$  flip-flop.

16.64

$64 K \Rightarrow 65,536$  transistors arranged in a  $256 \times 256$  array.

(a) Each column and row decoder required 8 inputs.

(b)

(i) Address = 01011110 so input =  $a_7\bar{a}_6a_5\bar{a}_4\bar{a}_3\bar{a}_2\bar{a}_1a_0$

(ii) Address = 11101111 so input =  $\bar{a}_7\bar{a}_6\bar{a}_5a_4\bar{a}_3\bar{a}_2\bar{a}_1\bar{a}_0$

(c)

(i) Address = 00100111 so input =  $a_7a_6\bar{a}_5a_4a_3\bar{a}_2\bar{a}_1\bar{a}_0$

(ii) Address = 01111011 so input =  $a_7\bar{a}_6\bar{a}_5\bar{a}_4\bar{a}_3a_2\bar{a}_1\bar{a}_0$

16.65

Put 128 words in a  $8 \times 16$  array, which means 8 row (or column) address lines and 16 column (or row) address lines.

16.66

Assume the address line is initially uncharged, then

$$I = C \frac{dV_c}{dt} \text{ or } V_c = \frac{1}{C} \int Idt = \frac{I}{C} \cdot t$$

$$\text{Then } t = \frac{V_c \cdot C}{I} = \frac{(2.7)(5.8 \times 10^{-12})}{250 \times 10^{-6}} \Rightarrow$$

$$t = 6.26 \times 10^{-8} \text{ s} \Rightarrow 62.6 \text{ ns}$$

16.67

$$(a) \frac{5-0.1}{1} = \left(\frac{35}{2}\right) \left(\frac{W}{L}\right) [2(5-0.7)(0.1) - (0.1)^2]$$

$$\text{or } \left(\frac{W}{L}\right) = 0.329$$

(b)  $16 K \Rightarrow 16,384$  cells

$$i_D \cong \frac{2}{1} = 2 \mu A$$

$$\text{Power per cell} = (2 \mu A)(2 V) = 4 \mu W$$

$$\text{Total Power} = P_T = (4 \mu W)(16,384) \Rightarrow$$

$$P_T = 65.5 \text{ mW}$$

$$\text{Standby current} = (2 \mu A)(16,384) \Rightarrow I_T = 32.8 \text{ mA}$$

16.68

$16 K \Rightarrow 16,384$  cells

$P_T = 200 \text{ mW} \Rightarrow$  Power per cell

$$= \frac{200}{16,384} \Rightarrow 12.2 \mu W$$

$$i_D = \frac{P}{V_{DD}} = \frac{12.2}{2.5} = 4.88 \mu A \cong \frac{V_{DD}}{R} = \frac{2.5}{R} \Rightarrow$$

$$R = 0.512 \text{ M}\Omega$$

If we want  $v_o = 0.1 V$  for a logic 0, then

$$i_D = \left(\frac{k'_n}{2}\right) \left(\frac{W}{L}\right) [2(V_{DD} - V_{TN})v_o - v_o^2]$$

$$4.88 = \left(\frac{35}{2}\right) \left(\frac{W}{L}\right) [2(2.5 - 0.7)(0.1) - (0.1)^2]$$

$$\text{So } \left(\frac{W}{L}\right) = 0.797$$

16.69

$$Q = 0, \bar{Q} = 1$$

$$\text{So } \bar{D} = \text{Logic } 1 = 5 V$$

A very short time after the row has been addressed,  $D$  remains charged at  $V_{DD} = 5 V$ . Then  $M_{P3}$ ,  $M_{A1}$ , and  $M_{N1}$  begin to conduct and  $D$  decreases. In steady-state, all three transistors are biased in the nonsaturation region. Then

$$K_{P3} [2(V_{DS3} + V_{TP3})V_{SD3} - V_{SD3}^2]$$

$$= K_{n1} [2(V_{GS1} - V_{TN1})V_{DS1} - V_{DS1}^2]$$

$$= K_{n1} [2(V_{GS1} - V_{TN1})V_{DS1} - V_{DS1}^2]$$

Or

$$K_{P3} [2(V_{DD} + V_{TP3})(V_{DD} - D) - (V_{DD} - D)^2]$$

$$= K_{n1} [2(V_{DD} - Q - V_{TN1})(D - Q) - (D - Q)^2]$$

$$= K_{n1} [2(V_{DD} - V_{TN1})Q - Q^2] \quad (1)$$

Equating the first and third terms:

$$\begin{aligned} \left(\frac{20}{2}\right)(1)[2(5-0.8)(5-D)-(5-D)^2] \\ = \left(\frac{40}{2}\right)(2)[2(5-0.8)Q-Q^2] \end{aligned} \quad (2)$$

As a first approximation, neglect the  $(5-D)^2$  and  $Q^2$  terms. We find

$$Q = 1.25 - 0.25D \quad (3)$$

Then, equating the first and second terms of Equation (1):

$$\begin{aligned} \left(\frac{20}{2}\right)(1)[2(5-0.8)(5-D)-(5-D)^2] \\ = \left(\frac{40}{2}\right)(1)[2(5-Q-0.8)(D-Q)-(D-Q)^2] \end{aligned}$$

Substituting Equation (3), we find as a first approximation:  $D = 2.14 V$

Substituting this value of  $D$  into equation (2), we find

$$8.4(5-2.14)-(5-2.14)^2 = 4[8.4Q-Q^2]$$

We find  $Q = 0.50 V$

Using this value of  $Q$ , we can find a second approximation for  $D$  by equating the second and third terms of equation (1). We have

$$\begin{aligned} 20[2(4.2-Q)(D-Q)-(D-Q)^2] \\ = 40[2(4.2Q)-Q^2] \end{aligned}$$

Using  $Q = 0.50 V$ , we find  $D = 1.79 V$

16.70

Initially  $M_{N1}$  and  $M_A$  turn on.

$M_{N1}$ , Nonsat;  $M_A$ , sat.

$$K_{nA}[V_{DD}-Q-V_{TN}]^2 = K_{n1}[2(V_{DD}-V_{TN1})Q-Q^2]$$

$$\left(\frac{40}{2}\right)(1)[5-Q-0.8]^2 = \left(\frac{40}{2}\right)(2)[2(5-0.8)Q-Q^2]$$

which yields

$$Q = 0.771 V$$

Initially  $M_{P2}$  and  $M_B$  turn on

Both biased in nonsaturation region

$$\begin{aligned} K_{p2}[2(V_{DD}+V_{TP3})(V_{DD}-\bar{Q})-(V_{DD}-\bar{Q})^2] \\ = K_{nB}[2(V_{DD}-V_{TNB})\bar{Q}-\bar{Q}^2] \end{aligned}$$

$$\left(\frac{20}{2}\right)(4)[2(5-0.8)(5-\bar{Q})-(5-\bar{Q})^2]$$

$$= \left(\frac{40}{2}\right)(1)[2(5-0.8)\bar{Q}-\bar{Q}^2]$$

which yields  $\bar{Q} = 3.78 V$

Note:  $(W/L)$  ratios do not satisfy Equation (16.95)

16.71

For Logic 1,  $v_1$ :

$$(5)(0.05) + (4)(1) = (1+0.05)v_1 \Rightarrow v_1 = 4.0476 V$$

$v_2$ :

$$(5)(0.025) + (4)(1) = (1+1.025)v_2 \Rightarrow v_2 = 4.0244 V$$

For Logic 0,  $v_1$ :

$$(0)(0.05) + (4)(1) = (1+0.05)v_1 \Rightarrow v_1 = 3.8095 V$$

$v_2$ :

$$(0)(0.025) + (4)(1) = (1+0.025)v_2 \Rightarrow v_2 = 3.9024 V$$

## Chapter 17

### Exercise Solutions

E17.1

a.  $i_E = \frac{-0.7 - (-5)}{R_E} = 1 \text{ mA} \Rightarrow \underline{R_E = 4.3 \text{ k}\Omega}$

$i_{C1} = i_{C2} = 0.5 \text{ mA} = \frac{5 - 3.5}{R_{C1}}$   
 $\Rightarrow \underline{R_{C1} = R_{C2} = 3 \text{ k}\Omega}$

b. i.  $v_1 = 1 \text{ V}$

$i_E = \frac{(1 - 0.7) - (-5)}{4.3} \Rightarrow \underline{i_E = 1.23 \text{ mA}}$

$i_{C1} = i_E = v_{01} = 5 - (1.23)(3)$   
 $\Rightarrow \underline{v_{01} = 1.31 \text{ V}}$   
 $\underline{v_{02} = 5 \text{ V}}$

ii.  $v_1 = -1 \text{ V}$

$i_E = 1 \text{ mA} \Rightarrow v_{02} = 5 - (1)(3)$   
 $\Rightarrow \underline{v_{02} = 2 \text{ V}}$   
 $\underline{v_{01} = 5 \text{ V}}$

E17.2

a.  $Q_R$  on

$i_E = \frac{1.5 - 0.7 - (-3.5)}{R_E} = 2 \text{ mA}$   
 $\Rightarrow \underline{R_E = 2.15 \text{ k}\Omega}$

$i_{CR} \approx i_E = 2 \text{ mA} = \frac{3.5 - 2}{R_{C2}}$   
 $\Rightarrow \underline{R_{C2} = 0.75 \text{ k}\Omega}$

b.  $v_X = v_Y = 2 \text{ V} \Rightarrow Q_1$  and  $Q_2$  on

$i_E = \frac{2 - 0.7 - (-3.5)}{R_E} = \frac{4.8}{2.15} \Rightarrow \underline{i_E = 2.23 \text{ mA}}$

$R_{C1} = \frac{3.5 - 2}{i_{CXY}} = \frac{1.5}{2.23} \Rightarrow \underline{R_{C1} = 0.673 \text{ k}\Omega}$

E17.3

logic 1 =  $-0.7 \text{ V}$

$Q_1$  and  $Q_2$  on when  $v_X = v_Y = -0.7 \text{ V}$

$i_E = \frac{-0.7 - 0.7 - (-5.2)}{R_E} = 2.5$   
 $\Rightarrow \underline{R_E = 1.52 \text{ k}\Omega}$

$v_{NOR} = -1.5 \Rightarrow R_{C1} = \frac{0 - (-1.5 + 0.7)}{2.5}$   
 $\Rightarrow \underline{R_{C1} = 320 \Omega}$

$V_R = \frac{-1.5 - 0.7}{2} \Rightarrow \underline{V_R = -1.1 \text{ V}}$

$Q_R$  on  $\Rightarrow i_E = \frac{-1.1 - 0.7 - (-5.2)}{1.52} = 2.24 \text{ mA}$

$R_{C2} = \frac{0 - (-1.5 + 0.7)}{2.24} \Rightarrow \underline{R_{C2} = 357 \Omega}$

$R_3 = R_4 = \frac{-0.7 - (-5.2)}{2.5} \Rightarrow \underline{R_3 = R_4 = 1.8 \text{ k}\Omega}$

E17.4

$P(i_{CXY} + i_{CR} + i_3 + i_4)(5.2)$

a.  $v_X = v_Y = \text{logic 1}$

$\Rightarrow i_{CXY} = 3.22 \text{ mA}$

$i_{CR} = 0$

$i_3 = \frac{-0.7 + 5.2}{1.5} = 3 \text{ mA}$

$i_4 = \frac{-1.4 + 5.2}{1.5} = 2.53 \text{ mA}$

$P = (3.22 + 0 + 3 + 2.53)(5.2)$

$\Rightarrow \underline{P = 45.5 \text{ mW}}$

b.  $v_X = v_Y = \text{logic 0}$

$\Rightarrow i_{CXY} = 0$

$i_{CR} = 2.92 \text{ mA}$


$i_3 = 2.53 \text{ mA}$

$i_4 = 3 \text{ mA}$

$P = (0 + 2.92 + 2.53 + 3)(5.2)$

$\Rightarrow \underline{P = 43.9 \text{ mW}}$

E17.5

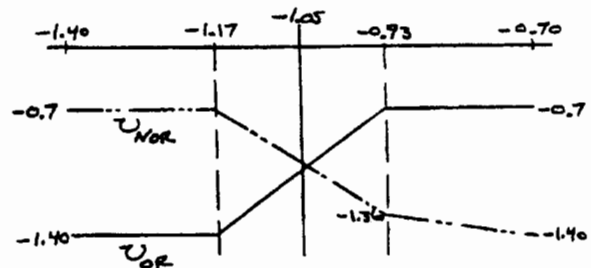

$NM_H = -0.70 - (-0.93) \Rightarrow \underline{NM_H = 0.23 \text{ V}}$

$NM_L = -1.17 - (-1.40) \Rightarrow \underline{NM_L = 0.23 \text{ V}}$

E17.6

$$P = I_Q \cdot V_{CC} \Rightarrow 0.2 = I_Q(1.7)$$

$$\Rightarrow I_Q = 118 \mu\text{A}$$

$$Q_R \text{ on} \Rightarrow v_0 = 1.7 - I_Q R_C = 1.7 - 0.4$$

$$\Rightarrow R_C = \frac{0.4}{0.118} \Rightarrow R_C = 3.39 \text{ k}\Omega$$

$$V_R = \frac{1.7 + 1.3}{2} \Rightarrow V_R = 1.5 \text{ V}$$

E17.7

State	A	B	C	Q <sub>01</sub>	Q <sub>02</sub>	Q <sub>03</sub>	Q <sub>1</sub>	Q <sub>2</sub>	Q <sub>R</sub>	v <sub>0</sub>
1	0	0	0	off	off	off	off	on	on	0
2	1	0	0	"on"	off	off	off	on	on	0
3	0	1	0	off	on	off	off	on	"off"	1
4	0	0	1	off	off	on	on	off	on	0
5	1	1	0	on	on	off	off	on	off	1
6	1	0	1	on	off	on	on	off	"off"	1
7	0	1	1	off	on	on	on	off	on	0
8	1	1	1	on	on	on	on	off	off	1

$(A \text{ AND } C)$  OR  $(B \text{ AND } \overline{C})$   
 true for states 6 and 8      true for states 3 and 5  
 Output goes high for these 4 states

E17.8

A	B	C	v <sub>0</sub>
0	0	0	0
1	0	0	1
0	1	0	1
0	0	1	1
1	1	0	0
1	0	1	0
0	1	1	0
1	1	1	1

$$\Rightarrow (A \oplus B) \oplus C$$

E17.9

$$i_C = \frac{5 - 0.1}{1} = 4.9 \text{ mA}$$

$$i_B = \frac{4.9}{30} = 0.163 \text{ mA} = \frac{v_I - 0.7}{R_B} = \frac{4.3}{R_B}$$

$$\Rightarrow R_B = 26.4 \text{ k}\Omega$$

E17.10

(a)  $v_X = v_Y = 5 \text{ V}$   
 $v_1 = V_{BE}(\text{sat}) + 2V_Y = 0.8 + 2(0.7) = 2.2 \text{ V}$   
 $i_1 = \frac{5 - 2.2}{4} = 0.70 \text{ mA}$   
 $i_{RC} = \frac{V_{CC} - V_{CE}(\text{sat})}{R_C} = \frac{5 - 0.1}{4} = 1.23 \text{ mA}$   
 $P = (i_1 + i_{RC})V_{CC} = (0.70 + 1.23)(5)$   
 or  $P = 9.65 \text{ mW}$

(b)  $v_X = v_Y = 0 \Rightarrow v_1 = 0.70 \text{ V}$   
 $i_1 = \frac{V_{CC} - v_1}{R_1} = \frac{5 - 0.70}{4} = 1.08 \text{ mA}$   
 $P = i_1 \cdot V_{CC} = (1.08)(5) \Rightarrow P = 5.4 \text{ mW}$

E17.11

a. Inputs high  $v_1 = 0.8 + 0.7 + 0.8 = 2.3 \text{ V}$   
 $i_1 = i_{B1} = \frac{5 - 2.3}{4} = 0.675 \text{ mA}$   
 $v_{C1} = 0.8 + 0.7 + 0.7 = 1.6 \text{ V}$   
 $i_2 = \frac{5 - 1.6}{2} = 1.7 \text{ mA}$   
 $i_3 = 1.7 + 0.675 = 2.38 \text{ mA}$   
 $i_4 = \frac{0.8}{10} = 0.08 \text{ mA}$   
 $i_{B0} = 2.38 - 0.08 = 2.3 \text{ mA}$   
 $i_{RC} = \frac{5 - 0.1}{4} = 1.23 \text{ mA}$   
 $i'_L = \frac{5 - 0.8}{4} = 1.05 \text{ mA}$   
 $\beta i_{B0} = N i'_L + i_{RC}$   
 $(30)(2.3) = N(1.05) + 1.23 \Rightarrow N = 64$

b.  $I_{C,\text{rated}} = 20 \text{ mA}$   
 $20 = N i'_L + i_{RC} = N(1.05) + 1.23$   
 $\Rightarrow N = 17$

E17.12

a.  $v_X = v_Y = 0.1 \Rightarrow v_1 = 0.8$

$$i_1 = \frac{5 - 0.8}{6} \Rightarrow \underline{i_1 = 0.7 \text{ mA}}$$

$$\underline{i_2 = i_R = i_B = i_{RC} = 0}$$

$$\underline{v_0 = 5 \text{ V}}$$

b. Same as part (a).

c.  $v_X = v_Y = 5 \text{ V} \Rightarrow v_1 = 0.8 + 0.7 + 0.7 = 2.2 \text{ V}$

$$i_1 = i_2 = \frac{5 - 2.2}{6} \Rightarrow \underline{i_1 = i_2 = 0.467 \text{ mA}}$$

$$i_R = \frac{0.8}{15} \Rightarrow \underline{i_R = 0.053 \text{ mA}}$$

$$i_B = i_2 - i_R \Rightarrow \underline{i_B = 0.414 \text{ mA}}$$

$$i_{RC} = \frac{5 - 0.1}{5} \Rightarrow \underline{i_{RC} = 0.98 \text{ mA}}$$

$$\underline{v_0 = 0.1 \text{ V}}$$

E17.13

a.  $v_X = v_Y = 0.1 \text{ V}$

$$i_1 = \frac{5 - 0.8}{8} = 0.525 \text{ mA}$$

$$P = i_1(5 - 0.1) = (0.525)(4.9)$$

$$\Rightarrow \underline{P = 2.57 \text{ mW}}$$

b.  $v_X = v_Y = 5 \text{ V}, v_1 = 2.3 \text{ V}$

$$i_1 = \frac{5 - 2.3}{8} = 0.338 \text{ mA}$$

$$v_{C1} = 1.6 \text{ V} \Rightarrow i_2 = \frac{5 - 1.6}{3.6} = 0.944 \text{ mA}$$

$$i_{RC} = \frac{5 - 0.1}{6} = 0.817 \text{ mA}$$

$$P = (i_1 + i_2 + i_{RC})(V_{CC})$$

$$= (0.338 + 0.944 + 0.817)(5)$$

$$\underline{P = 10.3 \text{ mW}}$$

E17.14

a.  $v_X = v_Y = 0.1 \text{ V}$

$$v_{B1} = 0.1 + 0.8 = 0.9 \text{ V}$$

$$i_{B1} = i_1 = \frac{5 - 0.9}{6} \Rightarrow \underline{i_1 = i_{B1} = 0.683 \text{ mA}}$$

$$i_{C1} \approx 0$$

$$i_{B2} = i_{C2} = 0$$

$$i_{B0} = i_{C0} = 0$$

b.  $v_X = v_Y = 3.6 \text{ V}$

$$v_{B1} = 0.8 + 0.8 + 0.7 = 2.3 \text{ V}$$

$$i_1 = i_{B1} = \frac{5 - 2.3}{6} \Rightarrow \underline{i_1 = i_{B1} = 0.45 \text{ mA}}$$

$$i_{B2} = i_{B3} = i_1 \cdot \beta_R = (0.45)(0.1) = 0.045 \text{ mA}$$

$$i_{B2} = |i_{C1}| = i_1 + i_{B2} + i_{B3} = 0.45 + 2(0.045)$$

$$\underline{i_{B2} = |i_{C1}| = 0.54 \text{ mA}}$$

$$v_{C2} = 0.8 + 0.1 = 0.9$$

$$i_2 = i_{C2} = \frac{5 - 0.9}{1.5} \Rightarrow \underline{i_2 = i_{C2} = 2.73 \text{ mA}}$$

$$i_{B2} = 2.73 + 0.54 = 3.27 \text{ mA}$$

$$i_4 = \frac{0.8}{1.5} = 0.533 \text{ mA}$$

$$i_{B0} = 3.27 - 0.533 \Rightarrow \underline{i_{B0} = 2.74 \text{ mA}}$$

$$i_3 = i_{C0} = \frac{5 - 0.1}{2.2} \Rightarrow \underline{i_3 = i_{C0} = 2.23 \text{ mA}}$$

For  $Q_2$ :

$$\frac{i_{C2}}{i_{B2}} = \frac{2.73}{0.54} = 5.06 < \beta_F \Rightarrow Q_2 \text{ in saturation}$$

For  $Q_0$ :

$$\frac{i_{C0}}{i_{B0}} = \frac{2.23}{2.74} = 0.81 < \beta_F \Rightarrow Q_0 \text{ in saturation}$$

E17.15

a. Output low:

$$i'_L = \frac{5 - (0.1 + 0.8)}{6} = 0.683$$

$$i_{C0}(\text{max}) = \beta_F \cdot i_{B0} = N i'_L + i_3$$

$$(20)(2.74) = N(0.683) + 2.23$$

$$\Rightarrow \underline{N = 76}$$

b. Output high:

$Q'_1$  inverse active

$$i'_1 = \frac{5 - 2.3}{6} = 0.45 \text{ mA}$$

$$i'_L = \beta_R \cdot i'_1 = (0.1)(0.45) = 0.045 \text{ mA}$$

$$v_0(\text{min}) = 2.4 \text{ V} \Rightarrow i_L(\text{max}) = \frac{5 - 2.4}{2.2} - N \cdot i'_L$$

$$1.18 = N(0.045)$$

$$\Rightarrow \underline{N = 26}$$

E17.16

a.  $v_X = v_Y = 0.1 \text{ V} \Rightarrow v_0(\text{max}) = 3.6 \text{ V}$

$Q'_1$  inverse active

$$i'_1 = \frac{5 - 2.3}{6} = 0.45 \text{ mA}$$

$$i'_L = \beta_R \cdot i'_1 = (0.1)(0.45) = 0.045$$

$$i_{B3} = \frac{0.1}{2} = 0.05 \text{ mA}$$

$$i_L = (1 + \beta_F)i_{B3} = (21)(0.05) = 1.05 \text{ mA}$$

$$i_L = N i'_L \Rightarrow 1.05 = N(0.045) \Rightarrow \underline{N = 23}$$

b.  $v_X = v_Y = 3.6$  V, Output low:

$$i_1 = \frac{5 - 2.3}{6} = 0.45 \text{ mA}$$

$$i_{B2} = (1 + 2\beta_R)i_1$$

$$i_{B2} = 0.54 \text{ mA}$$

$$v_{B3} = 0.8 + 0.1 = 0.9$$

$$i_2 = \frac{5 - 0.9}{2} = 2.05 \text{ mA}$$

$$i_{B0} = 2.05 + 0.54 - \frac{0.8}{1.5} \Rightarrow i_{B0} = 2.06 \text{ mA}$$

$$i'_L = \frac{5 - 0.9}{6} = 0.683 \text{ mA}$$

$$\beta_F \cdot i_{B0} = N \cdot i'_L \Rightarrow (20)(2.06) = N(0.683) \\ \Rightarrow \underline{N = 60}$$

E17.17

a.  $v_X = v_Y = 3.6$  V

$$i_{B1} = \frac{5 - 2.3}{4} = 0.675 \text{ mA} = i_{B1} = |i_{C1}| = i_{B2}$$

$$v_{B4} = 0.8 + 0.1 = 0.9 \text{ V}$$

$$i_2 = \frac{5 - 0.9}{1.6} = 2.56 \text{ mA}$$

$$i_{B4} = \frac{0.2}{(1 + \beta_F)(4)} = \frac{0.2}{(31)(4)} \Rightarrow \underline{i_{B4} = 1.61 \mu\text{A}}$$

$$\underline{i_{C4} = 48.3 \mu\text{A}}$$

$$\underline{i_{B3} = i_{C3} = 0}$$

$$\Rightarrow \underline{i_{C2} \approx i_2 = 2.56 \text{ mA}}$$

$$i_{B0} = 2.45 + 0.675 - \frac{0.8}{1} \Rightarrow \underline{i_{B0} = 2.44 \text{ mA}}$$

One load:

$$i'_L = i_{C0} = \frac{5 - 0.9}{4} \Rightarrow \underline{i_{C0}(\text{max}) = 1.03 \text{ mA}}$$

b.  $v_X = v_Y = 0.1$  V

$$i_{B1} = \frac{5 - 0.9}{4} \Rightarrow \underline{i_{B1} = 1.03 \text{ mA}}$$

$$\underline{|i_{C1}| = i_{B2} = i_{C2} = 0}$$

$$\underline{i_{B0} = i_{C0} = 0}$$

Output high,  $\beta_R = 0 \Rightarrow i_{B3} = i_{C3} = 0$

$$5 = i_{B4}(1.6) + 0.7 + (31)i_{B4}(4)$$

$$\Rightarrow \underline{i_{B4} = 0.0342 \text{ mA}}$$

$$\underline{i_{C4} = 1.03 \text{ mA}}$$

E17.18

$Q_1$  in saturation

$$i_{B1} = \frac{5 - 0.9}{6} \Rightarrow \underline{i_{B1} = 0.683 \text{ mA}}$$

$$\underline{|i_{C1}| = i_{B2} = i_{C2} = 0}$$

$$\underline{i_{B0} = i_{C0} = 0}$$

$$v_{B4} = 0.1 + 0.7 = 0.8 \text{ V}$$

$$i_{B4} = \frac{0.1}{(21)(4)} \Rightarrow \underline{i_{B4} = 1.19 \mu\text{A}}$$

$$\underline{i_{C4} = 23.8 \mu\text{A}}$$

$$\underline{i_{B3} = i_{C3} = 0}$$

E17.19

a.  $i_{RC} = \frac{5 - 0.4}{2.25} = 2.04 \text{ mA}$

$$i'_C = \frac{2 + 2.04}{1 + \frac{1}{10}} \Rightarrow \underline{i'_C = 3.67 \text{ mA}}$$

$$\underline{i'_B = \frac{3.67}{10} = 0.367 \text{ mA}}$$

$$i_D = 2 - 0.367 \Rightarrow \underline{i_D = 1.63 \text{ mA}}$$

b.  $i_D = 0 \Rightarrow i'_B = i_B = 2 \text{ mA}$

$$i'_C = \beta i'_B = (10)(2) = 20 \text{ mA} = i_{RC} + i_L$$

$$i_L = 20 - 2.04 \Rightarrow \underline{i_L(\text{max}) \approx 18 \text{ mA}}$$

## Chapter 17

## Problem Solutions

17.1

a.  $v_I = -1.5 \text{ V}$ ;  $Q_1$  off,  $Q_2$  on

$$i_E = \frac{-0.7 - (-3.5)}{5} \Rightarrow i_E = 0.56 \text{ mA}$$

$$i_{C1} = 0 \Rightarrow v_{O1} = 3.5 \text{ V}$$

$$i_{C2} = i_E \Rightarrow v_{O2} = 3.5 - i_E R_{C2} = 3.5 - (0.56)(2)$$

or

$$v_{O2} = 2.38 \text{ V}$$

b.  $v_I = 1.0 \text{ V}$ ;  $Q_1$  on,  $Q_2$  off

$$i_E = \frac{(1 - 0.7) - (-3.5)}{5} \Rightarrow i_E = 0.76 \text{ mA}$$

$$i_{C2} = 0 \Rightarrow v_{O2} = 3.5 \text{ V}$$

c. logic 0 at  $v_{O2}$  (low level) = 2.38 V

Then

$$v_{O1} = 2.38 = 3.5 - (0.76)R_{C1}$$

or

$$R_{C1} = 1.47 \text{ k}\Omega$$

17.2

(a)  $Q_2$  on,  $v_E = -1.2 - 0.7 = -1.9 \text{ V}$ 

$$i_E = i_{C2} = \frac{-1.9 - (-5.2)}{2.5} = 1.32 \text{ mA}$$

$$v_2 = -1 \text{ V} = -i_{C2} R_{C2} = -(1.32)(R_{C2})$$

$$R_{C2} = 0.758 \text{ k}\Omega$$

(b)  $Q_1$  on,  $v_E = -0.7 - 0.7 = -1.40 \text{ V}$ 

$$i_E = i_{C1} = \frac{-1.4 - (-5.2)}{2.5} = 1.52 \text{ mA}$$

$$v_1 = -1 \text{ V} = -i_{C1} R_{C1} = -(1.52)(R_{C1})$$

$$R_{C1} = 0.658 \text{ k}\Omega$$

(c) For  $v_{in} = -0.7 \text{ V}$ ,  $Q_1$  on,  $Q_2$  off

$$\Rightarrow v_{O1} = -0.70 \text{ V}$$

$$v_{O2} = -1 - 0.7 \Rightarrow v_{O2} = -1.7 \text{ V}$$

For  $v_{in} = -1.7 \text{ V}$ ,  $Q_1$  off,  $Q_2$  on

$$\Rightarrow v_{O2} = -0.7 \text{ V}$$

$$v_{O1} = -1 - 0.7 \Rightarrow v_{O1} = -1.7 \text{ V}$$

(d) (i) For  $v_{in} = -0.7 \text{ V}$ ,  $i_E = 1.52 \text{ mA}$ 

$$i_{C4} = \frac{-1.7 - (-5.2)}{3} = 1.17 \text{ mA}$$

$$i_{C3} = \frac{-0.7 - (-5.2)}{3} = 1.5 \text{ mA}$$

$$P = (i_E + i_{C4} + i_{C3})(5.2) = (1.52 + 1.17 + 1.5)(5.2)$$

$$\text{or } P = 21.8 \text{ mW}$$

(ii) For  $v_{in} = -1.7 \text{ V}$ ,  $i_E = 1.32 \text{ mA}$ 

$$i_{C4} = \frac{-0.7 - (-5.2)}{3} = 1.5 \text{ mA}$$

$$i_{C3} = \frac{-1.7 - (-5.2)}{3} = 1.17 \text{ mA}$$

$$P = (1.32 + 1.5 + 1.17)(5.2)$$

$$\text{or } P = 20.7 \text{ mW}$$

17.3

$$\text{a. } I_3 = \frac{3.7 - 0.7}{0.67 + 1.33} = 1.5 \text{ mA}$$

$$V_R = I_3 R_4 + V_7 = (1.5)(1.33) + 0.7$$

or

$$V_R = 2.70 \text{ V}$$

b. logic 1 level =  $3.7 - 0.7 \Rightarrow 3.0 \text{ V}$ For  $v_X = v_Y = \text{logic 1}$ ,

$$i_E = \frac{3 - 0.7}{0.8} = 2.875 \text{ mA} = i_{RC1}$$

$$v_{B3} = 3.7 - (2.875)(0.21) = 3.10 \text{ V}$$

$$\Rightarrow v_{O1} (\text{logic 0}) = 2.4 \text{ V}$$

For  $v_X = v_Y = \text{logic 0}$ ,  $Q_R$  on

$$i_E = \frac{2.7 - 0.7}{0.8} = 2.5 \text{ mA} = i_{RC2}$$

$$v_{B4} = 3.7 - (2.5)(0.24) = 3.1 \text{ V}$$

$$\Rightarrow v_{O2} (\text{logic 0}) = 2.4 \text{ V}$$

17.4

$$V_R = \frac{\text{logic 1} + \text{logic 0}}{2} = \frac{1 + 0}{2} = 0.5 \text{ V}$$

For  $i_2 = 1 \text{ mA}$ 

$$R_5 = \frac{0.5 - (-2.3)}{1} \Rightarrow R_5 = 2.8 \text{ k}\Omega$$

For  $Q_R$  on,

$$i_E = \frac{V_R - V_{BE} - (-2.3)}{R_E}$$

or

$$R_E = \frac{0.5 - 0.7 + 2.3}{1} \Rightarrow R_E = 2.1 \text{ k}\Omega$$

$$V_{B2} = V_R + V_{BE} = 0.5 + 0.7 = 1.2 \text{ V}$$

$$i_1 = \frac{1.2 - 1.4 - (-2.3)}{R_2}$$

or

$$R_2 = \frac{1.2 - 1.4 + 2.3}{1} \Rightarrow \underline{R_2 = 2.1 \text{ k}\Omega}$$

$$R_1 = \frac{1.7 - 1.2}{1} \Rightarrow \underline{R_1 = 0.5 \text{ k}\Omega}$$

$$i_3 = \frac{1 - (-2.3)}{R_3} = 3 \Rightarrow \underline{R_3 = 1.1 \text{ k}\Omega}$$

$$i_4 = \frac{0 - (-2.3)}{R_4} = 3 \Rightarrow \underline{R_4 = 0.767 \text{ k}\Omega}$$

For  $Q_R$  on,

$$v_{OR} = \text{logic } 0 = 0 \text{ V} \Rightarrow v_{B3} = 0.7 \text{ V}$$

$$i_E = i_{CR} = 1 \text{ mA}$$

So

$$R_{C2} = \frac{1.7 - 0.7}{1} \Rightarrow \underline{R_{C2} = 1 \text{ k}\Omega}$$

For  $v_I = \text{logic } 1 = 1 \text{ V}$ ,

$$i_E = \frac{1 - 0.7 - (-2.3)}{2.1} = 1.238 \text{ mA}$$

For  $v_{NOR} = \text{logic } 0 = 0 \text{ V}$ ,

$$v_{B4} = 0.7 \text{ V}$$

Then

$$R_{C1} = \frac{1.7 - 0.7}{1.238} \Rightarrow \underline{R_{C1} = 0.808 \text{ k}\Omega}$$

17.5

Maximum  $i_E$  for  $v_I = \text{logic } 1 = 3.3 \text{ V}$

$$\text{Then } i_E = 5 \text{ mA} = \frac{3.3 - 0.7}{R_E} \Rightarrow \underline{R_E = 0.52 \text{ k}\Omega}$$

For  $v_{O2} = \text{logic } 1 = 3.3 \text{ V}$

$$i_{E3} = \frac{3.3 - 0}{R_3} = 5 \text{ mA}$$

or

$$\underline{R_3 = 0.66 \text{ k}\Omega}$$

By symmetry,

$$\underline{R_2 = 0.66 \text{ k}\Omega}$$

For  $Q_1$  on,

$$i_E = i_{RC1} = 5 \text{ mA} = \frac{4 - (2.7 + 0.7)}{R_{C1}}$$

So

$$\underline{R_{C1} = 0.12 \text{ k}\Omega}$$

For  $Q_R$  on,

$$i_E = \frac{3 - 0.7}{0.52} = 4.423 \text{ mA} = i_{RC2}$$

$$\text{and } i_{RC2} = 4.423 = \frac{4 - (2.7 + 0.7)}{R_{C2}}$$

$$\Rightarrow \underline{R_{C2} = 0.136 \text{ k}\Omega}$$

17.6

Neglecting base currents:

(a)  $I_{E1} = 0, I_{E3} = 0$

$$I_{E5} = \frac{5 - 0.7}{2.5} \Rightarrow \underline{I_{E5} = 1.72 \text{ mA}}$$

$$Y = 0.7 \text{ V}$$

(b)  $I_{E1} = \frac{5 - 0.7}{18} \Rightarrow \underline{I_{E1} = 0.239 \text{ mA}}$

$$I_{E3} = 0$$

$$I_{E5} = \frac{5 - 0.7}{2.5} \Rightarrow \underline{I_{E5} = 1.72 \text{ mA}}$$

$$Y = 0.7 \text{ V}$$

(c)  $I_{E1} = I_{E3} = \frac{5 - 0.7}{18} \Rightarrow \underline{I_{E1} = I_{E3} = 0.239 \text{ mA}}$

$$I_{E5} = 0, Y = 5 \text{ V}$$

(d) Same as (c).

17.7

(a)  $V_R = -(1)(1) - 0.7 \Rightarrow V_R = -1.7 \text{ V}$

(b)  $Q_R$  off, then  $v_{O1} = \text{Logic } 1 = -0.7 \text{ V}$

$Q_R$  on, then  $v_{O1} = -(1)(2) - 0.7 \Rightarrow$

$$v_{O1} = \text{Logic } 0 = -2.7 \text{ V}$$

$Q_A / Q_B$  off, then  $v_{O2} = \text{Logic } 1 = -0.7 \text{ V}$

$Q_A / Q_B$  on, then  $v_{O2} = -(1)(2) - 0.7 \Rightarrow$

$$v_{O2} = \text{Logic } 0 = -2.7 \text{ V}$$

(c)  $A = B = \text{Logic } 0 = -2.7 \text{ V}$ ,  $Q_R$  on,

$$V_E = -1.7 - 0.7 \Rightarrow V_E = -2.4 \text{ V}$$

$A = B = \text{Logic } 1 = -0.7 \text{ V}$ ,  $Q_A / Q_B$  on,

$$V_E = -0.7 - 0.7 \Rightarrow V_E = -1.4 \text{ V}$$

(d)  $A = B = \text{Logic } 1 = -0.7 \text{ V}$ ,  $Q_A / Q_B$  on,

$$i_{C3} = \frac{-2.7 - (-5.2)}{15} = 1.67 \text{ mA}$$

$$i_{C2} = \frac{-0.7 - (-5.2)}{15} = 3 \text{ mA}$$

$$P = (1.67 + 1 + 1 + 1 + 3)(5.2) \Rightarrow \underline{P = 39.9 \text{ mW}}$$

$$A = B = \text{Logic } 0 = -2.7 \text{ V}$$

$$i_{C3} = 3 \text{ mA}, i_{C2} = 1.67 \text{ mA}$$

$$P = 39.9 \text{ mW}$$

17.8

a. **AND logic function**

b. **logic 0 = 0 V**

$Q_3$  on,  $i = \frac{5 - (1.6 + 0.7)}{1.2} = 2.25 \text{ mA}$

$$V_2 = (2.25)(0.8) \Rightarrow \underline{\text{logic } 1 = 1.8 \text{ V}}$$

c.  $i_{E1} = \frac{5 - 0.7}{2.6} \Rightarrow i_{E1} = 1.65 \text{ mA}$

$i_{E2} = \frac{5 - (0.7 + 0.7)}{1.2} \Rightarrow i_{E2} = 3 \text{ mA}$

$i_{C1} = 0, i_{C2} = i_{E2} = 3 \text{ mA}$

$V_2 = 0$

d.  $i_{E1} = \frac{5 - (1.8 + 0.7)}{2.6} \Rightarrow i_{E1} = 0.962 \text{ mA}$

$i_{E2} = \frac{5 - (1.6 + 0.7)}{1.2} \Rightarrow i_{E2} = 2.25 \text{ mA}$

$i_{C2} = 0, i_{C1} = i_{E2} = 2.25 \text{ mA}$

$V_2 = 1.8 \text{ V}$

17.9

a.  $V_R = \frac{3.5 + 3.1}{2} - 0.7 \Rightarrow V_R = 2.6 \text{ V}$

b. For  $Q_1$  on,  $v_X = v_Y = \text{logic } 1 = 3.5 \text{ V}$

$i_E = \frac{3.5 - (0.7 + 0.7)}{12} = 0.175 \text{ mA}$

Want  $i_{RC1} = \frac{0.175}{2} = \frac{0.4}{R_{C1}} \Rightarrow R_{C1} = 4.57 \text{ k}\Omega$

c. For  $Q_2$  on,  $i_E = \frac{2.6 - 0.7}{12} = 0.158 \text{ mA}$

Want  $i_{RC2} = \frac{0.158}{2} = \frac{0.4}{R_{C2}} \Rightarrow R_{C2} = 5.06 \text{ k}\Omega$

d. For  $v_Y = \text{logic } 1 = 3.5 \text{ V}$

$i_{R1} = \frac{3.5 - 0.7}{8} = 0.35 \text{ mA}, i_E = 0.175 \text{ mA}$

$P = (i_{R1} + i_E)(V_{CC}) = (0.35 + 0.175)(3.5) \Rightarrow P = 1.84 \text{ mW}$

17.10

a.  $\text{logic } 1 = 0.2 \text{ V}$

$\text{logic } 0 = -0.2 \text{ V}$

b.  $i_E = \frac{(0 - 0.7) - (-3.1)}{R_E} = 0.8$

So

$R_E = 3 \text{ k}\Omega$

c. Want  $i_{R1} = \frac{0.8}{2} = \frac{0.4}{R_1} \Rightarrow R_1 = 1 \text{ k}\Omega$

d. For  $v_X = v_Y = \text{logic } 1 = 0.2 \text{ V}$

$i_E = \frac{(0.2 - 0.7) - (-3.1)}{3} = 0.867 \text{ mA}$

$i_{R2} = \frac{0.4}{1} \Rightarrow i_{R2} = 0.4 \text{ mA}$

$i_{D2} = 0.467 \text{ mA}$

e.  $i_E = 0.867 \text{ mA}$

$i_3 = \frac{0.2 - (-3.1)}{3.3} = 1 \text{ mA}$

$i_4 = \frac{-0.2 - (-3.1)}{3.3} = 0.879 \text{ mA}$

$P = (0.867 + 1 + 0.879)(0.9 - (-3.1))$

or

$P = 11.0 \text{ mW}$

17.11

a.  $i_1 = \frac{(-0.9 - 0.7) - (-3)}{1} \Rightarrow i_1 = 1.4 \text{ mA}$

$i_3 = \frac{(-0.2 - 0.7) - (-3)}{15} \Rightarrow i_3 = 0.14 \text{ mA}$

$i_4 = \frac{(-0.2 - 0.7) - (-3)}{15} \Rightarrow i_4 = 0.14 \text{ mA}$

$i_2 + i_D = i_1 + i_3 = 1.4 + 0.14 = 1.54 \text{ mA}$

$i_2 = \frac{0.4}{0.5} \Rightarrow i_2 = 0.8 \text{ mA}$

$i_D = 0.74 \text{ mA}$

$v_0 = -0.4 \text{ V}$

b.  $i_1 = 1.4 \text{ mA}$

$i_3 = \frac{(0 - 0.7) - (-3)}{15} \Rightarrow i_3 = 0.153 \text{ mA}$

$i_4 = i_3 \Rightarrow i_4 = 0.153 \text{ mA}$

$i_2 + i_D = i_4 \Rightarrow i_2 = 0.153 \text{ mA}$

$i_D = 0$

$v_0 = -(0.153)(0.5) \Rightarrow v_0 = -0.0765 \text{ V}$

c.  $i_1 = \frac{(0 - 0.7 - 0.7) - (-3)}{1} \Rightarrow i_1 = 1.6 \text{ mA}$

$i_3 = \frac{(-0.2 - 0.7) - (-3)}{15} \Rightarrow i_3 = 0.14 \text{ mA}$

$i_4 = i_3 \Rightarrow i_4 = 0.14 \text{ mA}$

$i_2 + i_D = i_3 \Rightarrow i_2 = 0.14 \text{ mA}$

$i_D = 0.0$

$v_0 = -(0.14)(0.5) \Rightarrow v_0 = -0.07 \text{ V}$

d.  $i_1 = \frac{(0 - 0.7 - 0.7) - (-3)}{1} \Rightarrow i_1 = 1.6 \text{ mA}$

$i_3 = \frac{(0 - 0.7) - (-3)}{15} \Rightarrow i_3 = 0.153 \text{ mA}$

$i_4 = i_3 \Rightarrow i_4 = 0.153 \text{ mA}$

$i_2 + i_D = i_1 + i_4 = 1.6 + 0.153 = 1.753 \text{ mA}$

$i_2 = \frac{0.4}{0.5} \Rightarrow i_2 = 0.8 \text{ mA}$

$i_D = 0.953 \text{ mA}$

$v_0 = -0.40 \text{ V}$

17.12

a. i.  $A = B = C = D = 0 \Rightarrow Q_1 - Q_4$  cutoff

So

$$V_{DD} = 2I_E R_1 + V_{EB} + I_B R_2$$

and

$$I_B = \frac{I_E}{1 + \beta_P} = \frac{I_E}{51}$$

Then

$$2.5 = 2I_E(2) + 0.7 + \frac{I_E}{51} \cdot (15)$$

$$2.5 - 0.7 = I_E \cdot \left(4 + \frac{15}{51}\right)$$

So

$$I_E = 0.419 \text{ mA}$$

and

$$Y = 2.5 - 2(0.419)(2) \Rightarrow Y = 0.824 \text{ V}$$

ii.  $A = C = 0, B = D = 2.5 \text{ V}$

Now

$$v_{B5} = v_{B6} = 2.5 - 0.7 = 1.8 \text{ V}$$

and

$$Y = v_{B5} + 0.7 \Rightarrow Y = 2.5 \text{ V}$$

b.  $Y = (A \text{ OR } B) \text{ AND } (C \text{ OR } D)$

17.13

a. logic 1 = 0 V

logic 0 = -0.4 V

b.  $v_{01} = \overline{A \text{ OR } B}$

$$v_{02} = \overline{C \text{ OR } D}$$

$$v_{03} = \overline{v_{01} \text{ OR } v_{02}}$$

or

$$v_{03} = (A \text{ OR } B) \text{ AND } (C \text{ OR } D)$$

17.14

a. For CLOCK = high,  $I_{DC}$  flows through the left side of the circuit. If  $D$  is high,  $I_{DC}$  flows through the left  $R$  resistor pulling  $\overline{Q}$  low. If  $D$  is low,  $I_{DC}$  flows through the right  $R$  resistor pulling  $Q$  low.

For CLOCK = low,  $I_{DC}$  flows through the right side of the circuit maintaining  $Q$  and  $\overline{Q}$  in their previous state.

b.  $P = (I_{DC} + 0.5I_{DC} + 0.1I_{DC} + 0.1I_{DC})(3)$

$$P = 1.7I_{DC}(3) = (1.7)(50)(3) \Rightarrow P = 255 \mu\text{W}$$

17.15

i. For  $v_X = v_Y = 0.1 \text{ V} \Rightarrow v' = 0.8 \text{ V}$

$$i_1 = \frac{5 - 2.2}{8} \Rightarrow i_1 = 0.525 \text{ mA}$$

$$i_3 = i_4 = 0$$

ii. For  $v_X = v_Y = 5 \text{ V}$ ,

$$v' = 0.8 + 0.7 + 0.7 \Rightarrow v' = 2.2 \text{ V}$$

$$i_1 = \frac{5 - 2.2}{8} \Rightarrow i_1 = 0.35 \text{ mA}$$

$$i_4 = i_1 - \frac{0.8}{15} \Rightarrow i_4 = 0.297 \text{ mA}$$

$$i_3 = \frac{5 - 0.1}{2.4} \Rightarrow i_3 = 2.04 \text{ mA}$$

17.16

a. For  $v_X = v_Y = 5 \text{ V}$ , both  $Q_1$  and  $Q_2$  driven into saturation.

$$v_1 = 0.8 + 0.7 + 0.8 \Rightarrow v_1 = 2.3 \text{ V}$$

$$i_1 = \frac{5 - 2.3}{4} \Rightarrow i_1 = i_{B1} = 0.675 \text{ mA}$$

$$i_2 = \frac{5 - (0.8 + 0.7 + 0.1)}{2} \Rightarrow i_2 = 1.7 \text{ mA}$$

$$i_4 = i_{B1} + i_2 \Rightarrow i_4 = 2.375 \text{ mA}$$

$$i_5 = \frac{0.8}{10} \Rightarrow i_5 = 0.08 \text{ mA}$$

$$i_{B2} = i_4 - i_5 \Rightarrow i_{B2} = 2.295 \text{ mA}$$

$$i_3 = \frac{5 - 0.1}{4} \Rightarrow i_3 = 1.225 \text{ mA}$$

$$v_0 = 0.1 \text{ V}$$

b.  $i'_L = \frac{5 - (0.1 + 0.7)}{4} = 1.05 \text{ mA}$

$$i_C(\text{max}) = \beta i_{B2} = N i'_L + i_3$$

$$(20)(2.295) = N(1.05) + 1.225$$

So

$$N = 42$$

17.17

$D_X$  and  $D_Y$  off,  $Q_1$  forward active mode

$$v_1 = 0.8 + 0.7 + 0.7 = 2.2 \text{ V}$$

$$5 = i_1 R_1 + i_2 R_2 + v_1 \text{ and } i_1 = (1 + \beta) i_2$$

$$\text{So } 5 - 2.2 = i_2 [(1 + \beta) R_1 + R_2]$$

Assume  $\beta = 25$

$$i_2 = \frac{5 - 2.2}{(26)(1.75) + 2} \Rightarrow i_2 = 0.0589 \text{ mA}$$

$$i_1 = (1 + \beta) i_2 = (26)(0.0589) \Rightarrow i_1 = 1.53 \text{ mA}$$

$$i_3 = \beta i_2 \Rightarrow i_3 = 1.47 \text{ mA}$$

$$i_{B0} = i_2 + i_3 - \frac{0.8}{5} = 0.0589 + 1.47 - 0.16 \Rightarrow$$

$$i_{B0} = 1.37 \text{ mA}$$

$Q_0$  in saturation

$$i_{C0} = \frac{5 - 0.1}{6} \Rightarrow i_{C0} = 0.817 \text{ mA}$$

17.18

 a. i.  $v_X = v_Y = 0.1$  V, so  $Q_1$  in saturation.

$$i_1 = \frac{5 - (0.1 + 0.8)}{6} \Rightarrow \underline{i_1 = 0.683 \text{ mA}}$$

$$\Rightarrow \underline{i_{B2} = i_2 = i_4 = i_{B3} = i_3 = 0}$$

 ii.  $v_X = v_Y = 5$  V, so  $Q_1$  in inverse active mode.  
Assume  $Q_2$  and  $Q_3$  in saturation.

$$i_1 = \frac{5 - (0.8 + 0.8 + 0.7)}{6} \Rightarrow \underline{i_1 = i_{B2} = 0.45 \text{ mA}}$$

$$i_2 = \frac{5 - (0.8 + 0.1)}{2} \Rightarrow \underline{i_2 = 2.05 \text{ mA}}$$

$$i_4 = \frac{0.8}{1.5} \Rightarrow \underline{i_4 = 0.533 \text{ mA}}$$

$$i_{B3} = (i_{B2} + i_2) - i_4 = 0.45 + 2.05 - 0.533$$

or

$$\underline{i_{B3} = 1.97 \text{ mA}}$$

$$i_3 = \frac{5 - 0.1}{2.2} \Rightarrow \underline{i_3 = 2.23 \text{ mA}}$$

 b. For  $Q_3$ :

$$\frac{i_3}{i_{B3}} = \frac{2.23}{1.97} = 1.13 < \beta$$

 For  $Q_2$ :

$$\frac{i_2}{i_{B2}} = \frac{2.05}{0.45} = 4.56 < \beta$$

 Since  $(I_C/I_B) < \beta$ , then each transistor is in saturation.

17.19

 (a)  $v_X = v_Y = \text{Logic 1}$ 

$$v' = 0.8 + 2(0.7) = 2.2 \text{ V}$$

$$i_1 = \frac{5 - 2.2}{8} = 0.35 \text{ mA}$$

$$i_4 = i_1 - \frac{0.8}{15} = 0.35 - 0.0533 = 0.2967 \text{ mA}$$

$$i_3 = \frac{5 - 0.1}{2.4} = 2.04 \text{ mA}$$

$$i'_L = \frac{5 - (0.1 + 0.7)}{8} = 0.525 \text{ mA}$$

 Assume  $\beta = 25$ 

$$\text{Then } (25)(0.2967) = 2.04 + N(0.525)$$

$$\text{So } N = 10.2 \Rightarrow \underline{N = 10}$$

(b) Now

$$5 = 2.04 + N(0.525)$$

$$\text{So } N = 5.64 \Rightarrow \underline{N = 5}$$

17.20

 a. For  $v_X = v_Y = 5$  V,  $Q$  in inverse active mode.

$$i_{B1} = \frac{5 - (0.8 + 0.8 + 0.7)}{6} = 0.45 \text{ mA}$$

$$i_{B2} = i_{B1} + 2\beta_R i_{B1} = 0.45(1 + 2[0.1]) = 0.54 \text{ mA}$$

$$i_{C2} = \frac{5 - (0.8 + 0.1)}{2} = 2.05 \text{ mA}$$

$$i_{B3} = (i_{B2} + i_{C2}) - \frac{0.8}{1.5} = 0.54 + 2.05 - 0.533$$

or

$$\underline{i_{B3} = 2.06 \text{ mA}}$$

Now

$$i'_L = \frac{5 - (0.1 + 0.8)}{6} = 0.683 \text{ mA}$$

Then

$$i_{C3}(\text{max}) = \beta_F i_{B3} = N i'_L$$

$$\text{or } (20)(2.06) = N(0.683)$$

$$\Rightarrow \underline{N = 60}$$

 b. From above, for  $v_o$  high,  $I'_L = (0.1)(0.45) = 0.045$  mA. Now

$$I'_L(\text{max}) = (1 + \beta_F) \left( \frac{5 - 4.9}{R_2} \right) = \frac{(21)(0.1)}{2} = 1.05 \text{ mA}$$

So

$$I_L(\text{max}) = N I'_L$$

$$\text{or } 1.05 = N(0.045)$$

$$\Rightarrow \underline{N = 23}$$

17.21

 (a)  $V_{in} = 0.1$  V:  $Q_1$ , Sat;  $Q_2$ ,  $Q_3$ , Cutoff

$$i_1 = \frac{5 - (0.1 + 0.8)}{4} = 1.025 \text{ mA}$$

$$P = i_1(5 - 0.1) = (1.025)(4.9) \Rightarrow$$

$$P = 5.02 \text{ mW}$$

 (b)  $V_{in} = 5$  V,  $Q_1$ , Inverse Active;  $Q_2$ ,  $Q_3$ ,

Saturation

$$v_{B1} = 0.7 + 0.8 + 0.7 = 2.2 \text{ V}$$

$$i_1 = \frac{5 - 2.2}{4} = 0.7 \text{ mA}$$

$$i_{B2} = \beta_R \cdot i_1 = (0.1)(0.7) = 0.07 \text{ mA}$$

$$V_{out} = 0.7 + 0.1 = 0.8 \text{ V}$$

$$i_2 = \frac{5 - 0.8}{1} = 4.2 \text{ mA}$$

$$P = (i_1 + i_{B2} + i_2)(5) = (0.7 + 0.07 + 4.2)(5) \Rightarrow$$

$$P = 24.9 \text{ mW}$$

17.22

a.  $v_X = v_Y = v_Z = 0.1 \text{ V}$

$$i_{B1} = \frac{5 - (0.1 + 0.8)}{3.9} \Rightarrow \underline{i_{B1} = 1.05 \text{ mA}}$$

Then

$$\underline{i_{C1} = i_{B2} = i_{C2} = i_{B3} = i_{C3} = 0}$$

b.  $v_X = v_Y = v_Z = 5 \text{ V}$

$$i_{B1} = \frac{5 - (0.8 + 0.8 + 0.7)}{3.9} \Rightarrow \underline{i_{B1} = 0.692 \text{ mA}}$$

Then

$$i_{C1} = i_{B2} = i_{B1}(1 + 3\beta_R) = (0.692)(1 + 3[0.5]) \Rightarrow \underline{i_{C1} = i_{B2} = 1.73 \text{ mA}}$$

$$i_{C2} = \frac{5 - (0.1 + 0.8)}{2} \Rightarrow \underline{i_{C2} = 2.05 \text{ mA}}$$

$$i_{B3} = i_{B2} + i_{C2} - \frac{0.8}{0.8} = 1.73 + 2.05 - 1.0 \Rightarrow \underline{i_{B3} = 2.78 \text{ mA}}$$

$$i_{R3} = \frac{5 - 0.1}{2.4} = 2.04 \text{ mA}$$

$$i'_L = \frac{5 - (0.1 + 0.8)}{3.9} = 1.05 \text{ mA}$$

$$i_{C3} = i_{R3} + 5i'_L = 2.04 + (5)(1.05) \Rightarrow \underline{i_{C3} = 7.29 \text{ mA}}$$

17.23

a.  $v_X = v_Y = v_Z = 2.8 \text{ V}$ ,  $Q_1$  biased in the inverse active mode.

$$i_{B1} = \frac{2.8 - (0.8 + 0.8 + 0.7)}{2} \Rightarrow \underline{i_{B1} = 0.25 \text{ mA}}$$

$$i_{B2} = i_{B1}(1 + 3\beta_R) = 0.25(1 + 3[0.3]) \Rightarrow \underline{i_{B2} = 0.475 \text{ mA}}$$

$$v_{C2} = 0.8 + 0.1 = 0.9 \text{ V}$$

$$i_{B4} = \frac{0.9 - (0.7 + 0.1)}{(1 + \beta_F)(0.5)} = \frac{0.1}{(101)(0.5)} = 0.00198 \text{ mA (Negligible)}$$

$$i_{R2} = \frac{5 - 0.9}{0.9} = 4.56 \text{ mA} \Rightarrow \underline{i_{C2} = 4.56 \text{ mA}}$$

$$i_{B3} = i_{B2} + i_{C2} - \frac{0.8}{1} = 0.475 + 4.56 - 0.8 \Rightarrow \underline{i_{B3} = 4.235 \text{ mA}}$$

b.  $v_X = v_Y = v_Z = 0.1 \text{ V}$

$$i_{B1} = \frac{5 - (0.1 + 0.8)}{2} \Rightarrow \underline{i_{B1} = 2.05 \text{ mA}}$$

From part (a),

$$i'_L = \beta_R \cdot i_{B1} = (0.3)(2.05) = 0.075 \text{ mA}$$

Then

$$i_{B4} = \frac{5i'_L}{1 + \beta_F} = \frac{5(0.075)}{101} \Rightarrow \underline{i_{B4} = 0.00371 \text{ mA}}$$

17.24

a.  $v_X = v_Y = v_Z = 0.1 \text{ V}$

$$i_{B1} = \frac{5 - (0.1 + 0.8)}{R_{B1}} + i_{B3}$$

where

$$i_{B3} = \frac{(2 - 0.7) - (0.9)}{R_{B2}} = \frac{0.4}{1} \Rightarrow \underline{i_{B3} = 0.4 \text{ mA}}$$

Then

$$i_{B1} = \frac{1.1}{1} + 0.4 \Rightarrow \underline{i_{B1} = 1.5 \text{ mA}}$$

$$\underline{i_{B2} = 0 = i_{C2}}$$

$Q_3$  in saturation  $i_{C3} = 5i'_L$   
For  $v_o$  high,

$$v'_{B1} = 0.8 + 0.7 = 1.5 \text{ V} \Rightarrow Q'_3 \text{ off}$$

$$i'_{B1} = \frac{2 - 1.5}{1} = 0.5 \text{ mA}$$

$$i'_L = \beta_R i'_{B1} = (0.2)(0.5) = 0.1 \text{ mA}$$

Then

$$\underline{i_{C3} = 0.5 \text{ mA}}$$

b.  $v_X = v_Y = v_Z = 2 \text{ V}$

From part (a),

$$\Rightarrow \underline{i_{B1} = 0.5 \text{ mA}}$$

$$\underline{i_{B3} = 0 = i_{C3}}$$

$$i_{B2} = i_{B1}(1 + 3\beta_R) = (0.5)(1 + 3[0.2])$$

$$\underline{i_{B2} = 0.8 \text{ mA}}$$

$$i_{C2} = 5i'_L, \text{ and from part (a), } i'_L = 1.5 \text{ mA}$$

So

$$\underline{i_{C2} = 7.5 \text{ mA}}$$

17.25

$$(a) I_B + I_D = \frac{5.8 - 0.7}{10} = 0.51 \text{ mA}$$

$$I_C - I_D = \frac{5 - (0.7 - 0.3)}{1} = 4.6 \text{ mA}$$

Now

$$I_D = 0.51 - I_B = 0.51 - \frac{I_C}{\beta} = 0.51 - \frac{I_C}{50}$$

Then

$$I_C - I_D = I_C - \left(0.51 - \frac{I_C}{50}\right) = I_C \left(1 + \frac{1}{50}\right) - 0.51 = 4.6$$

So  $I_C = 5.01 \text{ mA}$ 

$$I_B = \frac{I_C}{\beta} = \frac{5.01}{50} \Rightarrow I_B = 0.1002 \text{ mA}$$

$$I_D = 0.51 - 0.1002 \Rightarrow I_D = 0.4098 \text{ mA}$$

$$V_{CE} = 0.4 \text{ V}$$

$$(b) I_D = 0, V_{CE} = V_{CE}(\text{sat}) = 0.1 \text{ V}$$

$$I_B = \frac{5.8 - 0.8}{10} \Rightarrow I_B = 0.5 \text{ mA}$$

$$I_C = \frac{5 - 0.1}{1} \Rightarrow I_C = 4.9 \text{ mA}$$

17.26

$$a. \quad v_X = v_Y = 0.4 \text{ V}$$

$$v_{B1} = 0.4 + 0.7 \Rightarrow v_{B1} = 1.1 \text{ V}$$

$$i_{B1} = \frac{5 - 1.1}{2.8} \Rightarrow i_{B1} = 1.39 \text{ mA}$$

$$v_{B2} = 0.4 + 0.4 \Rightarrow v_{B2} = 0.8 \text{ V}$$

$$i_{B2} = i_{C2} = i_{B0} = i_{C0} = i_{B5} = i_{C5}$$

$$= i_{B3} = i_{C3} = 0 \text{ (No load)}$$

$$5 = i_{B4} R_2 + V_{BE} + (1 + \beta) i_{B4} R_4$$

$$i_{B4} = \frac{5 - 0.7}{0.76 + (31)(3.5)}$$

$$\Rightarrow i_{B4} = 0.0394 \text{ mA}$$

$$i_{C4} = \beta F i_{B4}$$

$$\Rightarrow i_{C4} = 1.18 \text{ mA}$$

$$v_{B4} = 5 - (0.0394)(0.76)$$

$$\Rightarrow v_{B4} = 4.97 \text{ V}$$

$$b. \quad v_X = v_Y = 3.6 \text{ V}$$

$$v_{B1} = 0.7 + 0.7 + 0.3 \Rightarrow v_{B1} = 1.7 \text{ V}$$

$$v_{B2} = 1.4 \text{ V}$$

$$v_{B0} = 0.7 \text{ V}$$

$$v_{C2} = 1.1 \text{ V}$$

$$i_{B1} = \frac{5 - 1.7}{2.8}$$

$$\Rightarrow i_{B1} = 1.18 \text{ mA}$$

$$i_{B2} = i_{B1}(1 + 2\beta_R) = 1.18(1 + 2[0.1])$$

$$i_{B2} = 1.42 \text{ mA}$$

$$i_{B4} = \frac{1.1 - 0.7}{(31)(3.5)}$$

$$\Rightarrow i_{B4} = 0.00369 \text{ mA}$$

$$i_{R2} = \frac{5 - 1.1}{0.76} = 5.13 \text{ mA}$$

$$\Rightarrow i_{C2} \approx 5.13 \text{ mA}$$

$$i_{B0} \approx i_{B2} + i_{C2}$$

$$i_{B0} = 6.55 \text{ mA}$$

17.27

a. Assuming the output transistor  $Q_2$  is a Schottky transistor, then

$$v_0 = 0.4 \text{ V}, i'_L = \frac{2.5 - (0.4 + 0.3)}{R_{B1}} = 0.5$$

Then

$$R_{B1} = 3.6 \text{ k}\Omega$$

Then

$$i_{B1} = \frac{2.5 - (0.7 + 0.8)}{R_{B1}} = \frac{10}{3.6} = 0.278 \text{ mA}$$

$$i_{B2} = 0.5 \text{ mA}, i_{E1} = 0.5 + \frac{0.7}{0.7} = 1.50 \text{ mA}$$

$$i_{E1} = i_{B1} + i_{C1} \Rightarrow i_{C1} = 1.50 - 0.278 = 1.222 \text{ mA}$$

$$\text{and } i_{C1} = \frac{2.5 - (0.7 + 0.1)}{R_{C1}} = 1.222 \text{ mA}$$

$$\Rightarrow R_{C1} = 1.39 \text{ k}\Omega$$

$$b. \quad v_X = v_Y = 0.4 \text{ V}, v_{B1} = 0.7 \text{ V}$$

$$v_{C2} = 2.5 - 0.7 \Rightarrow v_{C2} = 1.8 \text{ V}$$

All transistor currents are zero.

$$c. \quad v_{B1} = 1.5 \text{ V}, v_{C1} = 0.8 \text{ V}$$

Currents calculated in part (a).

$$d. \quad i_{B2} = 0.5 \text{ mA}, i'_L = 0.5 \text{ mA}$$

$$i_{C2}(\text{max}) = \beta i_{B2} = N i'_L \text{ or } (50)(0.5) = N(0.5)$$

So

$$N = 50$$

17.28

$$a. \quad \text{For } v_X = v_Y = 3.6 \text{ V}$$

$$v_{B1} = 3(0.7) = 2.1$$

$$\Rightarrow i_{B1} = \frac{5 - 2.1}{10} = 0.29 \text{ mA}$$

$$v_{C1} = 0.7 + 0.7 + 0.4 = 1.8 \text{ V}$$

$$\Rightarrow i_{C1} = \frac{5 - 1.8}{10} = 0.32 \text{ mA}$$

$$i_{B2} = i_{B1} + i_{C1} - \frac{1.4}{15} = 0.29 + 0.32 - 0.0933$$

So

$$i_{B2} = 0.517 \text{ mA}$$

$$v_{C2} = 0.7 + 0.4 = 1.1 \text{ V}$$

$$i_{C2} = \frac{5 - 1.1}{4.1} = 0.951 \text{ mA}$$

$$i_{B5} = i_{B2} + i_{C2} - \frac{0.7}{4} = 0.517 + 0.951 - 0.175$$

$$\text{or } i_{B5} = 1.293 \text{ mA}$$

$$\text{For } v_0 = 0.4 \text{ V, } v'_{B1} = 0.4 + 0.7 = 1.1 \text{ V}$$

Then

$$i'_{B1} = \frac{1.1 - 0.7}{(31)(15)} = 0.00086 \text{ mA}$$

$$i'_L = \frac{5 - 1.1}{10} - 0.00086 \text{ or } i'_L \approx 0.39 \text{ mA}$$

$$\text{So } i_{C5}(\text{max}) = \beta i_{B5} = N i'_L$$

$$(30)(1.293) = N(0.39)$$

$$\Rightarrow N \approx 99$$

$$\text{b. } P = (0.29 + 0.32 + 0.951)(5) + (99)(0.39)(0.4)$$

$$P = 7.805 + 15.444 \text{ or } P \approx 23.2 \text{ mW}$$

(Assuming 99 load circuits which is unreasonably large.)

17.29

$$\text{a. Assume no load. For } v_X = \text{logic } 0 = 0.4 \text{ V}$$

$$i_{E1} = \frac{5 - (0.4 + 0.7)}{40} = 0.0975 \text{ mA}$$

Essentially all of this current goes to ground from  $V_{CC}$ .

$$P = i_{E1} \cdot V_{CC} = (0.0975)(5)$$

$$\Rightarrow P \approx 0.4875 \text{ mW}$$

$$\text{b. } i_{R1} = \frac{5 - (3)(0.7)}{40} = 0.0725 \text{ mA}$$

$$i_{R2} = \frac{5 - (0.7 + 0.7 + 0.4)}{50} = 0.064 \text{ mA}$$

$$i_{R3} = \frac{5 - (0.7 + 0.4)}{15} = 0.26 \text{ mA}$$

$$P = (0.0725 + 0.064 + 0.26)(5)$$

$$P \approx 1.98 \text{ mW}$$

$$\text{c. For } v_0 = 0, v_{C7} = 0.7 + 0.4 = 1.1 \text{ V}$$

$$i_{R7} = \frac{5 - 1.1}{0.050} \Rightarrow i_{R7} = 78 \text{ mA} \approx i_{SC}$$

17.30

$$\text{(a) } v_i = v_o = 2.5 \text{ V ; A transient situation}$$

$$v_{DS}(M_N) = 2.5 - 0.7 = 1.8 \text{ V}$$

$$v_{GS}(M_N) = 2.5 - 0.7 = 1.8 \text{ V} \Rightarrow M_N \text{ in saturation}$$

$$v_{SD}(M_P) = 5 - (2.5 + 0.7) = 1.8 \text{ V}$$

$$v_{SG}(M_P) = 5 - 2.5 = 2.5 \text{ V} \Rightarrow M_P \text{ in saturation}$$

$$i_{DN} = K_n(v_{GSN} - V_{TN})^2 = (0.1)(1.8 - 0.8)^2 \Rightarrow$$

$$i_{DN} = 0.1 \text{ mA}$$

$$i_{DP} = K_p(v_{SGP} + V_{TP})^2 = (0.1)(2.5 - 0.8)^2 \Rightarrow$$

$$i_{DP} = 0.289 \text{ mA}$$

$$i_{C1} = \beta i_{DP} = (50)(0.289) \Rightarrow i_{C1} = 14.45 \text{ mA}$$

$$i_{C2} = \beta i_{DN} = (50)(0.1) \Rightarrow i_{C2} = 5 \text{ mA}$$

Difference between  $i_{E1}$  and  $i_{DN} + i_{C2}$  is a load current.

$$\text{(b) Assume } i_{C1} = 14.45 \text{ mA is a constant}$$

$$V_C = \frac{1}{C} \int i_{C1} dt = \frac{i_{C1} \cdot t}{C} \Rightarrow t = \frac{(V_C)(C)}{i_{C1}}$$

$$t = \frac{(5)(15 \times 10^{-12})}{14.45 \times 10^{-3}} \Rightarrow t = 5.19 \text{ ns}$$

$$\text{(c) } t = \frac{(5)(15 \times 10^{-12})}{0.289 \times 10^{-3}} \Rightarrow t = 260 \text{ ns}$$

17.31

$$\text{Let } R_1 = R_2 = 10 \text{ k}\Omega$$

$$\text{(a) } i_{DN} = 0.1 \text{ mA, } i_{DP} = 0.289 \text{ mA}$$

(Same as Problem 17.30)

$$i_{R1} = \frac{0.7}{10} = 0.07 \text{ mA} \Rightarrow i_{B1} = 0.289 - 0.07 = 0.219 \text{ mA}$$


$$i_{C1} = (50)(0.219) \Rightarrow i_{C1} = 10.95 \text{ mA}$$

$$i_{R2} = \frac{0.7}{10} = 0.07 \text{ mA} \Rightarrow i_{B2} = 0.1 - 0.07 = 0.03 \text{ mA}$$

$$i_{C2} = (50)(0.03) \Rightarrow i_{C2} = 1.5 \text{ mA}$$

$$\text{(b) } t = \frac{(5)(15 \times 10^{-12})}{10.95 \times 10^{-3}} \Rightarrow t = 6.85 \text{ ns}$$

$$\text{(c) } t = 260 \text{ ns (Same as Problem 17.30)}$$

*McGraw-Hill Higher Education*   
A Division of The McGraw-Hill Companies

ISBN 0-07-232092-3



[www.mhhe.com](http://www.mhhe.com)