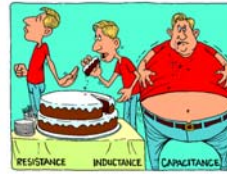



# Frequency response

- Static analysis
  - Low frequency response
  - Response without time dependent elements
- Real circuit response
  - Strongly dependent on frequency
  - Small signal behavior with reactive passives
    - capacitances
      - Planar technology have parasitic capacitors all over the place
    - Inductors
    - Reactances are also constructive



Typical operational amplifier response



- Gain strongly dependent on frequency

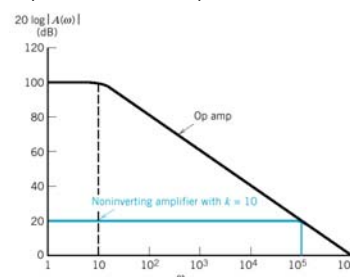

1
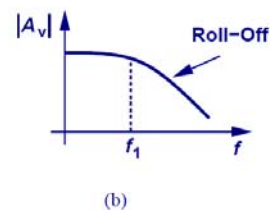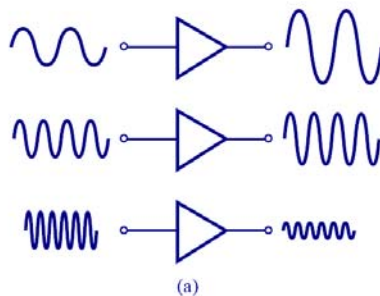
# Frequency response

- Signal out changing with input signal frequency




- Magnitude (amplitude) may change
- Phase (delay) may change

2

## Passive low-pass filter example



- Passive filter

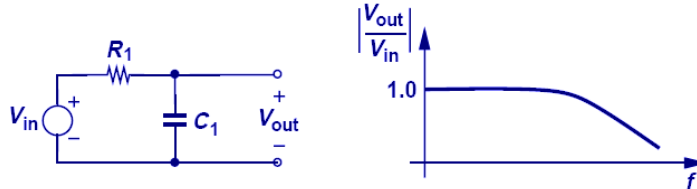



- high impedance a low frequency
- Reduced impedance with increasing frequency
- Giving gain of 1 in passband
- Higher frequencies → reduced gain (transition band)
- Phase?
- Circuit behavior with time-dependent elements

3

## Laplace transform



- Solving differential equations
  - Differentials → polynomials
- Reactive circuit elements time dependent
  - Capacitor:  $i(t) = C \frac{\partial V}{\partial t}$   Open at low frequency  
Short at high frequency
  - Inductor:  $v(t) = L \frac{\partial i}{\partial t}$   Short at low frequency  
Open at high frequency
- Laplace enable frequency analysis directly in frequency domain
  - Analysis for circuit performances
  - Analysis for circuit stability

4

## Transfer function



- In frequency domain (Laplace transformed from time-domain)

$$X_{out}(s) = H(s) X_{in}(s)$$

- Limited types of transfer functions
  - Stick to real values (avoid complex voltages and currents)
  - Limited to lumped circuit

- Transfer function form

$$H(s) = \frac{a_0 + a_1 s + \dots + a_m s^m}{1 + b_1 s + b_2 s^2 + \dots + b_n s^n}$$

- a and b are reals and normally  $m \leq n$
- All b positive for stability

- Alternative forms

$$H(s) = K \frac{(s + z_1)(s + z_2) \dots (s + z_m)}{(s + \omega_1)(s + \omega_2) \dots (s + \omega_n)} = a \frac{\left(1 + \frac{s}{z_1}\right) \left(1 + \frac{s}{z_2}\right) \dots \left(1 + \frac{s}{z_m}\right)}{\left(1 + \frac{s}{\omega_1}\right) \left(1 + \frac{s}{\omega_2}\right) \dots \left(1 + \frac{s}{\omega_n}\right)}$$

5

## Poles and zeros



$$H(s) = K \frac{(s + z_1)(s + z_2) \dots (s + z_m)}{(s + \omega_1)(s + \omega_2) \dots (s + \omega_n)} = a \frac{\left(1 + \frac{s}{z_1}\right) \left(1 + \frac{s}{z_2}\right) \dots \left(1 + \frac{s}{z_m}\right)}{\left(1 + \frac{s}{\omega_1}\right) \left(1 + \frac{s}{\omega_2}\right) \dots \left(1 + \frac{s}{\omega_n}\right)}$$

- Poles and zeros are real or complex conjugates
- The actual roots are the *negatives* of the poles and zeros
- Referred to as a positive frequency

- Magnitude and phase

Euler's formula

- Sinusoidal:  $x_{in}(t) = A_m \cos(\omega_m t) = A_m \frac{e^{j\omega_m t} + e^{-j\omega_m t}}{2}$

- Frequency domain two solutions  $s = j\omega_m$  and  $s = -j\omega_m$

- May find for particular  $s = j\omega_m$ :

$$x_{out}(t) = \frac{A_m}{2} |H(j\omega_m)| \left( e^{j(\omega_m t + \phi)} + e^{-j(\omega_m t + \phi)} \right) = A_m |H(j\omega_m)| \cos(\omega_m t + \phi)$$

- Where magnitude is  $|H(j\omega_m)|$  and phase  $\phi = \angle H(j\omega_m)$

6



## Impulse response



- Large signal step response
  - Slur-rate
    - Sharp transition → less steep
    - Problem in digital and analog
  - Ringing
    - More or less damped oscillations
    - Signal distortion



- Step response function

– Laplace  $u(t) = \begin{cases} 0 & \text{for } t \leq 0 \\ 1 & \text{for } t > 0 \end{cases} \quad U(s) = \frac{1}{s}$

- Output of linear system and step response

$$X_{out}(s) = A_{in} \frac{H(s)}{s}$$

9

## Slur rate



- Frequency → time

- 1. order LP filter

$$H(s) = \frac{A_0}{1 + \frac{s}{\omega_0}}$$

- Applied step response

$$X_{out}(s) = A_{in} \frac{1}{s} \frac{A_0}{1 + \frac{s}{\omega_0}}$$

- Residue method

$$X_{out}(s) = A_{in} A_0 \left[ \frac{1}{s} - \frac{1}{s + \omega_0} \right]$$

- Inverse Laplace give time domain

$$x_{out}(t) = u(t) A_{in} A_0 \left( 1 - e^{-\frac{t}{\tau}} \right) \quad \tau = \frac{1}{\omega_0}$$

10


## Slur rate with zero



- May be extended

$$H(s) = A_0 \frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{\omega_0}}$$

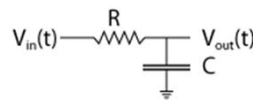- And solved  $x_{out}(t) = u(t) A_{in} A_0 \left( 1 - \left[ 1 - \frac{\omega_0}{\omega_z} \right] e^{-\frac{t}{\tau}} \right)$
- Example: 1. order passive LP filter




$$H(s) = \frac{1}{1 + sRC} \quad \omega_0 = \frac{1}{RC}$$

$$R = 10\Omega \text{ and } C = 0.1\mu F \rightarrow RC = 0.000001 \quad f_{-3dB} = \frac{1}{2\pi RC} = 1.59kHz$$

– Time constant:

– Voltage at  $2\mu s$  assuming 1V supply:  $RC = 10\mu s$
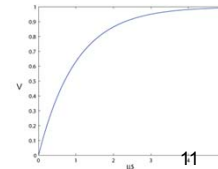
$$x_{out}(t + 2\mu s) = 1 \left( 1 - e^{-\frac{2 \cdot 10^{-6}}{10^{-6}}} \right) = 1 - e^{-2} = 0.8647V$$



## 2. order LP transfer function



- Real roots

$$H(s) = \frac{K}{(1 + s\tau_1)(1 + s\tau_2)} = \frac{K}{\left(1 + \frac{s}{\omega_{p1}}\right)\left(1 + \frac{s}{\omega_{p2}}\right)} = \frac{K\omega_{p1}\omega_{p2}}{(s + \omega_{p1})(s + \omega_{p2})}$$

- Coefficients real and positive or conjugate pairs

– Popular form

$$H(s) = \frac{K\omega_{p1}\omega_{p2}}{\omega_{p1}\omega_{p2} + s(\omega_{p1} + \omega_{p2}) + s^2} = \frac{K\omega_0^2}{\omega_0^2 + s\frac{\omega_0}{Q} + s^2}$$

–  $\omega_0$  – resonant frequency, Q – Q (quality) factor and K DC gain

– Avoiding complex numbers (almost)

## 2. order transfer



- Analyze some cases
  - May equate denominators

$$H(s) = \frac{K\omega_0^2}{\omega_0^2 + s\frac{\omega_0}{Q} + s^2}$$

$$D(s) = \omega_0^2 + s\frac{\omega_0}{Q} + s^2 = (s + \omega_{p1})(s + \omega_{p2}) = \omega_{p1}\omega_{p2} + s(\omega_{p1} + \omega_{p2}) + s^2$$

$$\text{Equating coefficients: } \omega_0^2 = \omega_{p1}\omega_{p2} \quad \frac{\omega_0}{Q} = (\omega_{p1} + \omega_{p2})$$

- Solving yields

$$\omega_{p1}, \omega_{p2} = \frac{\omega_0}{2Q} (1 \pm \sqrt{1 - 4Q^2})$$

- Assuming roots  $\omega_{p1} \ll \omega_{p2}$  giving  $Q \ll 1$  and  $\sqrt{1 - 4Q^2} \cong 1 - 2Q^2$

$$\omega_{p1} \approx \omega_0 Q \quad \omega_{p2} \approx \frac{\omega_0}{Q}$$

13

## Simplifications for 2. order LP



- $\omega \ll \omega_{p1}$

$$|H(\omega)| = K$$

- $\omega = \omega_{p1}$

$$|H(\omega)| = \frac{K}{\sqrt{2}} \quad \angle H(\omega) = -45^\circ$$

- $\omega_{p1} < \omega < \omega_{p2}$


$$|H(\omega)| = \frac{K\omega_{p1}}{\omega} \quad \angle H(\omega) \cong -90^\circ$$

- $\omega = \omega_{p2}$

$$|H(\omega)| = \frac{K\omega_{p1}}{\sqrt{2}\omega_{p2}} \quad \angle H(\omega) \cong -135^\circ$$

- $\omega > \omega_{p2}$


$$|H(\omega)| = \frac{K\omega_{p1}\omega_{p2}}{\omega^2} \quad \angle H(\omega) \cong -180^\circ$$

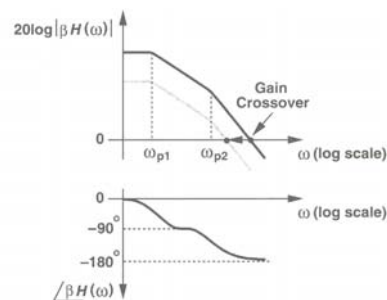

14

## Bode plot


- 1. order system

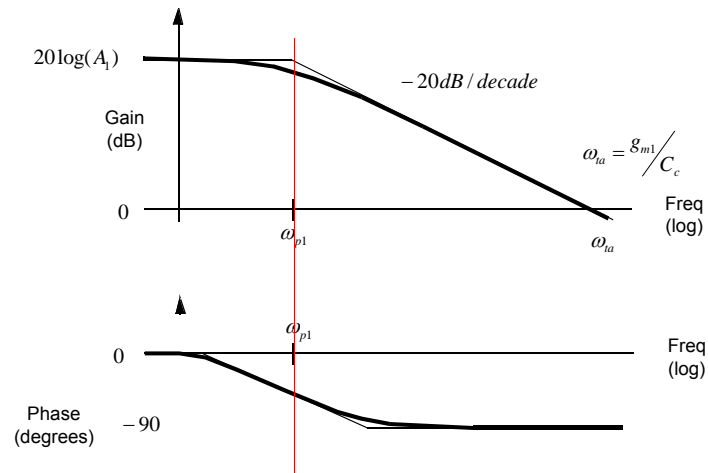

15

## Bode plot

- 2. order system

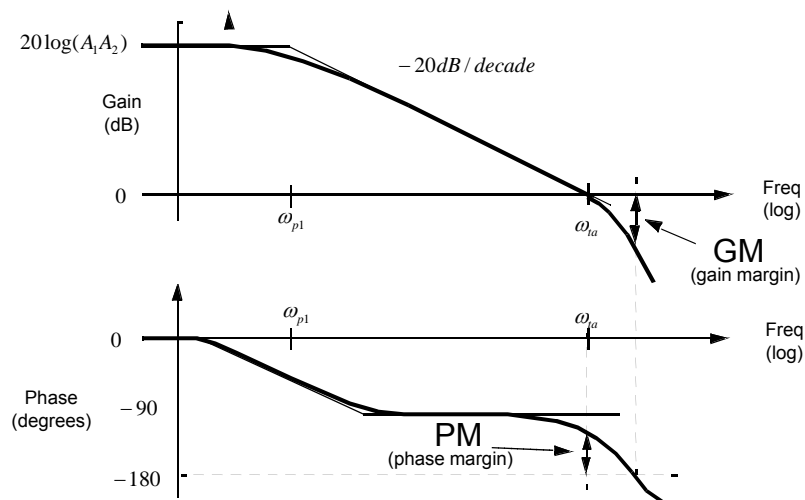

High frequency pole may give instability

16



## Analytical stability analysis



Determine stability

–  $\omega_0$  -- pole frequency

– Q – quality factor

$Q < 0.5$

• No overshoot (only real poles)

• Unconditionally stable

• Max magnitude at DC

$0.5 < Q < \sqrt{1/2} = 0.707$

• Ringing overshoot  $\%overshoot = 100e^{-\pi\sqrt{4Q^2-1}}$

$Q = \sqrt{1/2}$

• Critically damped system

• -3db frequency is  $\omega_0$

$Q > \sqrt{1/2}$

• Unstable and oscillations may occur

• May be carefully used for improved performance

$$A(s) = A(0) \frac{N(s)}{1 + \frac{s}{\omega_0 Q} + \frac{s^2}{\omega_0^2}}$$

17

## MOS caps in active region



• Gate capacitance

$$C_{gs} = \frac{2}{3} W L C_{ox}$$

• Fringing capacitances

– Overlap

$$C_{ov} = W L_{ov} C_{ox} \Rightarrow$$

$$C_{gs} = W C_{ox} \left( \frac{2}{3} L + L_{ov} \right)$$

• Source-bulk capacitance (+channel cap when present)


$$C'_{sb} = (A_s + A_{ch}) \frac{C_{j0}}{\sqrt{1 + V_{SB}/\Phi_0}}$$

$A_s$  – source area

$A_{ch}$  – channel area

$C_{j0}$  – unit depletion capacitance at 0V

$\Phi_0$  – build in junction potential

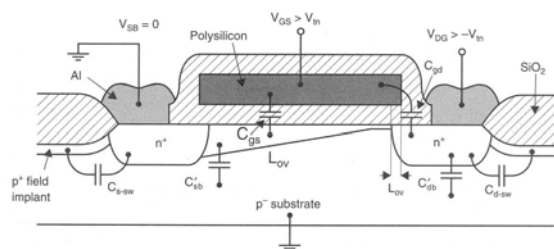

18

## MOS model active region



- Drain-bulk capacitance

$$C'_{sb} = A_D \frac{C_{j0}}{\sqrt{1 + V_{DB}/\Phi_0}}$$

- Gate-drain overlap
  - Miller capacitance

$$C_{gd} = C_{ox} W L_{ov}$$

- Sidewall capacitances

$$C_{s-sw} = P_S \frac{C_{j-sw0}}{\sqrt{1 + V_{DB}/\Phi_0}}$$


$$C_{d-sw} = P_D \frac{C_{j-sw0}}{\sqrt{1 + V_{SB}/\Phi_0}}$$

$P_{S(D)}$  – source (drain) perimeter

$C_{j-sw0}$  – unit sidewall capacitance at 0V

- Bulk capacitances
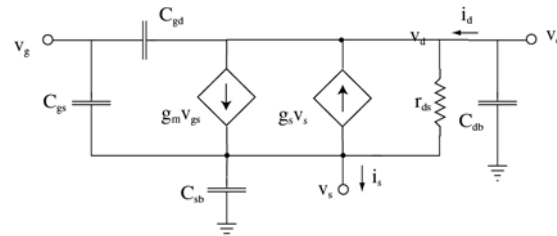
$$C_{sb} = C'_{sb} + C_{s-sw} \quad C_{db} = C'_{db} + C_{d-sw}$$



19

## MOS transistor model



- Triode region

- Gain give as slope


$$I_D = \mu_n C_{ox} \frac{W}{L} \left[ (V_{GS} - V_m) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

- Output conductance

$$\frac{1}{r_{ds}} = g_{ds} = \frac{\partial I_D}{\partial V_{DS}} = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_m - V_{DS})$$

- $V_{DS}$  is small and sometimes dropped
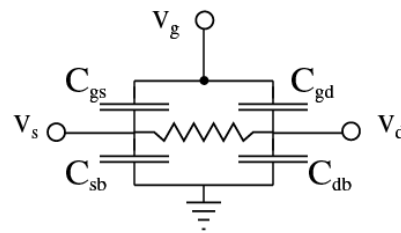
$$g_{ds} \approx \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_m)$$




20
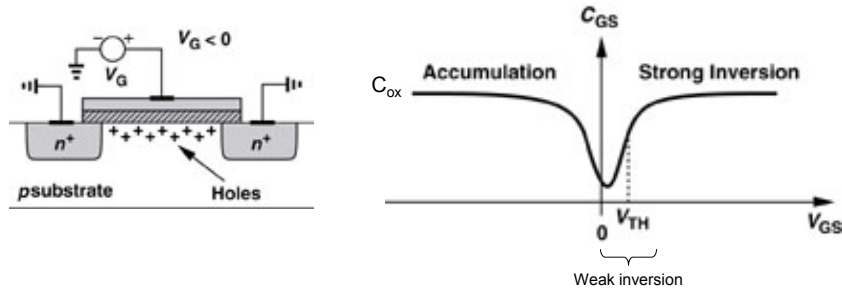
## MOS Capacitor



- Nonlinear gate capacitance
  - Dips in weak inversion
  - Often used in accumulation




21

## CS stage with load capacitor




- Finding transfer function

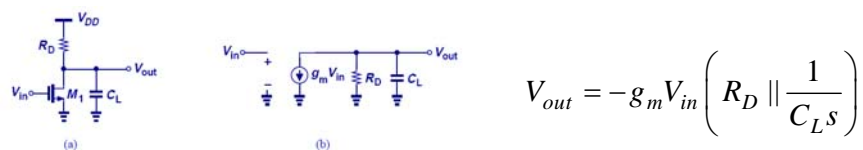

- Simply by adding capacitance impedance to output load

- magnitude

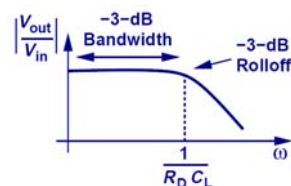


$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{g_m R_D}{\sqrt{R_D^2 C_L^2 \omega^2 + 1}}$$

22

## Bandwidth

- Example

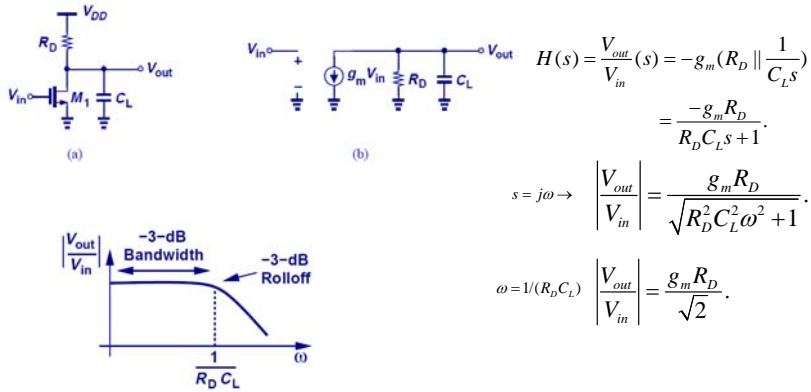

Time constant or -3dB bandwidth

23

## CS Frequency response

- Common source amp
  - Small signal, high frequency performance

$$C_2 = C_L + C_{db1} + C_{db2}$$

$$R_2 = r_{ds1} \parallel r_{ds2}$$

- Nodal analysis

- Sum currents

$$V_1: (v_1 - v_{in})G_{in} + v_1 s C_{gs1} + (v_1 - v_{out})s C_{gd1} = 0$$

$$v_1 (G_S + s C_{gs1} + s C_{gd1}) - v_{in} G_S - v_{out} s C_{gd1} = 0$$


$$V_{out}: v_{out} G_2 + (v_{out} - v_1)s C_{gd1} - v_{out} s C_2 + g_{m1} v_1 = 0$$

$$v_{out} (G_2 + s C_{gd1} + s C_2) - v_1 s C_{gd1} + g_{m1} v_1 = 0$$

$$\frac{v_{out}}{v_{in}} = - \frac{g_{m1} R_2 \left( 1 - s \frac{C_{gd1}}{g_{m1}} \right)}{1 + s a + s^2 b}$$

$$a = R_S (C_{gs1} + C_{gd1} (1 + g_{m1} R_2)) + R_2 (C_{gd1} + C_2)$$
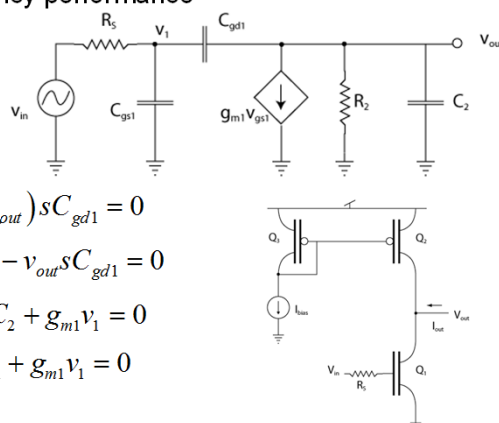
$$b = R_S R_2 (C_{gd1} C_{gs1} + C_{gs1} C_2 + C_{gd1} C_2)$$



24



## CS frequency response

- LF gain setting  $s=0$  is giving:  $A = -g_{m1}R_2$
- Assuming two poles  $\omega_{p1} \ll \omega_{p2}$  we may write denominator:

$$D(s) = \left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right) = 1 + \frac{s}{\omega_{p1}} + \frac{s^2}{\omega_{p1}\omega_{p2}}$$

- Giving  $\omega_{p1}$  :  $\omega_{p1} = \frac{1}{a} = \frac{1}{R_S(C_{gs1} + C_{gd1}(1 + g_{m1}R_2)) + R_2(C_{gd1} + C_2)}$
- And  $\omega_{p2}$  :  $\omega_{p2} = \frac{1}{\omega_{p1}b} \cong \frac{g_{m1}C_{gd1}}{C_{gs1}C_{gd1} + C_{gs1}C_2 + C_{gd1}C_2}$
- Zero at:  $\omega_z = -\frac{g_{m1}}{C_{gd1}}$ 
  - May cause issues at high frequencies
  - Actually maintain 1.order transition
- With large load capacitance:  $\omega_{p1} \cong \frac{1}{R_2C_2}$        $\omega_{p2} \cong \frac{C_{gd1}}{C_{gs1} + C_{gd1}} \frac{g_{m1}}{C_2}$

25



## Common source freq response

- At moderate frequencies  $-sC_{gd1}/g_{m1}$  and  $s^2b$  ignored

$$\frac{v_{out}}{v_{in}} = \frac{-g_{m1}R_2}{1 + s(R_S(C_{gs1} + C_{gd1}(1 + g_{m1}R_2)) + R_2(C_{gd1} + C_2))}$$

- Magnitude response at -3dB ( $\omega_0$ )

$$|A(j\omega)| = \frac{1}{\sqrt{2}} \Rightarrow 1 + (\omega/\omega_0)^2 = 2 \Rightarrow \omega_0 = \frac{1}{a}$$

$$|A(j\omega)| = \frac{|K|}{\sqrt{1 + (\omega/\omega_0)^2}}$$

$$\omega_0 = \frac{1}{R_S(C_{gs1} + C_{gd1}(1 + g_{m1}R_2)) + R_2(C_{gd1} + C_2)}$$

- First term in denominator dominates unless  $R_S \ll R_2$

$$\omega_0 = \frac{1}{R_S(C_{gs1} + C_{gd1}(1 + A))} \text{ for } A = g_{m1}R_2$$

**Miller capacitance  $\rightarrow C_{gd1}$  is multiplied by 1 plus the LF gain**

26

## CS frequency response




- Keypoints
  - Simple single transistor CS amplifier → complicated to analyze
  - Simplifications are important
  - CS stage
    - 2 poles
    - 1 zero
  - Gate-drain capacitance “amplified”
    - Miller-capacitance
    - Small, but significant

27

## What about this?



- CS stage with feedback

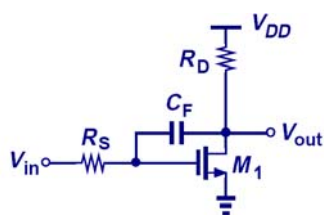


- Nodes connected by floating capacitor
- Simple node for each pole does not work
- Must transform before analysis
  - Caps to ground.....

28
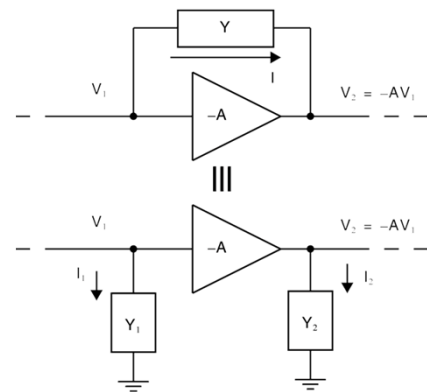
## Miller Theorem

- Simplifying conversion
  - Coupling  $\rightarrow$  decoupling
  - Let
 
$$Y_1(s) = Y(s)(1 + A)$$

$$Y_2(s) = Y(s)\left(1 + \frac{1}{A}\right)$$
  - Then same system behavior
  - Frequently used for capacitors
    - Coupling capacitors  $\rightarrow$  decoupling capacitors




*Approximation!*

29

## Example

- Ideal amp with feedback capacitor

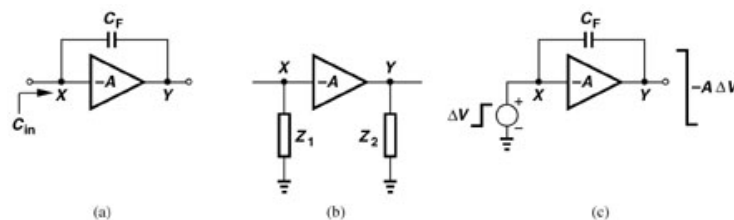

$$Z = 1/sC_F \Rightarrow Z_1 = (1/sC_F)/(1 + A)$$

$$\Rightarrow C_1 = C_F(1 + A)$$

$$Z = 1/sC_F \Rightarrow Z_2 = (1/sC_F)/(1 + 1/A)$$


$$\Rightarrow C_2 = C_F(1 + A^{-1}) \approx C_F$$

30

## Capacitive ratios



- Designed ground reference

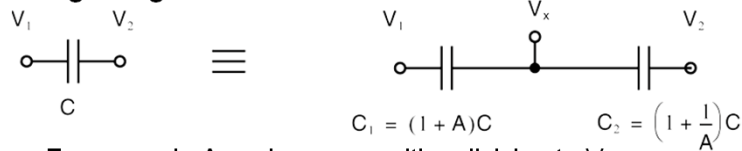

- For any gain A we have capacitive division to  $V_s$ :

$$\frac{C_1 C_2}{C_1 + C_2} = \frac{C(1+A)C(1+\frac{1}{A})}{C(1+A) + C(1+\frac{1}{A})} = \frac{(A+2+\frac{1}{A})C^2}{(A+2+\frac{1}{A})C} = C$$


$$V_s = V_1 + \frac{C_1 C_2}{C_1 + C_2} (V_2 - V_1)$$

- Inserting values give:

- $V_s = 0$
- With capacitive ratio matched to gain  $\rightarrow$  no signal on (virtual) middle node
- May as well ground.....

31

## Miller simplification in amps

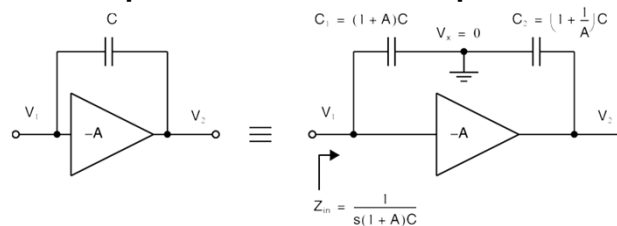

- Keypoints

- Miller effect  $\rightarrow$  dominant pole
- Quick and easy estimate with capacitor in inverting amplifiers
  - Assume LF gain:  $A = g_{m1} R_2$
  - Admittance:

$$Y_1(s) = sC_{gd1}(1+A) = sC_{gd1}(1+g_{m1}R_2) \quad Y_2(s) = sC_{gd1} \left( 1 + \frac{1}{g_{m1}R_2} \right)$$

$$\omega_0 = \frac{1}{R_1(C_{gs1} + C_{gd1}(1+A))} \quad \text{for } A = g_{m1}R_2$$

Miller effect

32



## Zero-value time-constant analysis




- Powerful high frequency estimation
  1. Set all independent source to zero.
  2. For each capacitor,  $C_k$ , determine time-constant with all other caps open circuit. Replace  $C_k$  with a voltage source and determine resistance.
  3. Dominant pole (-3dB) found by summing poles:

$$\omega_{-3dB} = \frac{1}{\sum \tau_k} = \frac{1}{\sum R_k C_k}$$

33

## CS stage as example

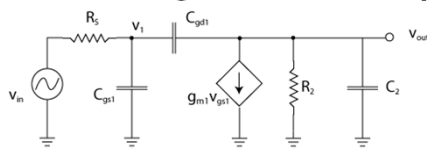

- Three capacitors
  - Timeconstant for  $C_{gs1}$ :  $\tau_1 = R_S C_{gs1}$
  - Timeconstant for  $C_2$ :  $\tau_2 = R_2 C_2$
  - Timeconstant for  $C_{gd1}$ :

- KCL at  $v_y$ :
 
$$\frac{(v_3 - v_y)}{R_2} - g_{m1} v_y - i_3 = 0 \text{ and } v_y = i_3 R_S \Rightarrow$$


$$R_3 = \frac{v_3}{i_3} = R_S (1 + g_{m1} R_2) + R_2$$

$$\tau_3 = [R_S (1 + g_{m1} R_2) + R_2] C_{gd1}$$

$$\omega_{-3dB} = \frac{1}{\sum \tau_k} = \frac{1}{R_S (C_{gs1} + C_{gd1} (1 + g_{m1} R_2)) + R_2 (C_{gd1} + C_2)}$$


Same as  
Already found

34

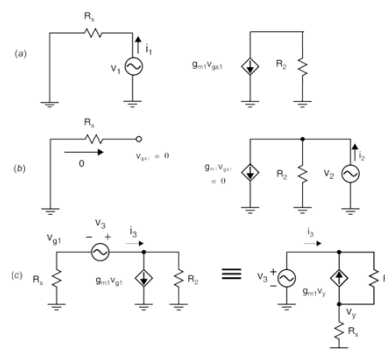
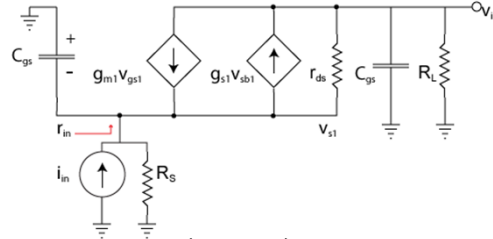
## Common-gate AMP

- Superior to CS amp
  - No Miller cap
  - Low impedance input
    - If matched
  - Modeling with current in
    - Norton



- Find time-constants:

- Timeconstant for  $C_{gs1}$ :  $\tau_1 = (r_{in} \parallel R_S) C_{gs} \approx \left( \frac{1}{g_{m1}} \parallel R_S \right) C_{gs} \approx \frac{C_{gs}}{g_{m1}}$
- Timeconstant for  $C_2$ :

$$\tau_2 = (r_{d1} \parallel R_L) C_2 = (r_{ds} (1 + g_m R_S) \parallel R_L) C_2$$

- $R_L$  often dominating giving


$$\tau_2 \approx R_L C_2$$

$$\omega_{-3dB} = \frac{1}{\tau_1 + \tau_2} = \frac{1}{\frac{C_{gs}}{g_{m1}} + R_L C_2}$$

35
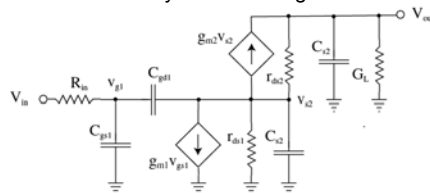
## Cascode gain stage

- Large gain, single stage solution
  - PMOS in folded cascode  $\rightarrow$  lower mobility and lower frequency
  - Current source on output not highres
    - Handled well by cascode stage



- Exact analysis complicated, use simulations
  - Approximation by zero-value time-constants
    - 4 capacitors  $\rightarrow$  4 time-constants
    - Parallel caps merged

36

- Time-constant at output  $C_{out}$ :

$$\tau_{out} = (r_{d2} \parallel R_L) C_{out} = (g_m r_{ds1} r_{ds2} \parallel R_L) C_{out}$$

- Time-constant at output  $C_{gs1}$ :

$$\tau_{gs1} = R_S C_{gs1}$$

- Time-constant at output  $C_2$ :

- Cascode input resistance determined earlier ( $g_{in2}$ )

$$\tau_{s2} = r_{in2} C_2$$

- Time-constant at output  $C_{gd1}$ :


- Like Miller cap in CS stage  $\tau_{gd1} = [R_S (1 + g_{m1} r_{in2}) + r_{in2}] C_{gd1}$

- If  $g_{m1} R_S \gg 1$

$$\tau_{gd1} \approx R_S (1 + g_{m1} r_{in2}) C_{gd1}$$

- Total time constant:
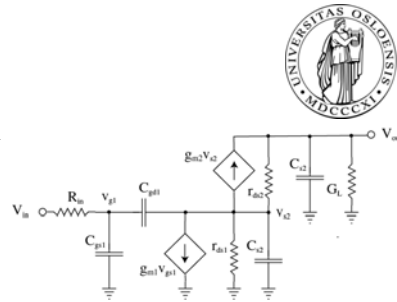
$$\tau_{total} = (g_m r_{ds1} r_{ds2} \parallel R_L) C_{out} + R_S C_{gs1} + r_{in2} C_2 + R_S (1 + g_{m1} r_{in2}) C_{gd1}$$



37

## Cascode approximations

- Assuming high quality current mirror for bias current

- In the order of:  $g_{m-p} r_{ds-p}^2$

- Assuming approximately same transconductance

$$A \cong -\frac{1}{2} g_m^2 r_{ds}^2$$

- Output resistance


$$R_{out} = r_{d2} \parallel R_L \approx \frac{1}{2} g_m r_{ds}^2$$

- Giving

- With large load cap, the output pole is dominating

$$\tau_{out} = (r_{d2} \parallel R_L) C_{out} = \frac{1}{2} g_m r_{ds}^2 C_{out}$$
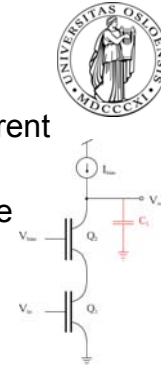
$$\omega_{-3dB} = \frac{1}{\tau_{out}} \approx \frac{2g_{ds}^2}{g_m C_{out}}$$




38
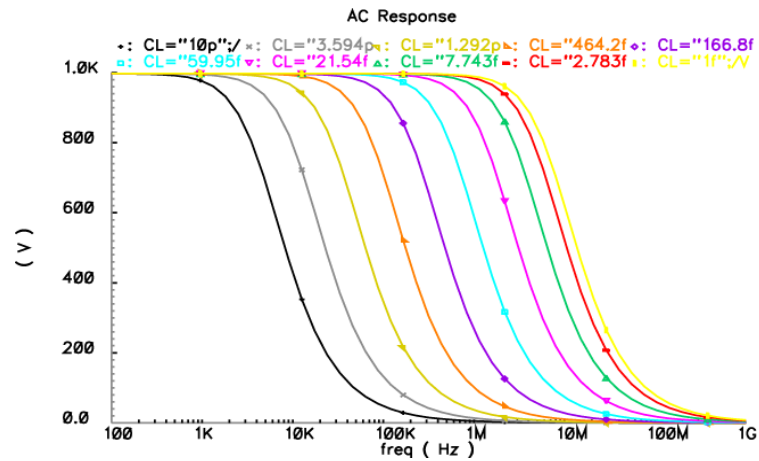
## Cascode gain stage



- Cadence simulation
  - Load capacitor 1fF – 10pF




39

## Source follower amp



- Intuitive understanding

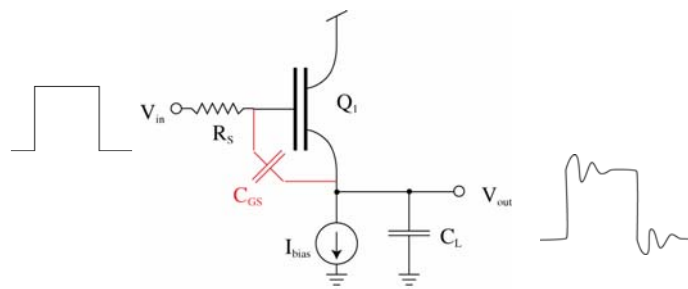

- The gate-source capacitance is feeding back output changes
- High input resistance,  $R_S$ , increase output ringing

40

# Source follower freq response



- Analysis for stability


- Reduced overshoot

$$R_{S1} = r_{ds1} \parallel r_{ds2} \parallel \frac{1}{g_{s1}}$$


$$C'_{in} = C_{in} + C_{gd1}$$

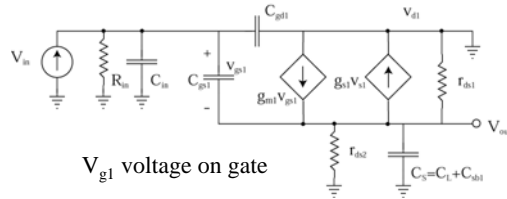- 1. Gain from input

$$\begin{aligned} V_{out}: \quad & v_{out} G_{S1} + (v_{out} - v_{g1}) s C_{gs1} + v_{out} s C_S - g_{m1} (v_{g1} - v_{out}) = 0 \\ & v_{out} (G_{S1} + s C_{gs1} + s C_S) - v_{g1} s C_{gs1} - g_{m1} (v_{g1} - v_{out}) = 0 \Rightarrow \\ & \frac{v_{out}}{v_{g1}} = \frac{s C_{gs1} + g_{m1}}{s (C_{gs1} + C_S) + g_{m1} + G_{S1}} \end{aligned}$$



$V_{g1}$  voltage on gate

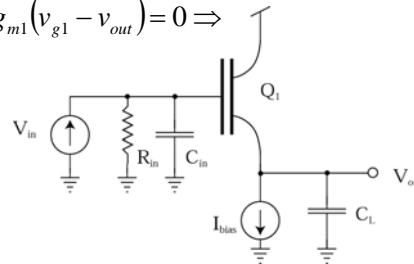

41


- 2. Admittance at input

- No  $C_{gd1}$

$$i_{g1} = (v_{g1} - v_{out}) s C_{gs1}$$

- Combining with previous
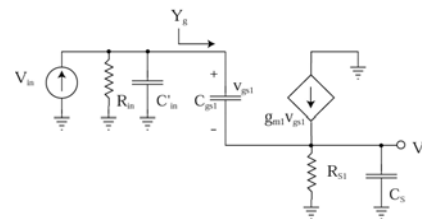
$$Y_{g1} = \frac{i_{g1}}{v_{g1}} = \frac{s C_{gs1} (s C_S + g_{m1})}{s (C_{gs1} + C_S) + g_{m1} + G_{S1}}$$



- 3. Transresistance

$$i_{in} = v_{g1} (s C'_{in} + G_{in} + Y_g)$$

$$\frac{v_{g1}}{i_{in}} = \frac{s (C_{gs1} + C_S) + g_{m1} + G_{S1}}{a + sb + s^2 c}$$

$$a = G_{in} (g_{m1} + G_{S1})$$

$$b = G_{in} (C_{gs1} + C_S) + C'_{in} (g_{m1} + G_{S1}) + C_{gs1} G_{S1}$$

$$c = C_{gs1} G_{S1} + C'_{in} (C_{gs1} + C_S)$$

- 4. Transfer function

- 2. order

$$A(s) = \frac{v_{out}}{i_{in}} = \frac{s C_{gs1} + g_{m1}}{a + sb + s^2 c}$$

42





## Source-follower analysis

- Equating coefficients

$$\omega_0 = \sqrt{\frac{G_{in}(g_{m1} + G_{S1})}{C_{gs1}G_{S1} + C_{in}'(C_{gs1} + C_S)}}$$

$$Q = \frac{\sqrt{G_{in}(g_{m1} + G_{S1})}[C_{gs1}G_{S1} + C_{in}'(C_{gs1} + C_S)]}{G_{in}(C_{gs1} + C_S) + C_{in}'(g_{m1} + G_{S1}) + C_{gs1}G_{S1}}$$

–  $Q < 0.5$ :  $C_{in}'$  and/or  $C_S$  large and stable


– Large  $Q$ :  $G_{S1}$ ,  $C_{in}'$  and  $G_{in} = \frac{1}{R_{in}}$  small

*Source follower may exhibit overshoot and ringing.*


43

## Diff pair frequency analysis

- Using MOS T-model with caps

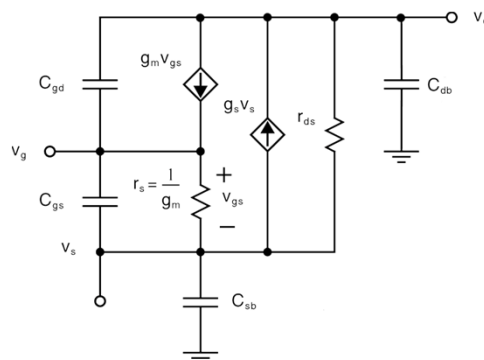

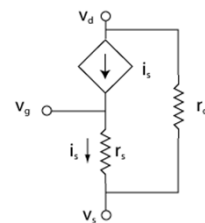– T-model used for simpler diff pair analysis



44

## Diff-par HF model

- Symmetric circuit

- Transistors and resistors are the same as indicated
- Input voltages balanced


$$V_{in}^+ = -V_{in}^-$$

- Common  $v_a$  voltage unchanged

- Virtual ground
- May ignore  $C_{sb}$  of both transistors


- May analyze as half-circuit

- → CS stage analysis

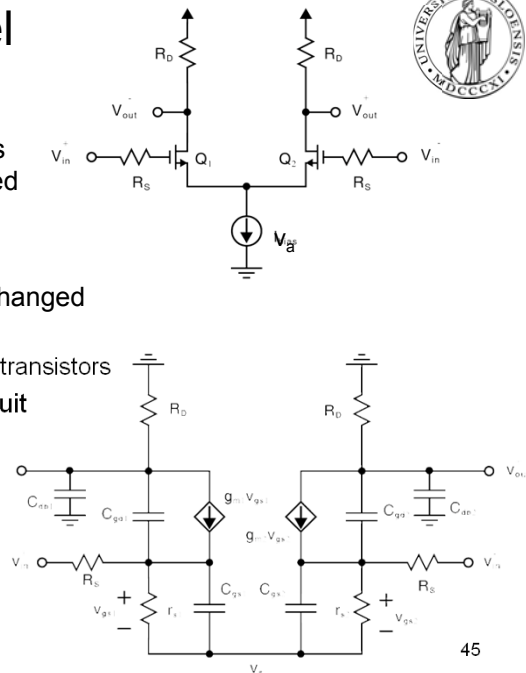

45

## Single-ended diff amp

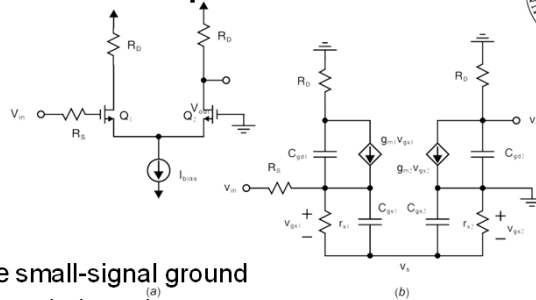

- $v_s$  considered to be small-signal ground

- Source-capacitors may be ignored
- The diff-pair → 2 x common source stages
- Dominant pole:

$$\omega_{-3dB} \approx \frac{1}{R_S (C_{gs1} + C_{gd1} (1 + g_{m1} R_2))}$$

- Giving bandwidth approximation assuming  $C_{db}$  to be small

46

## Differential amp with active load





- Active current-mirror load
  - Used as input stage in opamps
  - From chapter 3.8:

$$A_v = \frac{v_{out}}{v_{in}} = g_m r_{out}$$

- With capacitive load
  - Substitute  $r_{out}$  with  $z_{out}$  with:
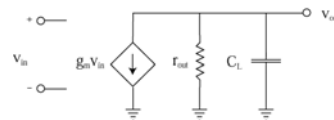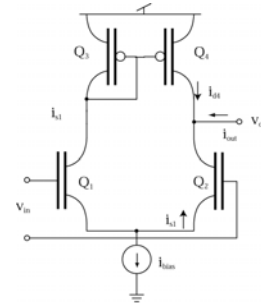
$$\omega_{-3dB} = \left( r_{out} \parallel \frac{1}{sC_L} \right) = \frac{1}{(r_{ds2} \parallel r_{ds4})C_L}$$



47

## Chapter 4 Keypoints



- Important fundamentals for circuit analysis!
- Limited analysis with real coefficients
- Sinusoidal in → Sinusoidal out
  - Phase and magnitude may still change
- Transfer functions with real poles and zero order numerator have monotonically decreasing magnitude (20dB/decade) and phase up to -90 degrees
- Big caps dominates small caps
- CS-stage → 2 poles and 1 zero
- Caps over inverting amps blow up in effective value (Miller caps)
- Zero-value time-constants method estimate circuit bandwidth
- Common-gate used in cascode stage increase gain and reduce Miller caps
- Source follower may be unstable (overshoot)
- Diff-pairs may be analyzed as half circuits → common source stage

48