 


# Biasing, references, regulators




- Providing suitable working conditions for analog circuit elements
  - Bias circuit
    - Setting DC voltages or currents
  - Reference
    - Generate constant and absolute voltage
      - Independent of working conditions
  - Regulator
    - Improve DC voltage or currents keeping them stable



1
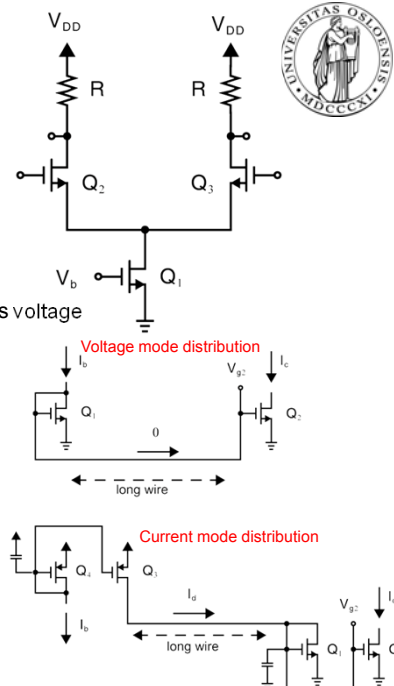
## Bias circuits


- What bias voltage?
  - Assuming 10-20% device variations
    - Constant drain current in match diff-pair?
    - Constant voltage drop over R?
    - Constant gain?
- Good bias circuit
  - Monitor important parameters and adapt bias voltage
  - May be large
  - Must be reused by several sub-circuits
  - Using current mirrors
    - Voltage mode
      - Major variations due to mismatch
    - Current mode distribution
      - Somewhat better
      - Local mirror
      - Decoupling caps added locally


 
# Reference circuits




- Provide some stable voltage for biasing
  - Simple combination of MOS + resistor
  - May size nMOS for suitable output voltage
    - Nonlinear element



TSL inf3410

3

# Regulator

 

- Reduce supply voltage
  - Stabilize supply voltage for improved performance
- Filter noisy supply
  - Ground ref may still convey noise

TSL inf3410

4

## Constant transconductance



- Bias circuit maintaining constant transconductance

- Assuming  $(W/L)_{10} = (W/L)_{11}$
- Same current in both branches
- We have  $V_{GS13} = V_{GS15} + I_{D15}R_B$
- Giving:  $V_{eff13} = V_{eff15} + I_{D15}R_B$
- Since  $I_{D13} = I_{D15}$   $g_m = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D}$

Giving

$$g_{mn} = \frac{2 \left[ 1 - \sqrt{\frac{(W/L)_{13}}{(W/L)_{15}}} \right]}{R_B} \approx g_{m13}$$

For  $(W/L)_{15} = 4(W/L)_{13} \Rightarrow g_{m13} = \frac{1}{R_B}$


- $G_{m13}$  and all other nMOS transconductances are stabilized

- Generated from same current

TSL inf3410

$$g_{mn} = \sqrt{\frac{(W/L)I_D}{(W/L)I_{15}}} \approx g_{m13}$$

5

 


## Constant transconductance



- PMOS devices

$$g_{mp} = \sqrt{\frac{\mu_p (W/L)I_D}{\mu_n (W/L)I_{15}}} \approx g_{m13}$$

 - Unfortunately mobility variations are significant
- Additional compensation for
  - Temp, body ...
- Second stable state
  - All zero  $\rightarrow$  bootstrap circuit
- May increase power at high temperatures



TSL inf3410

6

# References



- Reference voltage or current
  - Used for controlling opamp characteristics
  - *Never submit a bias voltage directly from pad*
  - *Always use current input for setting references!*
    - Voltage
    - Current
- High quality reference (V or I)
  - Independent of supply voltage
  - Independent of process variations
  - Independent or well-defined temperature behavior
    - Balancing negative temperature dependence of PN junction (forward biased) with a positive temperature dependence of PTAT (proportional to absolute temperature) circuits

TSL inf3410

7


## Reference circuit



- Generic reference
- Resistive current generator
  - Known load → good approximation
  - Sensitive to Vdd

$$\Delta I_{out} = \frac{\Delta V_{DD}}{R_1 + 1/g_{m1}} \cdot \frac{(W/L)_2}{(W/L)_1}$$

*Need some sort of self-biasing!*

 

TSL inf3410


8

# Supply independent current



- Bootstrapping reference
  - Using scaling
    - $I_{out} = K \cdot I_{REF}$ 
      - Ignoring channel shortening
  - Diodes driven by current sources
    - Relatively independent of supply
    - Giving any current level with K

*Tend to use power*

 

TSL inf3410

9


# Reference with current control



- Resistor reduce  $Q_2$  current
- P-mirror ensure  $I_{out} = I_{REF}$
- Output current
  - Strong inversion behavior

$$I_{out} = \frac{2}{\mu_n C_{ox} (W/L)_n} \cdot \frac{1}{R_s^2} \left( 1 - \frac{1}{\sqrt{K}} \right)^2$$

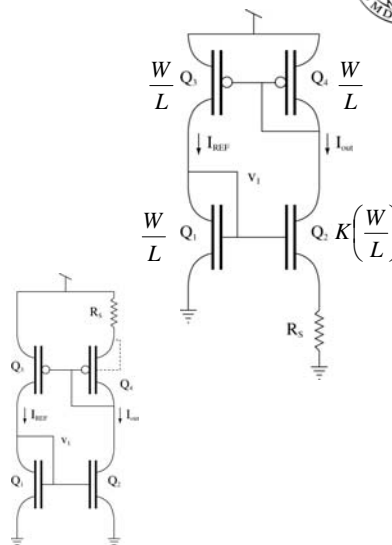- Independent of supply
  - Body effect error
- Channel length modulation
  - Problematic in all these circuits



TSL inf3410

10

# Start-up problem


- Two stable operating points
  - Current defined by  $R_s$  and  $K$
  - No current at all!
- Diode only working at start-up

$$V_{th1} + V_{th5} + |V_{th4}| < V_{DD}$$

- Get some current

$$V_{gs1} + V_{th5} + |V_{th4}| > V_{DD}$$

- Off during normal operation

 

TSL inf3410

11

# Temperature compensation

- Combining positive and negative temperature dependence

$$V_{REF} = V_{neg-Tc} + KV_{pos-Tc}$$

- Should give no temperature dependence (one must be scaled with  $K$ )

- Negative temperature source

- PN junction diode

$$I_C = I_S \exp(V_{BE}/V_T) \text{ for } V_T = kT/q, I_S \propto \mu k T n_i^2$$

$\mu$  - mobility

$n_i$  - minority carrier concentration

- Forward biased diode temperature dependence

$$\frac{\partial V_{BE}}{\partial T} = \frac{V_{BE} - (4+m)V_T - E_g/q}{T}$$

$$m \approx -3/2$$

$E_g \approx 1.12 \text{ eV}$  - bandgap energy of silicon

- Typical

$$V_{BE} \approx 750 \text{ mV}, T = 300^\circ \text{ K} \rightarrow \frac{\partial V_{BE}}{\partial T} \approx -1.5 \text{ mV}/^\circ \text{ K}$$

TSL inf3410



12




- Positive temperature circuit
  - Two bipolars with different currents
    - Base-emitter difference proportional to temperature
      - Discovery from 1964

$$\Delta V_{BE} = V_T \ln n \Rightarrow \frac{\partial V_{BE}}{\partial T} = \frac{k}{q} \ln n$$

- Room temperature
 
$$\frac{\partial V_T}{\partial T} \approx +0.087 \text{ mV}/^\circ\text{K}$$



- Bandgap reference

$$V_{REF} = V_{BE} + K(V_T \ln n)$$


- Let  $K \ln n \cdot 0.087 \text{ mV}/^\circ\text{K} = 1.5 \text{ mV}/^\circ\text{K} \Rightarrow K = 17.2$

- Give  $V_{REF} = V_{BE} + 17.2 V_T \approx 1.24 \text{ V}$

TSL inf3410

13

## Parasitic PNP bipolar in CMOS

 

- Bandgap CMOS circuit

- Left branch

$$V_{ref} = V_{EB1} + V_{R1}$$

- Assume high gain amp giving same voltage

$$V_{R2} = V_{EB1} - V_{EB2} = \Delta V_{EB}$$

- Current through  $R_2$  equal current through  $R_3$


$$V_{R3} = \frac{R_3}{R_2} V_{R2} = \frac{R_3}{R_2} \Delta V_{EB}$$

- Voltage over  $R_1$  equal voltage over  $R_3$

$$V_{ref} = V_{EB1} + \frac{R_3}{R_2} \Delta V_{EB}$$

- giving

$$K = \frac{R_3}{R_2}$$

 


TSL inf3410

14

# PTAT current generator



- Read off the compensated current

 

TSL inf3410

15

# Voltage regulators



- Quiet and stable on-chip voltage

- Input reference

- Amp gain

$$V_{ref} \approx V_{reg}$$

- Specifications


- Power-supply rejection ratio

$$PSSR(\omega) = 10 \log_{10} \left( \frac{V_{DD}}{V_{reg}} \right)$$

- Output impedance

- Dropout voltage

 - Minimum voltage between supply and regulated voltage



TSL inf3410

16



# Low Drop-out regulator



- Dropout voltage
  - Maximum regulated voltage
- pMOS for minimal voltage drop
  - Notice reversed amp polarity
- Regulating loop


$$L(s) = \frac{G_{ma} R_{od} g_{m1} R_L'}{\left(1 + \frac{s}{\omega_{pa}}\right) \left(1 + \frac{s}{\omega_{pL}}\right)}$$

- Amp pole
  - Amp pole dominant → worse rejection

- Output pole

$$\omega_{pL} = \frac{1}{R_L' C_L}$$

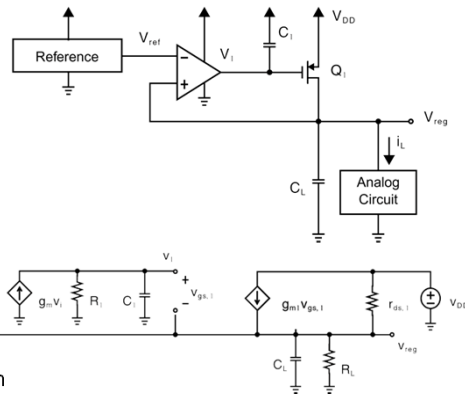- Output pole dominant → more power in feedback amp



TSL inf3410

17