 


# Analog design trade-offs



- Analog design octagon



- Balancing performance with real devices

TSL inf3410

1

## Current mirrors



- Large signal behavior
  - Current controlled current source
    - Equal transistor sizes with same gate voltage
      - Give same current



$$I_{out} = I_{in}$$

» Sink or source

- Assuming active region
- Ignoring channel shortening
- Fixed gain current amplifier

- Different transistor sizes
  
$$I_{out} = \frac{W_2 L_1}{W_1 L_2} I_{in}$$



TSL inf3410

2

## Diode connected MOS transistor



- Shorting drain-gate

- V-I relation


- Strong inversion
    - Active region by connection
    - Ignoring channel shortening

$$I_D = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{GS} - V_m)^2 \Rightarrow$$

$$(V_{GS} - V_m)^2 = \frac{2}{\mu_n C_{ox} (W/L)} I_D \Rightarrow$$

$$V_{GS} = V_m + \sqrt{\frac{2}{\mu_n C_{ox} (W/L)}} \cdot \sqrt{I_D}$$

 *Diode voltage is changing by the square of the drain current*



TSL inf3410

3

## Diode connected MOS transistor



- V-I relation

- Weak inversion
  - Active region by connection
  - Ignoring channel shortening

$$I_D = I_S e^{\frac{V_G - V_{T0} - nV_S}{nU_T}}$$


$$V_S = 0$$

$$I_D = I_S e^{\frac{V_G - V_{T0}}{nU_T}} \Rightarrow$$

$$V_G = V_{T0} + nU_T \cdot (\ln(I_D) - \ln(I_S))$$

*Diode voltage is changing with the natural logarithm of the current*

 *Diode connected transistors are also called compressors  
( $I \rightarrow \ln(V)$  or  $\sqrt{\ln(V)}$ )*



TSL inf3410


4
 
# Diode connected transistor



- Small signal model
  - Finding Thévenin equivalent
  - Applying test voltage  $v_y$  measuring  $i_y$

$$i_y = \frac{v_y}{r_{ds}} + g_m v_y \Rightarrow \frac{v_y}{i_y} = r_{ds} \parallel \frac{1}{g_m} \approx \frac{1}{g_m}$$




TSL inf3410

5


# Mirror equivalent



- Small signal model

 

 - No current through gate  $\rightarrow V_{gs1}=0$  implies  $V_{gs2}g_{m2}=0$



*The small signal output impedance is equal to the output impedance of the output transistor ( $r_{ds2}$ )*

- Current mirror output current is set by input, but some small-signal errors occur due to finite output resistance


TSL inf3410

6
 
# Current mirror example



- Current gain of 2
- Output error < 5μA at
  - 100μA current load
  - Max 1V output voltage change



$$\mu_n C_{ox} = 92 \frac{\mu A}{V^2}, V_m = 0.8V, r_{ds} = 8000 L(\mu m) / I_D(mA)$$

$$r_{out} = \frac{1V}{5\mu A} = 200k\Omega$$

Find the minimum output transistor length

$$r_{out} = r_{ds2} = \frac{8000L}{I_D} \Rightarrow L > \frac{r_{out} I_D}{8000} = \frac{200k \cdot 0.1}{8000} = 2.5\mu m$$

- Effective input voltage  $V_{eff} > 0.5V$

Find the maximum output transistor width

$$I_D = \frac{\mu_n C_{ox}}{2} \frac{W}{L} V_{eff}^2 \Rightarrow W < \frac{2LI_D}{\mu_n C_{ox} V_{eff}^2} = \frac{2 \cdot 2.5\mu m \cdot 50\mu A}{92 \frac{\mu A}{V^2} \cdot 0.25V^2} = 10.9\mu m$$

$$W_2/L_2 = 10\mu/3\mu \text{ and } W_1/L_1 = 5\mu/3\mu$$

Feasible transistor sizes



TSL inf3410

7
  
# Diode using source



- Diode-connected drain large signal behavior
  - Front-gate and back-gate



Lower impedance than standard diode! Why?

Other drawbacks?

$$V_g = -V_X, V_{sb} = V_X$$


$$i_X = \frac{V_X}{r_{ds}} + g_m V_X + g_s V_X \Rightarrow \frac{V_X}{i_X} = r_{ds} \parallel \frac{1}{g_m + g_s} \approx \frac{1}{g_m + g_s}$$

TSL inf3410

8
 
# Common-source amplifier

- Inverting amplifier - resistive load
  - Small signal gain



$$A_V = \frac{v_{out}}{v_{in}} = -g_{m1}(r_{ds1} || R_{load})$$


- High-impedance linear resistive load for high gain
  - high supply voltage

$$R_{load} = 200k\Omega, I_D = 100\mu A \Rightarrow$$

$$V_{supply} = 200k\Omega \cdot 100\mu A = 20V$$

Typical supply <3V!

TSL inf3410

 

9

# Common source with diode load

$$R_{load} = \frac{1}{g_{m2}}$$


$$A_V = \frac{v_{out}}{v_{in}} = -g_{m1} \left( r_{ds1} || \frac{1}{g_{m2}} \right) \approx -\frac{g_{m1}}{g_{m2}}$$

$$g_m = \sqrt{2\mu C_{ox} \frac{W}{L} I_D} \text{ with } I_{D1} = I_{D2} \Rightarrow$$

$$A_V = -\frac{g_{m1}}{g_{m2}} = -\frac{\sqrt{2\mu_n C_{ox} \frac{W_1}{L_1} I_{D1}}}{\sqrt{2\mu_p C_{ox} \frac{W_2}{L_2} I_{D2}}} = -\sqrt{\frac{\mu_n W_1 / L_1}{\mu_p W_2 / L_2}}$$

- The voltage gain is independent of bias current and voltages
  - Provided active region
- The gain set by design
- Headroom?

TSL inf3410

 

10

## CS stage with source diode




$$R_{load} = \frac{1}{g_{m2} + g_s}$$

$$A_v = \frac{v_{out}}{v_{in}} = -g_{m1} \left( r_{ds1} \parallel \frac{1}{g_{m2} + g_s} \right) \approx -\frac{g_{m1}}{g_{m2} + g_s} = -\frac{g_{m1}}{g_{m2}} \frac{1}{1 + \eta}$$

$$\text{for } \eta = \frac{g_s}{g_{m2}}$$

$$g_m = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D} \text{ with } I_{D1} = I_{D2} \Rightarrow$$
 
$$A_v = -\frac{g_{m1}}{g_{m2}} \frac{1}{1 + \eta} = -\frac{\sqrt{2\mu_n C_{ox} \frac{W_1}{L_1} I_{D1}}}{\sqrt{2\mu_n C_{ox} \frac{W_2}{L_2} I_{D2}}} \frac{1}{1 + \eta} = -\sqrt{\frac{W_1/L_1}{W_2/L_2}} \frac{1}{1 + \eta}$$



• Lower Q<sub>2</sub> impedance


TSL inf3410

11
 
## Common-source amplifier




- Popular gain stage
  - Inverting amplifier with current load
    - Triode or active region
  - Small signal equivalent



$$A_v = \frac{v_{out}}{v_{in}} = -g_{m1} \cdot R_2 = -g_{m1} (r_{ds1} \parallel r_{ds2})$$

 - Typical gain of -10 to -100
- High gain at low supply voltage
  - Exploring nonlinear transistor characteristics



TSL inf3410

12

## Common-source stage keypoints



- Simple and popular gain stage
- High input impedance
- Passive load for high frequency (RF)
- Active load provide high resistive equivalent due to non-linearity giving higher gain

TSL inf3410

13

## Source follower



- Large signal behavior
  - Output voltage “follows” input voltage

- Diode drop offset

- Unit gain amplifier ( $A \approx 1$ )
  - Voltage buffer
  - Current gain


$$V_{out} = V_{in} - V_{GS} \Rightarrow$$

$$V_{out} = V_{in} - \left( V_m + \sqrt{\frac{2}{\mu_n C_{ox} (W/L)}} \cdot \sqrt{I_D} \right)$$

- Ignoring channel shortening and body effect

- Voltage drop increase with square root of current

- Used as buffer/driver for larger loads

 



TSL inf3410

14

# Source follower



- Small signal model

  

$$\frac{1}{G_{S1}} = R_{S1} = r_{ds1} \parallel r_{ds2} \parallel \frac{1}{g_{s1}}$$

$$v_{gs1} = v_{in} - v_{out}$$

$$v_{out}G_{S1} - g_{m1}(v_{in} - v_{out}) = 0 \Rightarrow$$

$$A_v = \frac{v_{out}}{v_{in}} = \frac{g_{m1}}{g_{m1} + G_{S1}} = \frac{g_{m1}}{g_{m1} + g_{s1} + g_{ds1} + g_{ds2}}$$

*$g_{s1}$  is 1/10 of  $g_{m1}$  and  $g_{ds1(2)}$  is 1/10 of  $g_{s1}$   
•Body effect major error term*

TSL inf3410

15

## Source follower keypoints



- Voltage gain close to one
- Affected by body-effect
- Can provide large current gain

TSL inf3410

16



# Common gate application



- Impedance matching
  - 50Ω transmission line

$$A_V = -g_{m1} \cdot R_D$$


- With common gate

$$A_V = -g_{m1} \cdot R_D$$

$$\frac{1}{g_m + g_{mb}} = 50\Omega$$

*Achieved by proper sizing*

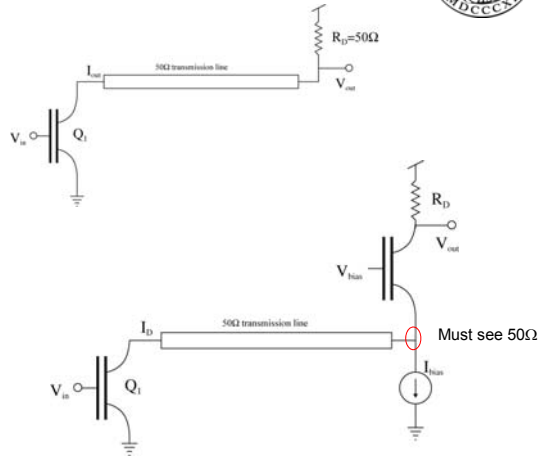- The common gate allow for much higher RD giving higher overall gain




TSL inf3410

17
 
# Common-gate amplifier



- Low impedance input
  - Typical 50Ω matching
  - Voltage gain as common-source



•Voltage gain


$$V_{gs1} = -V_{s1}$$

*For grounded gate circuits  
Always combine currents sources*

$$(g_{m1} + g_{s1})V_{s1}$$

$$v_{out}(G_L + g_{ds1}) - v_{s1}g_{ds1} - (g_{m1} + g_{s1})v_{s1} = 0 \Rightarrow$$


 
$$\frac{v_{out}}{v_{s1}} = \frac{g_{m1} + g_{s1} + g_{ds1}}{G_L + g_{ds1}} = (g_{m1} + g_{s1} + g_{ds1})(R_L \parallel r_{ds1}) \approx g_{m1}(R_L \parallel r_{ds1})$$



TSL inf3410

18

# Common gate amp analysis

  

- Source current  $i_s$

$$i_s = (g_{m1} + g_{s1})v_{s1} + (v_{s1} - v_{out})g_{ds1}$$

$$= (g_{m1} + g_{s1} + g_{ds1})v_{s1} - g_{ds1}v_{out}$$

- Input admittance

$$\frac{1}{r_{in}} = \frac{i_s}{v_{s1}} = \frac{(g_{m1} + g_{s1} + g_{ds1})}{1 + \frac{g_{ds1}}{G_L}} \approx \frac{g_{m1}}{1 + \frac{g_{ds1}}{G_L}} \Rightarrow r_{in} = \frac{1}{g_{m1}} \left( 1 + \frac{R_L}{r_{ds1}} \right)$$

$$r_{ds1} \approx R_L \Rightarrow r_{in} \approx \frac{1}{g_{m1}} \quad R_L \gg r_{ds1} \Rightarrow r_{in} > \frac{1}{g_{m1}}$$

Twice the expected input impedance

TSL inf3410

The drain voltages is too "weak"

19

## Common-gate keypoints



- Voltage gain similar to common-source stage
- Provide low input impedance
  - May increase for low frequency signals
- Suitable for matched transmission lines
- Used extensively in RF circuits


TSL inf3410

20
 
# Source-degeneration



- Increase output impedance
  - Reducing error due to output voltage variation
- Making soft reference
- Resistor
  - Linear voltage dependence
- MOS transistor
  - Linear drain resistance
  - Square (exponential) gate-source dependence
- Increased output current
  - Restricted by reduced gate-source voltage




TSL inf3410

21

# Source degenerated mirror



- Small signal model

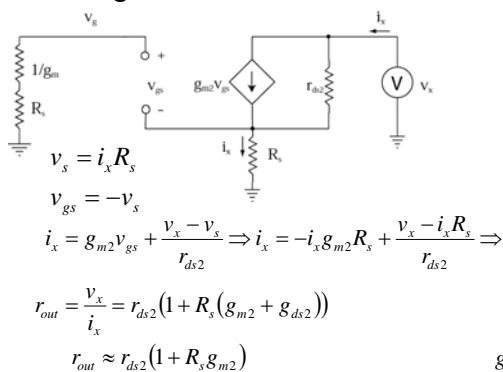

*With body effect*


$$g_{m2} \rightarrow (g_{m2} + g_{s2})$$

$$r_{out} \approx r_{ds2} (1 + R_s (g_{m2} + g_{s2}))$$

*Output impedance increased by  $(1 + R_s g_{m2})$*

- Increased output impedance  $\rightarrow$  more accurate current copy

*What about headroom?*

 

TSL inf3410

22

# High impedance mirrors

- Resistors hard to get in CMOS
  - Have to use MOS-devices for degeneration
- Cascode mirror
  - Softening sources with additional current-mirror

Using formula from source degeneration

$$r_{out} = r_{ds4} (1 + R_s (g_{m4} + g_{s4} + g_{ds4}))$$

$$\text{setting } R_s = r_{ds2} \Rightarrow$$

$$r_{out} = r_{ds4} (1 + r_{ds2} (g_{m4} + g_{s4} + g_{ds4}))$$

$$r_{out} \approx r_{ds4} (r_{ds2} g_{m4})$$


Output impedance increased by  $r_{ds2} g_{m4}$

TSL inf3410

Disadvantage:

$$V_{out} > 2V_{eff} + V_{tn}$$

23

 

# Cascode gain stage

- Single stage inverting amplifier
  - Improving performance
    - Combine common source feeding into common gate stage
  - Large gain
    - Low output impedance
    - High gain of common source transistor
    - High quality current sources
  - No speed loss with increased gain
  - Two variants
    - Telescopic configuration
    - Folded cascode configuration

TSL inf3410


24



 
# Cascode gain stage



- Improve output impedance
  - “locking” Q1 drain voltage absorbing output voltage variations with Q2
- Telescopic cascode gain stage
- Folded cascode gain stage



DC level shift or headroom reduction

 

Reduced gain due to PMOS transistor

TSL inf3410

25

# Cascode gain stage analysis



- Impedance looking into Q<sub>2</sub>

$$r_{d2} = g_{m2} r_{ds1} r_{ds2}$$

- Small signal total output impedance is  $r_{d2} \parallel R_L$ 
  - Assuming high quality current source

$$R_{out} = r_{d2} \parallel R_L$$

- Gain

- Common gate input admittance

$$g_{m2} = \frac{1}{r_{in2}} = \frac{(g_{m2} + g_{s2} + g_{ds2})}{1 + \frac{R_L}{r_{ds2}}} \cong \frac{g_{m2}}{1 + \frac{R_L}{r_{ds2}}}$$

- Common source gain


$$\frac{v_{s2}}{v_{in}} = -g_{m1} (r_{ds1} \parallel r_{in2}) = -\frac{g_{m1}}{g_{ds1} + g_{in2}}$$

- Common gate gain

$$\frac{v_{out}}{v_{s2}} = \frac{g_{m2} + g_{s2} + g_{ds2}}{G_L + g_{ds2}} \approx g_{m2} (R_L \parallel r_{ds2}) = \frac{g_{m2}}{g_{ds2} + G_L}$$

- Total gain
 
$$A = \frac{v_{s2}}{v_{in}} \frac{v_{out}}{v_{s2}} \cong -g_{m1} (r_{ds1} \parallel r_{in2}) g_{m2} (R_L \parallel r_{ds2})$$



TSL inf3410

26

# Cascode stage usage



- Large gain for low frequencies  $R_{out} = r_{ds2} \parallel R_L$ 
  - Giving  $R_L$  must be large provided by high quality current mirror
    - With output resistance in the order of:  $R_L = g_{m-p} r_{ds-p}^2$
  - Approximate by assuming transistors are close to equal
    - Dropping indices
  - Q2 admittance  $g_{m2} = \frac{1}{r_{in2}} \cong \frac{g_m}{1 + g_{ds} g_m r_{ds}^2} \cong g_{ds} \Rightarrow r_{in2} \cong r_{ds}$
  - CS gain:  $\frac{v_{s2}}{v_{in}} = -g_{m1} (r_{ds1} \parallel r_{in2}) = -\frac{1}{2} g_m r_{ds}$
  - CG gain:  $\frac{v_{out}}{v_{s2}} \approx g_{m2} (R_L \parallel r_{ds2}) = g_m r_{ds}$  for  $R_L \gg r_{ds}$
  - Overall gain

$$A = \frac{v_{s2}}{v_{in}} \frac{v_{out}}{v_{s2}} \cong -\frac{1}{2} g_m^2 r_{ds}^2$$



TSL inf3410

27
  
# Differential amplifiers



- Single ended signal
  - Signal swing relative to fixed potential
- Differential signal
  - Difference between two nodes
    - Equal swing around fixed potential
    - Opposite signal excursion
  - Better noise immunity
    - Common mode noise rejected
    - Power supply noise rejection



Important circuit invention with increased usage in advanced CMOS technology

TSL inf3410

28

# MOS differential pair



- Standard input stage

- Differential input  $v_{in} = v^+ - v^-$
- Ignoring output impedance

$$i_{d1} = i_{s1} = \frac{v_{in}}{r_{s1} + r_{s2}} = \frac{v_{in}}{1/g_{m1} + 1/g_{m2}}$$

- Assuming  $I_{bias}$  split equally

$$g_{m1} = g_{m2} \Rightarrow i_{d1} = \frac{g_m}{2} v_{in}$$


- Similar for other branch

$$i_{d2} = i_{s2} = -i_{d1} \Rightarrow i_{d2} = -\frac{g_m}{2} v_{in}$$

- Defining

$$i_{out} = i_{d2} - i_{d1} \Rightarrow i_{out} = g_m v_{in}$$

TSL inf3410

 

T-model

29

# Differential pair



- Adding a P mirror  $i_{d4} = i_{d3} = -i_{s1}$


- Output voltage

$$v_{out} = (i_{s1} - i_{d4})r_{out} = 2i_{s1}r_{out} = g_m r_{out} v_{in}$$


- Voltage gain

$$A_v = \frac{v_{out}}{v_{in}} = g_m r_{out}$$

- Simplified model

 

TSL inf3410

 

30

# Output impedance

$$r_{out} = v_x / i_x, \quad i_x = i_{x1} + i_{x2} + i_{x3} + i_{x4}$$

Finding currents  $i_{x1} = \frac{v_x}{r_{ds4}}$

assuming  $r_{ds1}, r_{ds2} \gg r_{s1}, r_{s2}$

$$i_{x2} = \frac{v_x}{r_{ds2}}$$

assuming  $r_{s1} = r_{s2}$


$$i_{s1} = i_{s2} = \frac{-v_x}{2r_{ds2}}$$

since  $i_{x4} = i_{x5}$

$$i_{x4} = -i_{s1} = -i_{s2} = -i_{x3}$$


$$r_{out} = \frac{v_x}{i_{x1} + i_{x2} + i_{x3} + i_{x4}} = \frac{v_x}{v_x/r_{ds4} + v_x/r_{ds2}}$$
 
$$r_{out} = r_{ds2} \parallel r_{ds4} \Rightarrow A_v = g_m (r_{ds2} \parallel r_{ds4})$$



31

# Weak inversion diff pair analysis

 

$$I_1 = I_0 \exp\left[\frac{v_1 - nv}{nU_T}\right] \quad (1)$$

$$i_2 = I_0 \exp\left[\frac{v_2 - nv}{nU_T}\right] \quad (2)$$

$$i_b = i_1 + i_2$$

$$i_b = I_0 \exp\left[-\frac{v}{U_T}\right] \left( \exp\left[\frac{v_1}{nU_T}\right] + \exp\left[\frac{v_2}{nU_T}\right] \right)$$

giving

$$\exp\left[-\frac{v}{U_T}\right] = \frac{i_b}{I_0} \frac{1}{\exp\left[\frac{v_1}{nU_T}\right] + \exp\left[\frac{v_2}{nU_T}\right]}$$

(1) and (2) gives :

$$i_1 = i_b \frac{\exp\left[\frac{v_1}{nU_T}\right]}{\exp\left[\frac{v_1}{nU_T}\right] + \exp\left[\frac{v_2}{nU_T}\right]}$$

$$i_2 = i_b \frac{\exp\left[\frac{v_2}{nU_T}\right]}{\exp\left[\frac{v_1}{nU_T}\right] + \exp\left[\frac{v_2}{nU_T}\right]}$$

32

TSL inf3410




# Transconductance amplifier



- Differential pair with current output
  - voltage  $\rightarrow$  current
  - Weak inversion characteristics

$$i_{1(2)} = \frac{i_b}{1 + e^{\frac{v_1 - v_2}{nU_T}}}$$
 
$$i_{out} = i_1 - i_2 = i_b \tanh\left(\frac{v_1 - v_2}{2nU_T}\right)$$



TSL inf3410

33

# Transconductance amplifier




- Transconductance

$$g_m = \frac{\partial i_{out}}{\partial (v_1 - v_2)}$$

$$= g_{m1(2)} = \frac{i_b}{2nU_T}$$

- Linear region
  - <200 mV

 

Cadence simulation

TSL inf3410

34

# Diff pair cadence analysis




Diff voltage in: 1V

Current out:

4 different bias voltages:

0.5V to 1V

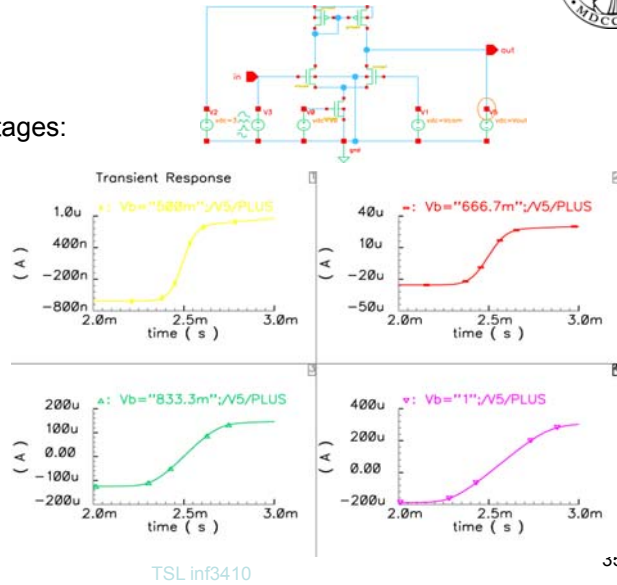


# Linear diff pair transfer



- Transconductance
  - Vdiff: [-25mV, 25mV]
  - Ib: [1nA, 10nA]

$$i_{out} = \frac{i_b}{2nU_T} (v_1 - v_2) \text{ giving}$$

$$g_m = \frac{i_b}{2nU_T}$$

 

Inserting values :

$$g_m \approx \frac{10nA}{2 \cdot 1.5 \cdot 25mV} = \frac{1}{7.5} nA/mV$$

reading graph (10nA) :


2.8nA change in 20mV gives :

$$\frac{2.8nA}{20mV} = \frac{1}{7.2} nA/mV$$
 
# Diff pair output conductance



- Cadence simulations
  - Varying output voltage
- Vout: [1V,2V]
- Input diff: [-25r]
- Ib=10nA



## Keypoints



- Simple mirror have a small signal input resistance  $\frac{1}{g_m}$
- CS stage is popular with high input impedance and active load maintain headroom
- CD stage, no voltage gain (=1) and may be unstable
- CG similar performance to CS, but with low input impedance
- Source degeneration increase output resistance
- Cascode techniques increase output resistance
- Diff pairs are very popular as input stage